
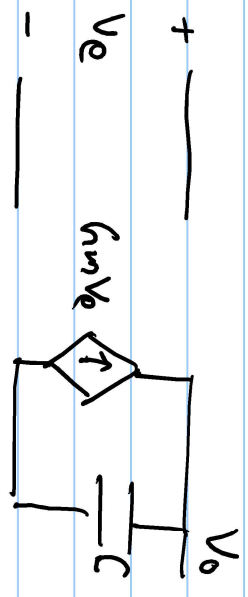


Ideal vs Real Integrator:

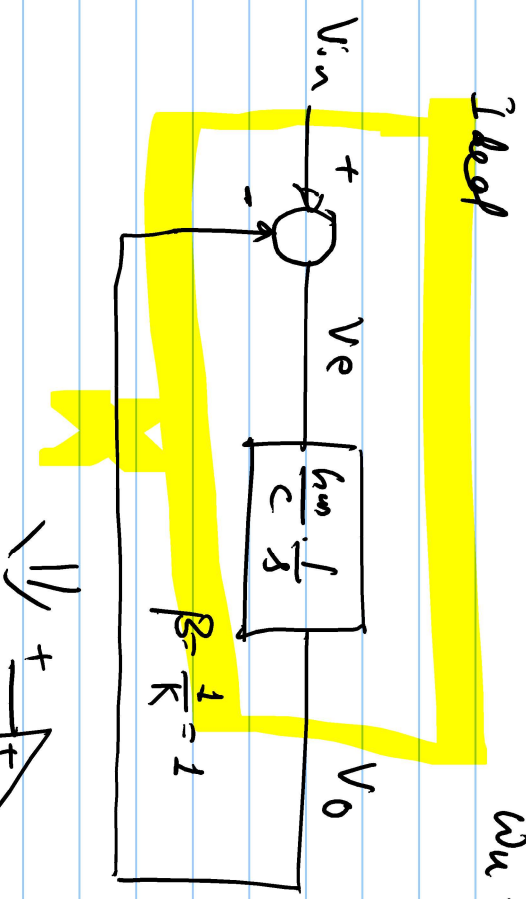


$$\frac{V_o}{V_e} = \frac{g_m}{C} \cdot \frac{1}{s}$$


$$\omega_{cu} = \frac{g_m}{C}$$



$$\frac{V_o}{V_{in}} = \frac{1}{1 + \frac{C}{g_m} s} = \frac{1}{1 + \frac{s}{\omega_{cu}}}$$


$$\omega_{cp} = \frac{g_m}{C}$$

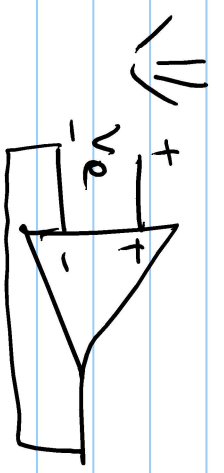


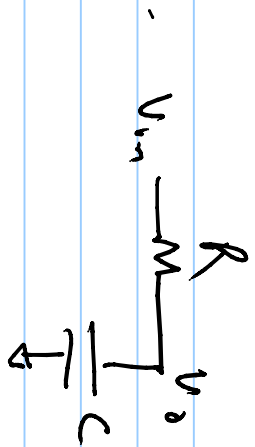

$$\frac{V_o}{V_{in}} = \frac{1}{1 + RCs}$$

$$\omega_p = \frac{1}{RC}$$

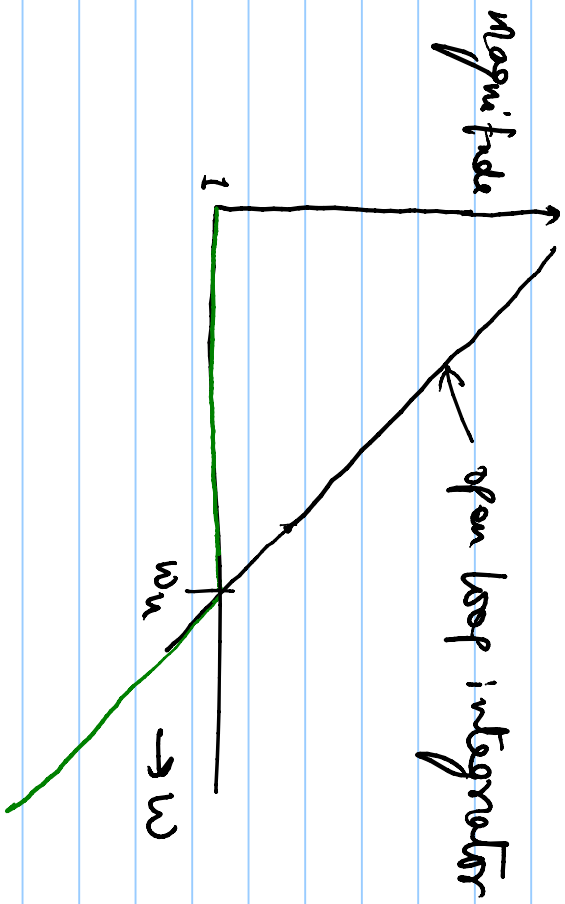

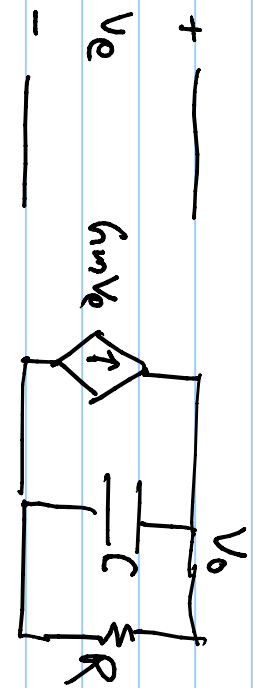

$$\frac{V_0}{V_e} = \frac{g_m R}{1 + R C g_m}, \quad \omega_p = \frac{1}{R C}$$

nm - Ideal or real


$$A_0 = g_m R$$

$$R = \frac{A_0}{g_m}$$

$$\frac{V_0}{V_e} = \frac{A_0}{1 + \frac{A_0 C}{g_m} s} = \frac{A_0}{1 + \frac{A_0}{\omega_n} s}$$

$$\omega_p = \frac{\omega_n}{A_0}$$
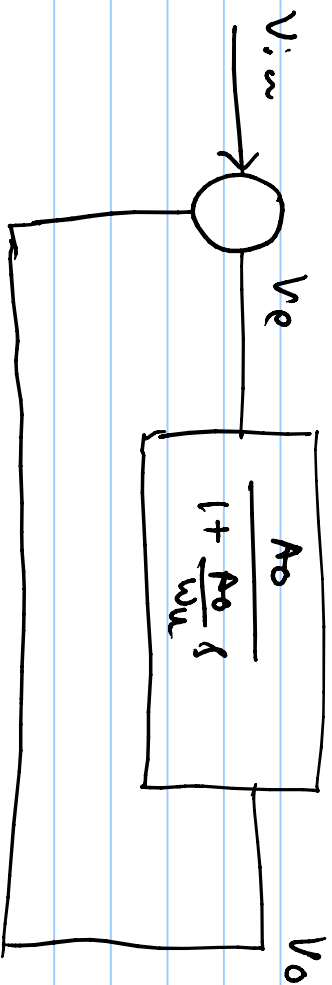
$$\frac{\omega_n}{A_0} = \frac{1}{R C} \quad \text{or} \quad \omega_n = A_0 \times \frac{1}{R C}$$



$$\frac{V_o}{V_{in}} = \frac{A_0}{1 + \frac{A_0}{\omega_u s}}$$


$$= \frac{A_0}{1 + \frac{A_0}{\omega_u s} + A_0}$$

$$= \frac{A_0}{1 + A_0} \cdot \frac{1 + \frac{A_0}{\omega_u s}}{1 + \frac{A_0}{\omega_u s} + A_0}$$


$A_0 \gg 1$

$$\frac{V_o}{V_{in}} \approx \frac{1}{1 + \frac{s}{\omega_n}}$$




which is same as ideal integrator.

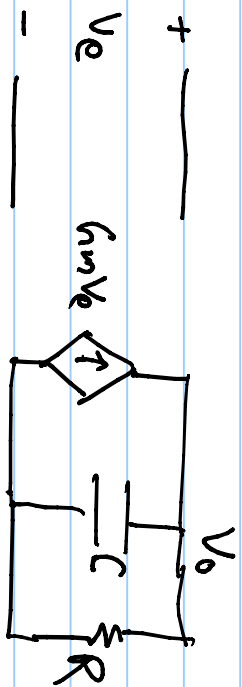


for ideal op-amp
 $A_o = \infty$

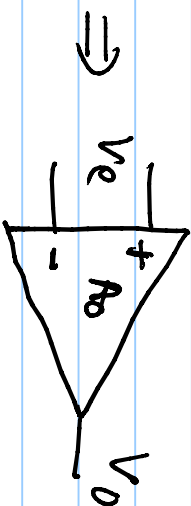

Operational - amplifier

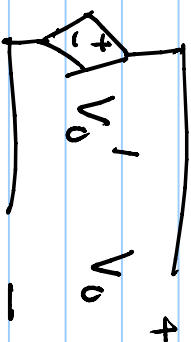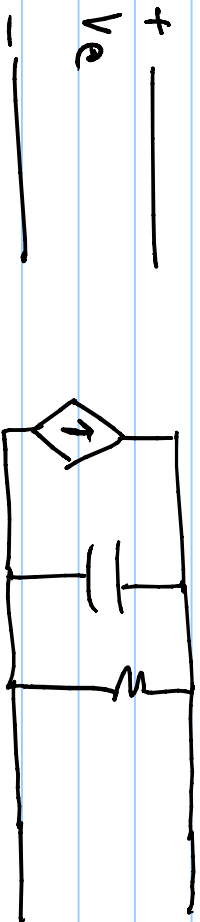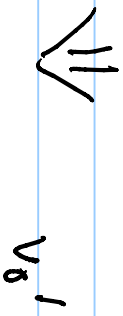


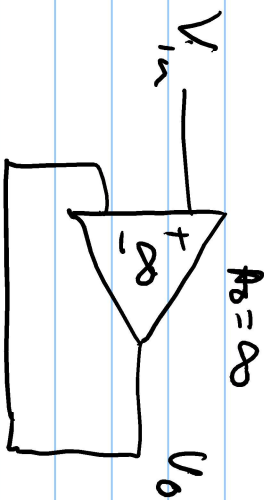

$$V_o = V_{in}$$

or $K = 1$

Unity Gain Amplifier or buffer

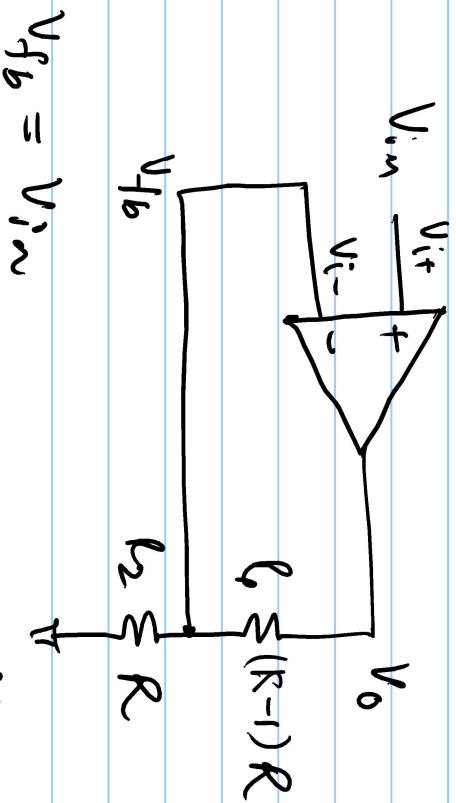


$$\frac{V_o}{V_{in}} = K = 1 + \frac{R_1}{R_2}$$

Non-inverting amplifier

$$V_{i+} = V_{i-} \Rightarrow \text{Virtual short}$$

$$V_{fb} = V_{in}$$

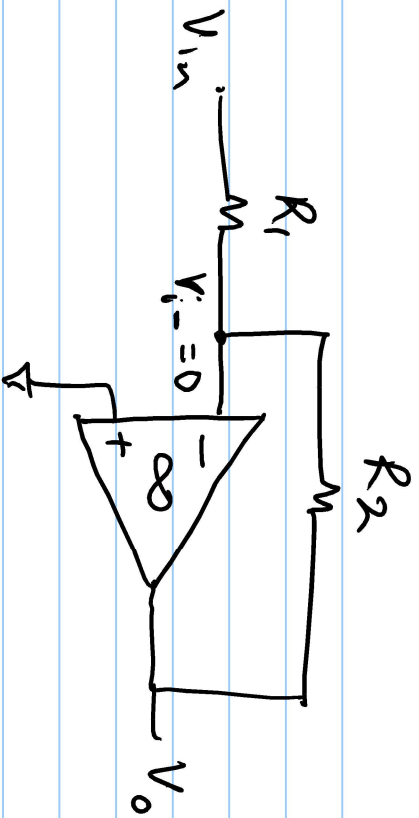

$$\frac{V_o}{V_{in}} =$$

$$\frac{V_{in} - 0}{R_1} = \frac{0 - V_o}{R_2} \Rightarrow \frac{V_o}{V_{in}} = -\frac{R_2}{R_1}$$

Inverting amplifier