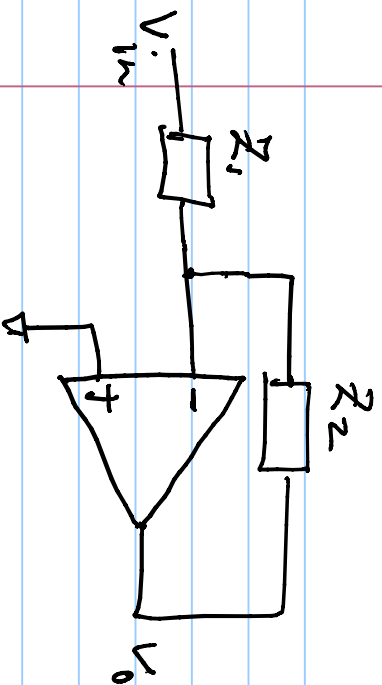


$$\frac{V_o}{V_{in}} =$$

$$\frac{V_{in} - 0}{R_1} = (0 - V_o) s C_1$$

$$\frac{V_o}{V_{in}} = -\frac{1}{R_1 C_1} \cdot \frac{1}{s} \rightarrow \text{Integrator}$$

$\omega_u = \frac{1}{R_1 C_1}$, R_1 & C_1 is external and can be changed to control ω_u



$$\frac{V_o}{V_{in}} = -\frac{Z_2}{Z_1}$$

if $Z_2 = R_2$ & $Z_1 = R_1$


$$\frac{V_o}{V_{in}} = -\frac{R_2}{R_1}$$

if $Z_2 = \frac{1}{sC_1}$ → capacitor

$\frac{V_o}{V_{in}} = -\frac{1}{R_1 C_1} \cdot \frac{1}{s}$ → Integrator

$Z_1 \rightarrow$ Capacitor & $Z_2 \rightarrow$ resistor
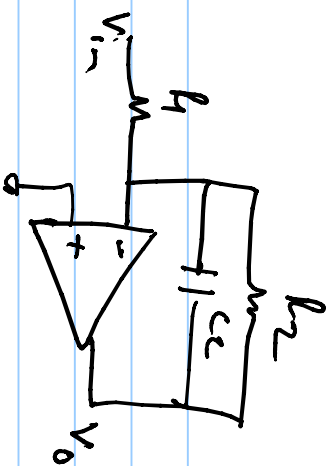
$$\frac{V_o}{V_{in}} = -R_2 C_2 s \rightarrow \text{differentiator}$$




$$Z_2 \rightarrow \left[\begin{array}{c} R_2 \\ \parallel \\ C_2 \end{array} \right] = \frac{1}{sC_2 + 1/R_2}$$


$$Z_1 \rightarrow R_1$$

$$\frac{V_o}{V_{in}} = -\frac{1}{R_1 (sC_2 + 1/R_2)} = -\frac{R_2}{R_1} \cdot \frac{1}{1 + sR_2C_2}$$
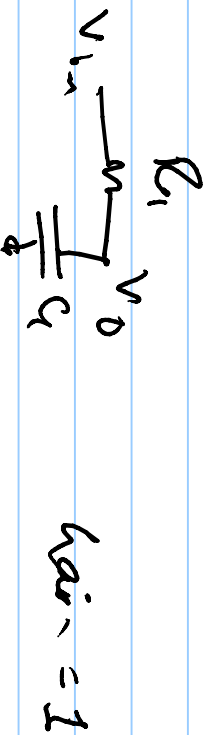
$$\omega_p = \frac{1}{R_2 C_2}, \quad \text{Gain} = \frac{R_2}{R_1}$$



$$\text{Gain} = 1$$

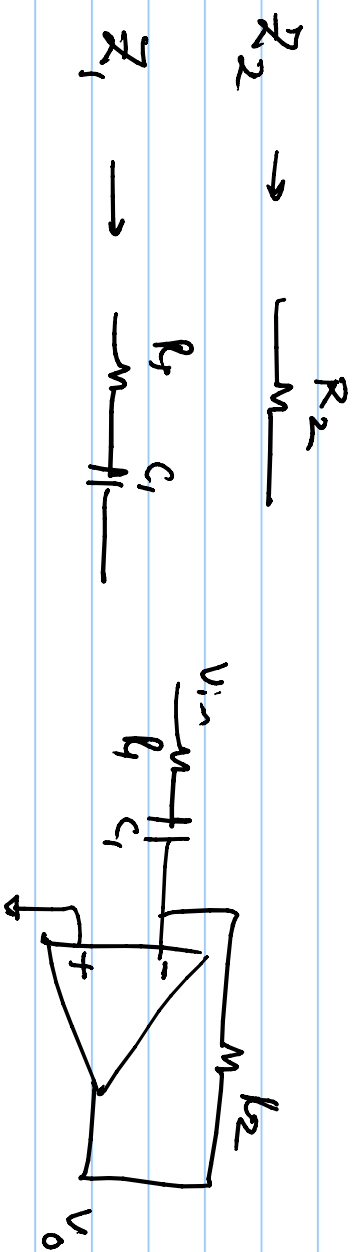


$$Z_1 = R_1 + \frac{1}{sC_1}$$

$$Z_2 = R_2$$


$$\frac{V_o}{V_{in}} = - \frac{R_2}{R_1 + \frac{1}{sC_1}} = \frac{R_2 s C_1}{1 + R_1 C_1 s}$$

Supply limited op-amp

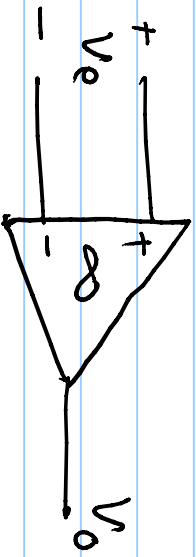


if $V_e > 0$, $V_o = \infty$



if $V_e < 0$, $V_o = -\infty$

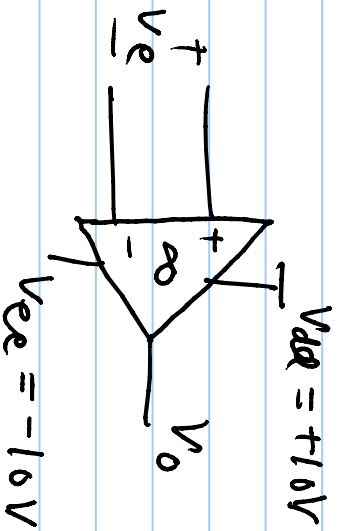

If $V_e > 0$, $V_o = +1.6V \rightarrow$ logic high (1)

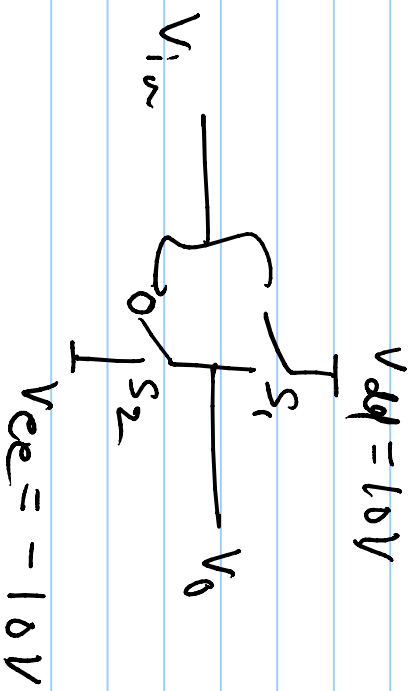if $V_e < 0$, $V_o = -1.6V \rightarrow$ logic low (0)



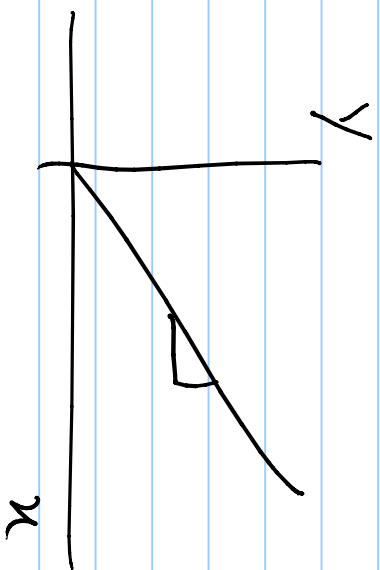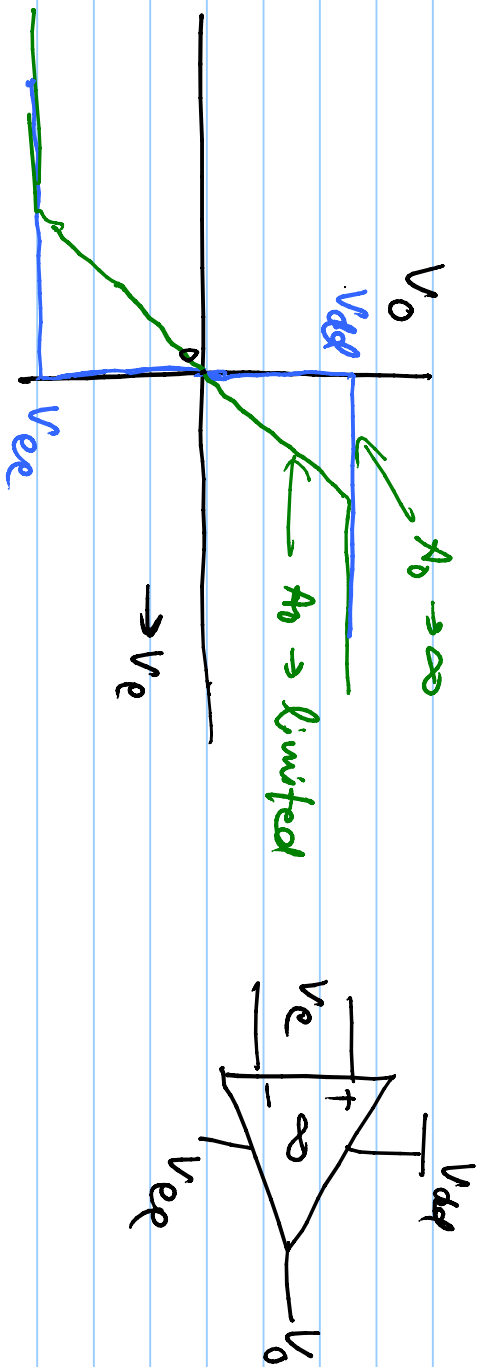

$$\frac{dy}{dx} = \text{sain}$$