
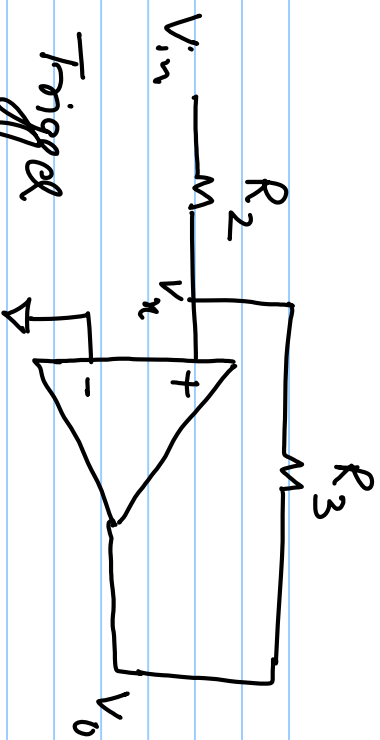


Schmitt Trigger

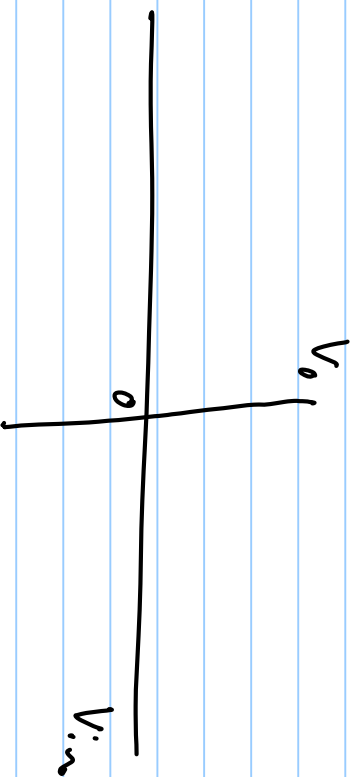

$$V_o = -\frac{R_3}{R_2} V_{in} \quad ?$$




Case-1 $V_0 = V_{dd}$

$$\frac{V_{in} - V_x}{R_2} = \frac{V_x - V_0}{R_3} \quad \text{--- (1)}$$

$V_x = 0, V_0 = V_{dd}$

$V_{in} = V_{thresp-low}$

Substituting in (1)

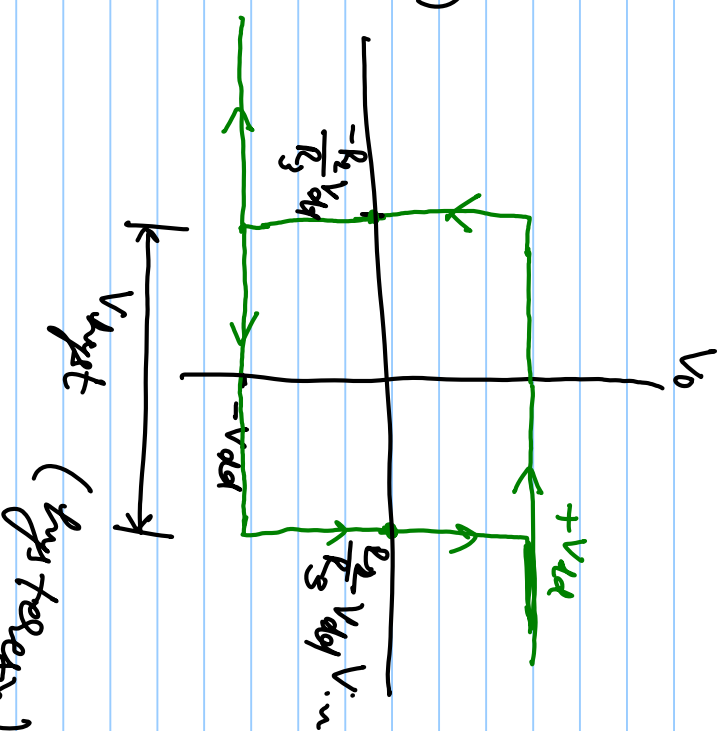

$$\frac{V_{\text{trip-low}}}{R_2} = -\frac{V_{\text{dd}}}{R_3} \Rightarrow V_{\text{trip-low}} = -\frac{R_2}{R_3} V_{\text{dd}} \quad \text{--- (2)}$$

Case-2 $V_0 = -V_{\text{dd}}$

$$V_{\text{in}} = V_{\text{trip-high}}, V_{\text{x}} = 0$$

Substituting in (1)

$$\frac{V_{\text{trip-high}}}{R_2} = \frac{V_{\text{dd}}}{R_3} \Rightarrow V_{\text{trip-high}} = \frac{R_2}{R_3} V_{\text{dd}} \quad \text{--- (3)}$$

$$V_{\text{out}} = V_{\text{trip-high}} - V_{\text{trip-low}}$$

$$\approx 2 \frac{R_2}{R_3} \cdot V_{\text{ref}} \quad \text{--- (4)}$$

$$R_3 \gg R_2$$

$$V_{\text{in}} \text{ (sine wave)} + \text{noise} = \text{output (sine wave with noise)}$$

