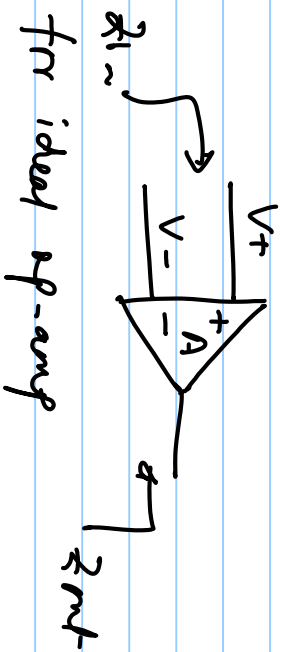


Analog systems & labs

Properties of operational Amplifier



$$\rightarrow Z_{in} = \infty$$

when connected in negative feedback

$$\rightarrow Z_{out} = 0$$

$V_+ = V_-$ (virtual short) \rightarrow no offset

$$\rightarrow A = \infty$$

Bandwidth = ∞

For non-ideal op-amp

$A \neq \infty$ ($> 80 dB$)

Bandwidth is limited (order of MHz)
(high \rightarrow unity gain BW)


$Z_{in} = \infty$ for MOSFET based


$Z_{in} \neq \infty$ (order of M Ω) for BJTs

$Z_{out} \neq \infty$ (low for resistive loads)



When connected in negative feedback

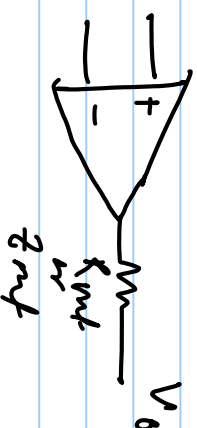$V_+ = V_-$ if no offset, $V_+ \neq V_-$ if there is an offset




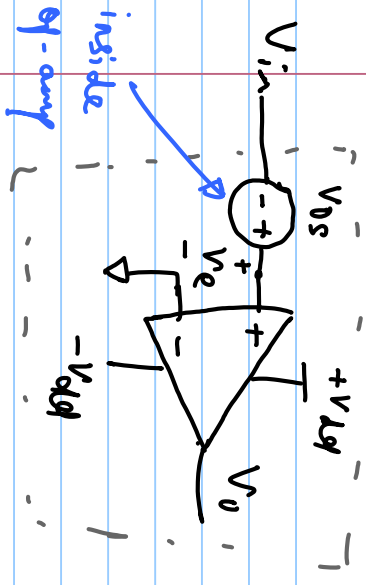

$$V_e = V_{in} + V_{0S}$$

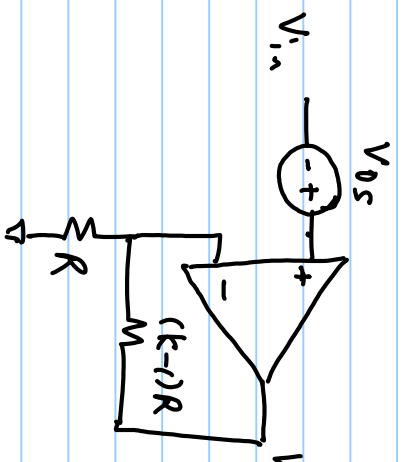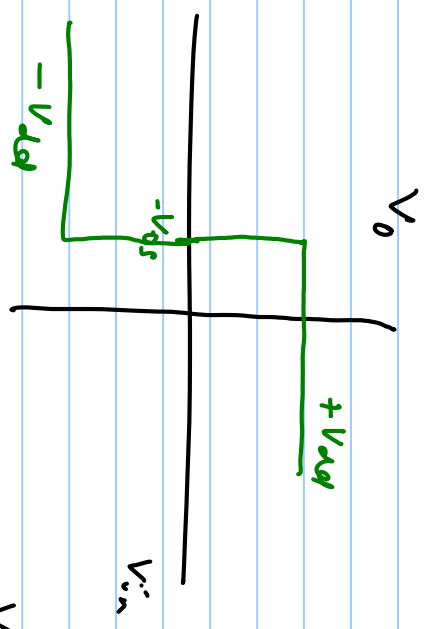


$$V_0 = K V_{0S}$$

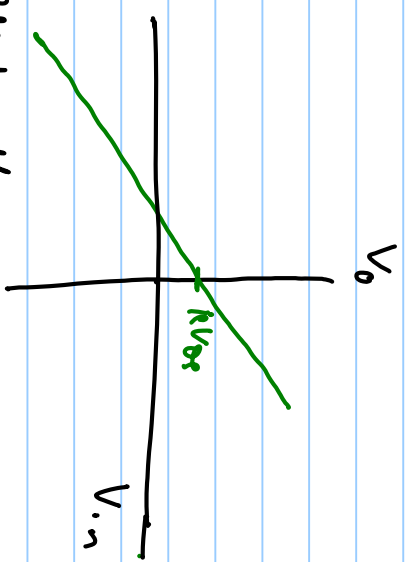

input-referred offset
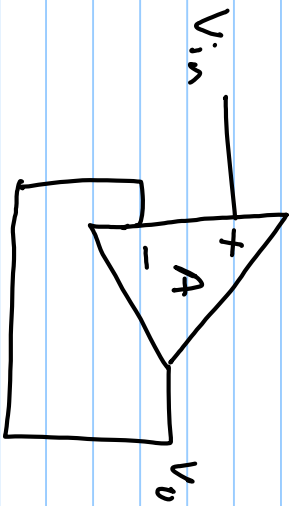
$$V_{0S} = V_0 / K \text{ when } V_{in} = 0$$




$$V_o = \frac{A}{1+A} V_{in}$$

$$A = 100$$

$$V_o = \frac{100}{101} V_{in} \approx -1\%, \text{ error}$$

Error due to finite gain
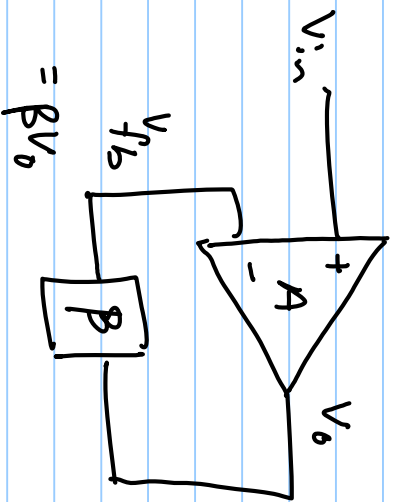
$$V_{o\text{-err}} = V_o - V_{in} = -V_{in} \left(1 - \frac{A}{1+A} \right) = -\frac{1}{1+A}$$



$$V_o = (V_{in} - V_{fb}) A$$

$$V_{fb} = \beta V_o$$

$$\beta = \frac{1}{k}$$

$$V_o = (V_{in} - \beta V_o) A = A V_{in} - \beta A V_o$$

$$A V_{in} = V_o (1 + \beta A) \Rightarrow V_o = \frac{A}{1 + \beta A} V_{in}$$

$$V_o - \text{error} = \frac{A}{1 + \beta A} V_{in} - \frac{V_{in}}{\beta} = V_{in} \frac{\beta A - 1 + \beta A}{(1 + \beta A) \beta} = \frac{1}{\beta} \left(\frac{1}{1 + \beta A} \right)$$

op-amp has two sources of error.

- ① finite gain
- ② offset

Biasing of signals

