


Signal Biading



$$V_{in} = V_{in(ac)} + V_{in(dc)}$$

$$V_{out} = V_{out(ac)} + V_{out(dc)}$$

$$V_{out(ac)} = K V_{in(ac)}$$

$$V_{out(dc)} = V_{in(dc)}$$


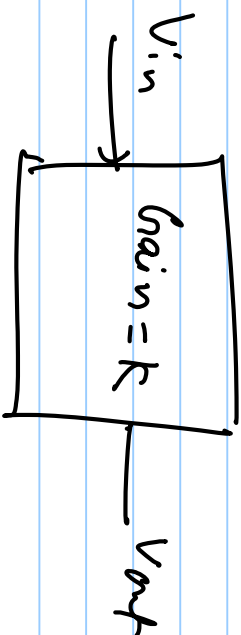


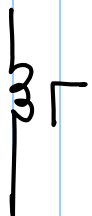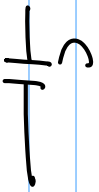

\Downarrow

open for d.c

short for d.c

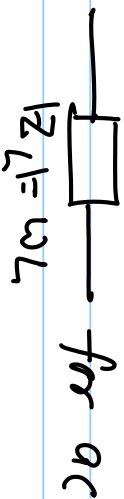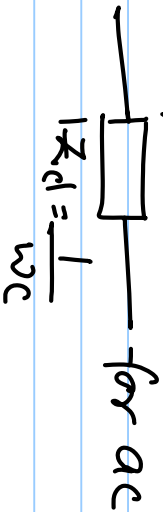

short if $w \rightarrow \infty$


open if $w \rightarrow \infty$

Shifting dc level

$$V_{in} = V_{in(ac)} + V_{dc1}$$

↓ Shift

$$V_{in} = V_{in(ac)} + V_{dc2}$$

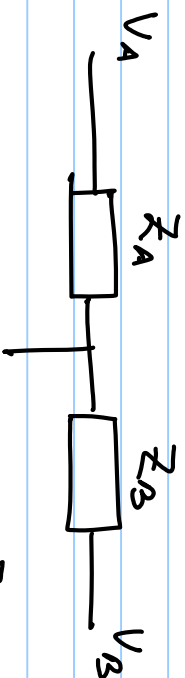

$$V_X = \frac{Z_A}{Z_A + Z_B} V_B + \frac{Z_B}{Z_A + Z_B} V_A$$


$$= \alpha V_B + \beta V_A$$

$$\text{dc} \quad = 0 \text{ for dc}$$

$$= \beta V_A \text{ for ac}$$

$$Z_A \rightarrow \text{cap}$$

$$Z_B \rightarrow \text{Resistor}$$

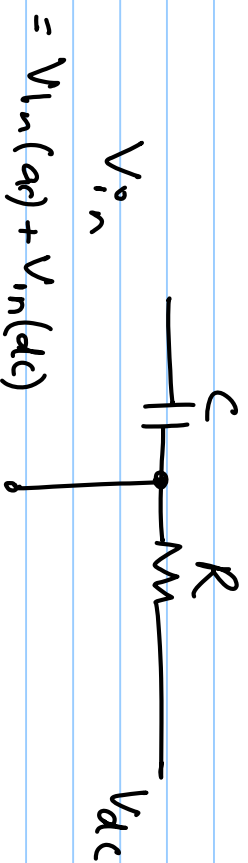

$$= V_{in}(a) + V_{in}(dc)$$

↓ $V_u = V_{in}(a) + V_{dc}$
 0 after capacitor.

$$Z_A = \frac{1}{sC} \quad \Rightarrow \quad Z_B = R$$

$$= \frac{Z_A}{Z_A + Z_B} V_u + \frac{Z_B}{Z_A + Z_B} V_A$$


$$V_u = \frac{1}{sC} \frac{1}{\frac{1}{sC} + R} V_{dc} + \frac{R}{\frac{1}{sC} + R} V_{in}$$

$$= \frac{1}{1 + RCs} V_{dc} + \frac{RCs}{1 + RCs} V_{in} \quad \sim 1 \text{ for ac}$$

for dc, $s=0$

$$RCs \gg 1 \quad \text{or} \quad R \gg \frac{1}{sC}$$
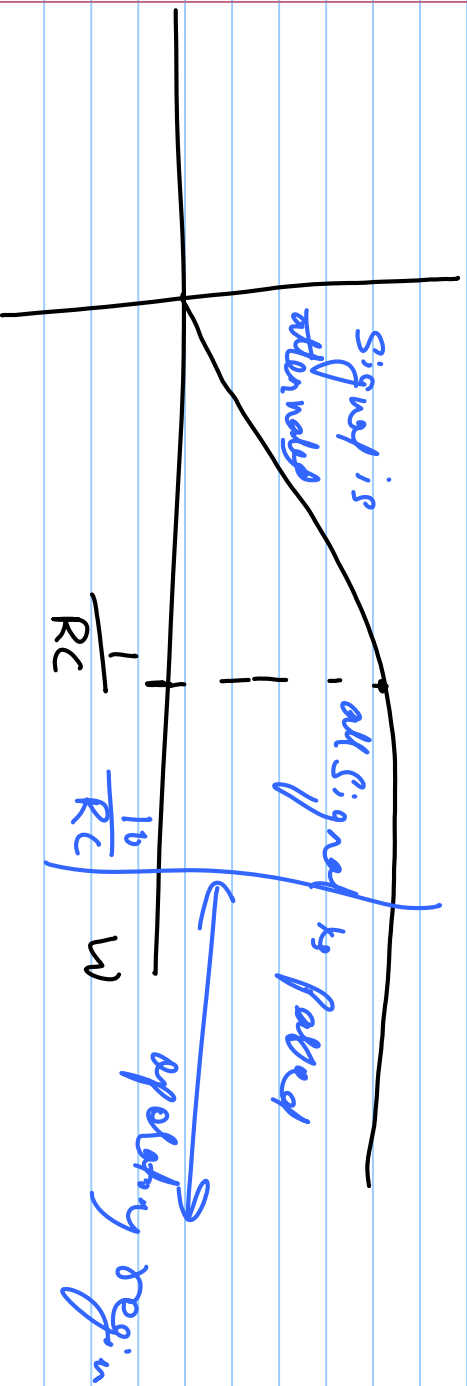
$$R \gg \frac{1}{\omega C} \approx 10 \times$$



$$W \gg \frac{1}{Rc} \Rightarrow R \gg \frac{1}{\omega c}$$