

## Input & Output Impedance


Impedance is ability to resist a signal & defined as

$$Z = \frac{\Delta V}{\Delta I} \rightarrow \text{has both magnitude \& phase}$$

$$Z = R \text{ for dc}$$


↑  
resistance.

$Z$  may be function of frequency

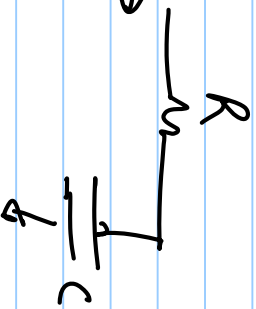

$$Z_{in} = R + \frac{1}{sC}$$


$$Z_{in} \Big|_{s=0} = \infty$$




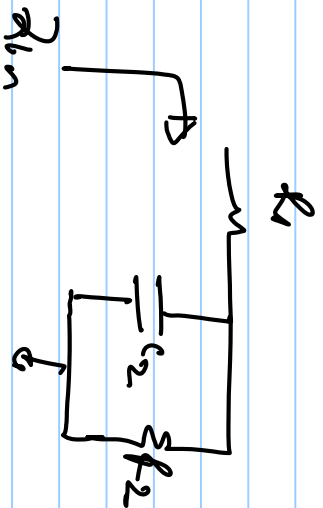




$$Z_{in} \Big|_{s=0} = R_1 + R_2$$

$$Z_{in}(s) = R_1 + \frac{1}{1/R_2 + sC_2}$$


$$Z_{in}(s) \Big|_{s \rightarrow \infty} = R_1 \quad \Big|_{Z_{in}(s)}$$

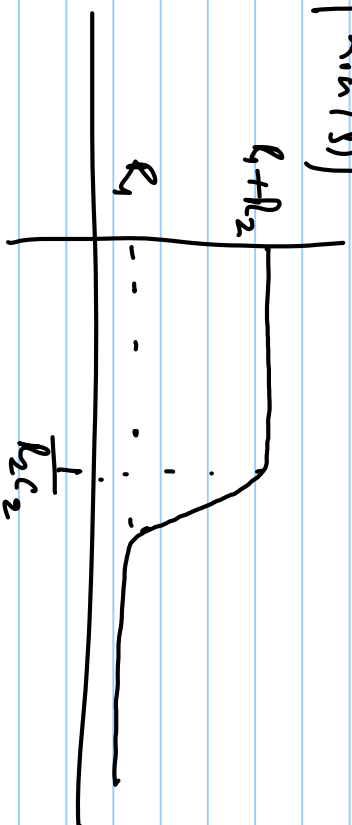

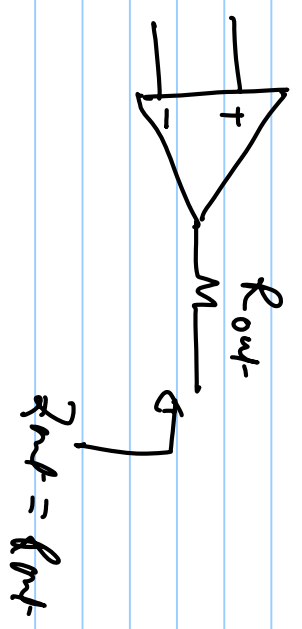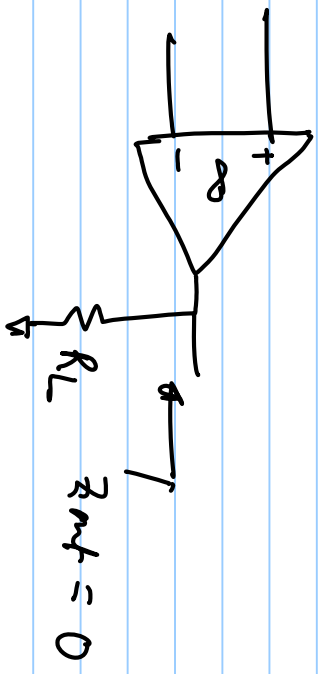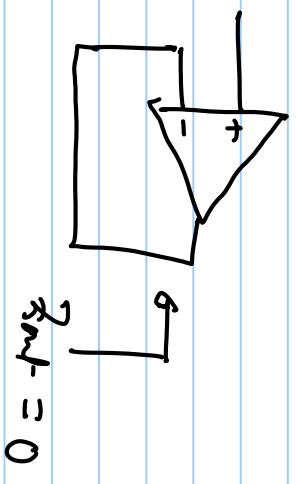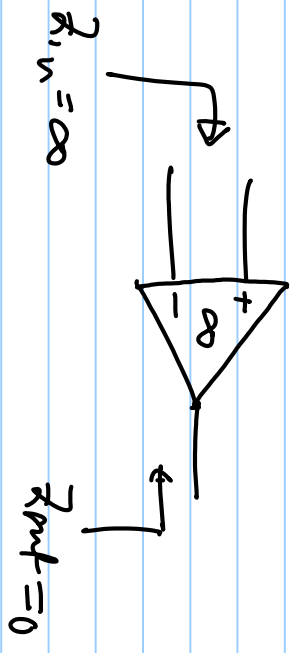

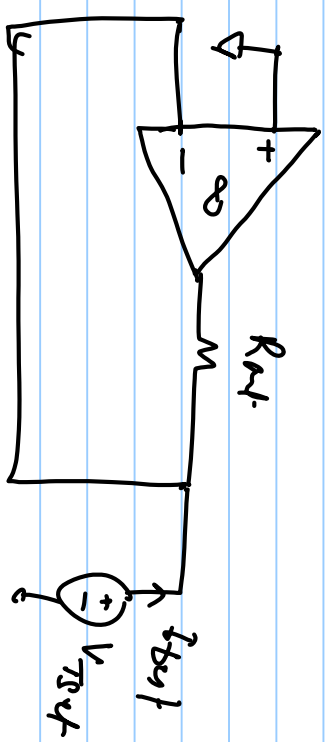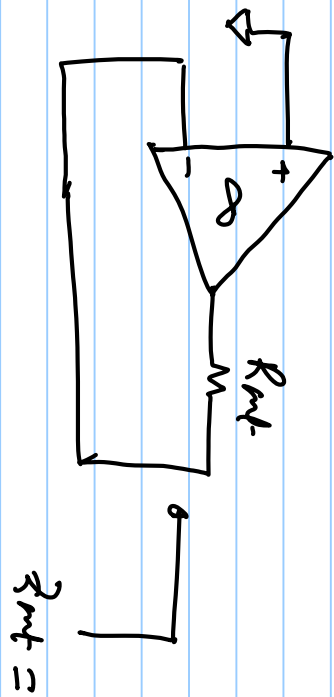
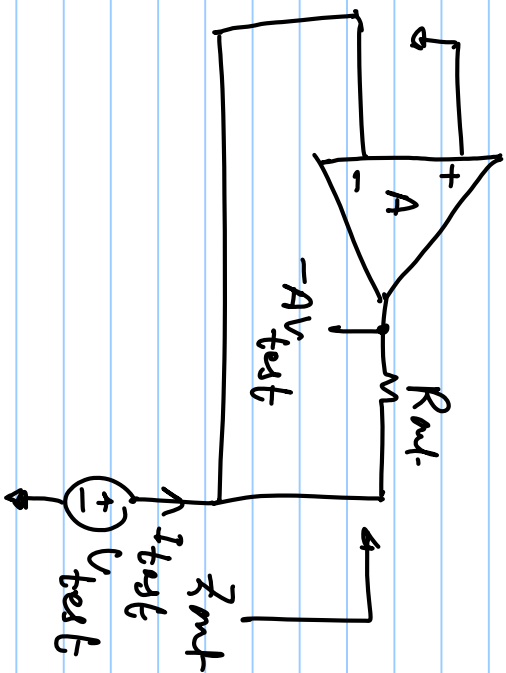
$$z_{out} = \frac{V_{Tsout}}{I_{Tsout}}$$




$$I_{test} = \frac{V_{test} - (-AV_{test})}{R_{out}} = \frac{V_{test}(1+A)}{R_{out}}$$

$$\frac{V_{\text{test}}}{I_{\text{test}}} = Z_{\text{out}} = \frac{R_{\text{out}}}{1+A} \approx \frac{R_{\text{out}}}{A} \quad \text{if } A \gg 1$$

if  $A \rightarrow \infty$

$Z_{\text{out}} \rightarrow 0$  as good as ideal voltage source.

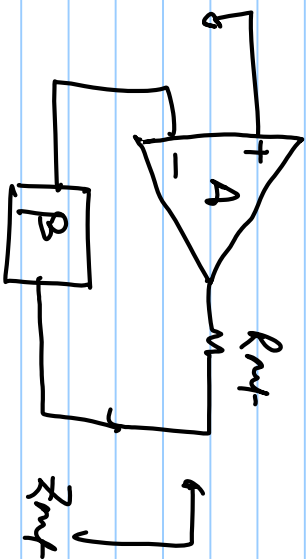
Opamp with negative feedback reduce the output impedance by factor of loop gain



$$Z_{out} = \frac{R_{mf}}{A\beta}$$

$A\beta \rightarrow$  loop gain



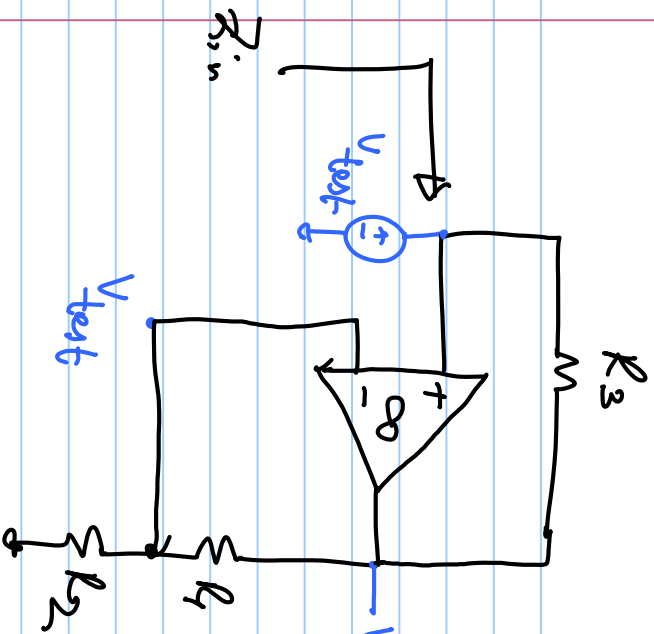

$$v_o = \left(1 + \frac{R_1}{R_2}\right) v_{\text{Test}}$$

$$I_{\text{Test}} = \frac{v_{\text{Test}}}{R_3} - \left(1 + \frac{R_1}{R_2}\right) v_{\text{Test}}$$

---


$$R_3$$

$$= - \frac{R_1}{R_2 R_3} v_{\text{Test}}$$

$$\frac{v_{\text{Test}}}{I_{\text{Test}}} = Z_{\text{in}} = - \frac{R_2 R_3}{R_1}$$

$R_3 \rightarrow Z_3, R_1 \rightarrow Z_1, R_2 \rightarrow Z_2$

$$Z_{in} = -\frac{Z_2 Z_3}{Z_1}$$

$Z_2 \rightarrow R_2, Z_3 \rightarrow R_3$

$$Z_1 \rightarrow \frac{1}{sC_1}$$

$$Z_{in} = -R_2 R_3 (sC_1) = -R_2 R_3 C_1 s \rightarrow \text{negative inductor}$$

$$L = -R_2 R_3 C_1$$

$$Z_2 \rightarrow \frac{1}{sR_2} \quad Z_3 \rightarrow \frac{1}{sC_3}$$

$$Z_1 = R_1$$

$$Z_{in} = \frac{\frac{1}{s^2 C_2 C_3}}{R_1} = \frac{1}{R_1 C_2 C_3 s^2} = \frac{1}{R_1 C_2 C_3 (j\omega)^2}$$

$$Z_{in} = \frac{1}{R_1 C_2 C_3 \omega^2}$$

→ frequency dependent resistance.