
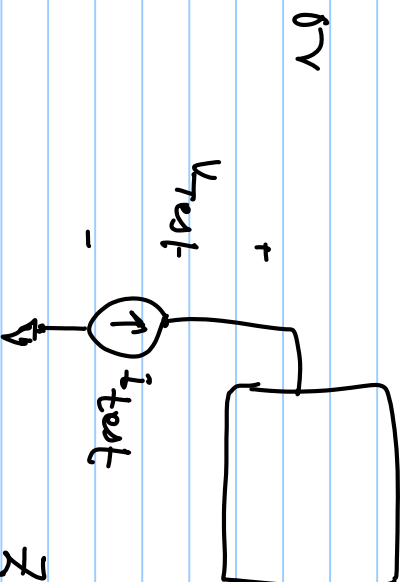


$$Z = \frac{V_{test}}{I_{test}}$$

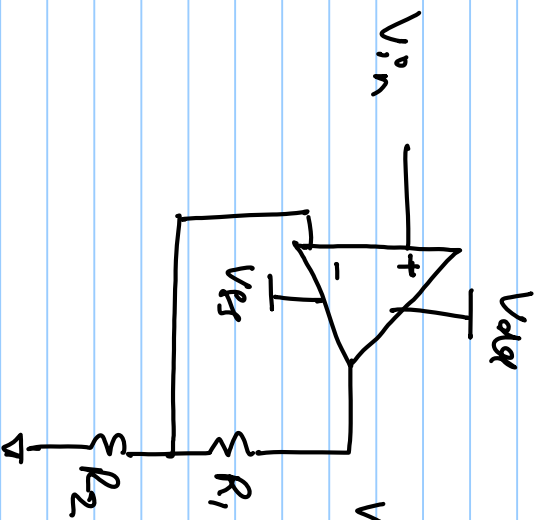


$$Z = \frac{V_{test}}{I_{test}}$$

Biasing a non-inverting amplifier


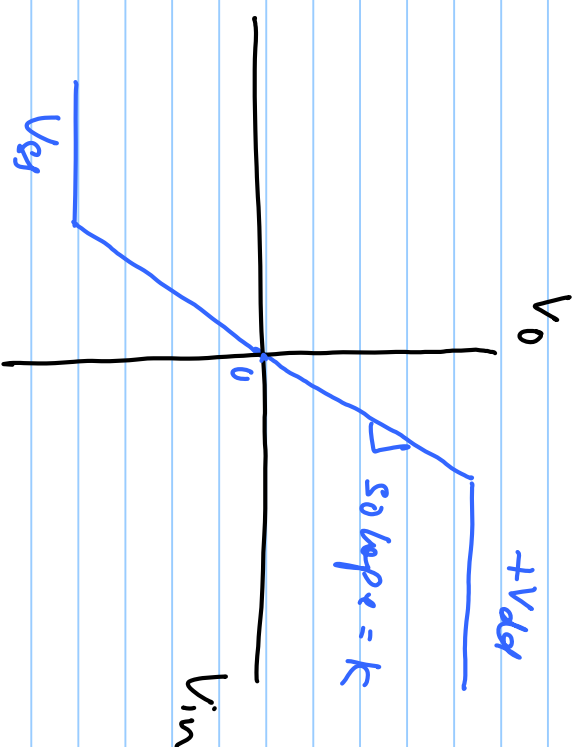
$$V_0 = \left(1 + \frac{R_1}{R_2}\right) V_{in}$$
$$= k V_{in}$$



if $V_{in} = 0$ & $V_{dc} = 10\text{ V}$

$$K = 2 \quad (R_1 = R_2)$$

Case-1, input- dc = 0

$$V_{in} = V_{in}(ac) + V_{dc}$$

$$V_{dc} = 0$$

no negative cycle in output because $V_{out}(dc) = 0$

Case-2 $V_{dc} = 5\text{ V}$

$V_{out}(dc) = 10\text{ V} \rightarrow$ no positive cycle in V_{out} because $V_{out}(dc) = 10\text{ V}$

Case-3 $V_{dc} = 2.5V \rightarrow V_{out}(dc) = 5V$


amplifier is properly biased at mid-point.

$V_{out}(dc)$ is function of amplifier gain.

we want-

$$V_{out} = K V_{in} + V_{dc}$$

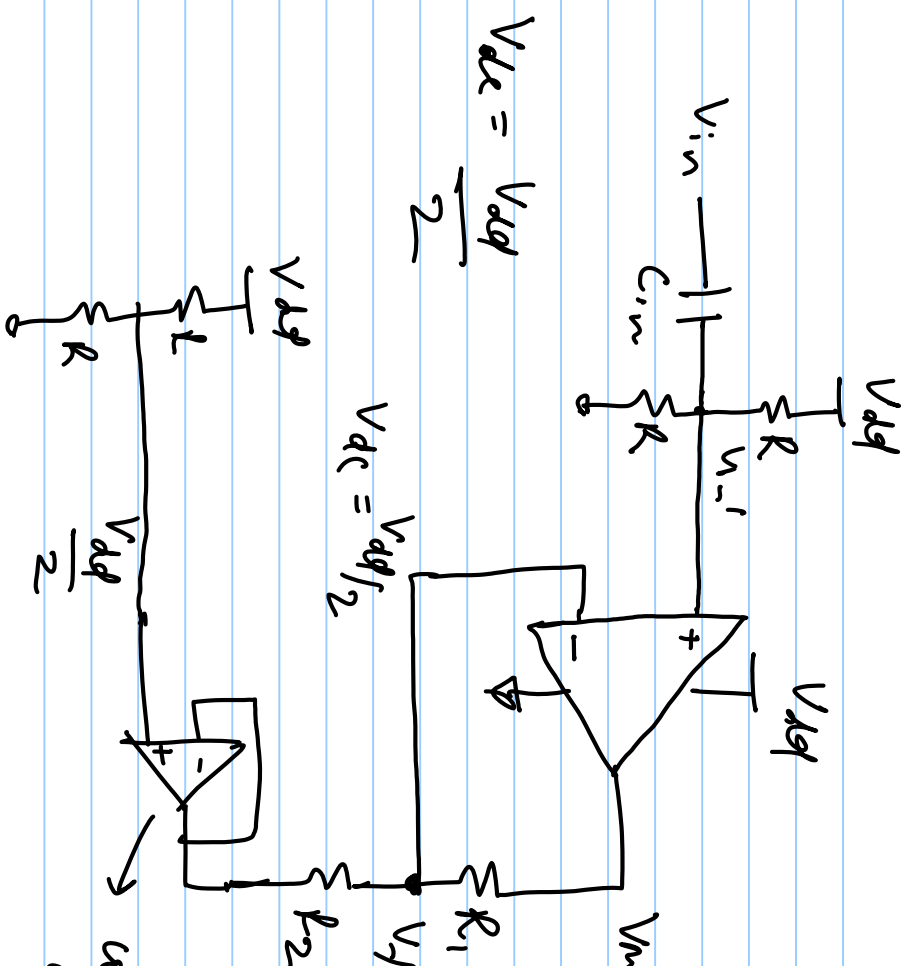We want to bias amplifier in such a way that V_{dc} level is independent of gain.




$$V_{out} = k V_{in} + \frac{V_{dd}}{2}$$

$$V_{dc} = \frac{V_{dd}}{2}$$


$$V_{dc} = \frac{V_{dd}}{2}$$

$$V_{fb} = V_{in} \left(\frac{R_2}{R_1 + R_2} \right) + \frac{V_{dd}}{2}$$

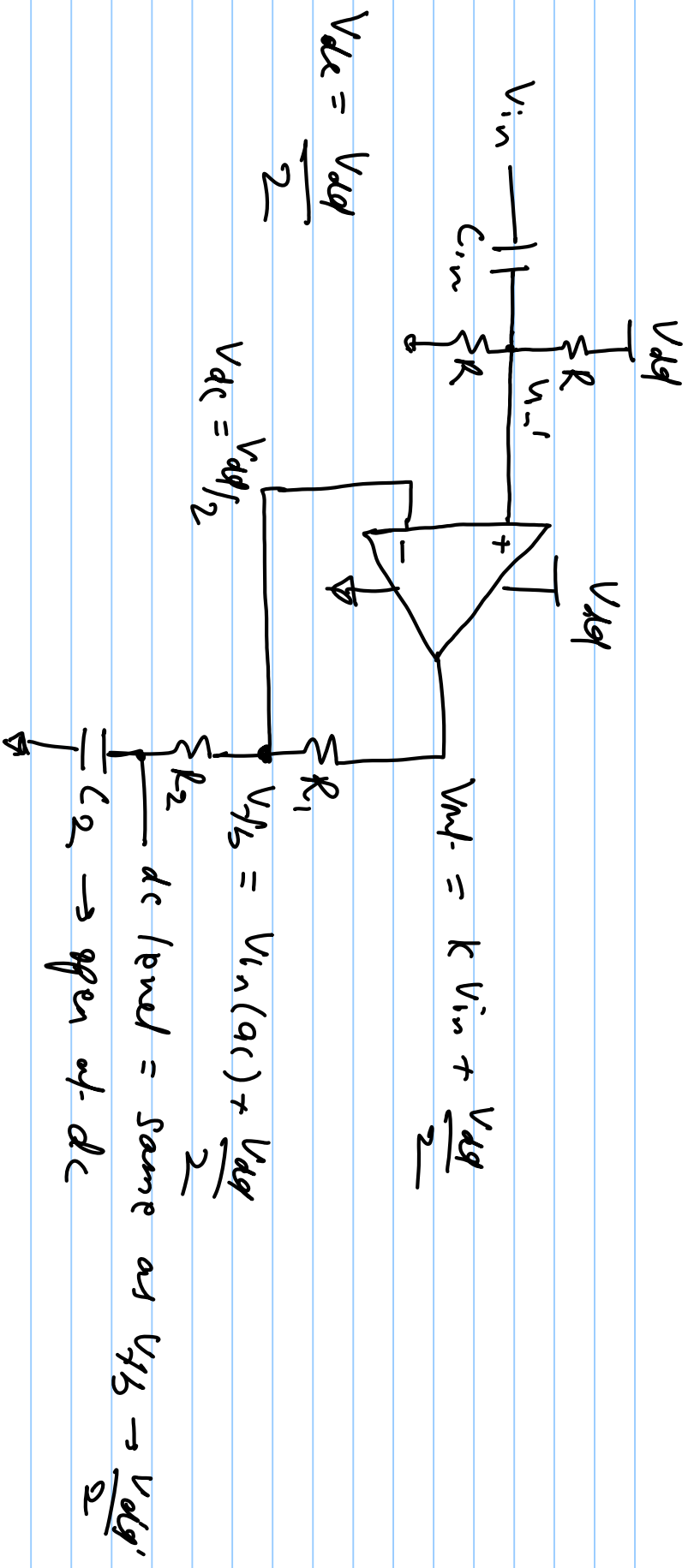works as an op-amp so not a preformed method



Pulse Width Modulation (PWM)

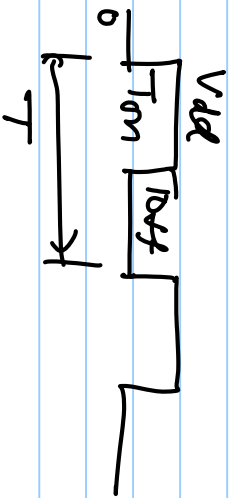

PWM \rightarrow converts voltage information into time.

Behaves like continuous time digital signal.

Duty cycle, $D = \frac{T_{on}}{T}$

$$D' = 1 - D = \frac{T_{off}}{T}$$

max $D = 1$

min $D = 0$

\rightarrow less sensitive to noise because we have only two voltage levels (0 & V_{dd})


Applications:

1. Audio amplifiers → Lab
2. Motor drive
3. Switching Regulators → Lab


Types of PWM

1. single edge modulation




Trailing Edge PWM

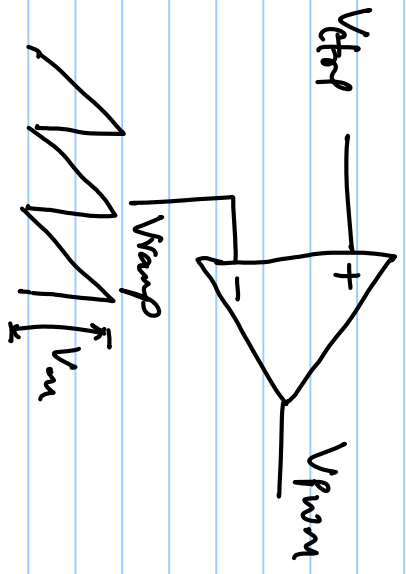

Trailing edge

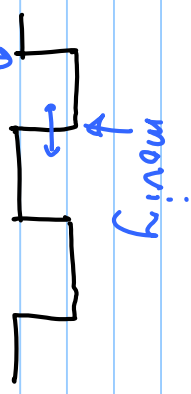



Leading edge

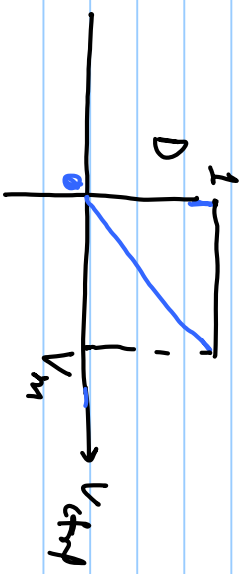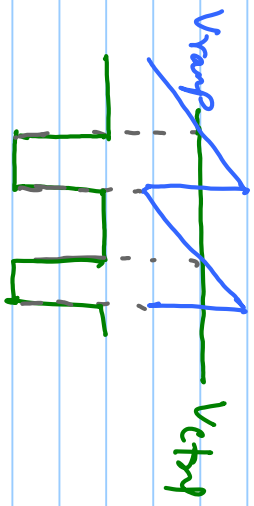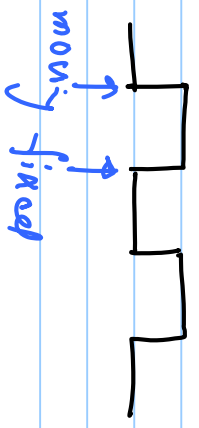

$$D = \frac{T_{on}}{T} = \frac{V_{thp}}{V_m}$$

Quasi Edge PWM

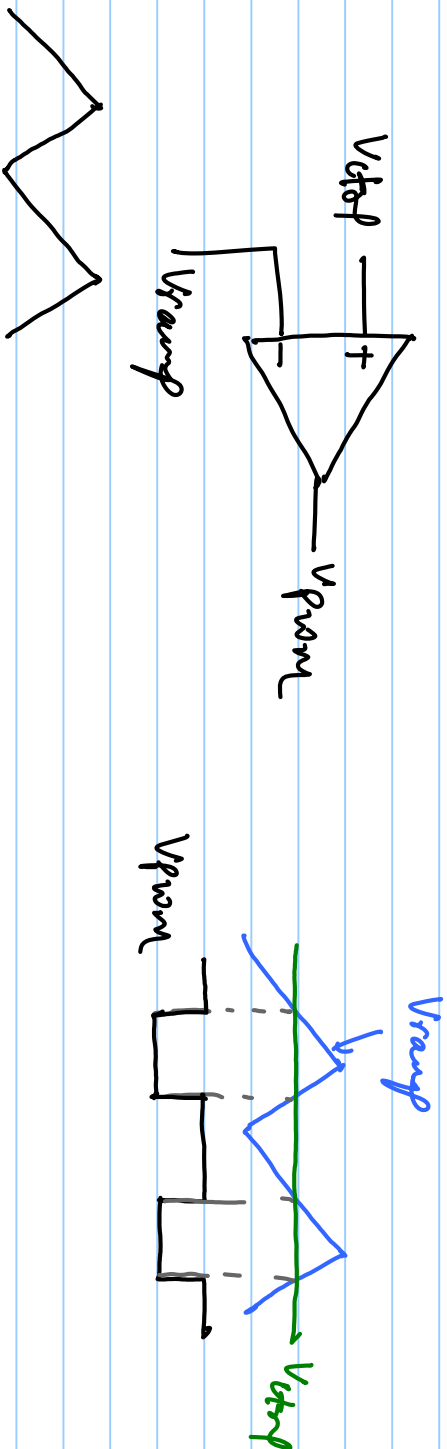



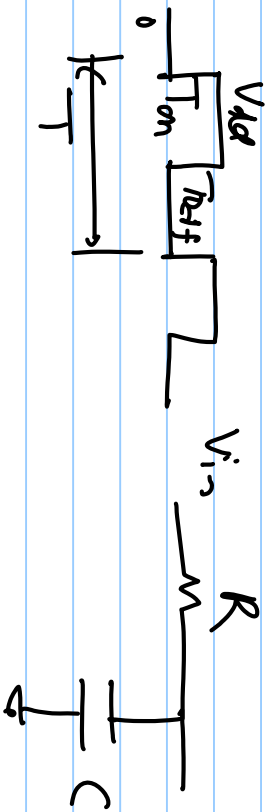


$$V_{out} = \text{average of } V_{in} = \frac{T_{on}}{T} \times V_{dd}$$

$$= D \cdot V_{dd}$$

$$RC \gg T$$

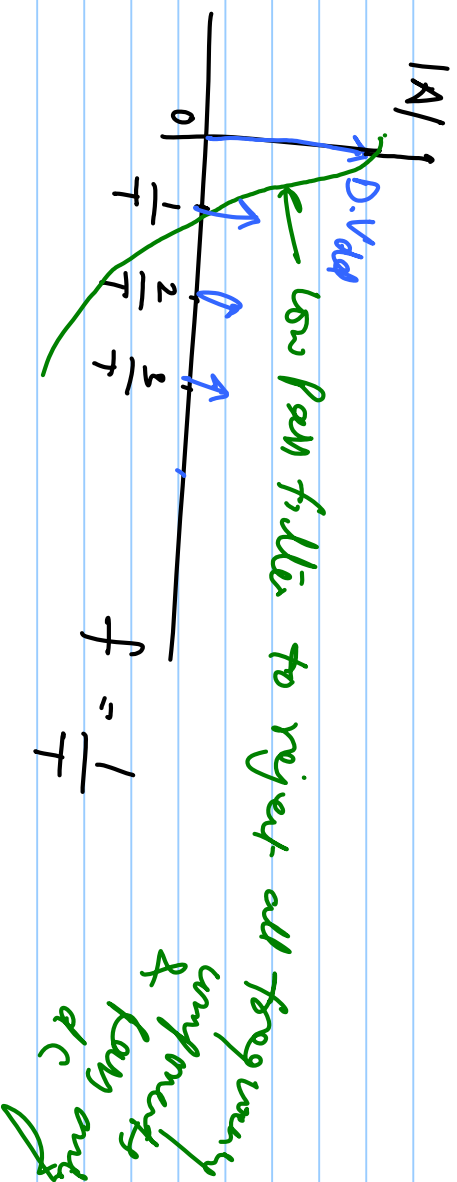


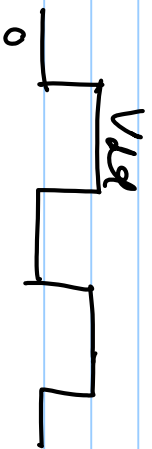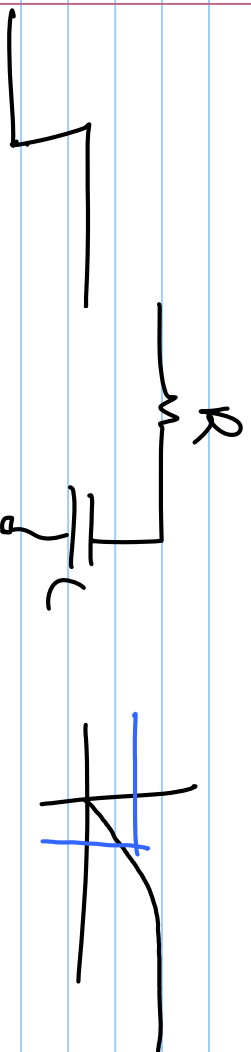

average = $D \cdot V_{dq}$

Peak-to-peak ripple depends upon RC time constant and T

for smaller ripple $RC \gg T$

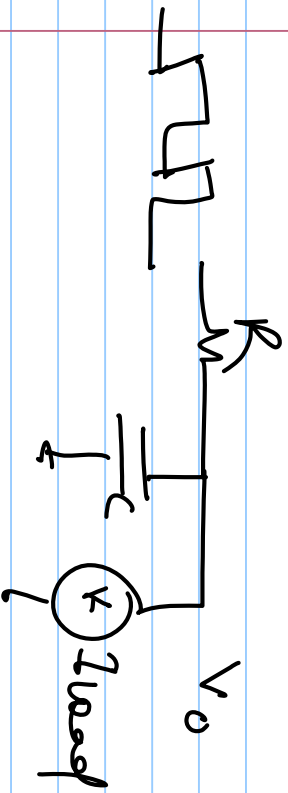

V_0 will drop as R_{load} increases