
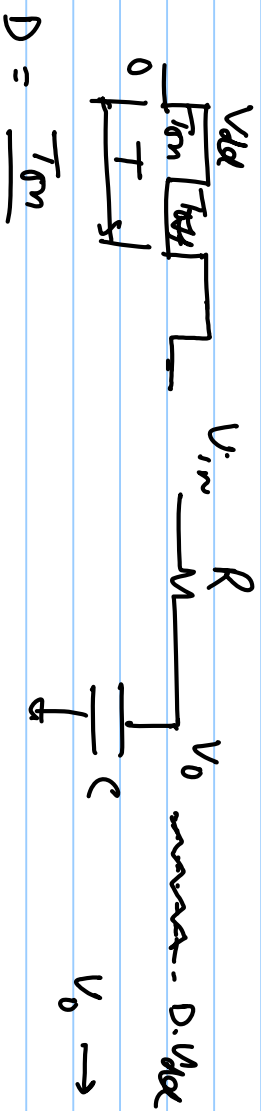



Pulse Width Modulation

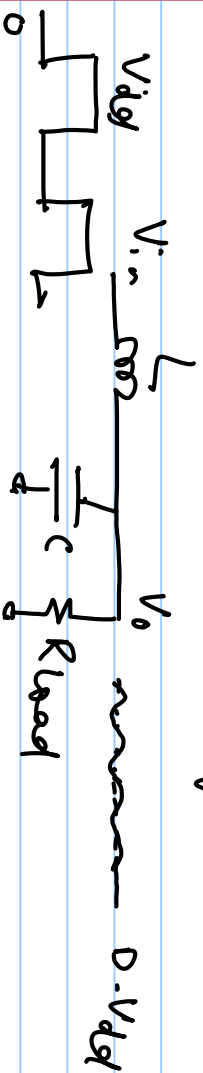Since  $R$  can't drive any load so we replace  $R$  with  $L$



$L$  is less than so no IR drop

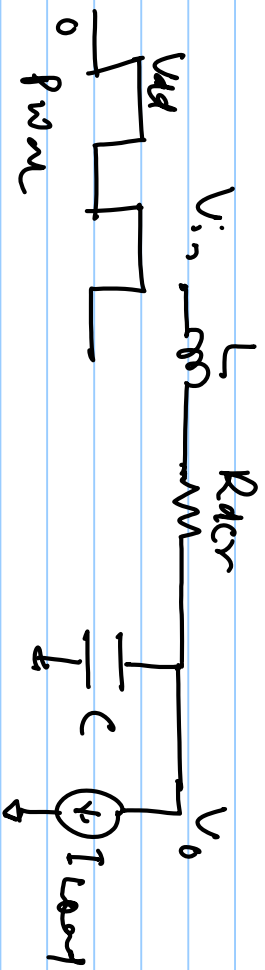In reality  $L$  is not less than and has some resistance.




$R_{dcr} \rightarrow$  range of 10s of m $\Omega$  to 100m $\Omega$

$$V_o = D \cdot V_{ds} - I_{load} \cdot R_{dcr}$$

$V_o$  can't remain constant for a fixed  $D$

$D$  must be varied in order to compensate for any change in  $V_o$

We need to operate in negative feedback.

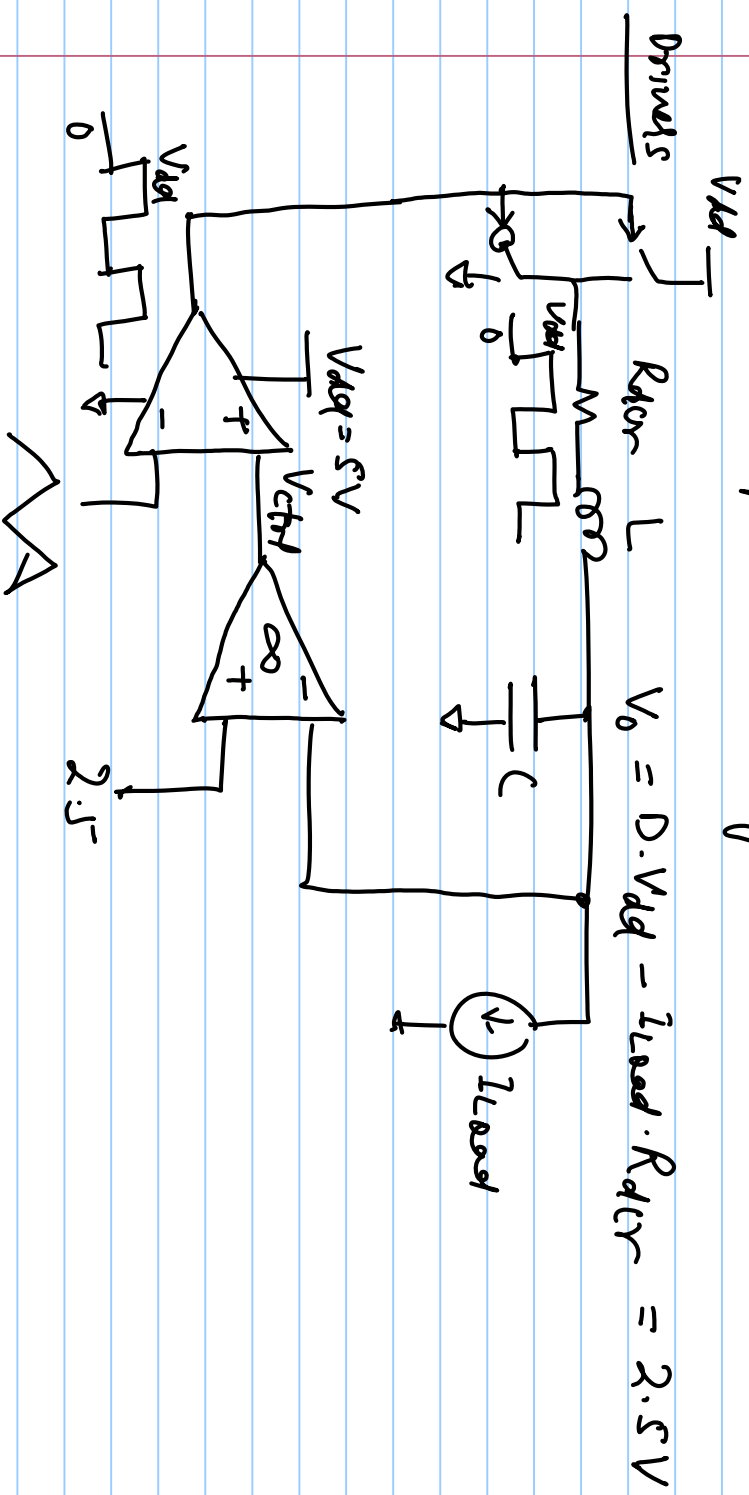


op-amp is replaced with op-amp RC integrator to stabilize the loop.
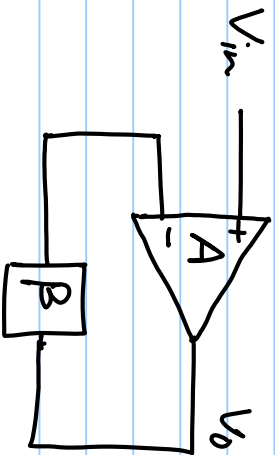
### stability

BIBO  $\rightarrow$  Bounded input bounded output

O/p signal must converge to a finite value for a finite input



$$\frac{V_o}{V_{in}} = \frac{A}{1 + AB}$$

if  $AB = -1$

$$\frac{V_o}{V_{in}} \rightarrow \infty \text{ unstable.}$$

$$\angle A\beta = 180^\circ$$

$$|A\beta| = 1$$

total phase shift in a negative feedback system =  $180^\circ$

if  $A\beta$  has additional phase shift of  $180^\circ$

Total phase shift of feedback loop =  $360^\circ$

$180^\circ \rightarrow -ve$  (negative feedback)

$360^\circ \rightarrow +ve$  (positive feedback)