
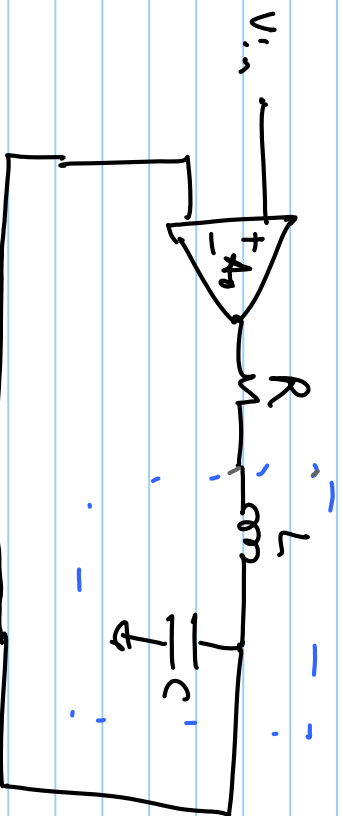


Dominant-Pole Compensation:

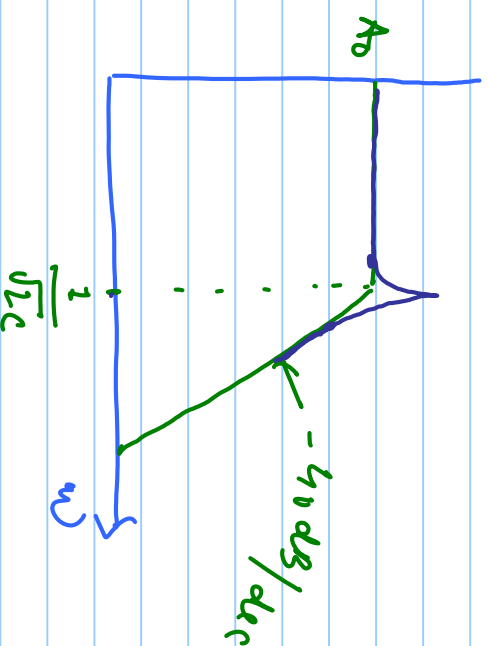


We can't make LC poles dominant so it can't be compensated by adding a capacitor.

$|G(s)|$



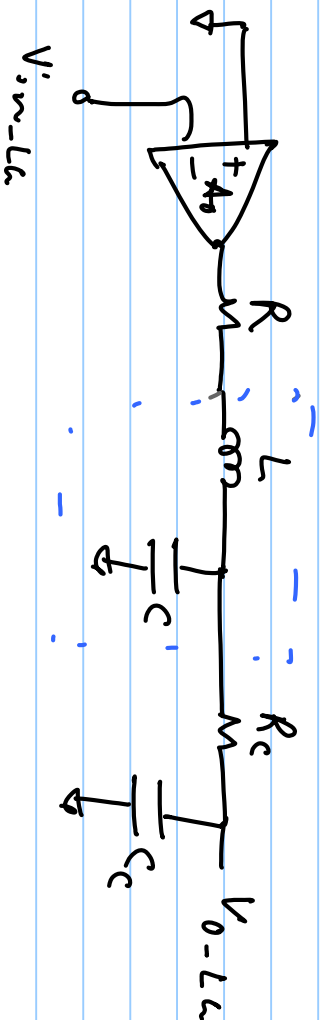we need to add one more pole and make that dominant.



$$L(s) = A_0 H_{LC}(s) \cdot \frac{1}{1 + R_c s}$$

$$H_{LC}(s) = \frac{1/s}{R + sL + 1/s} = \frac{1}{RCs + s^2L + 1} = \frac{1/LC}{s^2 + \frac{R}{L}s + 1/LC}$$

$$L G(s) = A_0 \cdot \frac{1/LC}{s^2 + \frac{R}{L}s + 1/LC} \times \frac{1}{1 + R_C C s}$$

\swarrow must be moved outside ω_{cl}
 \searrow dominant pole

for $\text{PM} = 60^\circ$

Phase contribution from LC poles

$$= -2 \tan^{-1} \frac{\omega_{cl}}{\omega_p} \quad \omega_p = \frac{1}{\sqrt{LC}}$$

$$\text{PM} = 90^\circ - 2 \tan^{-1} \frac{\omega_{cl}}{\omega_p} = 60^\circ$$

$$2 \tan^{-1} \frac{\omega_{\text{cglb}}}{\omega_p} = 36^\circ \quad \text{or} \quad \tan^{-1} \frac{\omega_{\text{cglb}}}{\omega_p} = 18^\circ$$

$$\frac{\omega_{\text{cglb}}}{\omega_p} = \tan 18^\circ = 0.227$$

$$\omega_{\text{cglb}} = \frac{\omega_p}{3.7} = \frac{1}{3.7 \times \sqrt{LC}}$$

-for $\frac{1}{RCc}$ dominant pole

$$\omega_{\text{cglb}} = A_0 \times \frac{1}{RCc} = \frac{1}{3.7 \sqrt{LC}}$$

$$\Rightarrow R_c C_c = A_0 \times 3.7 \times \sqrt{L_c}$$

$$R_c = 1 \text{ M}\Omega, \quad \frac{1}{\sqrt{L_c}} = 10 \text{ Krad/}\mu\text{s}$$

$$A_0 = 1000$$

$$C_c = \frac{1000 \times 3.7 \times 10^{-4}}{10^2} = 3.7 \times 10^{-7} = 370 \text{ nF}$$

