

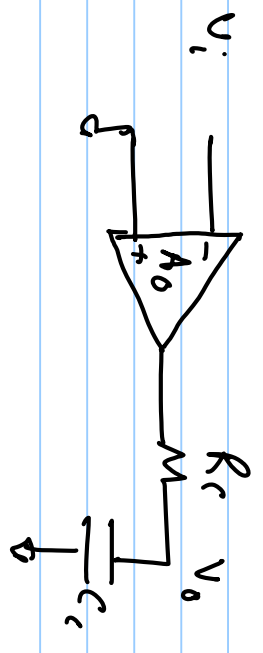


Miller compensation

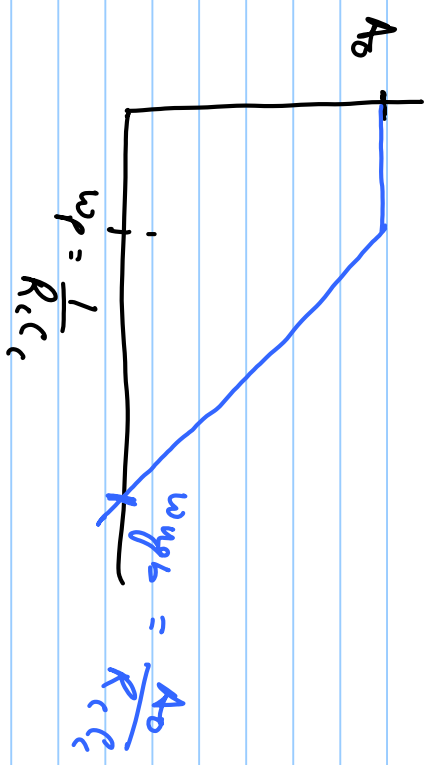


\Rightarrow

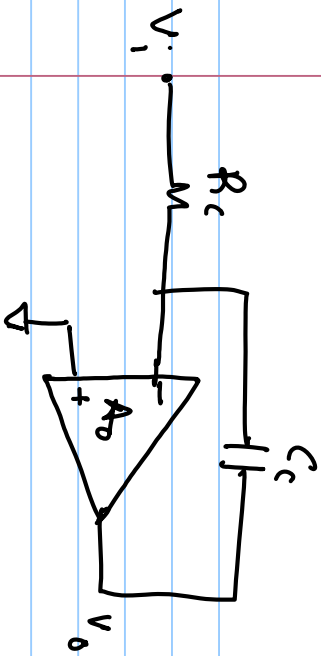




\$\Rightarrow\$

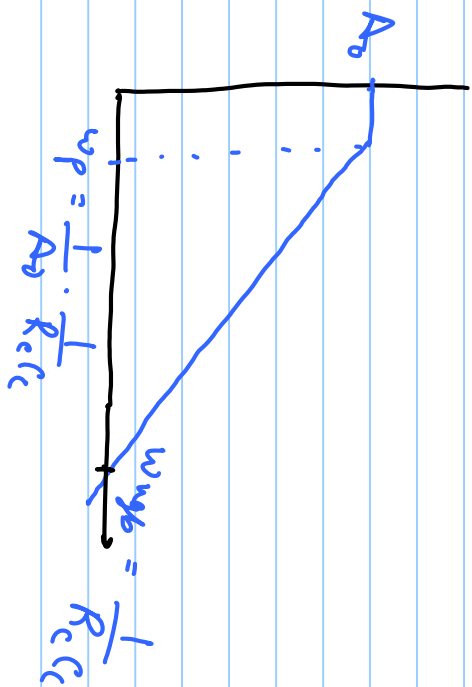


$$C_c = \frac{370 \text{ nF}}{A_0}$$

if $A_0 = 1000$


$$C_c = 370 \text{ pF}$$

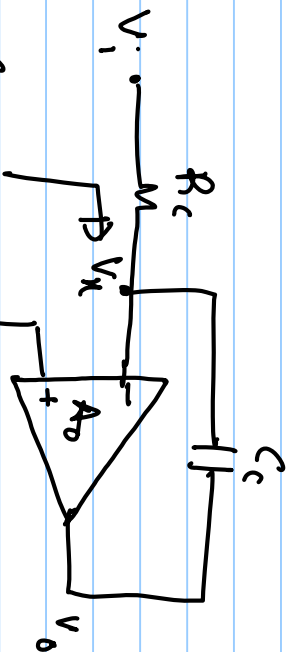

$C_{eff} = A_0 C_c$ capacitor multiplied


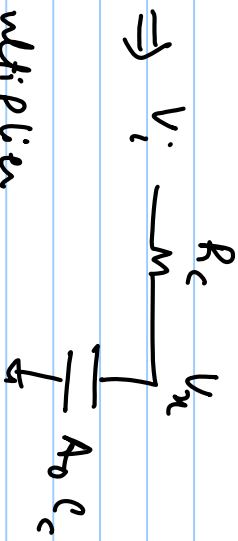

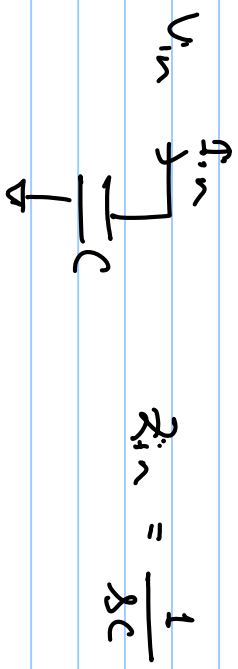
$$\frac{V_i}{V_u} = \frac{1}{1 + A_0 R_c C_c} \quad \Downarrow \quad \text{without effect}$$




if Z_{in} is reduced to $\frac{1}{m}$ times



for same V_{in} $I_{in} = m \times$

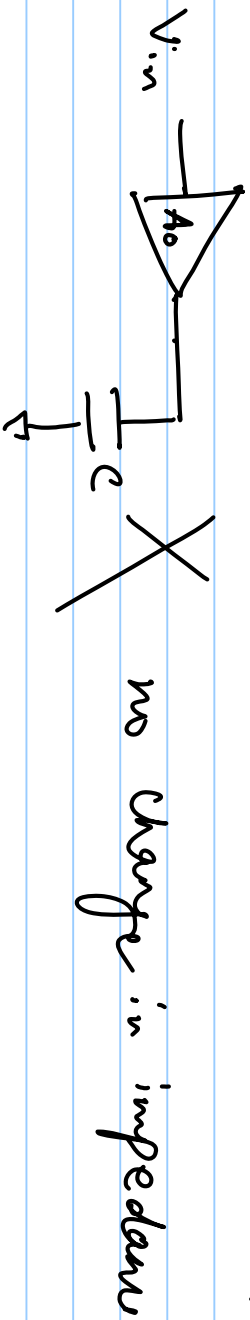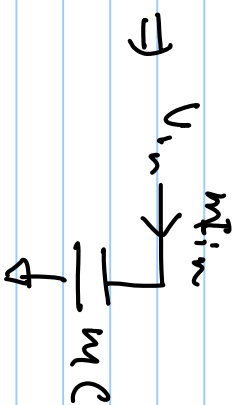

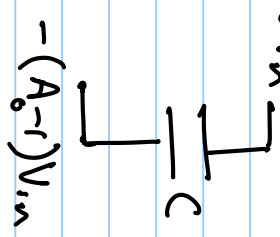
V_{in}
 $I_{in} = A_0 V_{in} \times g_c \Rightarrow C$ is multiplied by A_0



\Rightarrow

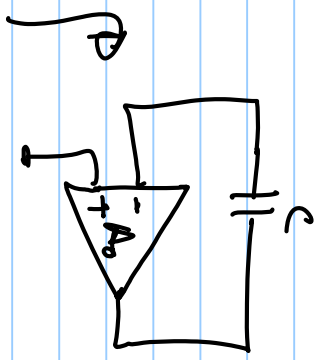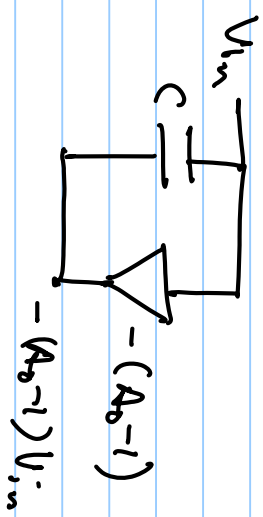

$C_{in} = (1 + A_0)C$

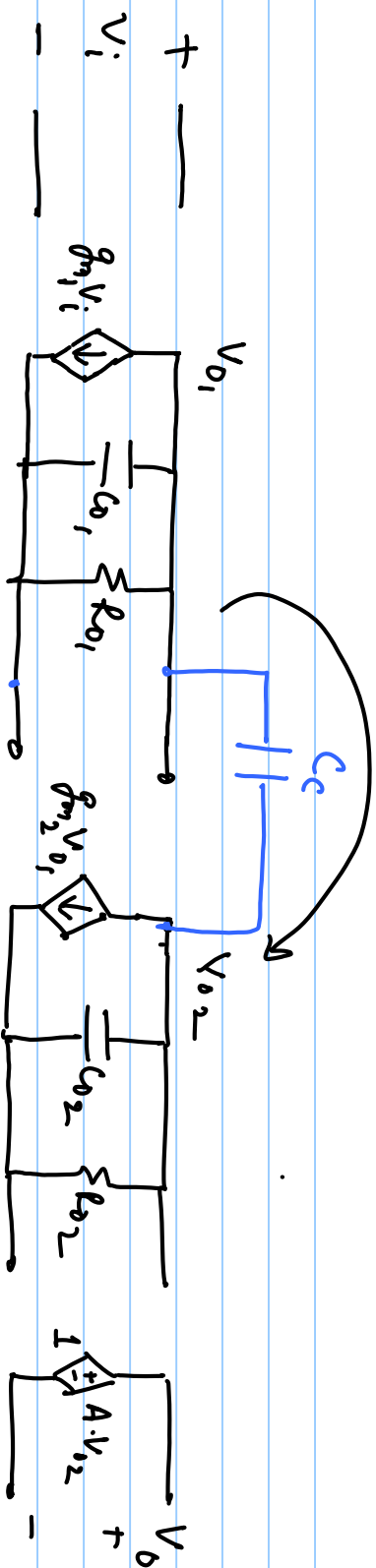

Apply KCL of V_{01}

$$g_{m1} V_i + V_{01} C_{01} s + V_{01} G_{01} + (V_{01} - V_{02}) s C_c \quad \left(G_{01} = \frac{1}{R_{01}} \right)$$

$$g_{m1} V_i + \underline{V_{01} C_{01} s} + \underline{V_{01} G_{01}} + \underline{V_{01} C_c s} - V_{02} C_c s$$

$$\Rightarrow V_{01} [G_{01} + (C_{01} + C_c) s] = V_{02} C_c s - g_{m1} V_i$$

$$V_{o1} = \frac{V_{o2} C_{e8} - g_{m1} V_i}{g_{o1} + (C_{o1} + C_c) s} \quad \text{--- (1)}$$

Apply KCL at V_{o2}

$$g_{m2} V_{o1} + G_{o2} V_{o2} + V_{o2} C_{o2} s + (V_{o2} - V_{o1}) C_{c8} = 0$$

$$V_{o1} (g_{m2} - C_{c8} s) + V_{o2} (G_{o2} + (C_{o2} + C_c) s) = 0$$

Substitute V_{o1} from (1)

$$\frac{(V_{o2} C_{c8} - g_{m1} V_i)}{g_{o1} + (C_{o1} + C_c) s} (g_{m2} - C_{c8} s) + V_{o2} (G_{o2} + (C_{o2} + C_c) s) = 0$$

$$V_{o2} (g_{o2} + (c_{o2} + c_c)g) (g_{o1} + (c_{o1} + c_c)g) = (V_i g_{m1} - V_{o2} c_c g) (g_{m2} - c_c g)$$

$$V_{o2} (g_{o2} + (c_{o2} + c_c)g) (g_{o1} + (c_{o1} + c_c)g) = g_{m1} (g_{m2} - c_c g) V_i - \underline{V_{o2} c_c g (g_{m2} - c_c g)}$$

$$V_{o2} (g_{o2} + c_{o2}g + c_c g) (g_{o1} + c_{o1}g + c_c g) + V_{o2} (g_{m2} c_c g - \underline{c_c^2 g^2}) = g_{m1} (g_{m2} - c_c g) V_i$$

$$V_{o2} (g_{o2} g_{o1} + \underline{g_{o2} c_{o1} g} + \underline{g_{o2} c_c g} + c_{o2} \underline{g_{o1} g} + c_{o1} \underline{g_{o2} g^2} + \underline{c_{o2} c_c g^2} + \underline{g_{o1} c_c g} + \underline{c_c c_{o1} g^2} + c_c^2 g^2 + \underline{g_{m2} c_c g} - \underline{c_c^2 g^2}) = g_{m1} (g_{m2} - c_c g) V_i$$

$$V_{O_2} \left[C_{O_1} C_{O_2} + C_{O_2} C_c + C_c C_{O_1} \right] R^2 + (G_{O_2} C_{O_1} + G_{O_2} C_c + G_{O_1} C_{O_2} + G_{O_1} C_c + q_{m_2} C_c) R + G_{T_0} h_{O_2}] = q_{m_1} (q_{m_2} - C_c) V_i$$