

EE2019

## Analogy Systems & Labs

Note Title

3/12/2020

$$V_{o2} (g_{o2} + (c_{o2} + c_c) s) (g_{o1} + (c_{o1} + c_c) s) = g_{m1} (g_{m2} - c_c s) V_i - \underline{V_{o2} c_c s (g_{m2} - c_c s)}$$

$$\begin{aligned} V_{o2} [g_{o2} g_{o1} + g_{o2} (c_{o1} + c_c) s + g_{o1} (c_{o2} + c_c) s + (c_{o2} + c_c) (c_{o1} + c_c) s^2] \\ = g_{m1} (g_{m2} - c_c s) V_i - V_{o2} c_c g_{m2} s + V_{o2} c_c^2 s^2 \end{aligned}$$

$$\begin{aligned} V_{o2} [g_{o2} g_{o1} + (g_{o2} (c_{o1} + c_c) + g_{o1} (c_{o2} + c_c)) s + c_{o1} c_{o2} s^2 + c_c c_{o1} s^2 + c_{o2} c_c s^2 \\ + c_c s^2] \\ = g_{m1} (g_{m2} - c_c s) V_i - V_{o2} c_c g_{m2} s + V_{o2} c_c^2 s^2 \end{aligned}$$

$$\Rightarrow V_{O_2} \left[ G_{O_2} G_{O_1} + \underbrace{(G_{O_2} (C_{O_1} + C_c) + G_{O_1} (C_{O_2} + C_c))}_{+ C_c C_{O_1} \delta^2 + C_{O_2} C_c \delta^2} \right] \delta + \underbrace{C_{O_1} C_{O_2} \delta^2 + C_c C_{O_1} \delta^2 + C_{O_2} C_c \delta^2}_{+ C_c \delta^2 + C_c \underbrace{p_{m_2} \delta - C_c \delta^2}}] \\ = p_{m_1} (p_{m_2} - C_c \delta) V_c$$

$$V_{O_2} \left[ (C_{O_1} C_{O_2} + C_c C_{O_1} + C_{O_2} C_c) \delta^2 + G_{O_2} (C_{O_1} + C_c) + G_{O_1} (C_{O_2} + C_c) + C_c p_{m_2} + G_{O_1} G_{O_2} \right] \\ = p_{m_1} (p_{m_2} - C_c \delta) V_c$$

$$\begin{aligned}
 \frac{V_{O2}}{V_i} &= \frac{V_o}{V_i} = \frac{g_{m1} g_{m2} \left(1 - \frac{C_c}{g_{m2}}\right)}{\left[ C_{O1} C_{O2} + C_c C_{O1} + C_{O2} C_c \right] s^2 + \left( G_{O2} (C_{O1} + C_c) + G_{O1} (C_{O2} + C_c) + C_c g_{m2} \right) s + \underbrace{G_{O1} G_{O2}} \\
 &= \frac{g_{m1} g_{m2}}{G_{O1} G_{O2}} \left( 1 - \frac{C_c}{g_{m2}} s \right) \frac{C_{O1} C_{O2} + C_c C_{O1} + C_{O2} C_c}{G_{O1} G_{O2}} + \left( \frac{C_{O1} + C_c}{G_{O1}} + \frac{C_{O2} + C_c}{G_{O2}} + \frac{C_c g_{m2}}{G_{O1} G_{O2}} \right) s + 1 \\
 &= A_o \frac{1 - s/\omega_z}{(1 + s/\omega_{p1}) (1 + s/\omega_{p2})} = A_o \frac{N(s)}{D(s)}
 \end{aligned}$$

It has two poles and one zero

Zero is in R.H.P.

$$\omega_z = \frac{p_{m2}}{c_c}$$

Roots of  $D(s)$  are poles.

$$D(s) = \frac{s_0, s_0 + c_c s_0 + s_0 c_c p_2}{s_0, s_0} + \left( \frac{s_0 + c_c}{s_0} + \frac{s_0 + c_c}{s_0} + \frac{c_c p_{m2}}{s_0, s_0} \right) s + z$$

Since after compensation,  $\omega_p < \omega_z$

$$ax^2 + bx + c = 0 \Rightarrow x^2 + \frac{b}{a}x + \frac{c}{a} = 0$$

assume  $x_1$  &  $x_2$  are the roots

$$(x - x_1)(x - x_2) = 0$$

$$x^2 - (x_1 + x_2)x + x_1x_2$$

$$x_2 \gg x_1$$

$$x_1 + x_2 \approx x_2$$

$$x^2 - x_2x + x_1x_2 = 0$$

$$x_2 = -\frac{b}{a}$$

$$x_1 x_2 = \frac{c}{a} \quad \Rightarrow \quad x_1 = \frac{1}{x_2} \times \frac{c}{a} = -\frac{c}{b}$$

$$\frac{c_0 + c_2 + c c_0 + c_2 c c_2}{g_0, g_2} + \left( \frac{c_0 + c c}{g_0} + \frac{c_2 + c c}{g_2} + c c g_2 \right) \delta + \gamma$$

$\downarrow$  ↪ ↵  
 $a$   $b$   $c$

$$w_{p_1} = \frac{c}{b} = \frac{1}{\frac{c_0 + c c}{g_0} + \frac{c_2 + c c}{g_2} + \frac{c c g_2}{g_0, g_2}}$$

$$w_{p1} = \frac{g_{o1} g_{o2}}{g_{o2} (C_{o1} + C_c) + g_{o1} (C_{o2} + C_c) + C_c g_{m2}}$$

↓ can be ignored

↓ dominant

$$w_{p1} \approx \frac{g_{o1} g_{o2}}{C_c g_{m2}} = \frac{1}{(g_{m2} R_{o2}) (R_{o1} C_c)}$$

→ Miller effect

role before compensation

$$w_{p1} = \frac{1}{R_{o1} C_{o1}}$$

$\omega_{p1}$  is shifted to lower frequency after compensation

$$\omega_{p2} = \frac{5}{a} = \frac{\frac{c_0 + c_c}{h_{01}} + \frac{c_{02} + c_c}{h_{02}} + \frac{c_c g_{m2}}{h_{01} h_{02}}}{\frac{c_0, c_{02} + c_c, c_{02} c_c}{g_{01} h_{02}}}$$



ignore  $g_{01} h_{02}$

$$= \frac{g_{02}(c_0 + c_c) + g_{01}(c_{02} + c_c) + c_c g_{m2}}{g_{02}(c_0 + c_c) + c_c c_0} \rightarrow \text{dominant}$$



$$= \frac{C_c g_{m2}}{\omega_2 (C_{o1} + C_c) + C_c \omega_1} = \frac{\frac{C_c}{\omega_1 + C_c}}{\omega_2 + \frac{C_c \omega_1}{\omega_1 + C_c}} \beta$$
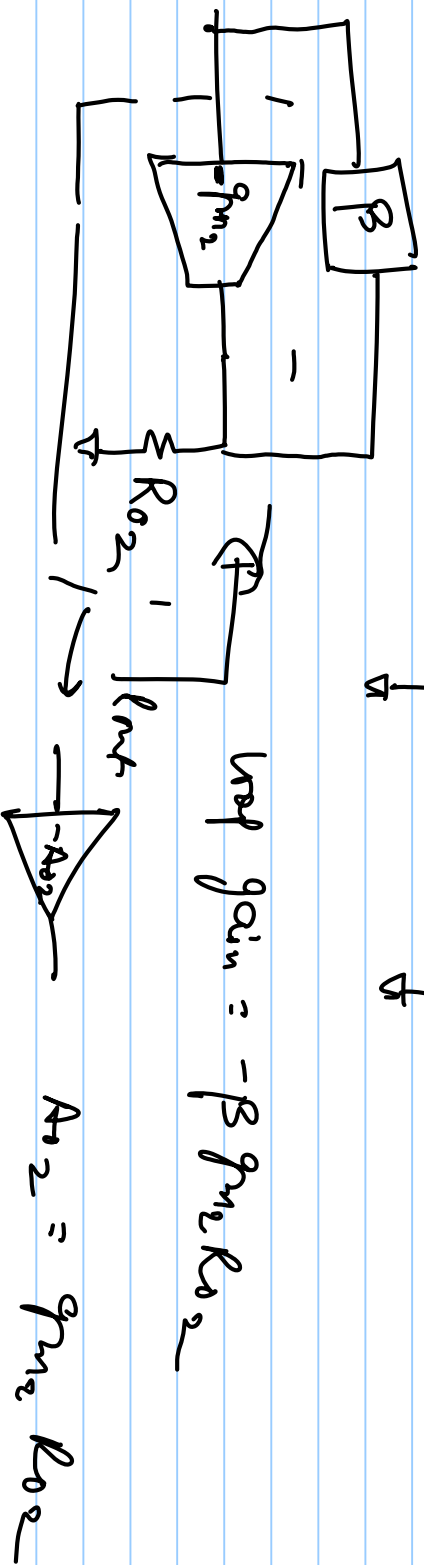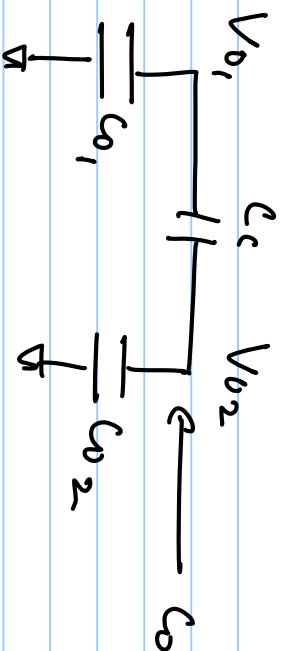
$$\omega_0 = \omega_2 + \frac{C_c \omega_1}{\omega_1 + C_c} \Rightarrow$$



---

Effective Rate