
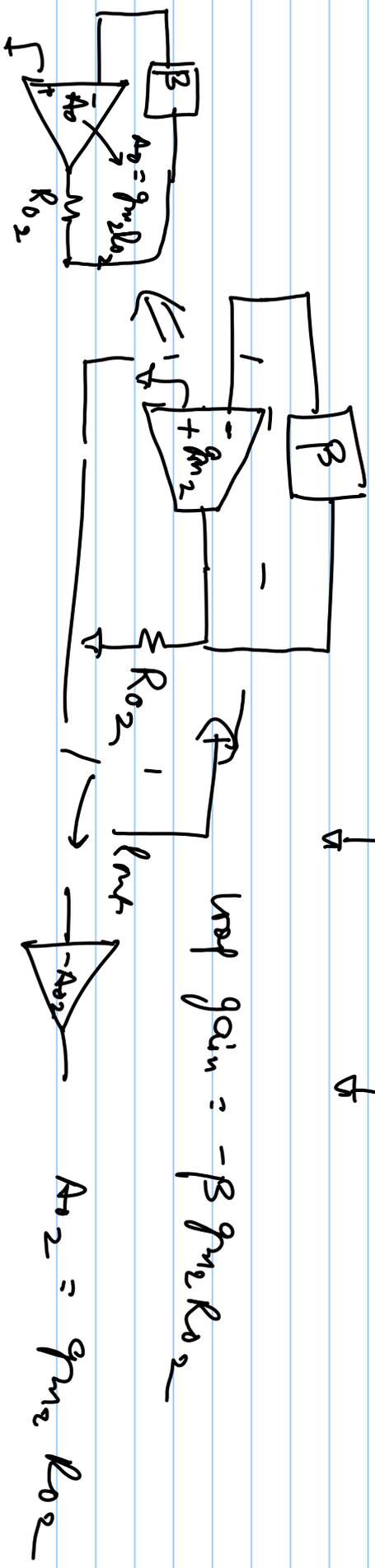


Analog Systems 4 Lab

$$= \frac{C_c g_{m2}}{\omega_2 (\omega_1 + C_c) + C_c \omega_1} = \frac{C_c}{\omega_1 + C_c} \cdot \frac{g_{m2}}{\omega_2 + \frac{C_c \omega_1}{\omega_1 + C_c}} \xrightarrow{\beta} \beta \frac{C_c g_{m2}}{\omega_2 + \frac{C_c \omega_1}{\omega_1 + C_c}}$$
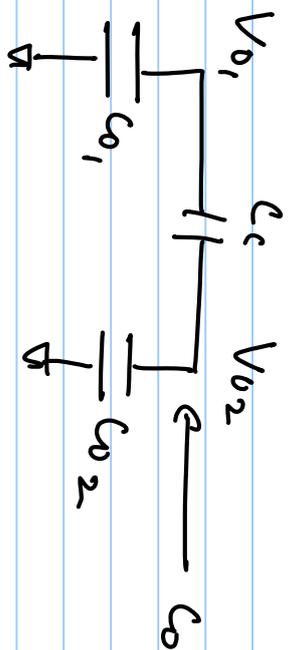
$$\omega_0 = \omega_2 + \frac{C_c \omega_1}{\omega_1 + C_c} \Rightarrow$$



$$\text{effective } R_{mf} = \frac{R_{o2}}{1 + A_{o\beta}} \approx \frac{R_{o2}}{A_{o\beta}} = \frac{\cancel{R_{o2}}}{g_{m2} \cancel{R_{o2}} \alpha \beta} = \frac{1}{\beta g_{m2}}$$

$$w_{p2} = \frac{1}{R_{mf} \times C_o}$$

$$C_o = C_{o2} + \frac{C_c C_{o1}}{C_{o1} + C_c} \quad \& \quad R_{mf} = \frac{1}{\beta g_{m2}}$$

without compensation

$$\omega_{p1} = \frac{1}{R_{o1} C_{o1}}$$

$$\omega_{p2} = \frac{1}{R_{o2} C_{o2}}$$

with compensation

$$\omega_{p1} = \frac{1}{R_{o1} (g_{m2} R_{o2}) C_c}$$

$$\omega_{p2} = \frac{\frac{C_c}{C_{o1} + C_c} g_{m2}}{C_{o2} + \frac{C_{o1} C_c}{C_{o1} + C_c}}$$

assume, $C_c \gg C_{o1}$

$$\omega_{p2} = \frac{g_{m2}}{C_{o2} + C_{o1}}$$

Assume, $A_0 = 1000$;

$g_{m1} = 100 \mu A/V$, $R_{01} = 1 M\Omega$, $g_{m2} = 100 \mu A/V$, $R_{02} = 10 k\Omega$

$$g_{m1}, R_{01} = 100$$

$$g_{m2}, R_{02} = 10$$

$$\rightarrow A_0 = 1000$$

$$\omega_{01} = 10 pF \quad \& \quad \omega_{02} = 10 pF$$

$$\omega_{p1} = \frac{1}{R_{01} C_{01}} = \frac{1}{10^6 \times 10^{-11}} = 10^5 \text{ rad/sec}$$

$$\omega_{p2} = \frac{1}{R_{02} C_{02}} = \frac{1}{10^4 \times 10^{-11}} = 10^6 \text{ rad/sec}$$

After compensation

$$\omega_{p2} = \frac{100 \mu}{(10 pF + 10 pF)} = 5 \times 10^6 \text{ rad/sec}$$

Wugs for 60° phase margin


$$\omega_{ugs} = \frac{1}{\sqrt{3}} \omega_{p2} = \frac{5}{1.7} \times 10^6 \text{ rad/sec} \approx 3 \times 10^6 \text{ rad/sec}$$

$$\omega_{p1} = \frac{\omega_{ugs}}{A_D} = \frac{3 \times 10^6 \text{ rad/sec}}{1000} = 3 \times 10^3 \text{ rad/sec}$$

$$\omega_{p1} = \frac{1}{R_{01}(R_{02}g_{m2})C_c} = 3 \times 10^3 \text{ rad/sec}$$

$$\begin{aligned} C_c &= \frac{1}{R_{01} (R_{02} g_{m_2}) \times 3 \times 10^3} = \frac{1}{10^6 \times (10) (3 \times 10^3)} \\ &= \frac{10^{-16}}{3} = 0.33 \times 10^{-16} \approx \boxed{33 \text{ PF}} \end{aligned}$$

S-Plane

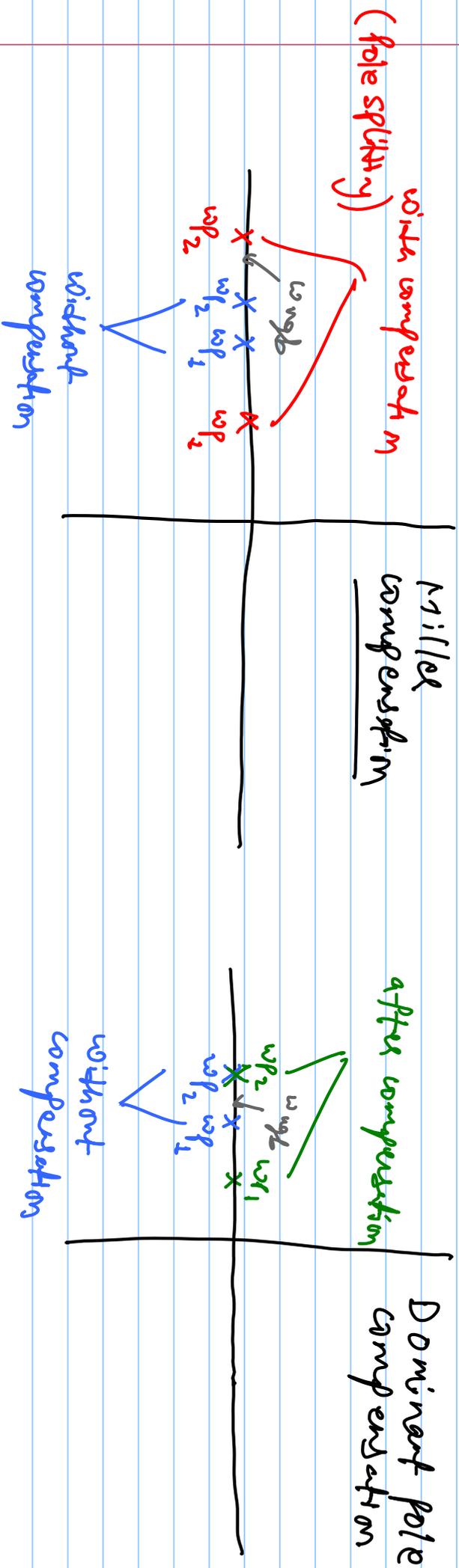


So far we have ignored R.H.P. zets

$$\omega_z = \frac{g_{m2}}{C_c} = \frac{100 \mu}{33 \text{ pF}} = \frac{10^{-4}}{33 \times 10^{-12}} = \frac{100}{33} \times 10^6$$

$$= 3.23 \text{ Mrad/sec}$$

$$\approx \omega_{ngb}$$

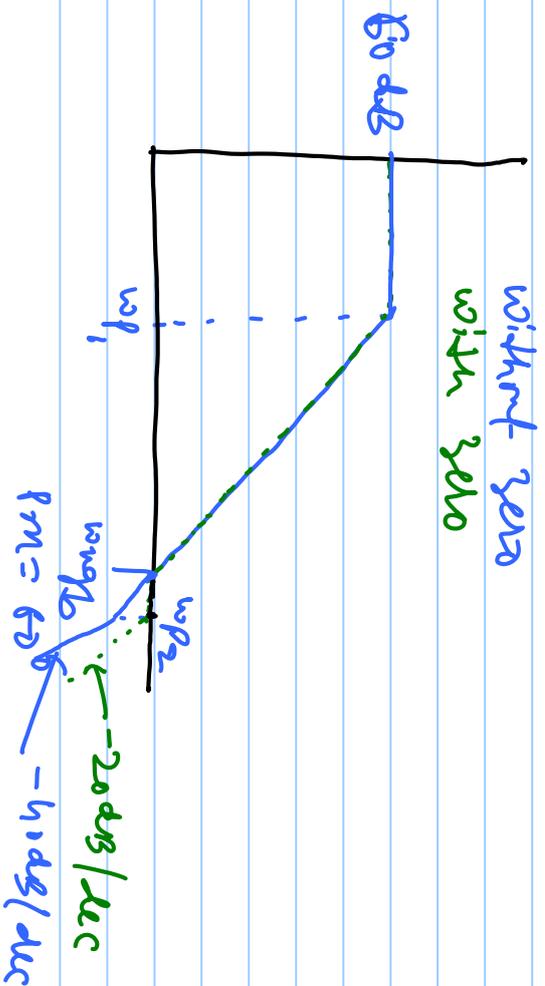

PM without zero = 60°

PM with zero ≈ 15°

$$\omega_{p1} = \frac{\omega_{ngb}}{A_0}$$

$$\Rightarrow \omega_{ngb} = A_0 \omega_{p1} = g_{m1} R_{D1} \cdot g_{m2} R_{D2} \times \frac{1}{R_{D1} (g_{D2} R_{D2}) C_c}$$

$$\omega_{ngb} = \frac{g_{m1}}{C_c} \quad \text{L.N.P.}$$

$$\omega_z = \frac{g_{m2}}{C_c} \quad \text{R.N.P.}$$

Phase Margin after Miller compensation

$$PM = 90^\circ - \tan^{-1} \frac{\omega_{ngb}}{\omega_{p2}} - \tan^{-1} \frac{\omega_{ngb}}{\omega_z}$$

$\underbrace{\qquad\qquad\qquad}_{\tan^{-1} \omega_{p2} / \omega_{ngb}}$


$$= \tan^{-1} \frac{\omega p_2}{\omega q_2} - \tan^{-1} \frac{\omega v q_2}{\omega^2} = \tan^{-1} \frac{q_2 / (\omega_1 + \omega_2)}{q_1 / \epsilon} - \tan^{-1} \frac{q_1 / d}{q_2 / \epsilon}$$

$$= \tan^{-1} \frac{q_2}{q_1} \left(\frac{\epsilon}{\omega_1 + \omega_2} \right) - \tan^{-1} \frac{q_1}{q_2}$$

$$\frac{q_1}{q_2} \ll \ll$$

$$q_2 \gg 10 \times q_1$$

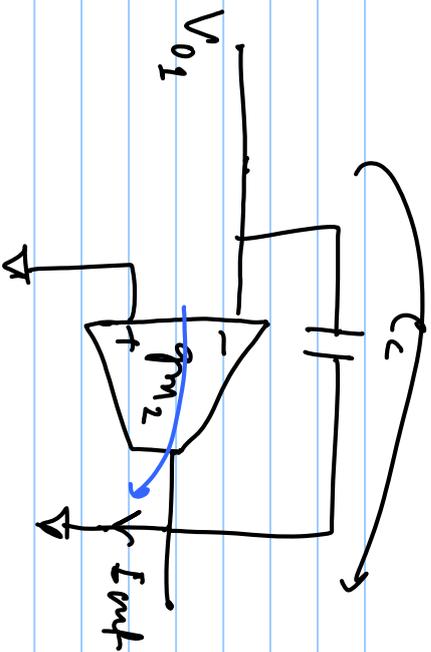↙ This should be minimized to
in case the P.M




without C_c

$$I_{out} = -g_{m2} V_{O1}$$

with C_c

$$I_{out} = -g_{m2} V_{O1} + V_{O1} C_c s$$

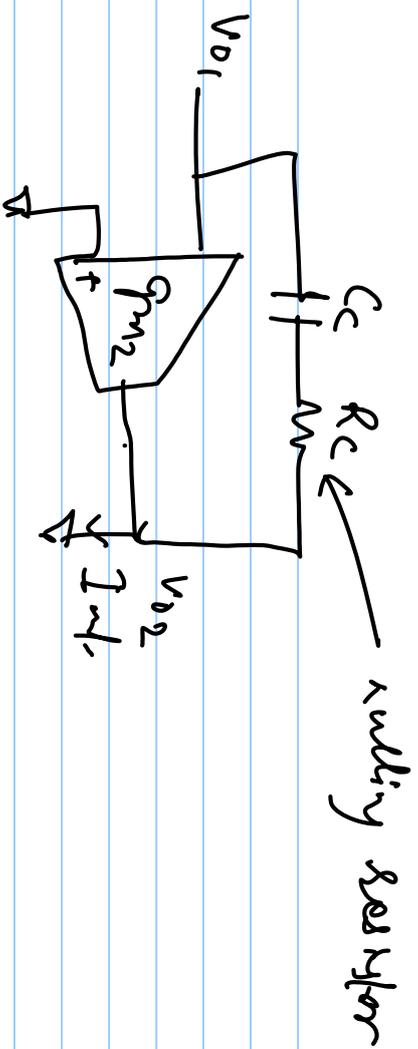in order to maintain -ve feedback, current through C_c should be less than current from g_{m2}



R_e will limit the cut-off frequency C_c unless R_c should be less than cut-off frequency g_{m2}

$$R_c > \frac{1}{g_{m2}}$$

$$\omega_z = -\frac{1}{(R_c - \frac{1}{g_{m2}}) C_c}$$

L.N.P if $R_c > \frac{1}{g_{m2}}$
 R.N.P if $R_c < \frac{1}{g_{m2}}$

$\rightarrow \infty$ if $R_c = \frac{1}{g_{m2}}$

if $R_c > \frac{L}{m_2}$

$\omega_z = \omega_{p2} \rightarrow \omega_{p2}$ is cancelled out Δ system becomes 1st

order

order

↙ pole-zero cancellation.

U.S.B can be expected at much higher frequency

always stable