


EE3002: Analog circuits

Note Title

1/28/2013


EE5310: Analog electronic circuits

Problem set #2 (Due on 1st Oct 2015)

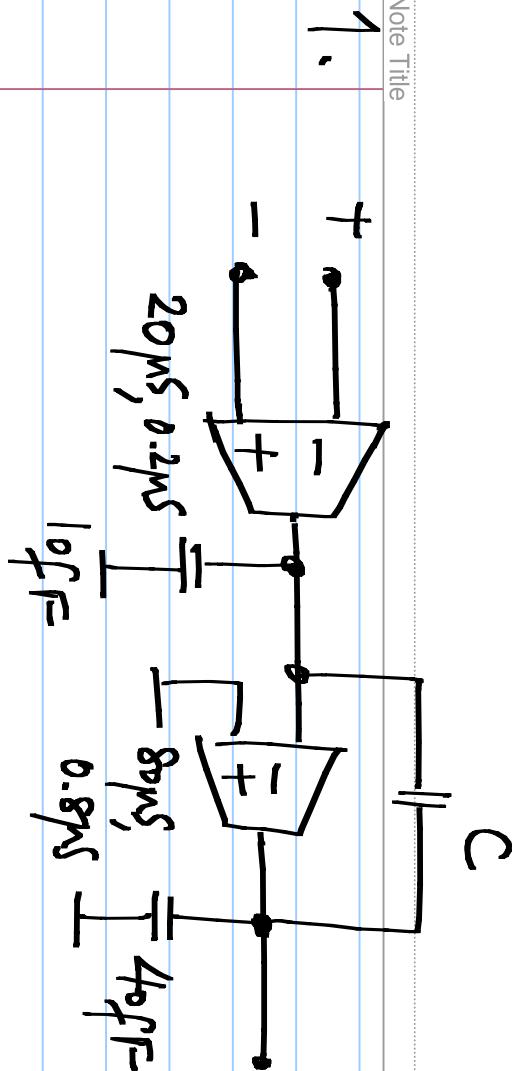

TWO STAGE OPAMP

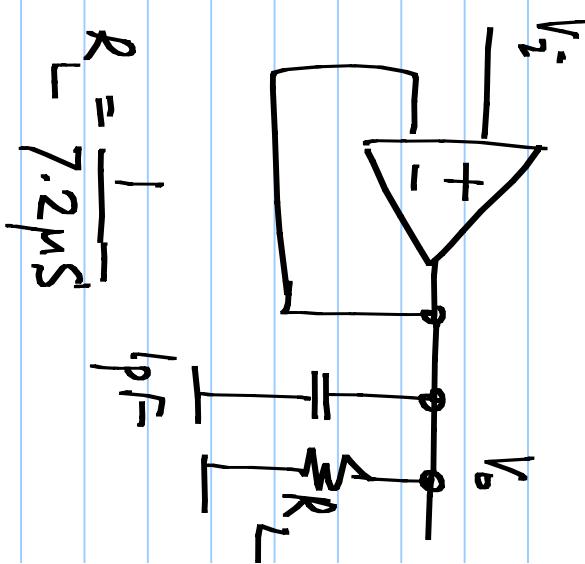
The two stage opamp above is used in the unity gain follower on the right. Determine C for $s\omega_0$ plane margin and the resulting bandwidth of the unity gain buffer.



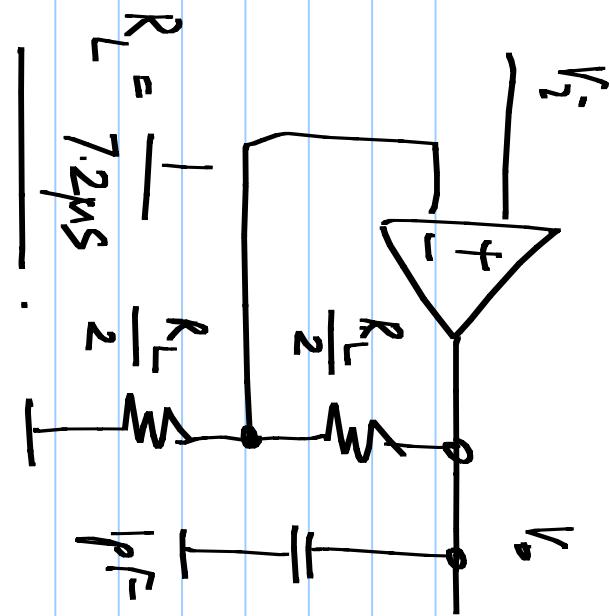2.

The two stage opamp above is used (as is) in the 2x amplifier on the right. What is the phase margin of the loop and the closed loop bandwidth of the amplifier?


margin of the loop and the closed loop bandwidth of the amplifier?



3.

If you are allowed to change "C" in the opamp in the above problem, what value would you use to get 60° phase margin? What is the bandwidth of the 2x amplifier in this case?

$12.5k\Omega$ C

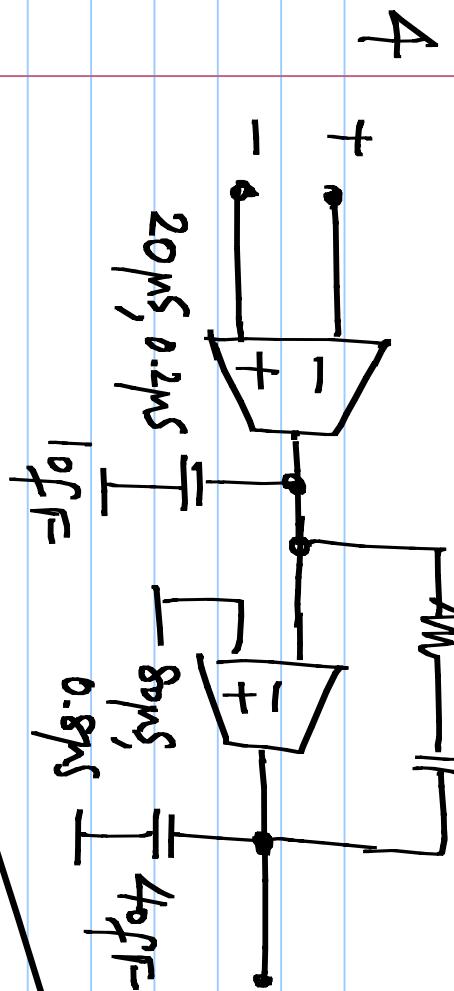

Analyze the !

A zero cancelling resistor is used in series with the integrating capacitor. Repeat prob #1 for this case.

5. Repeat prob #3 with the opamp above

6. In each of the above cases, you would have used some approximations. In each case, with the value of " C " that you used, determine the exact closed loop transfer function and determine the closed loop poles and zeros. You can use a numerical solver to determine these if necessary.