

Analog Circuits (EE3002/EE5310) : Problem Set 10

shanthi@ee.iitm.ac.in

1

For the transistor shown, $\beta = 99$, and V_{BE} is nominally 0.65 V. Find the quiescent V_{CE} , r_i , r_o and the incremental voltage gain. Assume $v_i = (1 \text{ mV}) \sin \omega t$. All capacitors are infinite.

 


Figure 1: Figure for problem 1.

2

In the circuit shown, use $\alpha = 0.995$, $V_T = 25 \text{ mV}$. The quiescent V_{CE} must be 5 V and r_i - the resistance presented by the circuit to the driving source v_i must be 1.5 K. Use $V_{BE} = 0.7 \text{ V}$ nominally. Calculate V_{cc} , R_1 & R_2 to get a small signal gain of -200 .

 


Figure 2: Circuit for problem 2.

3

The signal picture of an amplifier is as shown.

 


Figure 3: Circuit for problem 3.

Find R_i , R_o and $\frac{v_o}{v_i}$ in terms of g_m , β and r_o (the incremental output resistance of the device). Find their limits when $\beta \rightarrow \infty$. The signal is small.

4

Assume in the figure shown that g_m is high enough to make the incremental voltage gain $\frac{v_o}{v_i}$ independent of the device. Assume all capacitors are large. Also assume that $aR \parallel (1-a)R \ll (1+\beta)R$. Take $V_{EB} = 0.7 \text{ V}$ nominally; $I_E R_e = 4.3 \text{ V}$. A gain of -4 is needed with the circuit being just capable of handling a maximum amplitude of 2 V for the input sinusoid v_i . V_{ee} should be the minimum possible for the specified $I_E R_e$. Calculate R_1 , R_e , V_{ee} and a . Next remove the external load of 12 K. What will the limiting swings possible for v_o on either side now? To what maximum amplitude will you have to restrict v_s if v_o is to be a full undistorted sine wave?

5

The input sine wave has $v_i = 2.5 \text{ V}$. To get an undistorted output within swing limits, calculate V_{cc} and R . Take V_{BE} nominal = 0.65 V. Also calculate R_i for small signals given that $\beta = 100$ and $V_T = 25 \text{ mV}$.

 


Figure 4: Circuit for problem 4.

 


Figure 5: Circuit for problem 5.

6

$V_{BE} = 0.65 \text{ V}$ nominally. $V_T = 25 \text{ mV}$. For small signals, find R_i and $\frac{v_o}{i_s}$. Assume $\beta = 250$.

 


Figure 6: Circuit for problem 6.

7

The capacitances are very large. v_o , the output sinusoid, is to be linked with the input sinusoid by a device independent gain factor of 2, with a limiting amplitude of 8 V before clipping sets in. v_o should just begin to distort at both the extremes.

 


Figure 7: Circuit for problem 7.

Find V_{cc} , V_{bb} and R_e . V_{BE} is 0.7 V, nominally. Given that $R_b \ll (\beta + 1)R_e$, comment on the stability of the transistor operating point - that is, compute the change in emitter current when the nominal V_{BE} changes by $\pm 0.1 \text{ V}$ due to device variability and/or ambient temperature.

Now let $R_L \rightarrow \infty$. What are the limiting swings now possible for v_o on the either side? To what value will you restrict the amplitude of v_i to get an undistorted sinusoidal output?

8

The transistor has very high β . With minimum possible V_{bb} and V_{cc} , the circuit should be able to handle the given input of 5 V maximum amplitude. Calculate the values of V_{bb} and V_{cc} required.

 


Figure 8: Circuit for problem 8.

When the 3 K lead is removed, determine the swing possible for v_o on either side, and the maximum amplitude to which v_i must now be restricted if v_o is to be a full undistorted sine wave. Take $V_{BE} = 0.7$ V, nominally. Assume all capacitances are large.

9

All the coupling capacitors are very large in value. Take $V_T = 25$ mV, $\alpha = 0.99$. Find for small signals R_i , R_{o1} as seen from the output terminal 1, R_{o2} as seen from output terminal 2, v_{o1}/v_i and v_{o2}/v_i .

 


Figure 9: Circuit from problem 9.

10

$V_{BE} = 0.65$ V nominally. $V_T = 25$ mV. Calculate R_i for small signals. Also find the positive and negative limits for v_o if it is to be free from distortion. Take $\beta = 200$, $V_{cc} = 15.65$ V.

 


Figure 10: Circuit for problem 10.

11

The input v_i is a sine wave with an amplitude of 3.75 V. To get an undistorted output sine wave within swing limits, calculate V_{cc} and R .

 


Figure 11: Circuit for problem 11.

If $V_T = 25$ mV, $\beta = 200$, $r_o = 40$ K, Calculate R_o . Take $V_{BE} = 0.65$ V nominally.

12

For very small signals, find v_o/v_i with the proper sign. Take $V_{BE} = 0.65$ V, nominally, $V_T = 30$ mV, $\alpha = 0.995$ for all transistors. Also determine which transistor controls the upper limit of swing and which controls the lower one.

 


Figure 12: Circuit for problem 12.