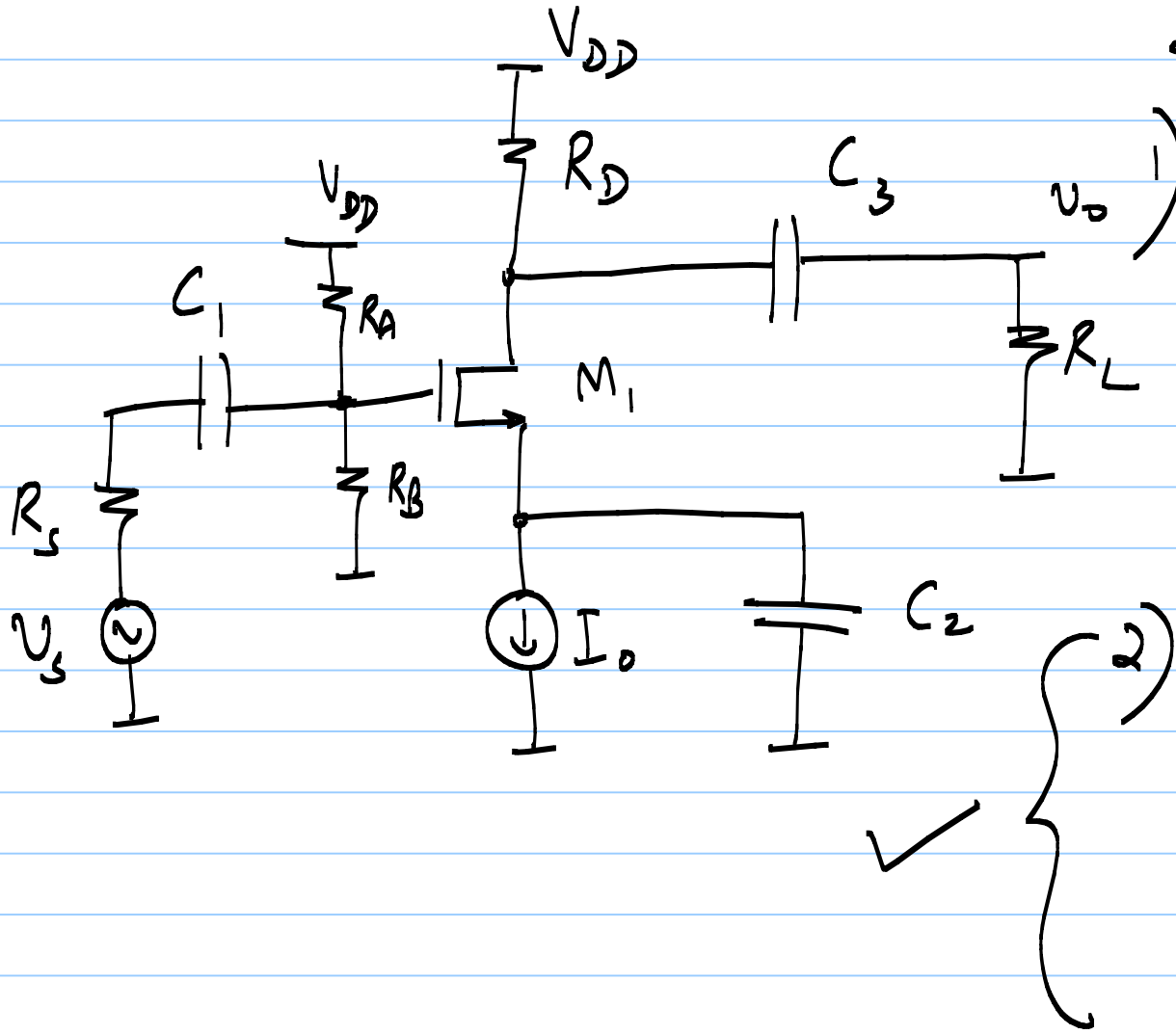


3/9/20

Lecture 18



So far : $C_1, C_2, C_3 = \infty$

1) Choose C_i based

on ac resistance

@ freq. of operation

\Rightarrow small ac resistance


Eg. @ input, you have

HPF \rightarrow plot Bode

curves & choose based

on freq. response

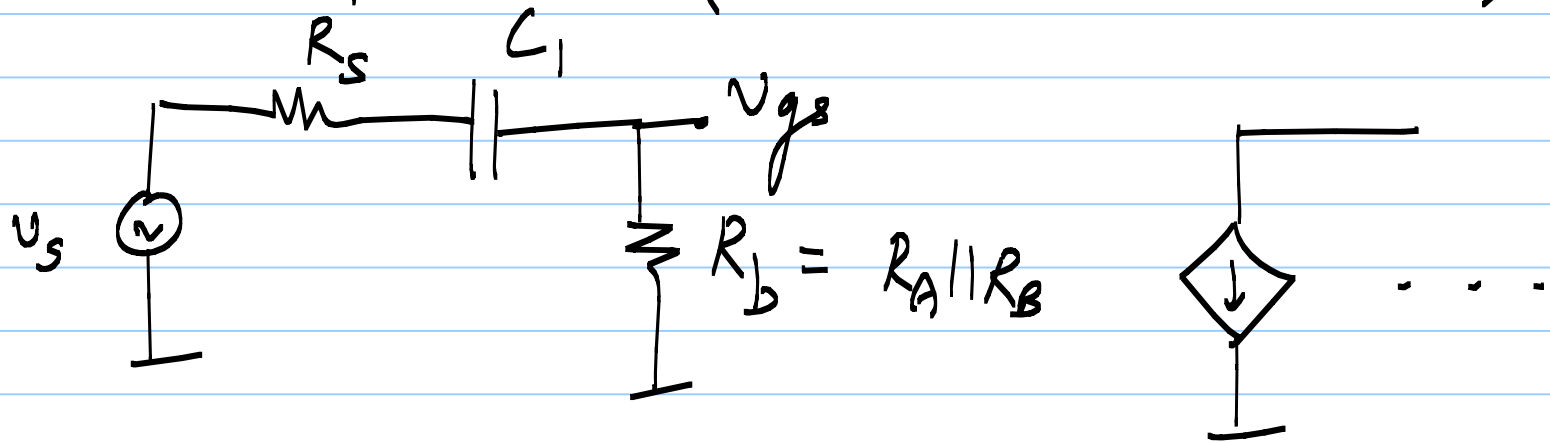SS eq. ckt. @ input: (assume $C_2 = \infty$, $C_3 = \infty$)



want $\rightarrow |v_{gs}| = |v_s|$
 $\searrow |v_o| = g_m(R_D || R_L) \cdot |v_s|$ ($R_b \rightarrow R_s$)


$$v_{gs} = \frac{R_b \cdot v_s}{R_s + R_b + \frac{1}{j\omega C_1}} = \frac{j\omega C_1 R_b \cdot v_s}{1 + j\omega C_1 (R_s + R_b)}$$

Plot $\left| \frac{v_{gs}}{v_s} \right|$

for C_1 : $\left| \frac{v_{gs}}{v_s} \right|$

$\frac{1}{\ln(R_D || R_L || r_{ds})} \cdot \left| \frac{v_o}{v_s} \right|$

for C_3 : \rightarrow
 for C_2 : HW3

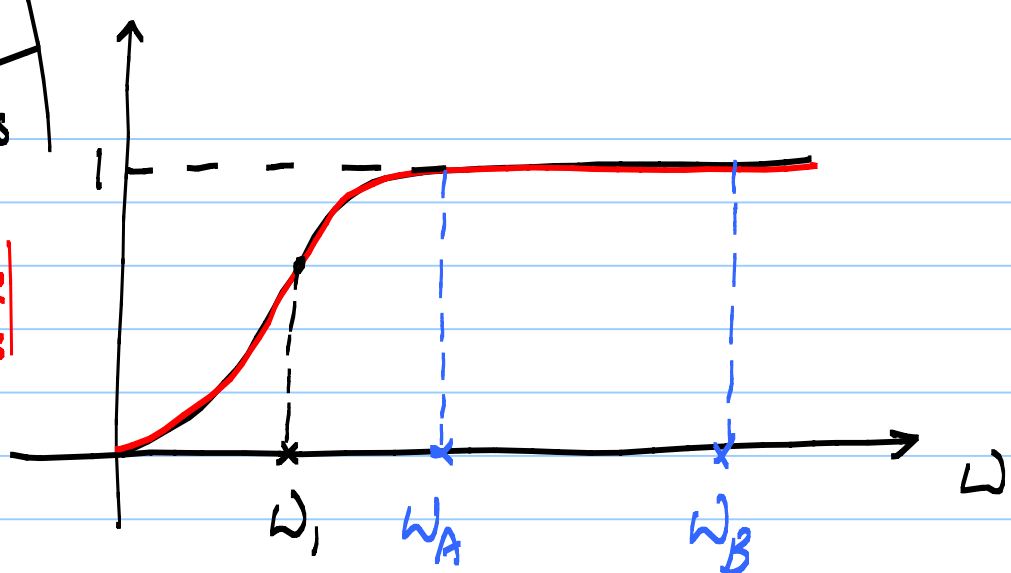

$\omega_1 = -3 \text{ dB}$ free of
 HPF $\left\{ \begin{array}{l} C_1, \phi \\ R_S + R_B \end{array} \right\}$


* Choose $\omega_1 \ll \omega_A$ e.g. $\omega_1 = \frac{1}{10} \omega_A$
 or $\frac{1}{20} \omega_A$ etc.

* pole for C_3 depends on R_D, R_L & r_{ds}

$$r_{ds} = f(\lambda, I_D)$$


$$\lambda = f(L)$$

* pole for C_2 depends on ? HW3


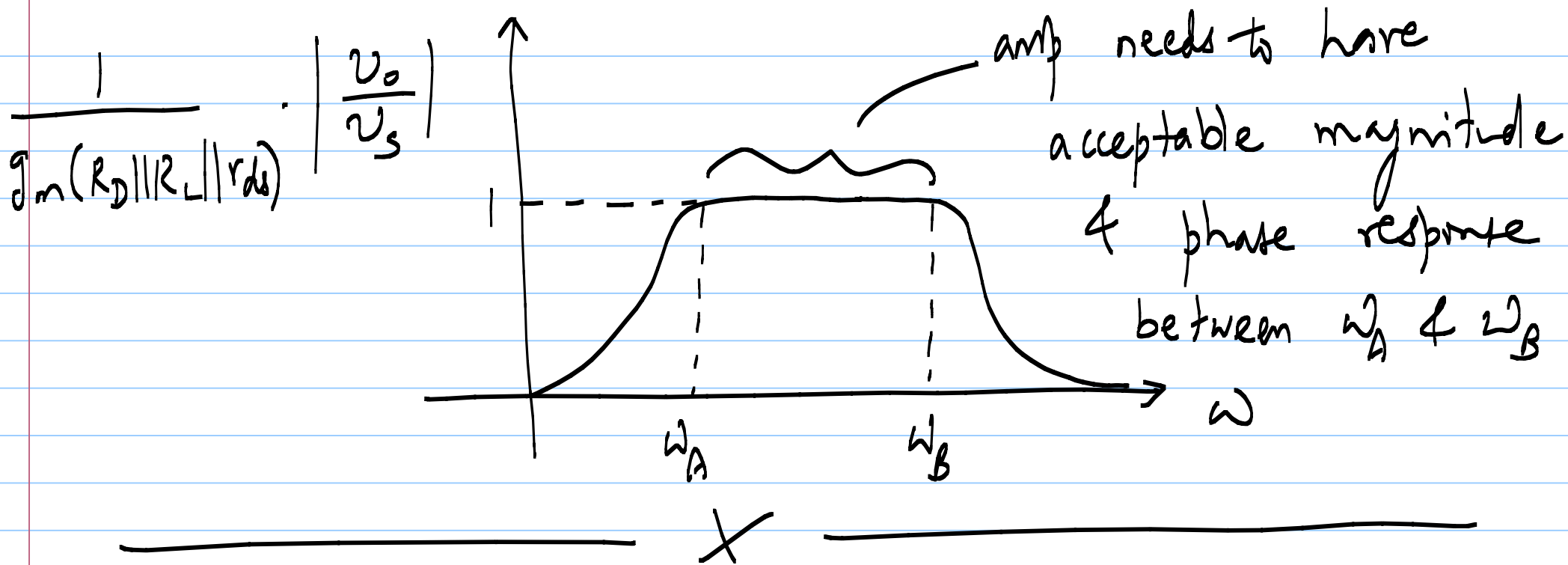


Bias
stab.

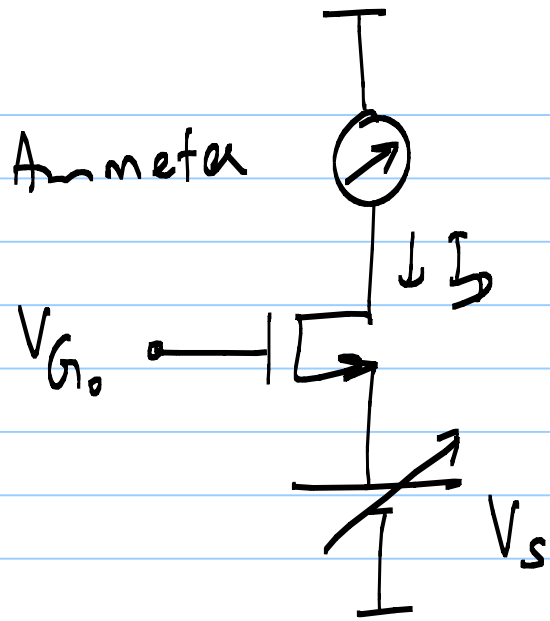- case 1 : Measure I_D , f.b. to V_{in}
- case 2 : Measure I_S , f.b. to V_S
- case 3 : Measure I_D , f.b. to V_S



tune V_s so that $I_D = I_0$

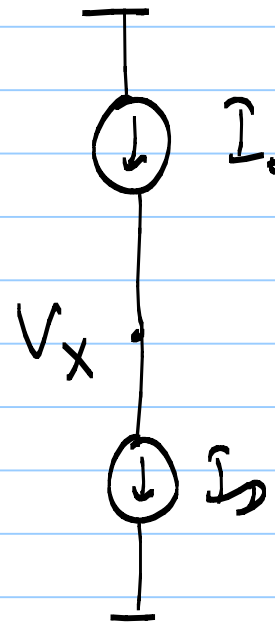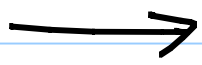

$I_0 < I_D : V_x \downarrow$
 $I_0 > I_D : V_x \uparrow$
 $I_0 = I_D : V_x \leftrightarrow$


e.g. $I_0 < I_D : V_x \downarrow$

We want to $\downarrow V_{as} \Rightarrow \uparrow V_s$

} change in direction of control

inversion in "polarity" of f.b

DC biasing for case 3:

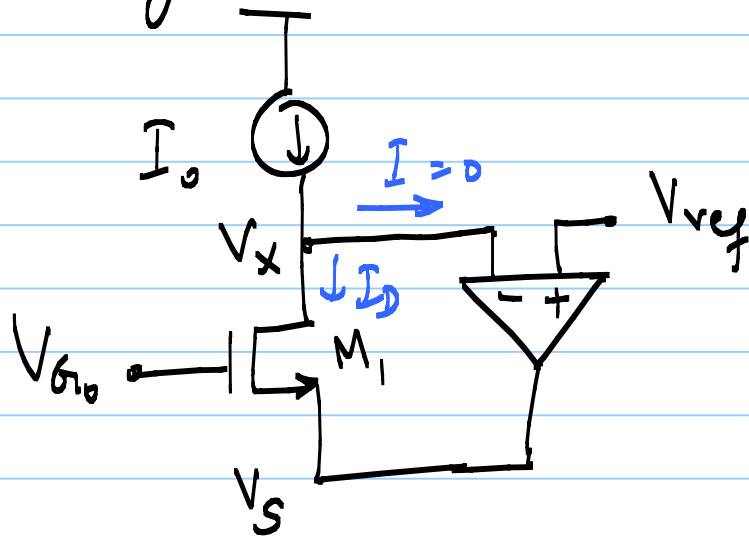


Ideal
 * opamp changes V_S to a value so that $V_x = V_{ref}$

in steady state


* $V_S = V_{G_0} - V_{as}(I_0)$

* opamp only for DC stab.

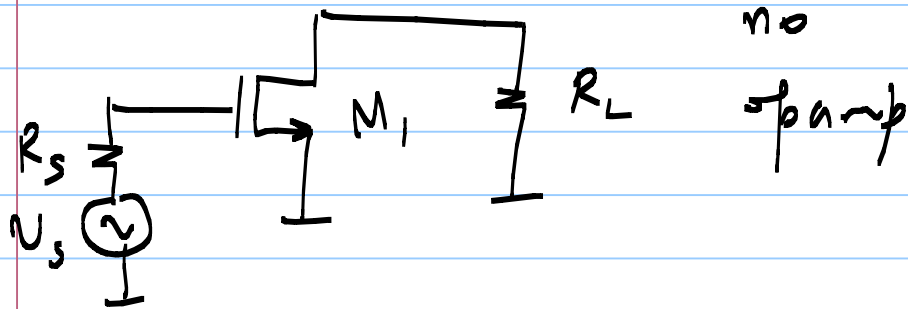
* V_{ref} chosen so that M_1 is biased in sat.



$V_{ref} \geq V_{G_0} - V_T$


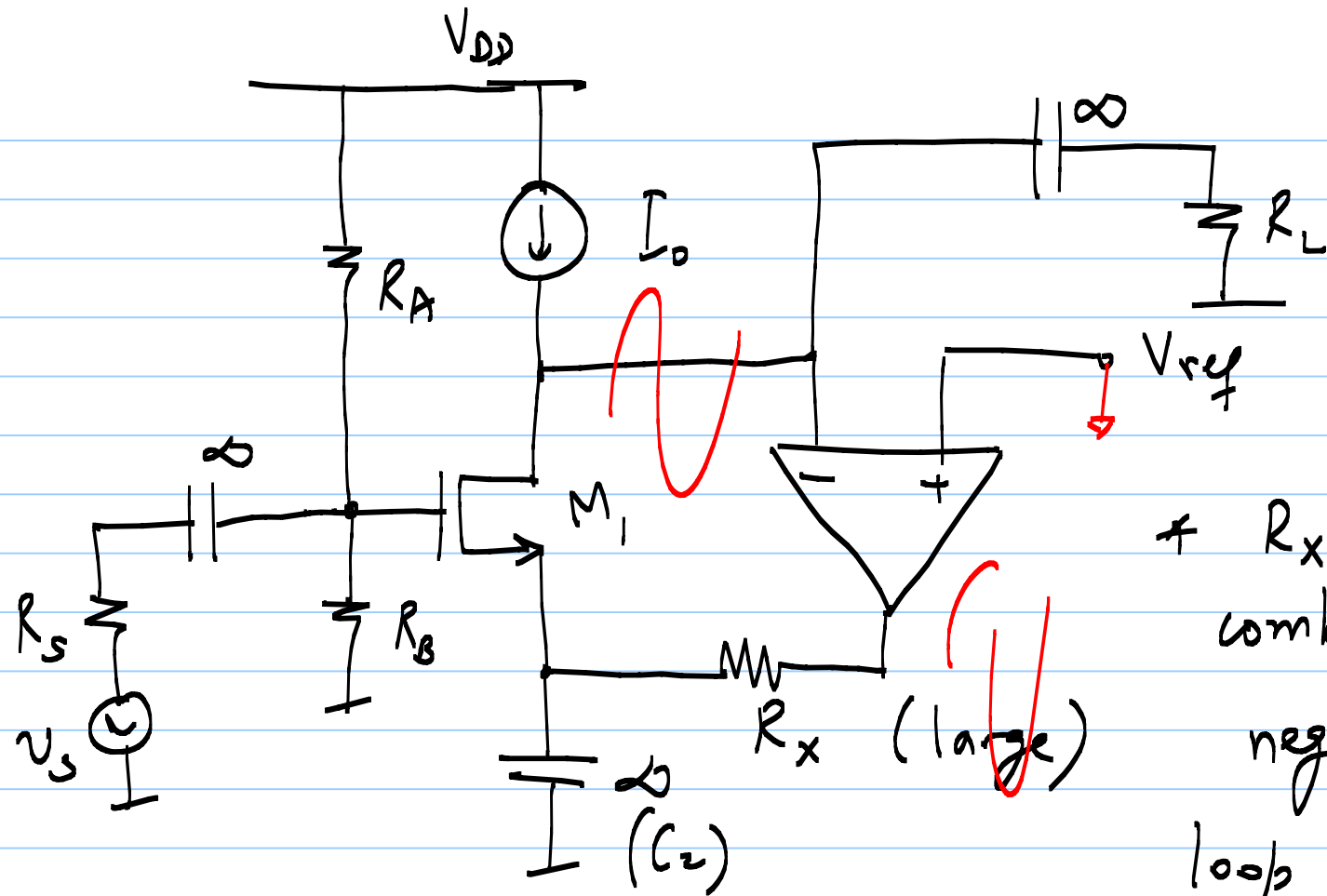


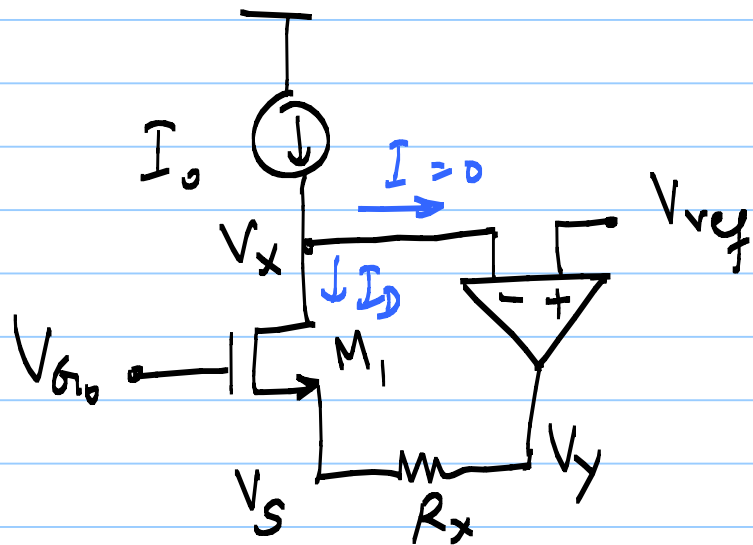$\neq R_x + C_2$
 combo break
 negative f.b.
 loop for small
 signal operation



$$V_y = V_s - I_0 R_x$$

as $R_x \uparrow$, $V_y \downarrow$

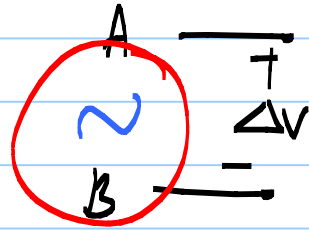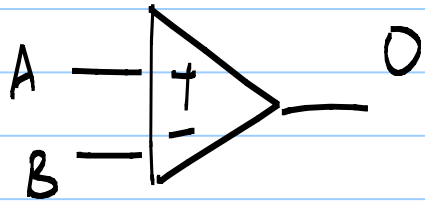

$A \rightarrow \infty$

