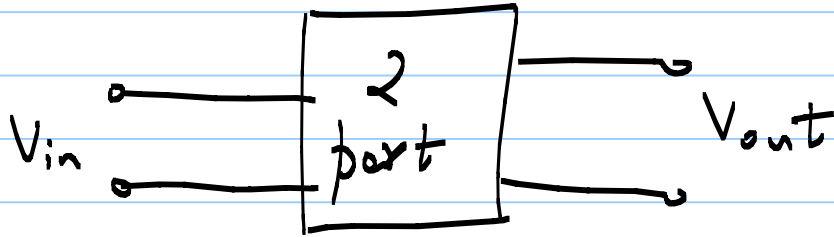


5/8/2020

Note Title

Lecture 2


05-08-2020



Is this linear?

Based on Superposition

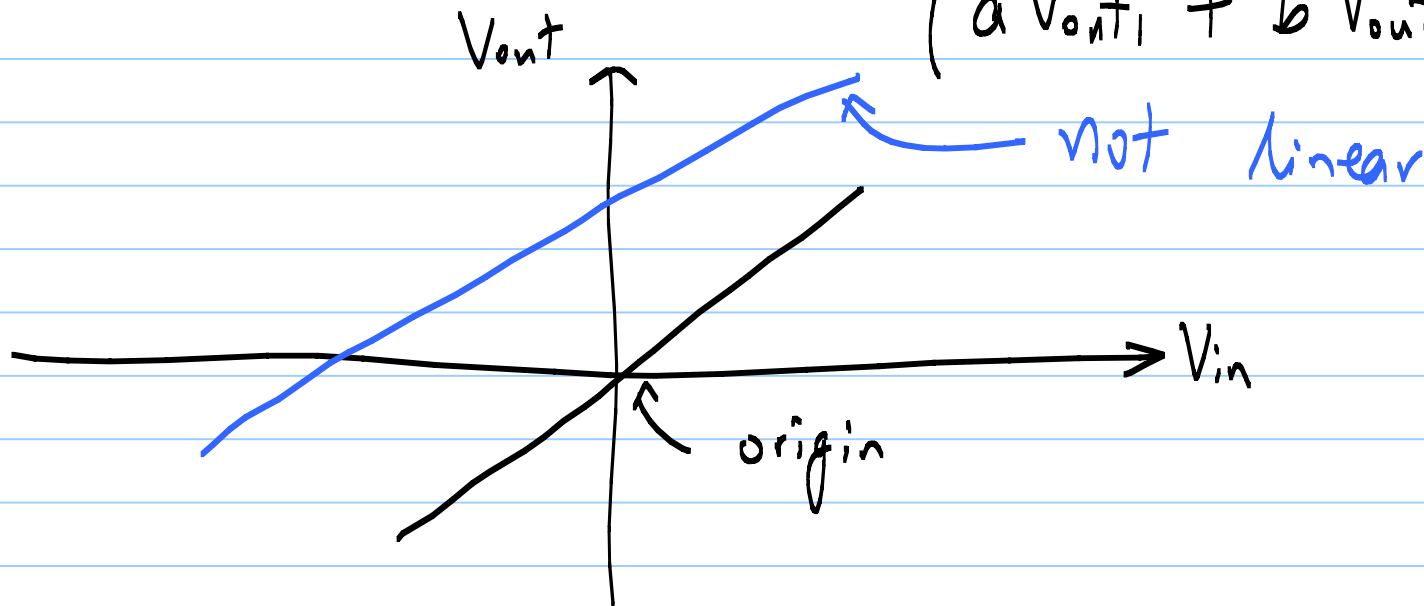
$$\left. \begin{array}{l} V_{in1} \rightarrow V_{out1} \\ V_{in2} \rightarrow V_{out2} \end{array} \right\} \begin{array}{l} (aV_{in1} + bV_{in2}) \\ \downarrow \\ \text{for all } a, b, V_{in1}, V_{in2} \\ (aV_{out1} + bV_{out2}) \end{array}$$



- * LTI systems characterized by Impulse Response
- * All practical systems are Non-linear


Linear Elements (2-terminal 1port systems) "elements"

linear elements

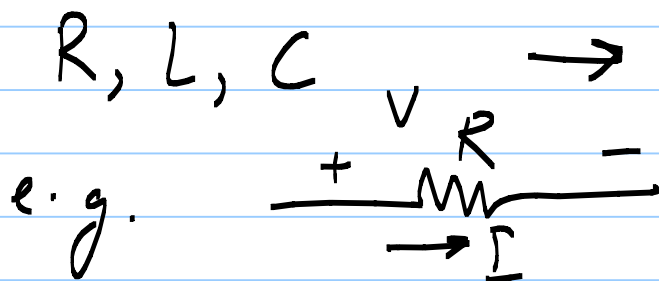

defined by V-I relationship


$$I = \frac{V}{R}$$

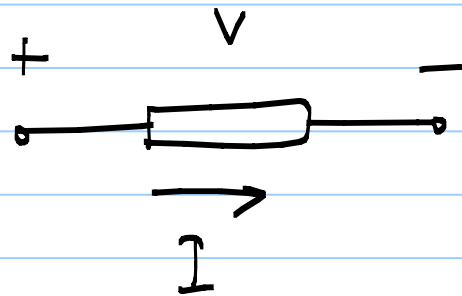

$$I = f(V)$$

Nonlinear 2-T element

Diode :

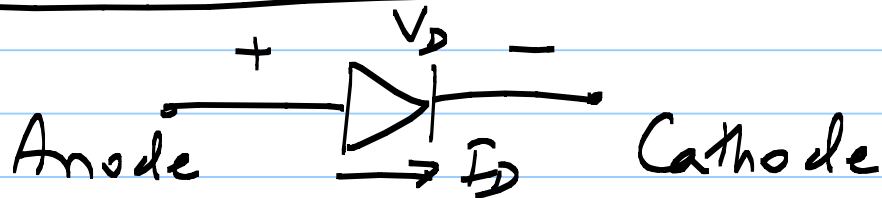

From ISD theory:

$$I_D = I_s \left[\exp\left(\frac{V_D}{V_t}\right) - 1 \right]$$

↑
saturation
current

↑ thermal voltage

$$V_t = \frac{kT}{q} \approx 25\text{mV} \text{ @ } 300\text{K}$$

I_f $V_D > 0 \Rightarrow$ Diode is "forward biased"

$V_D < 0 \Rightarrow$ "reverse biased"

Some approximations:


1) If $V_D \gg V_T$, then $\exp\left(\frac{V_D}{V_T}\right) \gg 1$

$$I_D \approx I_S \exp\left(\frac{V_D}{V_T}\right)$$


$$V_D = V_T \ln\left(\frac{I_D}{I_S}\right)$$

2) If $\frac{V_D}{V_T} \ll 0$, then $\exp\left(\frac{V_D}{V_T}\right) \ll 1$

$$\Rightarrow I_D \approx -I_S$$

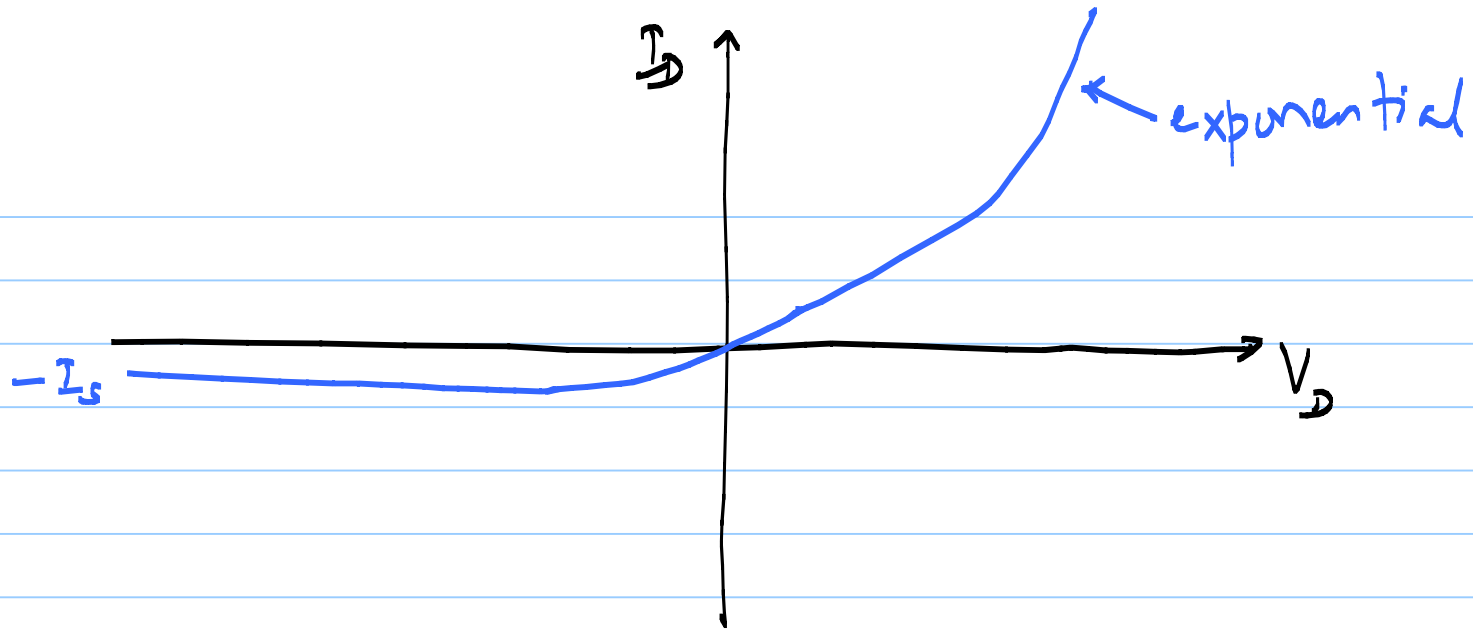

Circuit Analysis w/ diodes

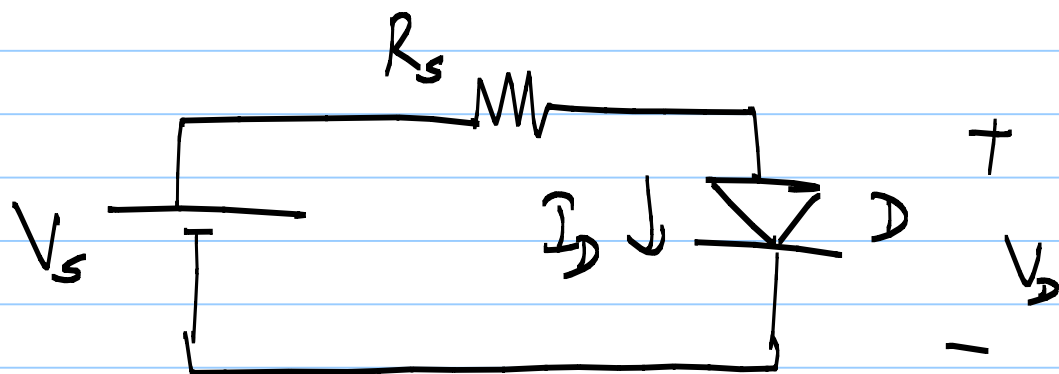

KVL :

$$V_s = V_{R_s} + V_D$$


$$V_s = I_D R_s + V_D = I_D R_s + V_T \ln \left(1 + \frac{I_D}{I_s} \right)$$

Solution

1) Zeroth order:

Assume that the voltage drop across


a forward biased diode $\approx 0.65V$

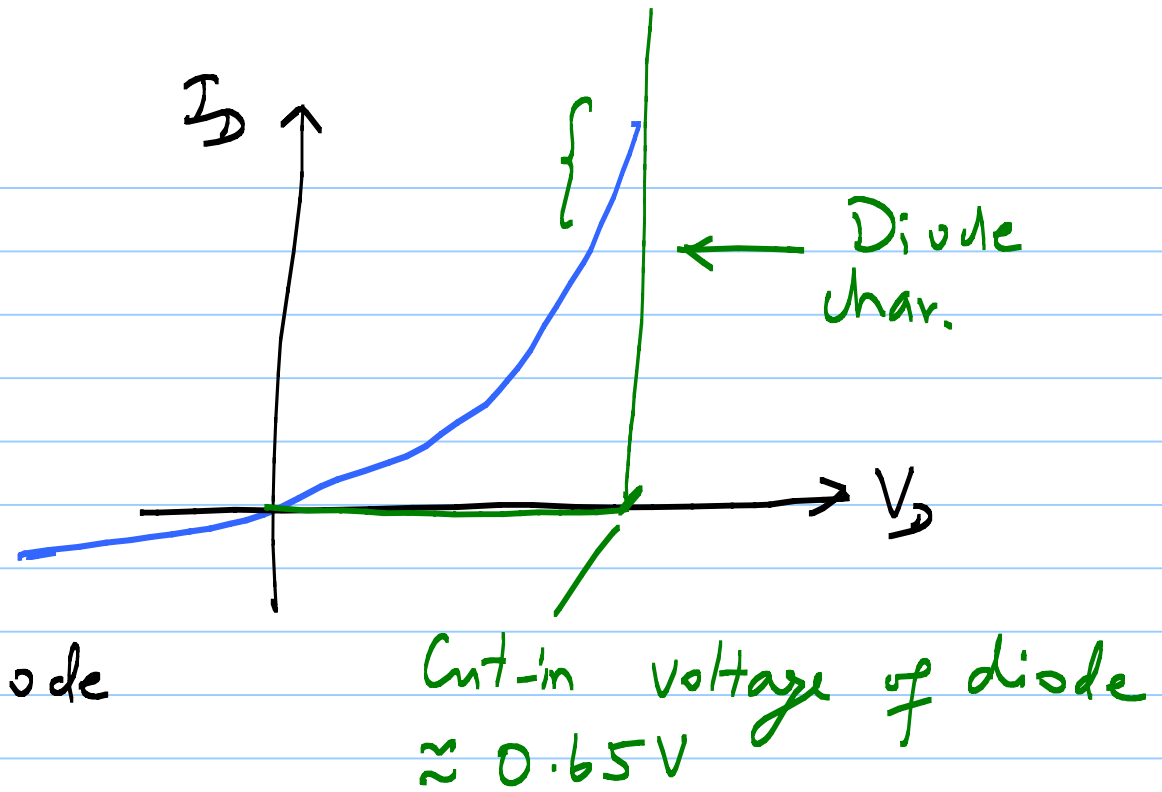

$$I_D \approx \frac{V_s - 0.65}{R_s}$$

2) Exact solution: Iteration (actual characteristic)^{NL}
Numerical Solution

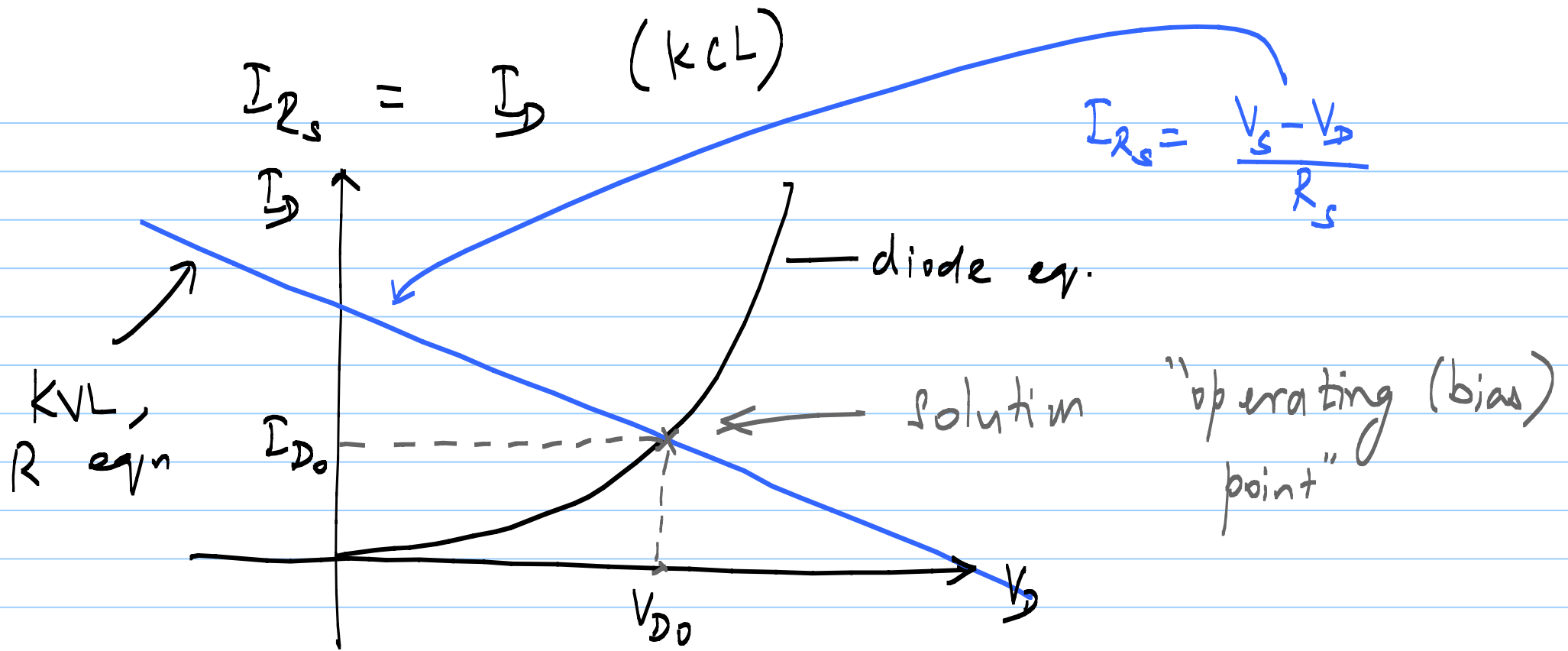3) Graphical solution in $I_D - V_D$ plot



I_f $V_s \rightarrow V_s' = V_s + \Delta V_s$
 new op. pt. ?