
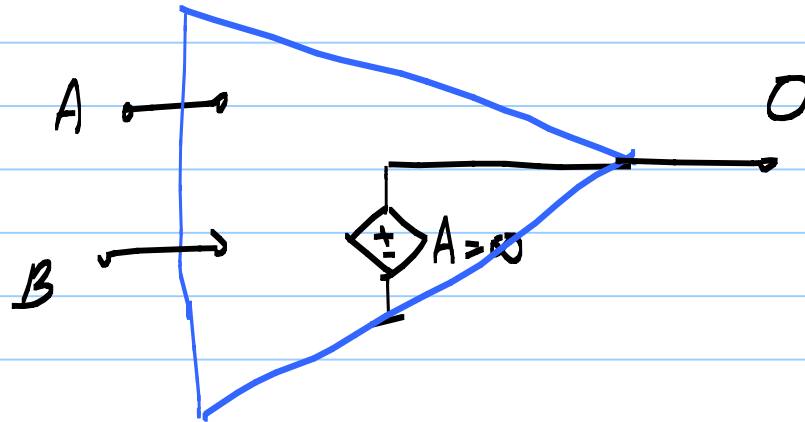


8/9/20


# Lecture 20

Negative f.b. to create small signal controlled sources

## VCVS using opamp

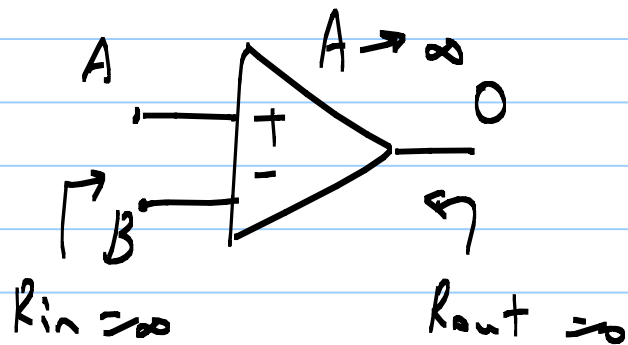



opamp  
VCVS = 1

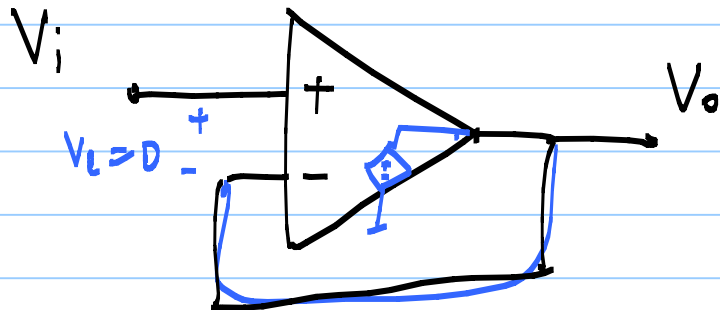

# VCVS using MOSFET (any controlled source)


1) Works only for small-signal

2) Idealized view for MOSFET:

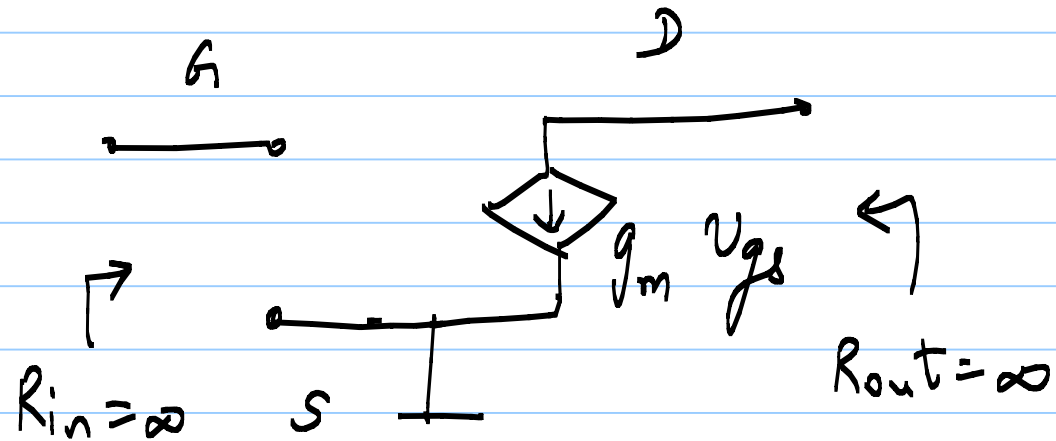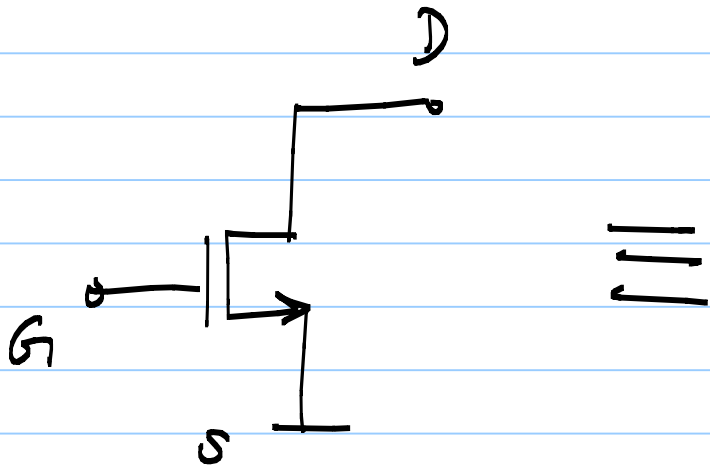

$$G_m = g_m$$

allow  $g_m \rightarrow \infty$

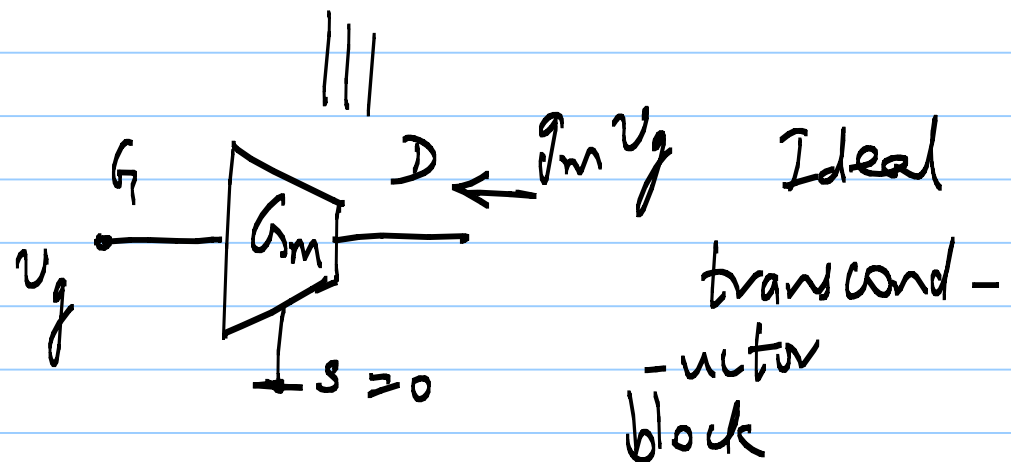

i.e.  $\left(\frac{W}{L}\right) \propto I_D$  can be as large as required

to set  $g_m =$  as large as required.


Ideal VCVS = 1 :  $V_{out} = V_{in}$  ( $g_m \rightarrow \infty$ )

\* measure  $V_{in}$ ,  $V_{out}$ ; compare

\* change  $V_{out}$


\* If  $V_{out} > V_{in}$ , reduce  $i_x$

If  $V_{out} < V_{in}$ , increase  $i_x$

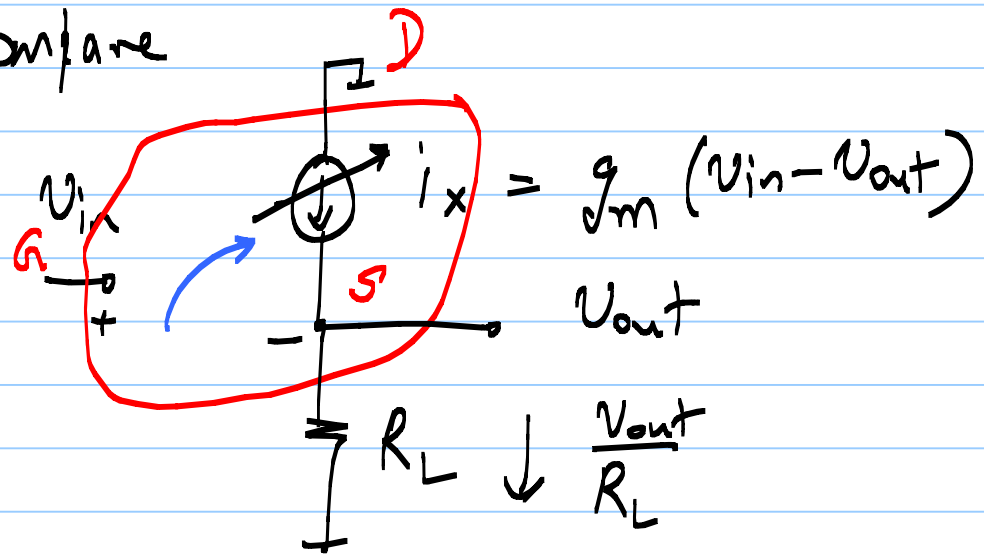


output current  $\frac{V_{out}}{R_L} = g_m(V_{in} - V_{out})$  if in neg. f.b.

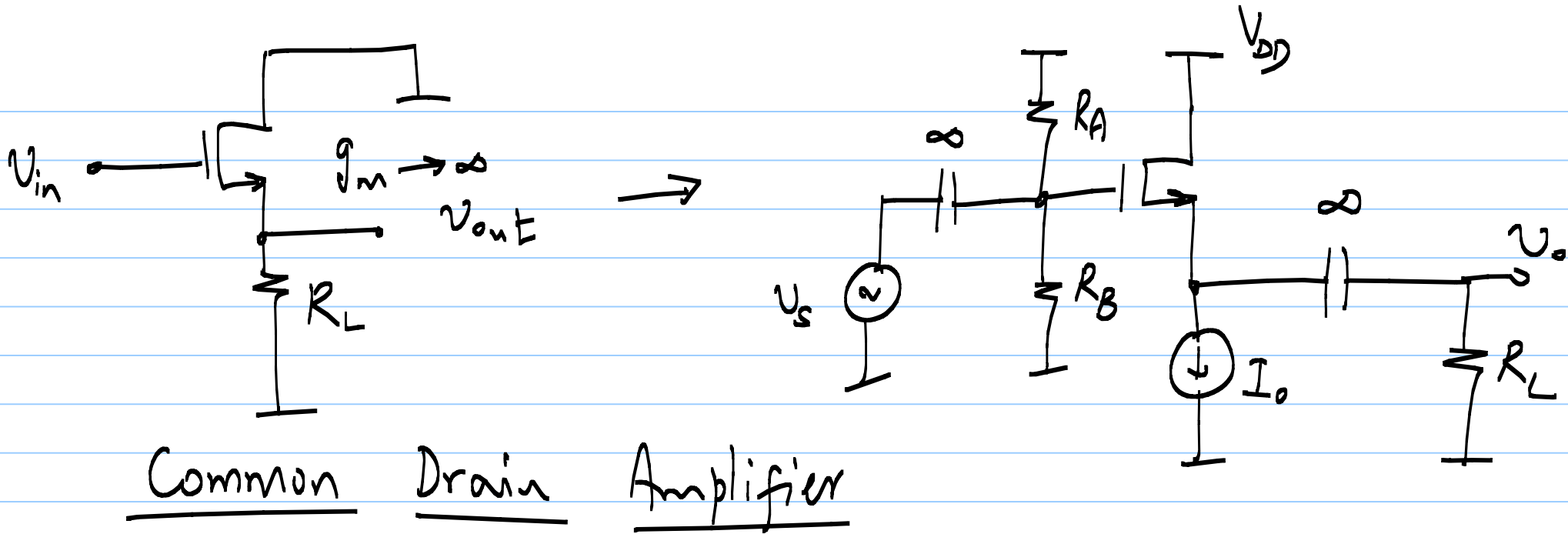we want  $V_{out} = V_{in} \Rightarrow g_m \rightarrow \infty$  so that  $V_{in} - V_{out} \rightarrow 0$





VCVS

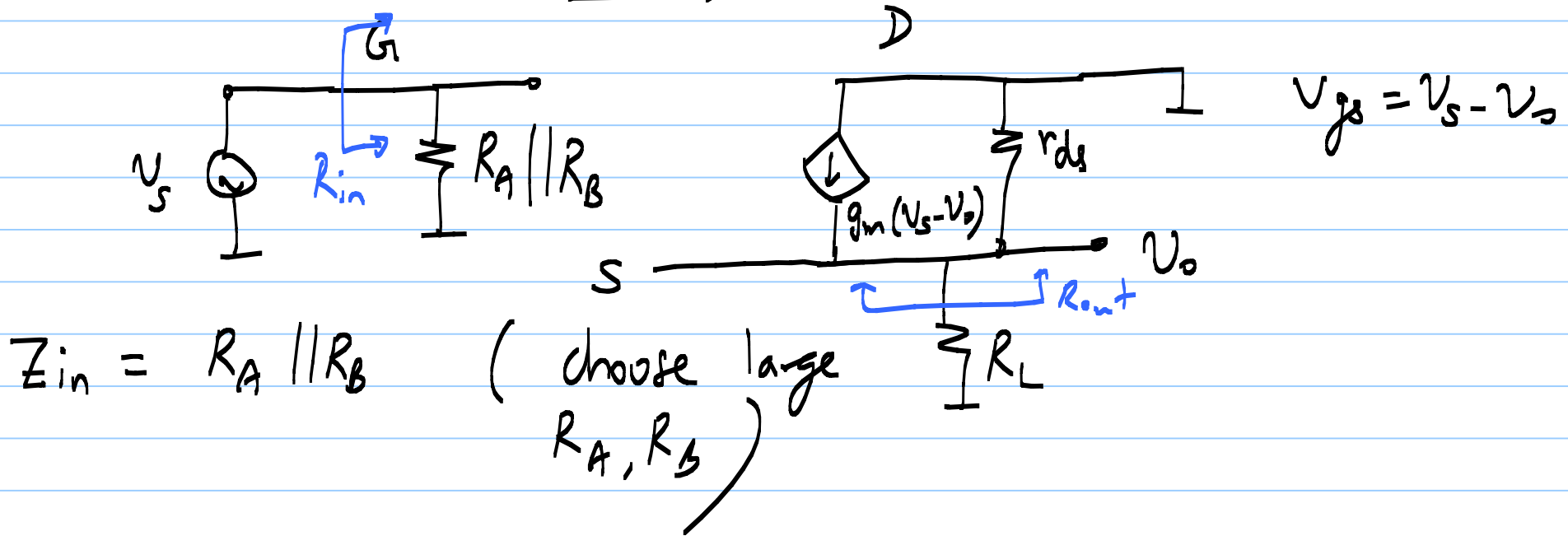

$Z_{in} = R_A \parallel R_B$  (choose large  $R_A, R_B$ )

$Z_{out} = ?$

set  
 $v_s = 0$

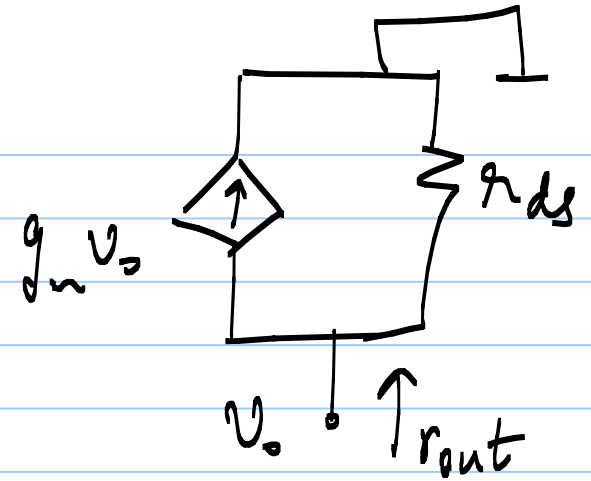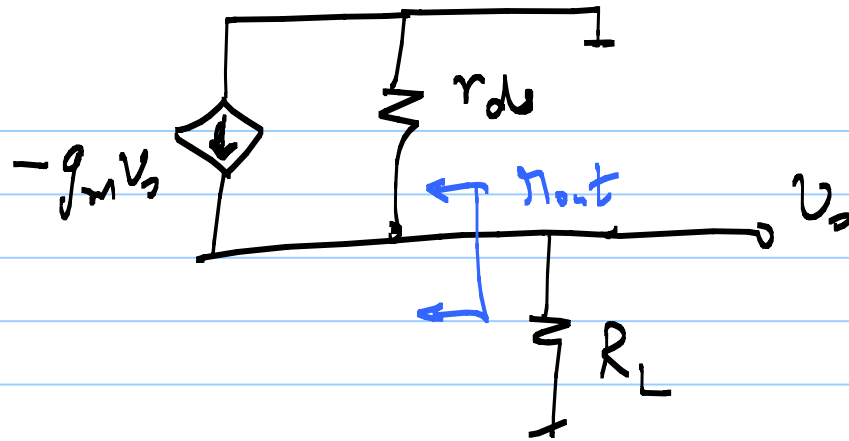

$$r_{out} = \frac{1}{g_m} \parallel r_{ds}$$

$$Z_{out} = \frac{r_{ds}}{1 + g_m r_{ds}} = \frac{1}{g_m} \cdot \frac{g_m r_{ds}}{1 + g_m r_{ds}}$$

$$\text{If } g_m r_{ds} \gg 1, \quad Z_{out} = \frac{1}{g_m}$$

KCL @ S node:

$$g_m (v_s - v_o) = v_o (G_L + g_{ds})$$

$$v_o (g_m + g_{ds} + G_L) = g_m v_s$$

$$\frac{v_o}{v_s} = \frac{g_m}{g_m + g_{ds} + G_L} < 1$$

$$\rightarrow 1 \quad \text{if } g_m \rightarrow \infty$$

$$\hookrightarrow Z_{out} \rightarrow 0$$

