

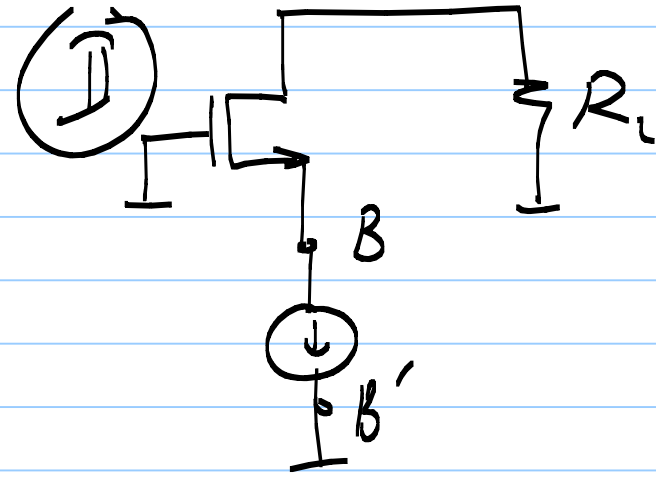
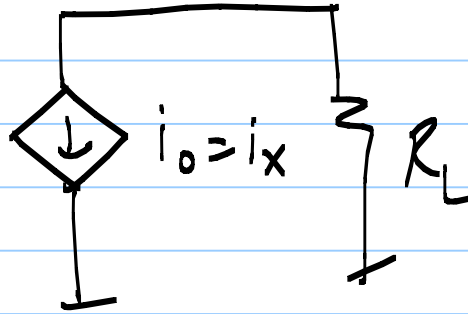


11/9/2020


Lecture 23


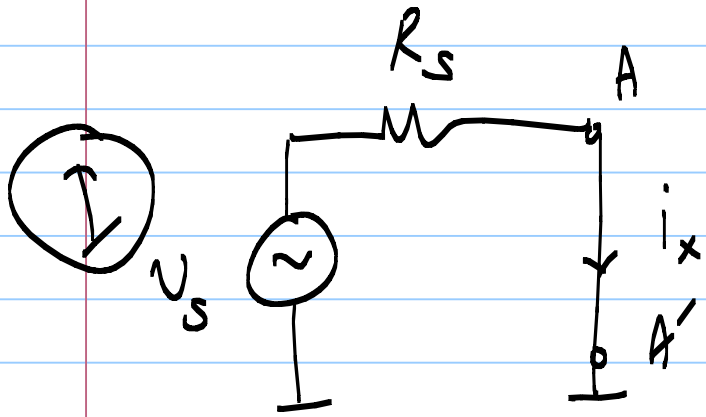




III

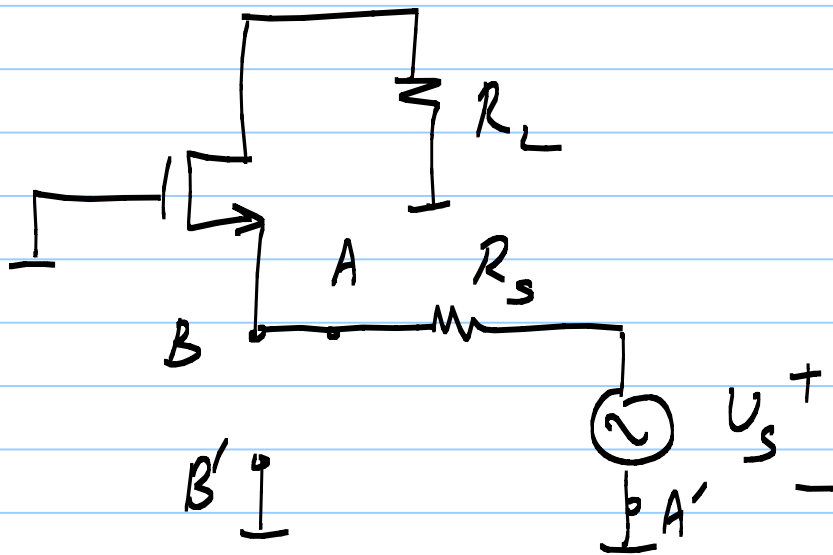

IV

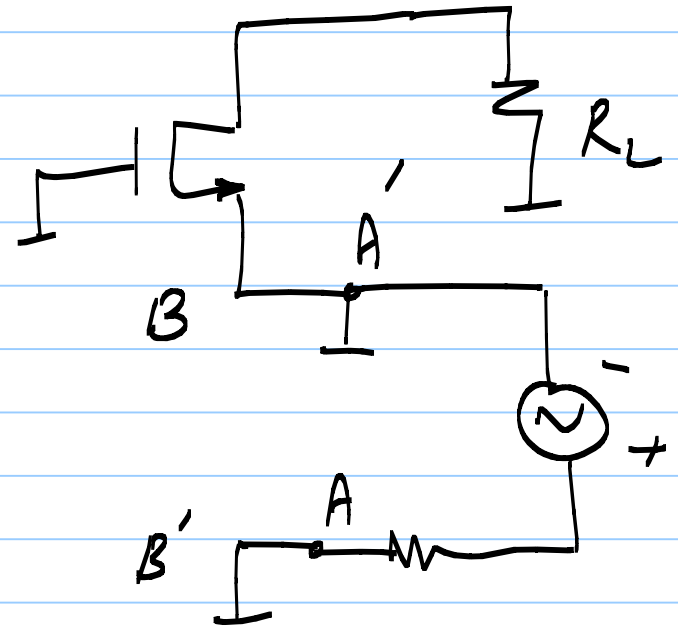

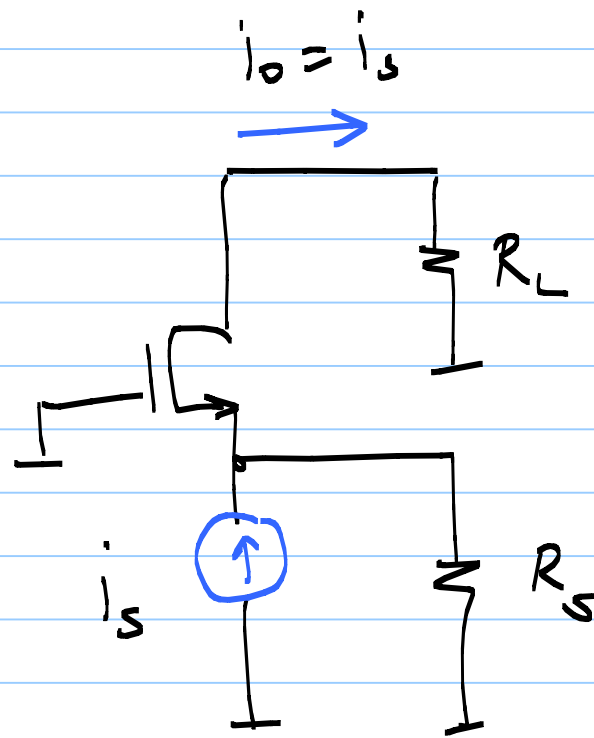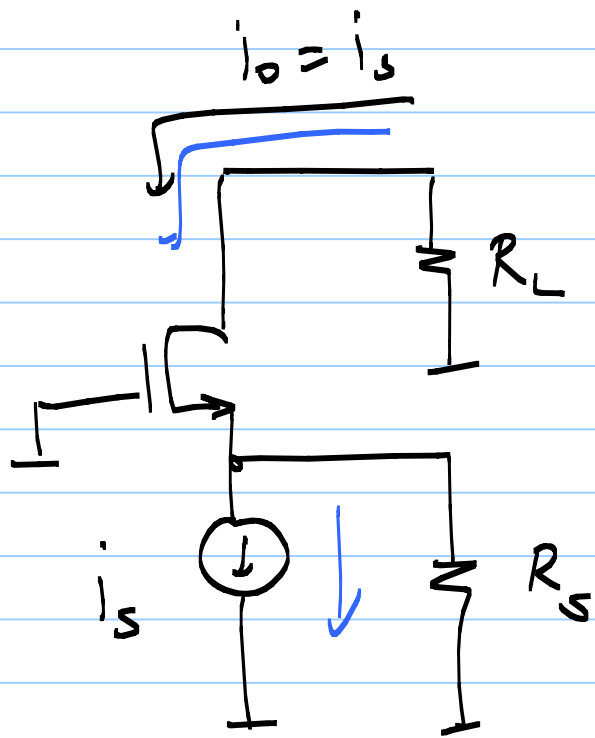


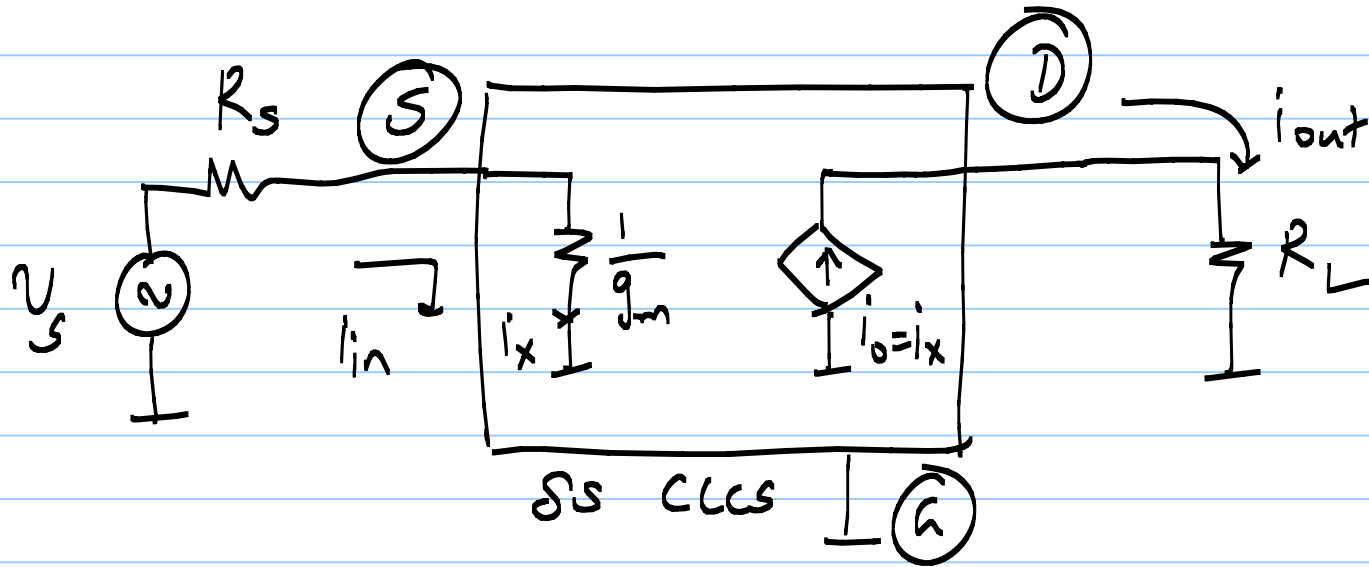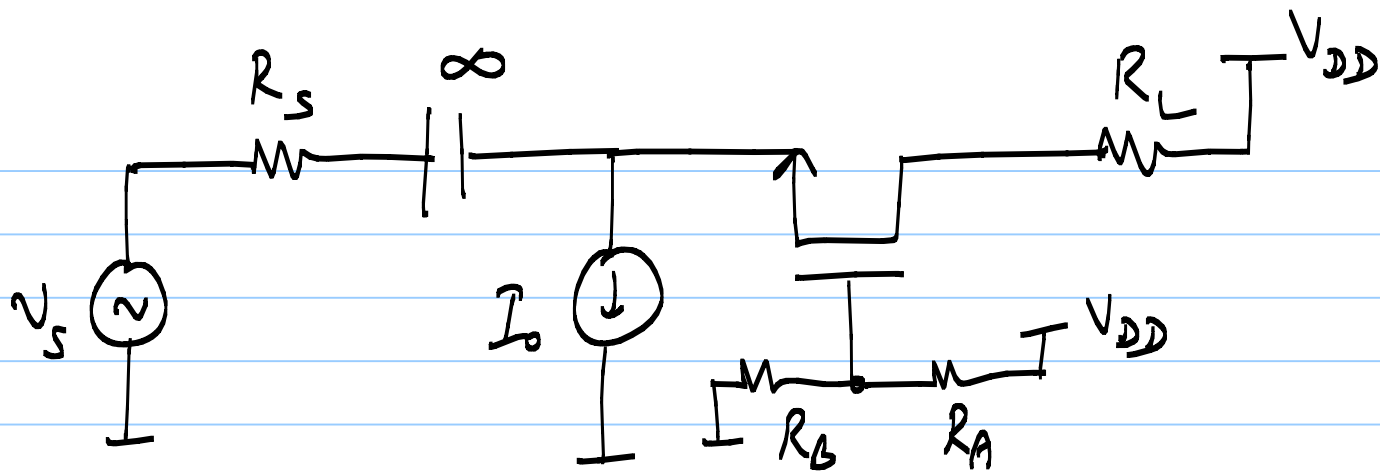

$$i_{in} \approx \frac{v_s}{R_s} \quad \text{if} \quad g_m \gg \frac{1}{R_s}$$

$$\frac{i_{out}}{v_s} = \frac{1}{R_s} \quad ; \quad \frac{v_{out}}{v_s} = \frac{R_L}{R_s}$$

with r_{ds} :

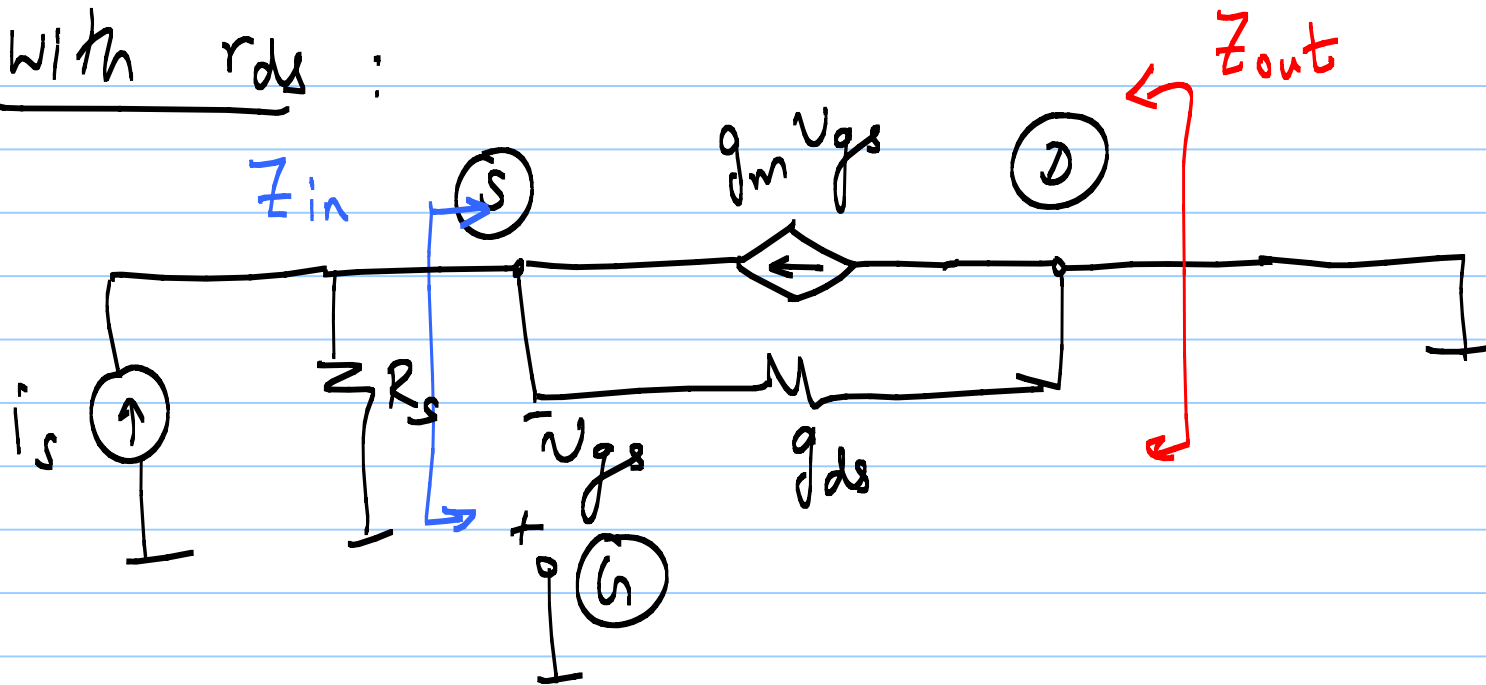


without g_{ds} : $Z_{in} = 1/g_m$

with g_{ds} , without R_L : $Z_{in} = \frac{1}{g_m + g_{ds}}$

with g_{ds} , R_L : HW 8 $Z_{in} = ?$

without g_{ds} : $Z_{out} = \infty$

With g_{ds}
& R_s

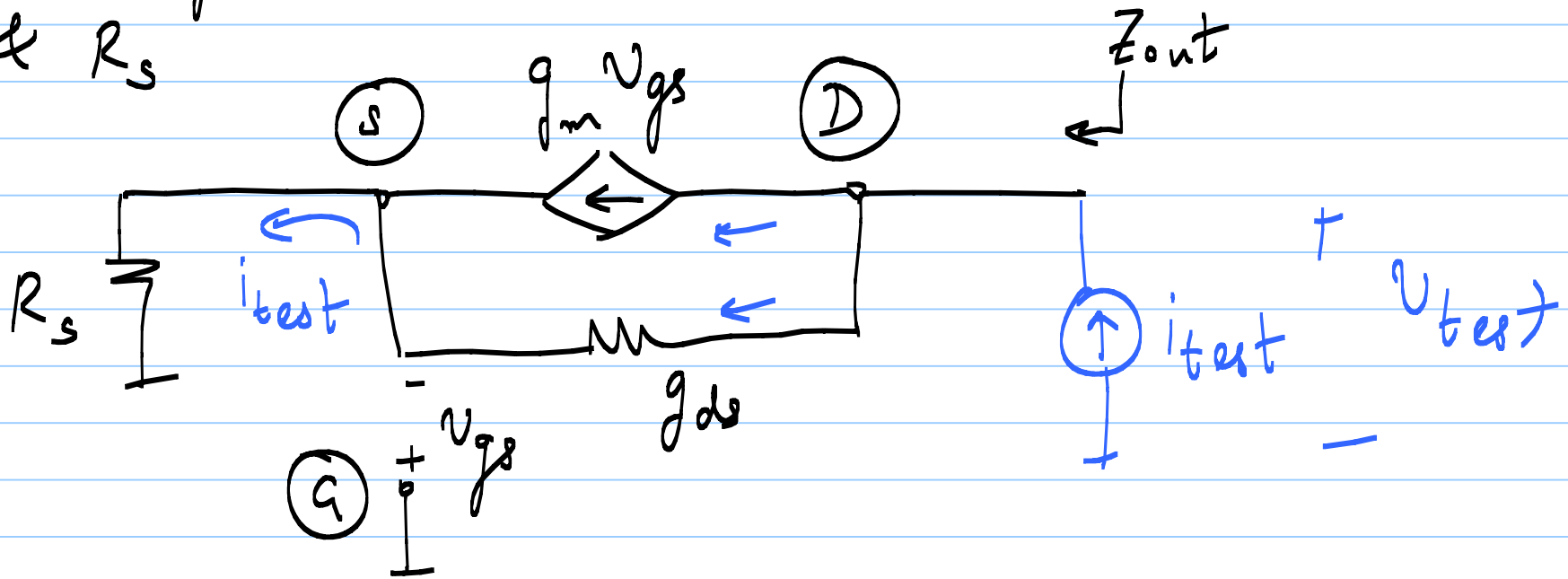


$$Z_{out} = R_s + r_{ds} + g_m r_{ds} R_s$$

$$v_{(S)} = R_s \cdot i_{test} = -v_{gs} \dots$$

HW9 : swing limits for CGA

MOSFET incremental CCVS


Trans-impedance amplifier

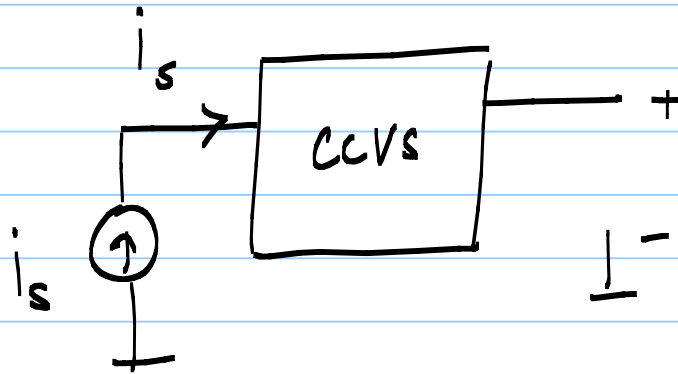



$$v_{out} = R i_s ; \quad Z_{in} = 0$$

$$Z_{out} = 0$$
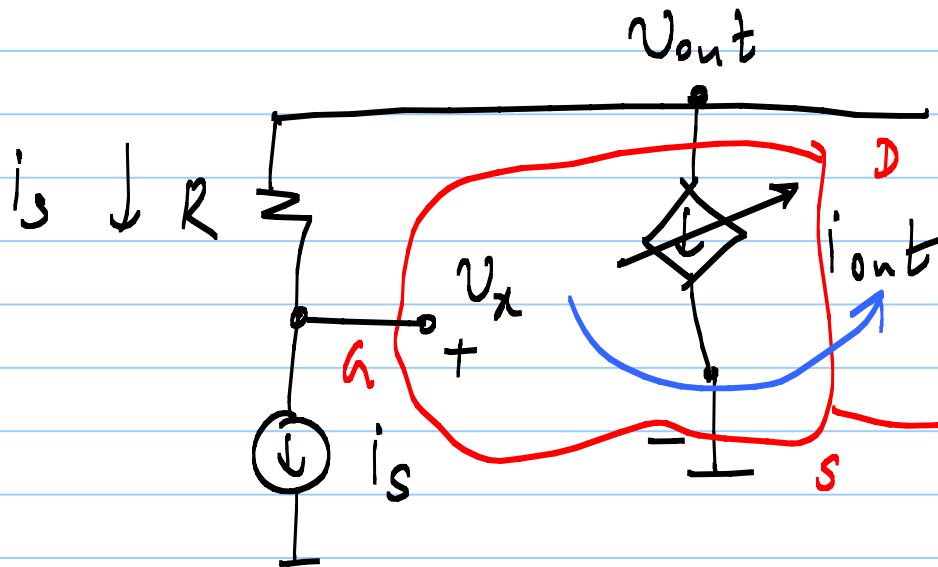
$$v_{out} = R i_s \Rightarrow v_{out} - R i_s = 0 \quad \left(\text{if } g_m \rightarrow \infty \right)$$




$$v_x = v_{out} - R i_s$$

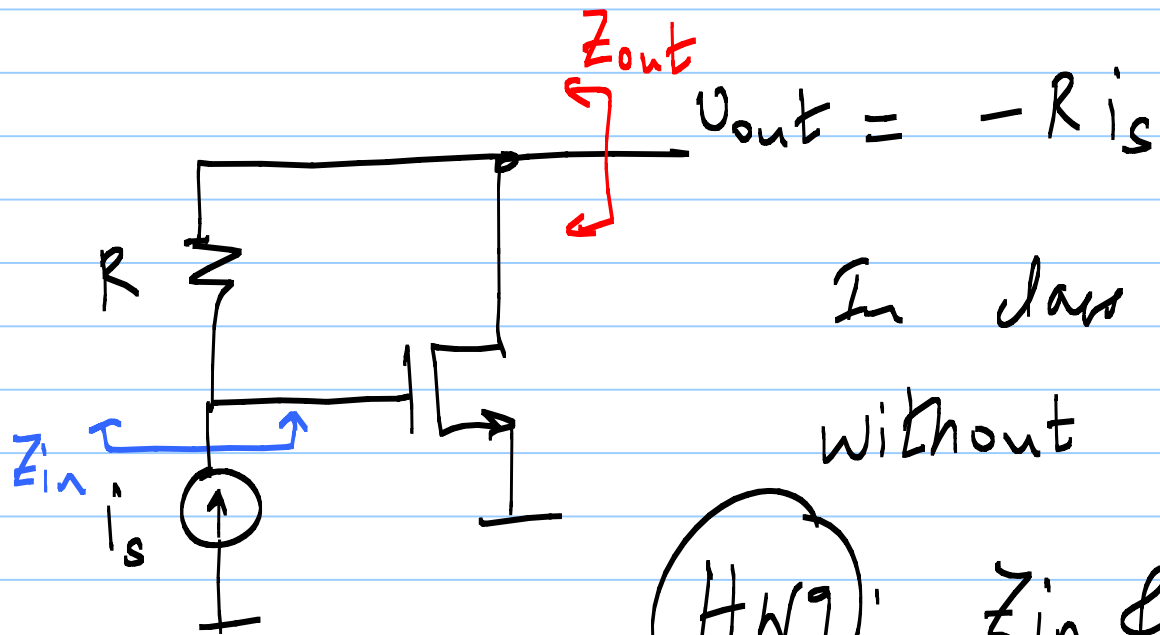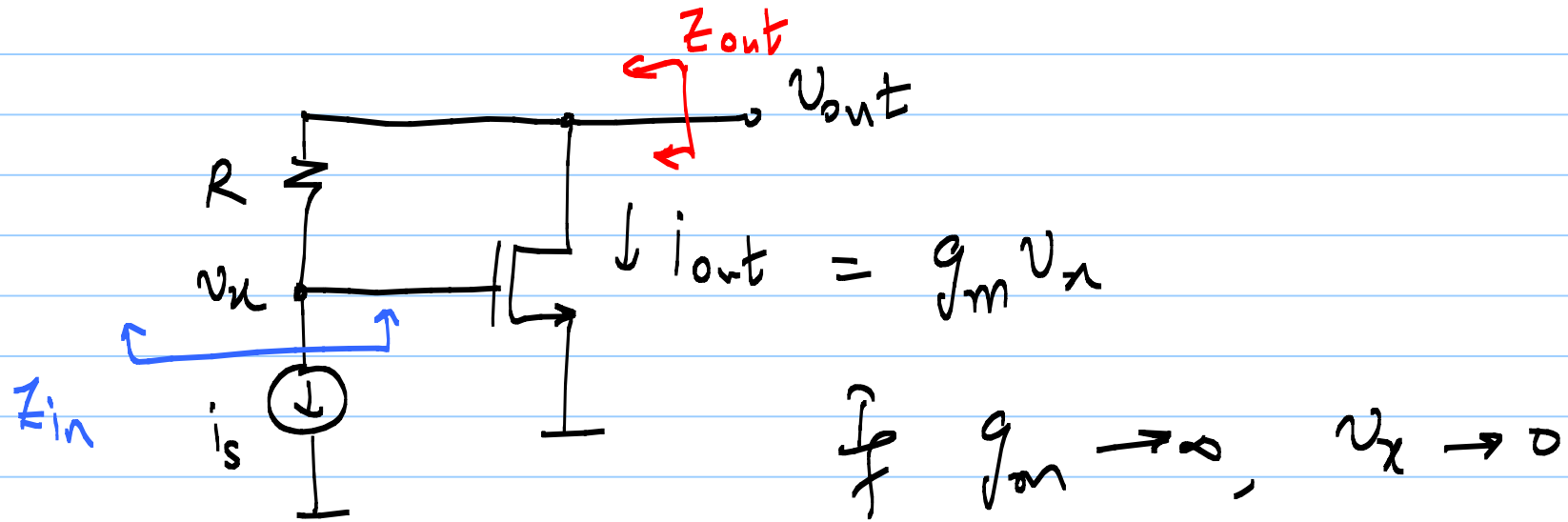



In class: Z_{in} & Z_{out}
 without R_s & R_L

HW9: Z_{in} & Z_{out}
 with R_s & R_L

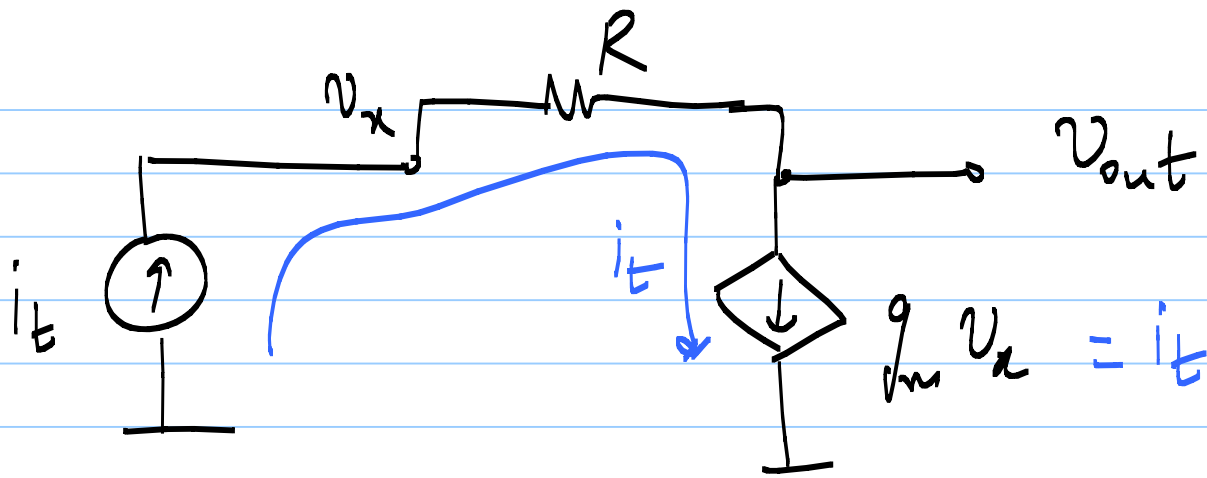
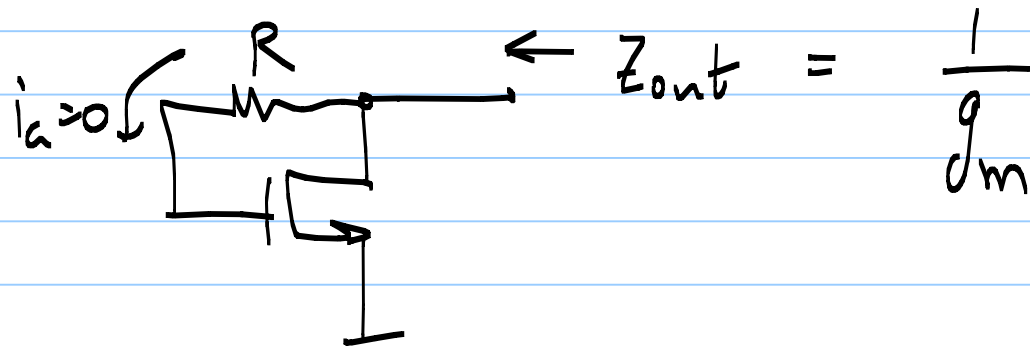
$$i_t = g_m v_x \Rightarrow Z_{in} = \frac{v_x}{i_t} = \frac{1}{g_m}$$



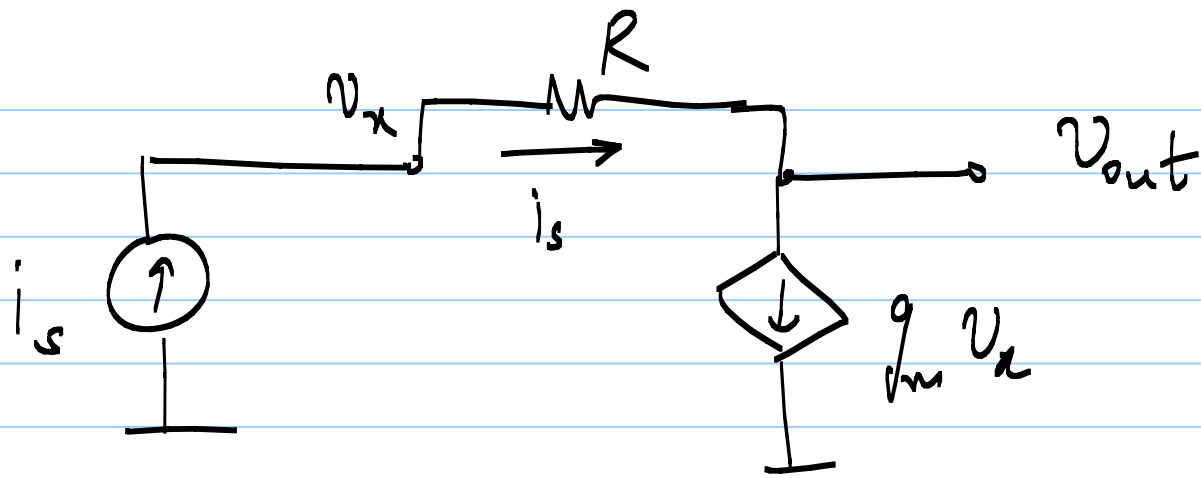

$$i_s = g_m v_x$$



$$v_{out} = v_x - i_s \cdot R$$

$$v_{out} = i_s \left[\frac{1}{g_m} - R \right]$$

$$\frac{v_{out}}{i_s} = \left[\frac{1}{g_m} - R \right] = -R \left[1 - \frac{1}{g_m R} \right]$$

$$\text{If } g_m R \rightarrow \infty, \quad \frac{v_{out}}{i_s} \rightarrow -R$$
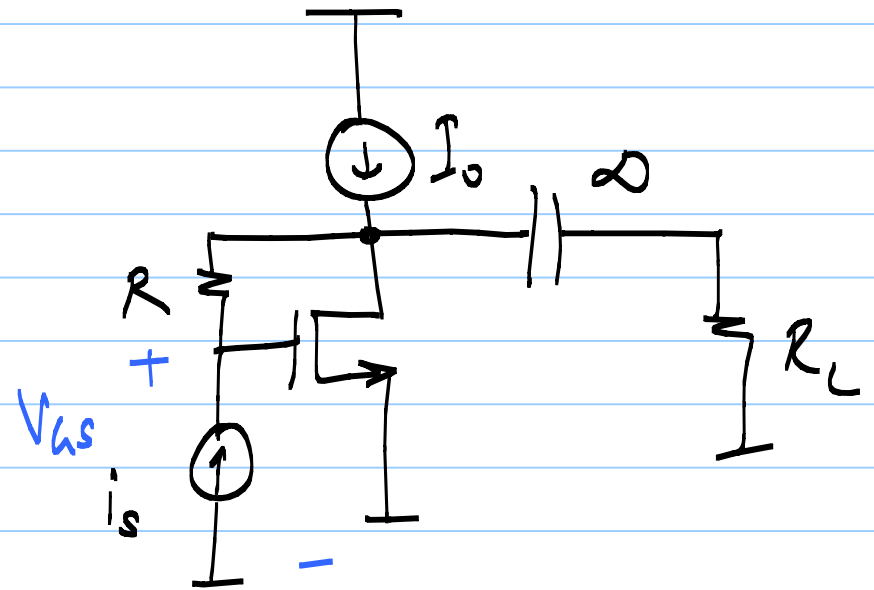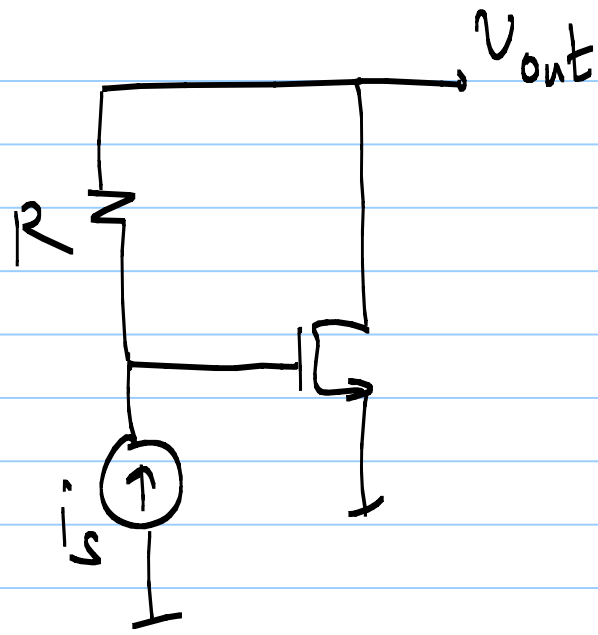
$$\text{large } g_m \Rightarrow g_m R \gg 1 \quad (\text{or}) \quad \boxed{g_m \gg \frac{1}{R}}$$



with biasing