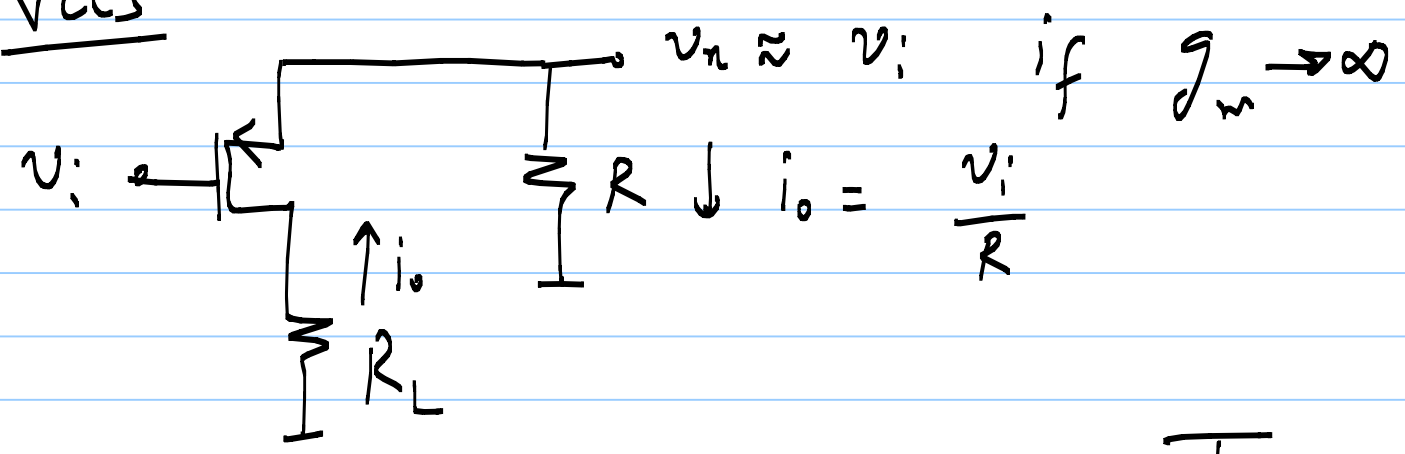


17/9/2020


Lecture 26

PMOS based controlled sources




2) VCCS



PMOS
Transadmittance
amplifier

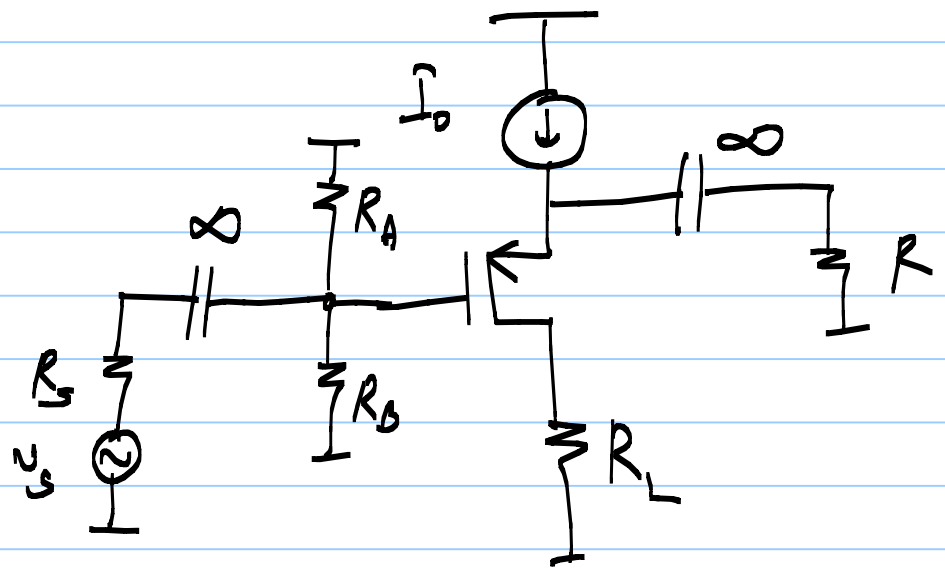


3) CCCS - Common Gate Amplifier

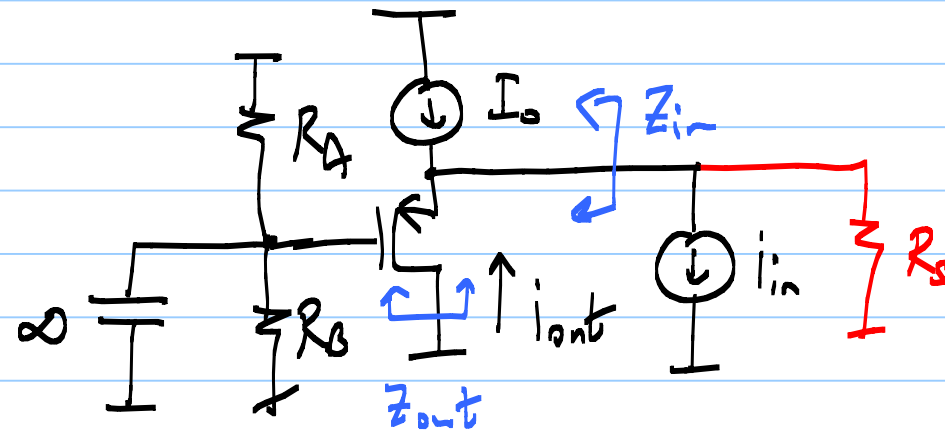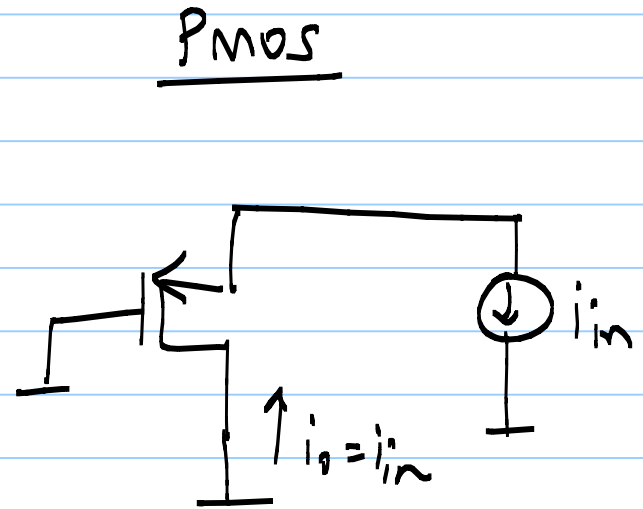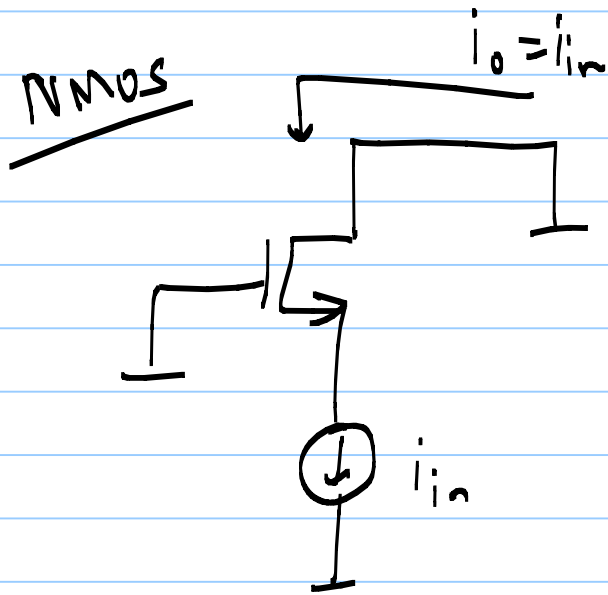

$$Z_{in} = \frac{1}{g_m + g_{ds}} \approx \frac{1}{g_m}$$


$$Z_{out} = \infty$$

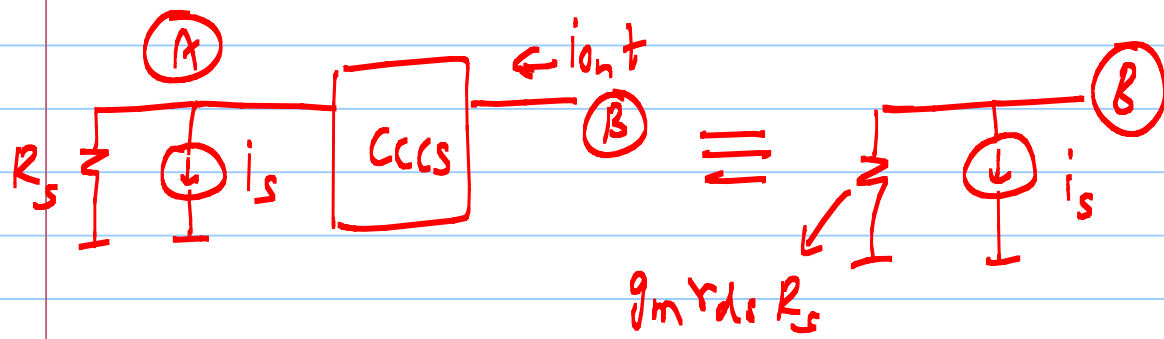

$$Z_{out} = R_S + r_{ds} +$$


$$g_m r_{ds} R_S \approx g_m r_{ds} R_S$$

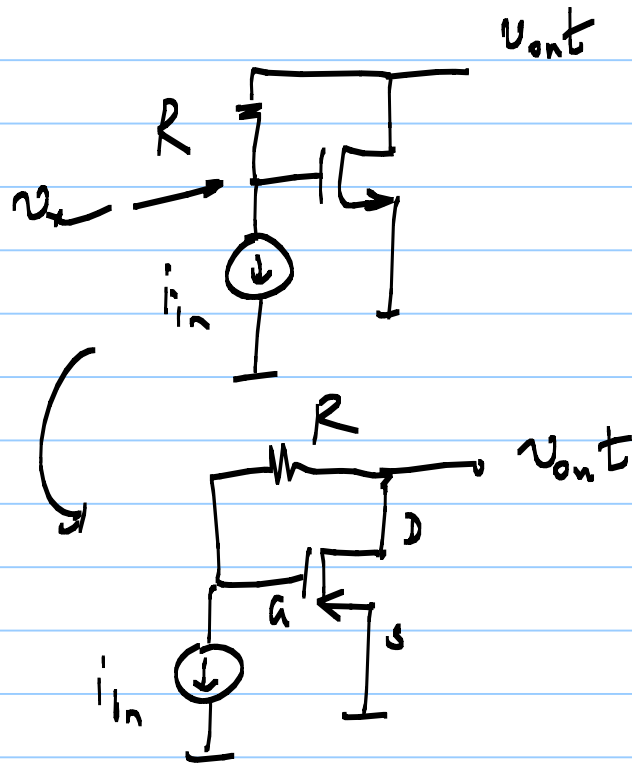
4) CCVS (Transimpedance amplifier) $v_{out} = R \cdot i_{in}$



$$v_{gs} = v_{out} - i_{in} \cdot R$$
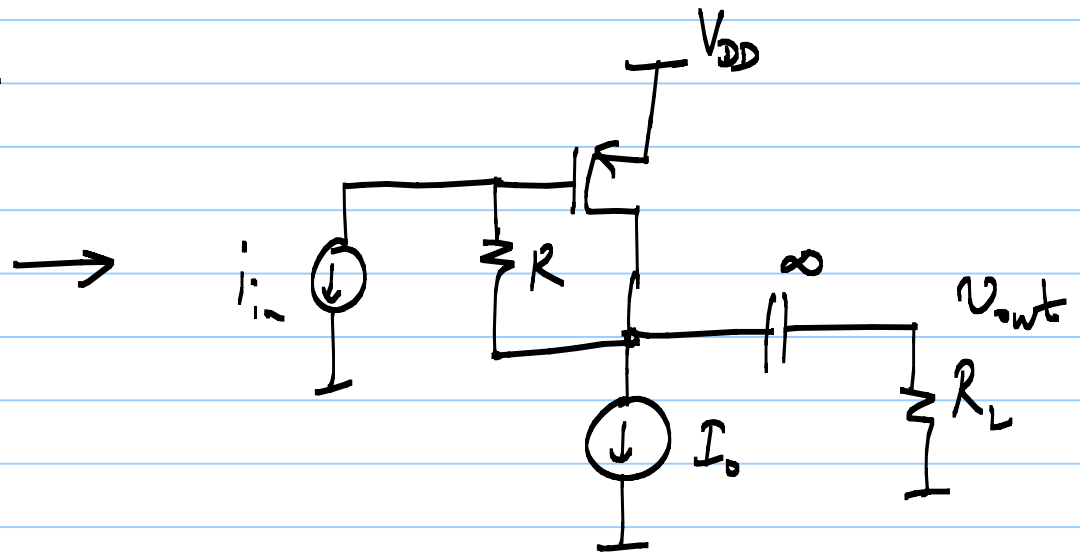
$$\text{as } g_m \rightarrow \infty, \quad v_{gs} \rightarrow 0$$






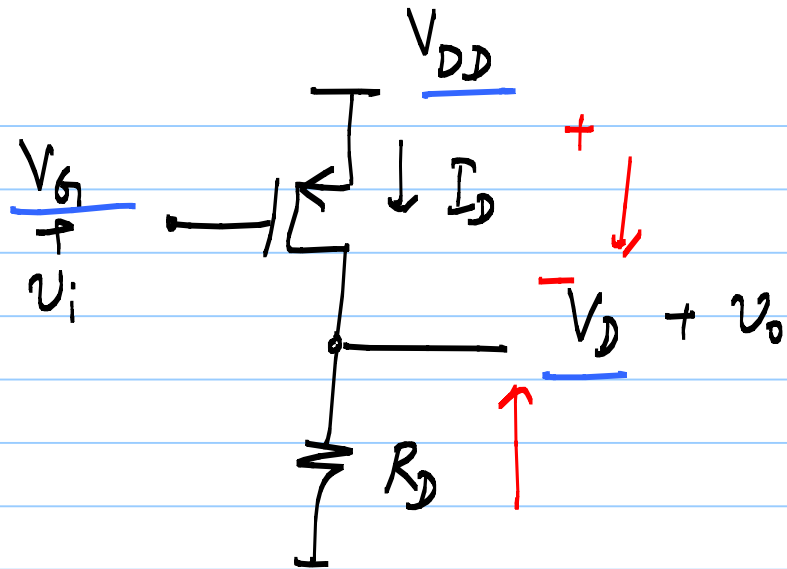



$$\frac{v_o}{v_i} = -g_m R_D$$

$$V_D = I_D R_D$$




$$V_{SD} = V_{DD} - V_D$$

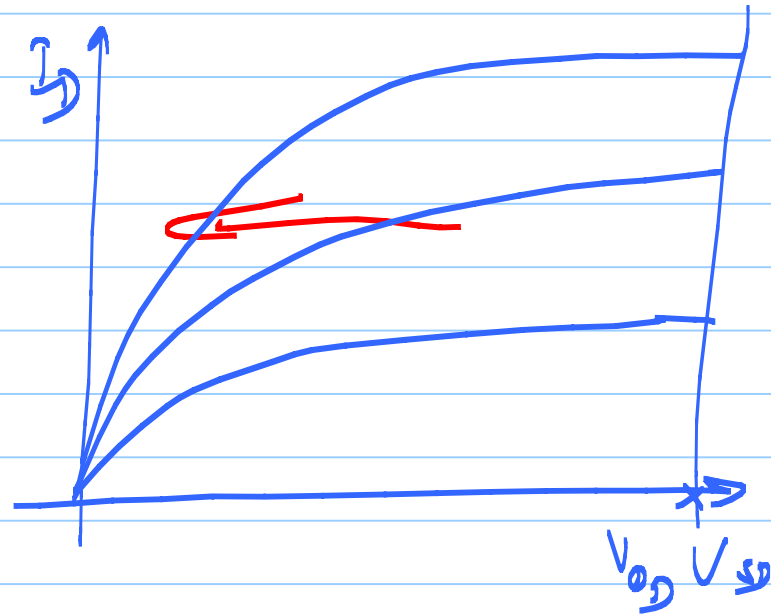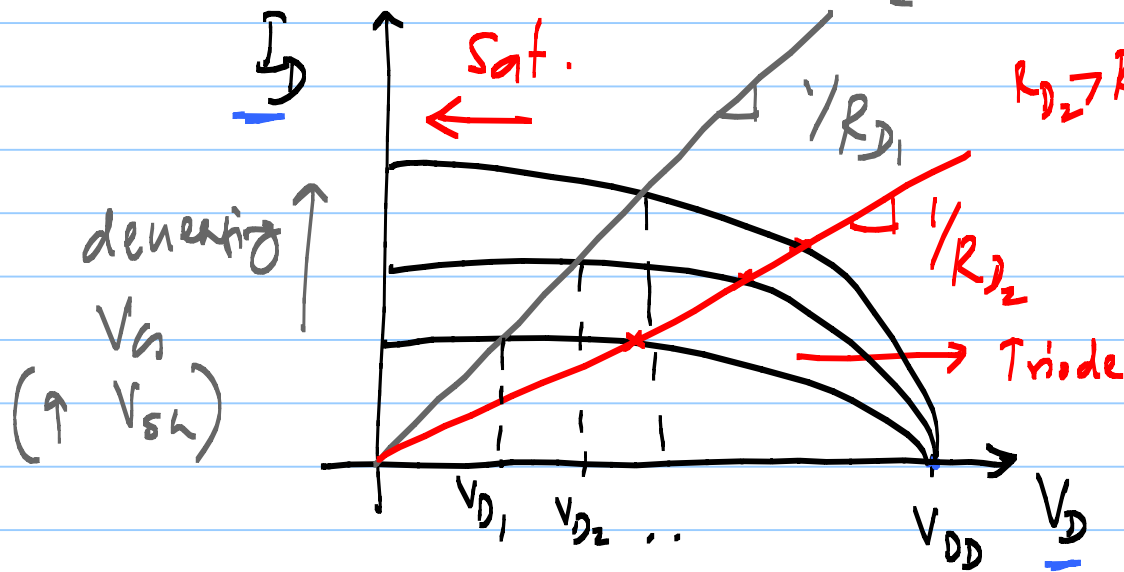

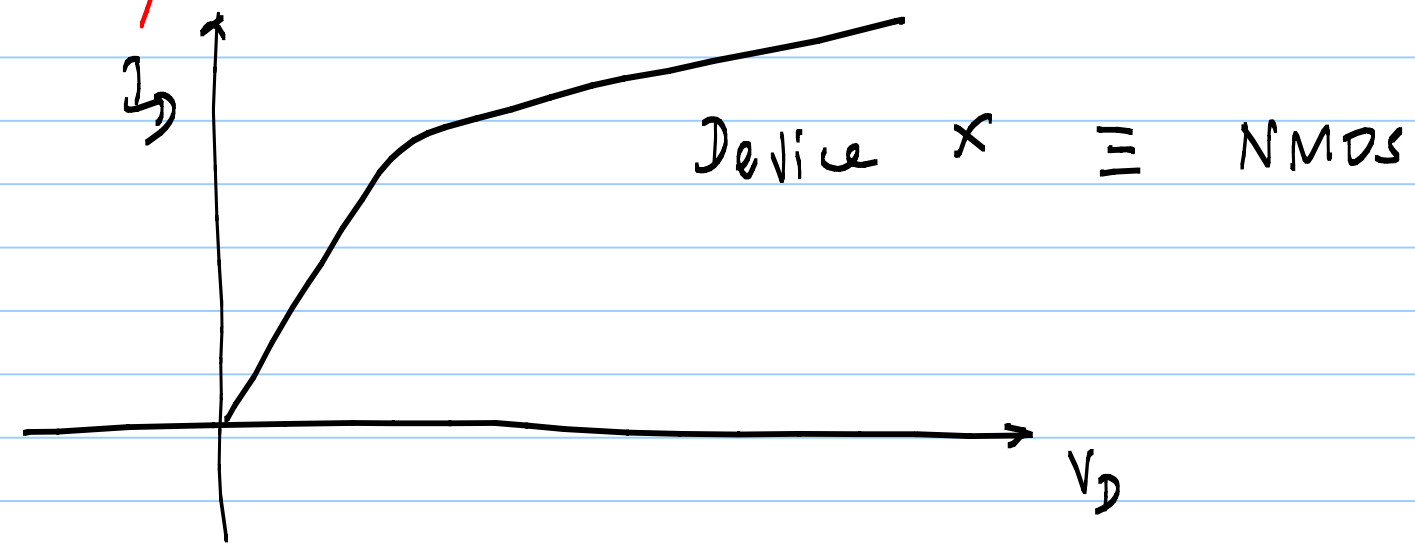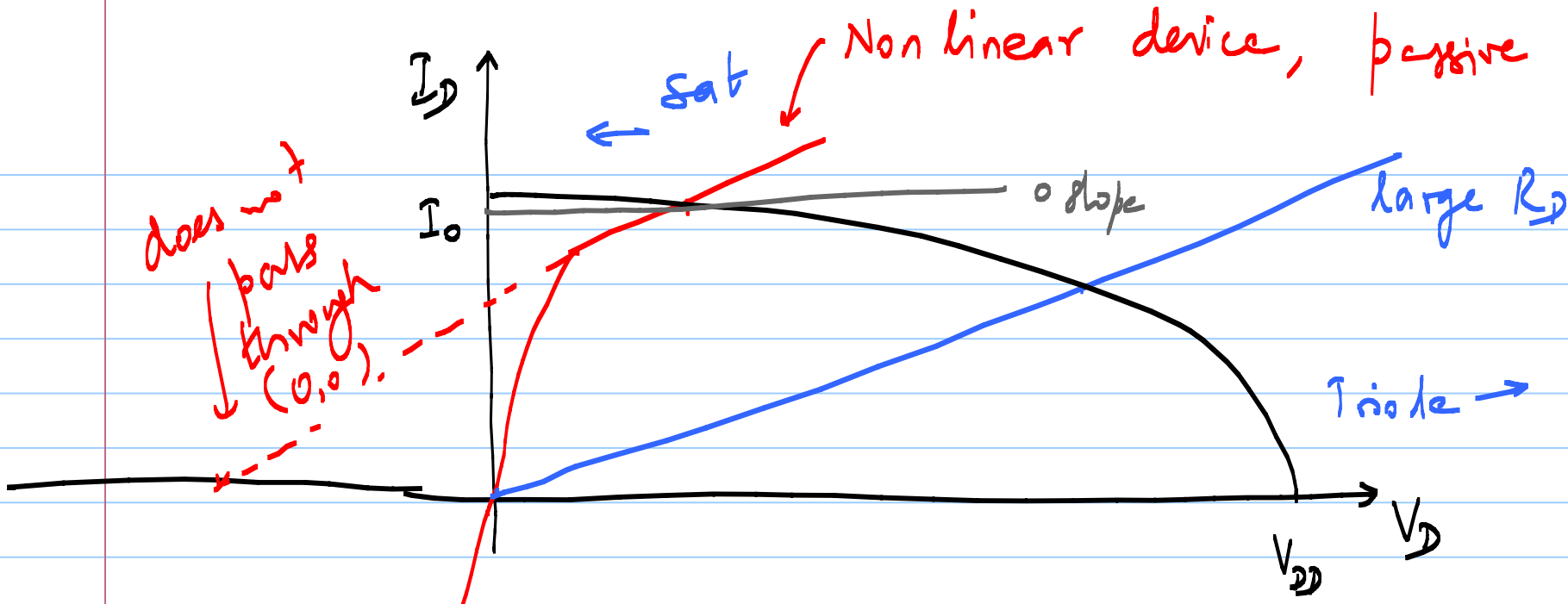

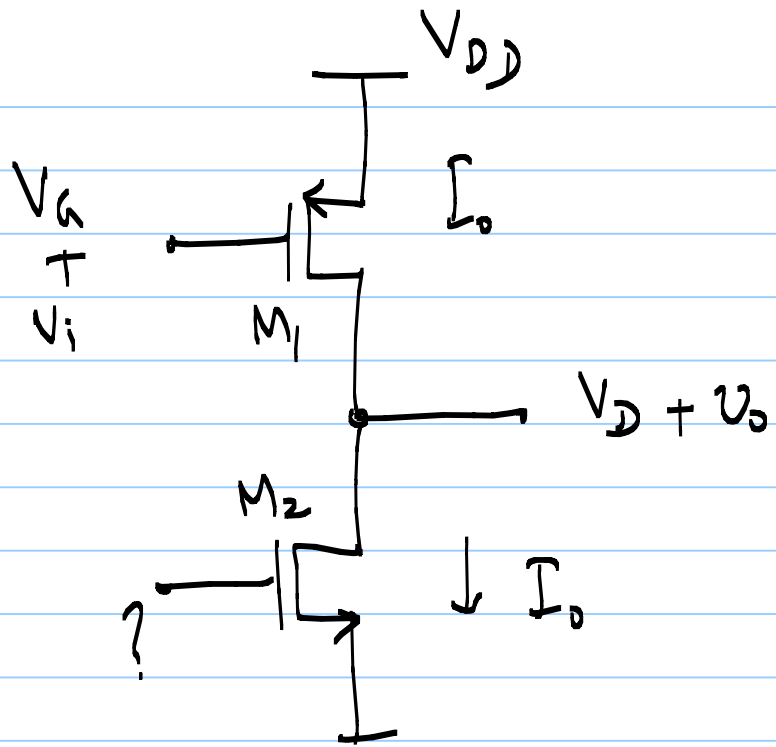

|||

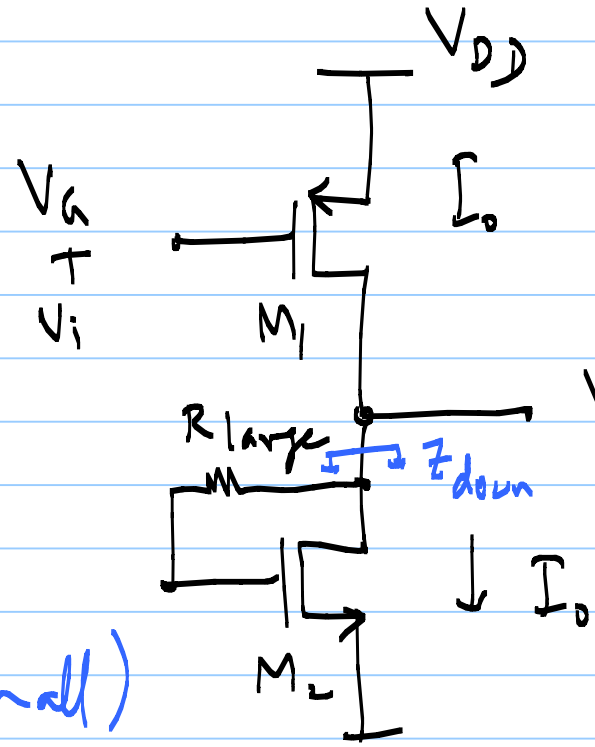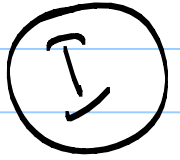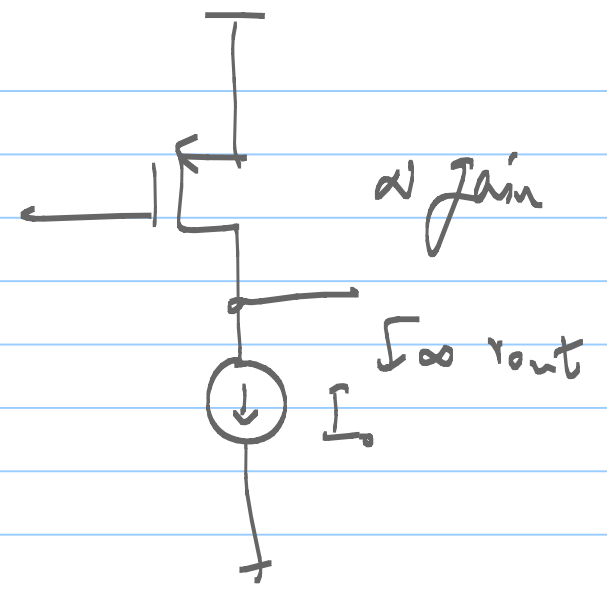

$V_{SG2} = V_{DD} - V_L$
 \rightarrow decides I_o

$$Z_{down} = \frac{1}{g_{m2}}$$

$$gain = -\frac{g_{m1}}{g_{m2}} \text{ (small)}$$

$$V_D = V_{G2} | I_o$$