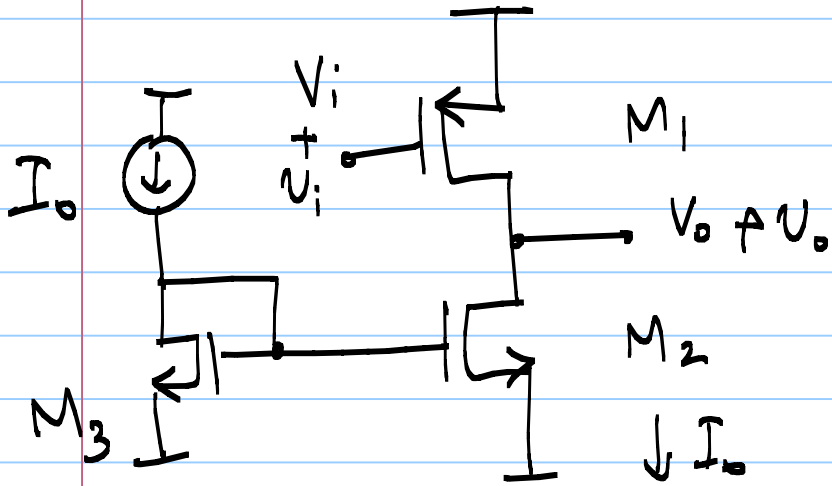



22/9/2020


Lecture 28




$$\frac{v_o}{v_i} = -g_{m1} (r_{ds1} \parallel r_{ds2})$$




$$= \frac{-g_{m1}}{g_{ds1} + g_{ds2}}$$

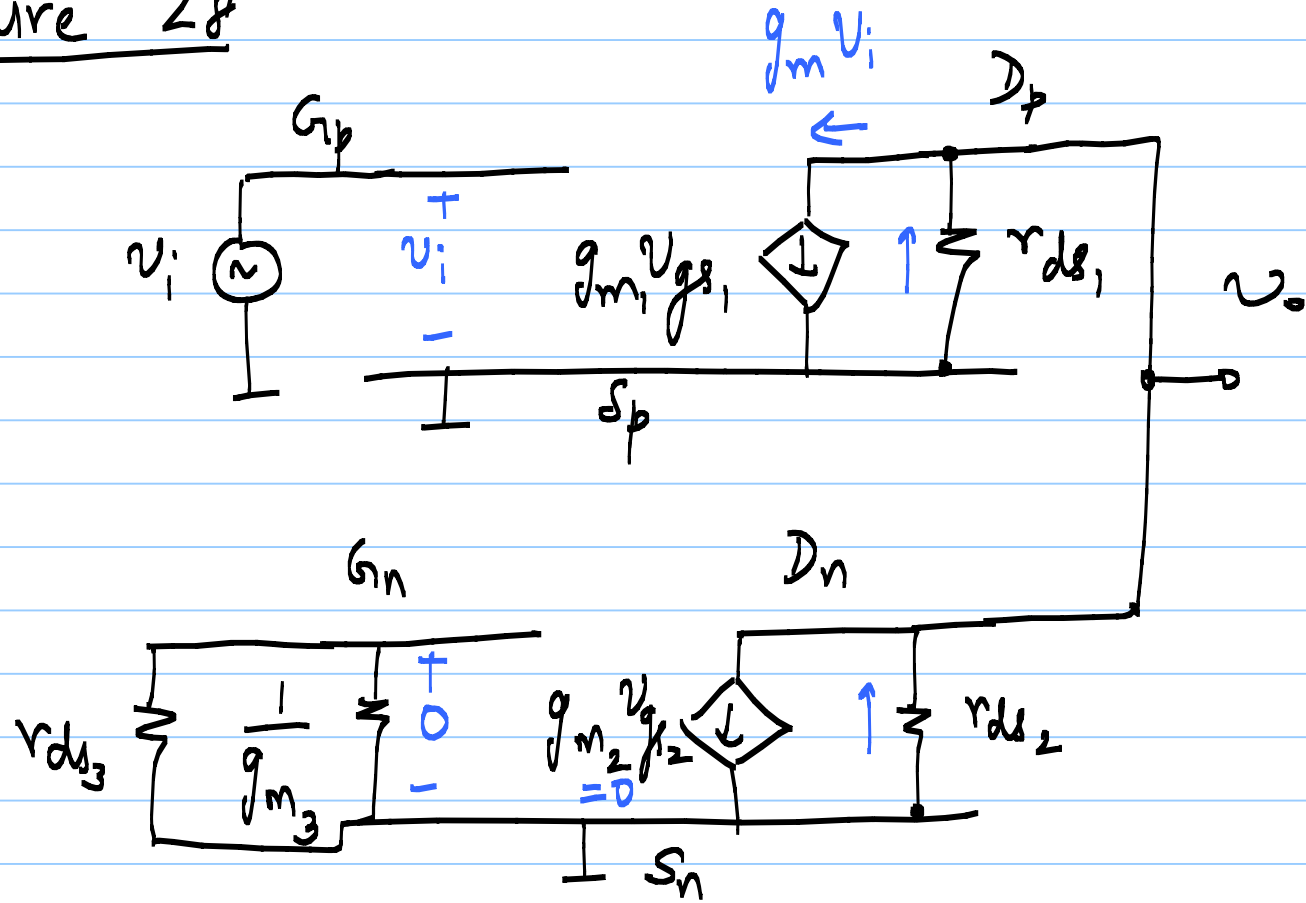

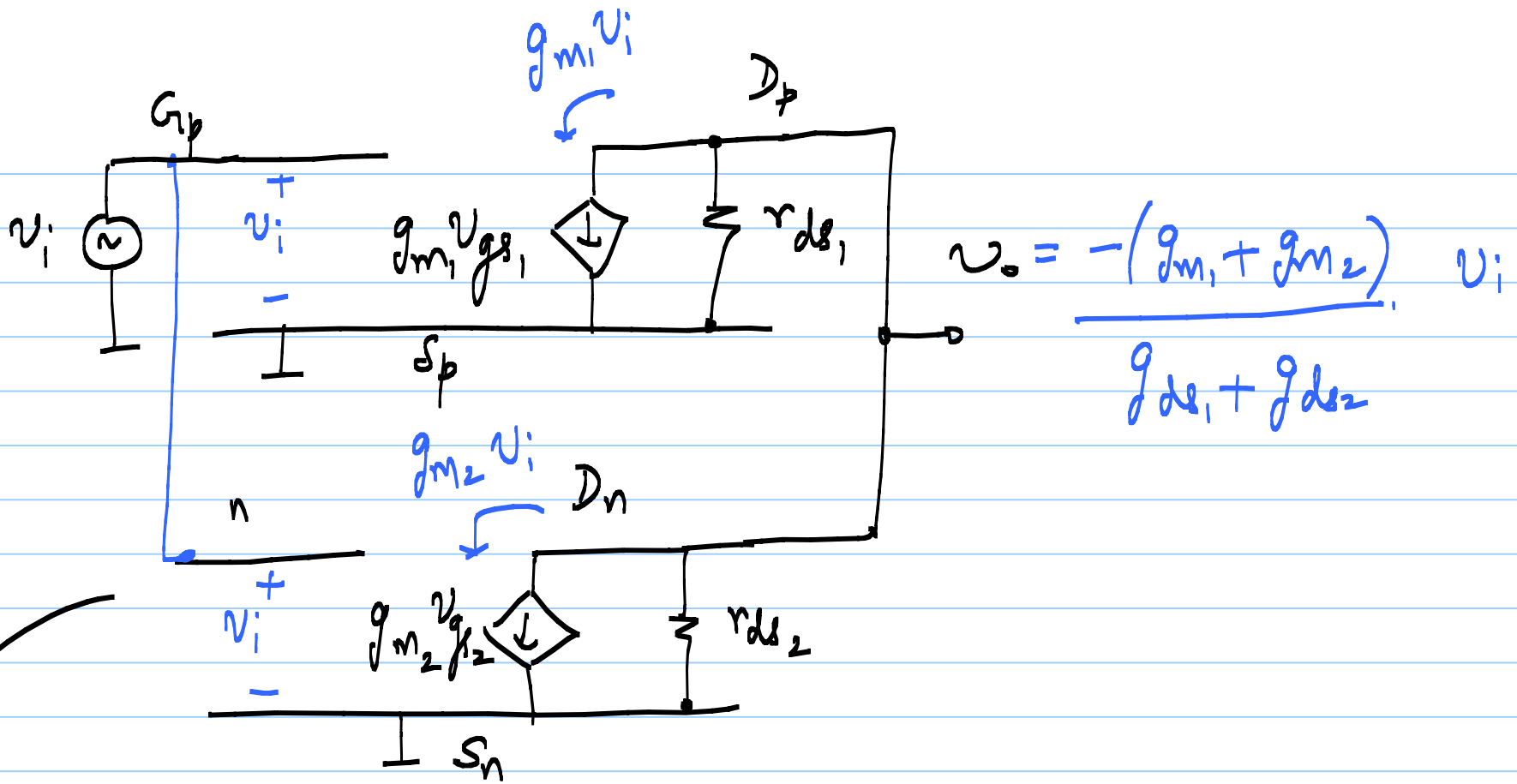

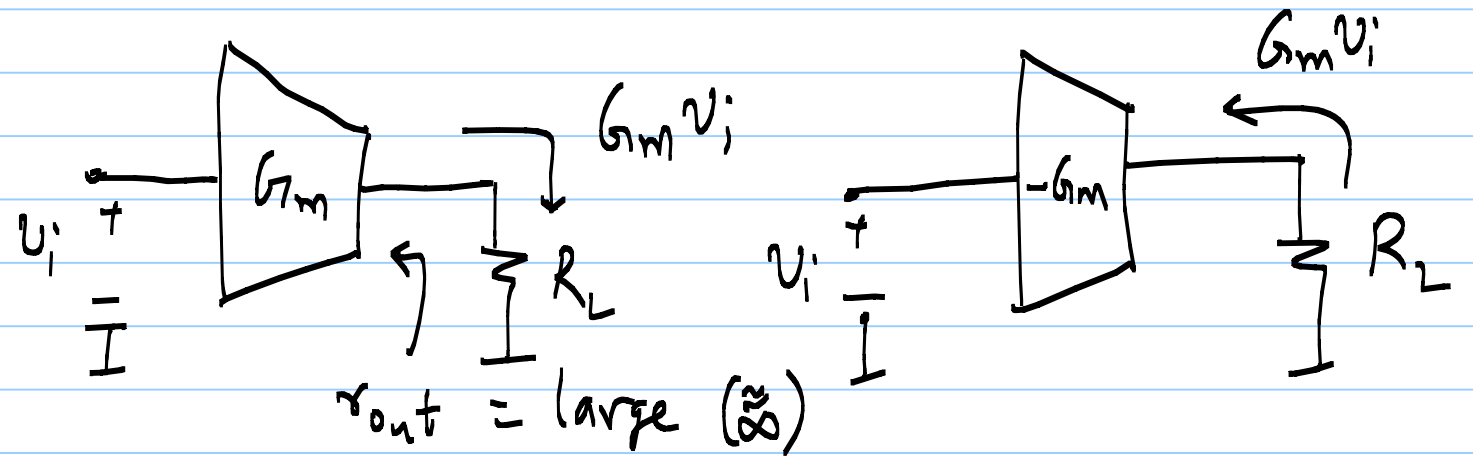\hat{I}_f r_{ds1} & r_{ds2} were ∞ , gain = ∞



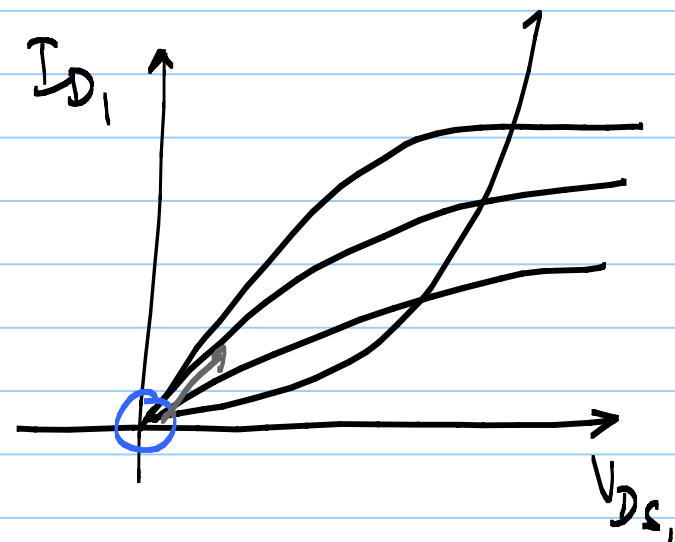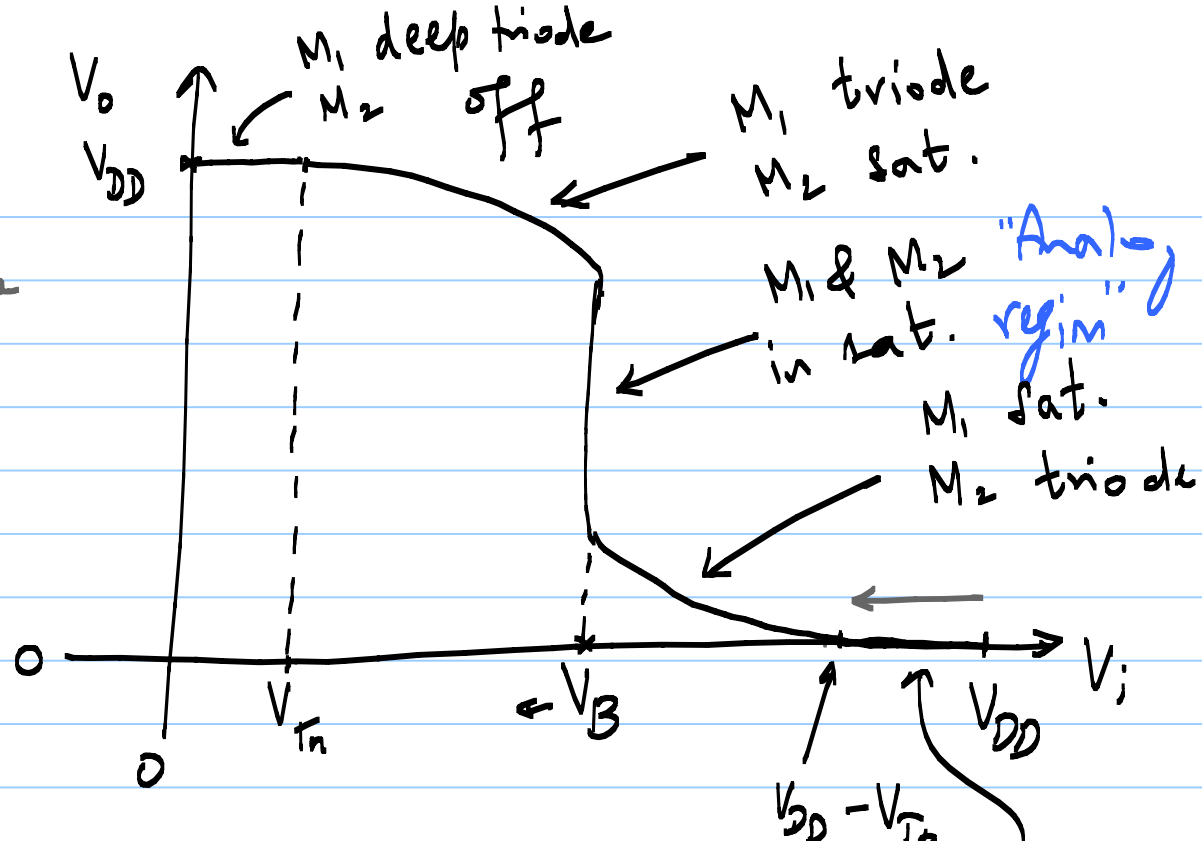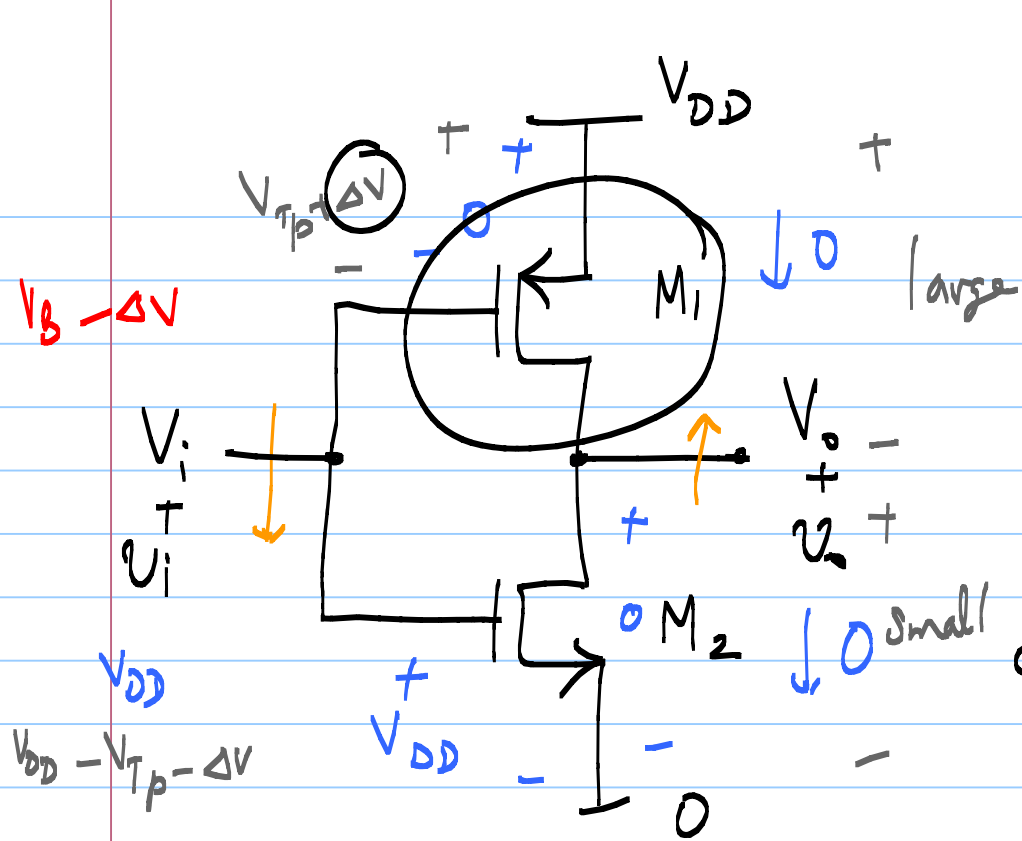

assume $r_{ds} = \infty$

"CMOS Inverter"

M1 off
M2 deep triode

$$V_i = V_{DD} - V_{TP} - \Delta V \quad \therefore I_{D1}(\text{sat.}) = I_{D2}(\text{triode})$$

Determine V_B :

$$I_{D_1}(\text{sat}) = I_{D_2}(\text{sat})$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_p [V_{DD} - V_B - V_{Tp}]^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_n [V_B - V_{Tn}]^2$$


$$K_n = \mu_n \left(\frac{W}{L}\right)_n ; K_p = \mu_p \left(\frac{W}{L}\right)_p$$

$$V_B - V_{Tn} = \sqrt{\frac{K_p}{K_n}} \cdot (V_{DD} - V_B - V_{Tp})$$

$$V_B \left[1 + \sqrt{\frac{K_p}{K_n}} \right] = V_{Tn} + (V_{DD} - V_{Tp}) \left[\sqrt{\frac{K_p}{K_n}} \right]$$

$$V_B = \frac{V_{Tn} + (V_{DD} - V_{Tp}) \left[\sqrt{\frac{k_p}{k_n}} \right]}{1 + \sqrt{\frac{k_p}{k_n}}}$$

* $\mu_n \approx 3 \mu_p$

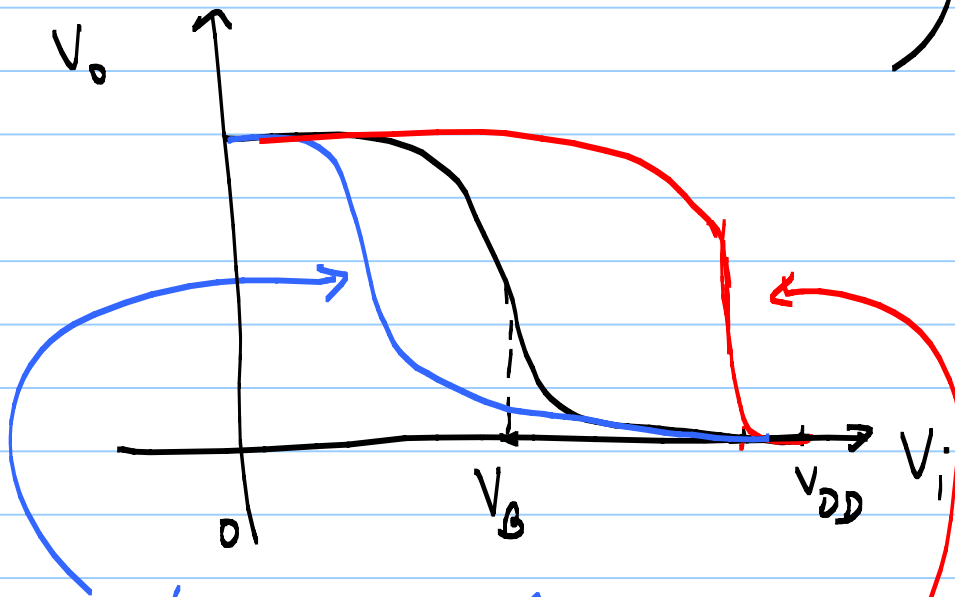

1) $V_{Tn} = V_{Tp} = V_T$

We want $V_B = V_{DD}/2$

$$\Rightarrow k_p = k_n \Rightarrow \left(\frac{W}{L} \right)_p = 3 \left(\frac{W}{L} \right)_n$$

$$\left(\frac{W}{L} \right)_p = \left(\frac{\mu_n}{\mu_p} \right) \left(\frac{W}{L} \right)_n$$

2) $\uparrow \left(\frac{W}{L} \right)_n \Rightarrow \left(\frac{W}{L} \right)_p$

$V_B \approx V_{Tn}$

3) $\uparrow \left(\frac{W}{L} \right)_p \Rightarrow \left(\frac{W}{L} \right)_n$

$V_B \approx V_{DD} - V_{Tp}$