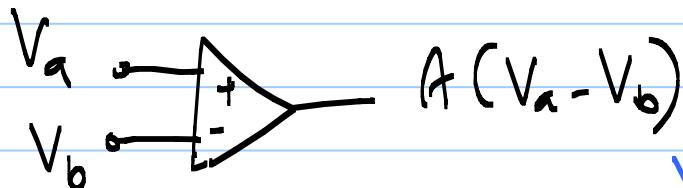



29 | 1 | 20

Lecture 32




$$V_{CM} = \frac{V_a + V_b}{2}$$


$$\Delta V = V_a - V_b$$

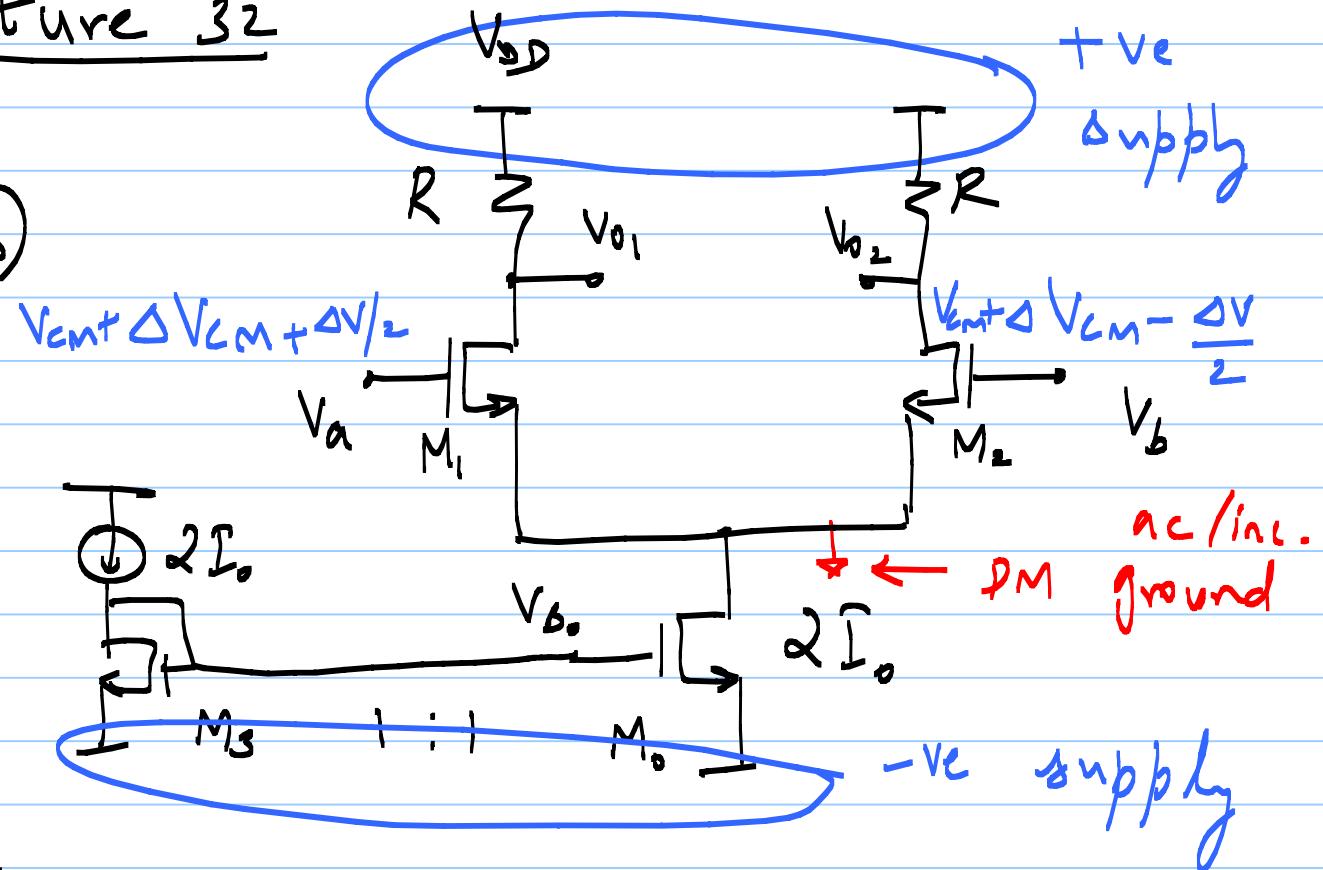


DM eq. circuit

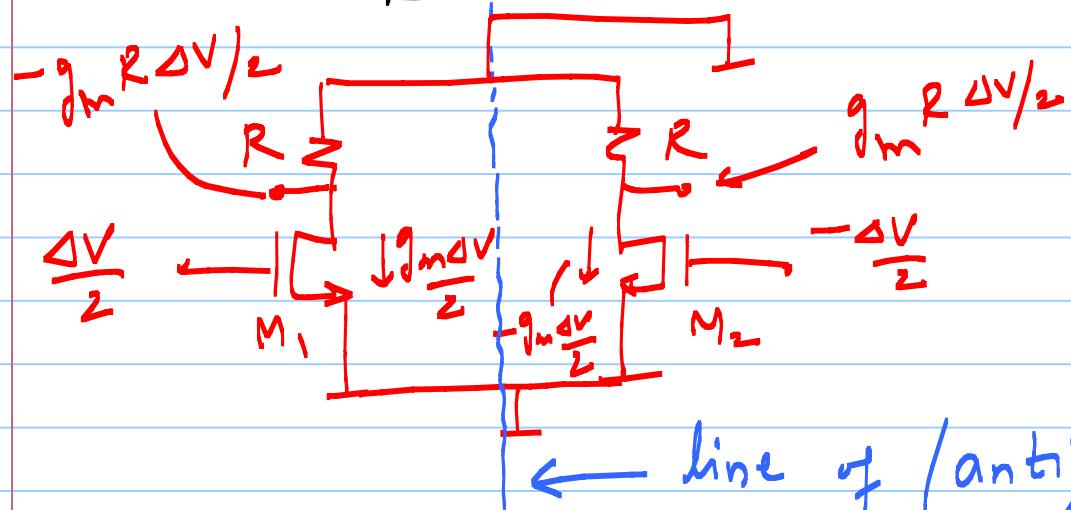

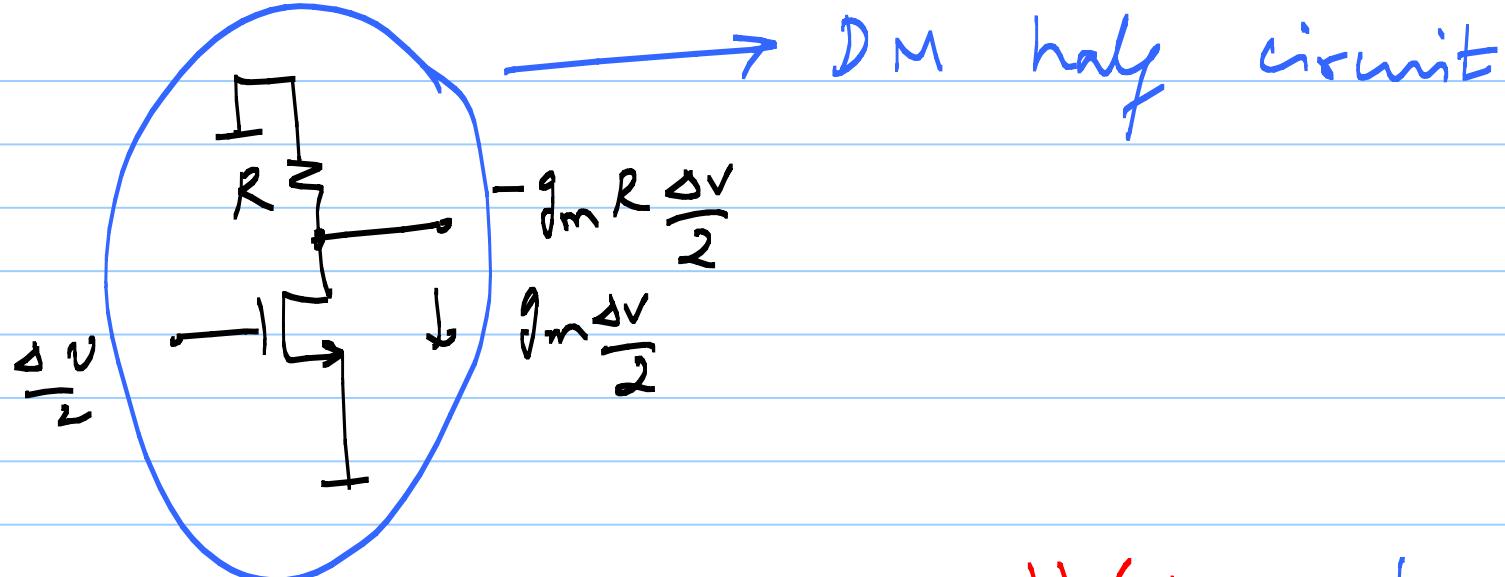
"V's and i's on each
"half-circuit" have
equal magnitude & opposite
phase




CM eq. cir.

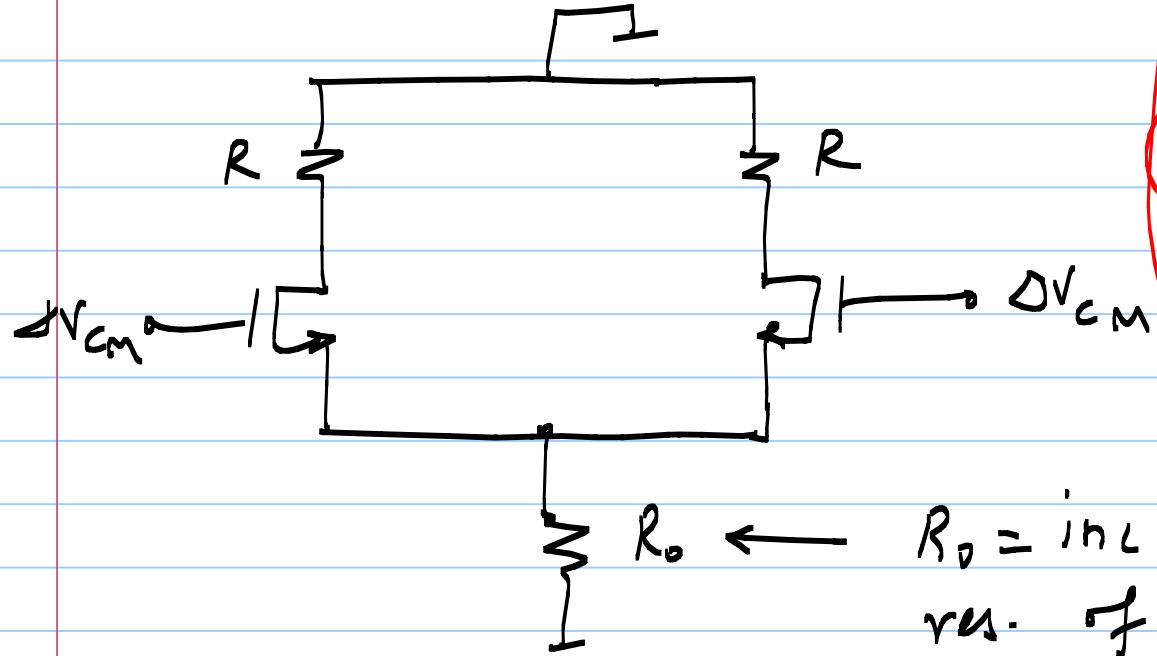


CM H.C.

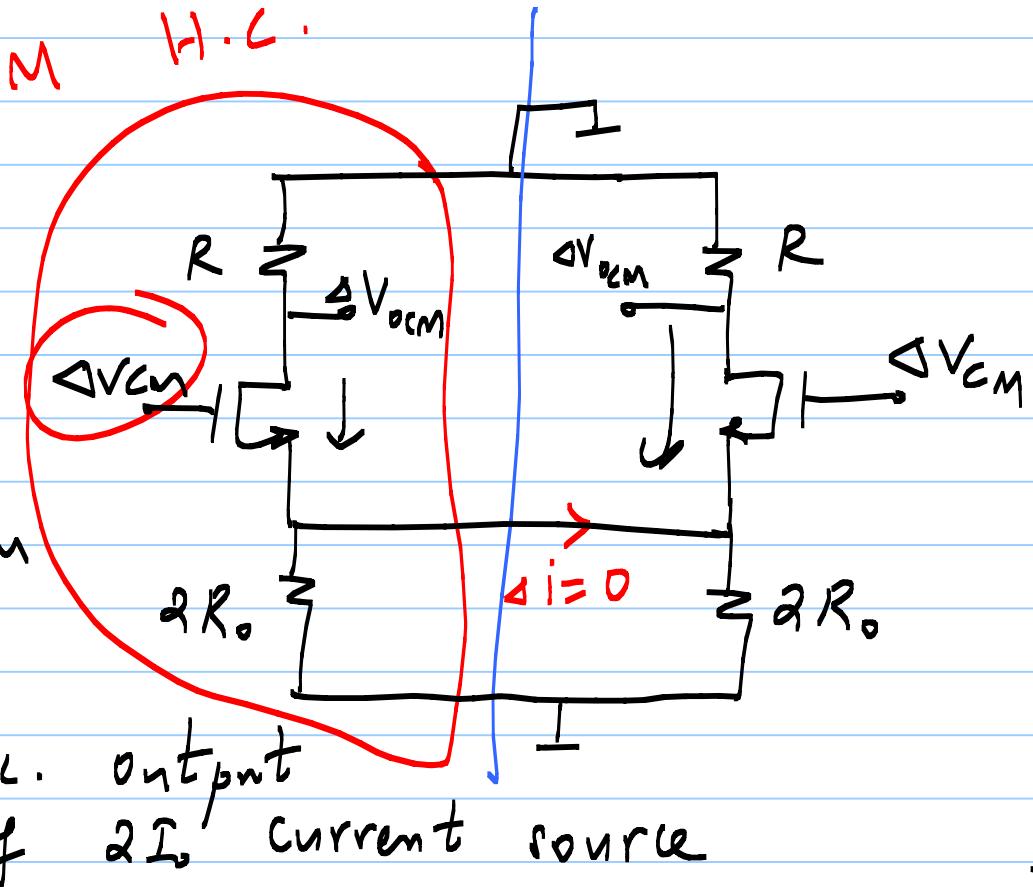


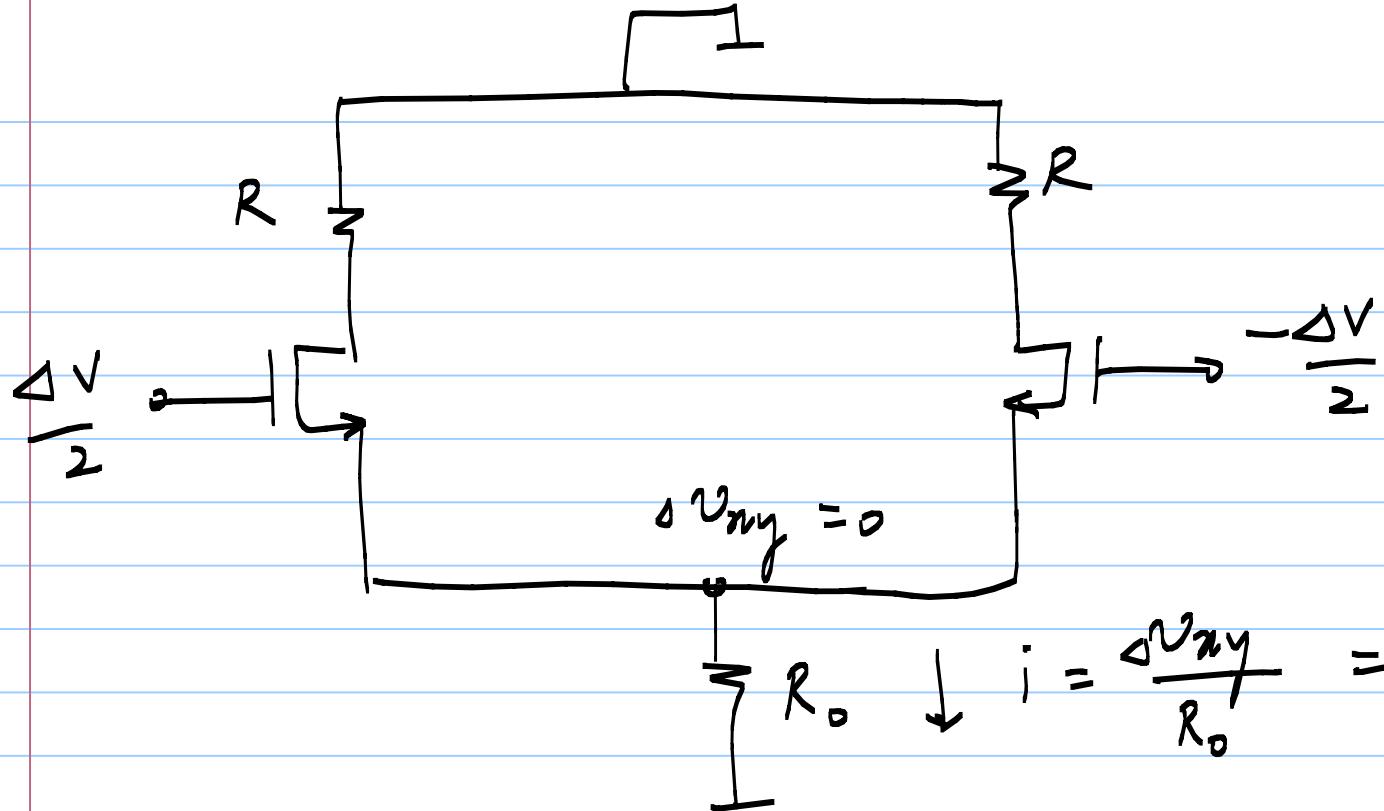

$i = \frac{\Delta V_{xy}}{R_0} = 0$ is the only possible state of the DM cir.

$$\Delta V_{CM} = ?$$

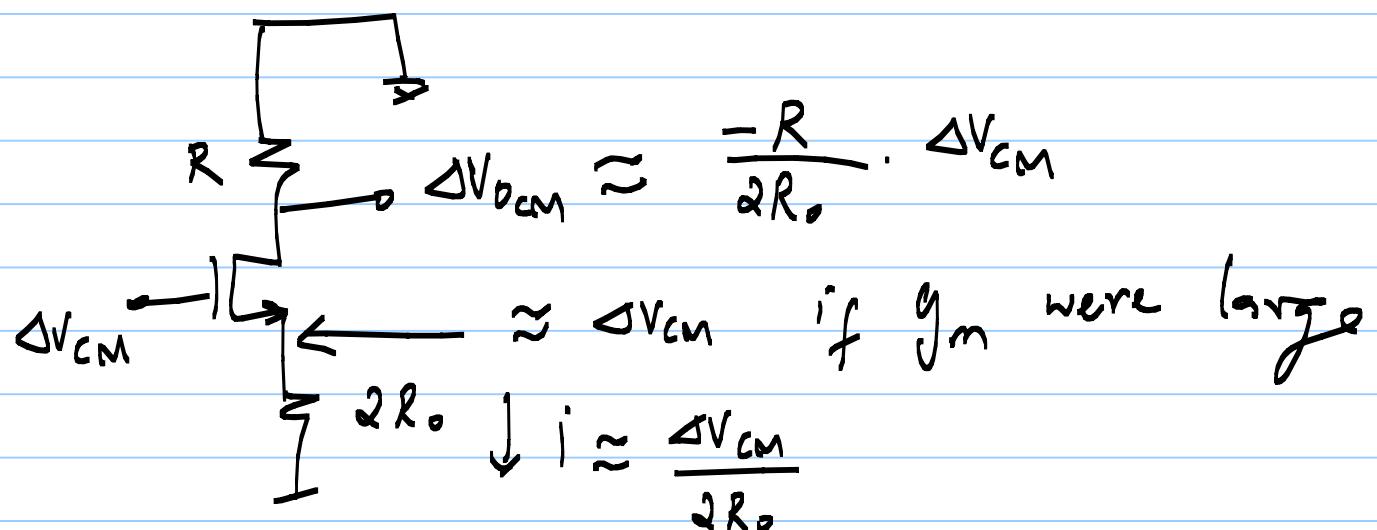

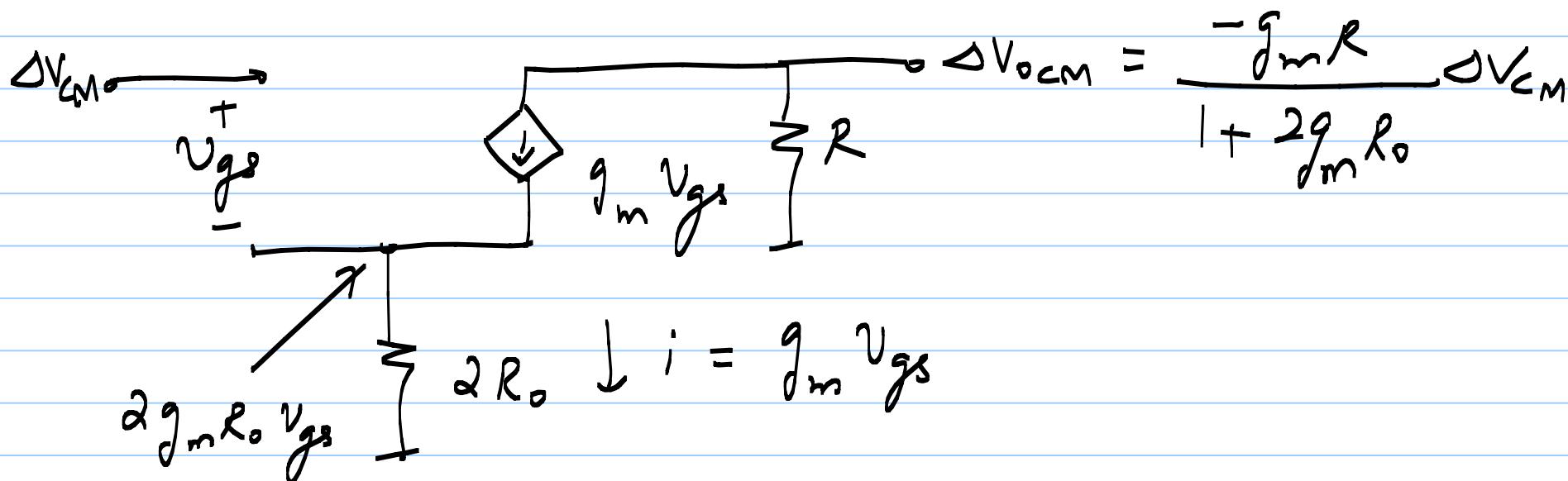

$$A_{DM} = -g_m R$$


$$A_{CM} = -\frac{g_m R}{1 + 2g_m R_o}$$

$$CMRR = \left| \frac{A_{DM}}{A_{CM}} \right|$$

Common Mode
Rejection Ratio

$$CMRR_{dB} = 20 \log \left| \frac{A_{DM}}{A_{CM}} \right|$$

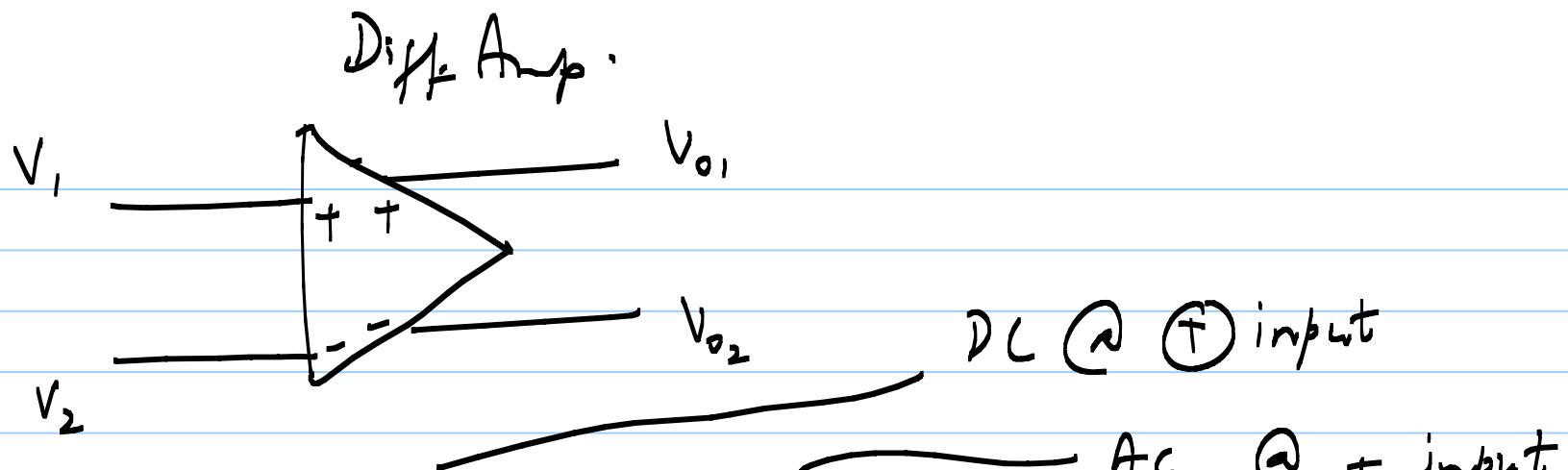large CMRR = "good" differential amplifier



e.g. $V_1 = 1V + 2mV \sin \omega t + 5mV (DC)$

$$V_2 = (.01V + 1mV \sin \omega t + 5mV (DC))$$

$$V_{iCM} = \frac{V_1 + V_2}{2} = 1.005V + 1.5mV \sin \omega t + 1\mu V \cos \omega t$$

$$V_{iDM} = \frac{V_1 - V_2}{2} = -0.005V + 0.5mV \sin \omega t + 2\mu V \cos \omega t$$

$$V_1 = V_{iCM} + V_{iDM} ; V_2 = V_{iCM} - V_{iDM}$$

$$V_{iDC} = V_{iCM} = 1.005V \rightarrow 1.01V$$

$$v_{CM} = 1.5mV \sin \omega t$$

$$\Delta V_{DM} = -0.005$$

$$v_{DM} = 0.5mV \sin \omega t$$