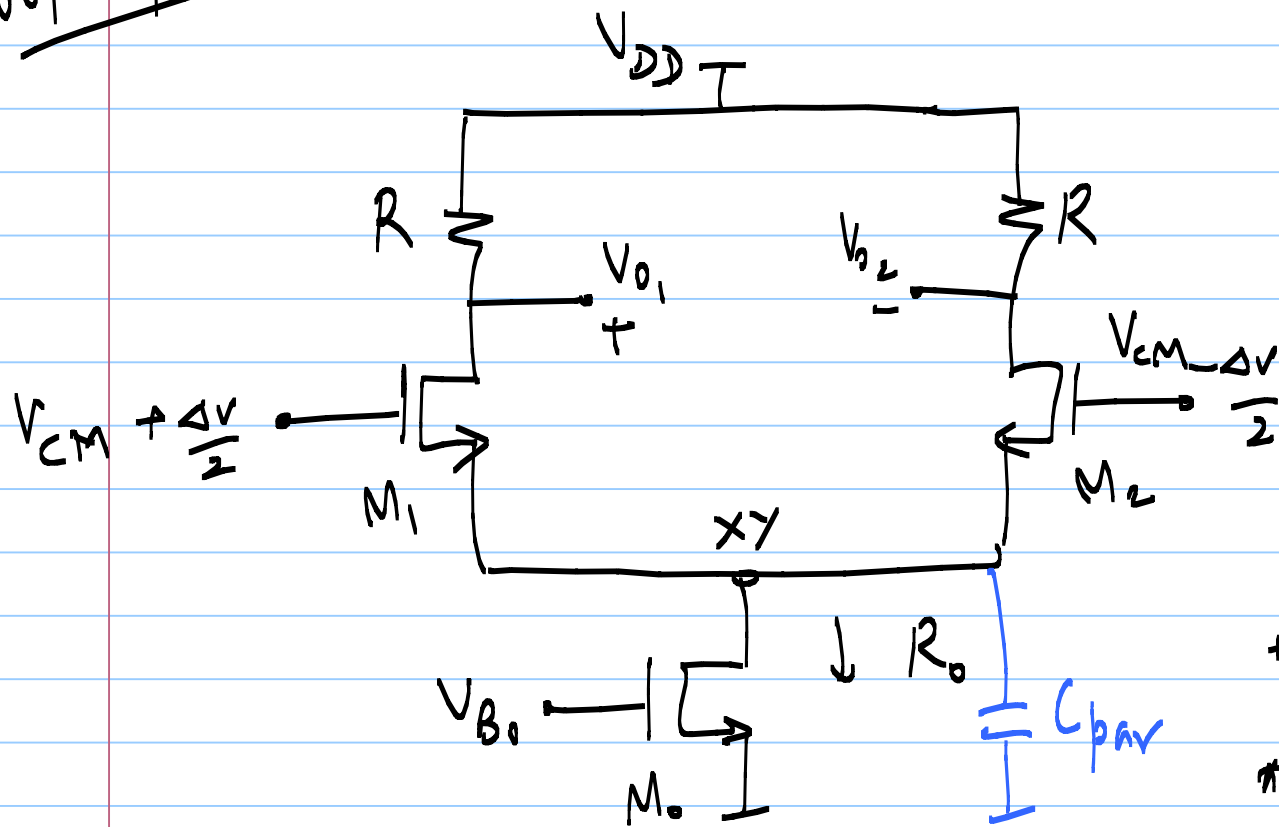


06/10/2020

Lecture 33



A_{DM} is large ($-g_m R$)

A_{CM} is small (dep. on R_0)

CMRR is large

We want to

- * have a single ended o/p


- * have more gain

- * Ensure C_{par} is as low as possible

Possibilities

- * SE o/p - discard V_{O1} or V_{O2} {not good}

- * more gain - active load

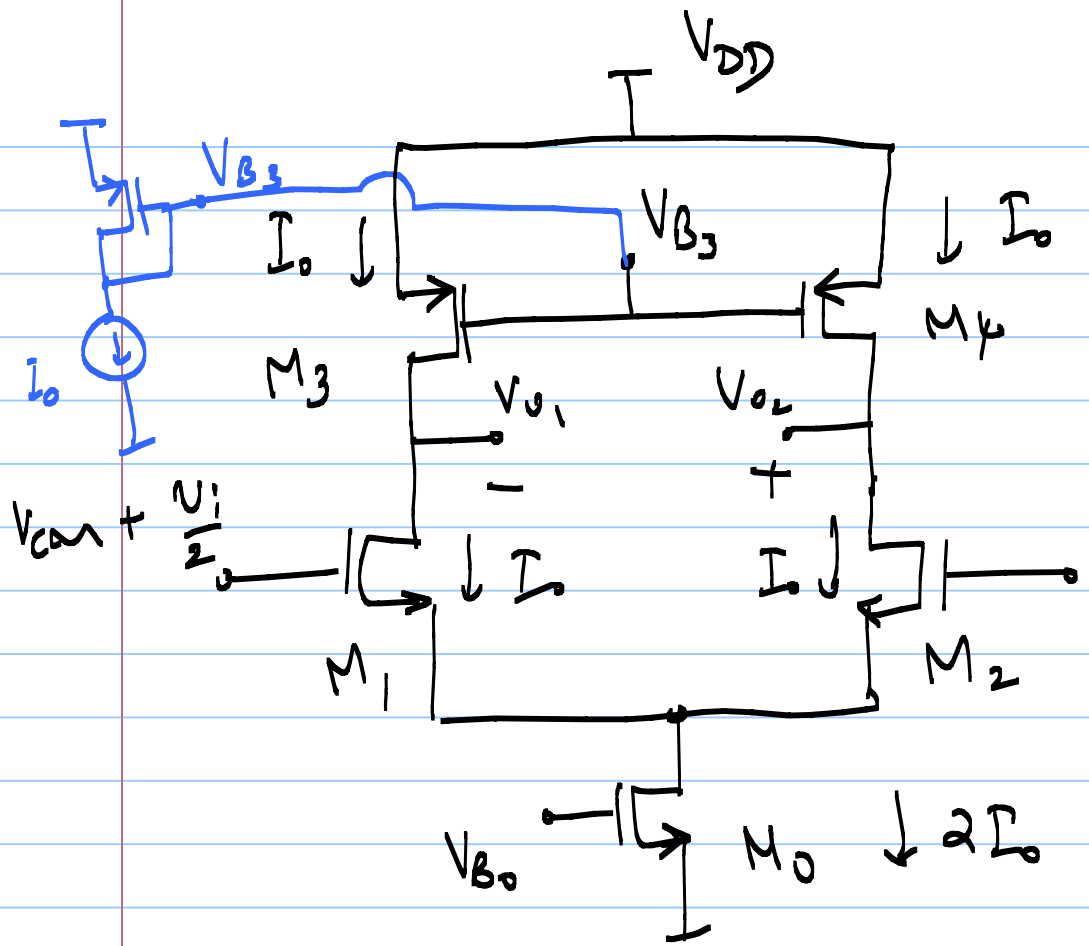

* Set V_{B3} so that
 $I_{D3} = I_{D4} = I_0$

$$v_{o1} = -g_{m1} (r_{ds1} || r_{ds3}) \cdot \left(\frac{v_i}{2}\right)$$


$$v_{o2} = -g_{m2} (r_{ds2} || r_{ds4}) \cdot \left(-\frac{v_i}{2}\right)$$

$$v_{cm} = \frac{v_i}{2} = +g_{m1} (r_{ds1} || r_{ds3}) \cdot \frac{v_i}{2}$$

$$v_o = v_{o2} - v_{o1}$$

$$= +g_{m1} (r_{ds1} || r_{ds3}) \cdot v_i$$

gain similar to
 CSA with active load

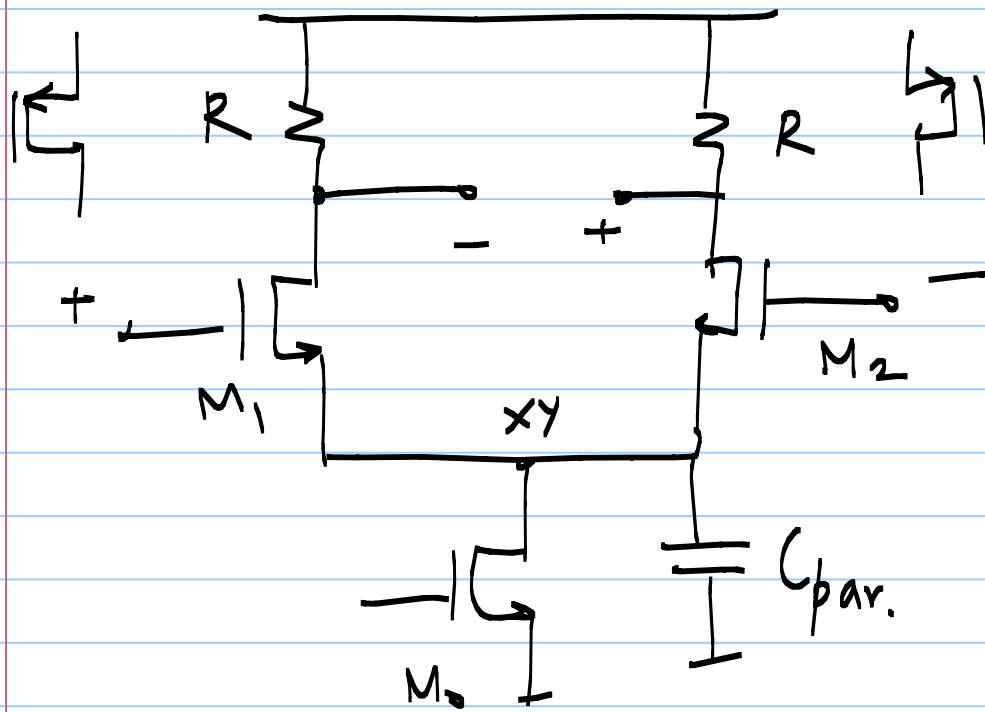

* C_{par} = "parasitic" cap
(undesired cap)

* Normally C_{par} @ xy
dominated by device cap.
(M_0 , M_1 & M_2)
(Not M_3 & M_4)



* C_{par} does not affect DM performance
significantly

* C_{par} affect CM performance



e.g. R_o (r_{ds-}) = ∞

original $A_{cm} = 0$ (without C_{par})

With C_{par} :

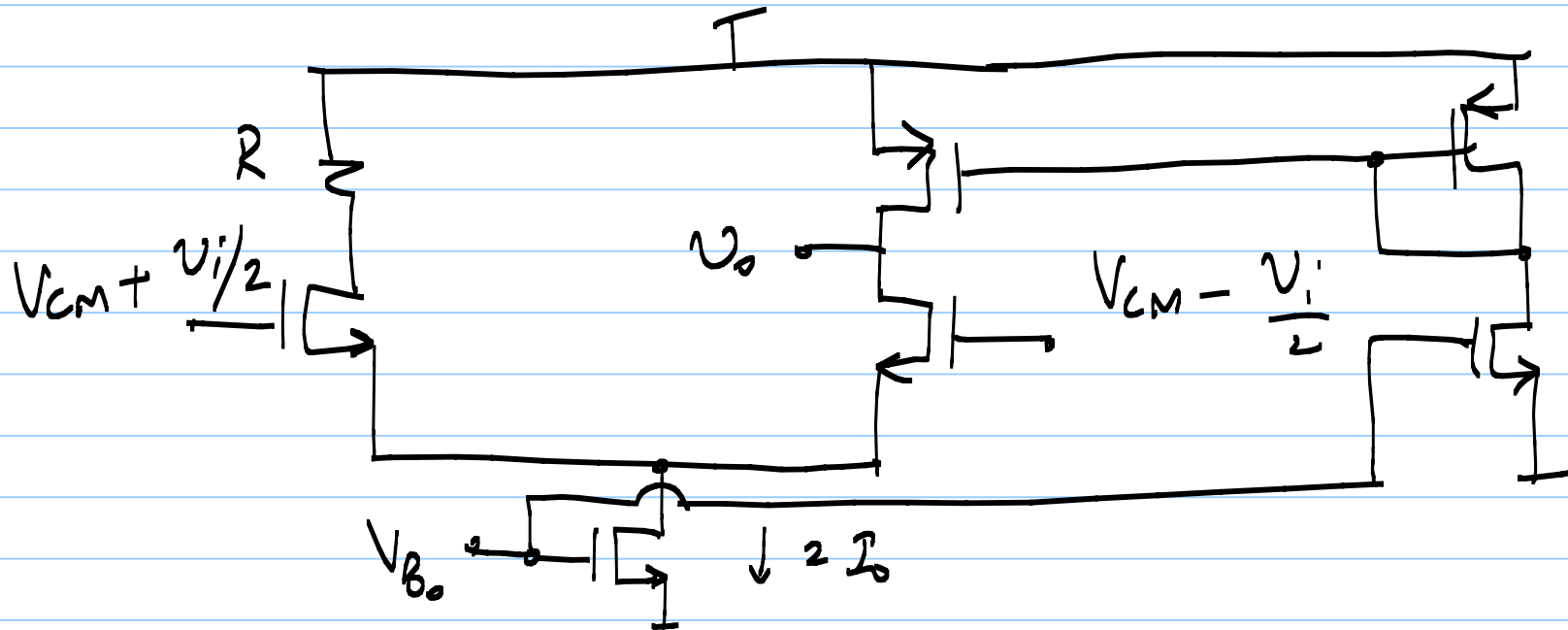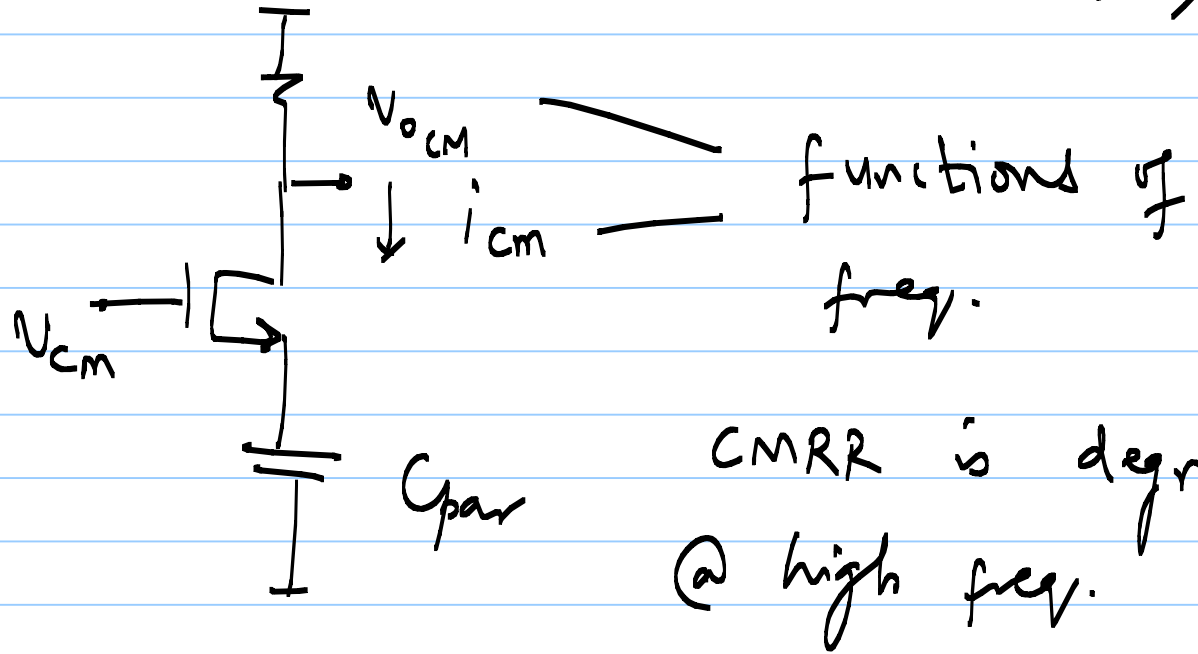

* only half the original gain

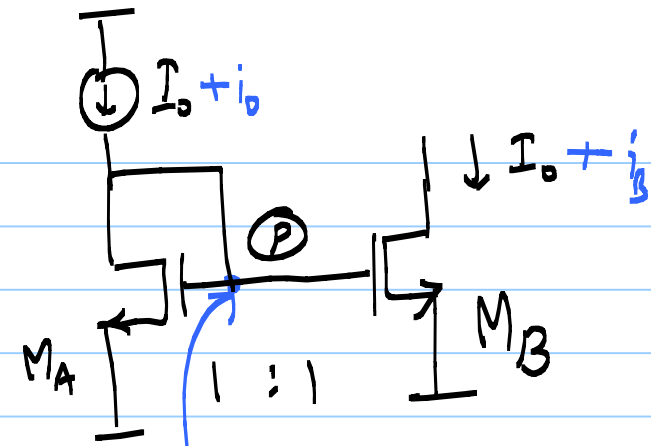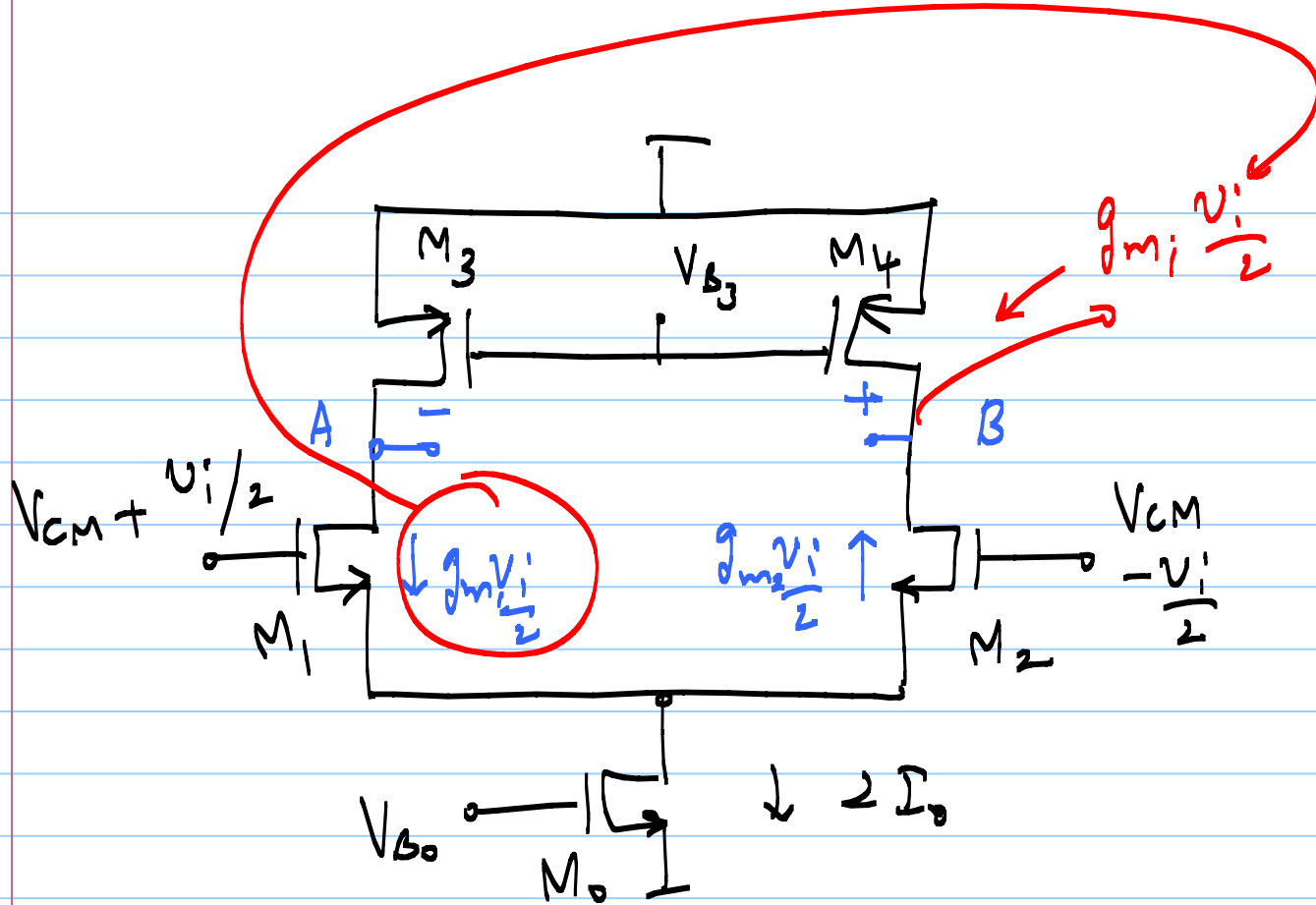


$$v_p = V_{AS_A} \left(I_o + \frac{i_o}{g_{m_A}} \right)$$


$$I_{D_B} = I_o + \frac{i_o \cdot g_{m_B}}{g_{m_A}}$$

$i_o = i_o$ here (1:1 CM)

C.G.A.

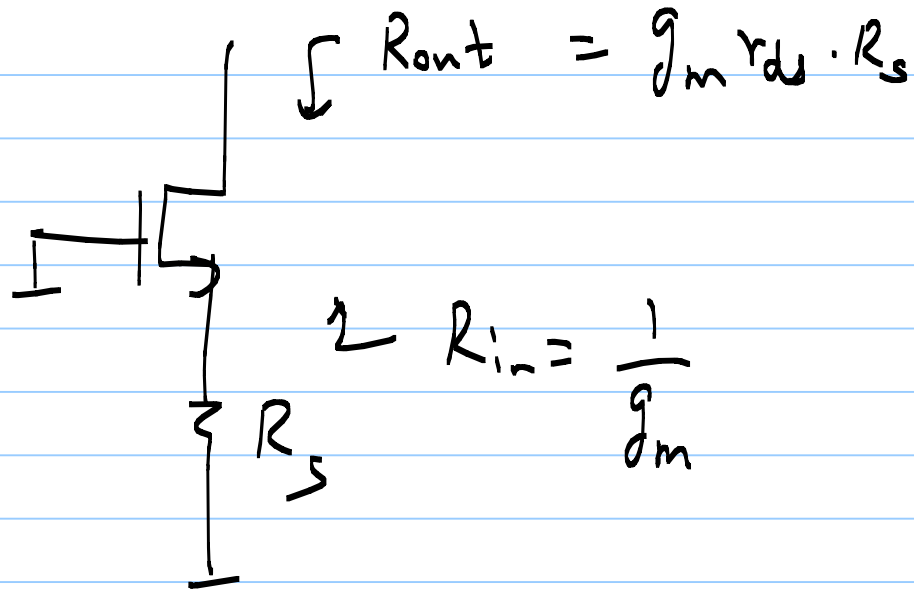

$R_{in} = \frac{1}{g_m}$

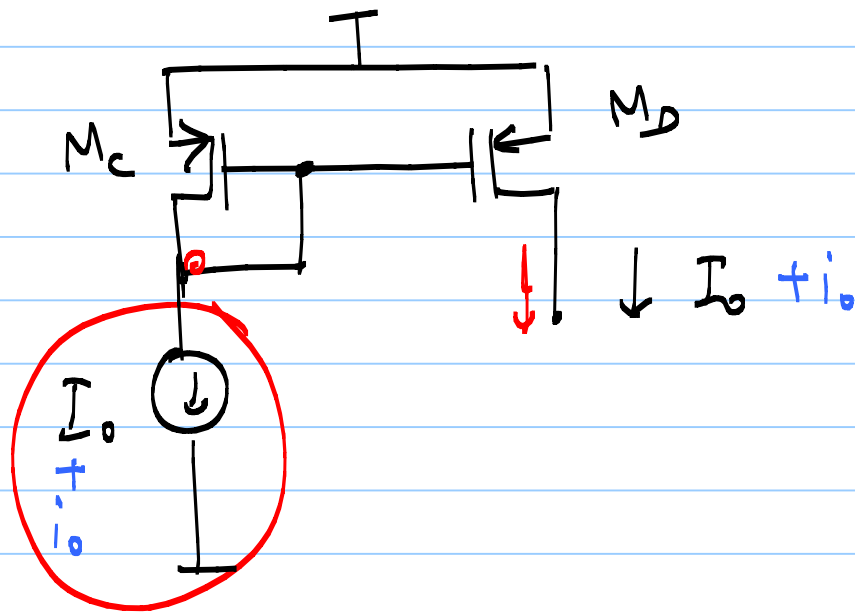

* Repurpose M_3 & M_4
to form $M_c - M_d$ C.M.

$$V_{DD} - V_{GS3} \quad I_D$$

$$-g_{m1} r_A \frac{v_i}{2} \approx -\frac{g_{m1}}{g_{m3}} \cdot \frac{v_i}{2}$$

$$\approx -\frac{g_{m1}}{g_{m3}} \cdot \frac{v_i}{2}$$

{i.e. $g_{m1} \gg g_{m3}, g_{ds3}$ }


$$r_A = r_{ds1} \parallel \frac{1}{g_{m3}} \parallel r_{ds3} \text{ (low imp)}$$

$$\approx \frac{1}{g_{m3}}$$

(originally high imp.)

$$g_{m1} \frac{v_i}{2} + I_{D0}$$

$$V_{CM} + \frac{v_i}{2}$$

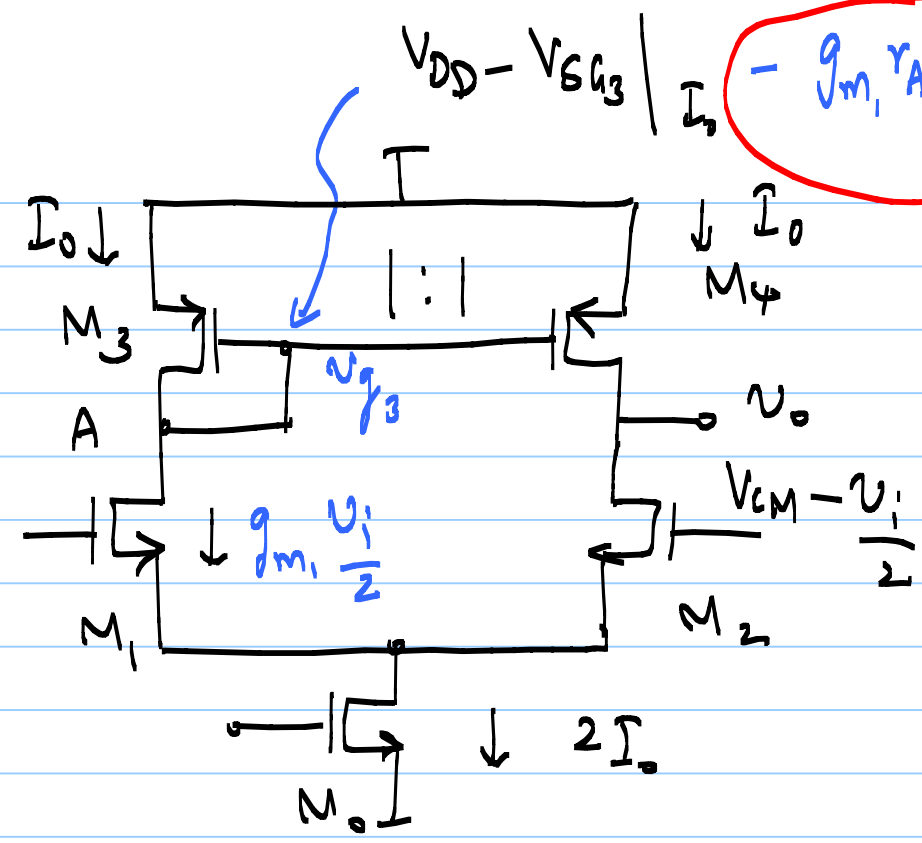

$$v_{g3} = \frac{-g_{m1}}{g_{m3}} \cdot \frac{v_i}{2}$$

$$g_{m4} v_{g4} = g_{m4} v_{g3}$$

$$-g_{m4} v_{g3} = -g_{m4} \cdot \frac{-g_{m1}}{g_{m3}} \cdot \frac{v_i}{2} = +g_{m1} \frac{v_i}{2}$$

