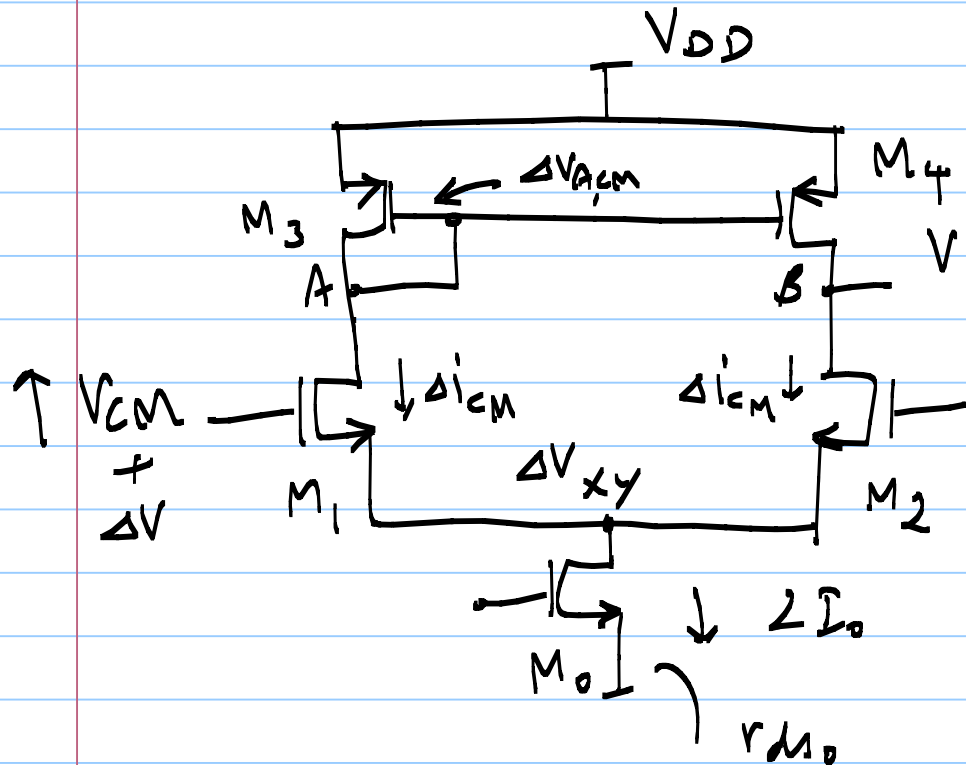


8/10/2020

Lecture 35

"Single Stage Amp"



$$V_{OCM} = V_{DD} - V_{SQ3} + \Delta V_{OCM}$$

$$\frac{\Delta V_{OCM}}{\Delta V} = A_{CM} \quad \{ HW \}$$


V_{CM} = input CM level \rightarrow range?

V_{OCM} = output CM level \rightarrow range?

ICMR - input CM range

OCMR - output CM range

ICMR: 1) keep $\downarrow V_{CM}$

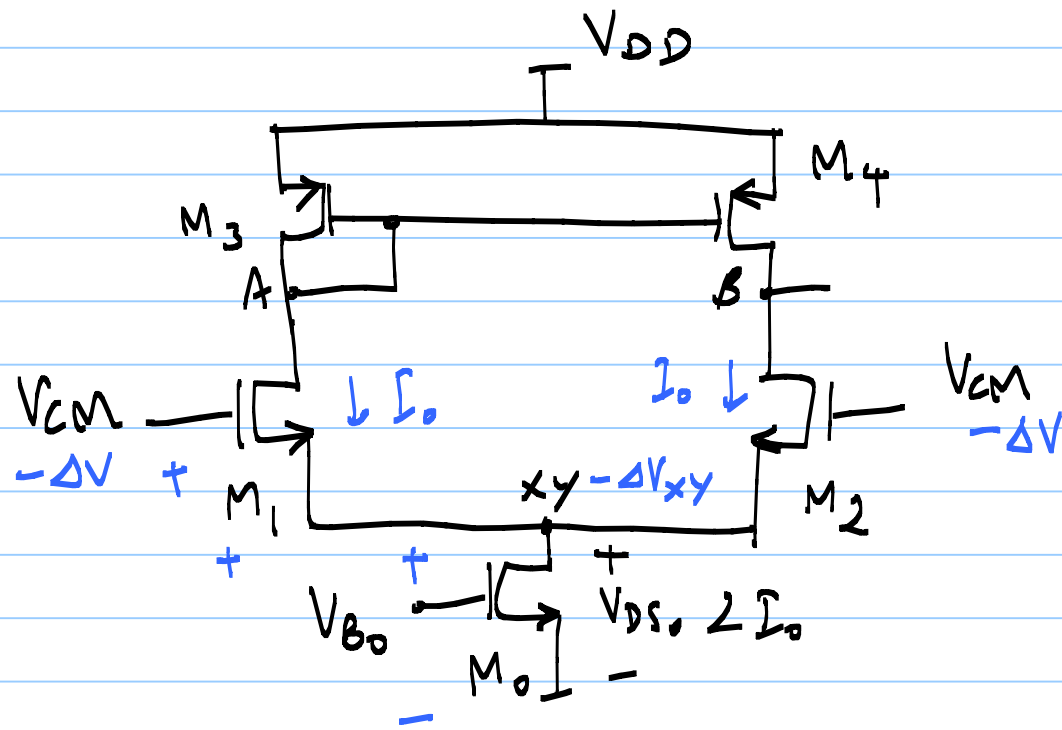

$\Delta V_{xy} = \Delta V$ if M_0 current does not change

ΔV_{xy} slightly less than ΔV

if M_0 has large r_{ds}

{ $V_{DS_0} \downarrow$ }

Eventually M_0 will go into triode region


When $V_{DS_0} = V_{B_0} - V_{T_0} = V_{DS_{sat_0}}$

$$V_{CM \min.} = V_{DS_{sat_0}} + V_{GS_1} \Big|_{I_0} \Big|_{2I_0}$$

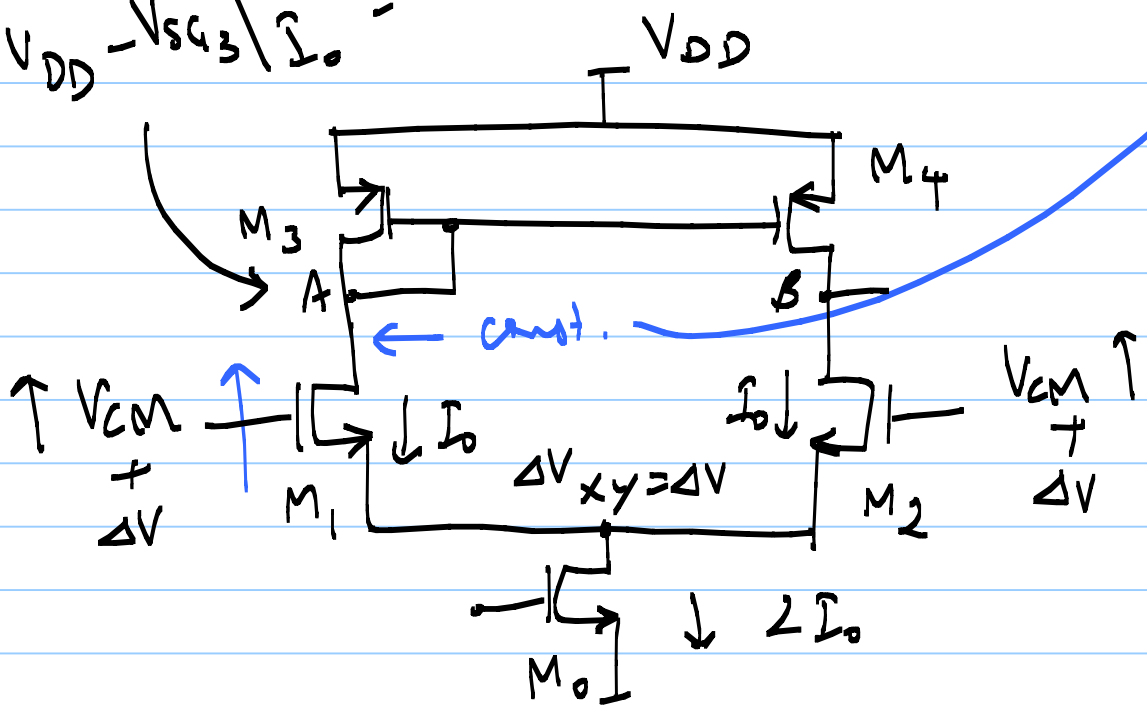2) $V_{CM} \uparrow \rightarrow V_{CM \max}$

M_0 moves away from triode boundary

$$V_A = V_{DD} - V_{SG3} / I_0 = \text{constant}$$



Moving M_1 & M_2 towards triode boundary


M_1 & M_2 will go into triode!

$$V_{D1} = V_{A1} - V_{T1}$$

$$V_{DD} - V_{SG3} / I_0 = V_{CM_{max}} - V_{T1}$$


$$V_{CM_{max}} = V_{DD} - V_{SG3} / I_0 + V_{T1}$$
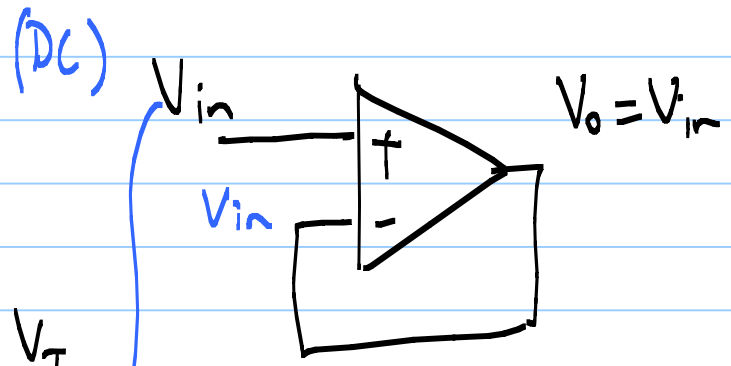
$$ICMR = \{ V_{CM_{min}}, V_{CM_{max}} \}$$



OCMR

constant

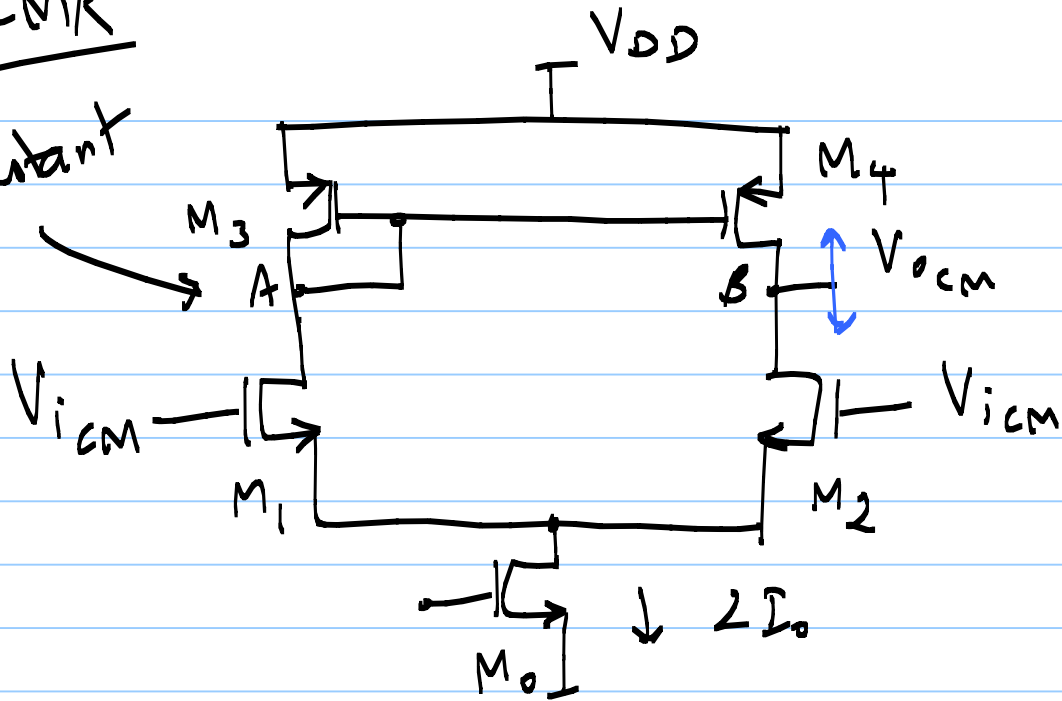

* V_{ocm} is set by

f.b.

1) $V_{ocm\ max}$ = voltage at which M_4 goes into triode

$$V_A = V_{DD} - V_{sg3} / I_o$$

$$V_{D4} = V_{A4} + V_{T4}$$

$$V_{ocm\ max} = V_A + V_{T4}$$

$$V_{ocm\ max} = V_{DD} - V_{sg3} / I_o + V_{T4}$$

$$V_{T3} + V_{SDsat3}$$

$$V_{ocm\ max} = V_{DD} - V_{SDsat4}$$


2) $\downarrow V_{ocm} \rightarrow V_{ocm\ min.}$ = voltage at which M_2 goes into triode

$$V_{D2} = V_{A2} - V_{T2}$$

$$V_{OCM \min.} = \underbrace{V_{ICM}} - V_{T2}$$

range of values within ICMR
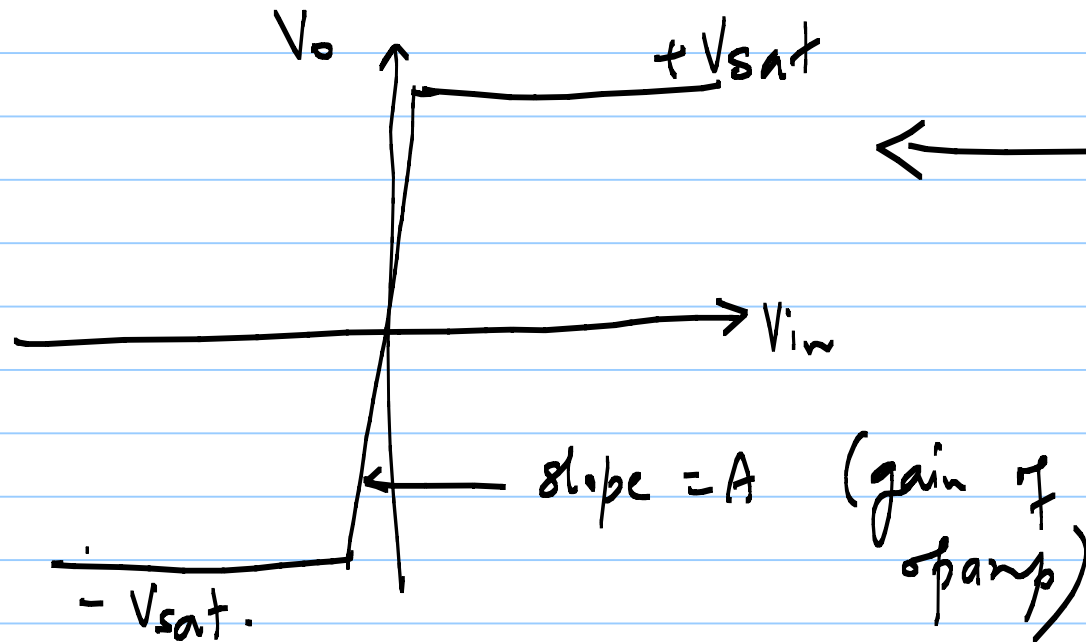
$$OCMR = \{ V_{CM \min.}, V_{CM \max.} \}$$



← Ideal opamp characteristics

One stage of amp :

