
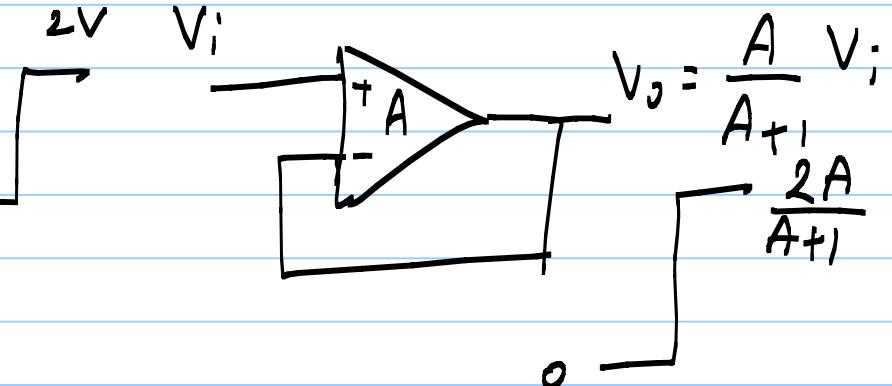


9/10/2020

Lecture 36

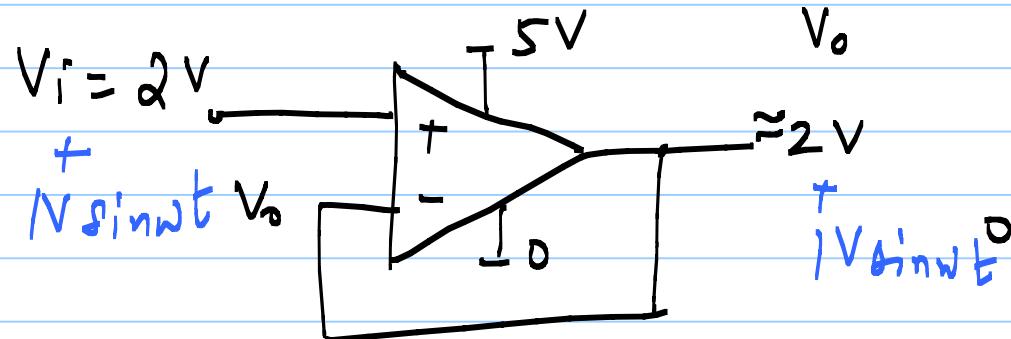

$$A = 100$$

$$\text{here } V_o = \frac{100}{101} \cdot 2V$$

$$V_{CM} = \frac{V_+ + V_-}{2} = \frac{V_i + V_o}{2} = \frac{1}{2} \left[V_i + \frac{100}{101} V_i \right]$$


$$= \frac{201}{202} \cdot V_i \approx V_i$$

$$V_{DM} = \frac{V_+ - V_-}{2} = \frac{V_i - V_o}{2} = \frac{1}{2} \left[V_i - \frac{100}{101} V_i \right]$$

$$V_{DM} = \frac{V_i}{2} \cdot \frac{1}{101} = \frac{V_i}{202}$$


$$V_+ = V_{CM} + V_{DM} = \frac{201}{202} V_i + \frac{V_i}{202} = V_i$$


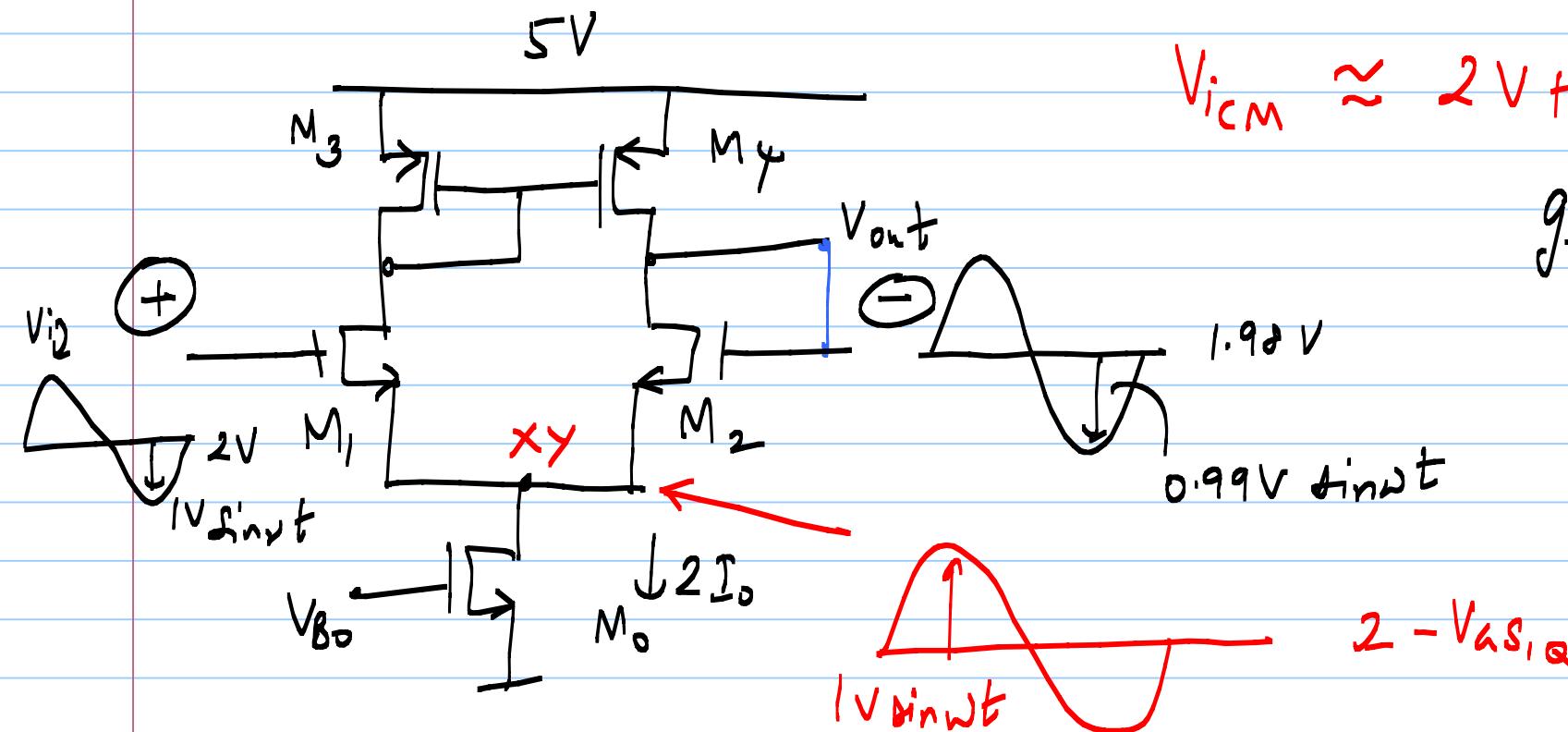
$$V_- = V_{CM} - V_{DM} = \frac{100}{101} V_i$$




$$V_{iCM} \approx 2V_+ - 1V \sin \omega t$$

$$g_m, r_{ds} \gg 1$$

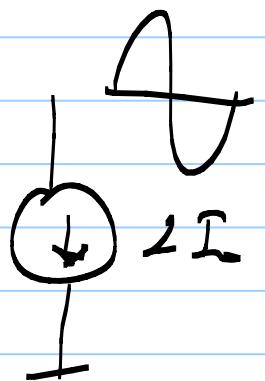

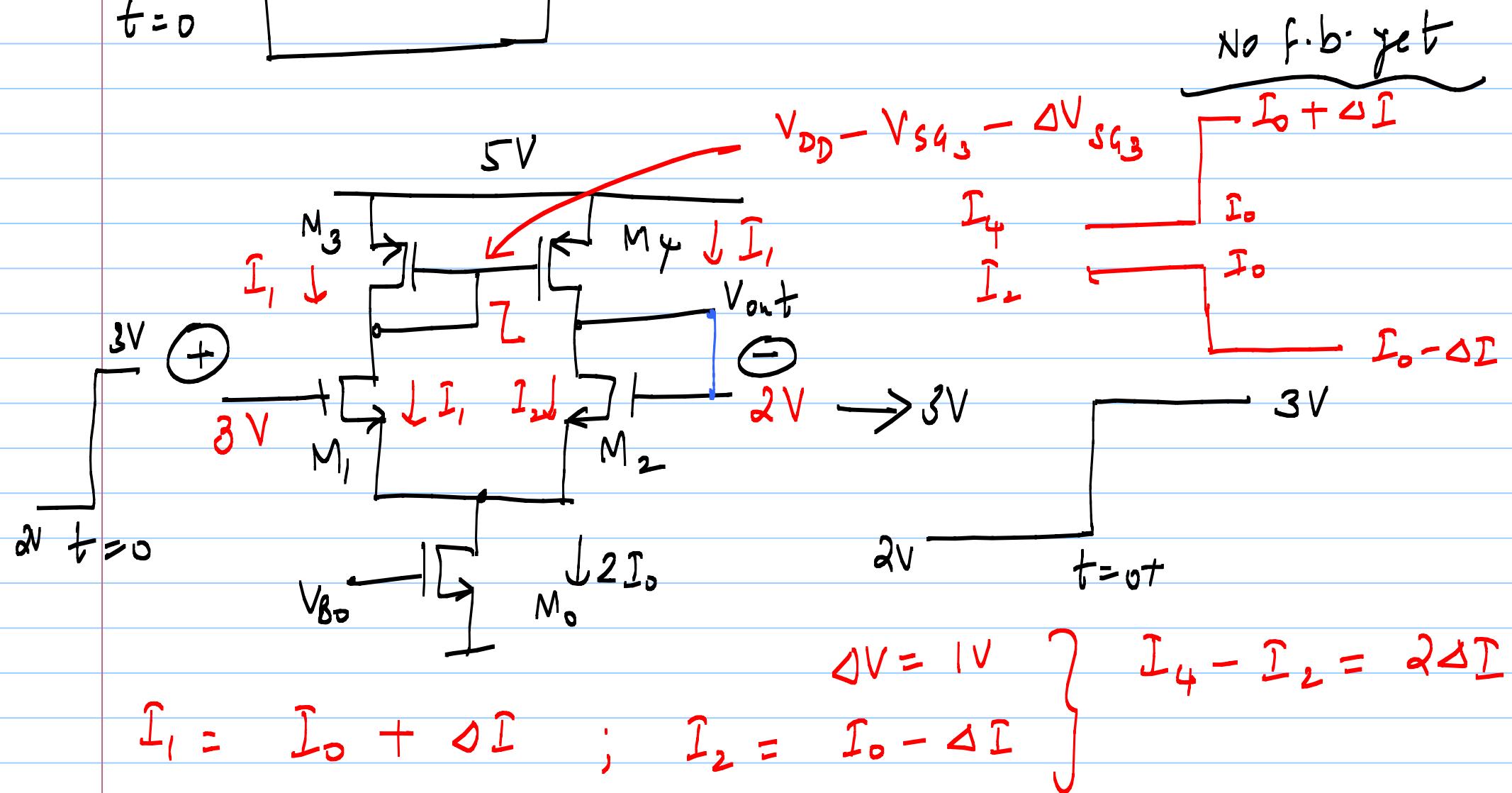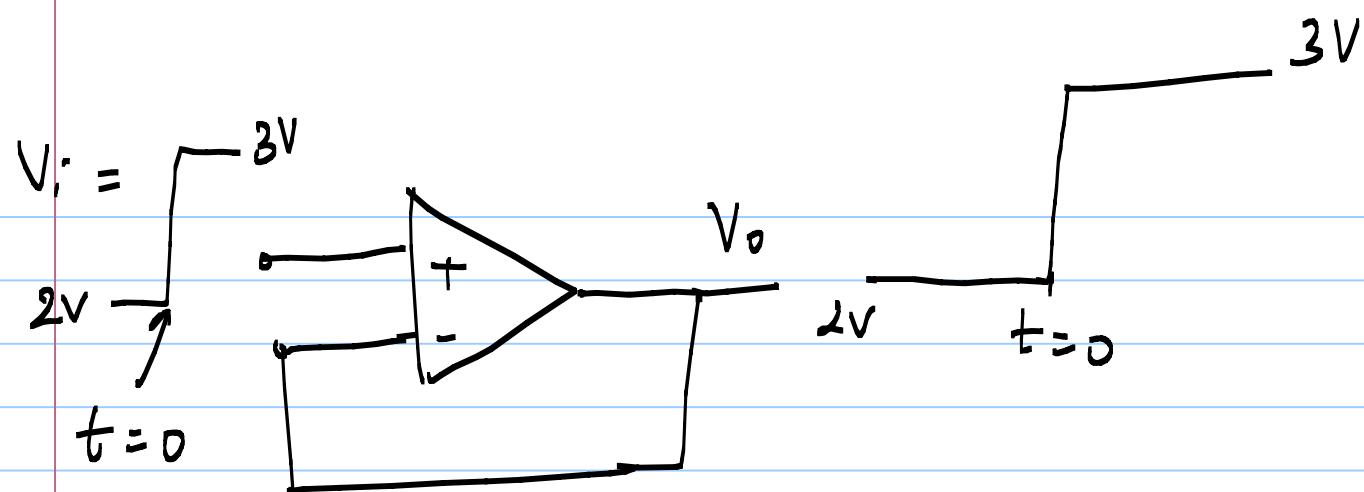

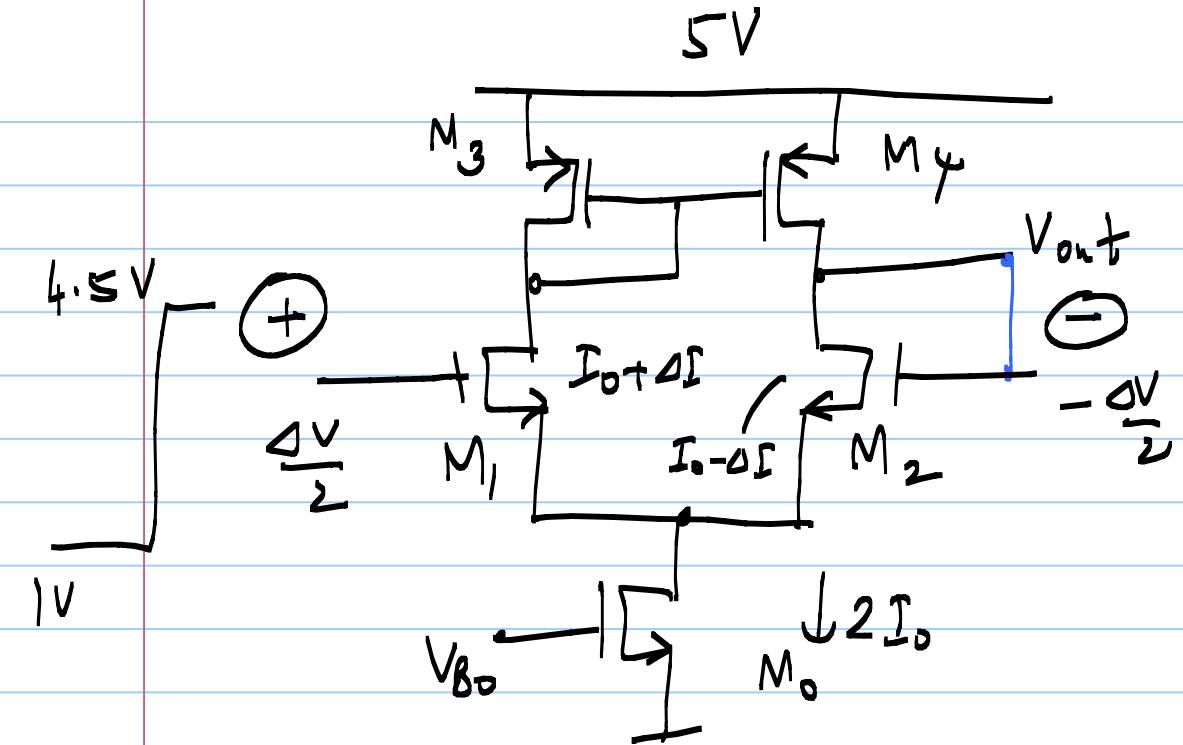

ΔI depends on $\frac{\Delta V}{2}$

larger $\frac{\Delta V}{2} \rightarrow$ larger ΔI

small signals: $\Delta I = g_m \frac{\Delta V}{2}$

large signals (large ΔV)


larger $\frac{\Delta V}{2} \rightarrow$ larger ΔI

still true

$$M_2 = 0$$

(largest possible $\Delta I = I_o$ { $I_1 = 2I_o$, $I_2 = 0$ })

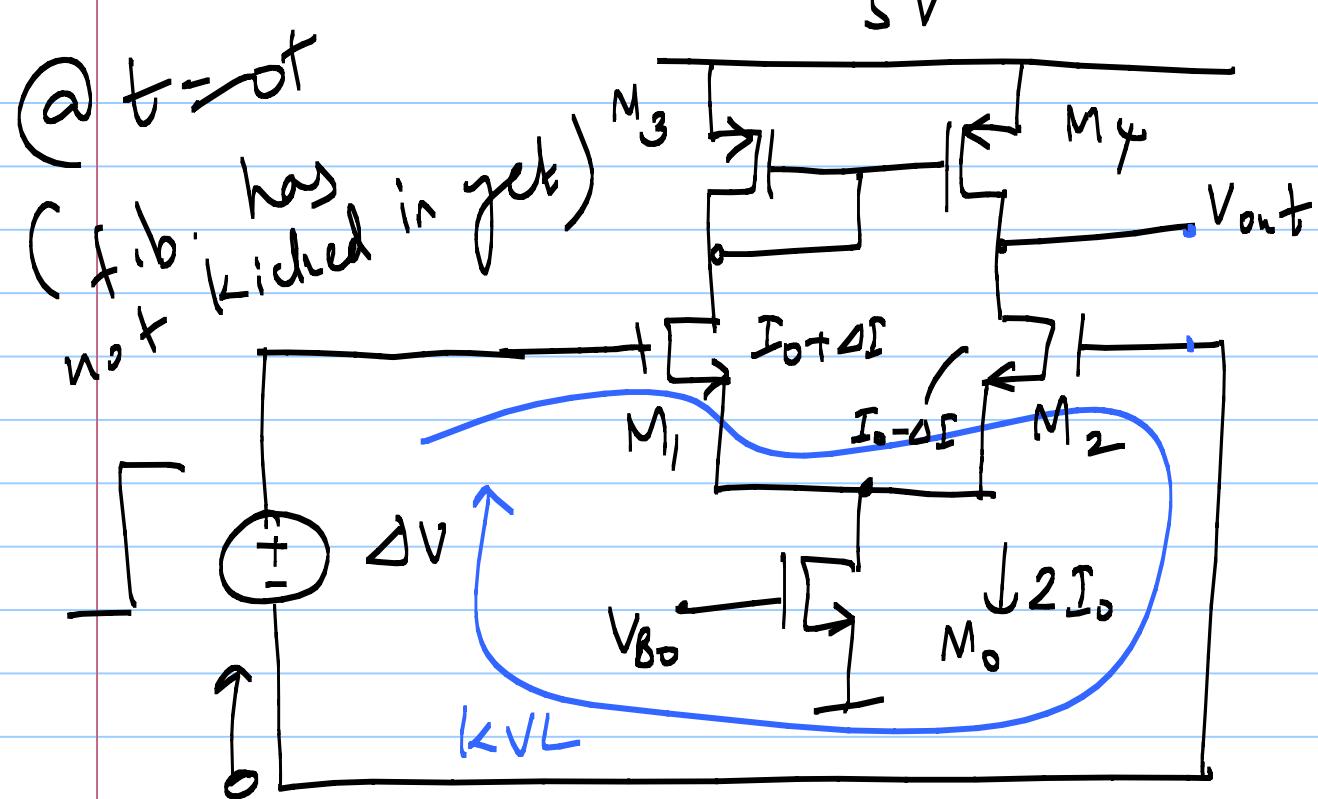Beyond this: larger $\Delta V \not\Rightarrow$ larger ΔI



$$\begin{aligned}
 &+ \Delta V - V_{GS_1} + V_{GS_2} = 0 \\
 \Delta V &= V_{GS_1} - V_{GS_2}
 \end{aligned}$$

