

14/10/2020


Lecture 38

* MOSFET caps - C_{gs} , C_{gd} , C_{db} , C_{sb}


largest \nearrow C_{gs} \nearrow C_{gd} smallest

$\frac{2}{3} WL C_{ox}$


1) Assume C_{gd} is negligible

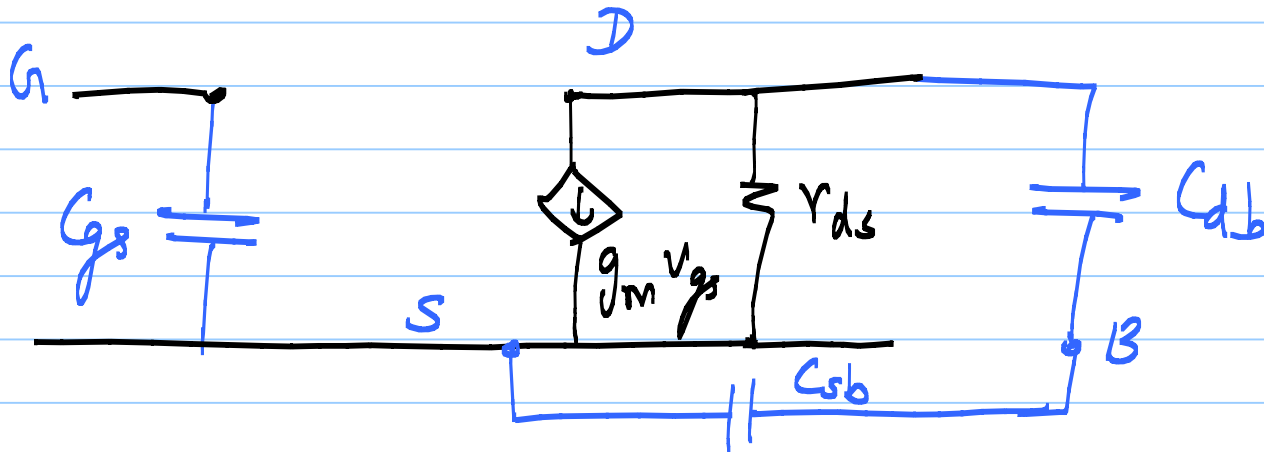

CSA

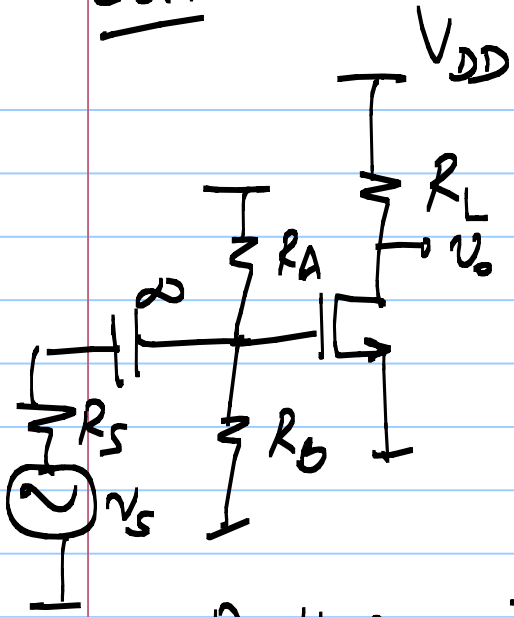

$$R_A \parallel R_B \gg R_s$$

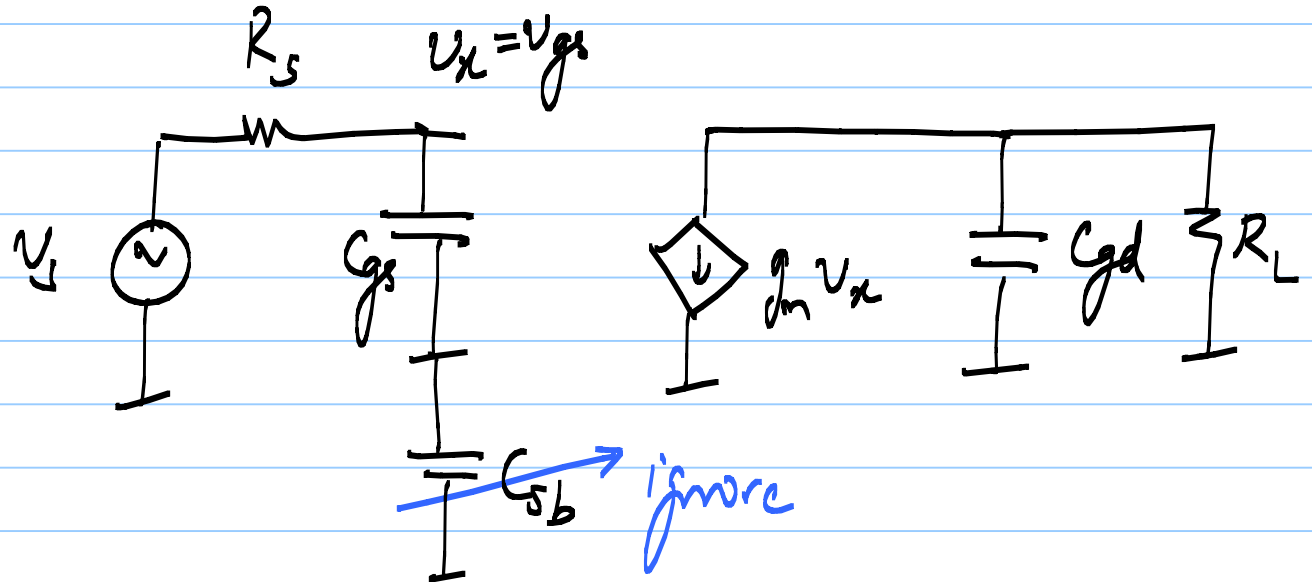

$$v_x(s) = \frac{1/s C_{gs}}{R_s + 1/s C_{gs}} \cdot v_s(s)$$

$$v_o(s) = -g_m \cdot \frac{1}{G_L + s C_{db}} \cdot v_x(s)$$

$$\frac{v_o}{v_s}(s) = \frac{1}{1 + s C_{gs} R_s} \cdot \frac{R_L}{1 + s C_{db} R_L} \cdot -g_m$$

$$\frac{v_o}{v_s}(s) = (-g_m R_L) \cdot \frac{1}{(1 + s C_{gs} R_S)(1 + s C_{db} R_L)}$$


input pole

$$p_1 = -\frac{1}{R_S C_{gs}}$$

output pole



$$p_2 = -\frac{1}{R_L C_{db}}$$

2) With C_{gd} :

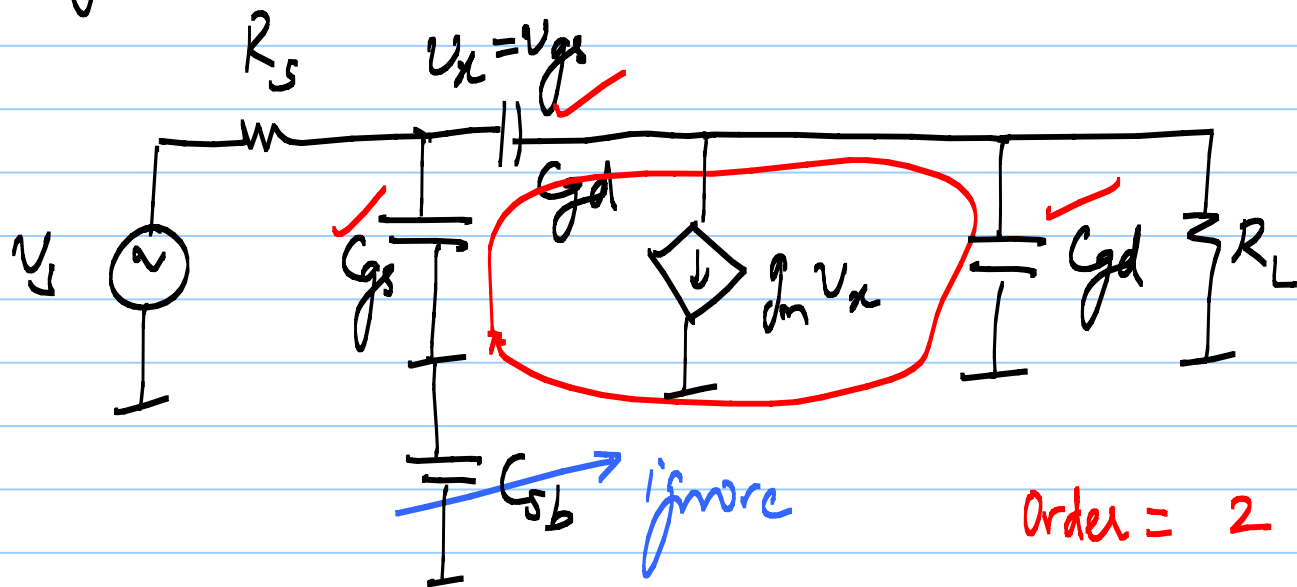


quadratic }
order = 2 { D(s) }

2 poles + 1 zero

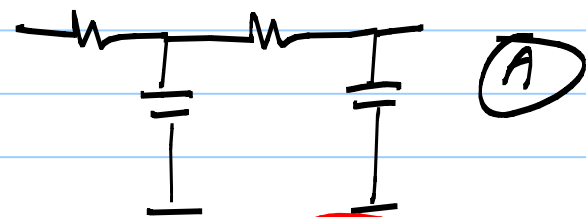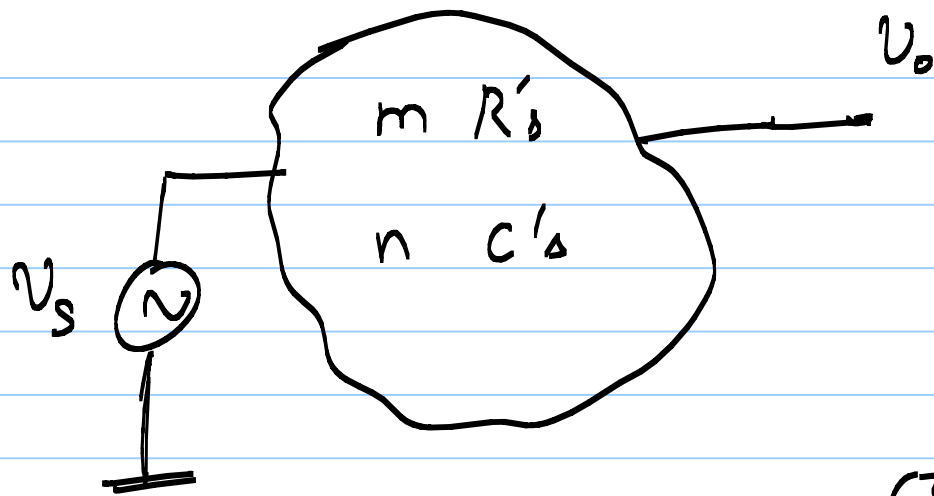





$$\frac{v_o}{v_s} = \frac{N(s)}{D(s)}$$

order = degree of $D(s)$

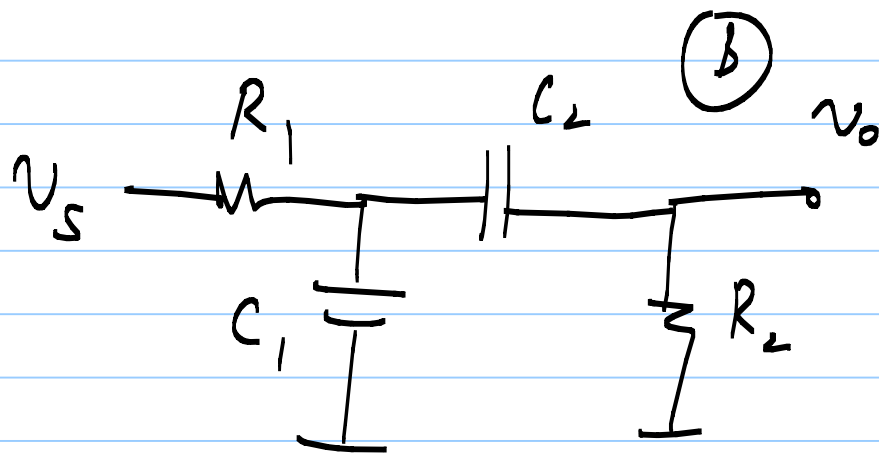

1 cap. \Rightarrow order = 1

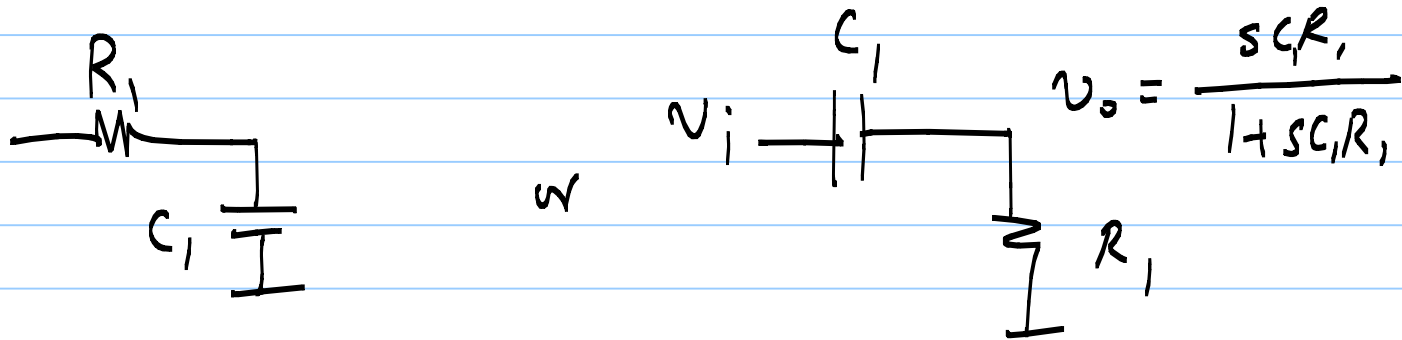

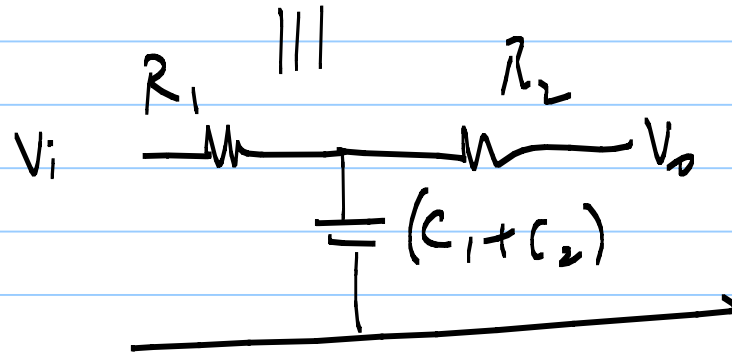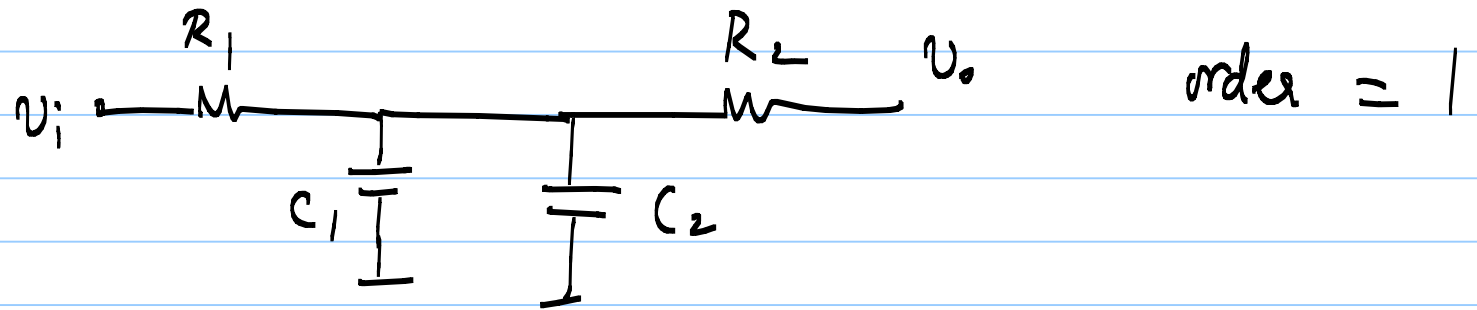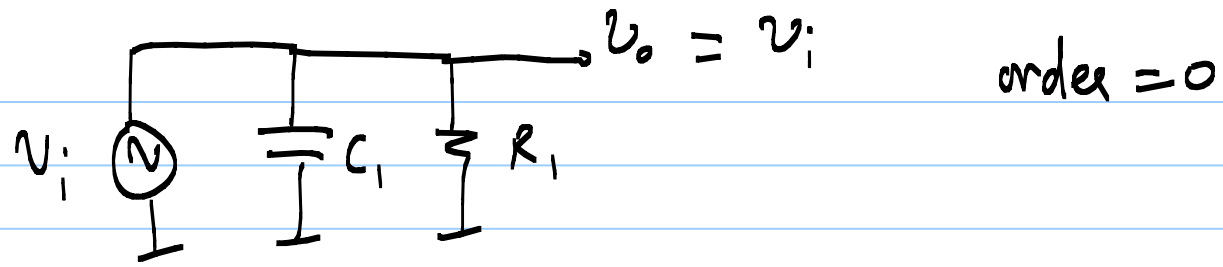


Order = # of capacitors - # of all-capacitor loops
 - # of capacitor-voltage source loops
 = Degree of $D(s)$



$N(s)$ degree = # of zeroes

$$\frac{v_o}{v_s}(s) = \frac{N(s)}{D(s)}$$

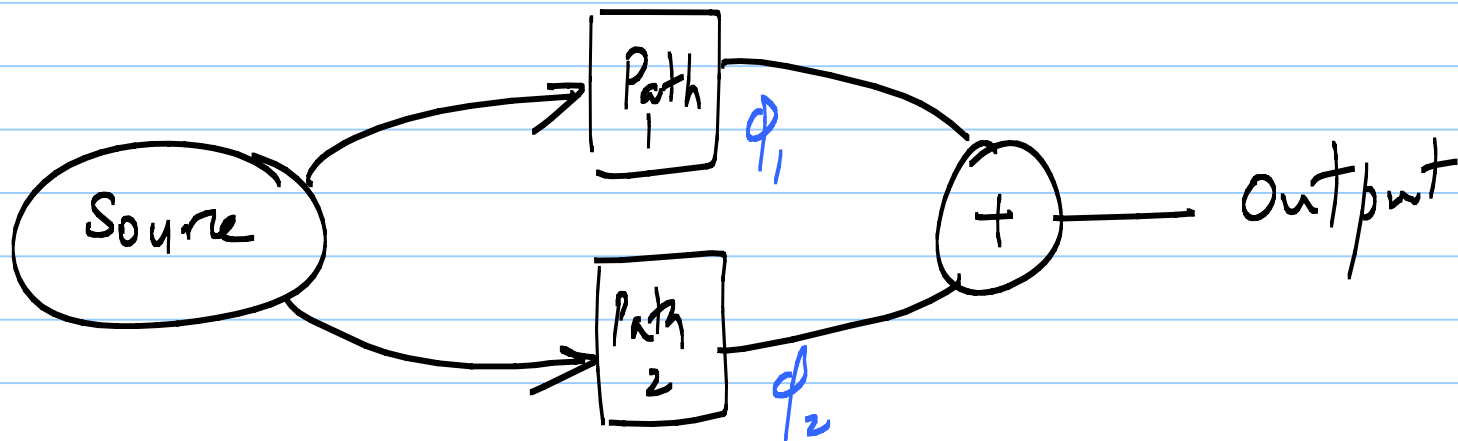@ zero frequency ($s=0$), $v_o(s) = 0$
independent of v_s



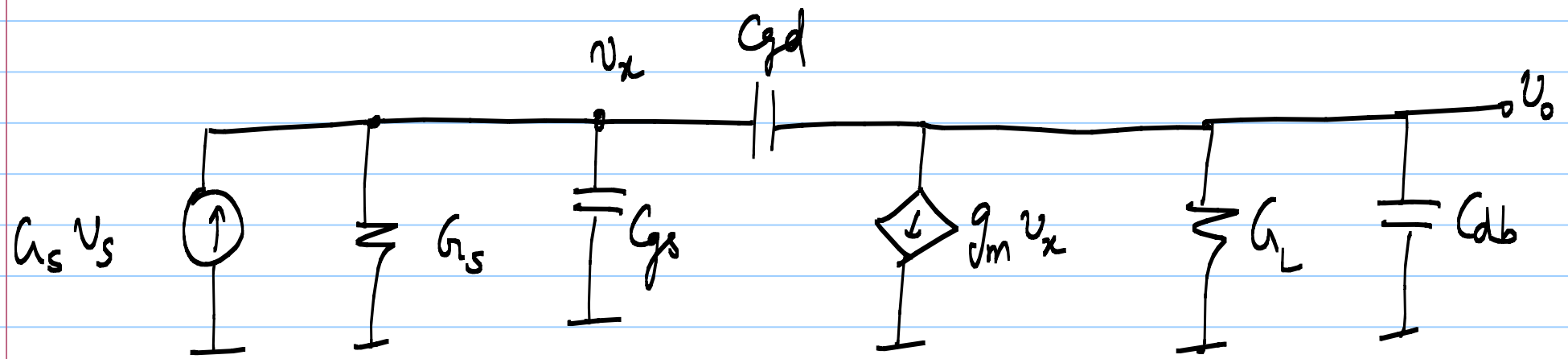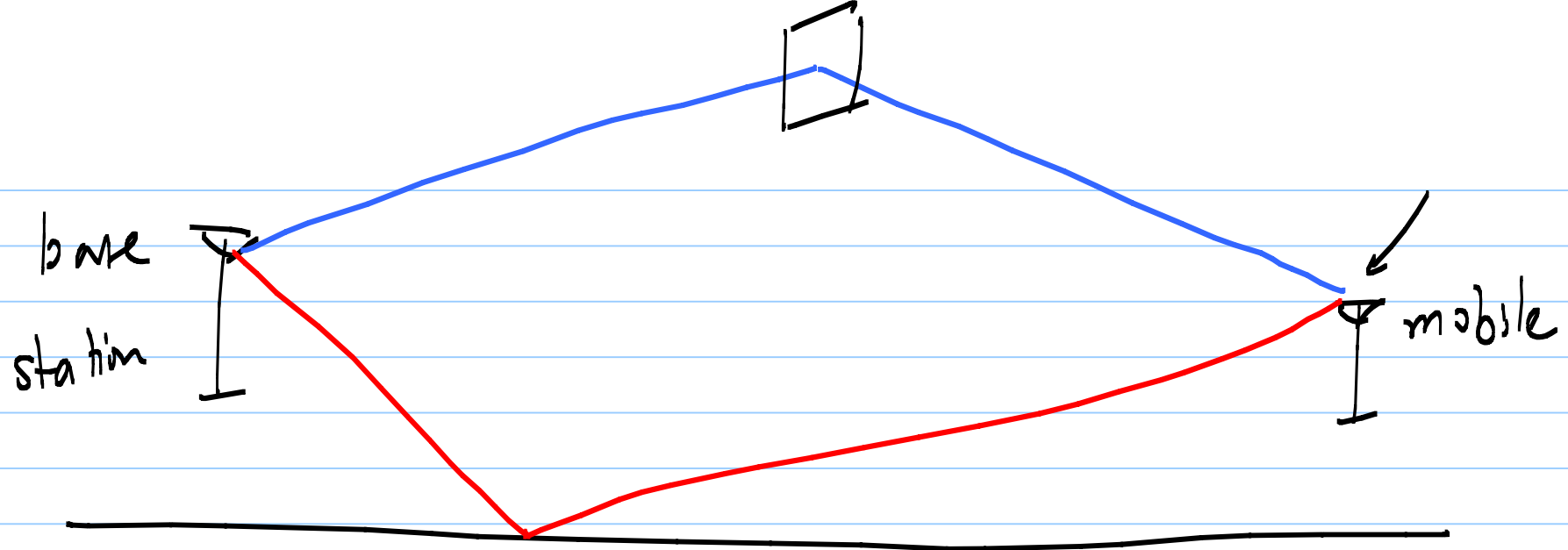Zero \Rightarrow * multiple paths from input to output
and * phase shifts along paths are different



KCL @ input :

$$v_x s C_{gs} + v_x G_s + (v_x - v_o) s C_{gd} = v_s G_s$$

$$\Rightarrow v_x [G_s + s(C_{gs} + C_{gd})] = v_s G_s + v_o s C_{gd}$$

$$v_x = \frac{v_s G_s + v_o s C_{gd}}{G_s + s(C_{gs} + C_{gd})}$$

KCL @ output :

$$(v_o - v_x) s C_{gd} + v_o (G_L + s C_{db}) + g_m v_x = 0$$

$\textcircled{\text{HW}} \rightarrow \frac{v_o}{v_s}(s) = ?$

$$\frac{V_o}{V_s} = \left(\begin{array}{c} \text{low freq.} \\ \text{gain} \end{array} \right) \frac{\text{zeros } (N(s))}{\text{poles } (D(s))}$$

$$= \left(-\frac{g_m}{G_L} \right) \frac{\text{1st order } N(s)}{\text{2nd order } D(s)}$$