
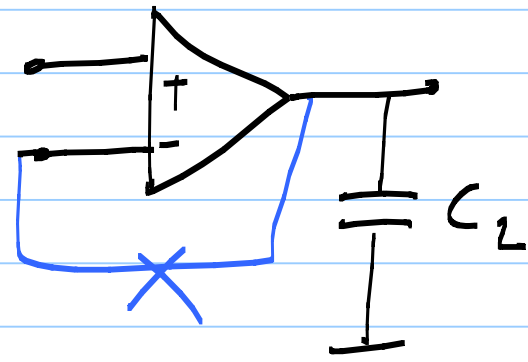


27/10/2020

Lecture 45

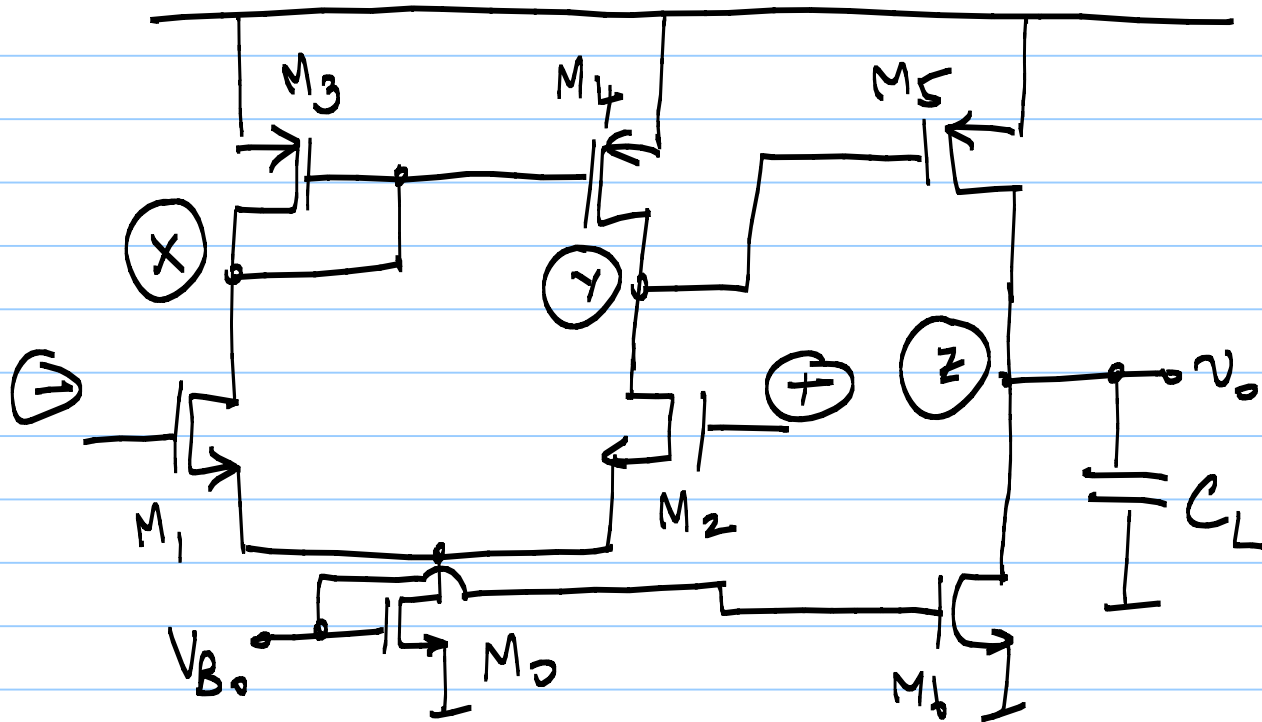

3 poles @ X, Y, Z
 1 zero @ $2p_x$ (z_x)

$$C_x \approx 2C_{gs3} \quad ; \quad C_y \approx C_{gs5} \quad ; \quad C_z \approx C_L$$


$$G_x \approx g_{m3} \quad ; \quad G_y = g_{ds2} + g_{ds4} \quad ; \quad G_z = g_{ds5} + g_{ds1}$$

$$p_x \approx \frac{g_{m5}}{2C_{gs3}} \quad ; \quad p_y \approx \frac{g_{ds2} + g_{ds4}}{C_{gs5}} \quad ; \quad p_z \approx \frac{g_{ds5} + g_{ds1}}{C_L}$$

(FW)


$p_x \gg p_y, p_z$; so, ignore p_x & $z_x = 2p_x$

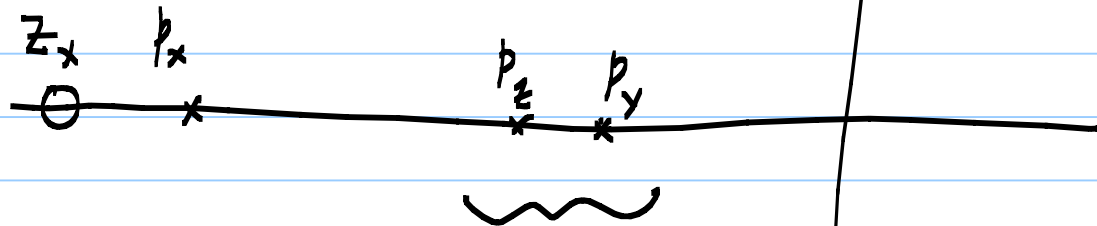So \rightarrow effectively a 2-pole system (p_y & p_z) with high DC gain



high Q , low ζ , ringing in step response

problem

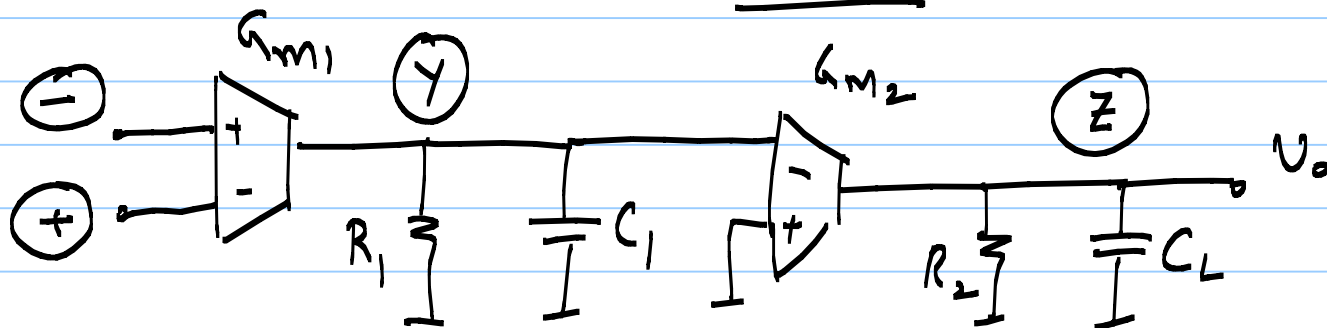


Block level view of 2-stage opamp

$$G_{m1} = g_{m1} \quad ; \quad G_{m2} = g_{m5}$$

$$R_1 = \frac{1}{g_{ds2} + g_{ds4}} \quad ; \quad R_2 = \frac{1}{g_{ds5} + g_{ds6}}$$
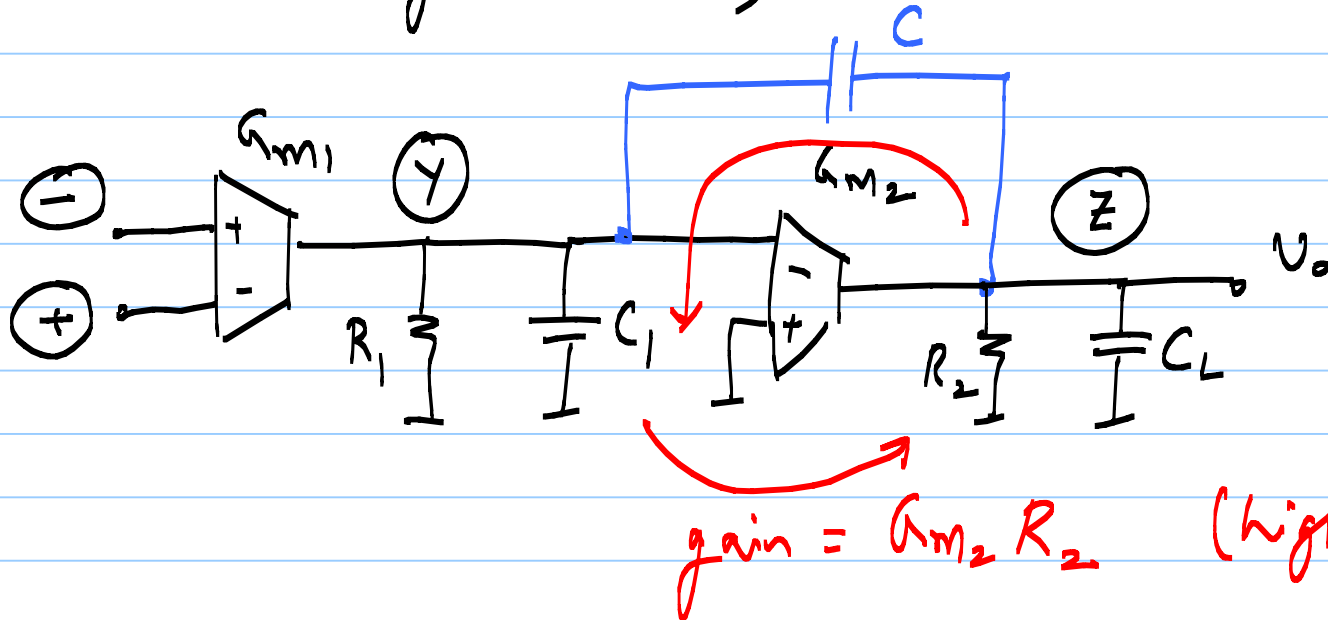
$$C_1 = C_{gs5} \quad ; \quad C_2 = C_L$$




G_{m2} reduces
due to AC
feedback
through C_f

$$C_1' \approx C_1 + \underbrace{G_{m2} R_2 C}_{\text{Miller Capacitance}}$$

$$p_{y'} \approx \frac{1}{R_1 C_1'} \ll p_y$$

↓
Dominant pole

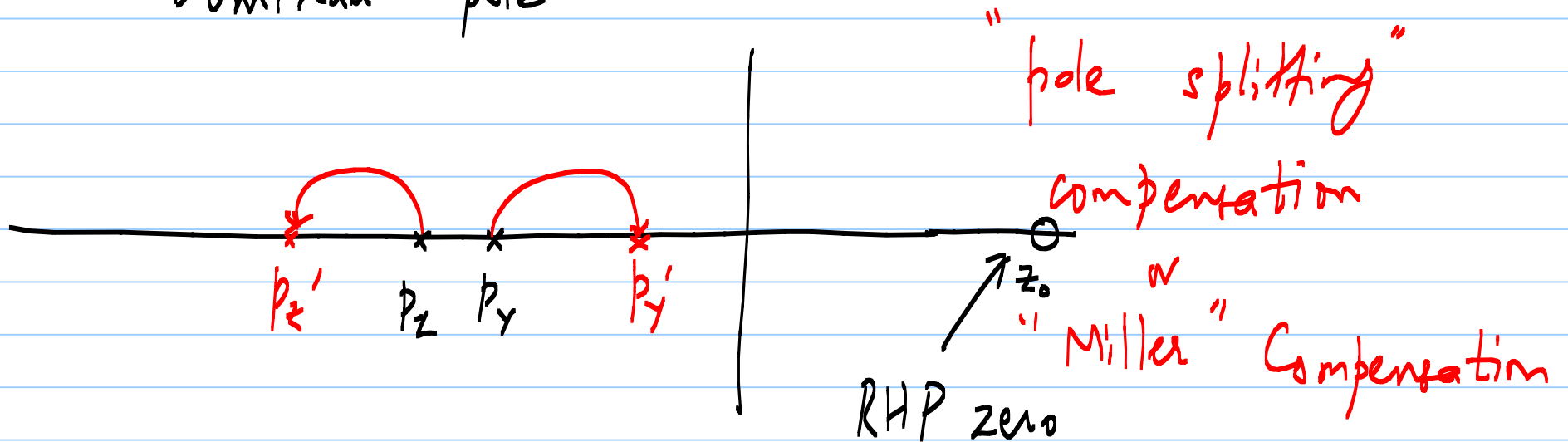

required value of C is small due to
Miller multiplication

HW

G_{out} of \rightarrow

