
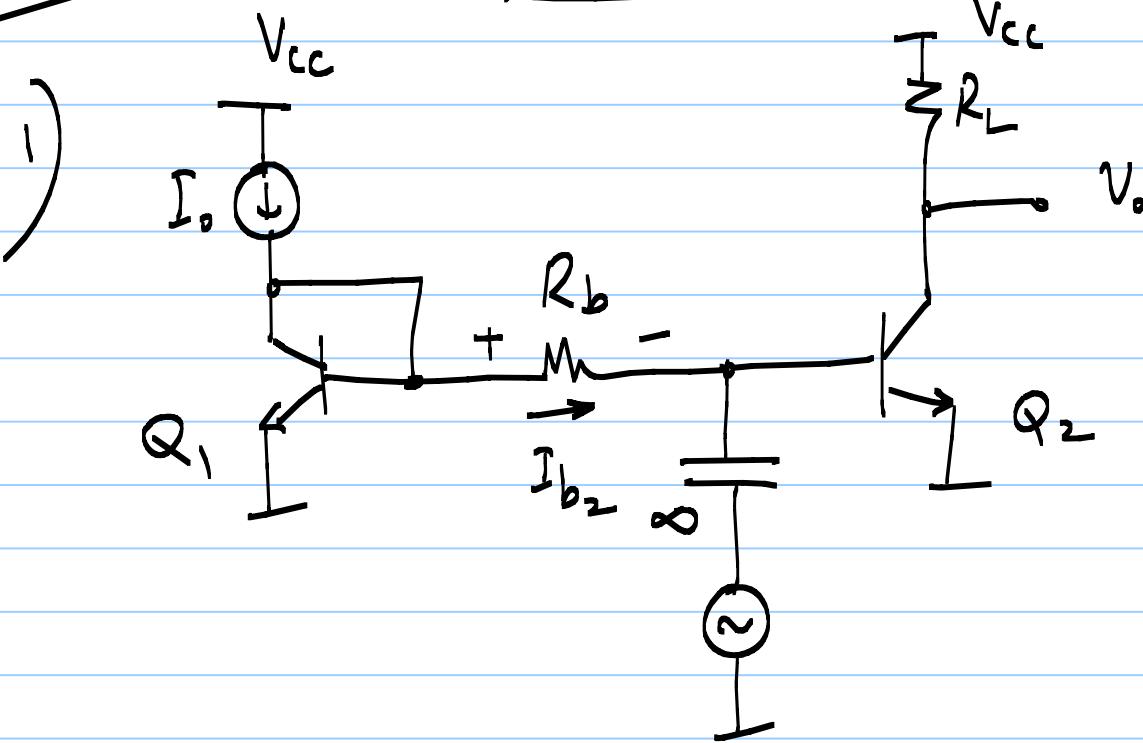


3/11/20


## Lecture 48

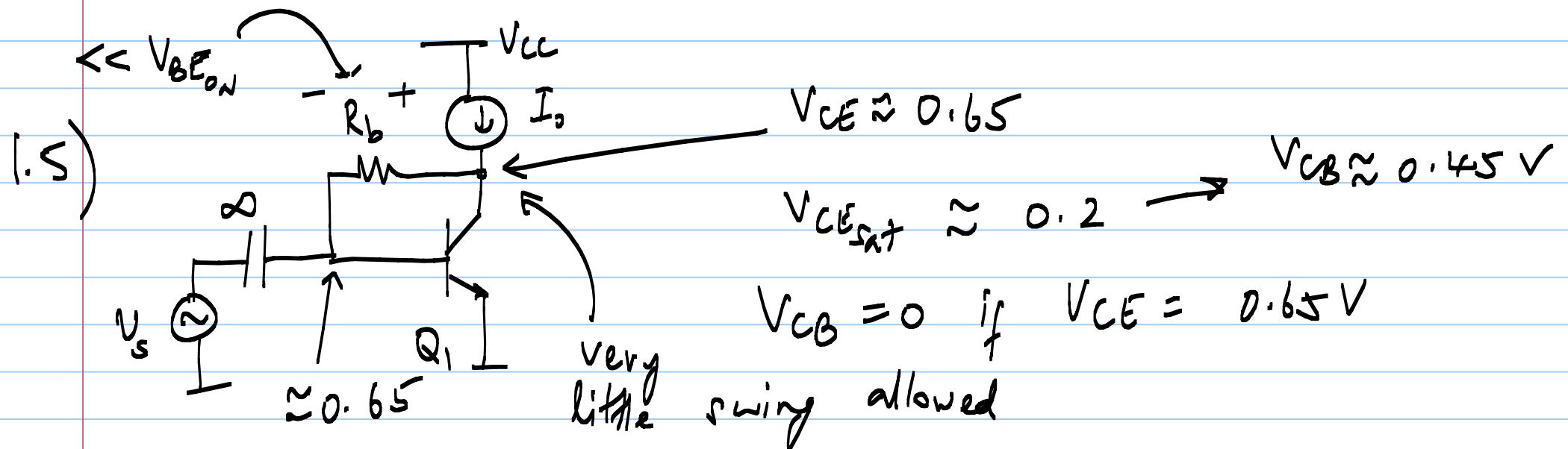

Not a good  
way of biasing.




2)

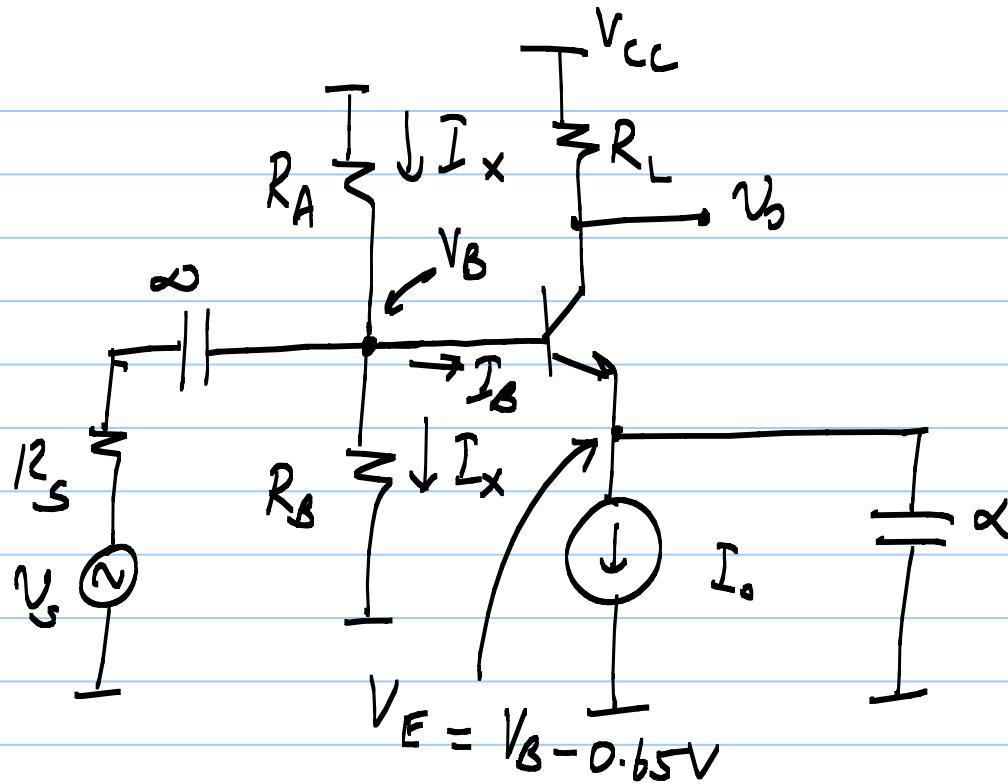

$$I_x > I_B$$

"Common Emitter  
Amplifier"


2.5)

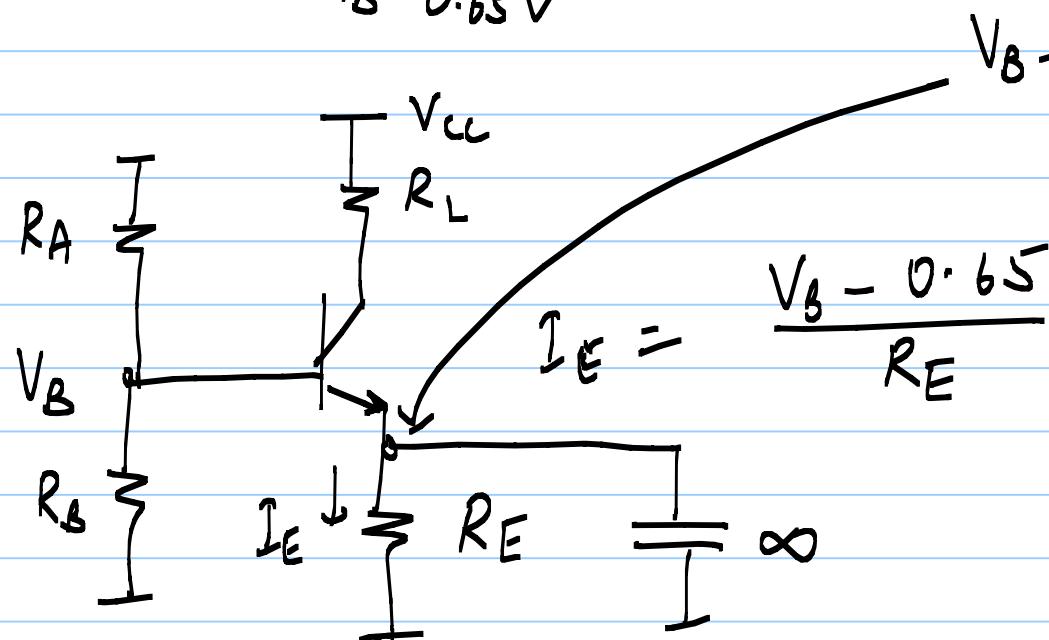

$$V_B - 0.65V$$

Circuits (3) & (4) - HW { require opamps}

4)

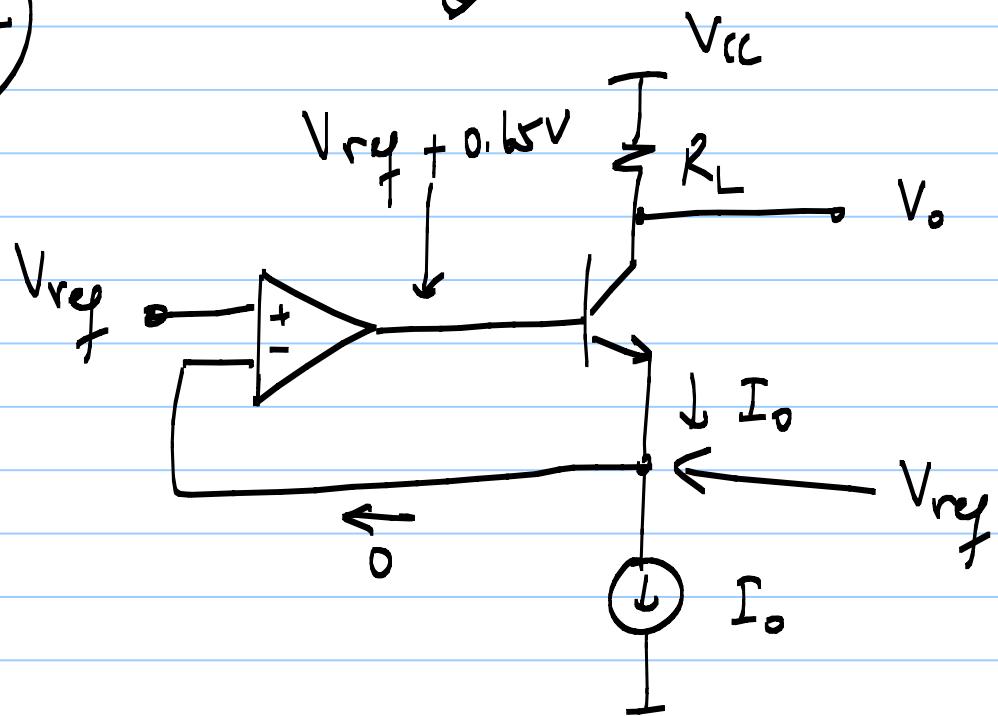

## Swing Limits

i) Saturation limit


$$V_{CE_{sat}} = 0.2 \text{ V}$$

e.g. for circuit (2):

$$V_C - V_E = 0.2 \text{ V}$$

$$V_{CC} - I_o R_L + A \underbrace{V_A \sin \omega t}_{-g_m R_L} - (V_B - 0.65 \text{ V}) = 0.2 \text{ V}$$

$A$  = gain of CE amplifier

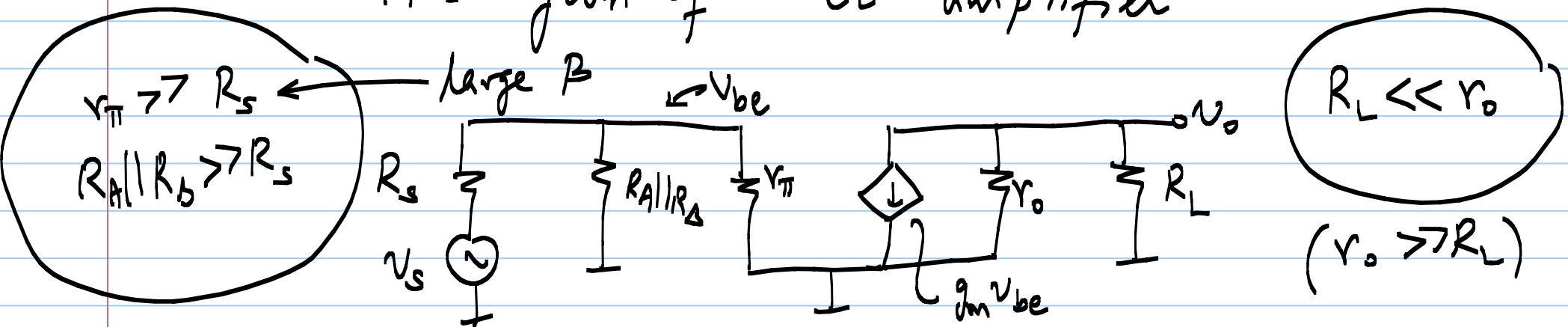

$$V_{be} \approx V_s$$

$$V_o = -g_m R_L V_s$$

$$A = \frac{V_o}{V_s} = -g_m R_L$$

2) Cut off limit

$$I_c = 0$$

$$I_o + g_m V_A \sin \omega t = 0 \Rightarrow V_A = \frac{I_o}{g_m}$$

