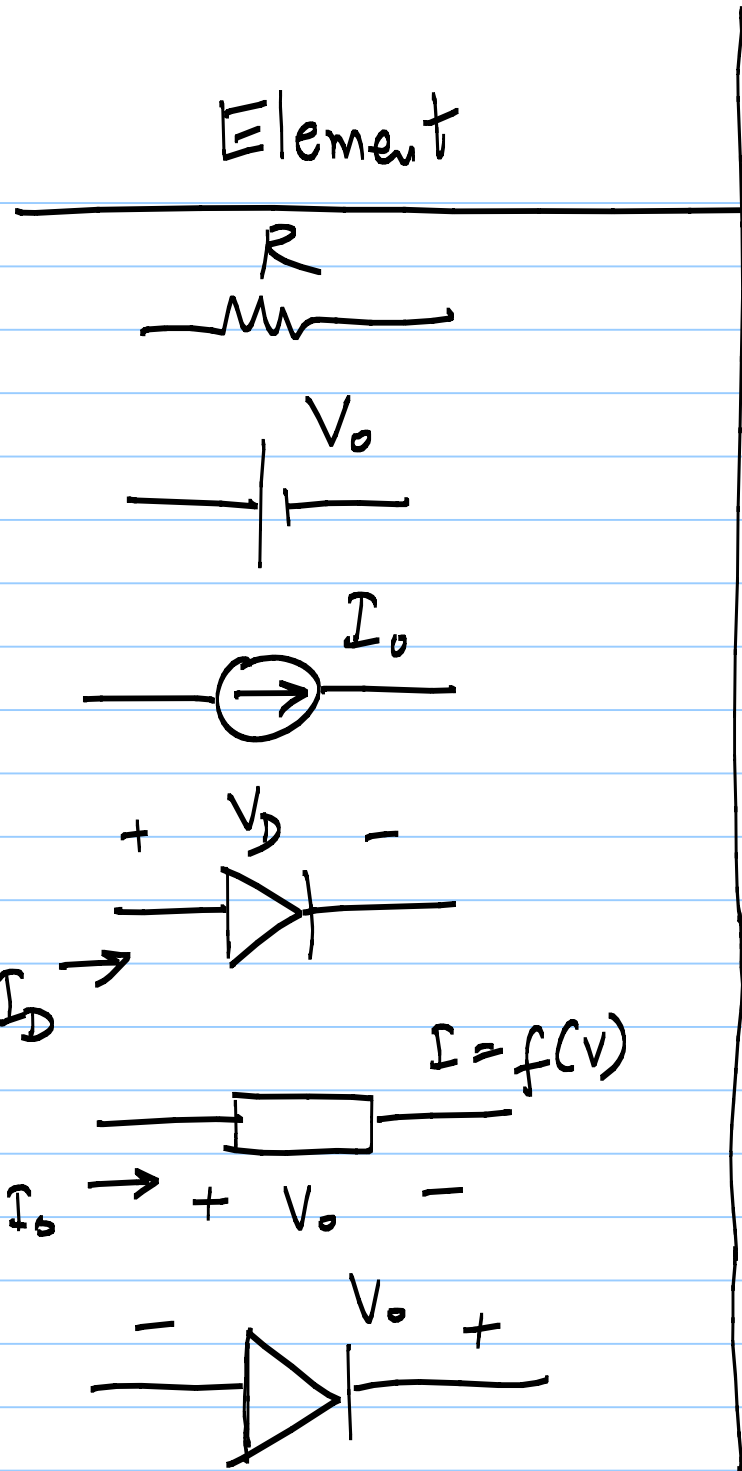



12/8/2020



Lecture 5

- 1) Find operating point
 - solve non-linear equations
 - incremental ΔV_s & ΔI_s are dependent on the Q-pt (r_i 's are dep. on Q-pt.)
- 2) Draw the incremental equivalent circuit (linear network) and solve for ΔV_s & ΔI_s
- 3) Total V_s and I_s
= Quiescent V/I + Incremental V/I




Incremental equivalent

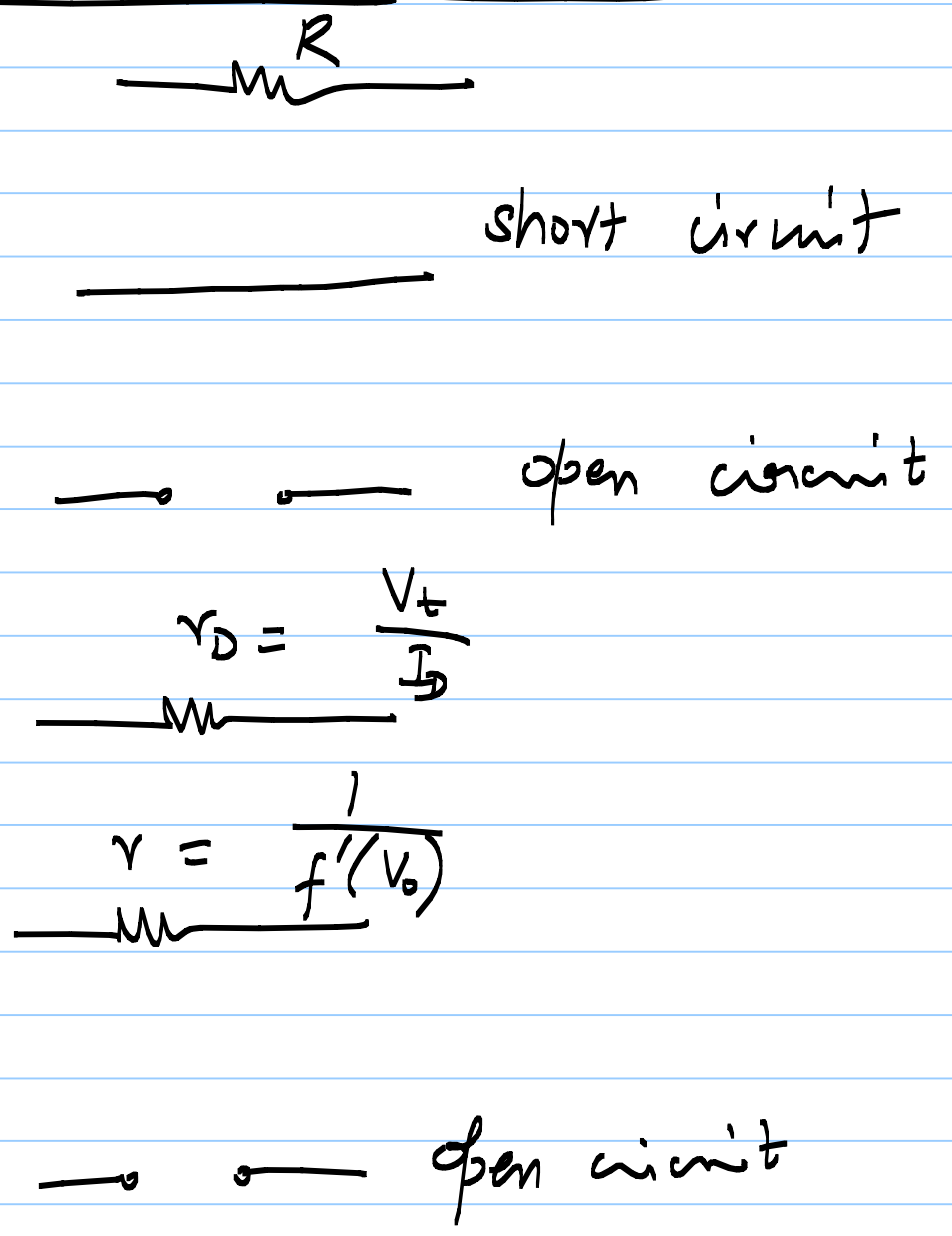

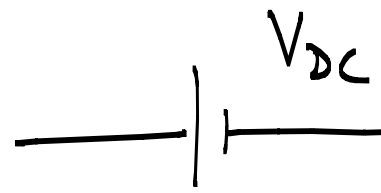
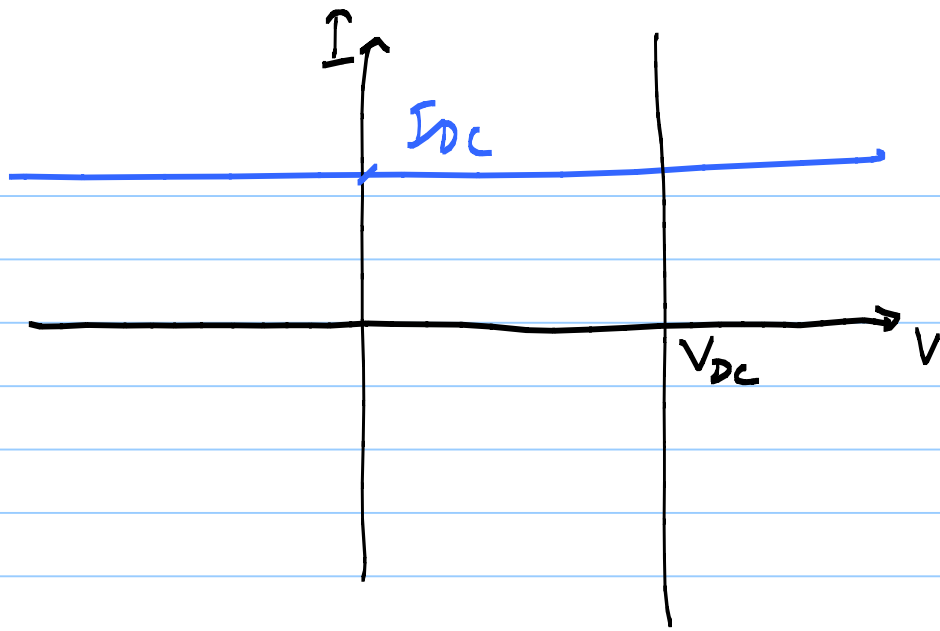


$$r_{V_{dc}} = \frac{1}{f'(V)} = 0$$


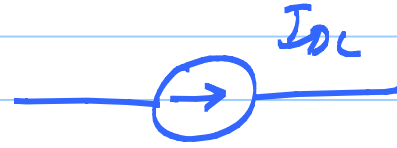



$$r_{I_{dc}} = \frac{1}{f'(V)} = \infty$$

HW :

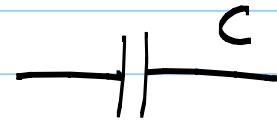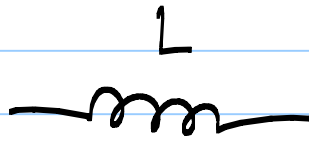

Th. eq.

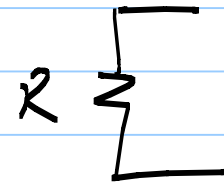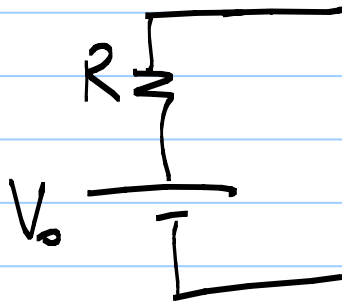


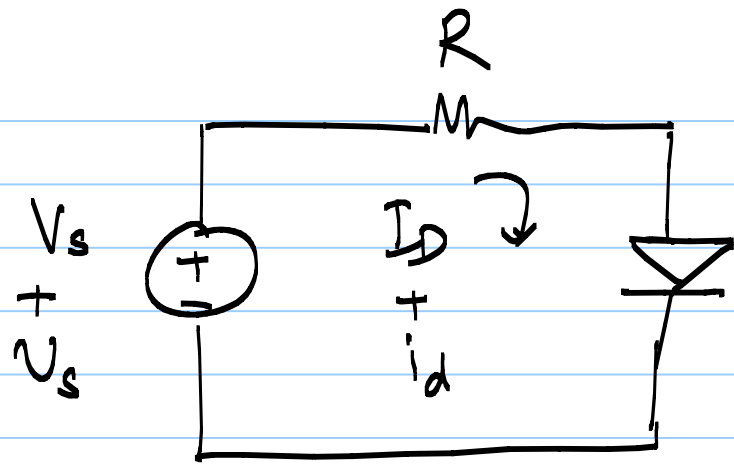

$$+ u_d + u_d$$

$$-$$

Is it possible
for
 $u_d > u_s$?

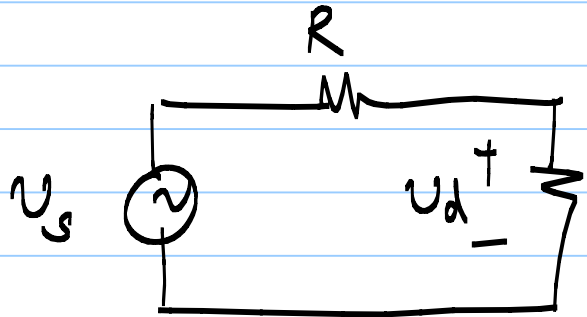


$$r_d = \frac{V_t}{I_D}$$

$$u_d = \frac{r_d}{R + r_d} \cdot u_s$$


small-signal gain = $\frac{u_d}{u_s}$

$$= \frac{r_d}{R + r_d}$$

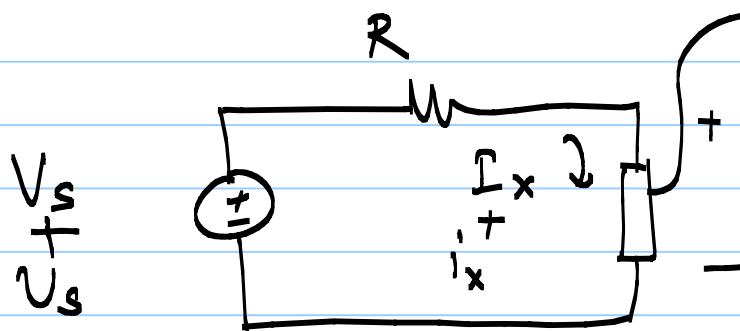

$$I = f(V)$$

$$r_x = \frac{1}{f'(V_x)}$$

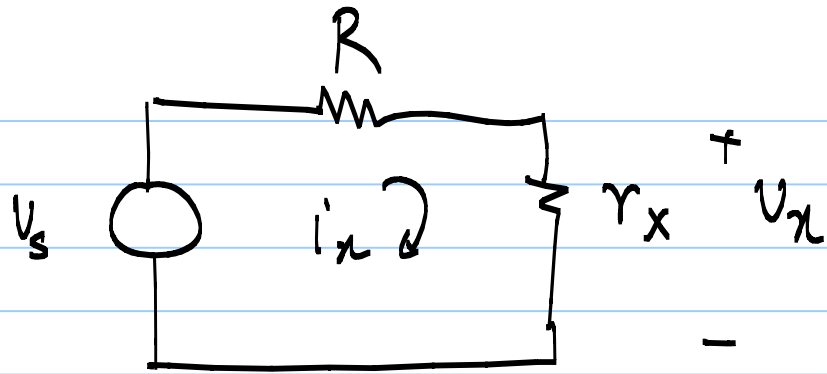

$$\frac{v_x}{v_s} = \frac{r_x}{R + r_x}$$


If

r_x is negative, it is possible for




$\left| \frac{v_x}{v_s} \right|$ to be > 1


slope of $f(v)$ is negative

"Tunnel Diode"

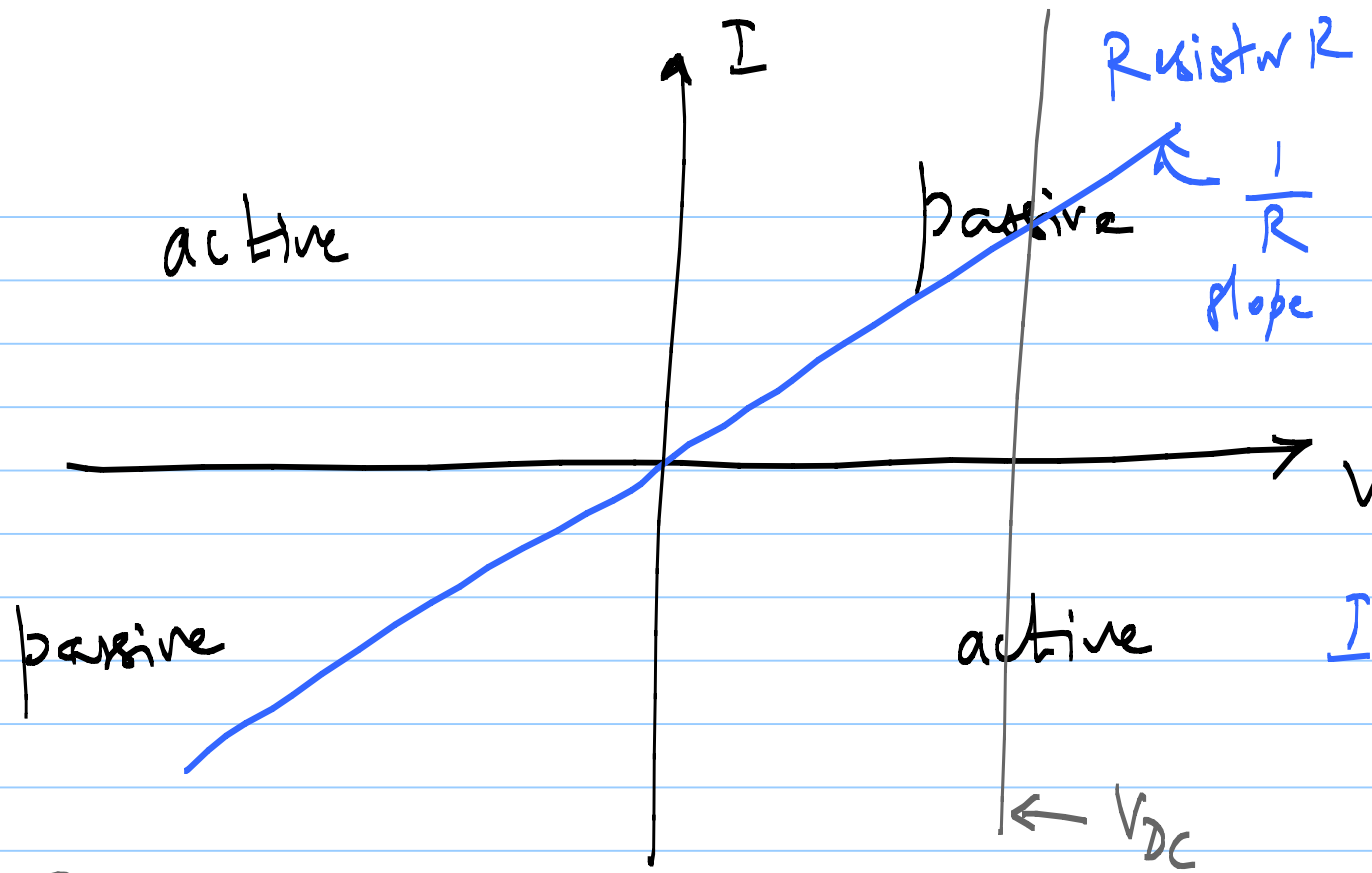

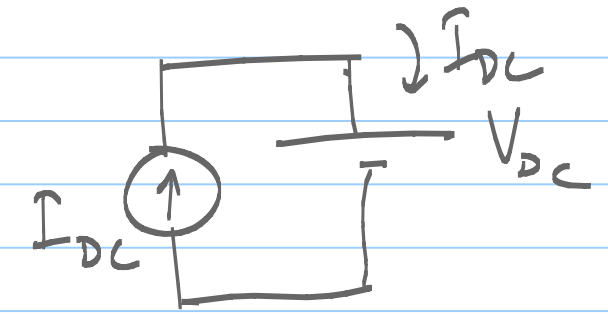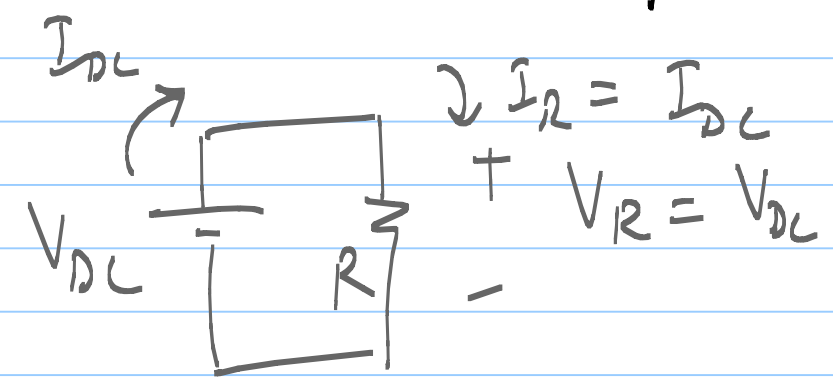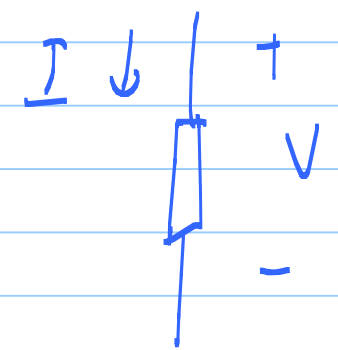absorbs or
dissipates
electrical
power
= passive



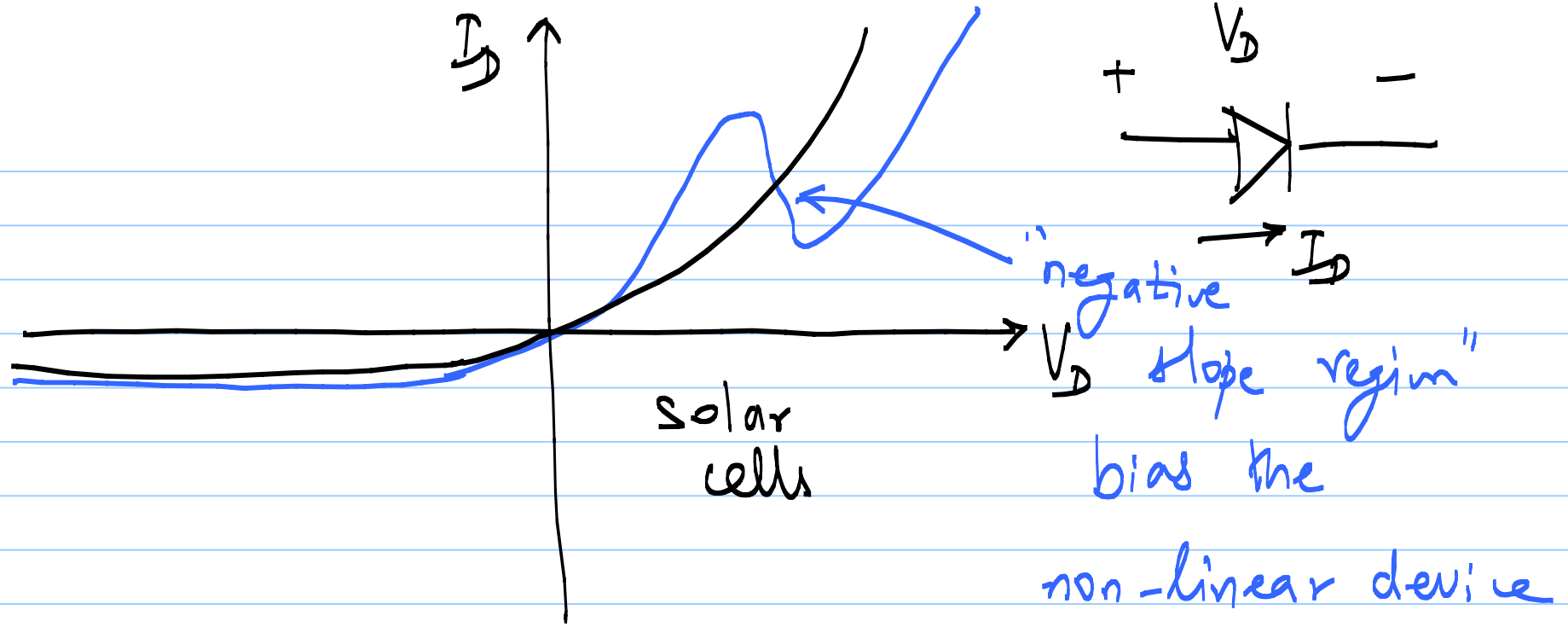

1) Is it possible to get "gain" from purely linear passive devices? in this region
to get "gain"


* No power gain possible

* v or i gain possible (transformers...)

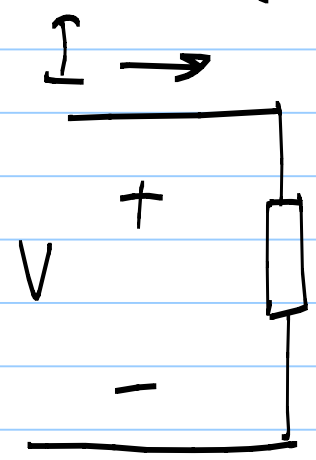2) Non linear passive devices?

→ incremental / small-signal voltage
and power gain possible

→ Battery power is used up
(in overall power)




2-T
1-port

$$Y = \frac{1}{f'(V_Q)}$$

ss parameter describes
behaviour

2-port networks

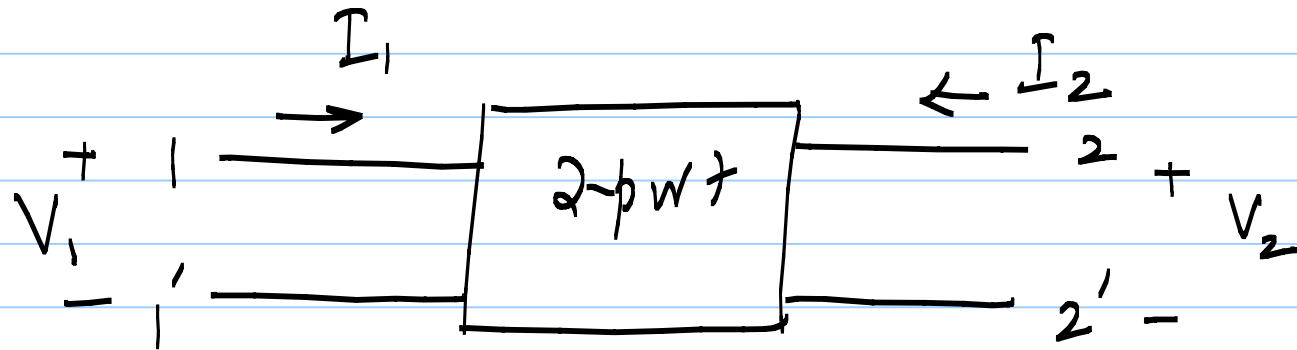

4 parameters
required
to describe
2-port network

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \underbrace{\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}}_{\text{(impedance) } Z\text{-parameters}} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

(impedance) Z -parameters

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \underbrace{\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}}_{\text{(Admittance) } Y\text{-parameters}} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

(Admittance)
 Y -parameters