
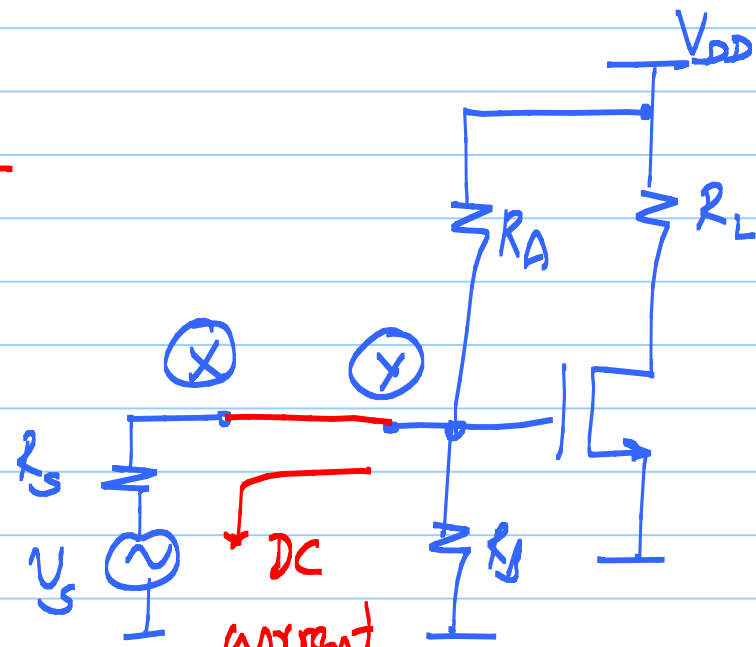
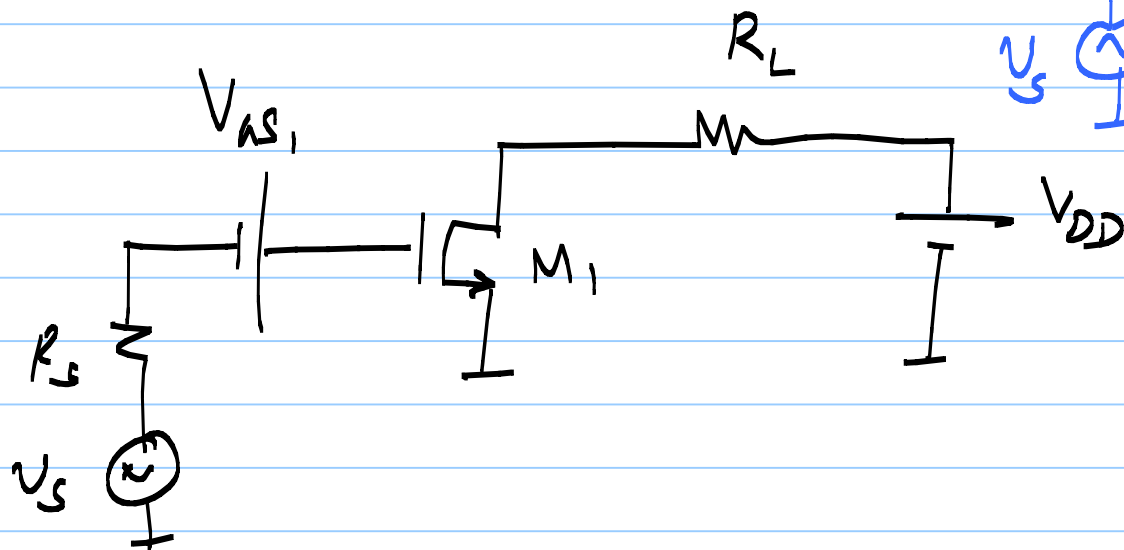


19/8/2020

Lecture 9

NL 2-port (incremental view)

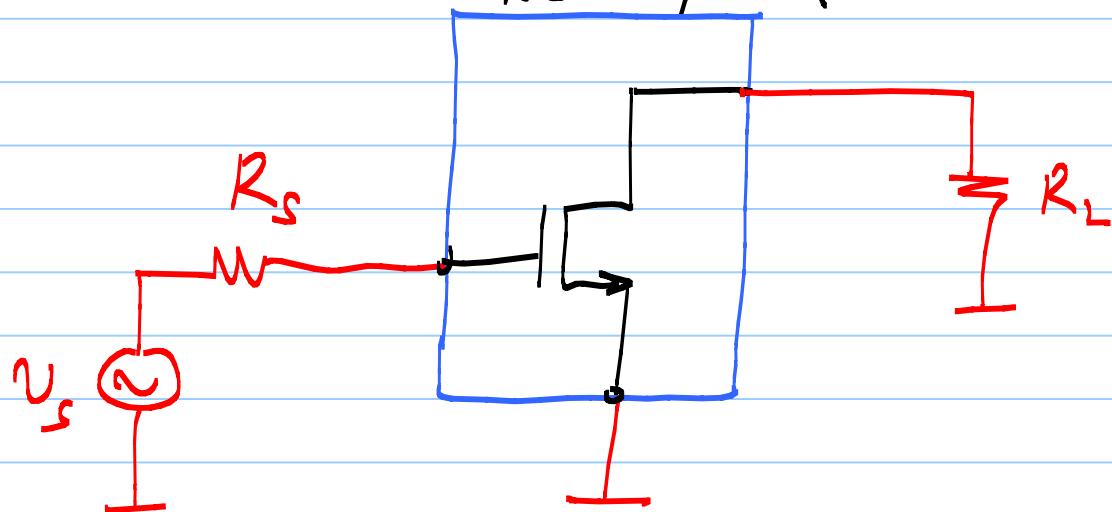


DC current flow

* Might disturb op pt. of preceding circuit

* V_{GS1} itself changes


$$V_{GS1}' = \frac{R_A || R_S}{R_A + 2R_S || R_S} \cdot V_{DD}$$

* We want no DC current flow through R_L


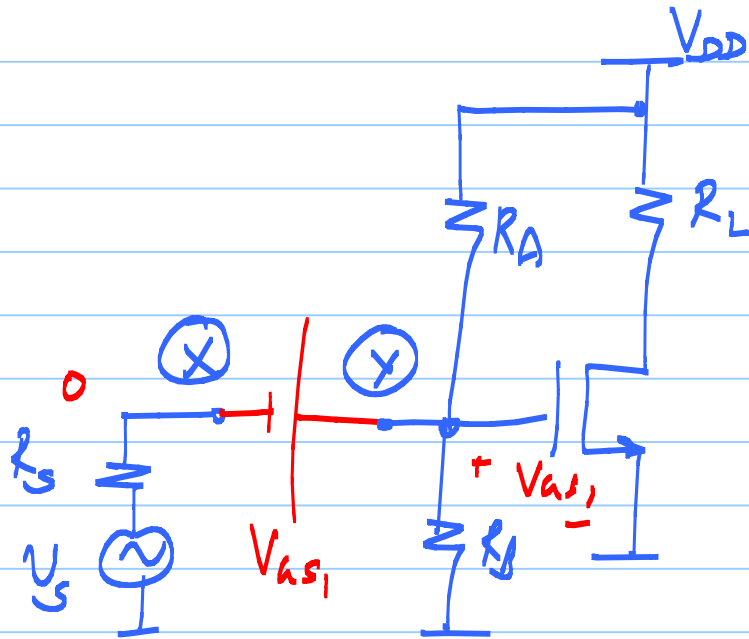


Ensure $V_x = V_y$
(N)



Don't add additional battery

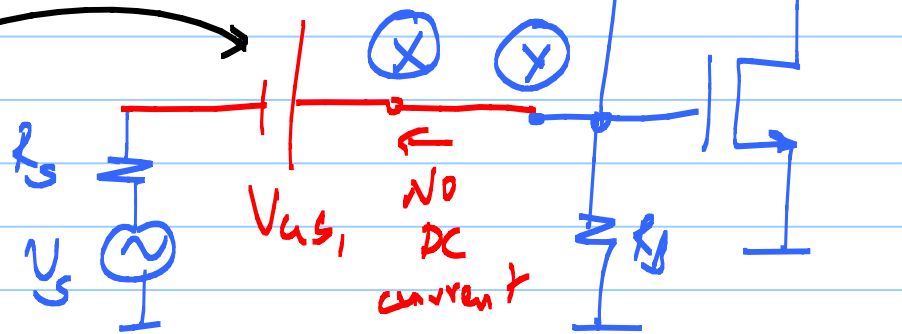


$V_x = V_y$

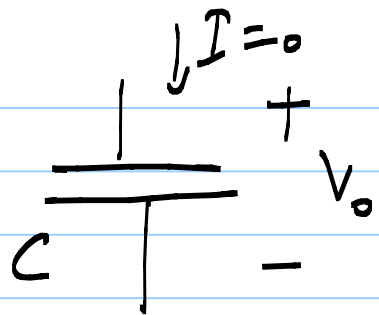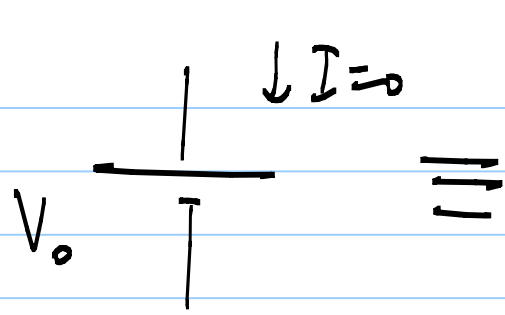

iff no current is drawn

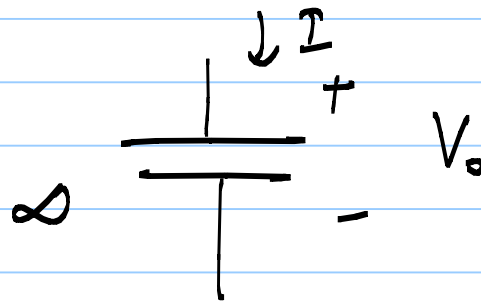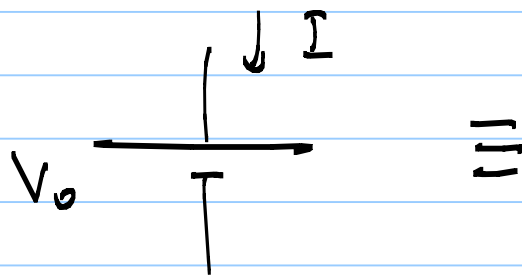


even if you draw current

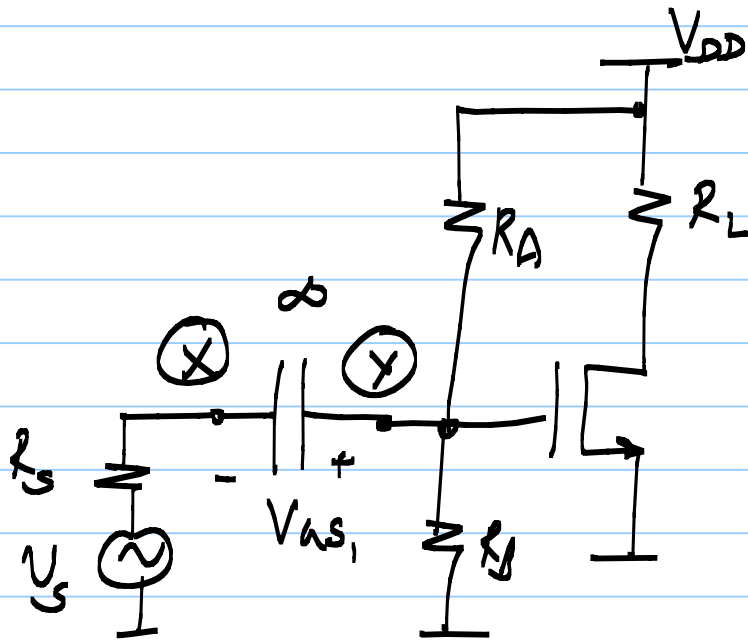

MOSFET
Amplifier

Common-Source

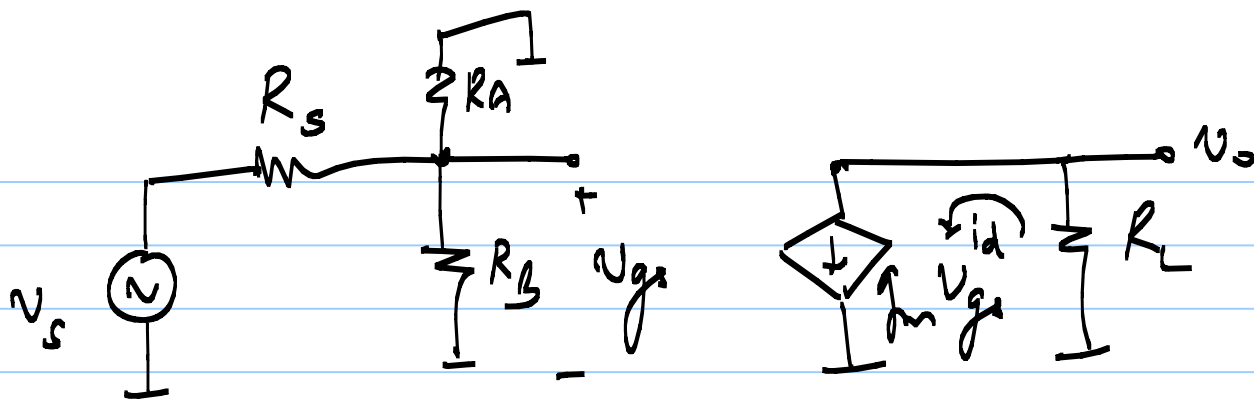

$$u_{gs} = \frac{R_A \parallel R_B}{R_s + R_A \parallel R_B} \cdot u_s$$

$y_{11} \neq 0$

$$u_o = -g_m R_L \cdot u_{gs} = -g_m R_L \cdot \frac{R_A \parallel R_B}{R_s + R_A \parallel R_B} \cdot u_s$$

1) Choose $R_A \parallel R_B \rightarrow R_s$


$$\frac{R_B}{R_A + R_B} \cdot u_{DD} = u_{GS}$$

2) then $\frac{u_o}{u_s} \approx -g_m R_L$



$$i_d = g_m v_{gs} = g_m \cdot \left(\frac{R_A \parallel R_S}{R_S + R_A \parallel R_B} \right) \cdot v_s$$

$$v_d = v_o = -i_d R_L$$

3) Suppose: No DC current through R_L :

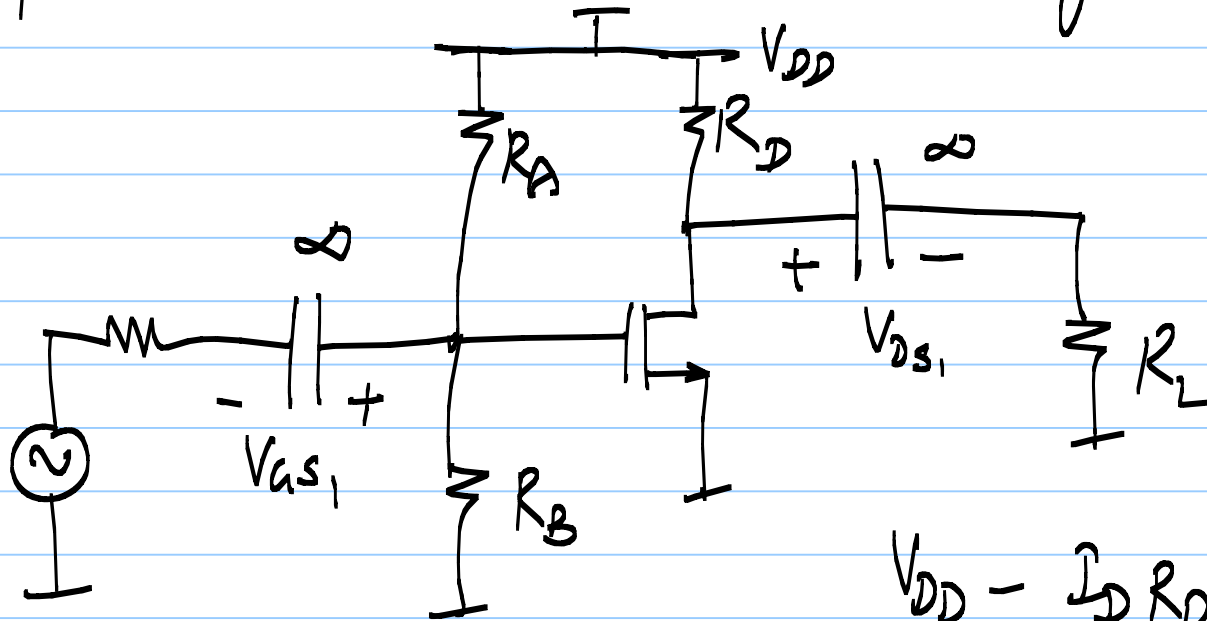


$$V_{DD} - I_D R_D = V_{DS}$$

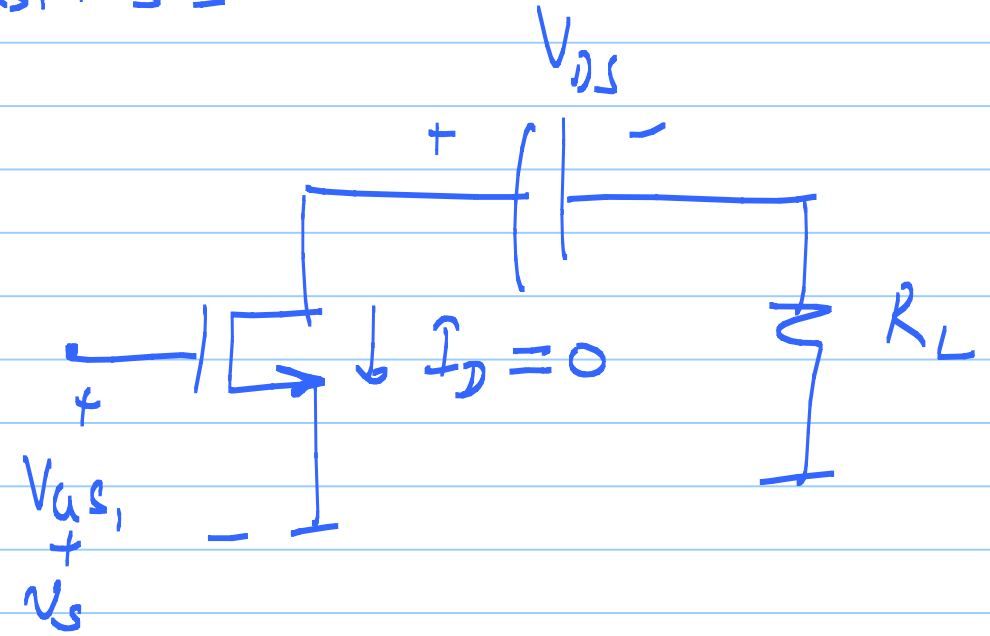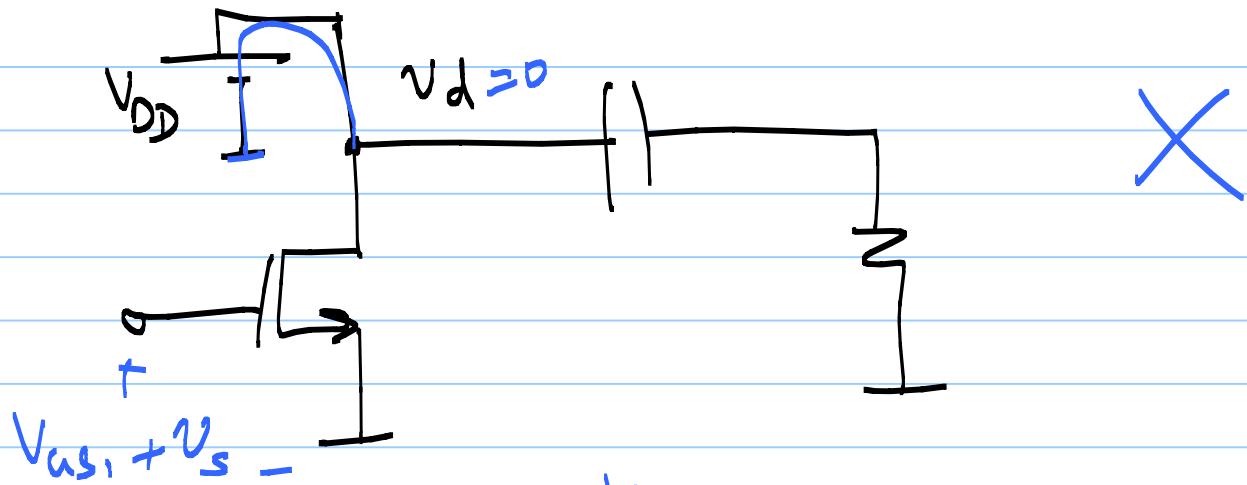

Assume $V_{DS1} > V_{GS1}$


CSA

$$\frac{v_o}{v_s} = -g_m(R_D || R_L)$$

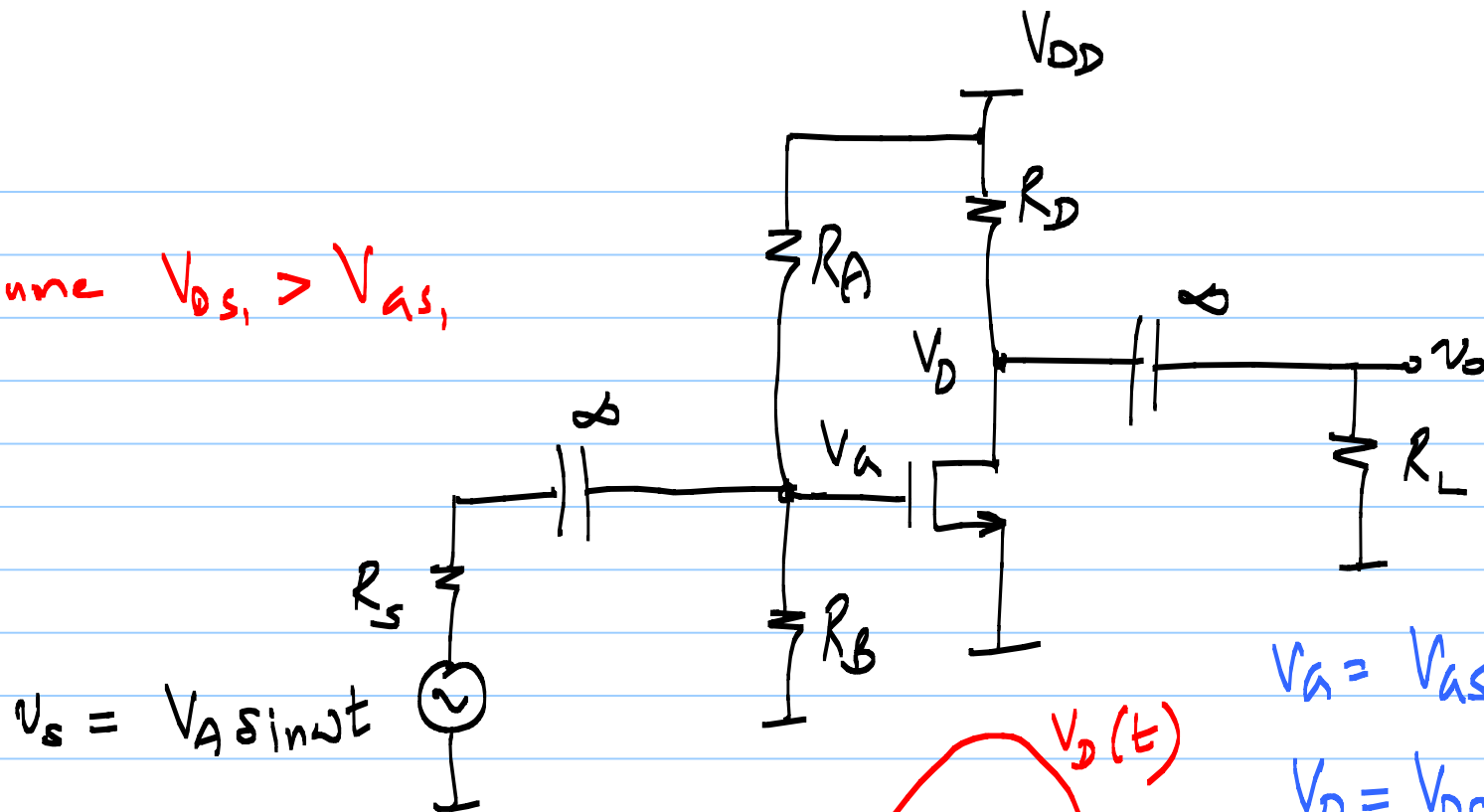

$$v_G = V_{GS1} + V_A \sin \omega t$$


$$v_D = V_{DS1} - g_m(R_D || R_L) V_A \sin \omega t$$

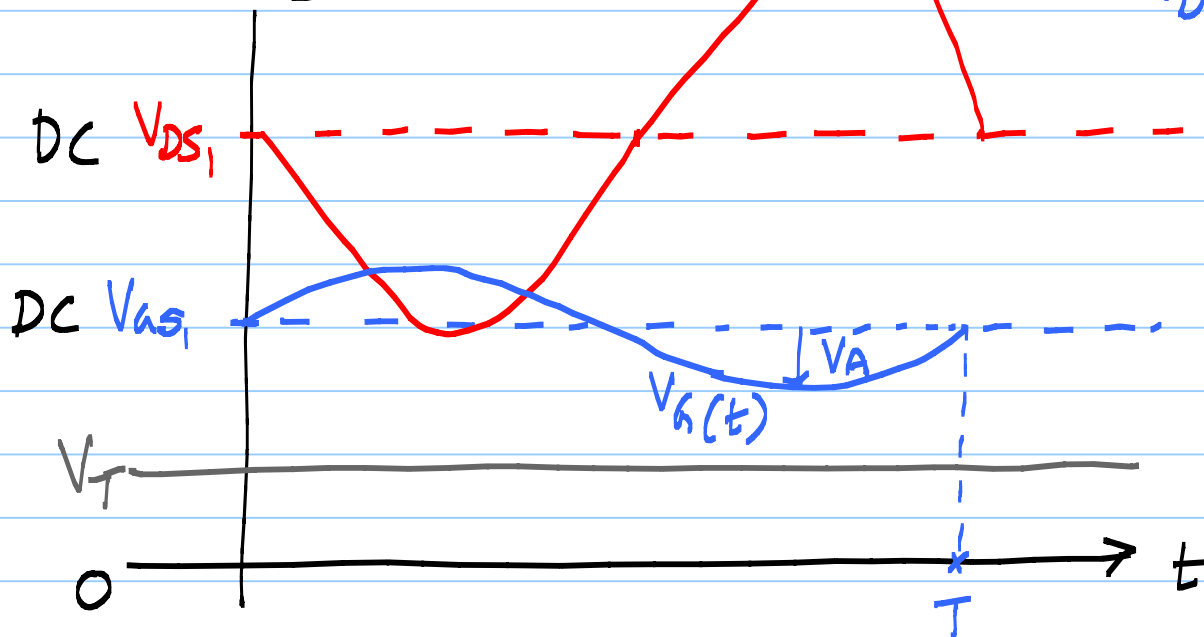

$$= V_{DS1} - G V_A \sin \omega t$$

Triode boundary

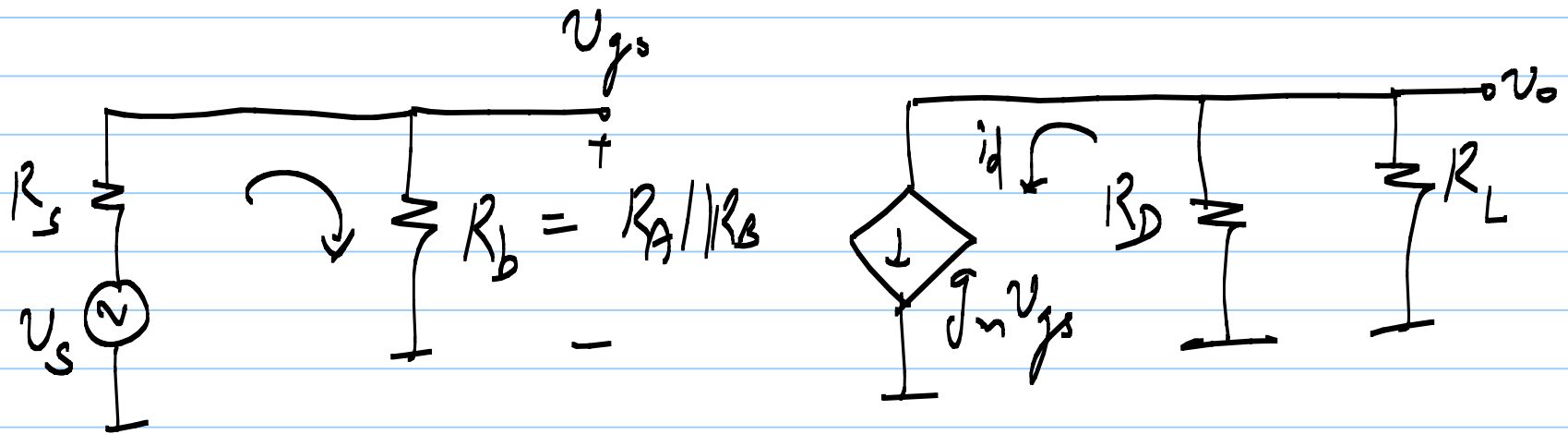$V_{DS} > V_{GS} - V_T$
at all time
instants.



$$v_{gs} = \frac{R_b}{R_s + R_b} \cdot v_s \approx v_s \quad \text{if } R_s \ll R_b$$

$$i_d = g_m v_{gs} \approx g_m v_s$$

$$v_o = -i_d \cdot (R_D \parallel R_L) = -g_m v_s (R_D \parallel R_L)$$

$$\frac{v_o}{v_s} = -g_m (R_D \parallel R_L) = -G$$