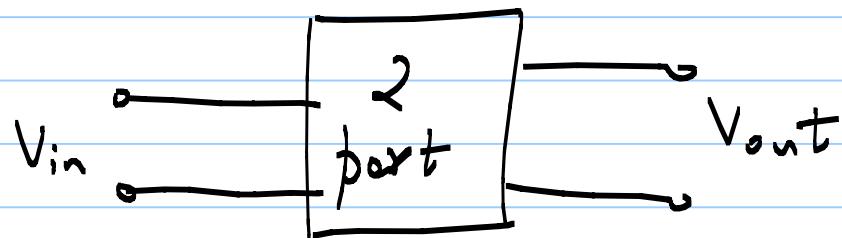


5/8/2020

Note Title

Lecture 2


05-08-2020



Is this linear?

Based on Superposition

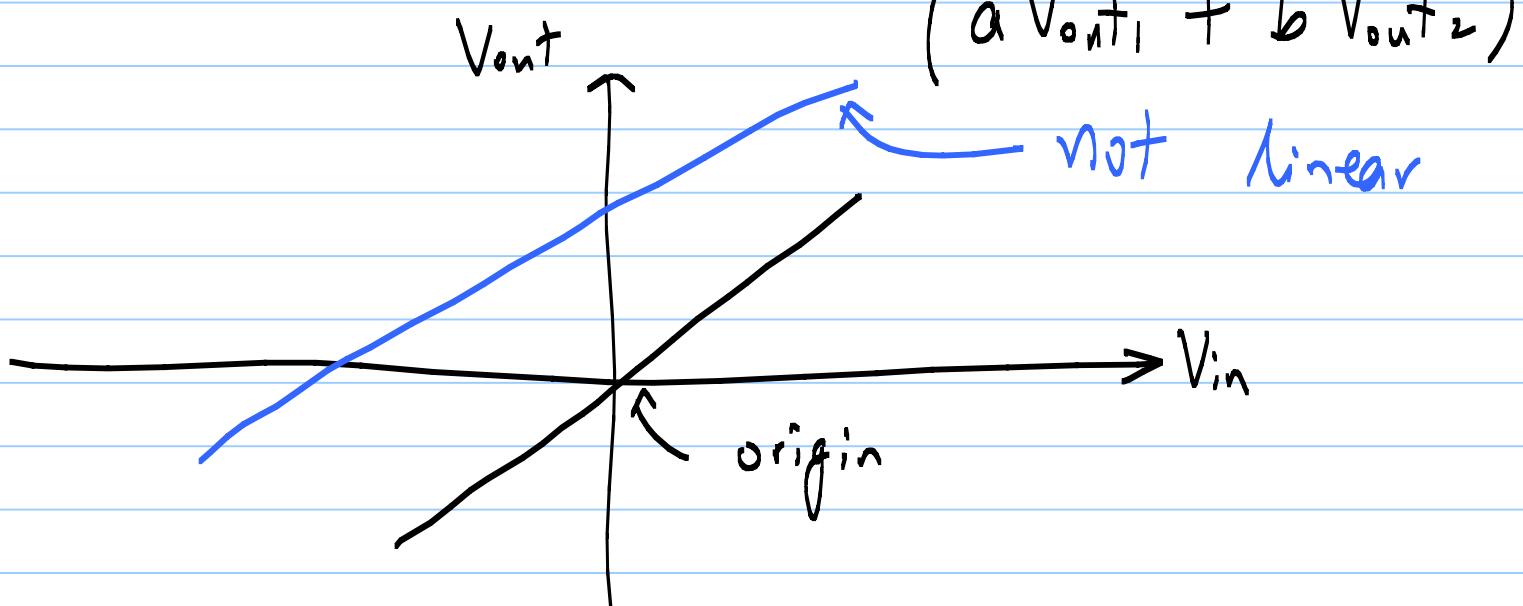
$$\begin{aligned} V_{in_1} \rightarrow V_{out_1} \\ V_{in_2} \rightarrow V_{out_2} \end{aligned} \quad \left. \begin{array}{l} V_{out_1} \\ V_{out_2} \end{array} \right\} \quad \left. \begin{array}{l} (aV_{in_1} + bV_{in_2}) \\ (aV_{out_1} + bV_{out_2}) \end{array} \right\} \quad \downarrow \quad \text{for all } a, b, V_n, V_{in_2}$$




- * LTI systems characterized by Impulse Response
- * All practical systems are Non-linear

Linear Elements (2-terminal 1-port systems)
"elements"


linear elements $R, L, C \rightarrow$ defined by $V-I$ relationship

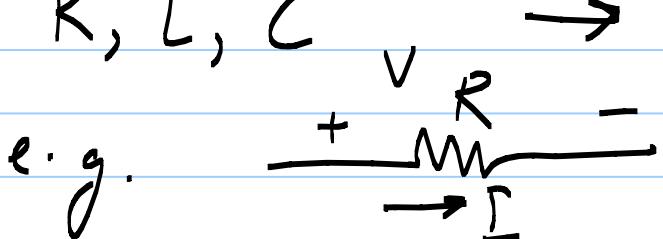e.g.  $I = \frac{V}{R}$

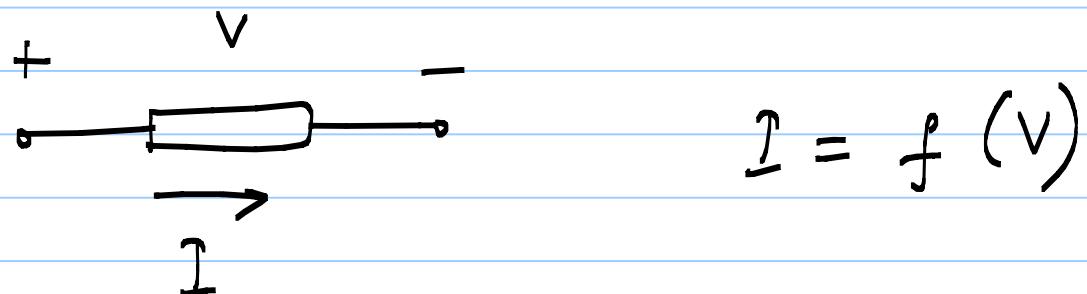

Nonlinear 2-T element

Diode :

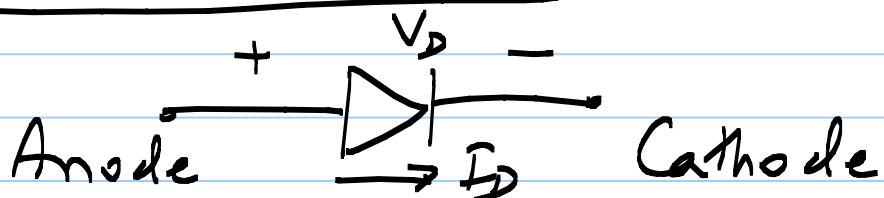

From JSD theory:

$$I_D = I_s \left[\exp \left(\frac{V_D}{V_t} \right) - 1 \right]$$

saturation current

thermal voltage

$$V_t = \frac{kT}{q} \approx 25mV @ 300K$$

If $V_D > 0 \Rightarrow$ Diode is "forward biased"

$V_D < 0 \Rightarrow$ "reverse biased"

Some approximations:

1) If $V_D \gg$ few V_{t_s}


$$\exp\left(\frac{V_D}{V_{t_s}}\right) \gg 1$$

$$I_D \approx I_s \exp\left(\frac{V_D}{V_{t_s}}\right)$$


$$V_D = V_{t_s} \ln\left(\frac{I_D}{I_s}\right)$$

2) If $\frac{V_D}{V_{t_s}} \ll 0$, $\exp\left(\frac{V_D}{V_{t_s}}\right) \ll 1$

$$\Rightarrow I_D \approx -I_s$$

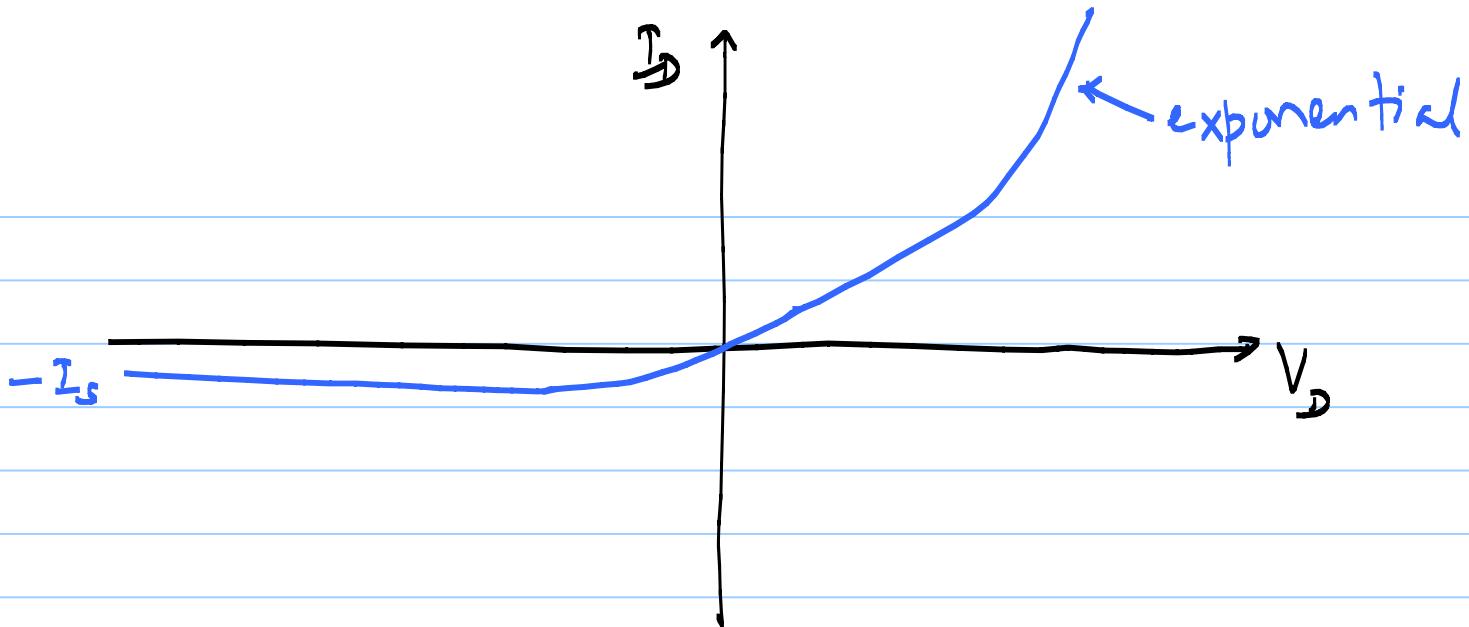

Circuit Analysis w/ diodes

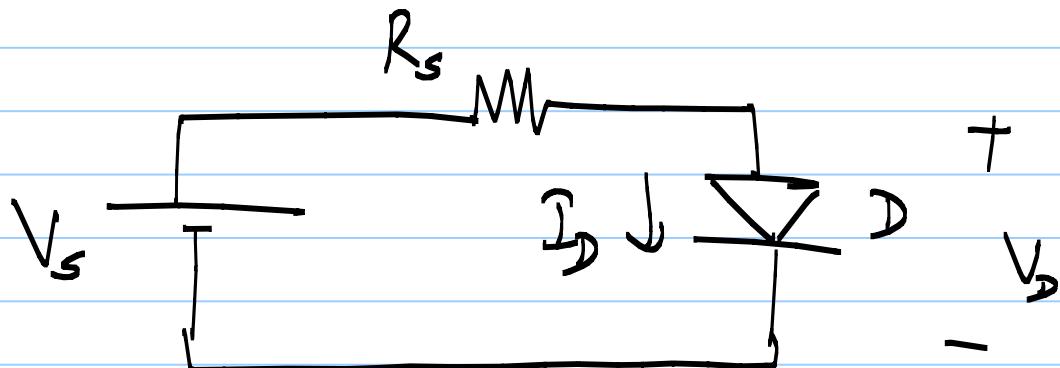

KVL :


$$V_s = V_{R_s} + V_D$$

$$V_s = I_D R_s + V_D = I_D R_s + V_T \ln \left(1 + \frac{I_D}{I_s} \right)$$

Solution

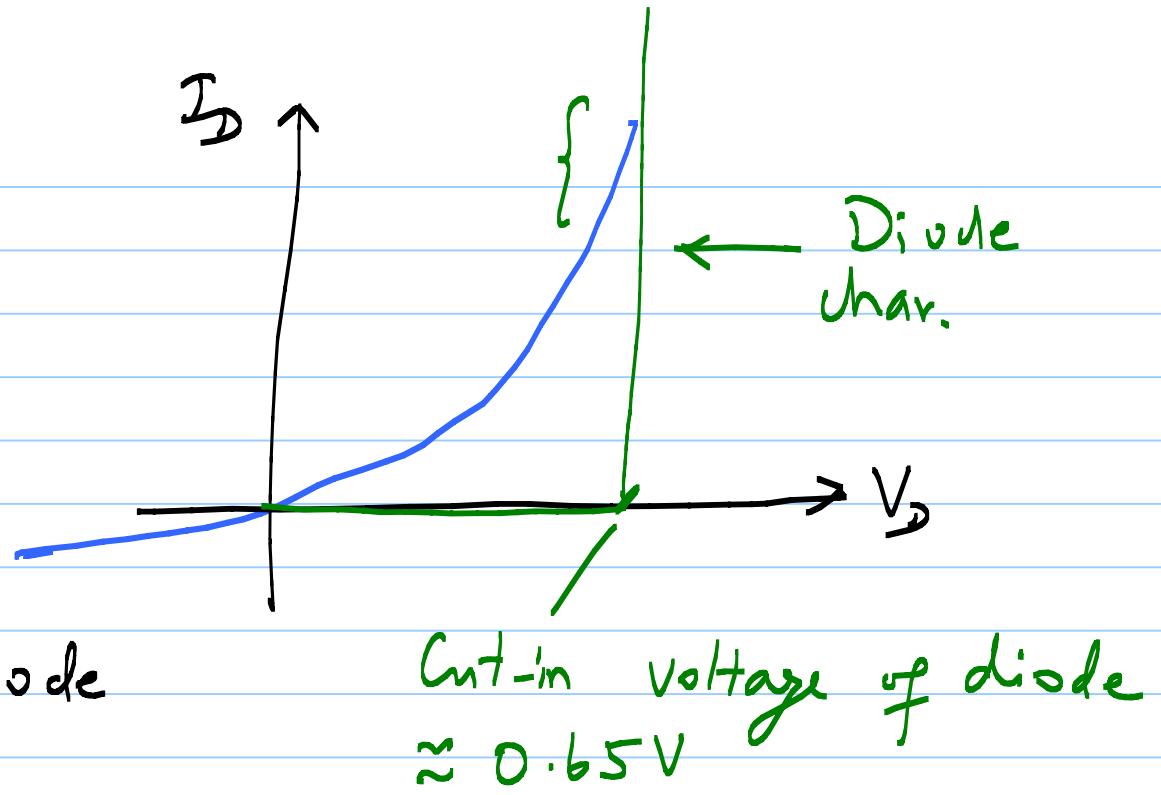
- 1) Zeroth order:

Assume that the voltage drop across a forward biased diode $\approx 0.65V$



$$I_D \approx \frac{V_S - 0.65}{R_s}$$

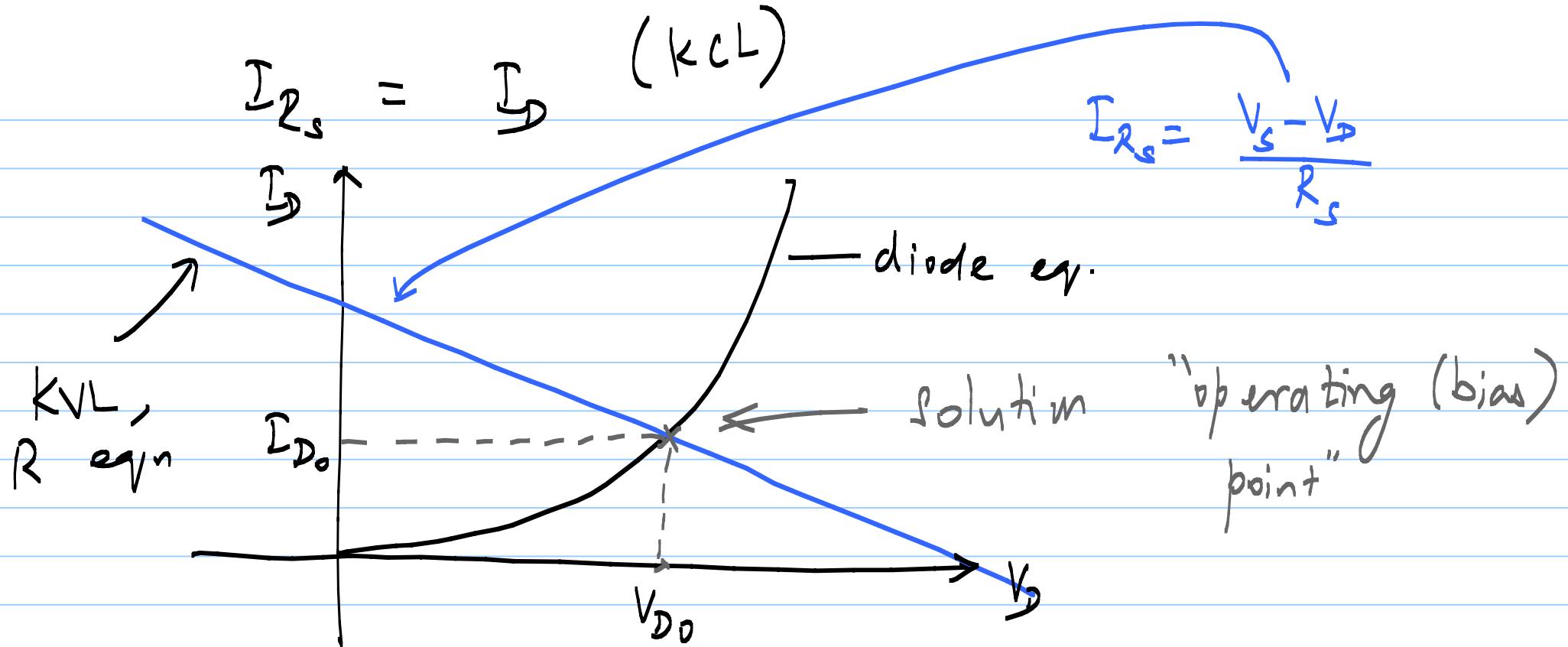- 2) Exact solution : Iteration (N_L characteristic)
- 3) Numerical Solution
- 3) Graphical solution in $I_D - V_D$ plot





$$I_f \quad V_s \rightarrow V_s' = V_s + \Delta V_s$$

new op. pt. ?

6/8/2020

Lecture 3

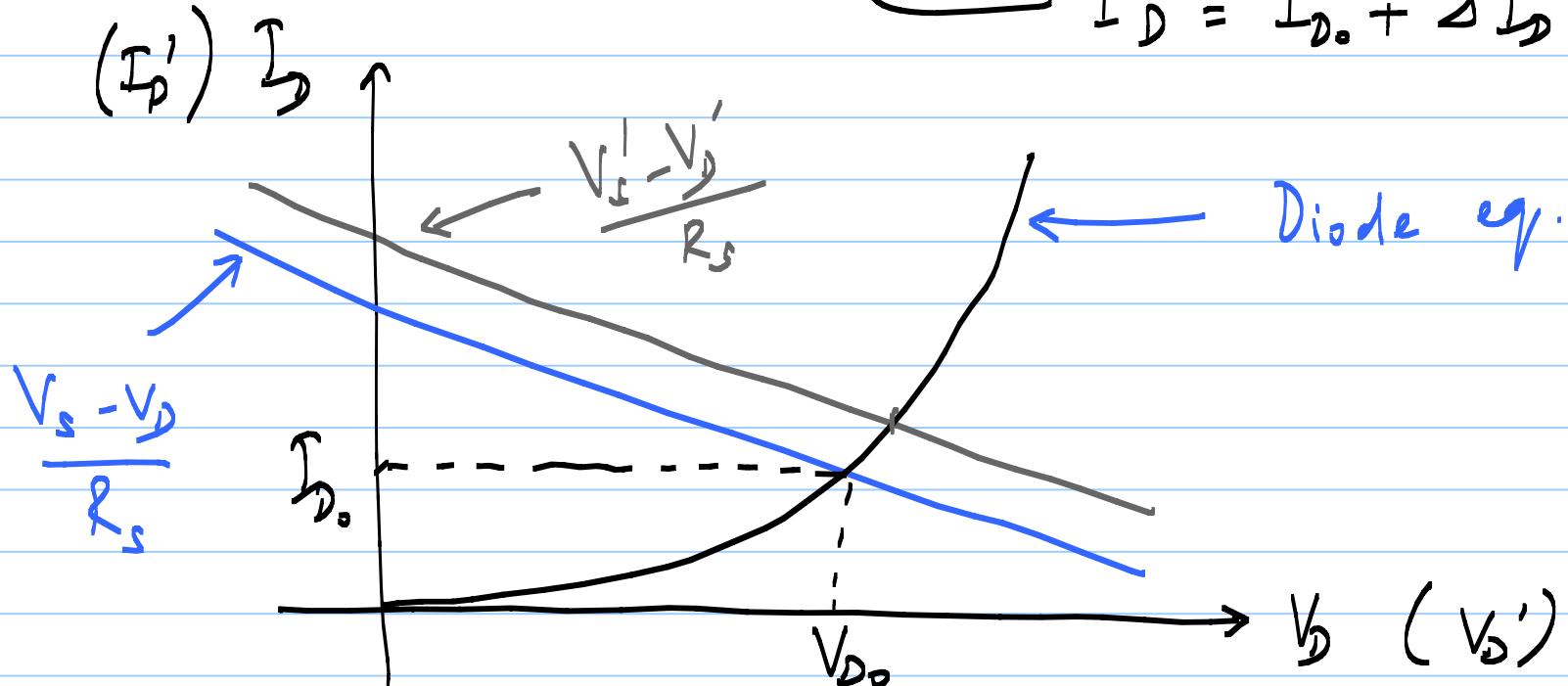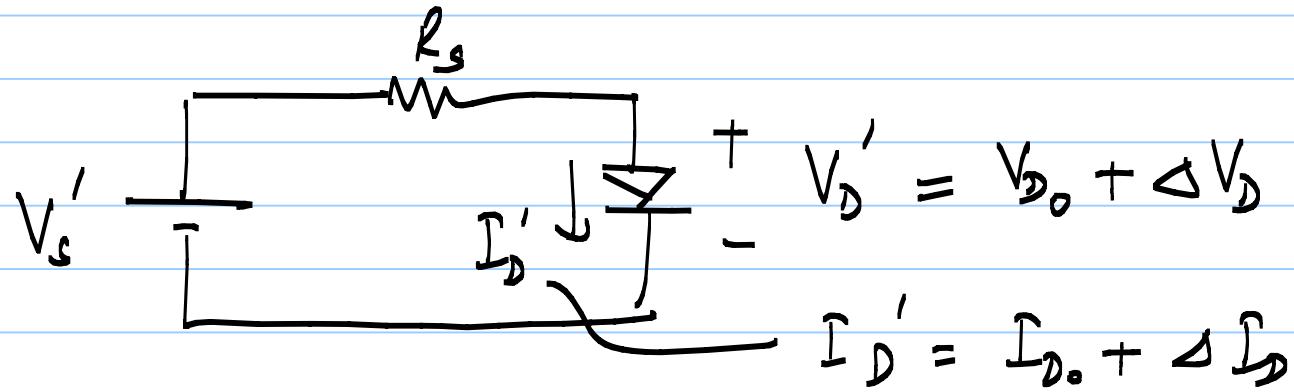* $I_f V_s' = V_s + \Delta V_s$ What is V_D' , I_D'
 \curvearrowleft incident



Orig.

$$\frac{V_s - V_{D_0}}{R_s} = I_{D_0} = I_s \left[\exp \left(\frac{V_{D_0}}{V_t} \right) - 1 \right]$$

New

$$\frac{V_s' - V_b'}{R_s} = I_D' = I_s \left[\exp \left(\frac{V_b'}{V_t} \right) - 1 \right]$$

$$\frac{(V_s + \Delta V_s) - (V_{D_0} + \Delta V_b)}{R_s} = I_{D_0} + \Delta I_D$$

$$= I_s \left[\exp \left(\frac{V_{D_0} + \Delta V_b}{V_t} \right) - 1 \right]$$

$$\frac{V_s - V_{D_0}}{R_s} + \frac{\Delta V_s - \Delta V_{D_0}}{R_s} = I_{D_0} + \Delta I_D$$

= ? — Taylor series
expantion around
(V_{D_0}, I_{D_0})

for $y = f(x)$ around x_0

$$y = \sum_{n=0}^{\infty} \frac{f^{(n)}(x_0)}{n!} \cdot (x - x_0)^n$$

$$= f(x_0) + f'(x_0) \cdot (x - x_0)$$

oper. pt.



$$+ \left(f''(x_0)/2 \right) \cdot (x - x_0)^2 + \dots$$

$$I_s \left[\exp \left(\frac{V_{D_0} + \Delta V_D}{V_T} \right) - 1 \right] = I_s \left[\exp \left(\frac{V_{D_0}}{V_T} \right) - 1 \right]$$

+

$$\frac{I_s}{V_T} \exp \left(\frac{V_{D_0}}{V_T} \right) \cdot (\Delta V_D)$$

$$+ \dots \rightarrow \Delta V_D^2, \Delta V_D^3 \dots$$


* For small increments (ΔV_D etc.), neglect

$$\Delta V_D^2, \Delta V_D^3 \dots$$


$$\frac{V_S - V_{D_0}}{R_S} + \frac{\Delta V_S - \Delta V_{D_0}}{R_S} = I_D + \Delta I_D = I_s \left[\exp \left(\frac{V_{D_0}}{V_T} \right) - 1 \right] + \frac{I_s}{V_T} \exp \left(\frac{V_{D_0}}{V_T} \right) \cdot \Delta V_D$$

$$\frac{\Delta V_S - \Delta V_D}{R_s} = \Delta I_D = \frac{I_S}{V_T} \exp\left(\frac{V_{D0}}{V_T}\right) \cdot \Delta V_D$$

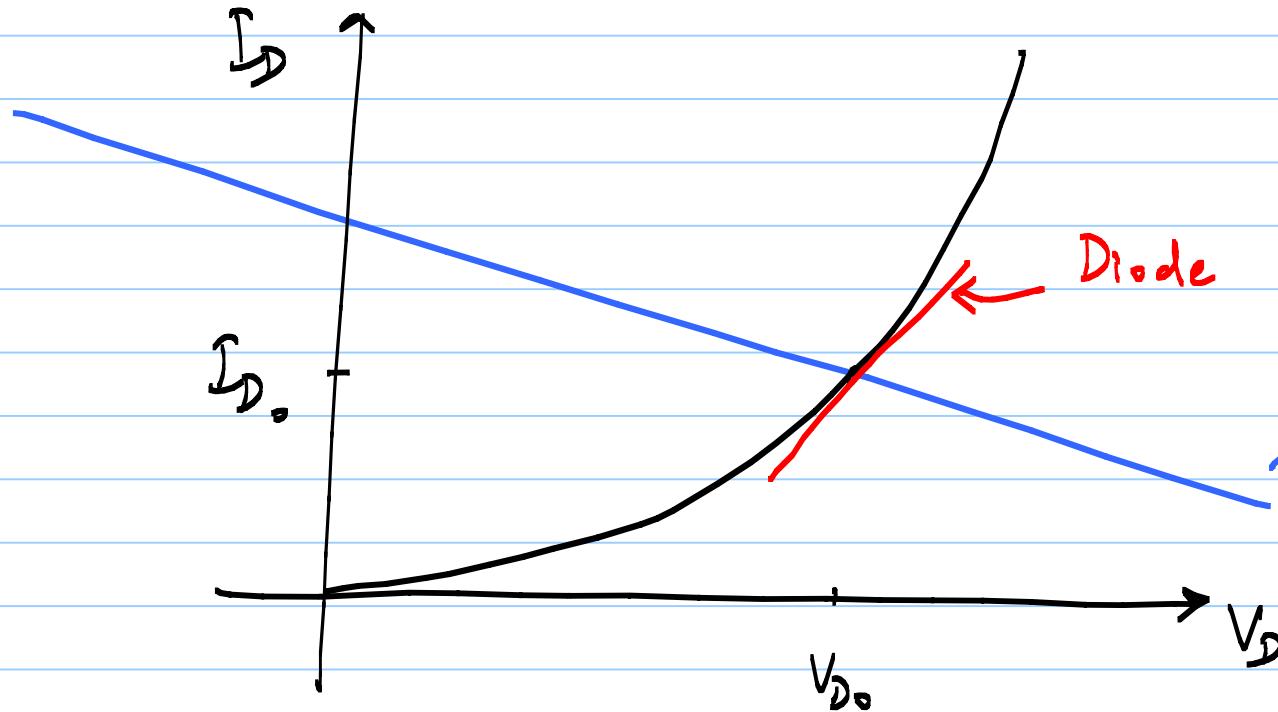Linear equations in $\Delta V_S, \Delta V_D, \Delta I_D$



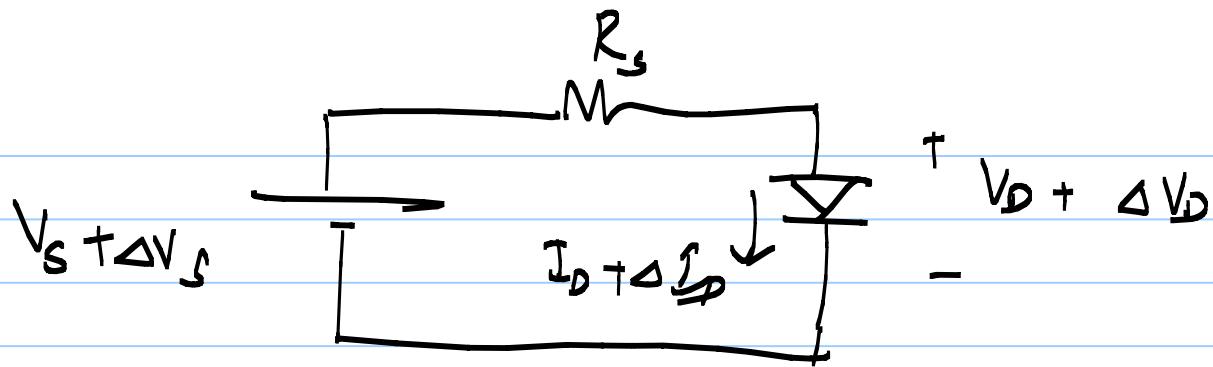Diode can be replaced by
a linearized
element
for $\Delta V_D, \Delta I_D$



$$\Delta V_s = \Delta I_D \cdot R_s + \Delta V_D \approx I_{D_0}$$

$$\Delta I_D = \frac{I_s}{V_t} \exp\left(\frac{V_{D_0}}{V_t}\right) \cdot \Delta V_D \approx \frac{I_{D_0}}{V_t} \cdot \Delta V_D$$

$$\Delta V_D = \frac{V_t}{I_{D_0}} \cdot \Delta I_D$$



"incremental resistance" of diode

$$\Delta V_s = \Delta I_D \cdot R_s + \Delta I_D \cdot \frac{V_t}{I_{D_0}}$$

* Any $I = f(V)$ can be linearised around the op. pt.

* Assume $\Delta V_D, \Delta I_D$ etc are "small"

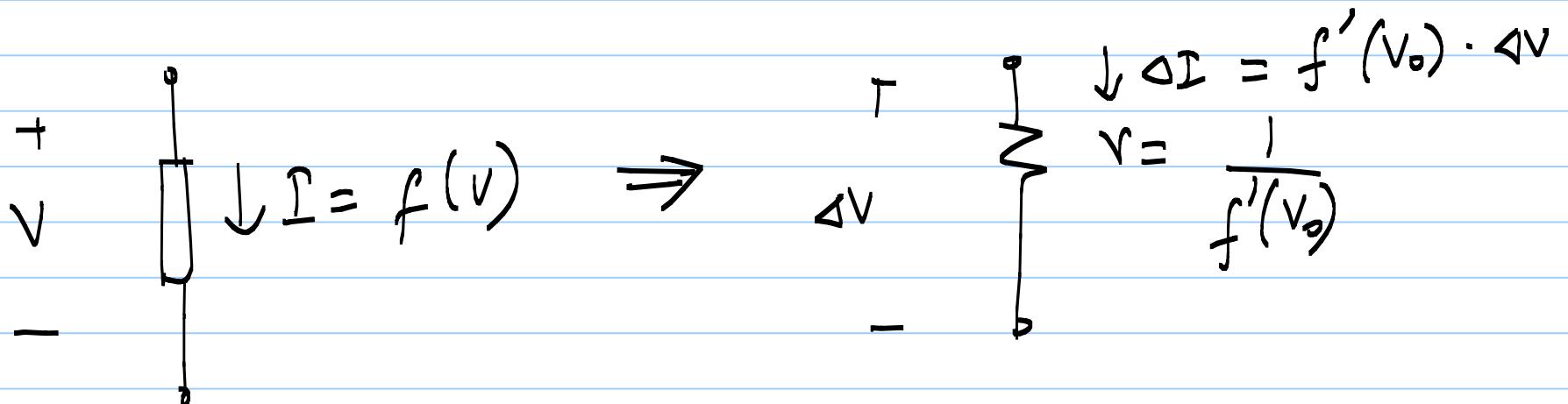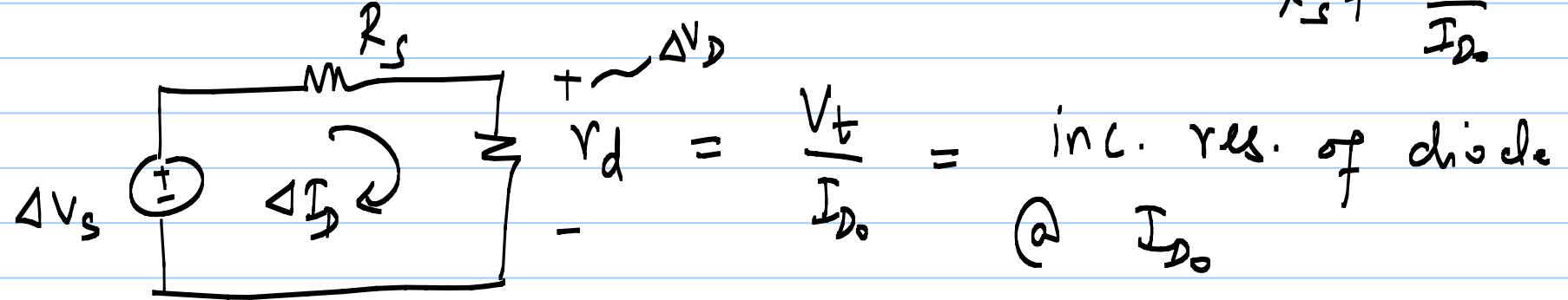(linear) Incremental eq. circuit for $\Delta I_D = \frac{\Delta V_s}{R_s + \frac{V_t}{I_{D_0}}}$



I , V , etc. \Rightarrow DC


I_0 , V_0 etc \Rightarrow operating point,
bias point

Quiescent point

Δi , $\Delta v \Rightarrow$ incremental quantities

i , $v \Rightarrow$ small-signal quantities

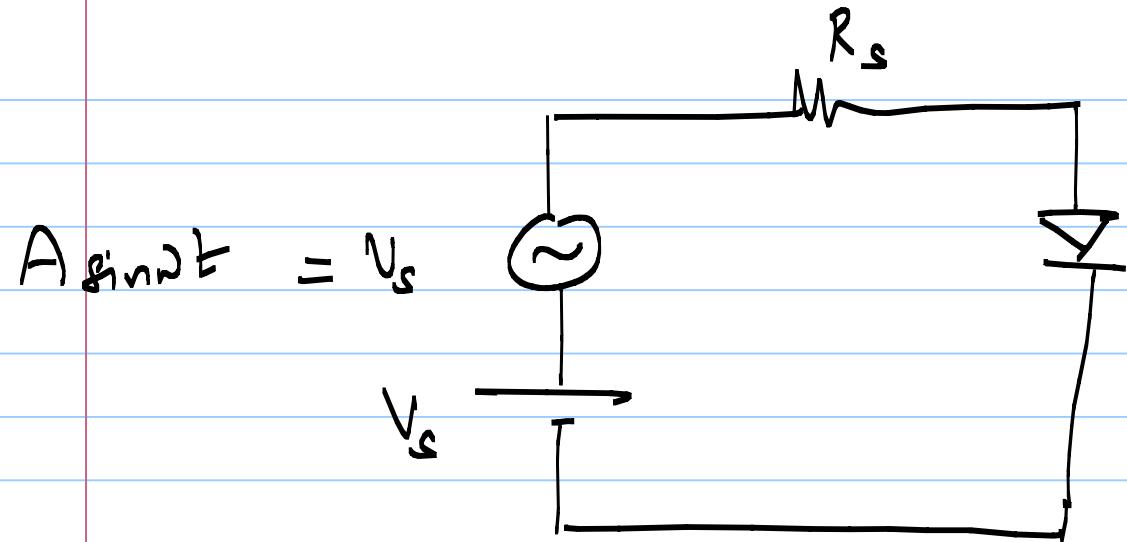$V_D = V_{D0} + \Delta V_D \text{ or.} \Rightarrow$ total quantities




If A is very small :

@ every point of time,
instantaneous increments

are small enough that

linear approx. is valid

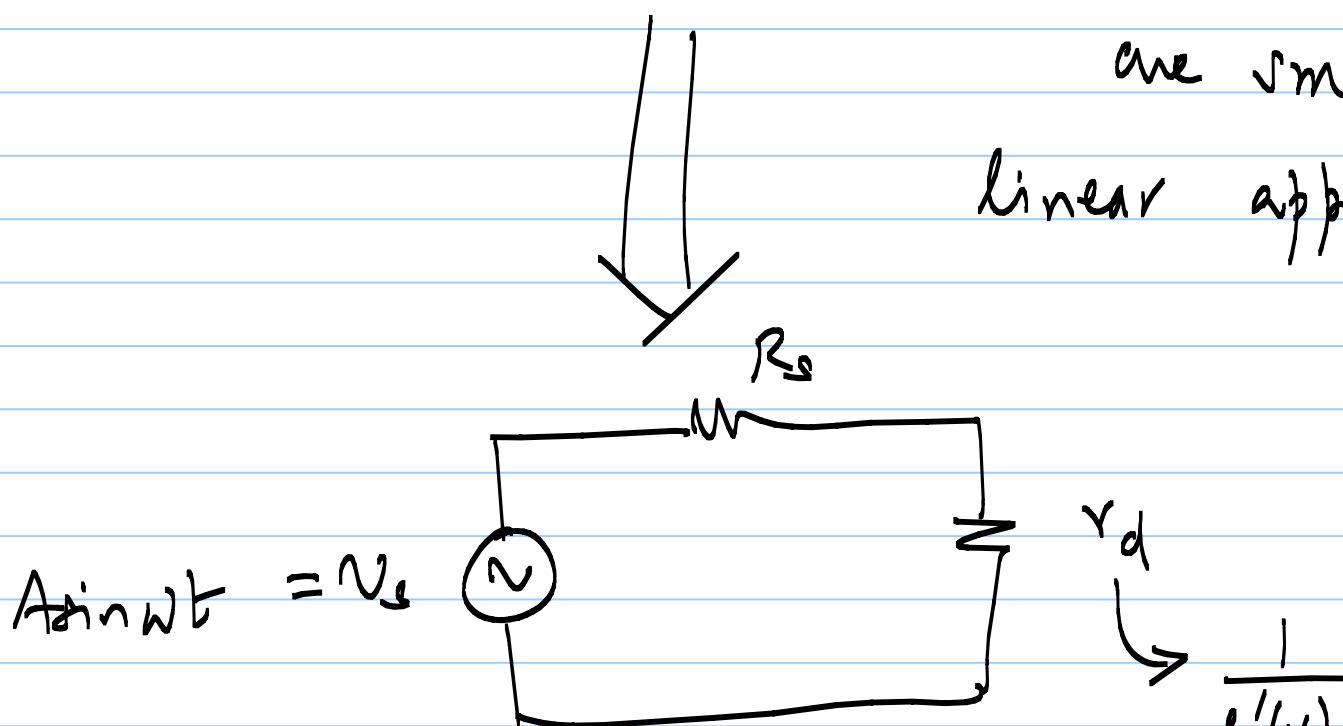


small - signal
equivalent network

$$\frac{1}{f'(V_b)}$$

For op. pt. : you have to solve the
system of non-linear equations to determine
 I_{D0} , V_{D0} etc.

7/8/2020


Lecture 4

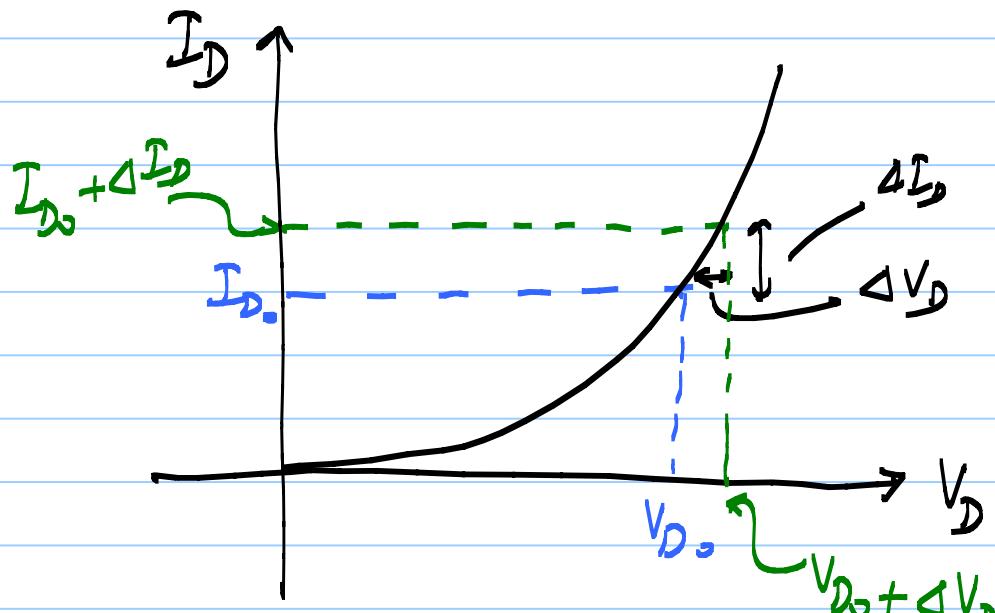

$$\frac{\Delta I_D}{\Delta V_D} = \left. \frac{d I_D}{d V_D} \right|_{(I_{D_0}, V_{D_0})}$$


= incremental conductance
(w)
dynamic " "
small-signal "

Example

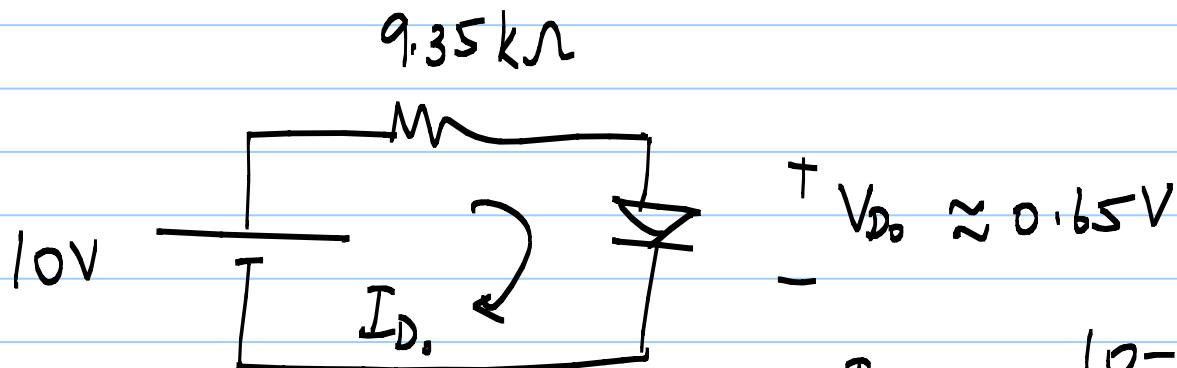


$$I_{D_0} = \frac{10 - 0.65}{9.35\text{ k}\Omega} = 1\text{ mA}$$

Change 10V → 11V

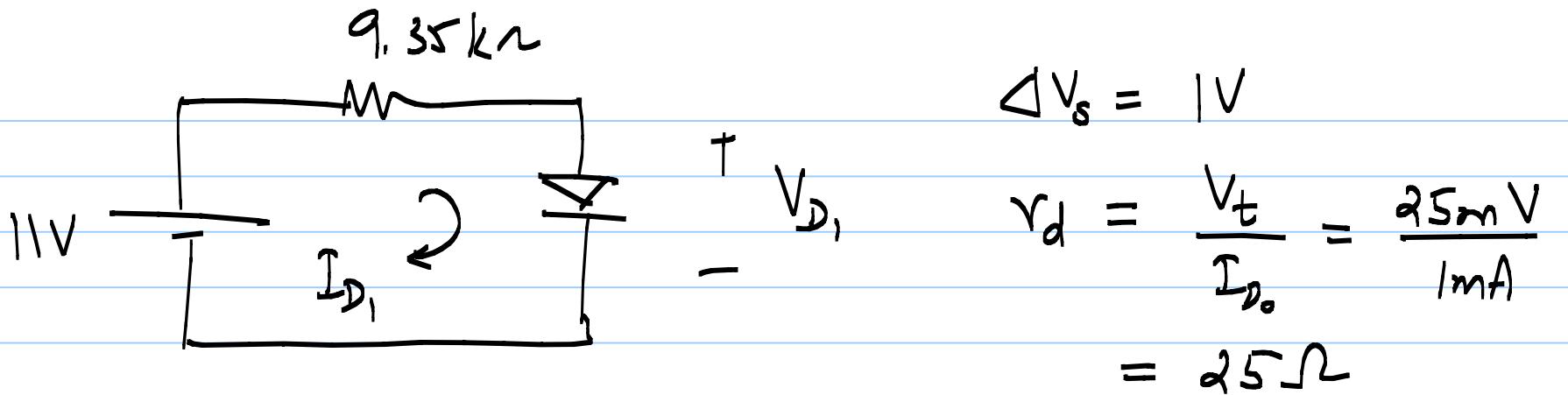

Incremental Equivalent Circuit

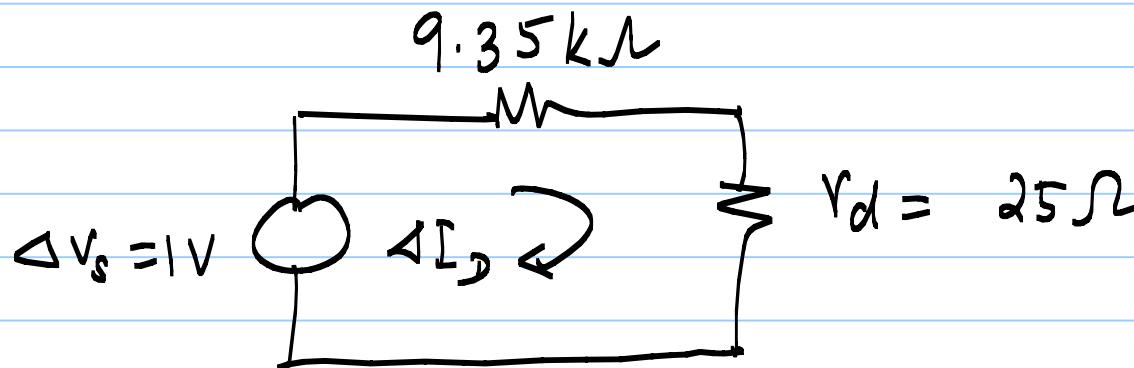

$$\Delta I_D = \frac{1V}{9350 + 25} \approx 106\text{ mA}$$

$$I_{D_1} = I_{D_0} + \Delta I_D = 1.106\text{ mA}$$

$$* I_f \quad V_s = 9V, \quad I_{D_2} = ?$$

$$\Delta V_S = -1V \Rightarrow \Delta I_D = -106 \mu A$$

$$\Rightarrow I_{D_2} = 0.894 \text{ mA}$$

* If $V_S = 9.5 \text{ V}$, $I_{D_3} = I_{D_0} - \frac{1}{2} (106 \mu \text{A})$

.....

* If $V_S = 10 \text{ V} + (1 \text{ V}) \sin \omega t$

$$I_D = 1 \text{ mA} + (106 \mu \text{A}) \sin \omega t$$

Next : Is linear apprxn. valid?

$$\Delta V_D = \Delta I_D \cdot r_d = 106 \mu \text{A} \times 25 \approx 2.7 \text{ mV}$$

$$f''(V_{D_0}) = ?$$


$$I_D = I_s \exp\left(\frac{V_D}{V_T}\right)$$

$$f''(V_{D_0}) = \frac{I_s}{V_t^2} \exp\left(\frac{V_{D_0}}{V_t}\right) \approx \frac{I_{D_0}}{V_t^2}$$

$$\text{Taylor Series 3rd term} = \frac{f''(V_{D_0})}{2} (\Delta V_D)^2$$


$$= \frac{I_{D_0}}{2V_t^2} \cdot (\Delta V_D)^2$$
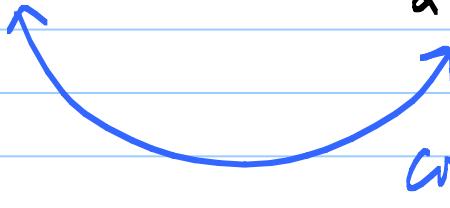
$$I_D = I_{D_0} + \frac{I_{D_0}}{V_t} (\Delta V_D) + \frac{I_{D_0}}{2V_t^2} (\Delta V_D)^2 + \dots$$



Compare these two

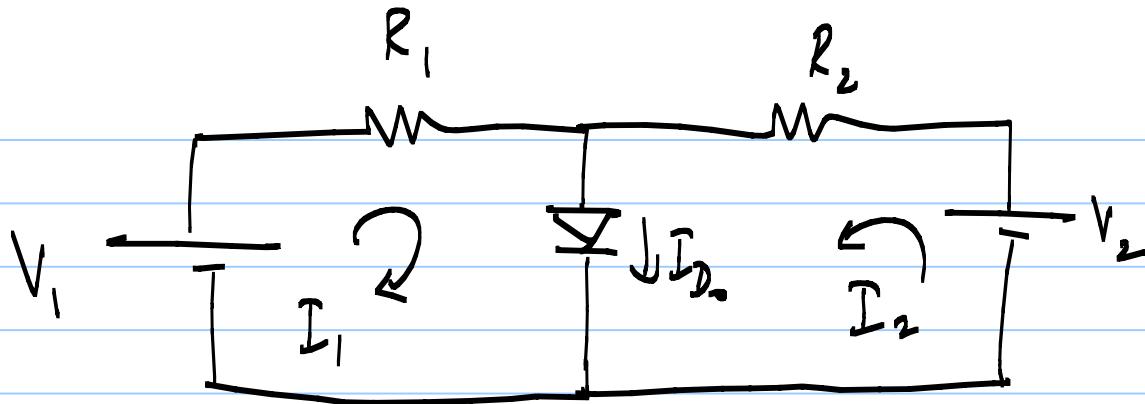first error term is small if $\Delta V_D \ll 2V_t$ valid
 $\Delta V_D \approx 7mV$ 50mV



Assume

$$V_D = 0.65$$

if fwd. biased

Op. pt.


Use NL eqns.

$$I_1 = \frac{V_1 - 0.65}{R_1} \quad \& \quad I_2 = \frac{V_2 - 0.65}{R_2}$$

$$I_{D0} = I_1 + I_2$$

$$V_1 \rightarrow V_1 + \Delta V_1 \quad \& \quad V_2 \rightarrow V_2 + \Delta V_2$$

Inc. picture :

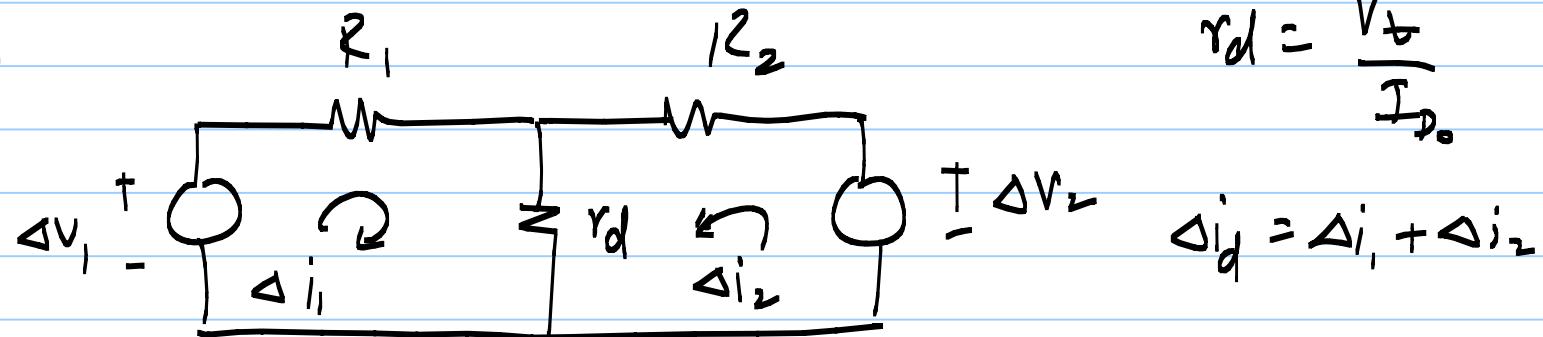

Incremental network

* All elements are linear

* No dc sources

* Inc. voltage across NL element

$$\Delta V_d = \Delta i_d \cdot r_d \quad \left\{ \Delta V_d = \frac{r_d}{r_d + 9.35k\Omega} \cdot \Delta V_s \right\}$$

* Total voltage across diode

$$= \text{Quiescent voltage} + \text{Incremental voltage}$$

$$\{ 0.65V + \Delta V_d \}$$

* Can extend to networks with multiple NL elements

→ replace each NL element with its
inc. resistance $r_i = \frac{1}{f'_i(V_{io})}$

12/8/2020

Lecture 5

1) Find operating point

→ solve non-linear equations

→ incremental ΔV_s & ΔI_s are dependent




on the Q-pt (r_i 's are dep. in Q-pt.)

2) Draw the incremental equivalent circuit
(linear network) and solve for ΔV_s & ΔI_s

3) Total V_s and I_s


$$= \text{Quiescent } V/I + \text{Incremental } V/I$$

Element

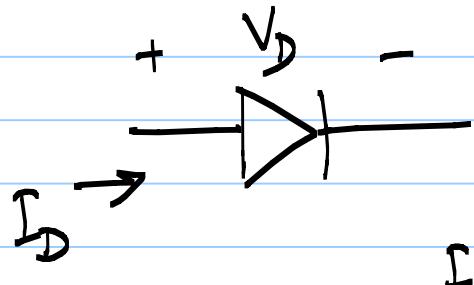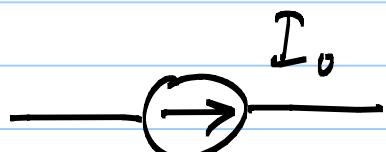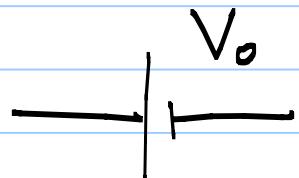

$$I = f(V)$$

$$I_o \rightarrow + V_o -$$

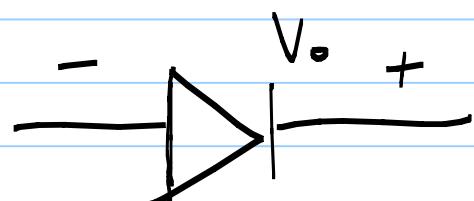

Incremental equivalent



short circuit





open circuit


$$r_D = \frac{V_t}{I_D}$$

$$r = \frac{1}{f'(V_o)}$$

open circuit

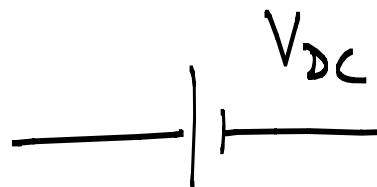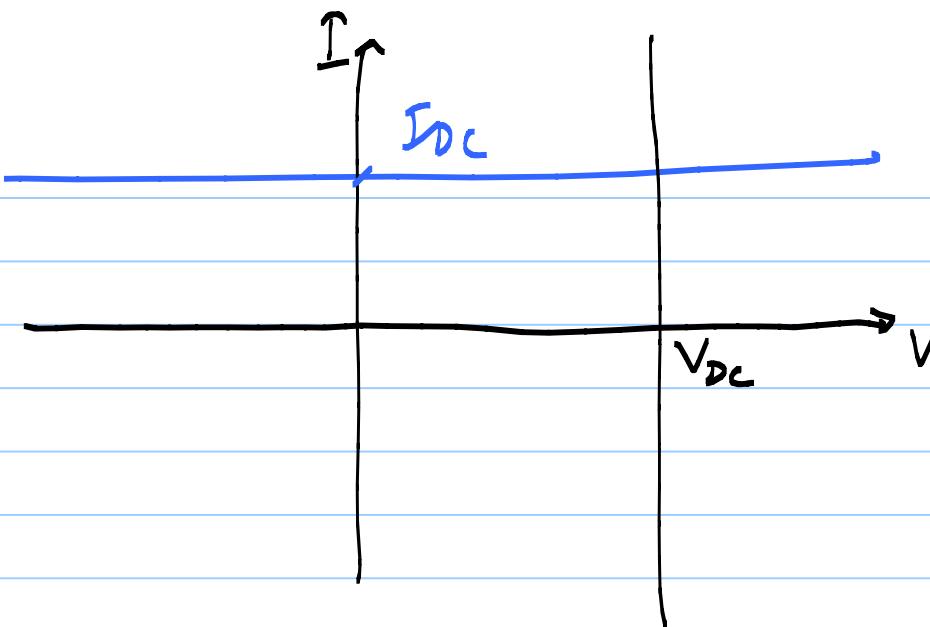

$$r_{V_{DC}} = \frac{1}{f'(v)} = 0$$


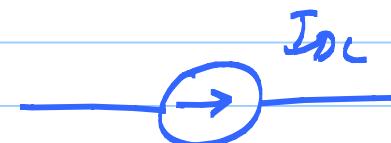



$$r_{I_{DC}} = \frac{1}{f'(v)} = \infty$$

Hw : $\text{---}^L_m\text{---}$




Ind. eq.

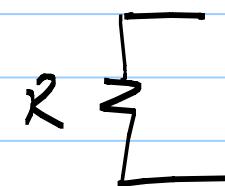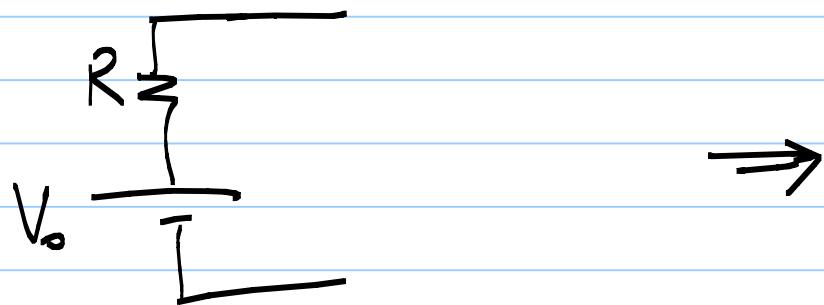

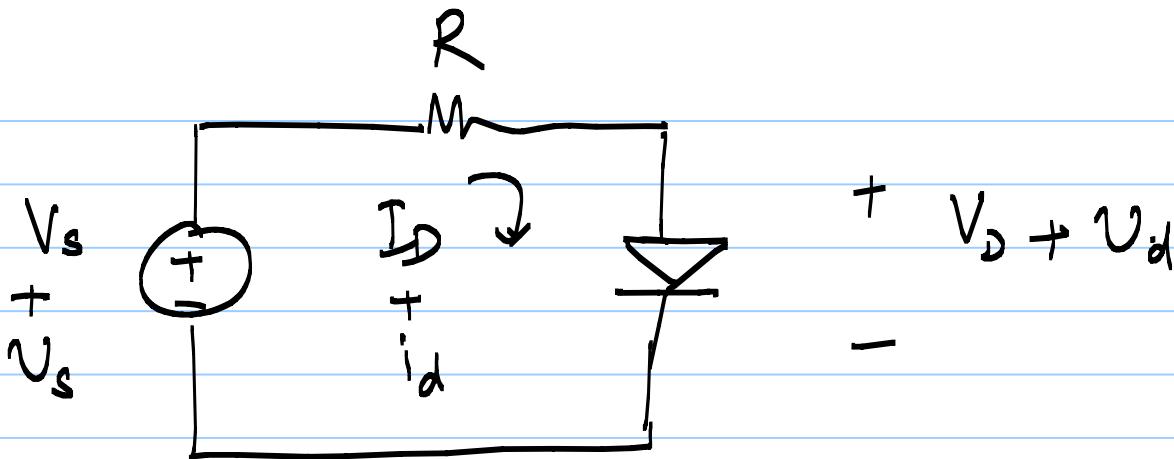

Is it possible
for
 $V_d > V_s$?

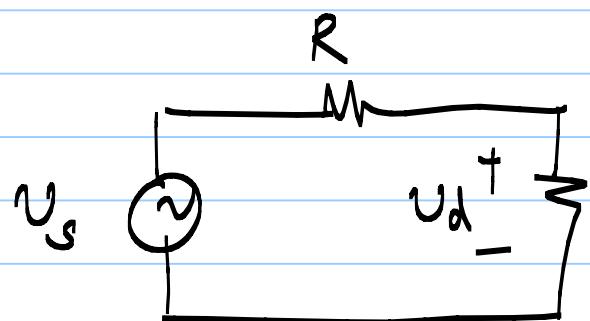


$$r_d = \frac{V_t}{I_D}$$


$$v_d = \frac{r_d}{R + r_d} \cdot v_s$$

small-signal gain = $\frac{v_d}{v_s}$

$$= \frac{r_d}{R + r_d}$$

$$r_x = \frac{1}{f'(V_x)}$$

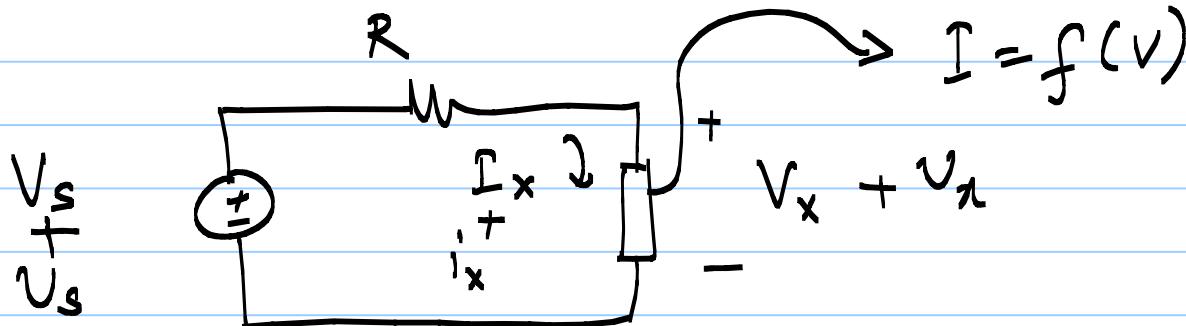




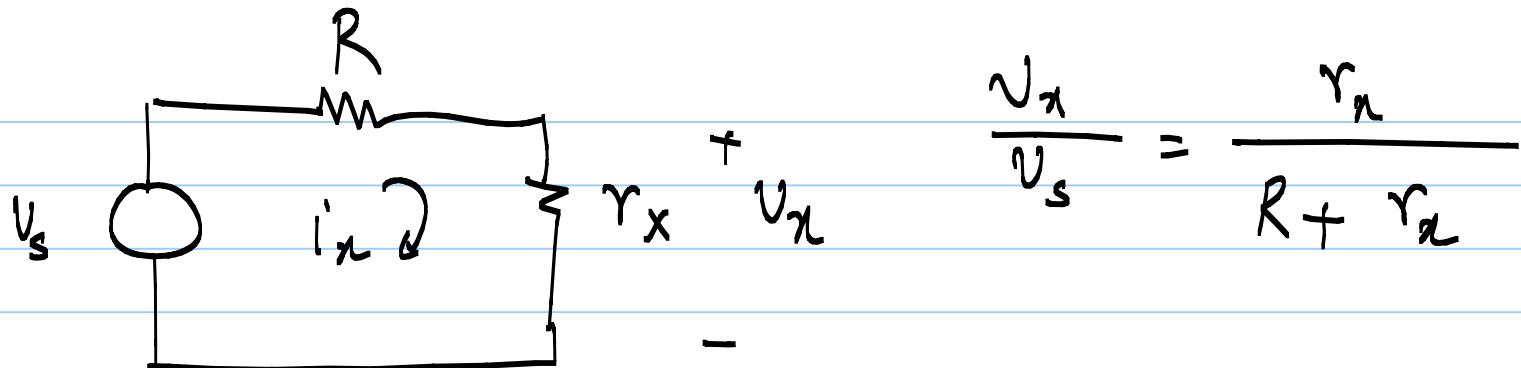



If r_x is negative, it is possible for

$$\left| \frac{v_x}{v_s} \right| \text{ to be } > 1$$

slope of $f(v)$ is negative

"Tunnel Diode"

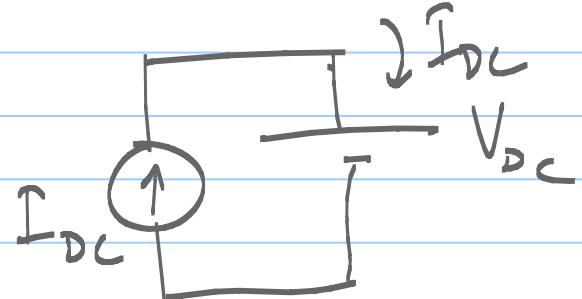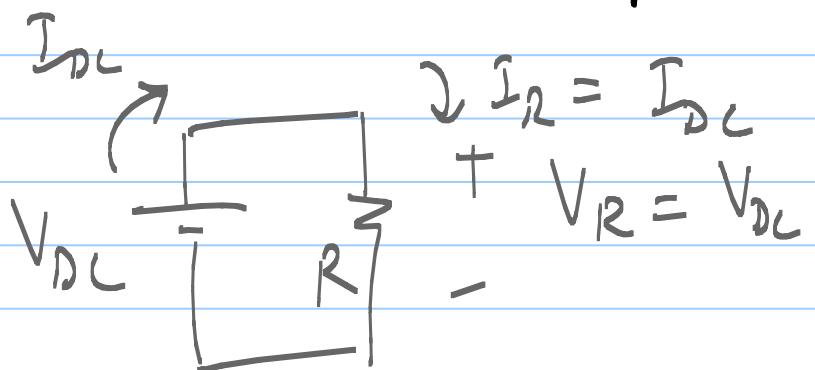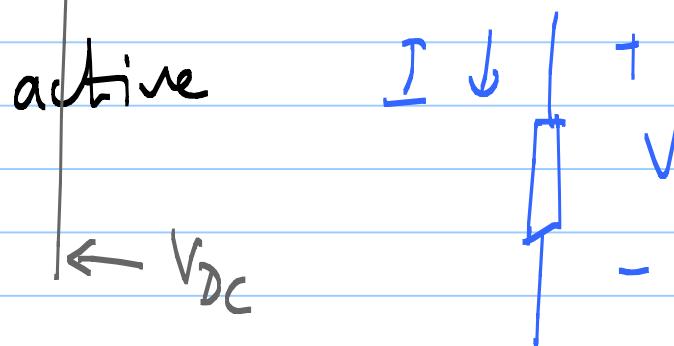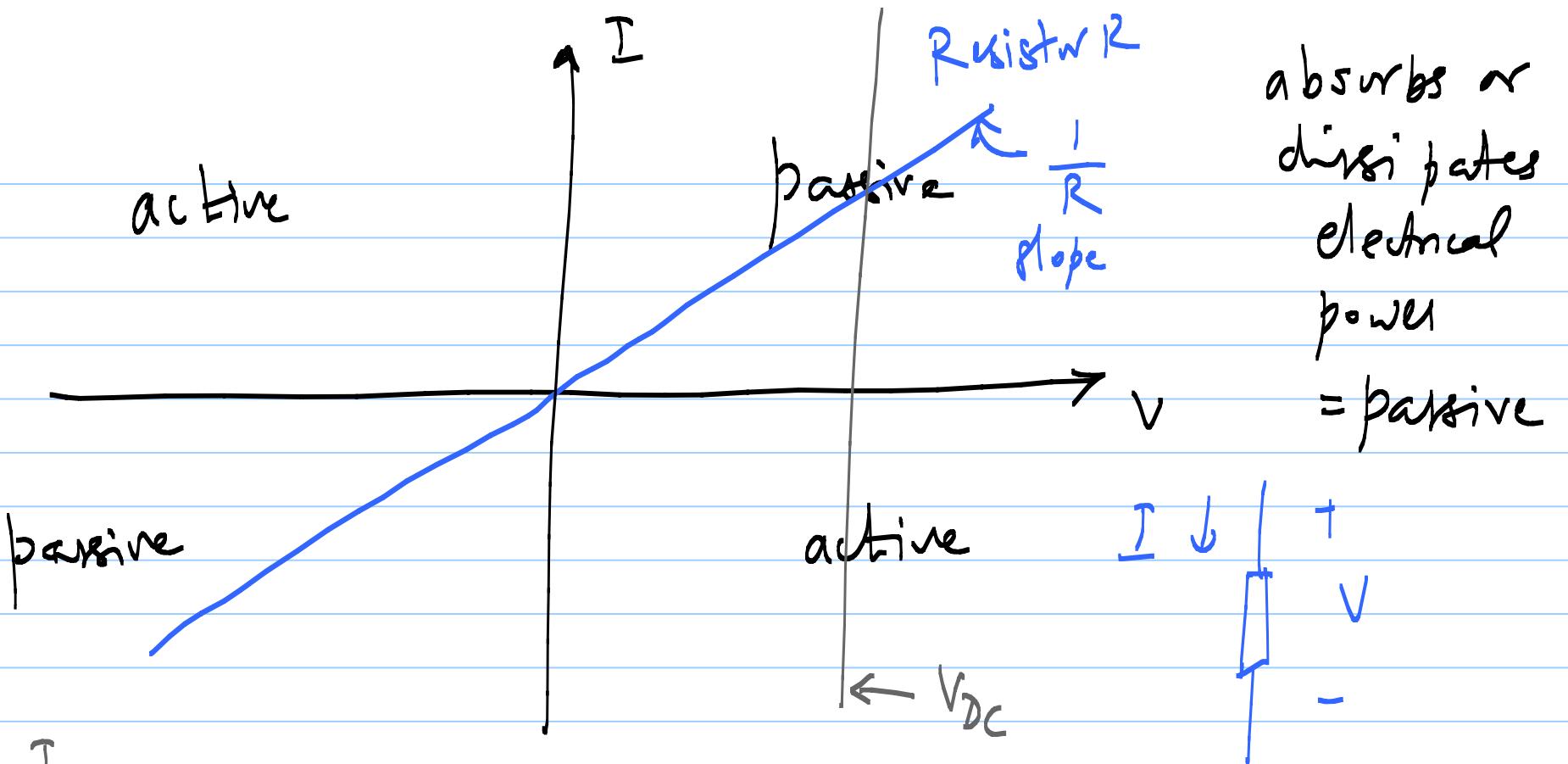

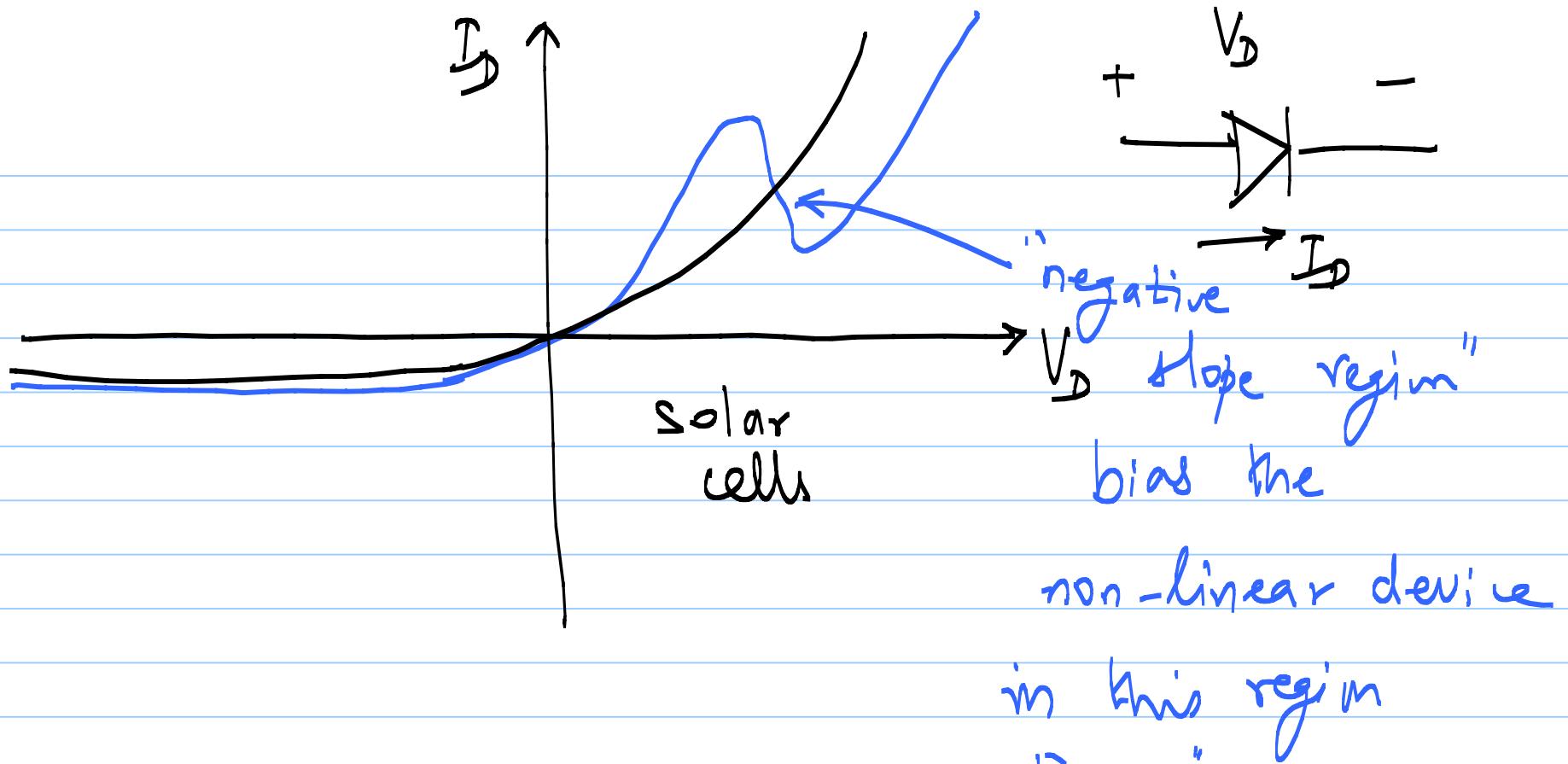

)
 Is it possible to get "gain" from purely linear passive devices?


- * No power gain possible

- * Only gain possible (transformers ...)

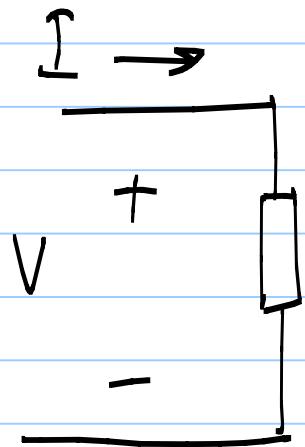2)

Non linear passive devices?

- incremental / small-signal voltage
and power gain possible
- Battery power is used up
(in overall power)




2-T
l-purt

I parameter describes
ss behaviour

$$Y = \frac{1}{f'(v_0)}$$

2-port networks

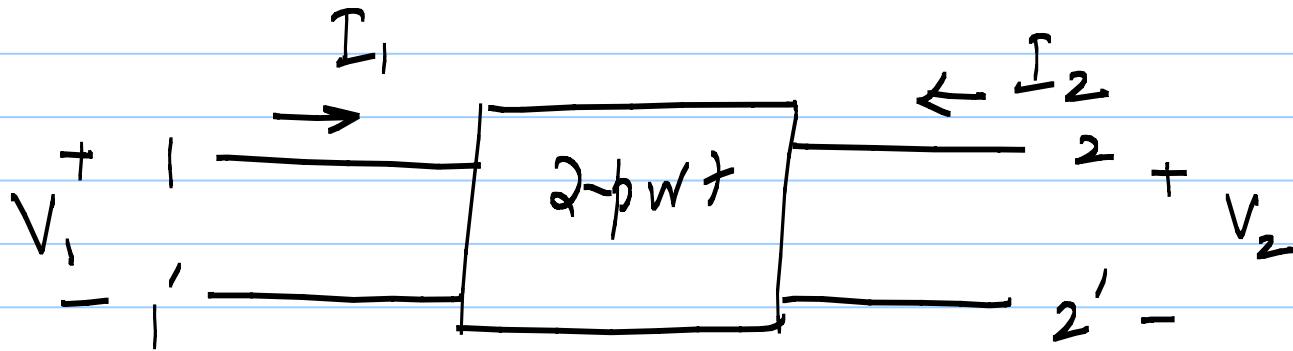

4 parameters required to describe

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \underbrace{\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}}_{\text{(impedance) } Z\text{-parameters}} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


2-port network

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \underbrace{\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}}_{\text{(Admittance) } Y\text{-parameters}} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

13/8/20

Lecture 6

$$[I] = [Y] [V]$$

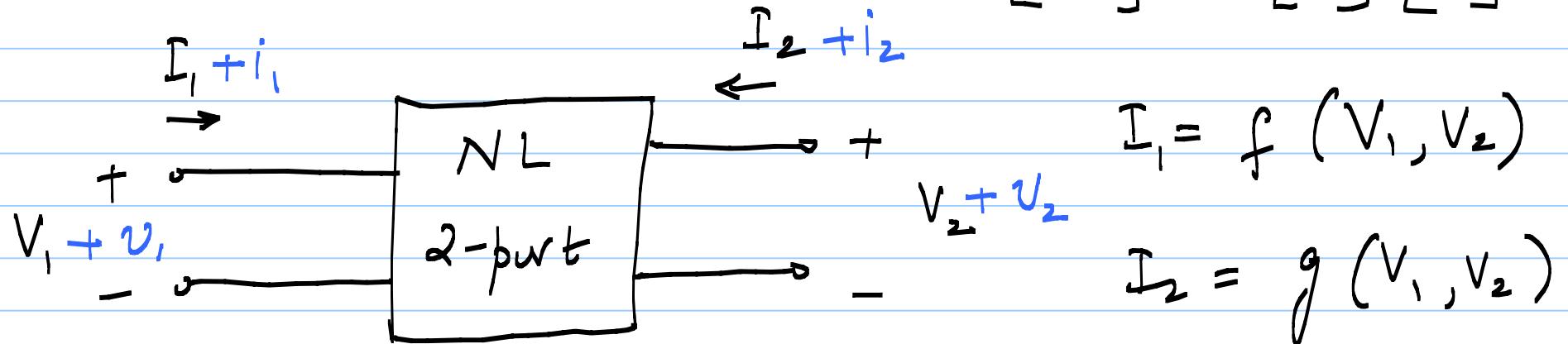

$$I_1' = I_1 + i_1 = f(V_1 + v_1, V_2 + v_2)$$

$$I_1 = f(V_1, V_2)$$

* If v_1 & v_2 are small, $f()$ & $g()$ can be expanded in a 2-D Taylor Series

around op. pt. { approx. 3D surface by a tangential plane @ op. pt. }

$$I'_1 = I_1 + i_1 \approx I_1 + \frac{\partial f}{\partial V_1} \cdot v_1 + \frac{\partial f}{\partial V_2} \cdot v_2$$

$$\Rightarrow i_1 = \frac{\partial f}{\partial V_1} \cdot v_1 + \frac{\partial f}{\partial V_2} \cdot v_2 \quad \left. \begin{array}{l} \text{linear} \\ \text{relationship} \end{array} \right\}$$

$$i_2 = \frac{\partial g}{\partial V_1} \cdot v_1 + \frac{\partial g}{\partial V_2} \cdot v_2 \quad \left. \begin{array}{l} \text{between} \\ i_1, i_2, v_1, v_2 \end{array} \right\}$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} \frac{\partial f}{\partial V_1} & \frac{\partial f}{\partial V_2} \\ \frac{\partial g}{\partial V_1} & \frac{\partial g}{\partial V_2} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$


y₁₁ y₁₂
y₂₁ y₂₂

y-matrix


y-matrix

Graphical Representation


1) Linear v 1-port
passive

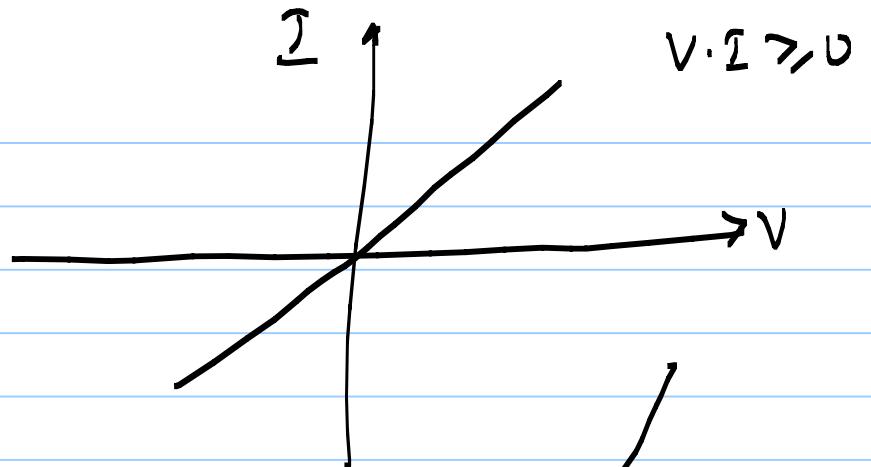

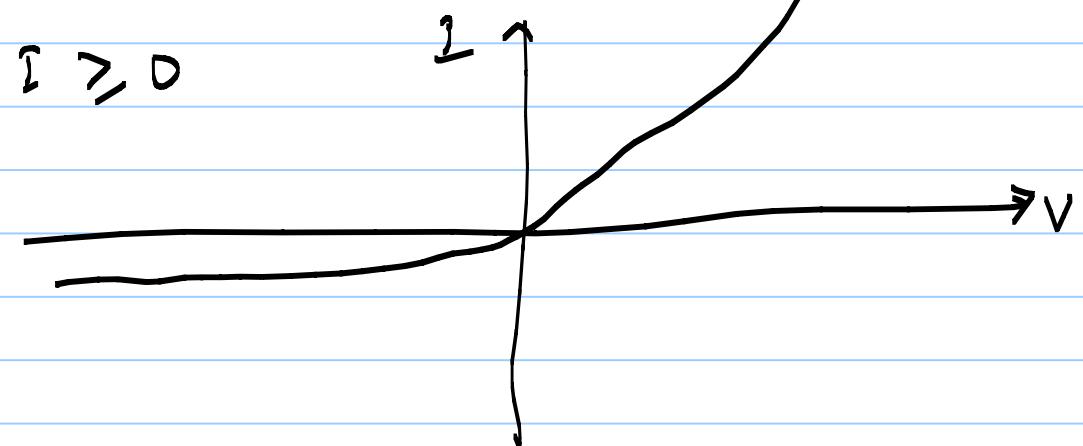2) NL \wedge ^{passive} 1-port $V \cdot I \geq 0$



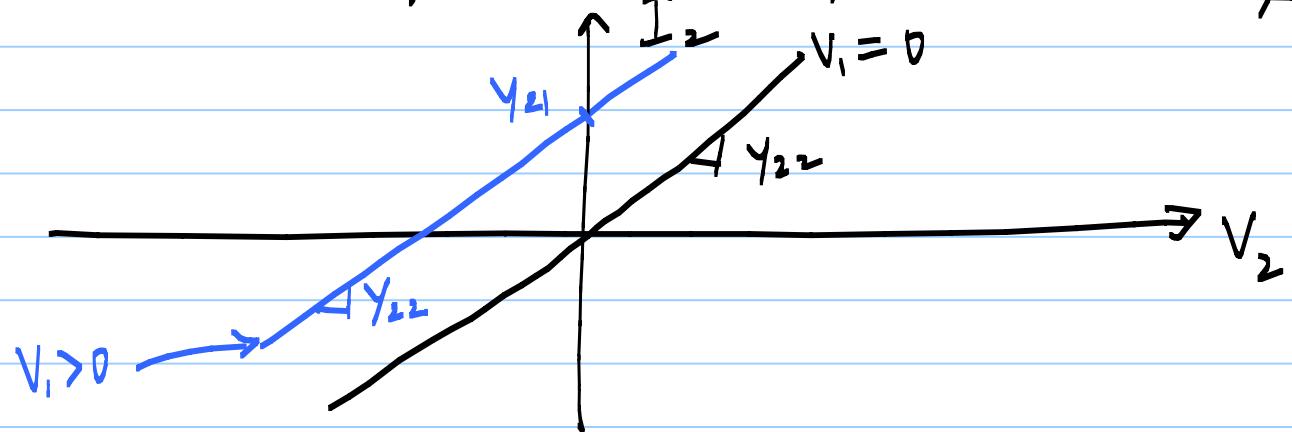3) Linear 2-port : Input & output characteristics



$$I_1 = \gamma_{11}V_1 + \gamma_{12}V_2$$


$$I_2 = \gamma_{21}V_1 + \gamma_{22}V_2$$


Input characteristics $\Rightarrow I_1$ vs. V_1 for various V_2

passivity : $V_1 I_1 + V_2 I_2 \geq 0$

(Lin. or Non Lin.)

Amplifiers

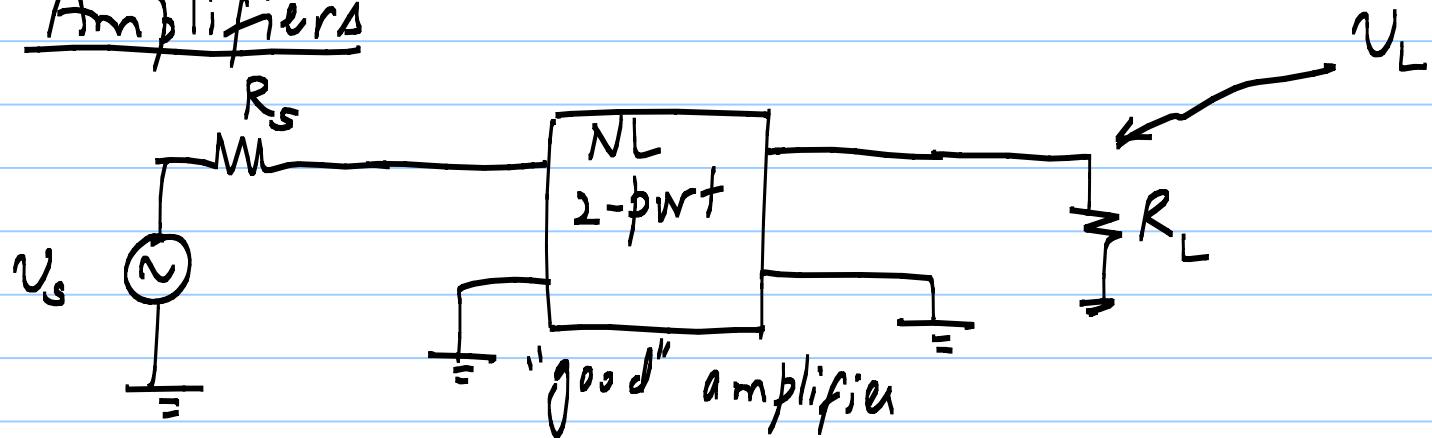

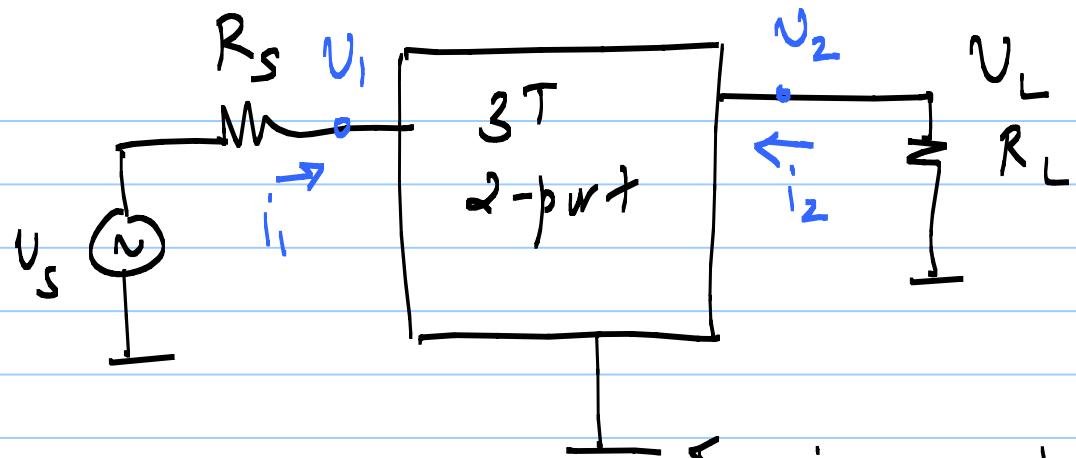



Good Amplifier:

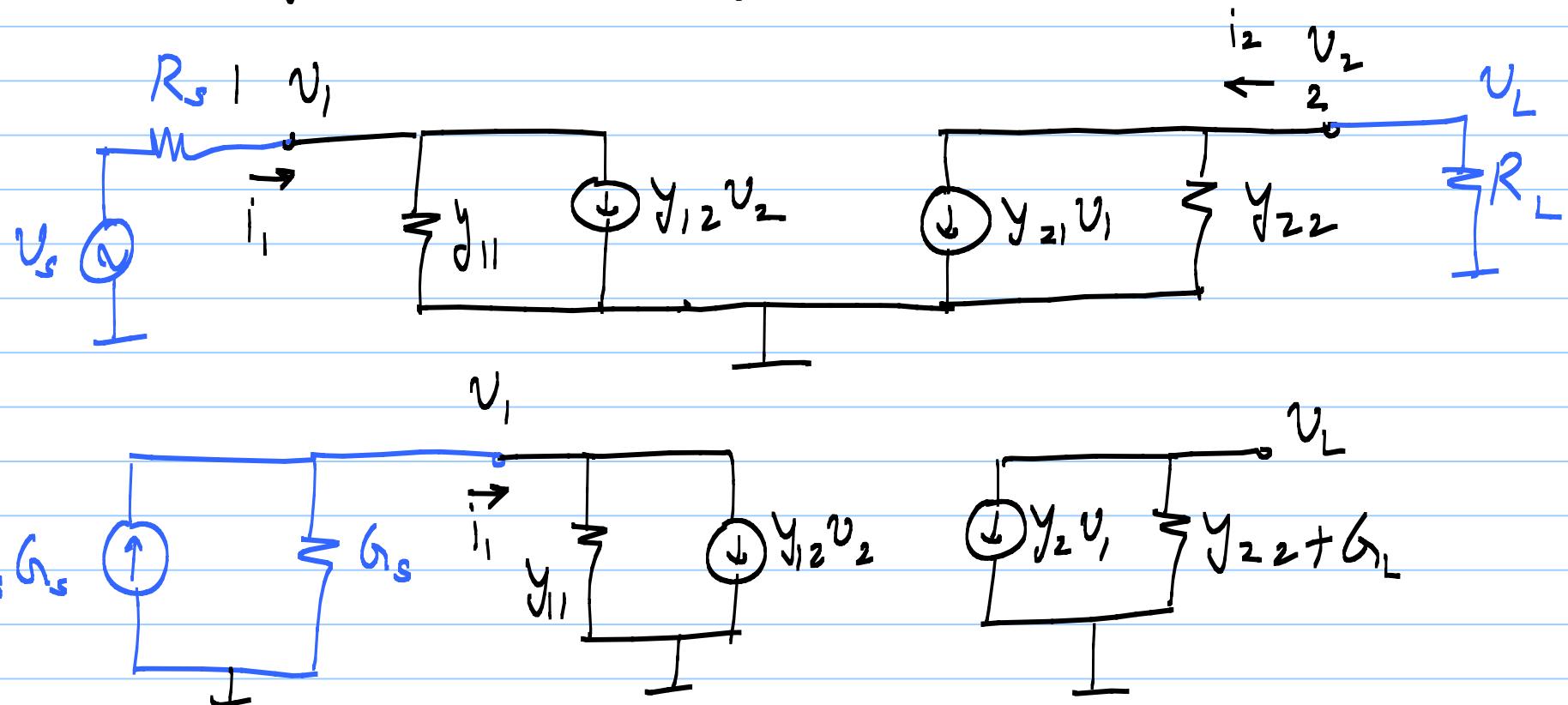- 1) Large gain : $\frac{v_L}{v_s}$ as large as possible
- 2) Independent of source quality : v_L independent of R_s
and gain independent of R_s
- 3) gain independent of R_L too.
- 4) We want i_1 independent of v_2
"unilateral" $y_{12} = 0$ is desired

Derive constraints on $[y]$ to achieve a "good" amp.

$$\begin{aligned} i_1 &= y_{11}v_1 + y_{12}v_2 \\ i_2 &= y_{21}v_1 + y_{22}v_2 \end{aligned} \quad \left. \begin{array}{l} \text{replace by equivalent} \\ \text{network} \end{array} \right\}$$



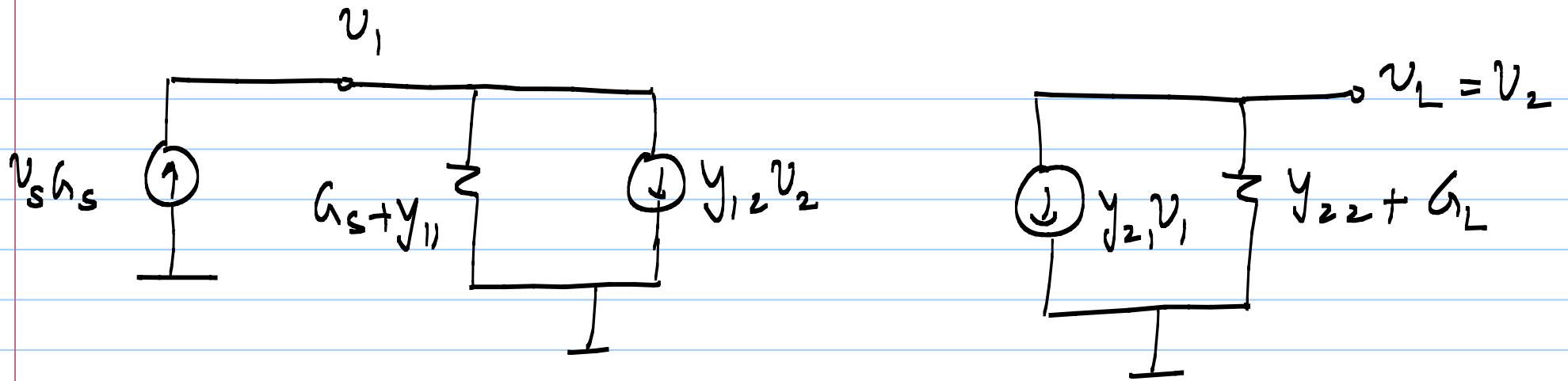

KCL @ input & output.

@ input: $v_s h_s = v_1 (g_s + y_{11}) + y_{12} v_2$

$$\Rightarrow v_1 = \frac{v_s h_s - y_{12} v_2}{g_s + y_{11}}$$

(blue arrow) plug into

@ output: $y_{21} v_1 + v_2 (y_{22} + g_L) = 0$

$$y_{21} \left[\frac{v_s h_s - y_{12} v_2}{g_s + y_{11}} \right] + (y_{22} + g_L) \cdot v_2 = 0$$

$$v_s \left[\frac{y_{21} + g_s}{y_{11} + g_s} \right] = v_2 \left[\frac{y_{12} y_{21}}{y_{11} + g_s} - (y_{22} + g_L) \right]$$

$$= v_2 \left[\frac{y_{12} y_{21} - (y_{22} + g_L)(y_{11} + g_s)}{y_{11} + g_s} \right]$$

$$\frac{v_2}{v_s} = \frac{v_L}{v_s} = \frac{y_{21} g_s}{y_{12} y_{21} - (y_{22} + g_L)(y_{11} + g_s)}$$


* If $y_{12} y_{21} = (y_{22} + g_L)(y_{11} + g_s)$, gain $\rightarrow \infty$
 Undesired situation, gain needs to be a
 function of y_{11} , etc.

* Make amplifier unilateral: $y_{12} = 0$

$$\Rightarrow \frac{v_L}{v_s} = \frac{-y_{21}h_s}{(y_{22} + h_L)(y_{11} + h_s)}$$

14/8/2020

Lecture 7

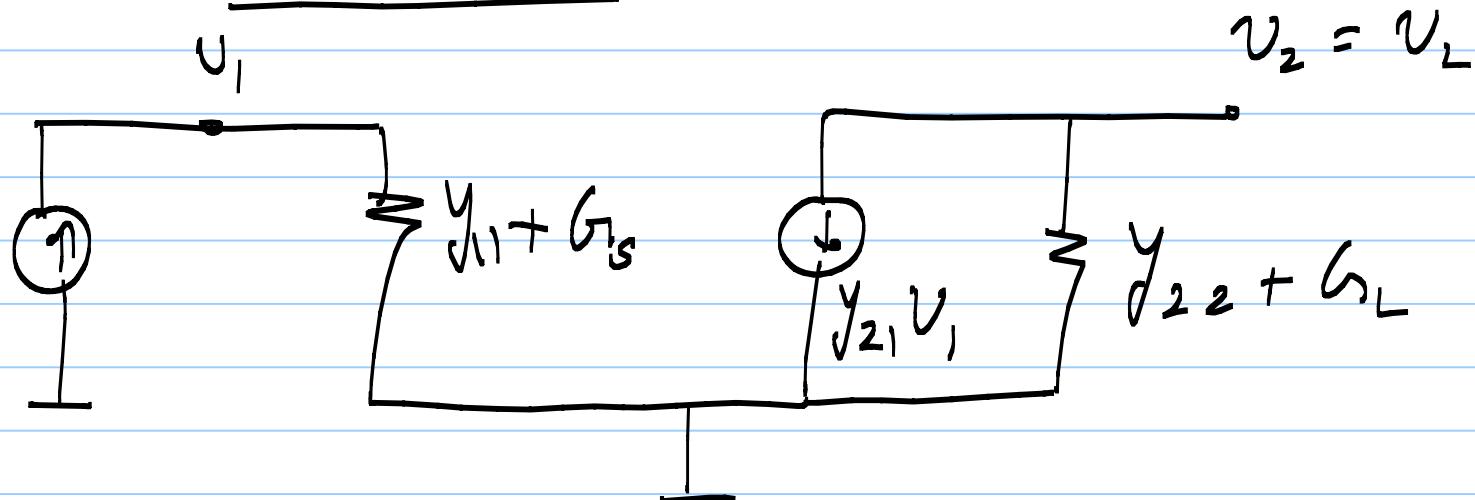

$$\text{Gain} = \frac{-y_{21}}{(y_{22} + G_L)} \cdot \left(\frac{G_s}{y_{11} + G_s} \right)$$

i) Gain independent of G_s : set $y_{11} = 0$
 $\Rightarrow i_1 = 0$

$$\frac{v_L}{v_s} = \frac{-y_{21}}{y_{22} + G_L}$$

2)

Gain as large as possible:

y_{21} as large as possible

and

$y_{22} + G_L$ as small as possible

set $y_{22} = 0$

$$\boxed{\frac{v_L}{v_s} = -\frac{y_{21}}{G_L}}$$

gain of amplifier
still dep. on G_L

We need a 2-port network with inc(γ):

$$[\gamma] = \begin{bmatrix} 0 & 0 \\ \text{as large as possible} & 0 \end{bmatrix} = \begin{bmatrix} \partial f / \partial v_1 & \partial f / \partial v_2 \\ \partial g / \partial v_1 & \partial g / \partial v_2 \end{bmatrix}$$

$$I_1 = f(V_1, V_2) \quad ; \quad I_2 = g(V_1, V_2)$$


$$y_{11}, y_{12} = 0 \Rightarrow \frac{\partial f}{\partial V_1}, \frac{\partial f}{\partial V_2} = 0 \Rightarrow I_1 = I_o$$

constant
current

$$y_{22} = 0, y_{21} = \text{large} \Rightarrow I_2 = g(V_1) \text{ only}$$

$$I_1 = I_o$$

$$I_2 = g(V_1)$$

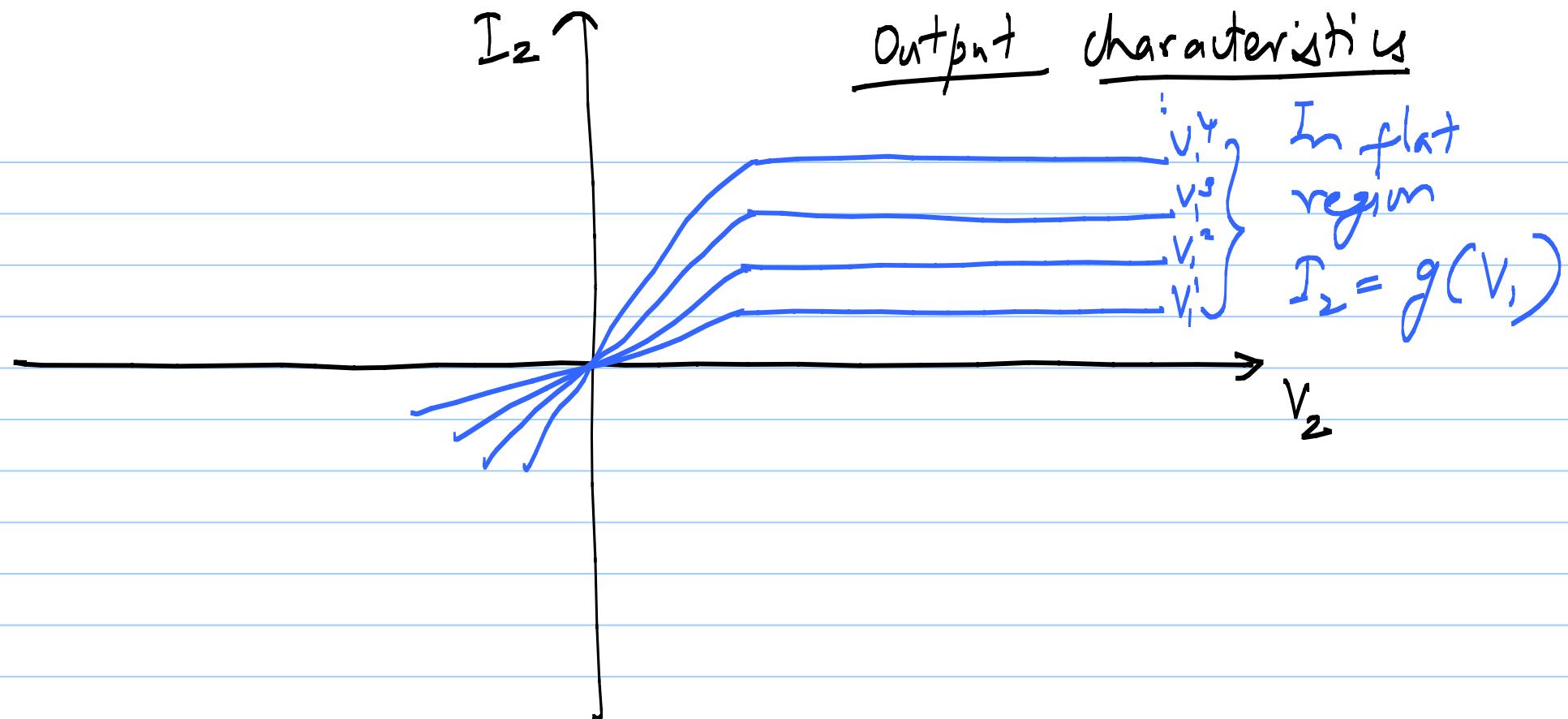


Special case : $I_1 = 0 \Rightarrow$ passivity : $V_1 I_1 + V_2 I_2 \geq 0$
 $\Rightarrow V_2 I_2 \geq 0$

All devices that exhibit "good" amplifier behaviour
 (high g_{m} etc.) have such characteristics

MOSFET $\Rightarrow I_1 = 0$; $\left. \begin{matrix} \text{BJT} \\ \text{JFET} \end{matrix} \right\} \Rightarrow I_1 \text{ very small}$

MOSFET

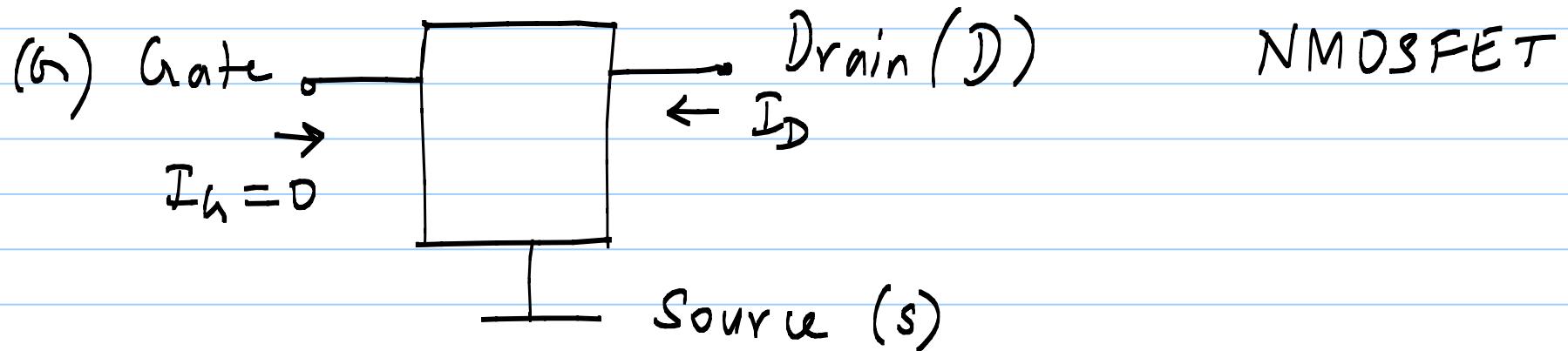

$$I_D = 0 \quad \text{if} \quad V_{GS} < V_T$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2 \quad \text{if} \quad V_{DS} \geq (V_{GS} - V_T)$$

"saturation"

$$I_D = \mu_n C_{ox} \left(\frac{W}{L} \right) \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right] \quad \text{if} \quad V_{DS} \leq (V_{GS} - V_T)$$



"triode", "linear"

V_T = Threshold voltage

M_n = mobility of electrons

C_{ox} = oxide cap. per unit area

W, L = geometric parameters of MOSFET

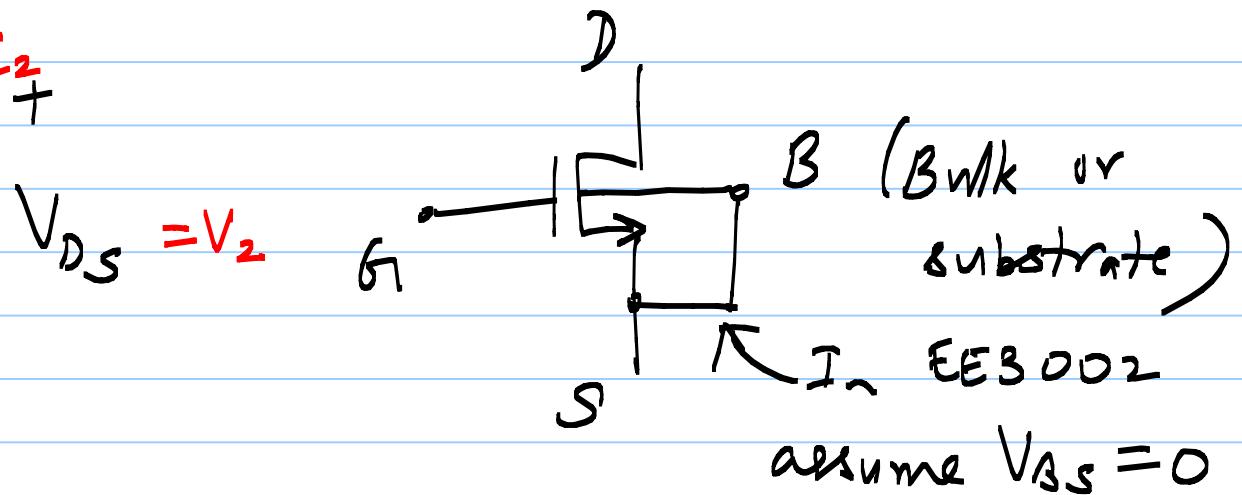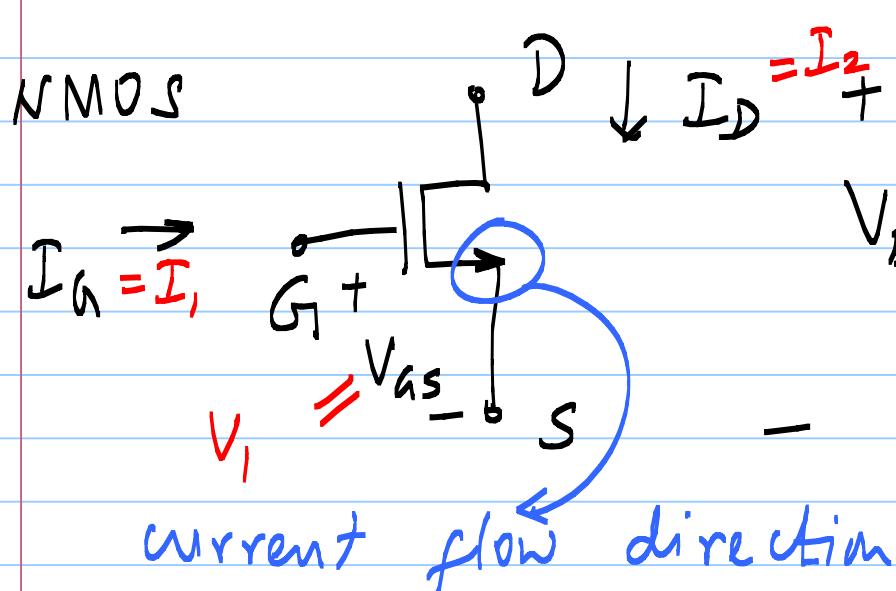

$$I_A = 0 \Rightarrow Y_{11} = Y_{12} = 0$$


In sat., I_D is independent of V_{DS}

Operate MOSFET in sat. for building a good amplifier

I_2 is indep. of $V_2 \Rightarrow y_{22} = 0$

$$y_{21} = \frac{\partial I_2}{\partial V_1} = \frac{\partial I_D}{\partial V_{AS}} = \mu_n C_0 \left(\frac{w}{L}\right) (V_{AS} - V_T)$$

for $V_{AS} > V_T$ and

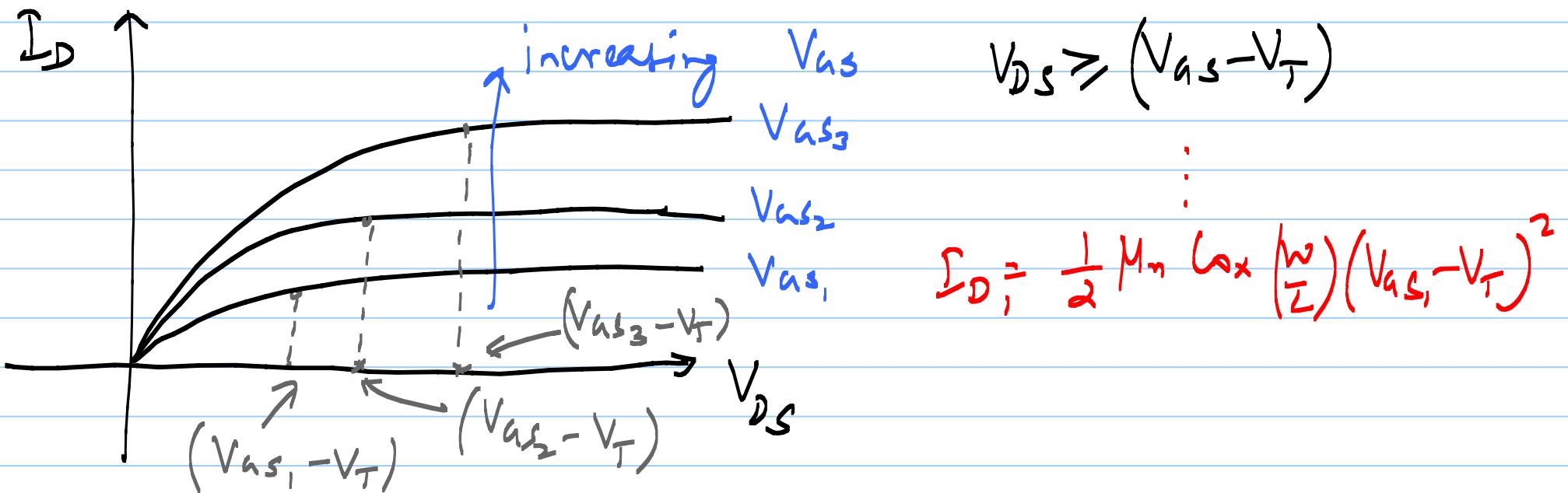




In this course, assume $V_T > 0$

- 1) "Enhancement mode" MOSFET (Normally OFF)

i.e. $V_T > 0$; @ $V_{GS} = 0$, $I_D = 0$



- 2) "Depletion mode" MOSFET (normally ON)

$V_T < 0$; @ $V_{GS} = 0$, $I_D > 0$

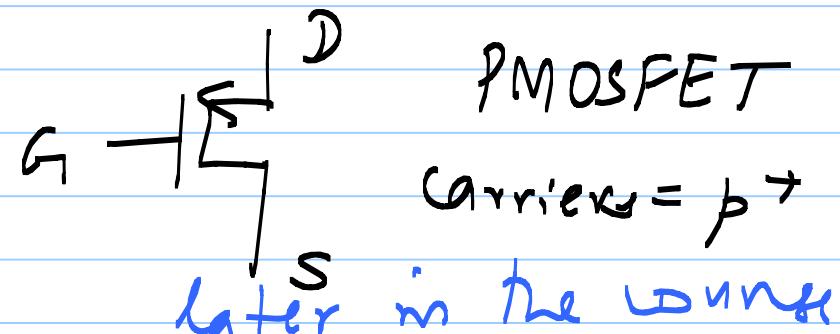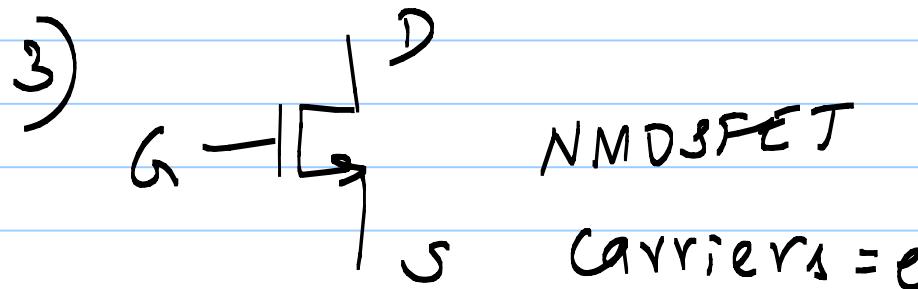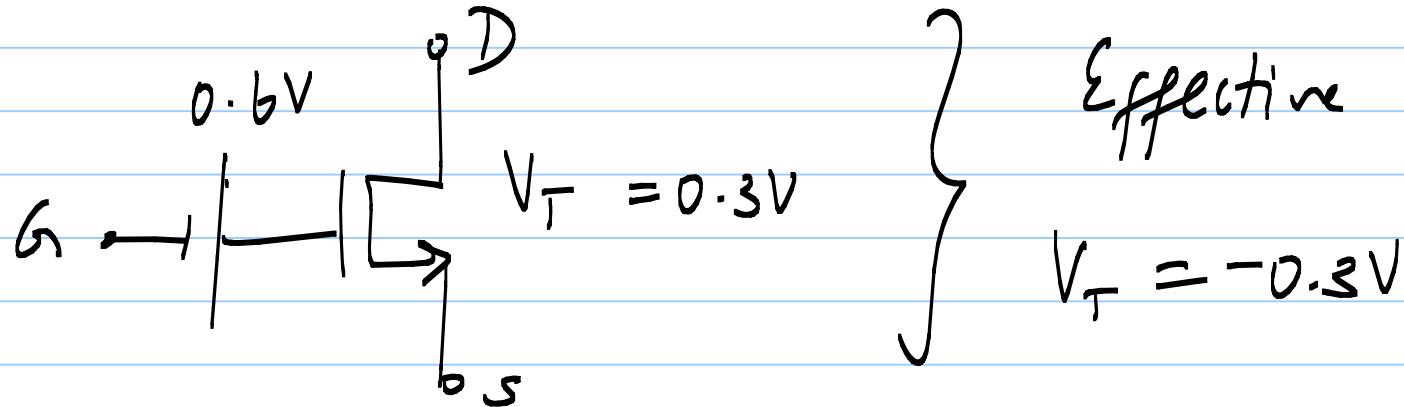

18/8/2020


Lecture 8

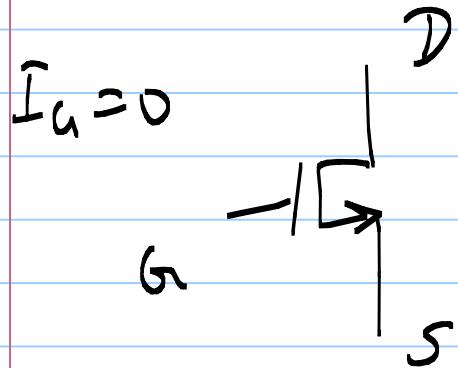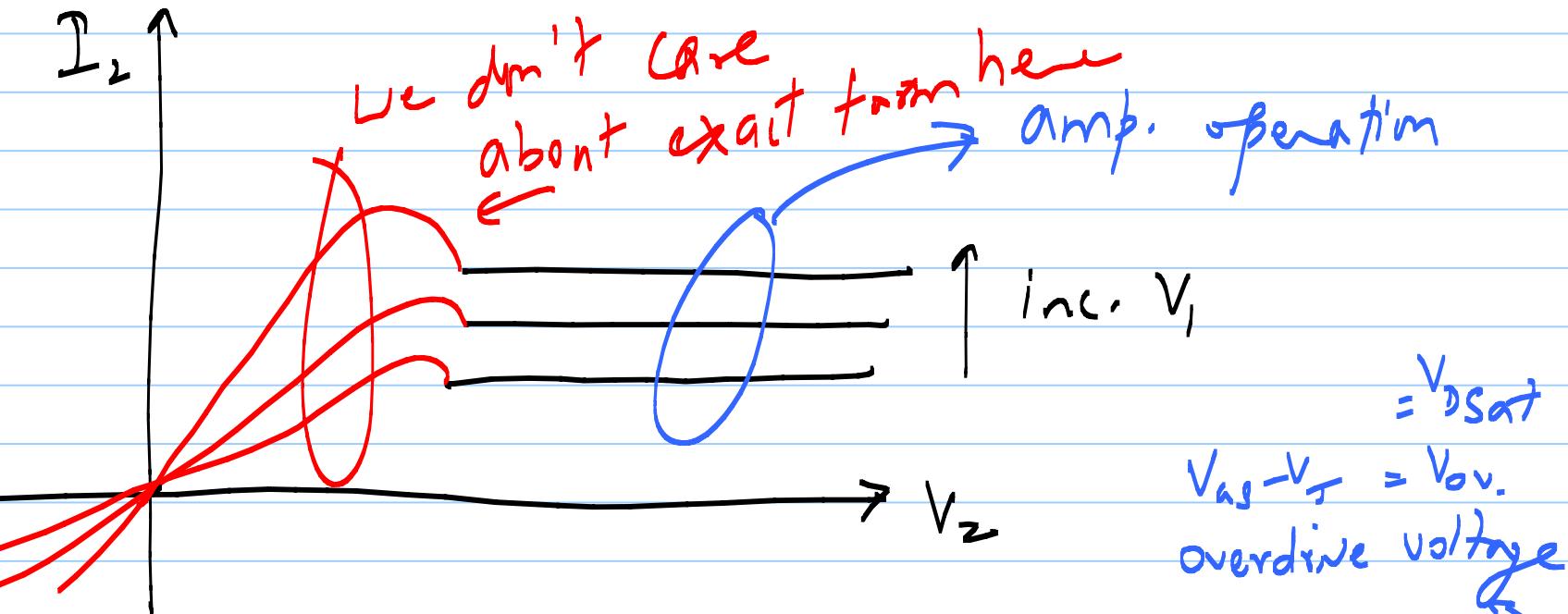

$$I_D = 0 \text{ if } V_{GS} < V_T \quad (\text{off})$$

$$I_D = \frac{1}{2} \mu_n C_ox \frac{W}{L} (V_{GS} - V_T)^2 \quad \text{if } V_{DS} \geq V_{GS} - V_T \quad (\text{sat.})$$
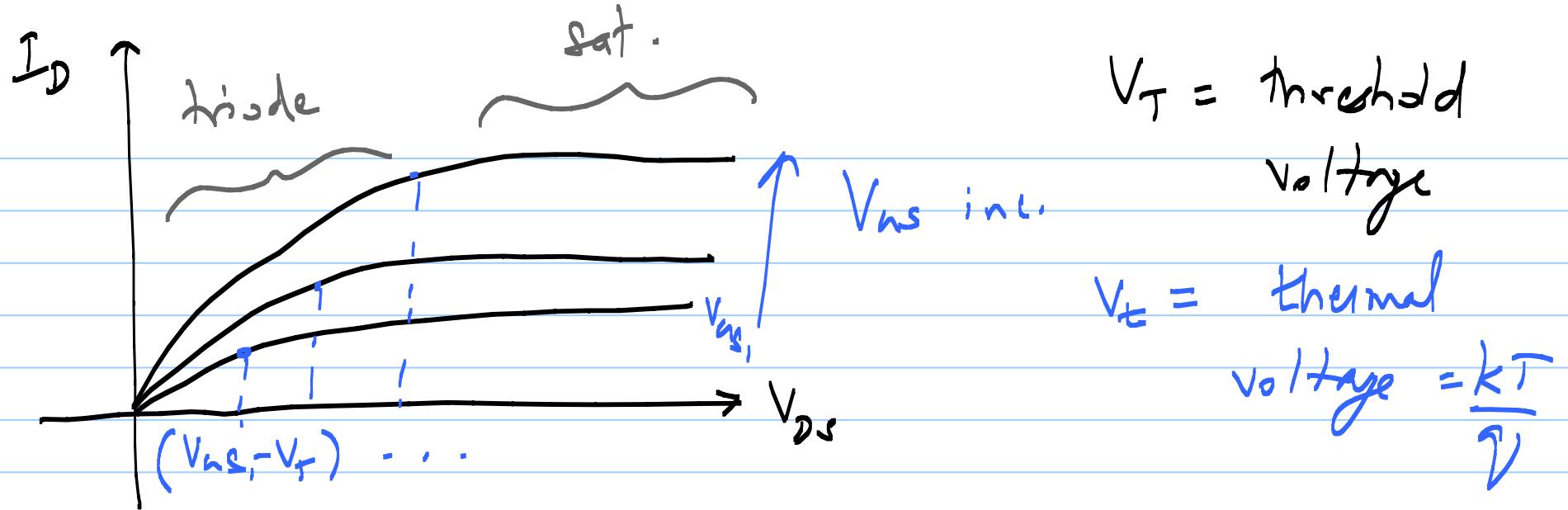
$$I_D = \mu_n C_ox \frac{W}{L} (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \quad \text{if } V_{GS} > V_T \text{ and } V_{DS} \leq V_{GS} - V_T$$



Amplifier: Use sat. region

$$I_A = 0 ; \quad I_D = \frac{1}{2} \mu_n C_{ox} \times \frac{W}{L} (V_{ds} - V_T)^2$$

use this to derive op. pt.

$$y_{11} = \frac{\partial I_A}{\partial V_{ds}} = 0 ; \quad y_{12} = \frac{\partial I_A}{\partial V_{ds}} = 0 ;$$

$$y_{22} = \frac{\partial I_D}{\partial V_{ds}} = 0 ; \quad y_{21} = \frac{\partial I_D}{\partial V_{ds}}$$

$$y_{21} = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T) = g_m$$

transconductance

^{of}
MOSFET

$$1) \quad g_m = \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)$$

$$2) \quad g_m = 2 \times \frac{1}{2} \times \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2 \times \frac{1}{(V_{GS} - V_T)}$$

$$= \frac{2 I_D}{V_{GS} - V_T}$$


$$3) \quad g_m^2 = 2 \times \frac{1}{2} \mu_n^2 C_{ox}^2 \left(\frac{W}{L} \right)^2 (V_{GS} - V_T)^2$$

$$= 2 \mu_n C_{ox} \left(\frac{W}{L} \right) I_D$$

$$g_m = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D}$$

$$[Y] = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix}$$

MOSFET Amplifier

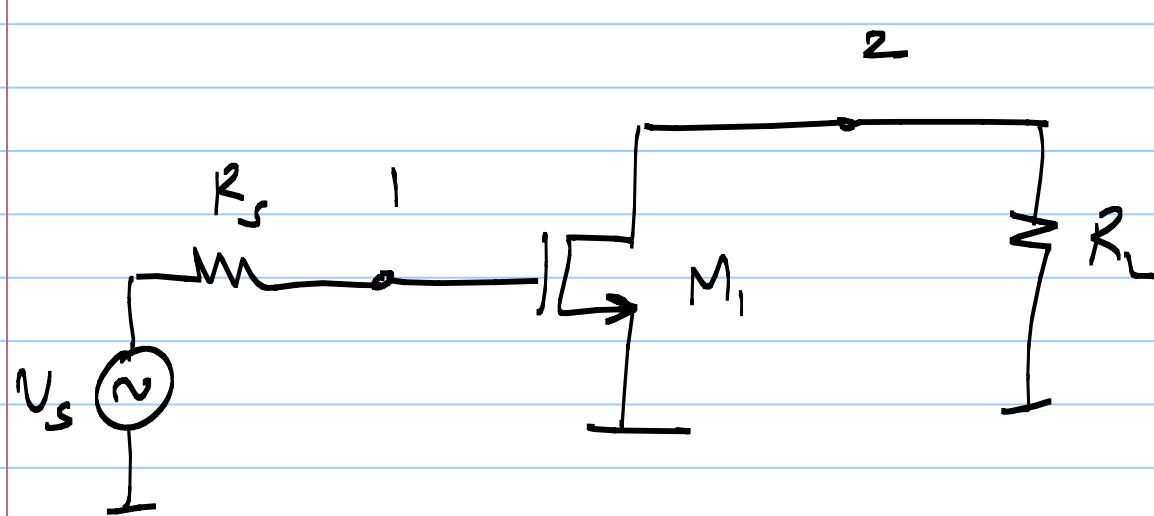

Small-signal picture
(op. pt. should be such that M_1 is biased in sat.)


In triode region :

$$y_{11} = y_{12} = 0$$

$$y_{22} = \frac{\partial I_D}{\partial V_{DS}} = \frac{\partial}{\partial V_{DS}} \left[\mu_n C_{ox} \left(\frac{w}{L} \right) \left\{ (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right\} \right]$$
$$= \mu_n C_{ox} \left(\frac{w}{L} \right) (V_{GS} - V_T - V_{DS}) \neq 0$$

$$y_{21} = \frac{\partial I_D}{\partial V_{GS}}$$


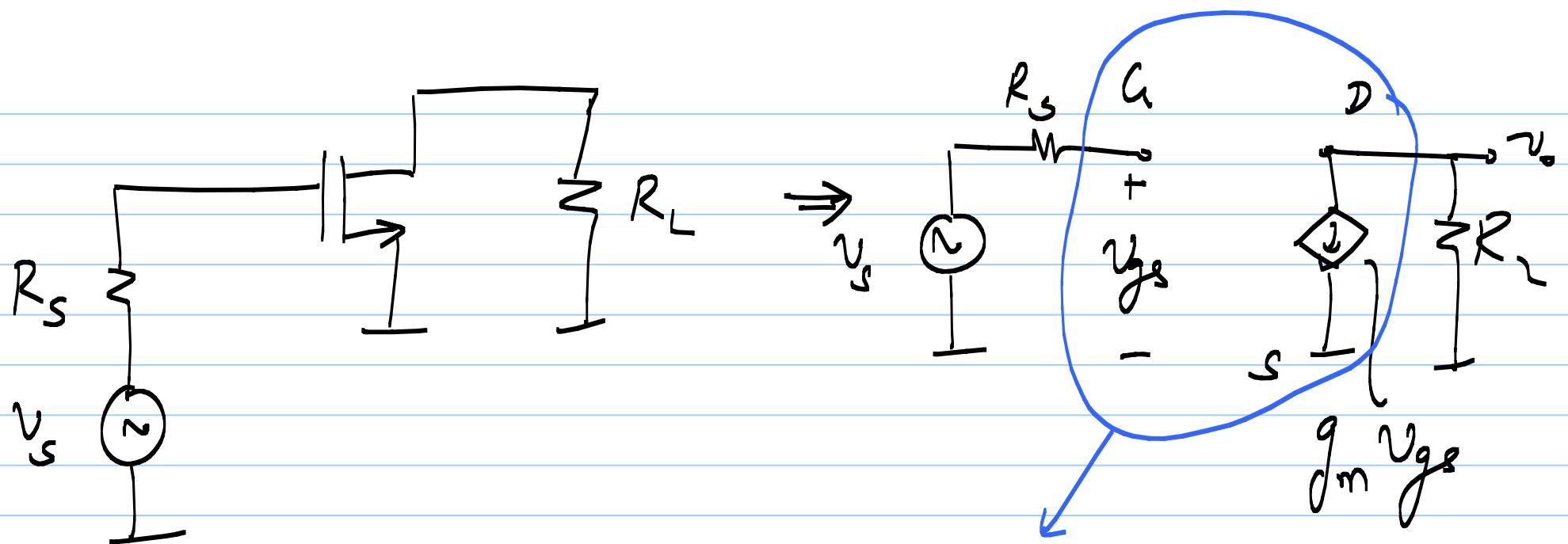
$$= \mu_n C_{ox} \left(\frac{w}{L} \right) \cdot V_{DS} \quad \left\{ \begin{array}{l} V_{DS} < (V_{GS} - V_T) \end{array} \right\}$$



SS model of MOSFET


$$\text{gain} = \frac{v_o}{v_s} = -g_m R_L$$

MOSFET Biasing :

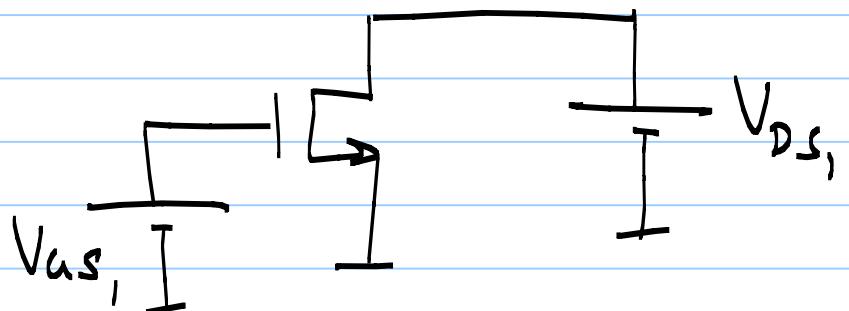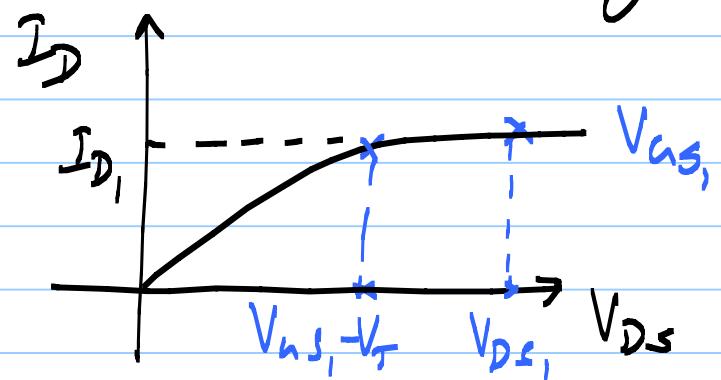

Add signal source & load to DC biased MOSFET:

$$- R_L + V_{R_L} = I_D \cdot R_L$$


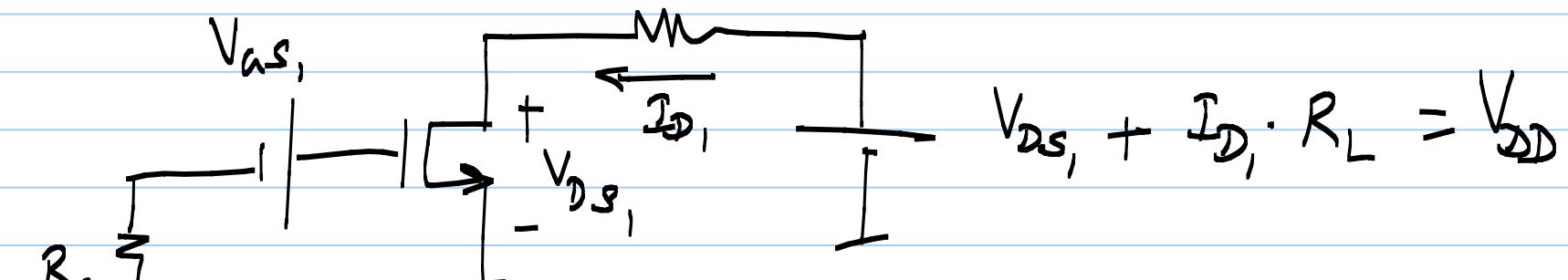


$$V_{DS} + I_D \cdot R_L = V_{DD}$$

$$v_s$$

DC

SS

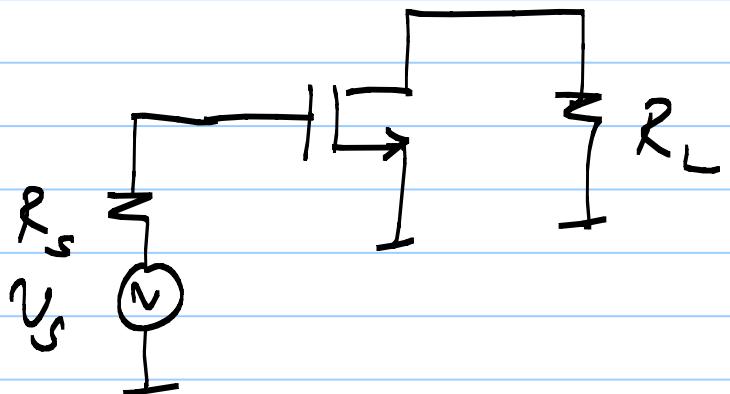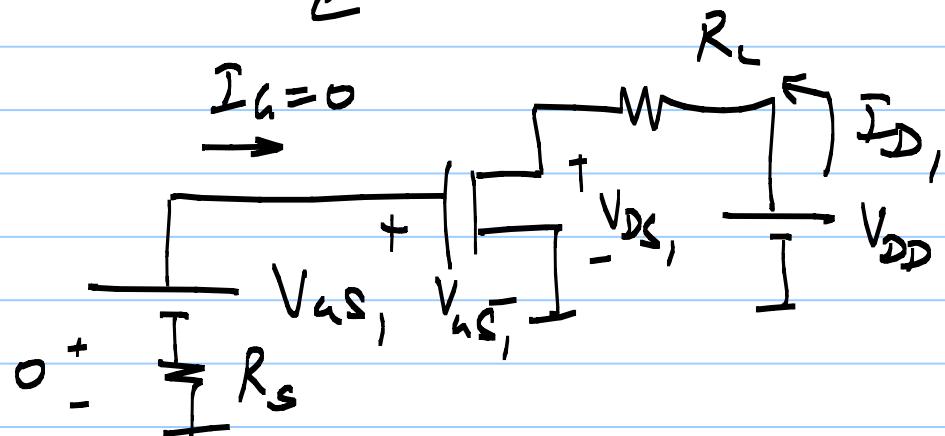



* Avoid use of 2 batteries:

⇒ generate V_{GS} , from V_{DD}

$$(V_{DD} > V_{GS})$$

largest voltage
in the circuit

DC:

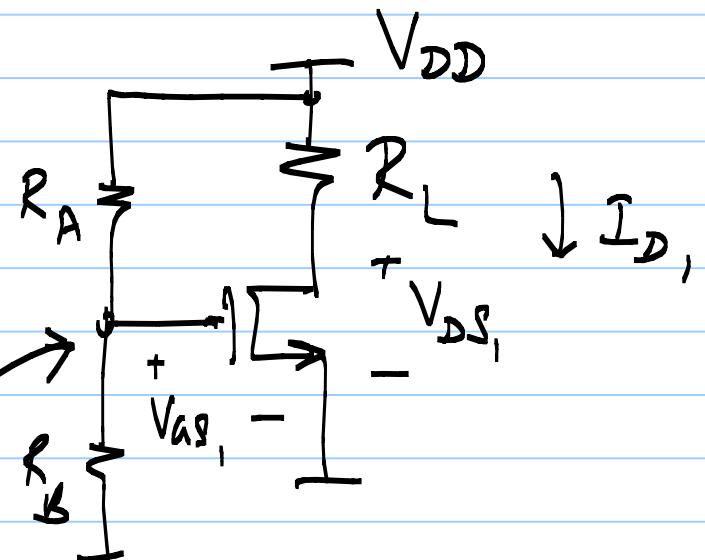
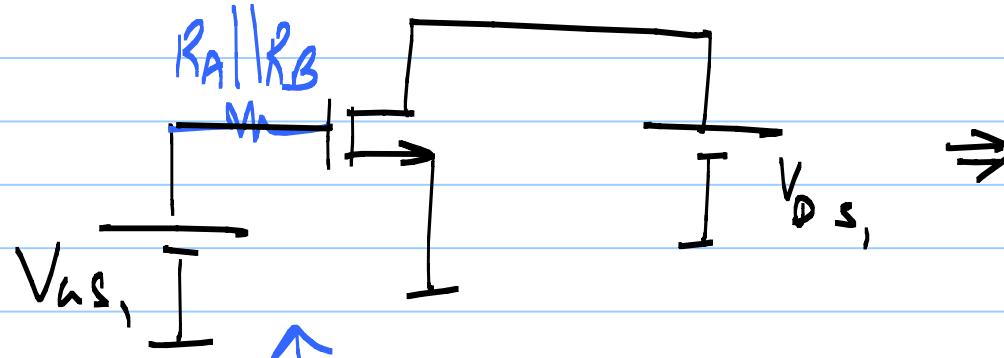


$$V_{GS} = \frac{R_B}{R_A + R_B} \cdot V_{DD}$$

19 | 8 | 2020

Lecture 9

NL 2-port (incremental view)


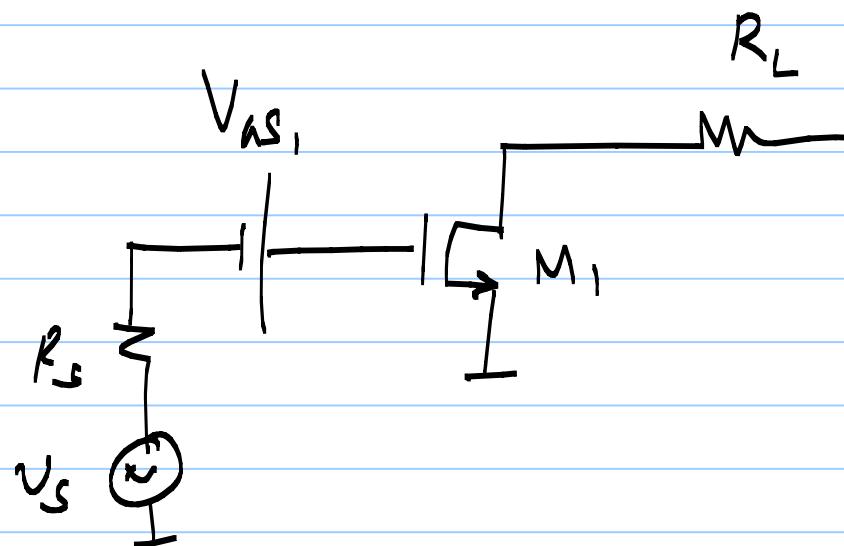
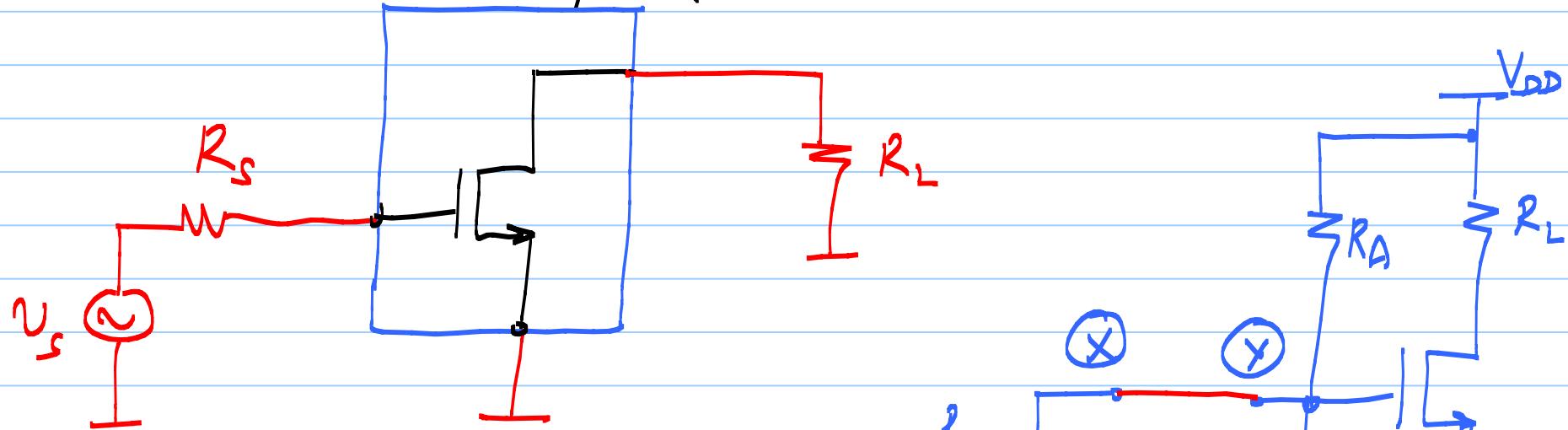





v_s \rightarrow DC current flow \rightarrow * Might disturb op. pt. of preceding circuit


* V_{AS1} itself changes

$$V_{AS1}' = \frac{R_B || R_s}{R_A + 2B || R_s} \cdot V_{DD}$$

* We want no DC current flow through R_s

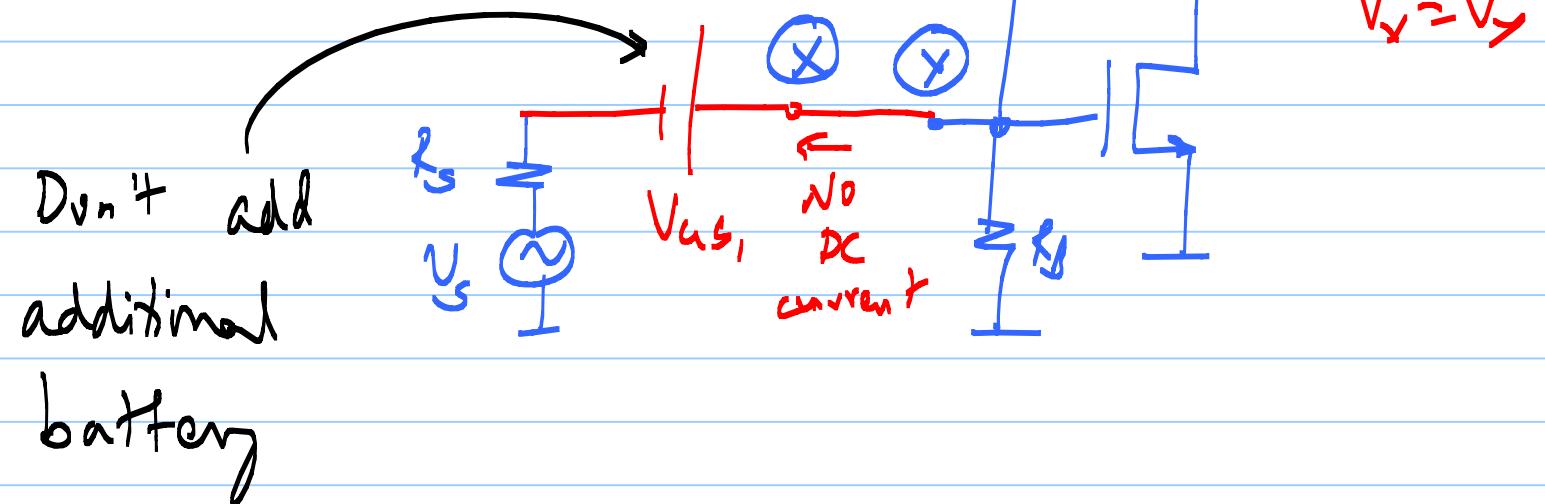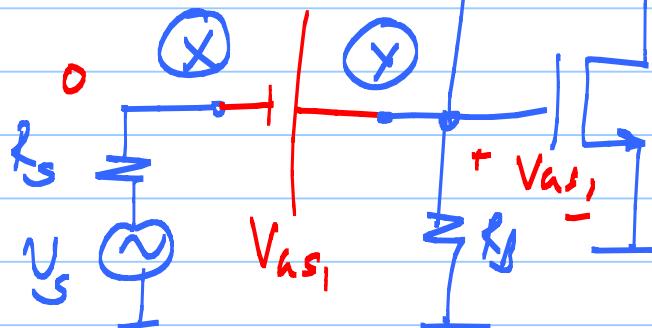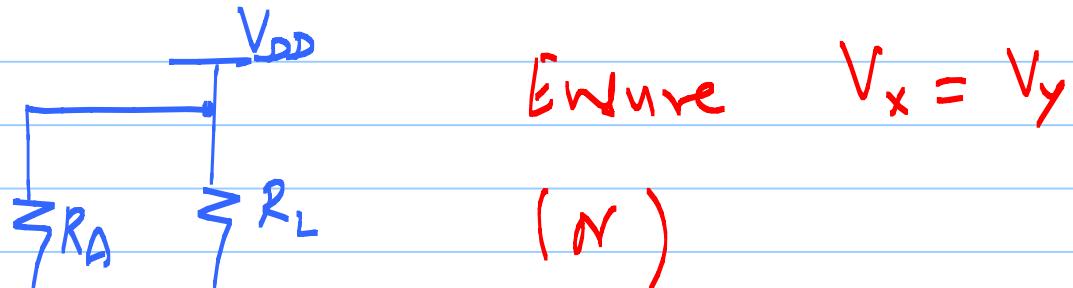

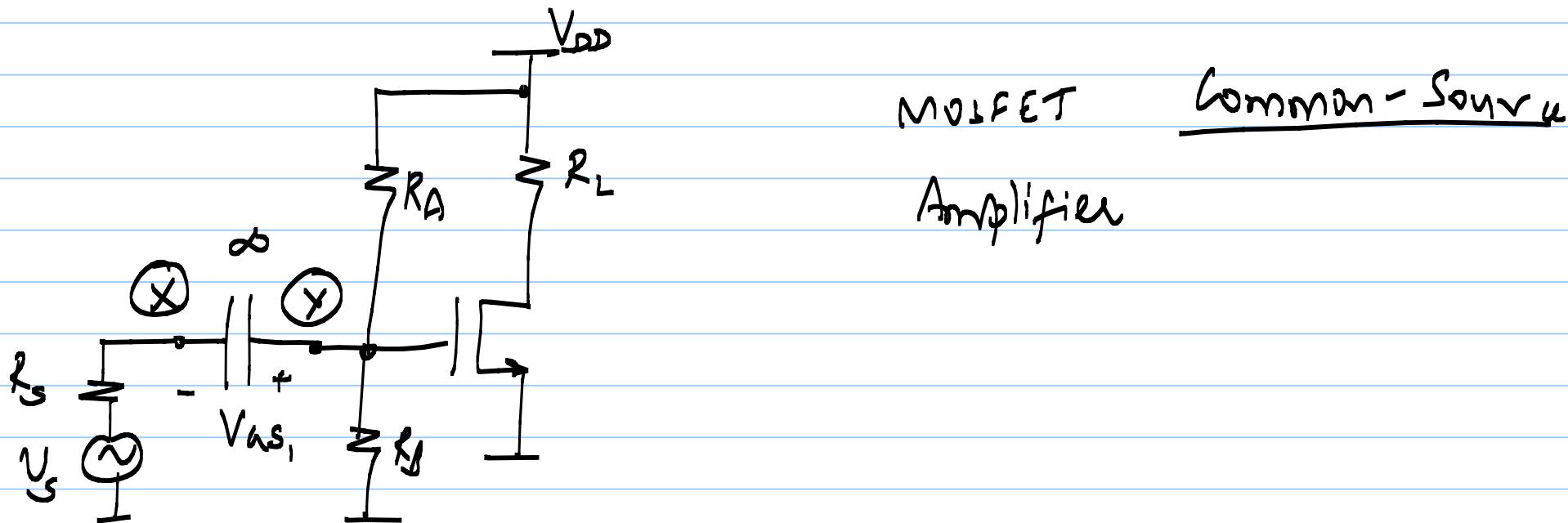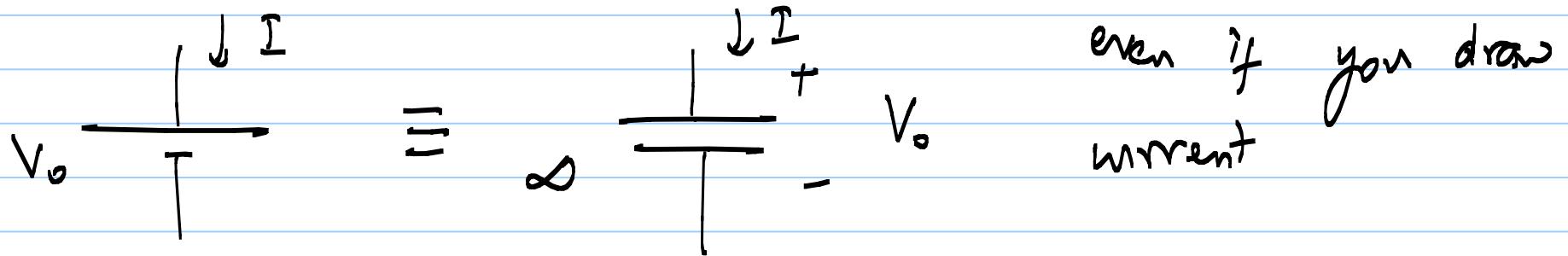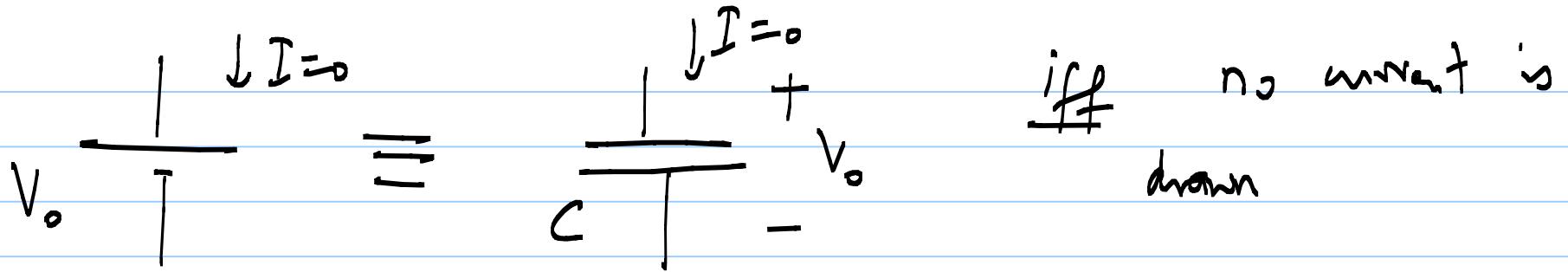

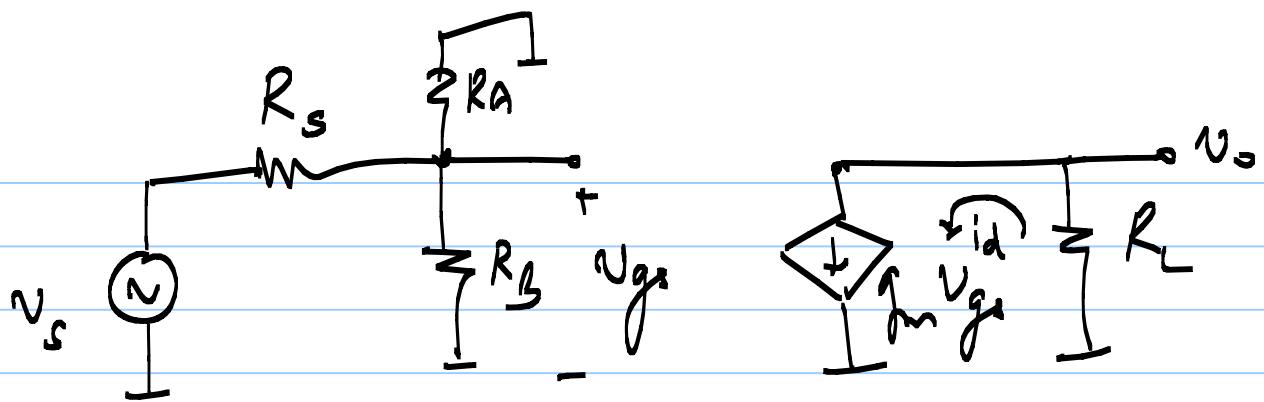

$y_{11} \neq 0$

$$v_{gs} = \frac{R_A \parallel R_B}{R_s + R_A \parallel R_B} \cdot v_s$$

$$v_o = -g_m R_L \cdot v_{gs} = -g_m R_L \cdot \frac{R_A \parallel R_B}{R_s + R_A \parallel R_B} \cdot v_s$$

1) Choose $R_A \parallel R_B \gg R_s$


$$\frac{R_B}{R_A + R_B} \cdot v_{o0} = V_{LS},$$

2) then $\frac{V_o}{V_s} \approx -g_m R_L$


$$i_d = g_m v_{gs} = g_m \cdot \left(\frac{R_A || R_S}{R_S + R_A || R_B} \right) \cdot v_s$$

$$v_d = v_o = - i_d R_L$$


3) Suppose : No DC current through R_L :

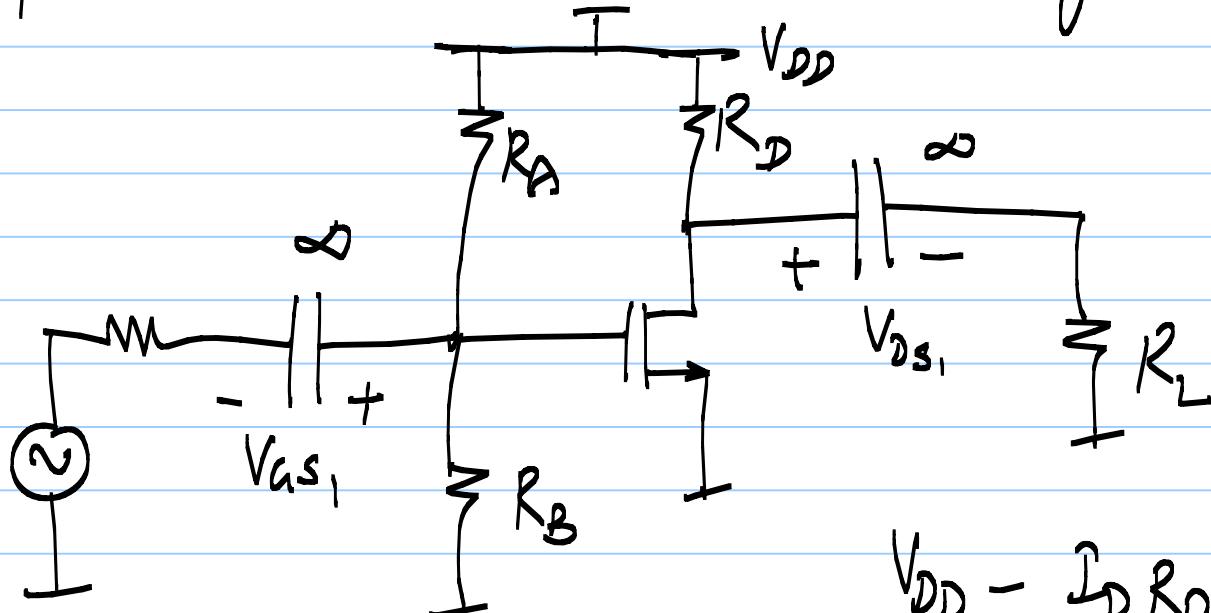


$$V_{DD} - I_D R_D = V_{DS_1}$$

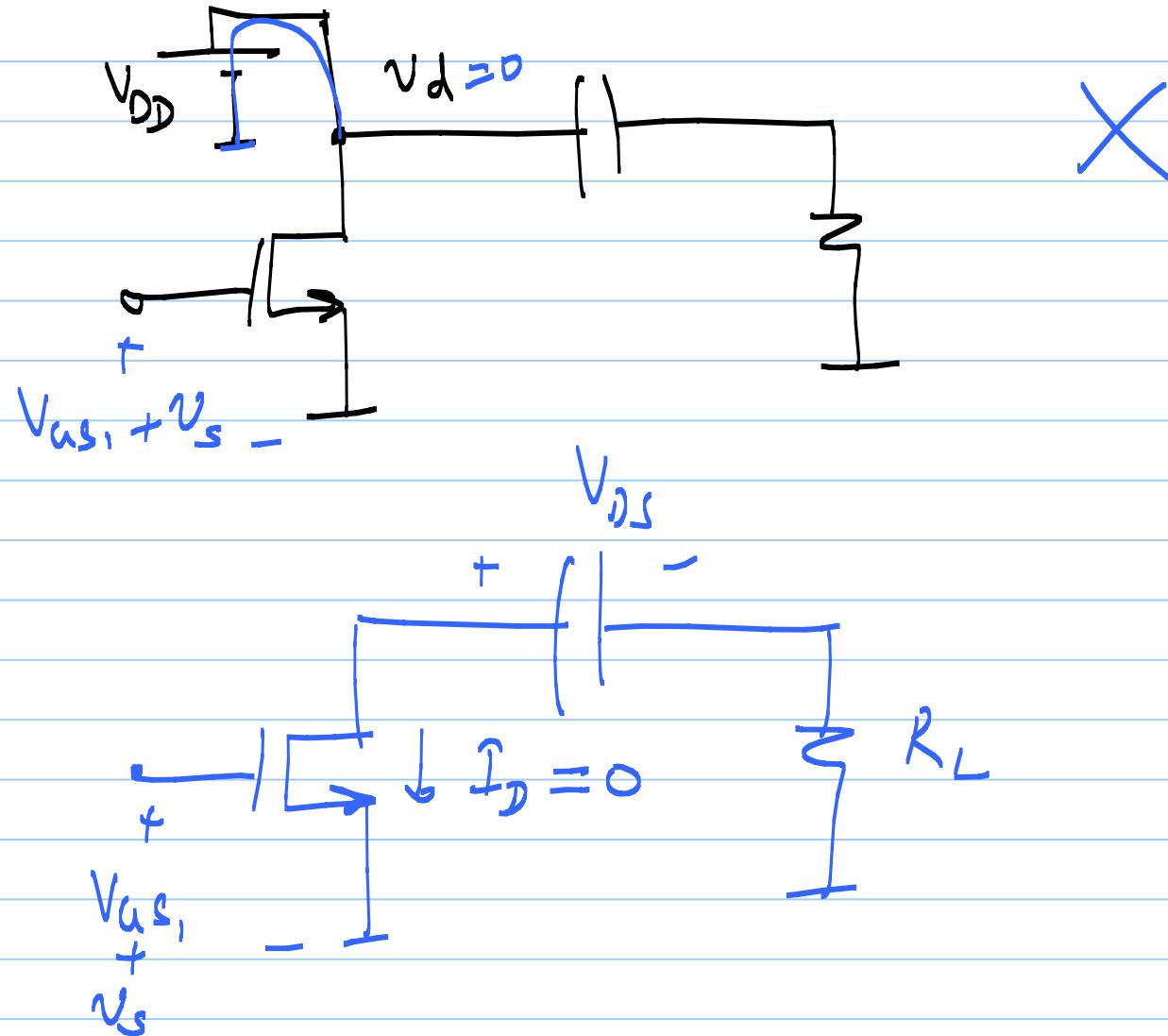

Assume $V_{DS_1} > V_{AS_1}$

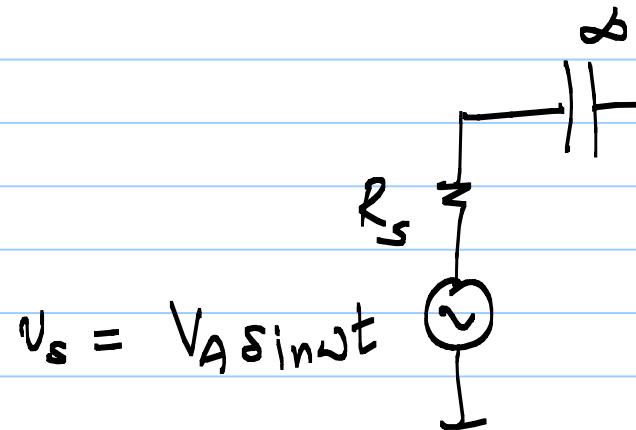

$$v_s = V_A \sin \omega t$$

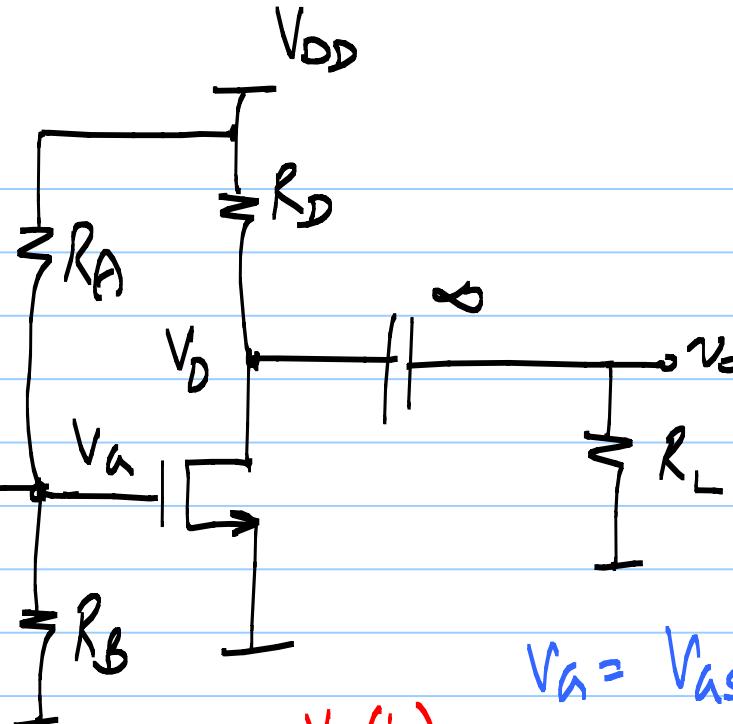


C SA

$$\frac{v_o}{v_s} = -g_m(R_D || R_L)$$

$$V_A = V_{AS_1} + V_A \sin \omega t$$

$$V_D = V_{DS_1} - g_m(R_D || R_L) V_A \sin \omega t$$


$$= V_{DS_1} - G V_A \sin \omega t$$

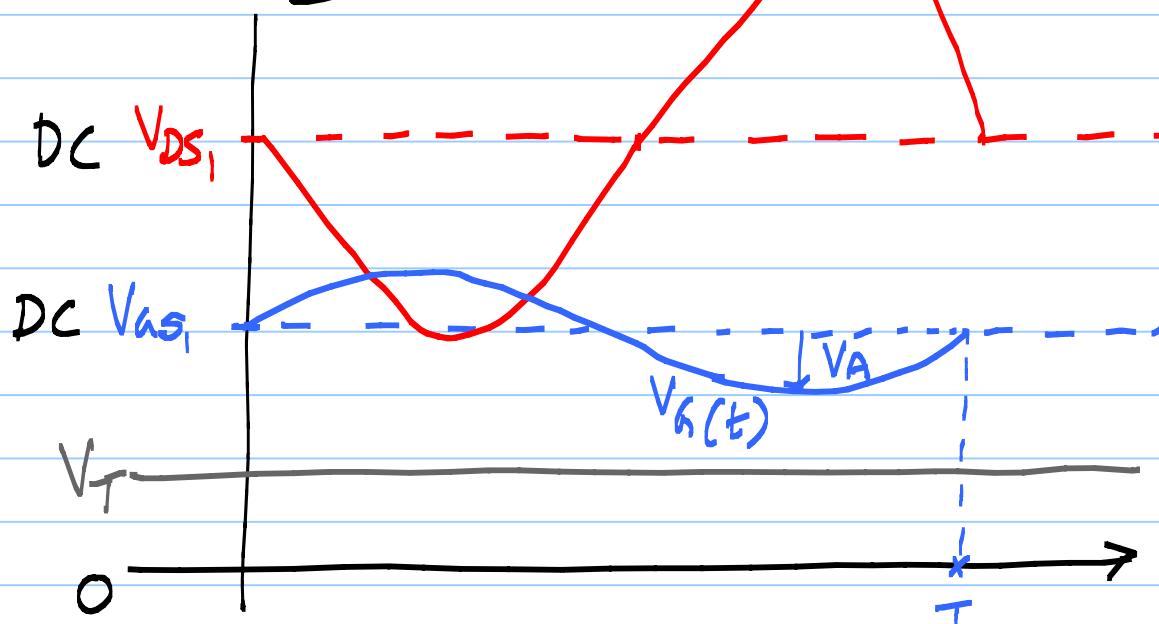

Triode boundary

$$V_{DS} > V_{AS} - V_T$$

at all time instants.

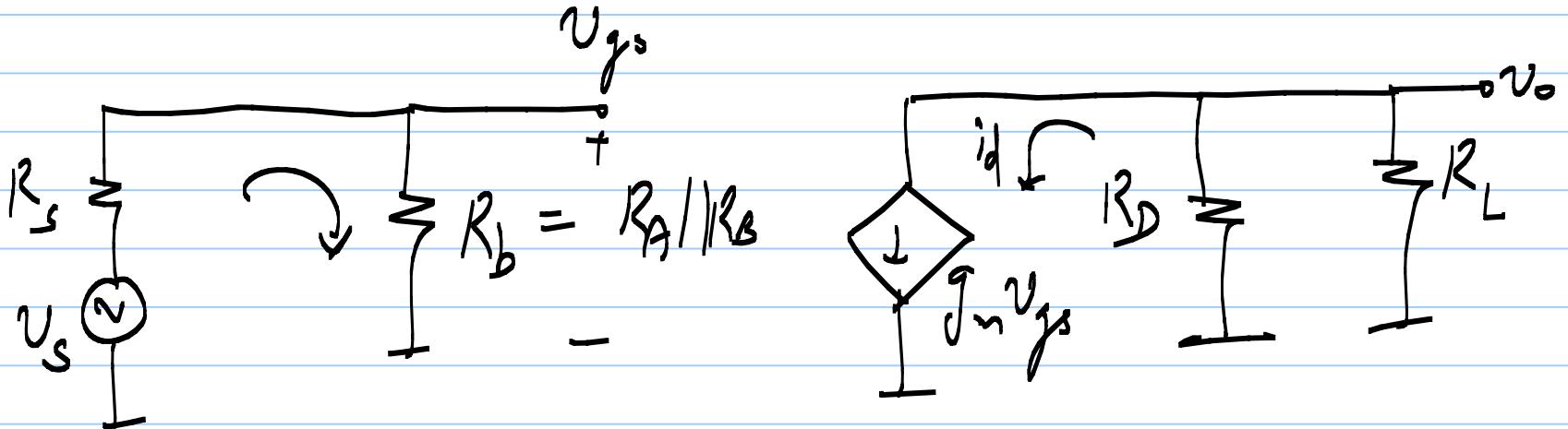

$$v_{gs} = \frac{R_b}{R_s + R_b} \cdot v_s \approx v_s \quad \text{if} \quad R_s \ll R_b$$


$$i_d = g_m v_{gs} \approx g_m v_s$$

$$v_o = -i_d \cdot (R_D || R_L) = -g_m v_s (R_D || R_L)$$


$$\frac{v_o}{v_s} = -g_m (R_D || R_L) = -G$$

20/8/2020

Lecture 10

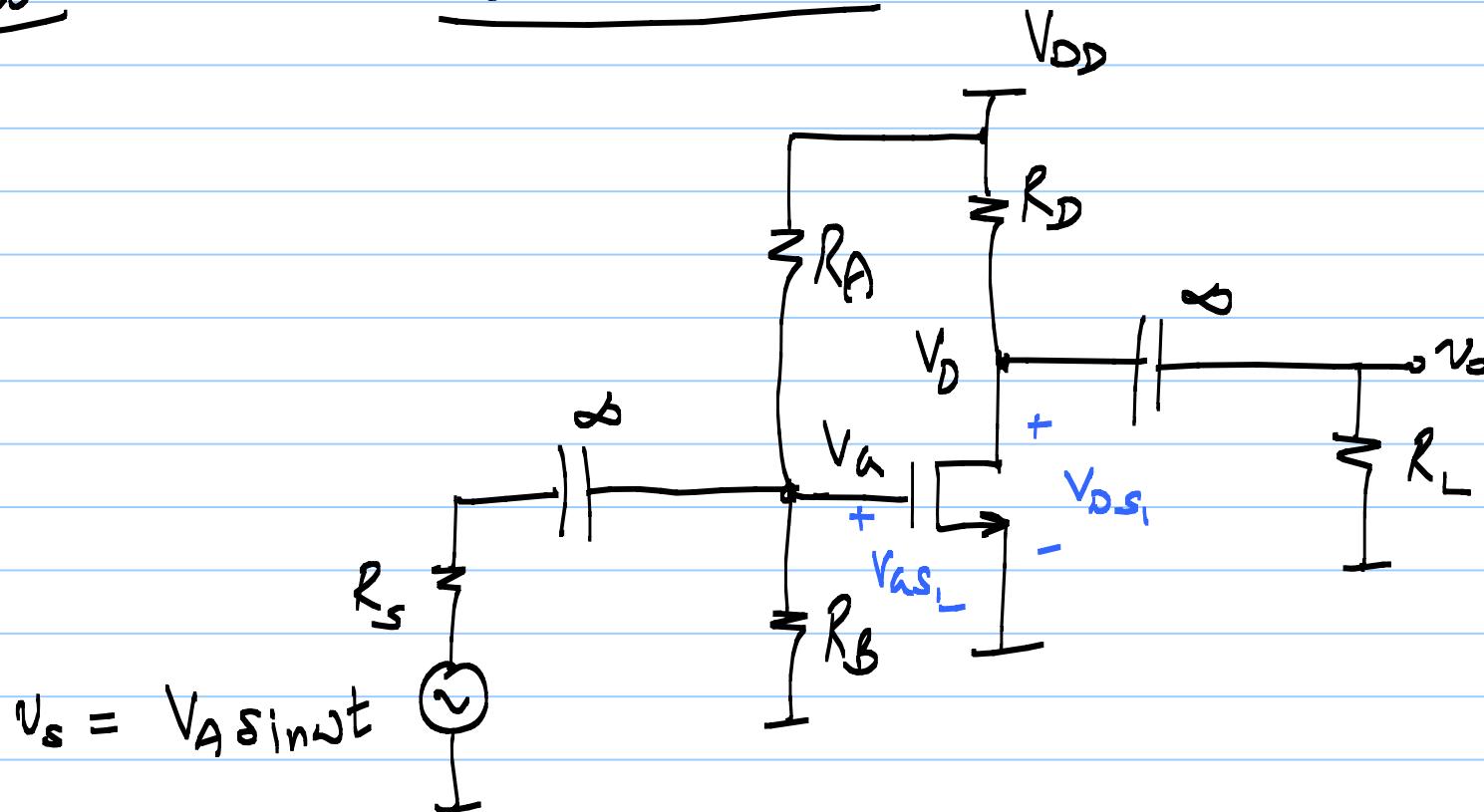

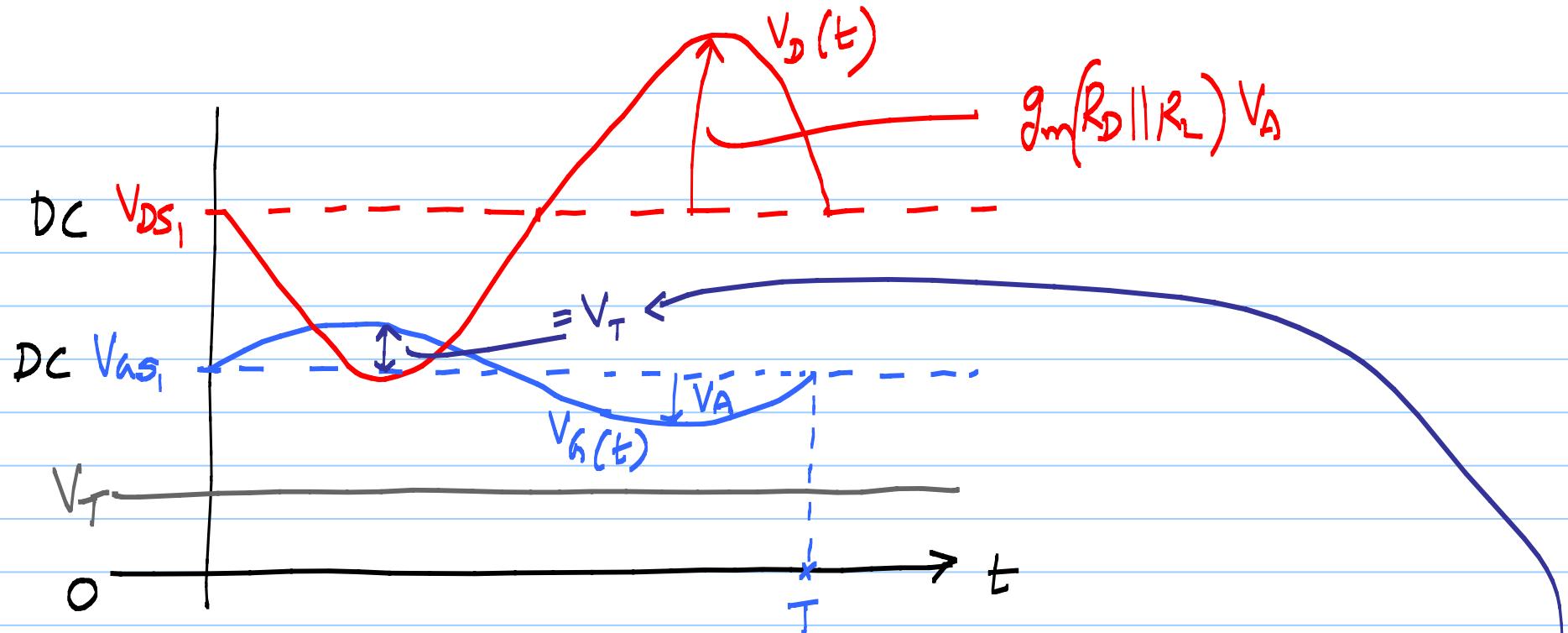
- * $V_{DS}(t) > V_{ASL}(t) - V_T$ at all times in the period so that device is in saturation.



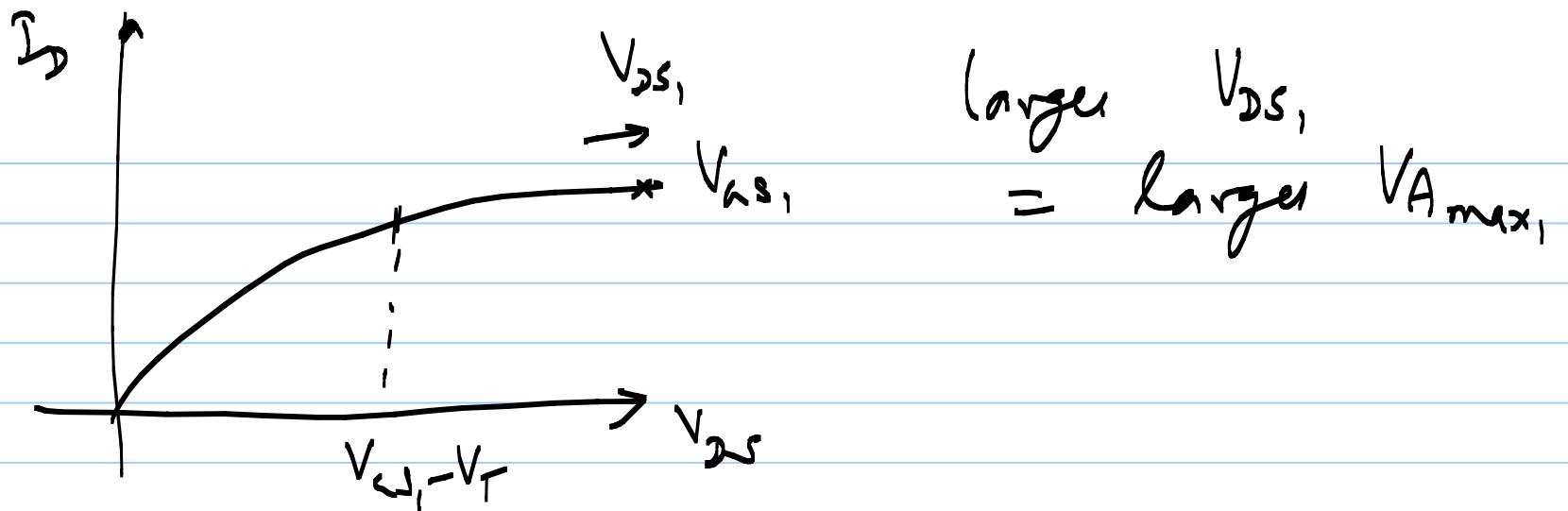1) Limit of V_A : instantaneous $V_{DS}(t) = V_{AS}(t) - V_T$


$$(N) \quad V_D(t) = V_A(t) - V_T$$

$V_{A_{max}}$ = maximum value of V_A that keeps M₁ from going into triode (+ve Half cycle of input sinusoid)



$$V_{DS1} - g_m (R_D || R_L) \cdot V_{Amax1} = V_{AS1} + V_{Amax1} - V_T$$

$$V_{Amax1} = \frac{V_{DS1} - V_{AS1} + V_T}{1 + g_m (R_D || R_L)}$$

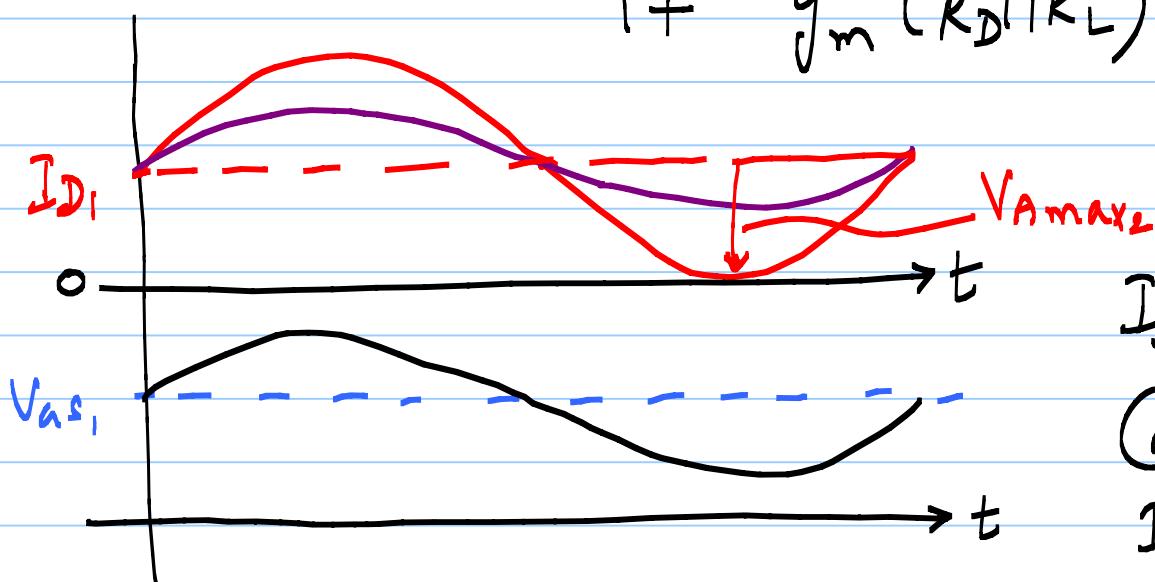

$$I_D = I_{D1} + i_d$$

$$I_D(t) = I_{D1} + g_m V_A \sin \omega t$$

$$\textcircled{a} \quad V_A = V_{Amax2}$$

$$I_D(t) = 0 \quad \textcircled{b} \quad \text{neg. peak.}$$


Device M_1 cuts off. @ $V_{A_{max_2}}$
just

Any further increase in $V_A \rightarrow$ clipped sinusoid (current)

Set $I_D(t) = 0$ @ -ve peak

$$I_{D_1} - g_m V_{A_{max_2}} = 0 \Rightarrow V_{A_{max_2}} = \frac{I_{D_1}}{g_m}$$

What is $V_D(t)$ when $I_D(t) = 0$?

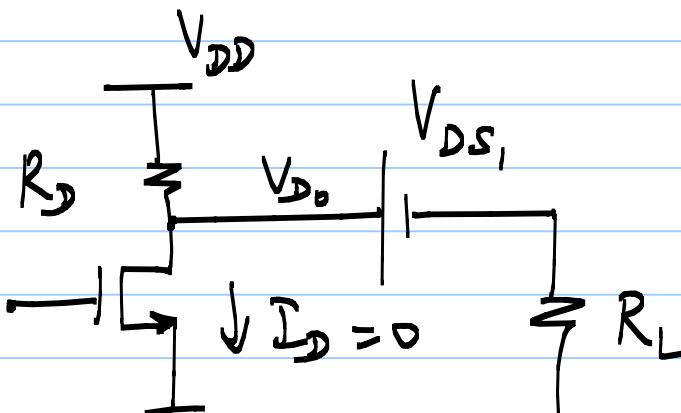

$$\star I_D = 0$$

* KCL @ drain

$$\frac{V_{DD} - V_{DS0}}{R_D} = \frac{V_{DS0} - V_{DS1}}{R_L}$$

$$V_{DS0} = \frac{R_L V_{DS0} + R_D V_{DS1}}{R_L + R_D}$$

Swing limits of CSA


* In general, $V_{A_{max_1}} \neq V_{A_{max_2}}$

* swing limit = $\min \{V_{A_{max_1}}, V_{A_{max_2}}\}$

* hood design : choose $V_{A_{max_1}} = V_{A_{max_2}}$

choose (I_D, V_{DS}) { @ +ve H.C. peak, M₁ just enters triode
@ -ve H.C. peak, M₁ just cuts off

Example :

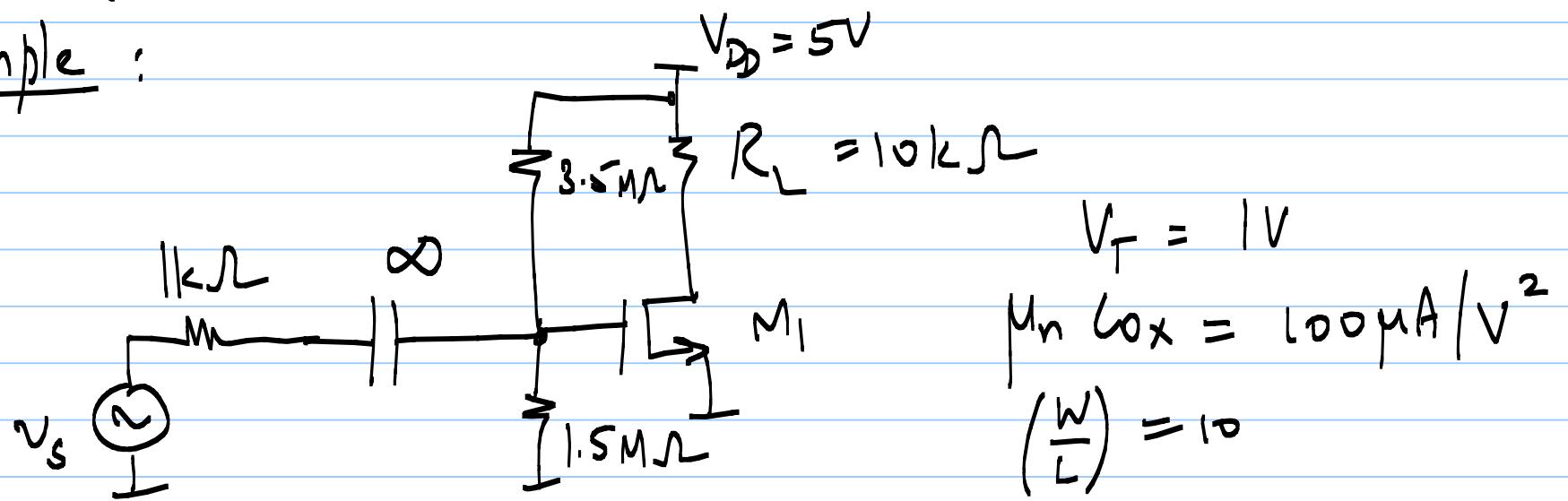

$$V_{AS_1} = 1.5V$$

$$I_{D_1} = \frac{1}{2} 100 \times 10^{-6} \times 10 \times (0.5)^2 = 125 \mu A$$

$$\begin{aligned} V_{DS_1} &= V_{DD} - I_{D_1} \cdot R_L = 5 - (125 \times 10^{-6}) (10 \times 10^3) \\ &= 3.75V \end{aligned}$$

$$g_{m_1} = \frac{2I_{D_1}}{V_{AS_1} - V_T} = \frac{0.25mA}{0.5} = 0.5 mS$$

Inc. gain $b = -g_{m_1} R_L = -5$

Triode limit (+ve hc)

$$V_a = 1.5V + V_A \sin \omega t \quad \left. \right) \quad V_D = V_C - V_T$$

$$V_D = 3.75V - 5V_A \sin \omega t$$

$$3.75 - 5V_{A_1} = 1.5 + V_{A_1} - 1$$


$$V_{A_1} = \frac{3.25}{6} = 541.67 \text{ mV} = V_{A_{\max}}$$

Cut off limit (-ve H.C.)

$$\begin{aligned} I_D &= I_{D_1} + g_m V_A \sin \omega t \\ &= 125 \mu\text{A} + (0.5 \text{ mS}) V_A \sin \omega t \end{aligned}$$




$$V_{A_2} = \frac{I_{D_1}}{g_m} = \frac{125 \mu\text{A}}{0.5 \text{ mS}} = 250 \text{ mV} = V_{A_{\max_2}}$$
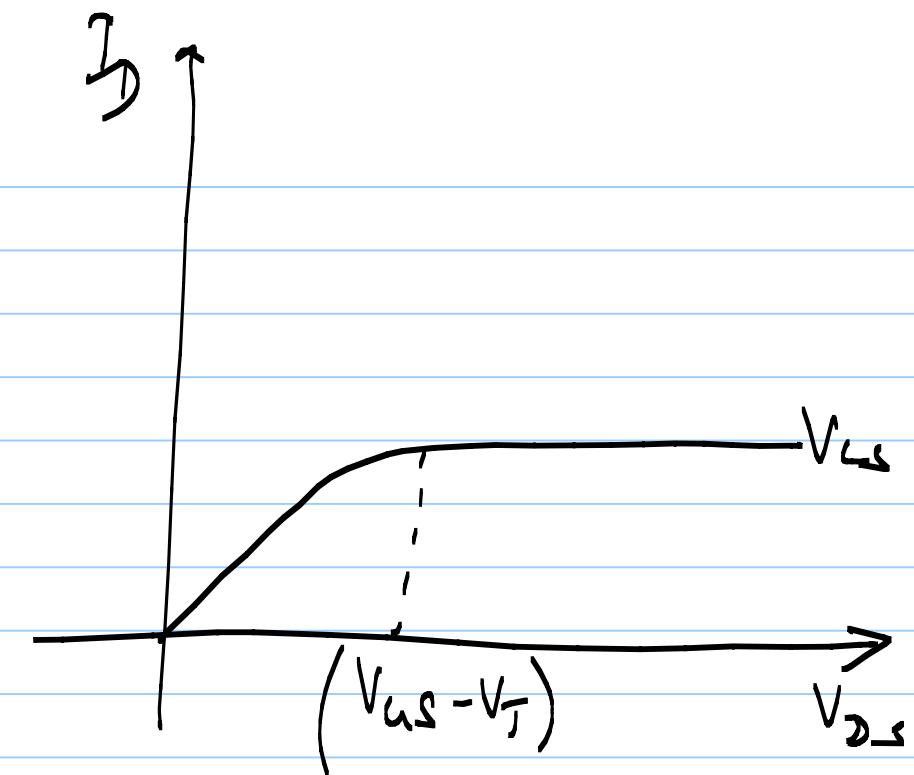
$$V_{A_{\max}} = \min. \{ V_{A_1}, V_{A_2} \} = 250 \text{ mV}$$



21/8/2020

Lecture 11

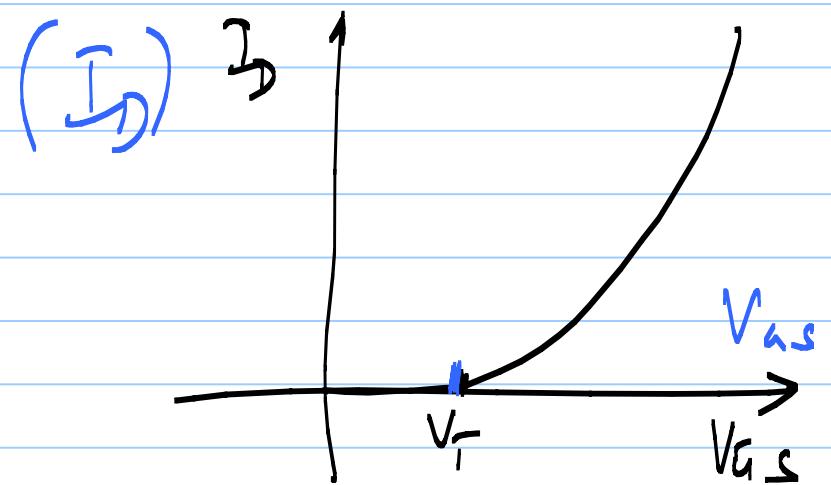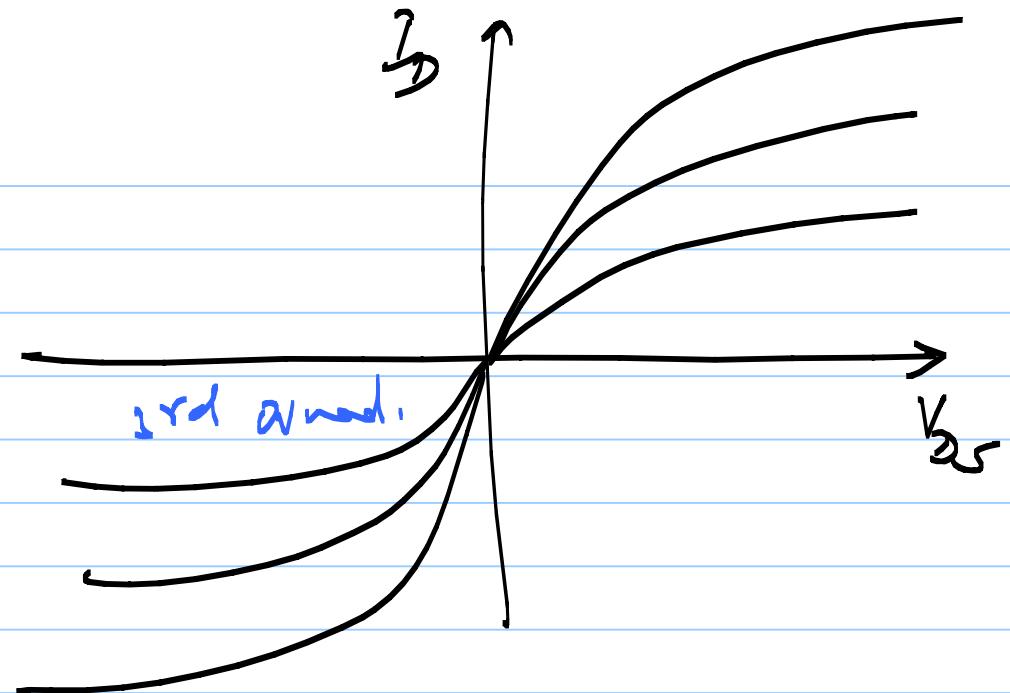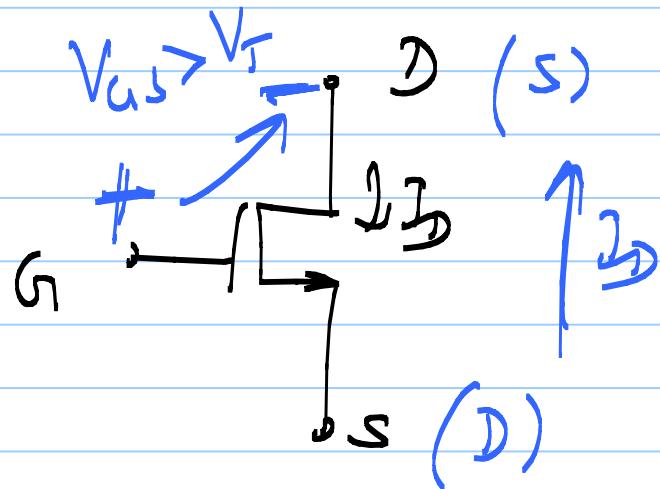


Cut off condition @ V_{as}

$$I_D = 0 \Rightarrow V_{as} \leq V_T$$

$V_{us} = V_T$ limit

$$V_{as,} + V_A \underbrace{\sin \omega t}_{-1} = V_T$$
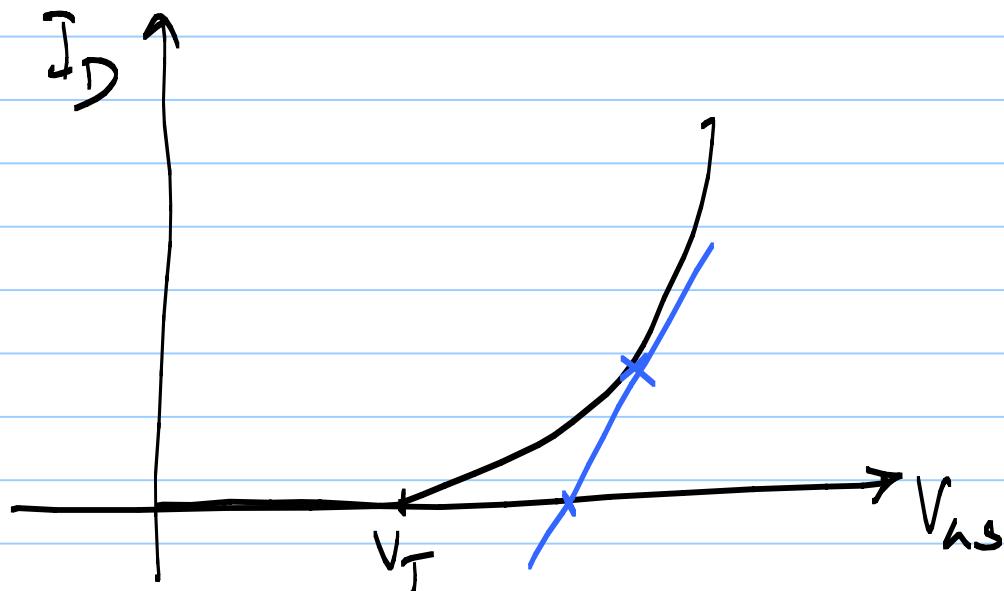
$$V_{A_3} = V_{as,} - V_T = 1.5V - 1V = 50mV$$



In sat. region

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{ds} - V_T)^2 \quad \text{No dep. in } V_{ds}$$

$$I_D = f(V_{ds}, V_{gs})$$

$$I_D + i_d = f(V_{ds} + v_{gs}, V_{ds} + v_{ds})$$

$$= f(V_{gs}, V_{ds}) + \frac{\partial I_D}{\partial V_{gs}} \cdot v_{gs} + \frac{\partial I_D}{\partial V_{ds}} \cdot v_{ds} \xrightarrow{g_m}$$

$$+ \frac{1}{2} \frac{\partial^2 I_D}{\partial V_{gs}^2} \cdot v_{gs}^2 + \frac{1}{2} \frac{\partial^2 I_D}{\partial V_{ds}^2} \cdot v_{ds}^2$$

$$+ \frac{\partial^2 I_D}{\partial V_{gs} \partial V_{ds}} \cdot v_{gs} \cdot v_{ds} + \dots$$

$$\vec{I_D} + \vec{i_d} = \vec{B_D} + g_m v_{gs} + \frac{1}{2} \mu_n C_{ox} \left(\frac{w}{L} \right) \cdot v_{gs}^2$$

desired term
undefined term (NL)

(A)
(B)

$$(B) \ll (A)$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{w}{L} \right) \cdot v_{gs}^2 \ll g_m v_{gs}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{w}{L} \right) \cdot v_{gs}^2 \ll \mu_n C_{ox} \left(\frac{w}{L} \right) (V_{as} - V_T) \cdot v_{gs}$$

$$\underline{\underline{v_{gs} \ll 2(V_{as} - V_T)}}$$

In our example : $V_{GS} = \min \{ V_{A_1}, V_{A_2} \} = D \cdot 25V$

$$2(V_{AS} - V_T) = 1V$$

(B) \approx 25% of (A) { Not small enough }


THD : "Total Harmonic Distortion"

y. age.

25/8/20

Lecture 12

Real MOSFET characteristics

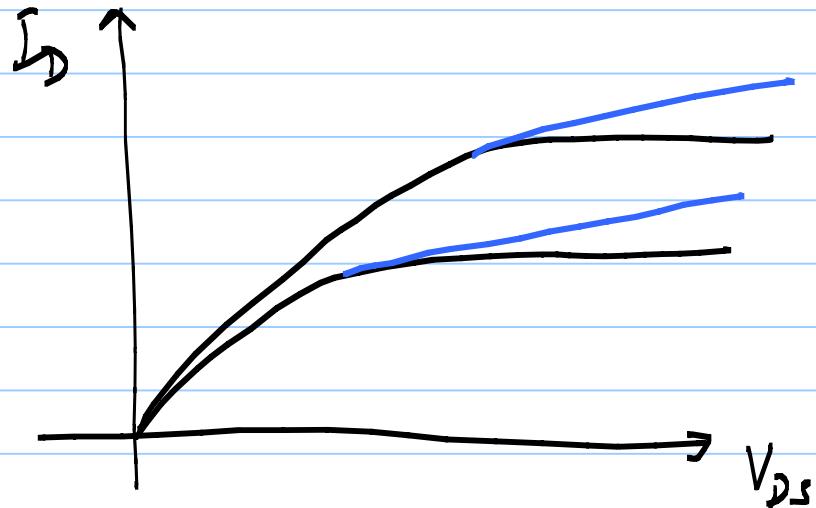

We assumed that in sat.,

$$I_D = f(V_{GS}) \text{ only}$$

In reality,

$$I_D = f(V_{GS}, V_{DS})$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

for a good MOSFET, $\lambda \ll 1$

"Channel Length Modulation"

for op. pt. calculations, we: $I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2$

2-part parameters:

$$y_{11} = y_{12} = 0$$

$$y_{21} = g_m = \frac{\partial I_D}{\partial V_{DS}} = \mu_n \text{Lox} \left(\frac{W}{L} \right) (V_{GS} - V_T) (1 + \lambda V_{DS})$$

$$\approx \mu_n \text{Lox} \left(\frac{W}{L} \right) (V_{GS} - V_T) \quad \left. \begin{array}{l} \text{assume same} \\ \text{as before} \end{array} \right\}$$


$$g_{DS} = y_{22} = \frac{\partial I_D}{\partial V_{DS}} = \frac{1}{2} \mu_n \text{Lox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2 \cdot \lambda$$

Output conductance
MOSFET


$$\approx I_D$$

$$g_{DS} \approx \lambda \cdot I_D$$
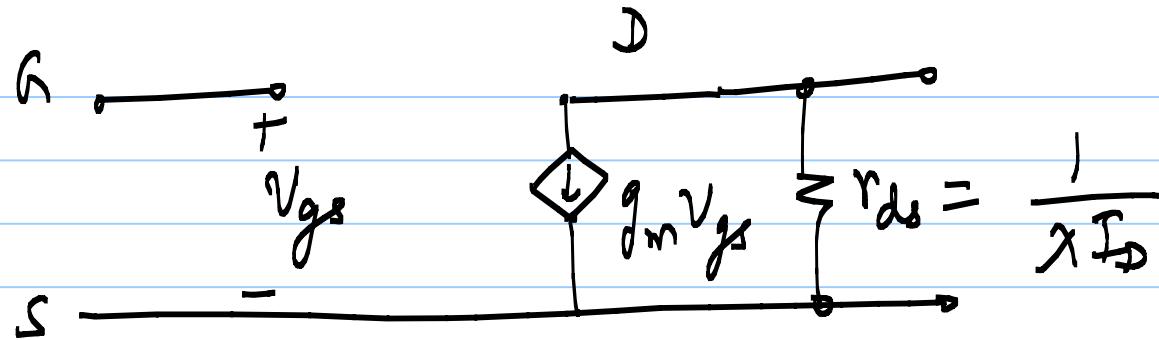
$$r_{DS} = \frac{1}{g_{DS}} = \frac{1}{\lambda I_D}$$




Common-Source amp:

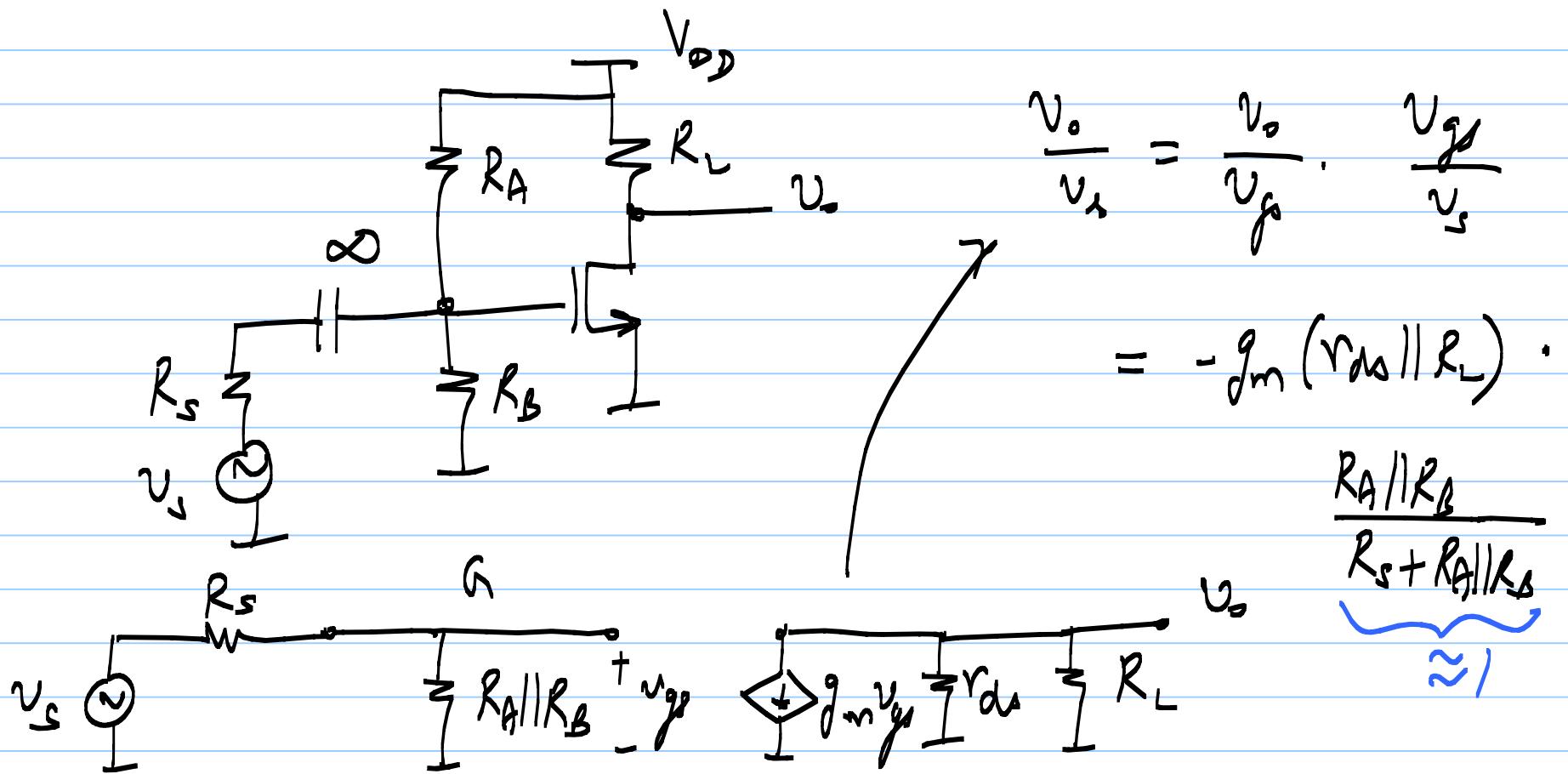


$$\frac{v_o}{v_s} \approx -g_m (r_{ds} || R_L) \quad \text{gain is smaller}$$

Max possible gain : $R_L = \infty$

$$| \text{max. gain} | = g_m r_{ds} \equiv \text{"intrinsic gain" of MOSFET}$$

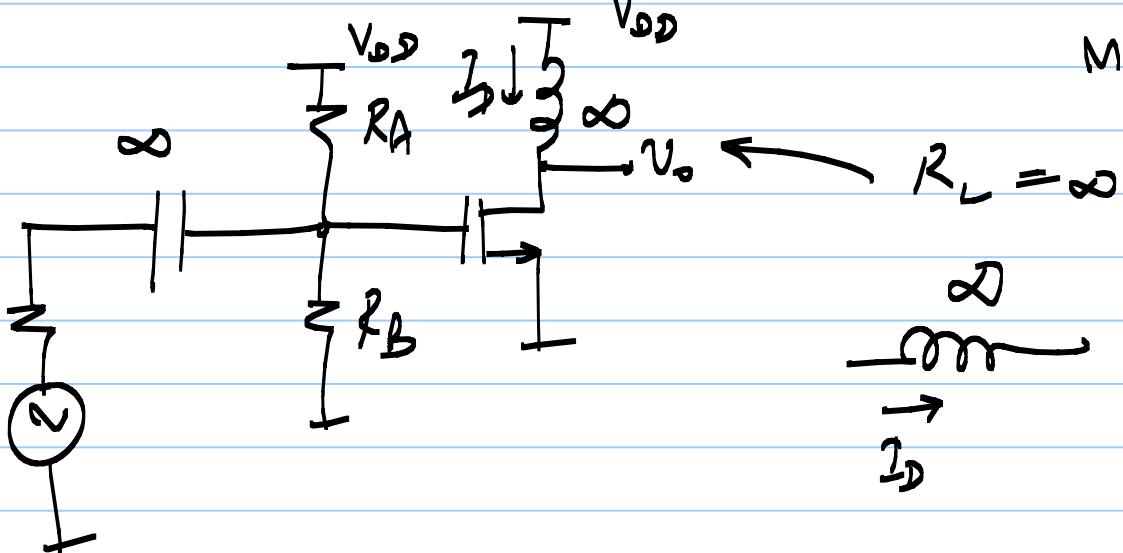

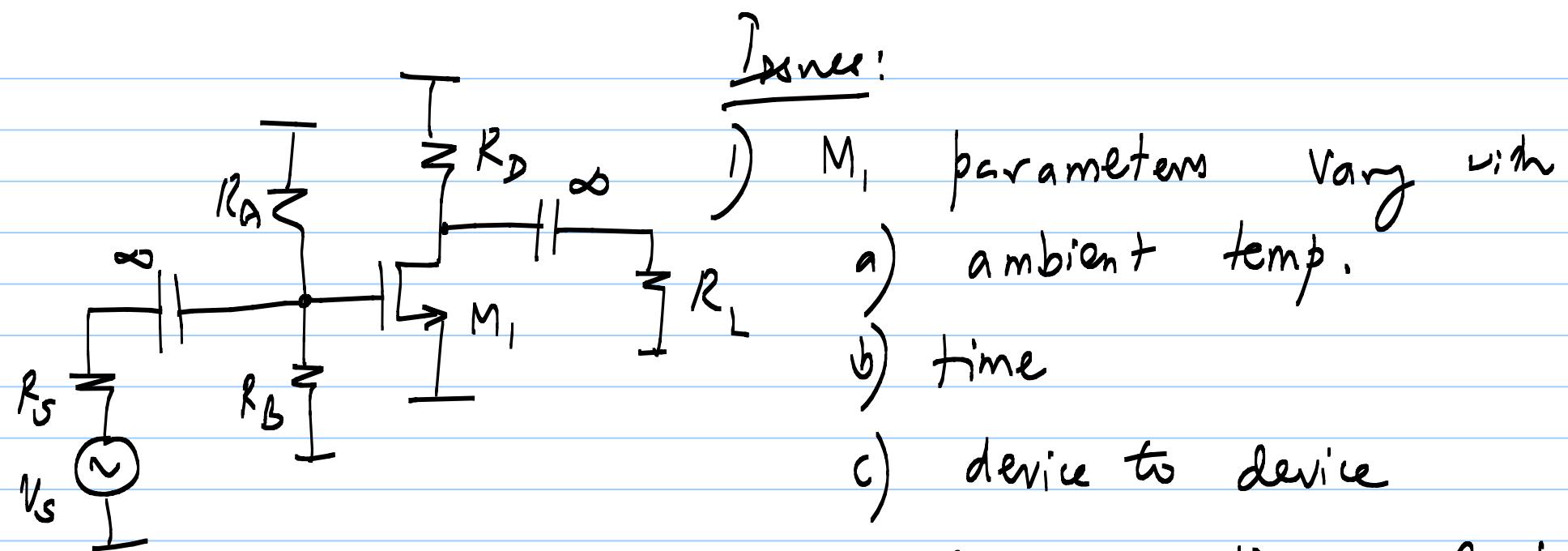$\frac{\omega}{\omega_m} : DC \text{ short}$
 $\vec{I_D} : AC \text{ open}$



- 1) M₁ parameters vary with
- ambient temp.
 - time
 - device to device

i.e. random variations in device


e.g. if V_T changes, \rightarrow properties change \rightarrow changes in g_m , r_{th} , V_{DS} , V_{OV} etc.
 ⇒ Undesirable

2) Tolerance in R_A , R_B etc

On an IC :

(
R, C, MOSFET etc.)

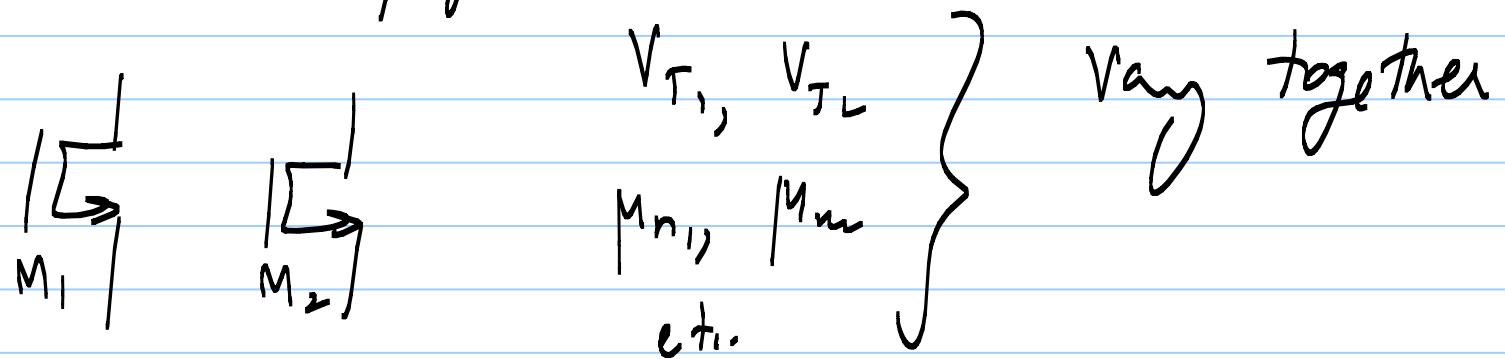- 1) Multiple copies of the same device nominally have same properties, (on the same IC)



- 2) Properties may vary across multiple ICs
3) Ratios of like components vary similarly

$$\frac{1}{R} \quad \frac{1}{2R}$$

$$\frac{R_B}{R_A + R_B}$$

— used to generate V_{AS} from V_{DD}

Innes still exist:

1) V_{AS} is constant ($\propto V_{DD}$), but V_T etc. can vary $\Rightarrow I_D$ varies \Rightarrow gain, swing limits vary.

\Rightarrow Make V_{AS} vary with V_T to get desired I_D

Use "negative feedback" to generate V_{AS}

* Desired Value (desired drain current = I_0)

* Measure actual value (I_D)


* Compare actual with desired ($I_D \leftrightarrow I_0$)

* Use error to move actual value towards
defined value (make $F_D \rightarrow 0$, using V_{us})

26/8/2020

Lecture 13

Negative feedback biasing

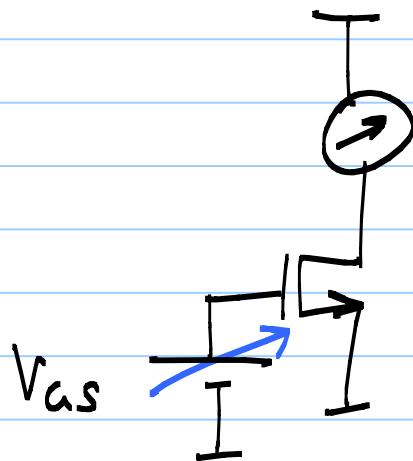

1) Apply V_{AS}


2) Measure I_D

3) If $I_D > I_o$, $\downarrow V_{AS}$

4) If $I_D < I_o$, $\uparrow V_{AS}$

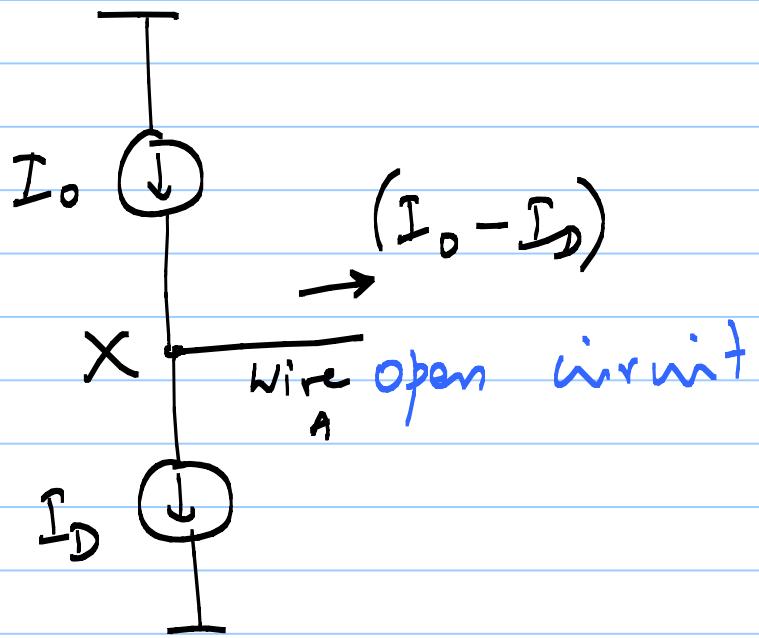5) If $I_D = I_o$, $V_{AS} = \text{same as before}$

$(I_o - I_D) \equiv \text{comparing } I_o \text{ with } I_D$



In a MOSFET:


V_{as} is cause

I_D is effect

If wire A is open
circuit:

- 1) If $I > I_D$: $V_x \uparrow$
(need to $\uparrow V_{as}$)
- 2) If $I < I_D$: $V_x \downarrow$
(need to $\downarrow V_{as}$)
- 3) If $I = I_D$: V_x stays constant

(need to keep V_{as}
at same value)

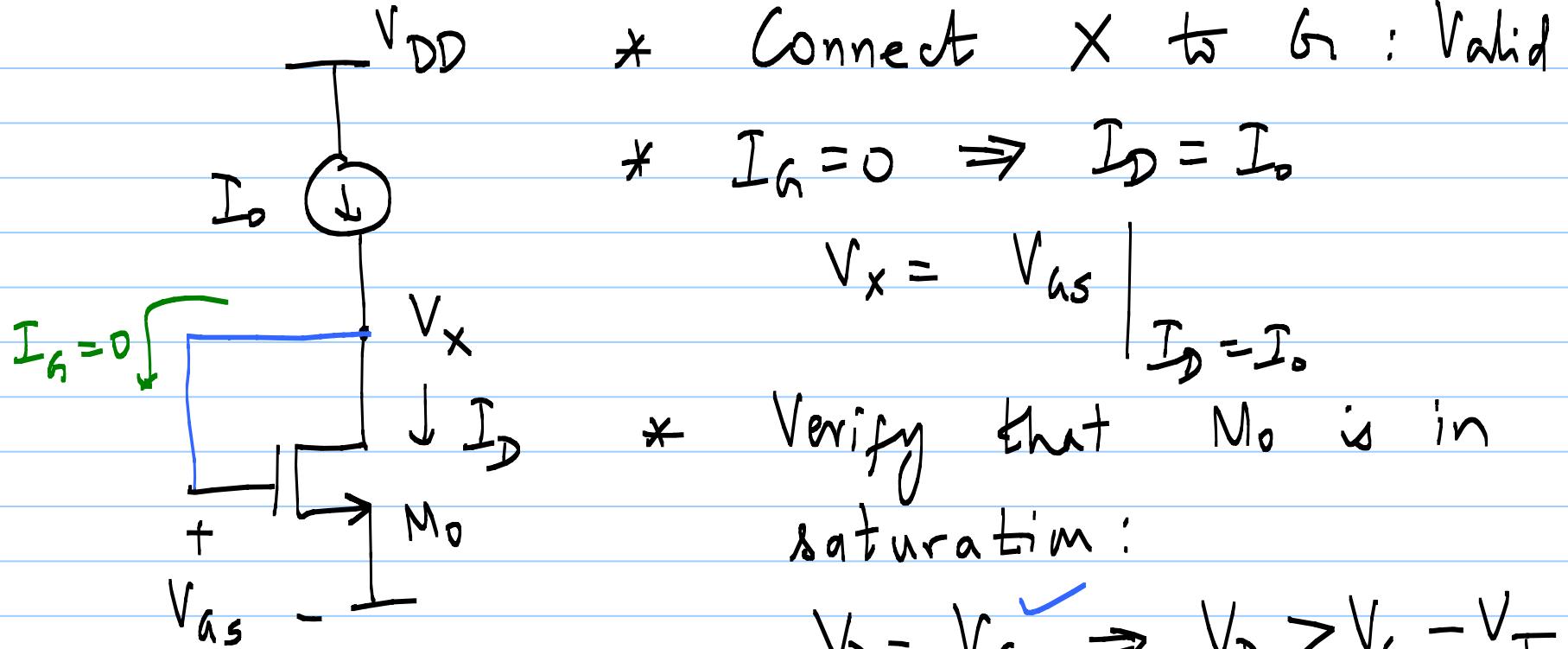

M_o is in sat.

$$V_x / (R_1 + R_2) = f_o$$



$$V_x = \left(\frac{R_1 + R_2}{R_2} \right) \cdot V_{as}$$

$$R_1 = \frac{V_a}{f_o}$$



$$R_2 = \frac{V_x}{f_o}$$

$$I_D = I_o - \left(\frac{V_x}{R_1 + R_2} \right)$$

CSA

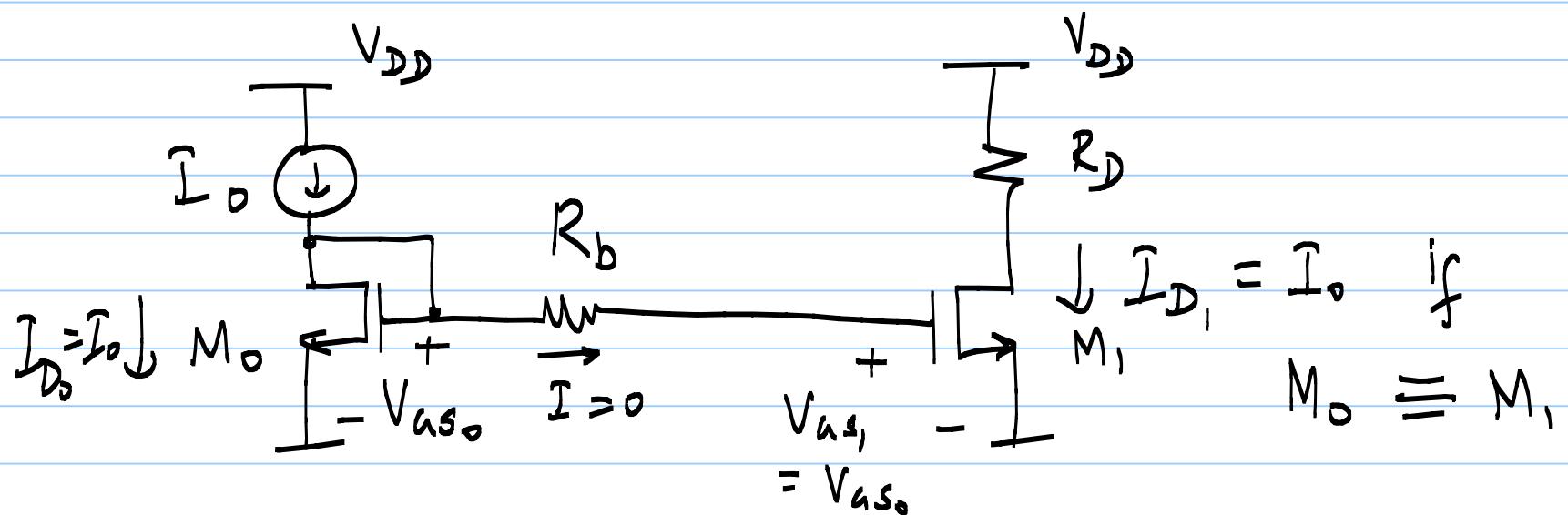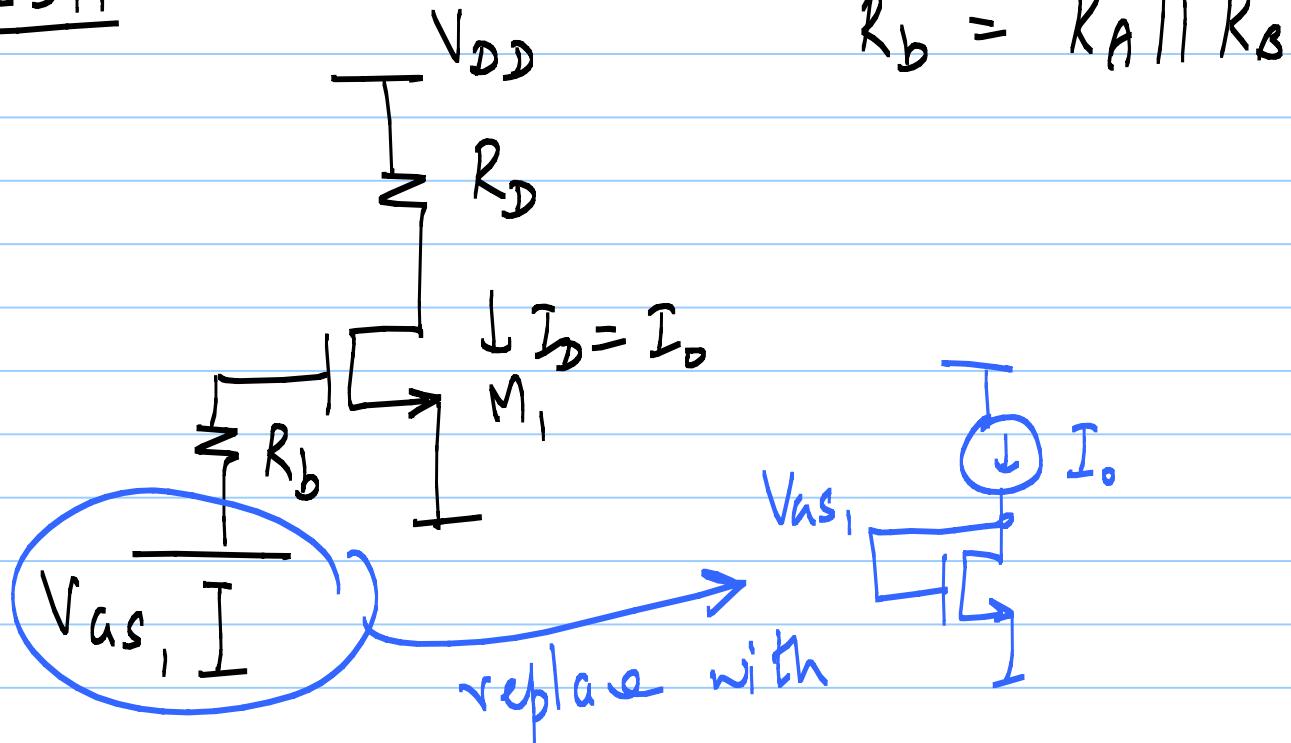

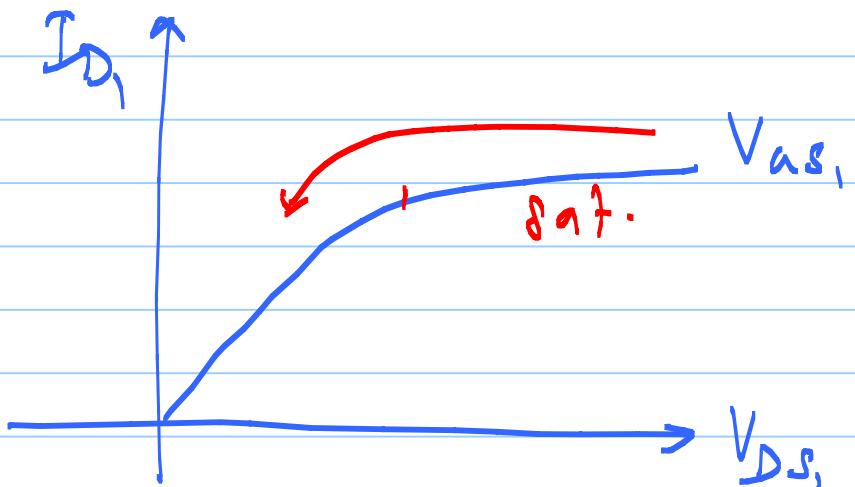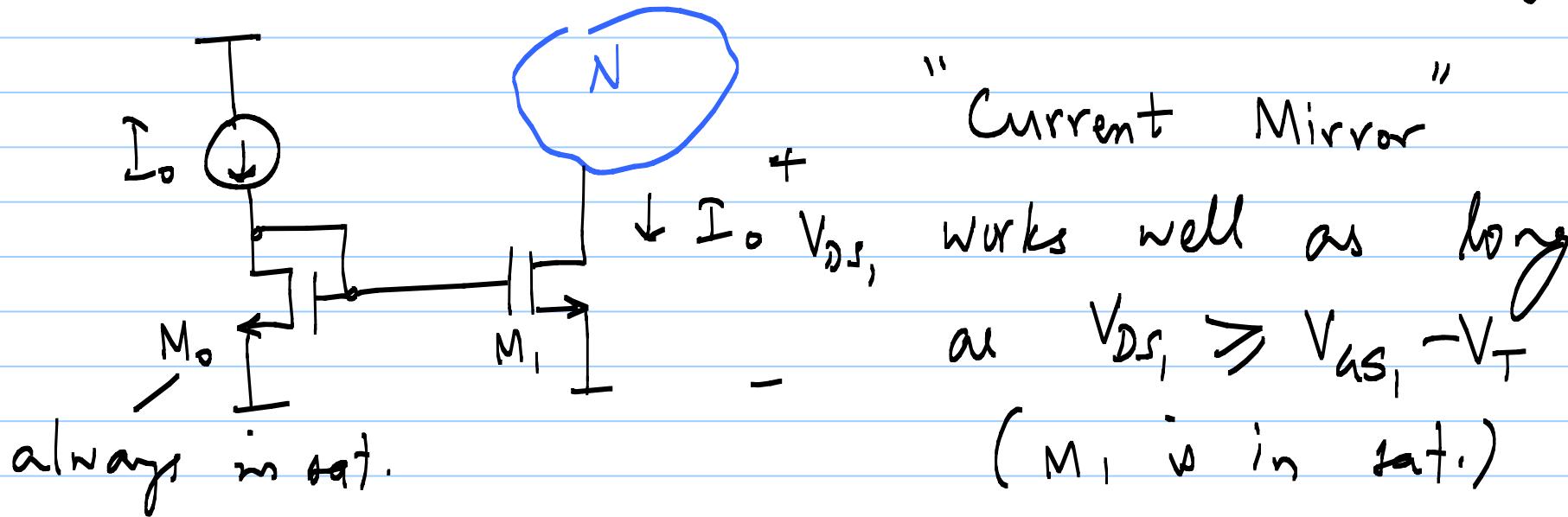$M_0 \equiv M_1$ means same $\mu_n, C_{ox}, V_T, \left(\frac{W}{L}\right)$
 { same W and L }



27/8/2020

Lecture 14


$$I_1 = I_o \text{ if } M_1 \text{ is in sat.}$$

$$V_{DS1} \geq V_{AS1} - V_T$$


* small deviations
due to CLM (r_{ds})

$$V_{DS1} \neq V_{DS2}$$

$$V_{DS1} \neq V_{AS1}$$

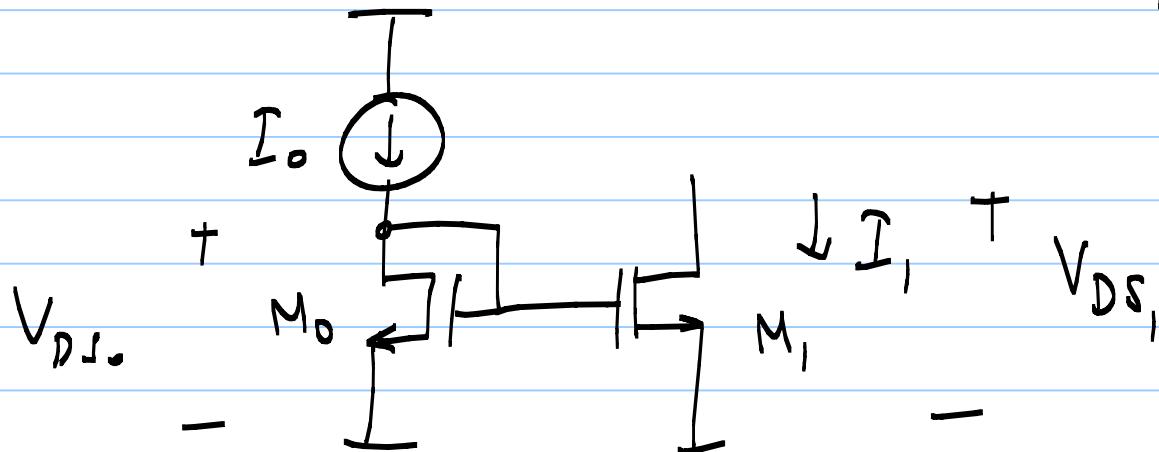

$$V_{AS1} = V_{AS2} = V_{DS}$$

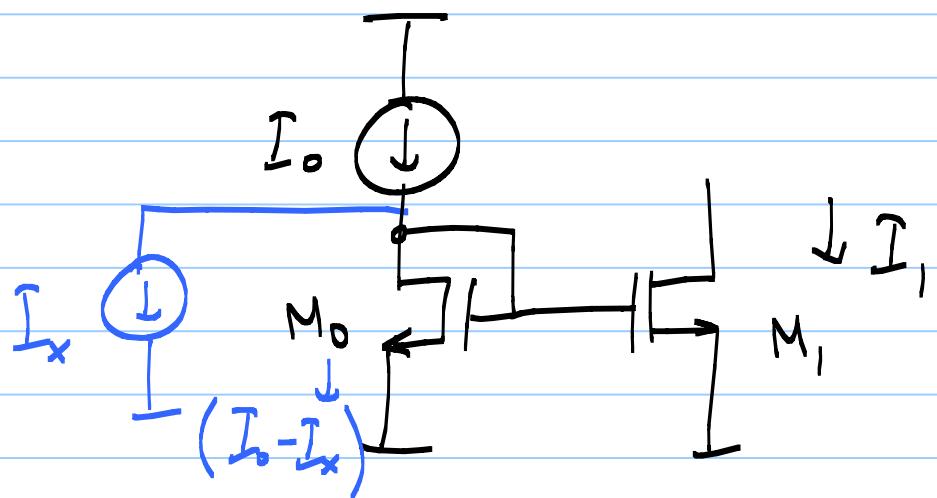

i) I want $I_1 = k I_o$

$$I_1 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) \left(V_{AS1} - V_T \right)^2$$


$$V_{AS_1} = V_{AS_0}$$

$$V_{AS_1} - V_T = V_{AS_0} - V_T$$

$$(V_{AS_1} - V_T)^2 = (V_{AS_0} - V_T)^2 = \frac{2I_0}{\mu_n C_{ox} \left(\frac{W}{L}\right)_0}$$

$$I_1 = I_0 \cdot \frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_0}$$

k

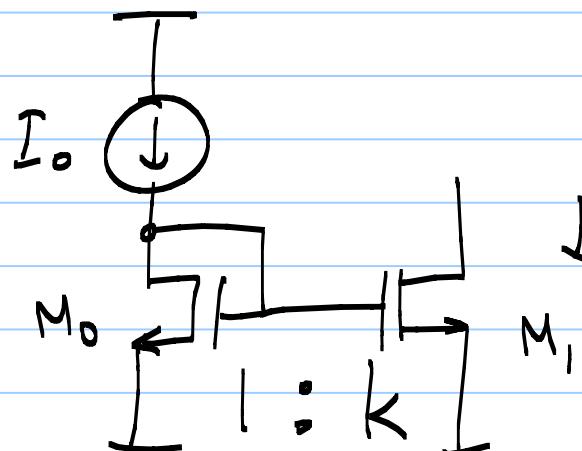

$$\downarrow I_1 = k I_0$$


Ensure:

$$L_1 = L_0$$

$$W_1 = k W_0$$


λ - models $\Delta L/L$ (CLM)

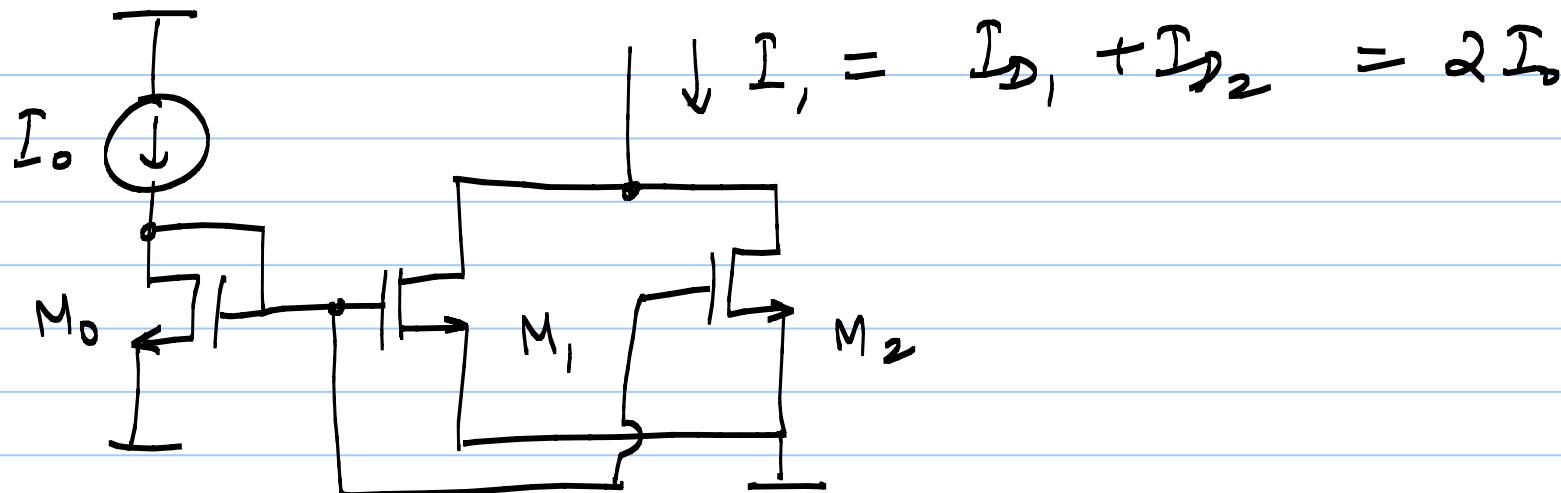larger $L \rightarrow$ smaller $\Delta L/L \rightarrow$ smaller $\lambda \rightarrow$ larger r_d



$$M_0 \equiv M_1 \equiv M_2$$

2)

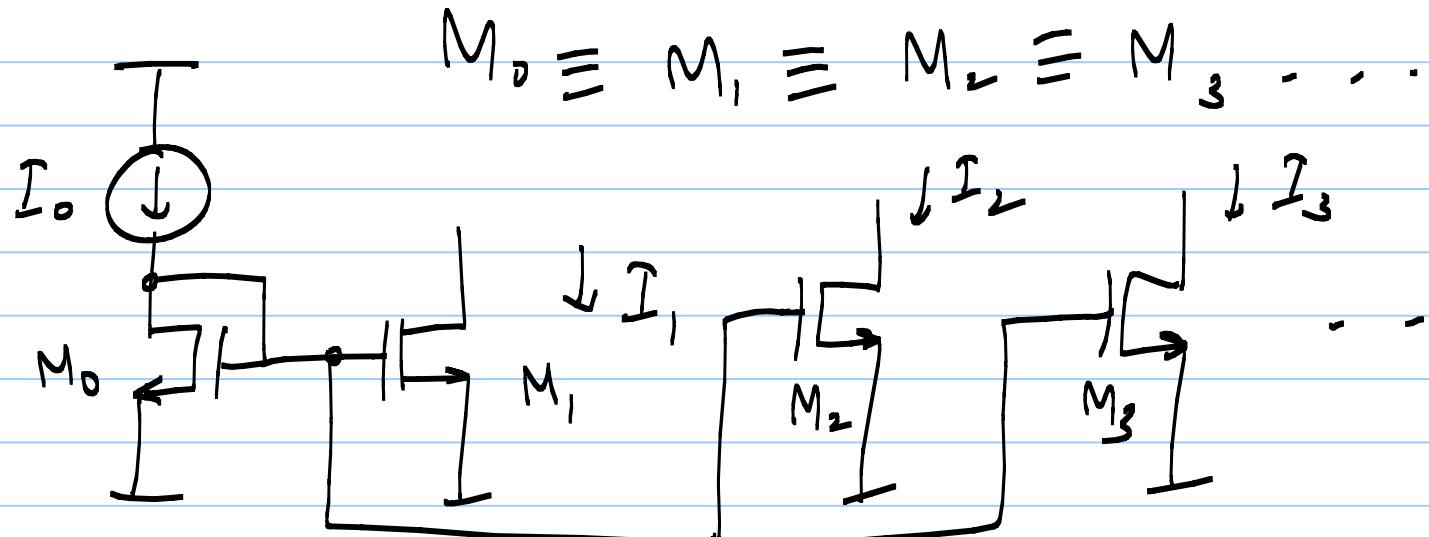


all V_{DS} 's



$\geq V_{AS} - V_S$

[all devices
in sat.]


Make as many copies as you want

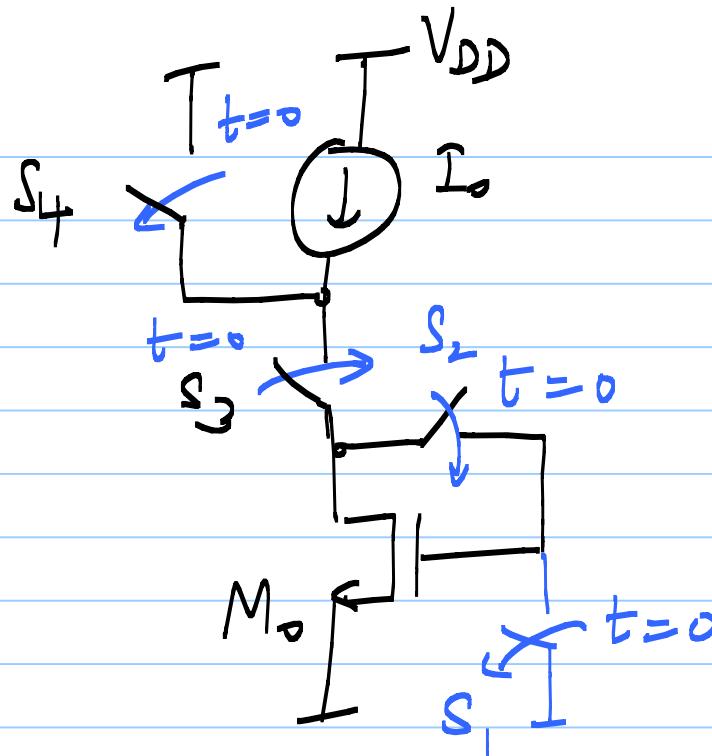

$t < 0 :$

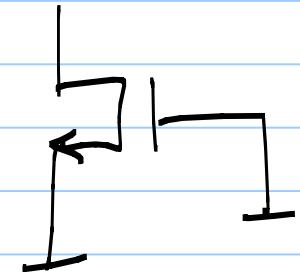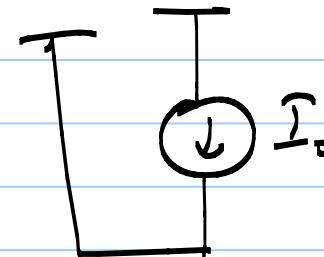

$t = 0^+$

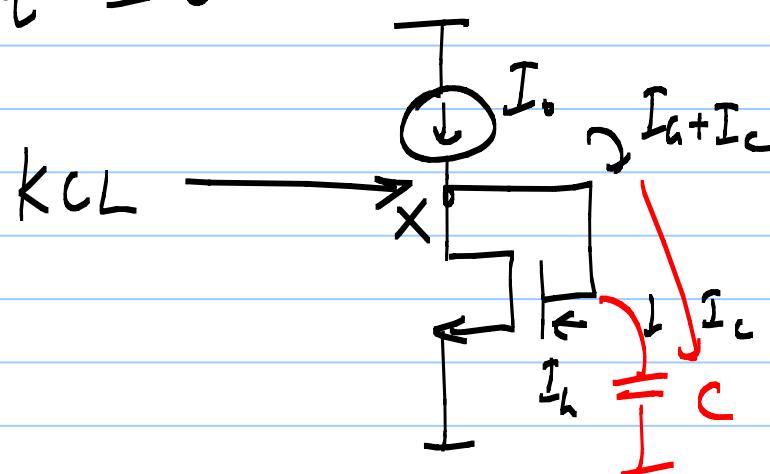


@ $t = 0^-$ $V_{us} = 0$

@ $t = 0^+$: $I_h = 0, I_D = 0$

$\rightarrow V_x \uparrow \rightarrow V_{us} \uparrow \rightarrow I_D \uparrow$

$\rightarrow I_D = I_0$

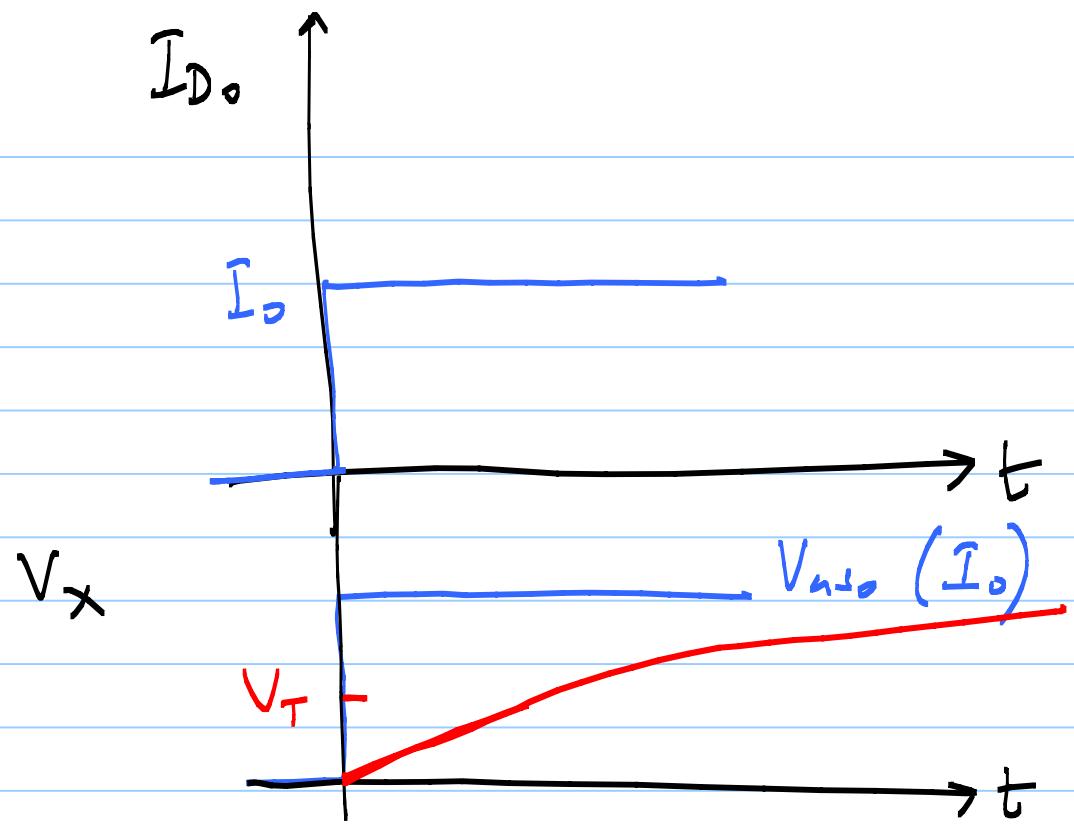



$$I_0 = I_C + I_{D0} + \cancel{I_h^D}$$

↑


$\Rightarrow 0 @ t=0^+$

$$I_D = 0 \quad t \parallel \quad V_{hs} = V_x = V_T \Rightarrow I_C = I_0$$



$$I = C \frac{dV}{dt}$$

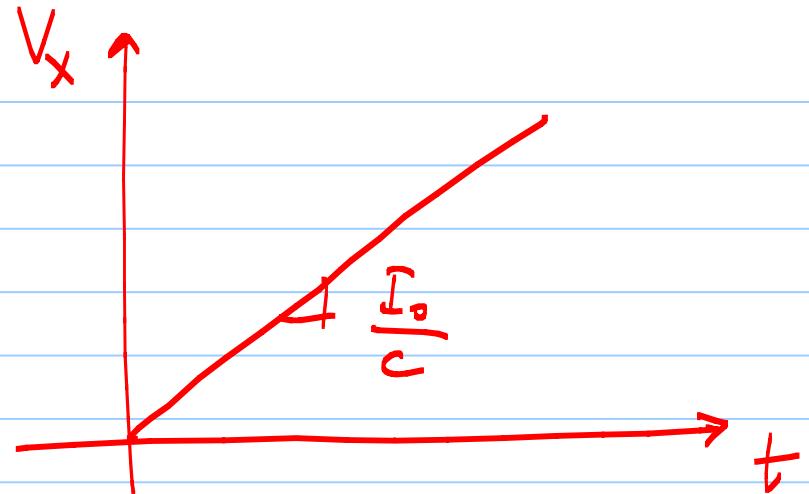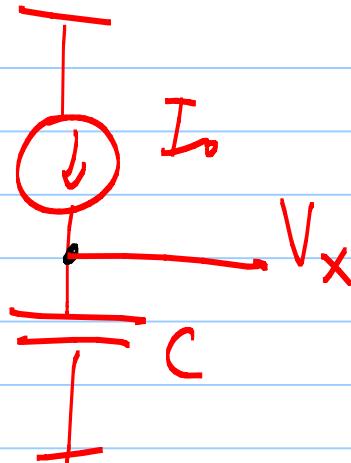

CSA

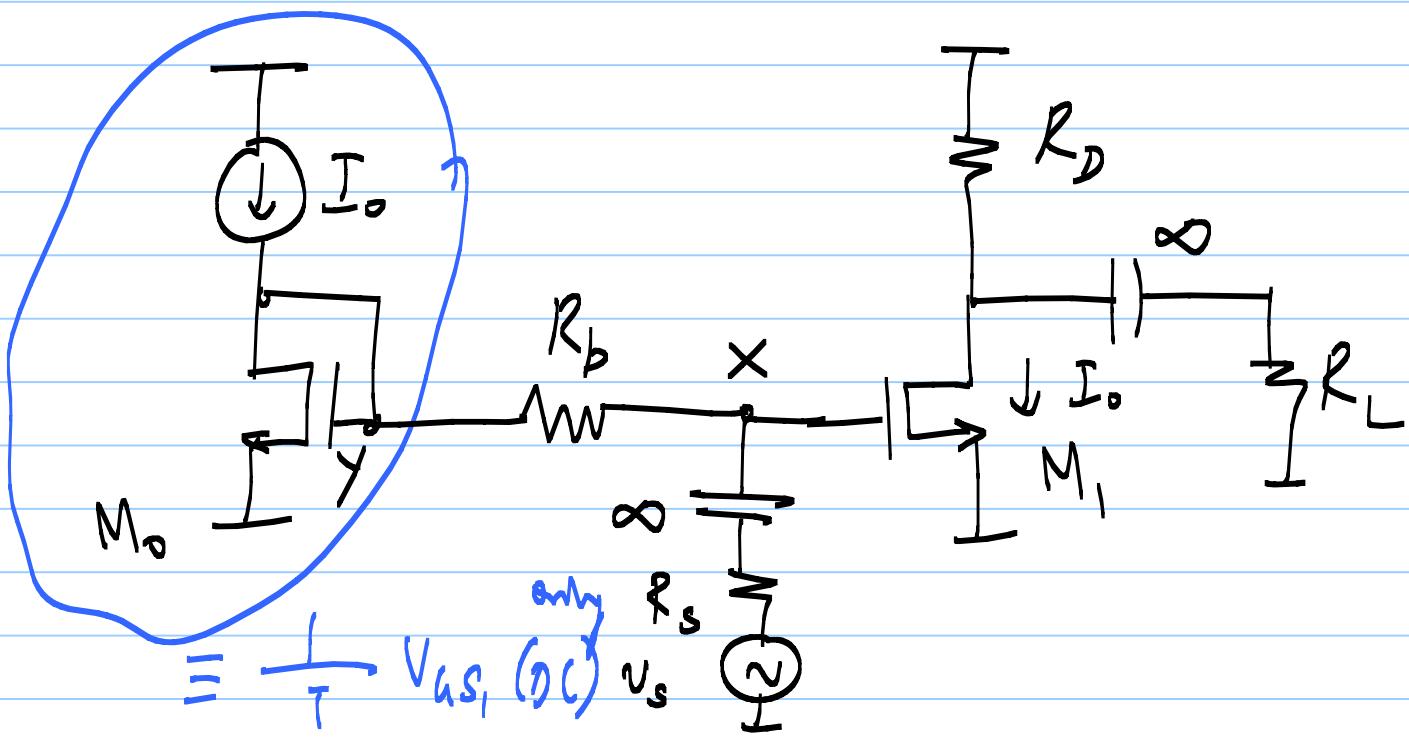

$$M_0 = M_1$$

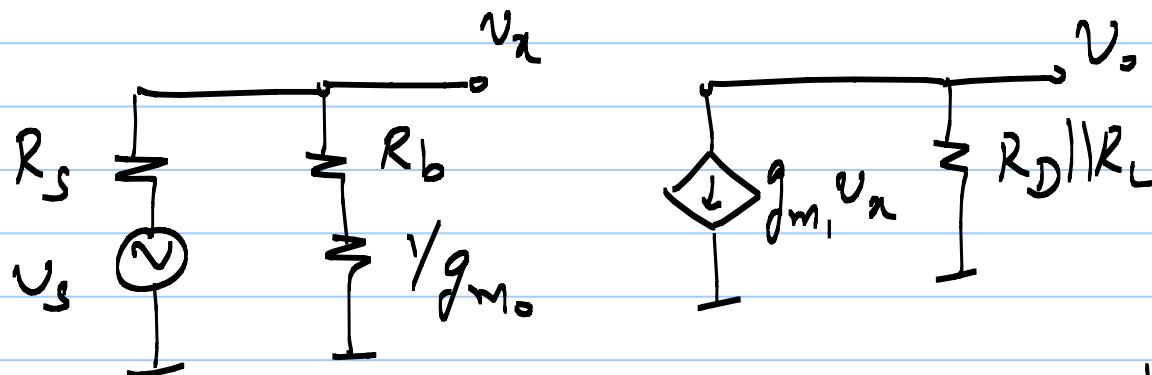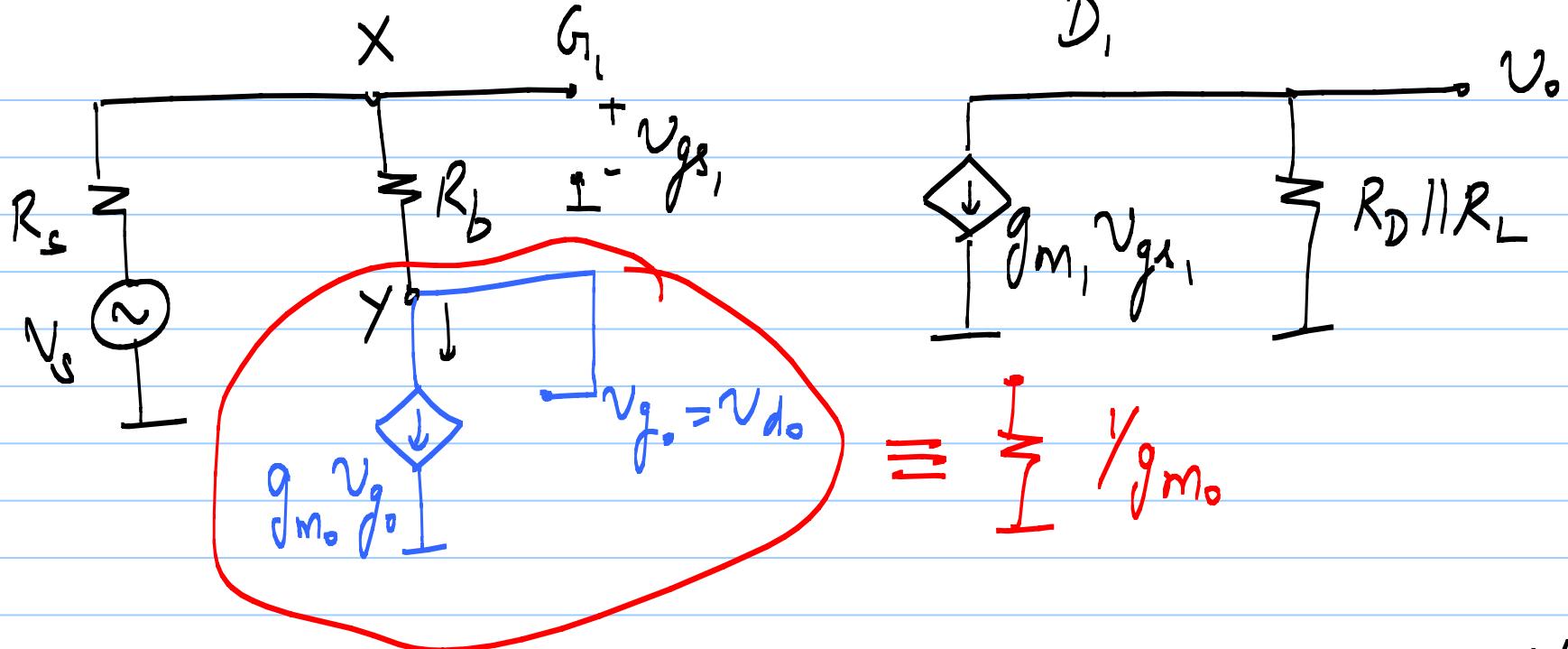


$$\frac{v_x}{v_s} = \frac{R_b + \frac{1}{g_m}}{R_s + R_b + \frac{1}{g_m}}$$

$g_m = g_m = \text{large}$

choose $R_b \gg \frac{1}{g_m}, R_s$

$$\Rightarrow v_x \approx v_s$$

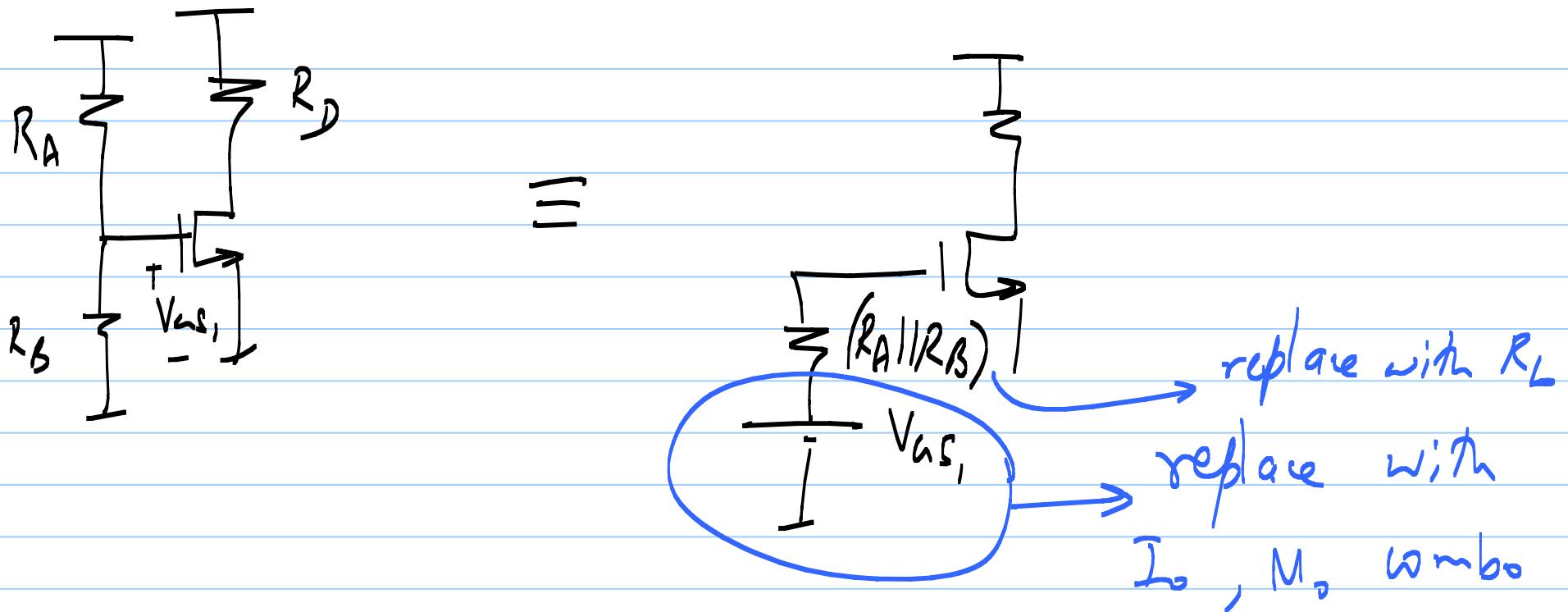

$$V_o = -g_m \cdot V_s \cdot (R_D || R_L)$$

$$\approx -g_m \cdot (R_D || R_L) \cdot V_s$$


$$\frac{V_o}{V_s} \approx -g_m \cdot (R_D || R_L)$$

same as before

I_D , V_{AS1} , V_{DS} - same as before \Rightarrow swing limits are the same too.

28/8/20


Lecture 15

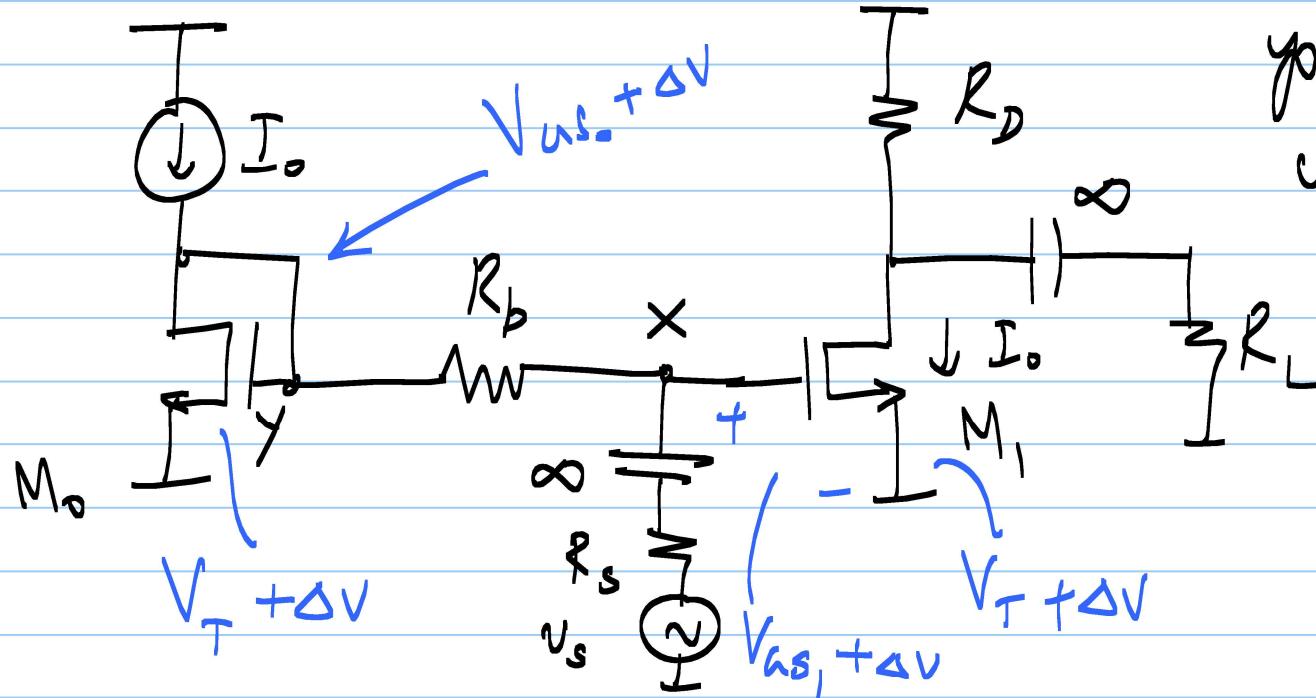


* If V_{T_1} changes by ΔV , you expect V_{T_0} to also change by ΔV

Can you do this with
a single MOSFET?



DC bias

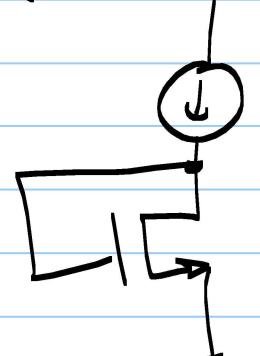


M_1

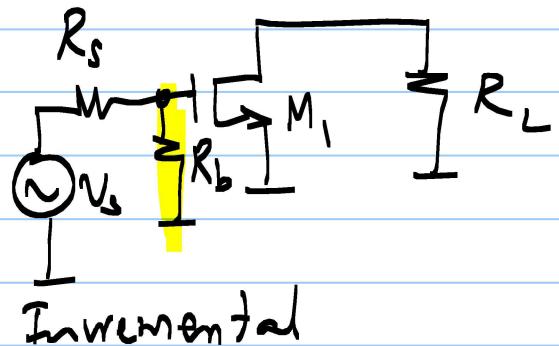


Incremental

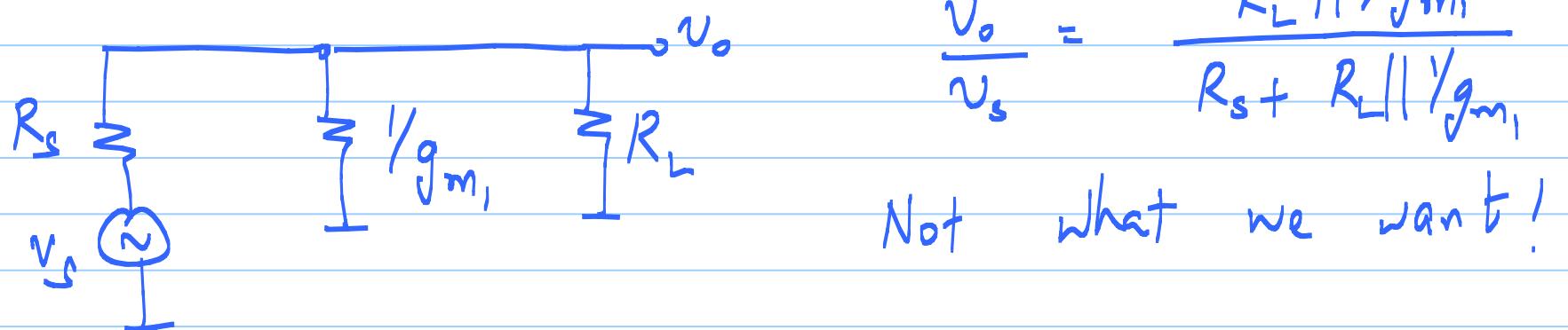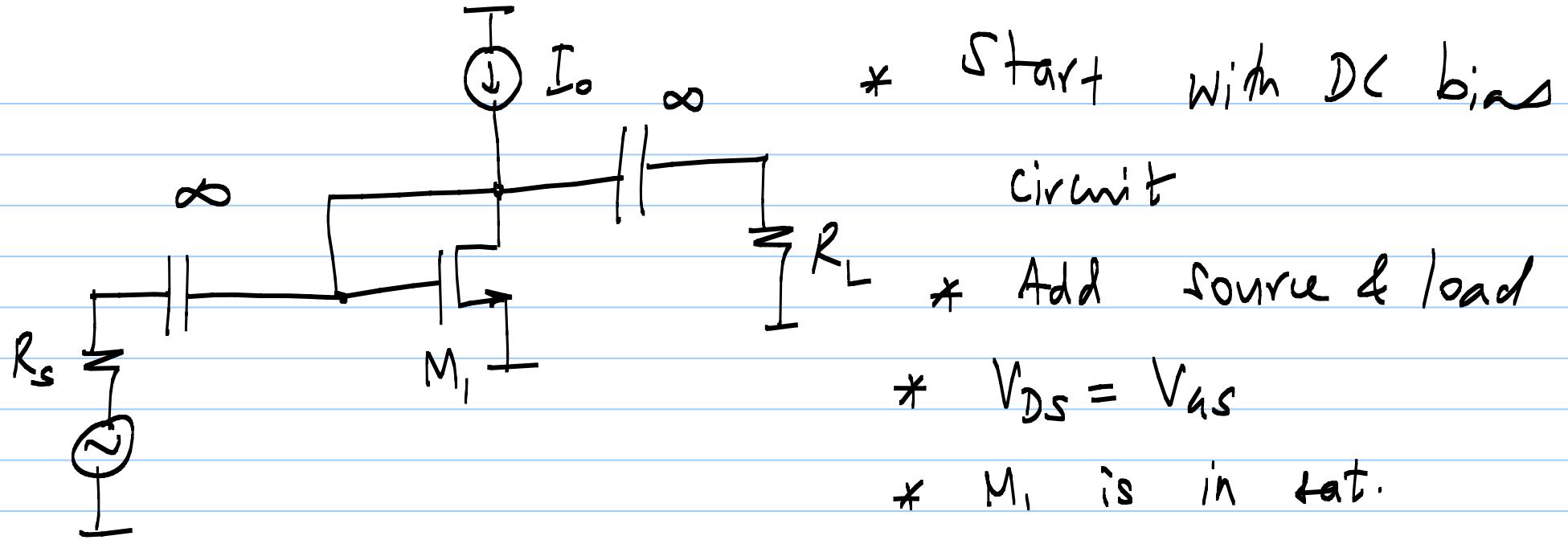

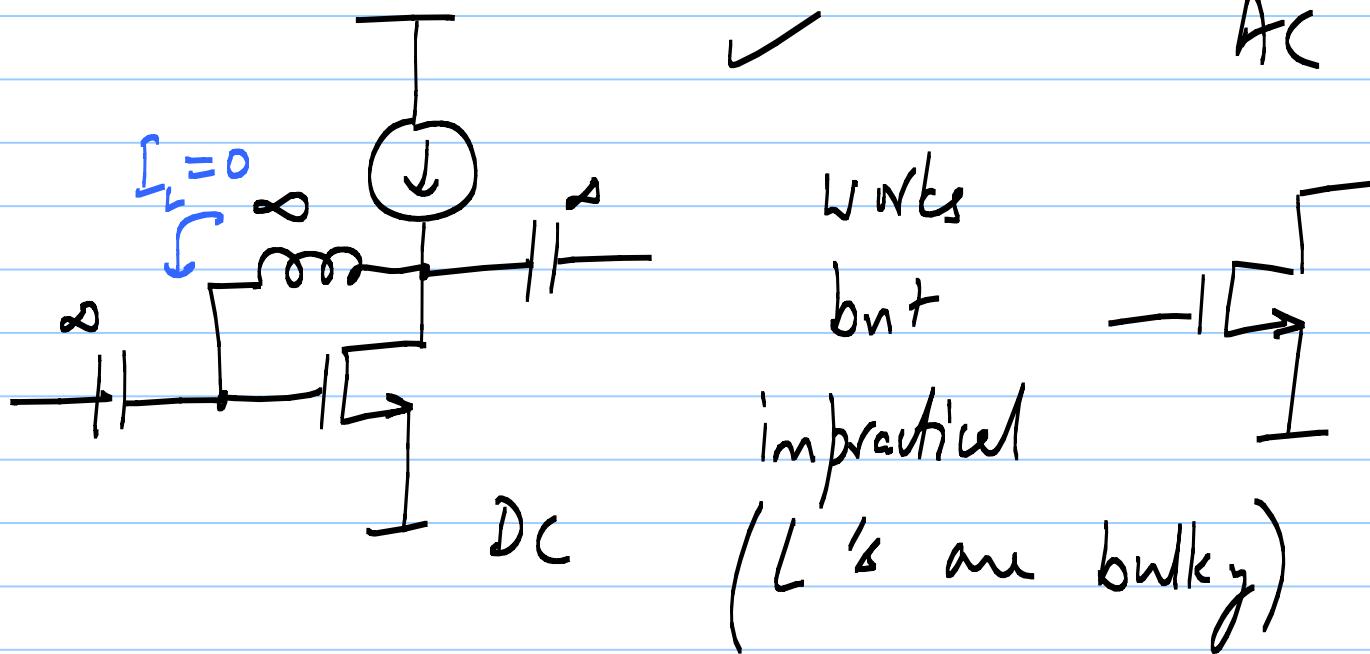Options : 1) Add ∞ inductor between G & D



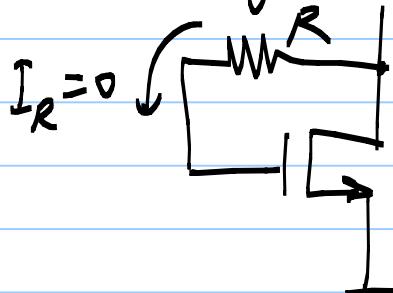2) V_{KE} large resistor (because $I_L = 0$)




$$V_{DS_1} = V_{AS_1}, \text{ feedback maintained}$$

$$V_{DS_1} = V_{GS_1} \Big|_{I_0}$$

$$I_D = I_0$$


DC is okay

$$V_s$$

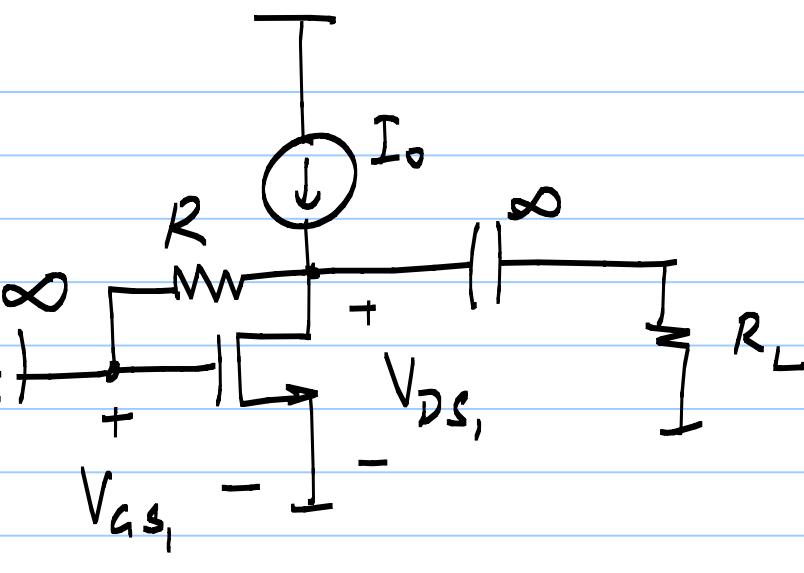

HW1 : Analyse
with R_s

SS eq.:

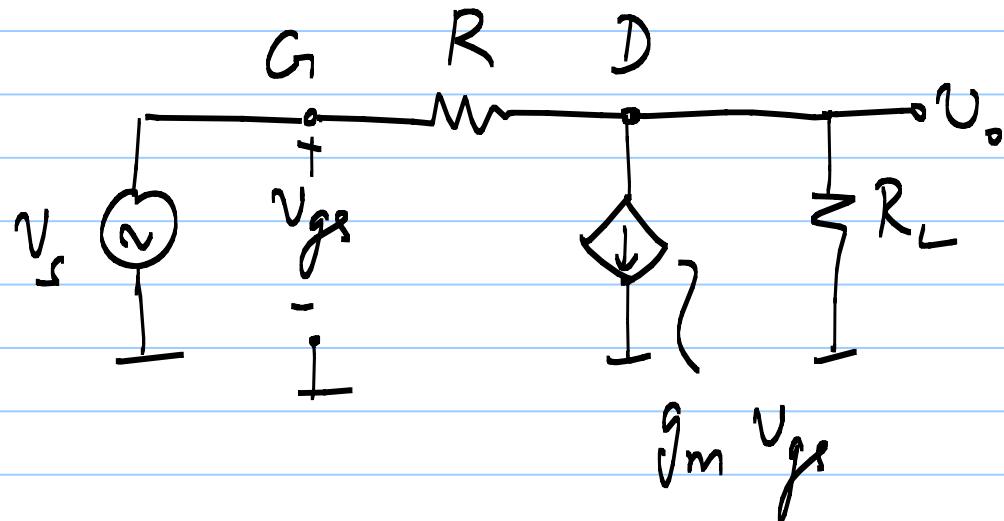

$$V_{DS} = V_s$$

KCL @ drain node :

$$\frac{V_s - V_o}{R} = g_m V_s + \frac{V_o}{R_L}$$

$$\frac{1}{R} = G, \quad \frac{1}{R_L} = G_L$$

$$V_s [G - g_m] = V_o [G_L + G]$$

$$\frac{V_o}{V_s} = \frac{G - g_m}{G + G_L} = \frac{-g_m}{G_L} \left[\frac{1 - G/g_m}{1 + G/G_L} \right]$$

We want


- * $g_m \gg G_L$ (large gain)
 - * $G \ll G_L \Rightarrow G \ll g_m$
- ≈ 1 (desired)

By "large R ", we mean $R \gg R_L$

$$\text{gain} \approx -g_m R_L$$

Swing limits :

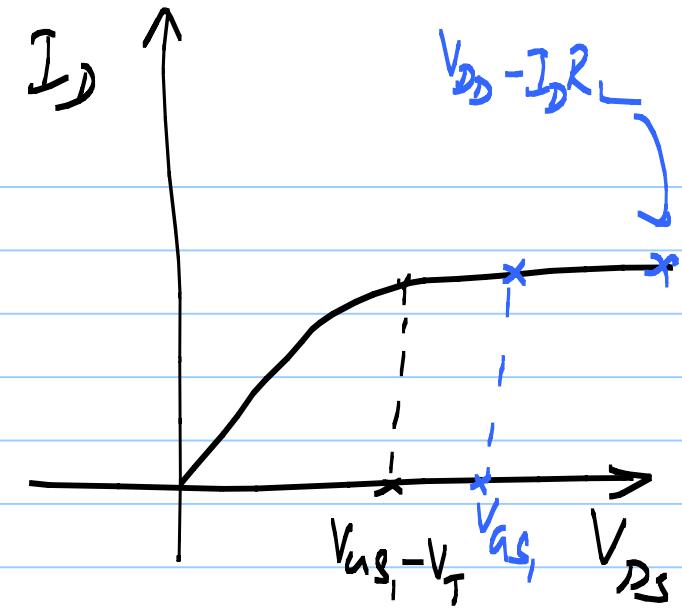- * Triode limit is lower because $V_{DS} = V_{AS}$
- * Cut-off limit is same as before ; I_D = same as before




1/9/20

Lecture 1b

We want to bias the MOSFET with stable
Quiescent current :

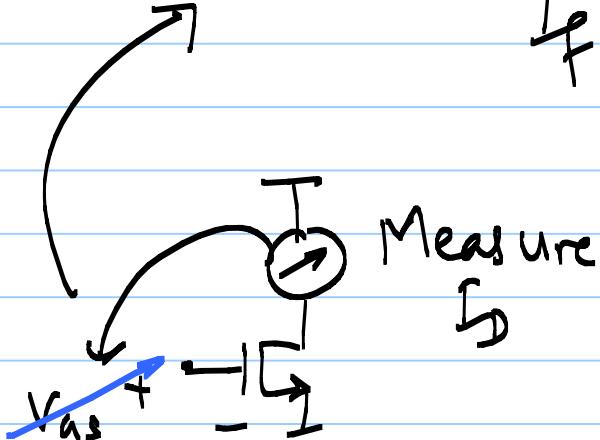- 1) Measure I_D (I_S)
- 2) Compare I_D (I_S) with I_0
- 3) If $I_D > I_0 \Rightarrow$ reduce V_{GS} ($\downarrow V_G$ or $\uparrow V_S$)
If $I_D < I_0 \Rightarrow$ increase V_{GS} ($\uparrow V_G$ or $\downarrow V_S$)



For MOSFET : $I_G = 0$

$\Rightarrow I_S = I_D$ always (1)
→ Measure I_S or I_D


$$\text{We control } V_{AS} = V_A - V_S \quad (2)$$

keep s fixed
Vary h


keep h fixed
Vary s

* 4 ways of negative feedback bias stabilization

1)

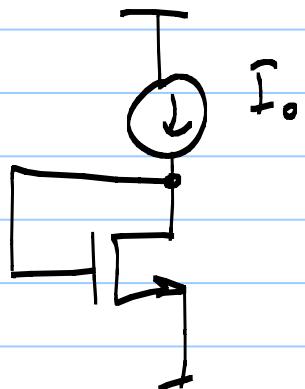

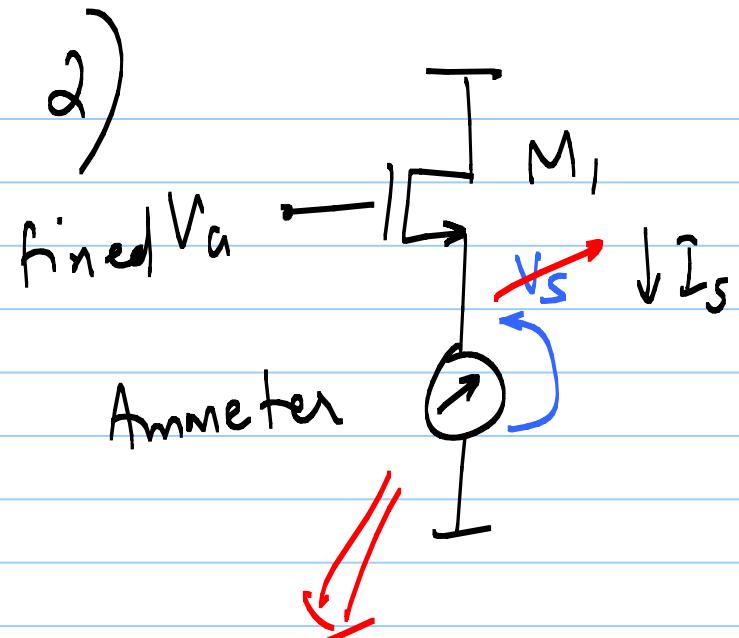Measure I_s , f.b. to V_h ,
keep V_s fixed



Measure I_S , f.b to V_S ,
keep V_A fixed

step 0: M_1 in sat.

$$\Rightarrow V_{DD} > V_A - V_T$$


step 1: Measure I_S


step 2: If $I_S > I_0 \Rightarrow$ need to $\downarrow V_{AS}$

$$\Rightarrow \uparrow V_S$$

If $I_S < I_0 \Rightarrow$ need to $\uparrow V_{AS}$

$$\Rightarrow \downarrow V_S$$

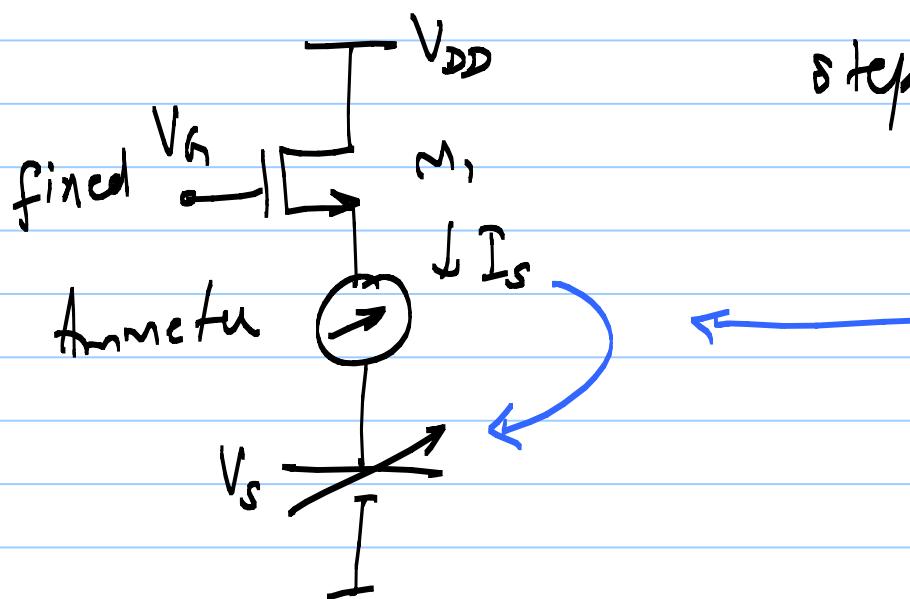

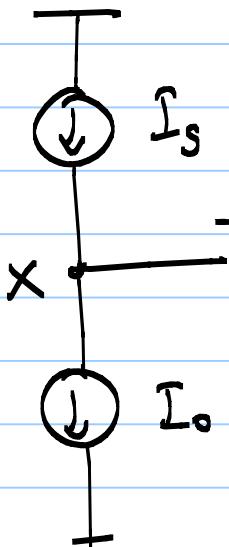

magnitude & sign of $(I_s - I_o)$
tells you what to do

If $I_c > I_o \Rightarrow V_x \uparrow$ [need to $\uparrow V_s$]

$I_s < I_o \Rightarrow V_x \downarrow$ [need to $\downarrow V_s$]

$I_s = I_o \Rightarrow V_x$ same [V_s same]

Due to negative f.b. action:

$$I_s = I_o = I_D$$

$$V_s = ?$$


M_1 is in sat. $\Rightarrow I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2$

$$V_G - V_s = V_{GS} = V_T + \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L} \right)}} = V_{OV}$$

or V_{DSAT} .


$$V_s = V_a - V_{GS}$$

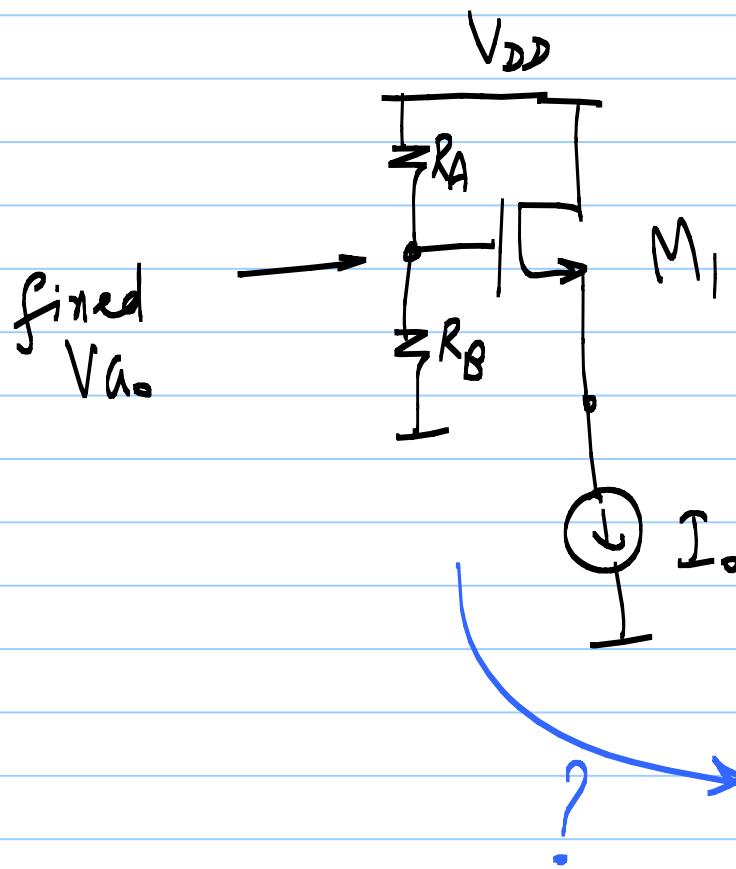
$$V_s = V_{A_0} - \sqrt{\frac{2 I_o}{\mu_n C_{ox} \left(\frac{W}{L} \right)}} - V_T$$



$$V_{A_0} = \frac{R_B}{R_A + R_B} \cdot V_{DD}$$

Small-signal:

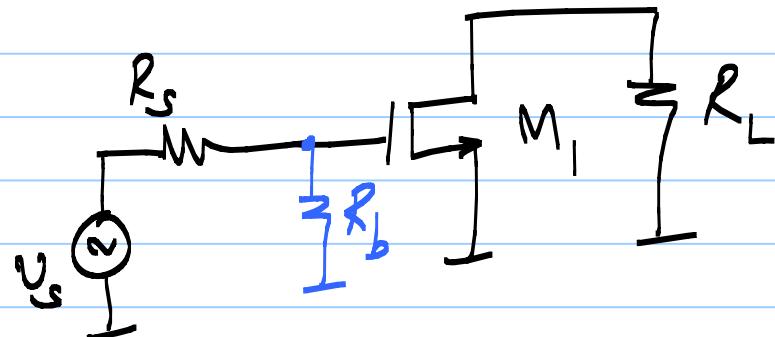

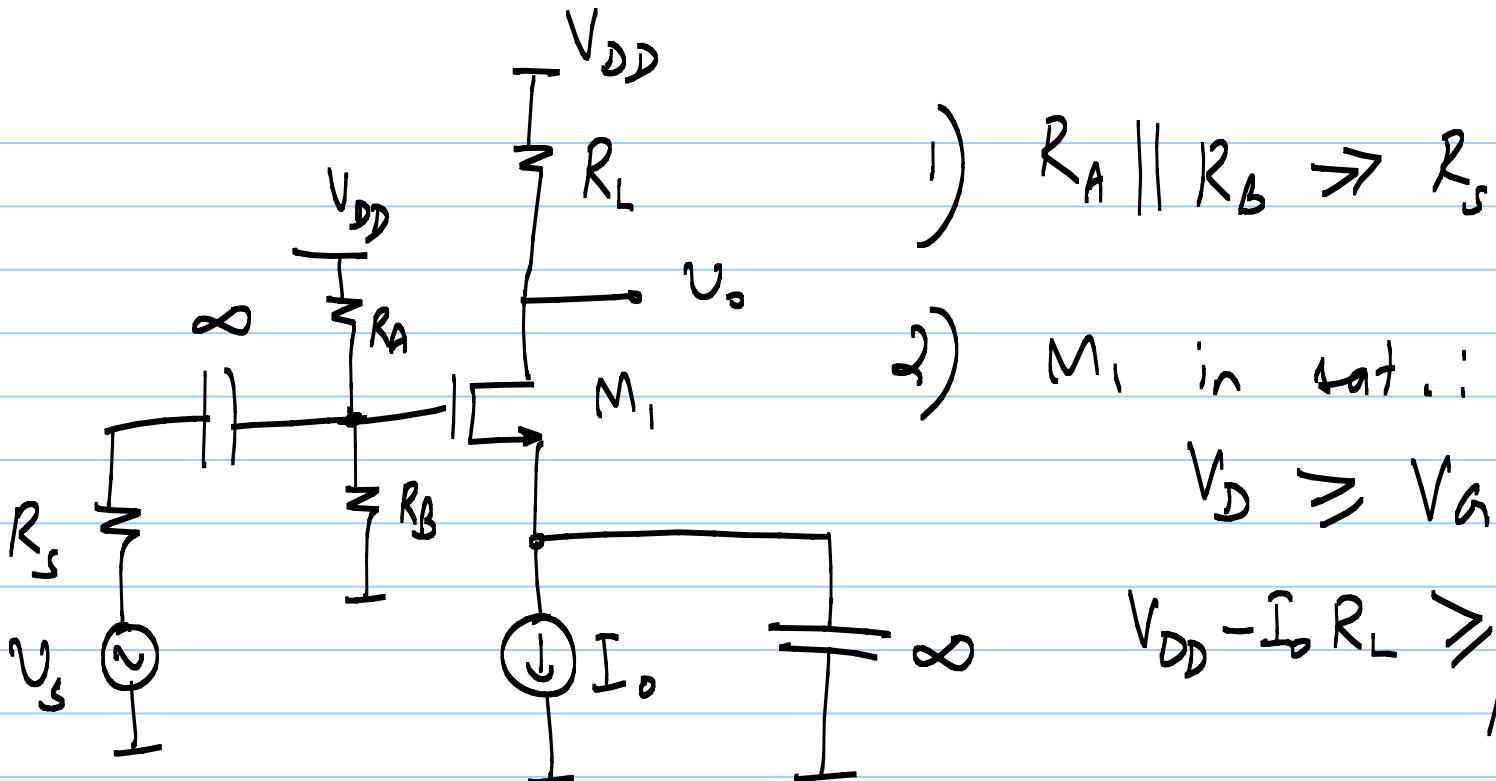

$$1) R_A \parallel R_B \gg R_s$$

2) M_1 in sat.:

$$V_D \geq V_G - V_T$$

$$V_{DD} - I_o R_L \geq \frac{R_B}{R_A + R_B} V_{DD} - V_T$$

Swing limits

1) Cut off limit: $I_o + g_m V_A \text{ limit} = 0$

$$V_{A,1} = \frac{I_o}{g_m}$$


2) Triode limit $V_D(t) = V_G(t) - V_T$

$$V_{DD} - I_o R_L - g_m R_L V_A \sin \omega t = \frac{V_{DD} R_B}{R_A + R_B} + V_A \sin \omega t - V_T$$


$$V_A_2 = \left[V_T + \frac{V_{DD} \cdot R_A}{R_A + R_B} - I_o R_L \right] \frac{1}{(1 + g_m R_L)}$$

2/9/20

Lecture 17

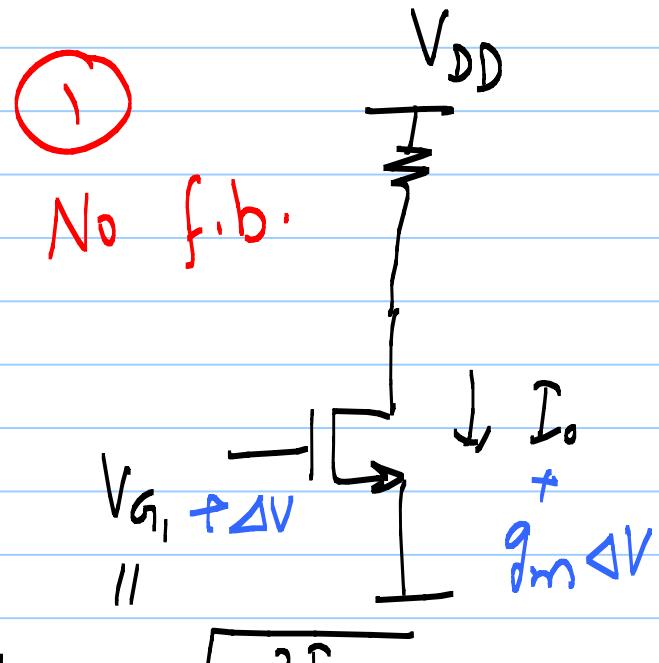

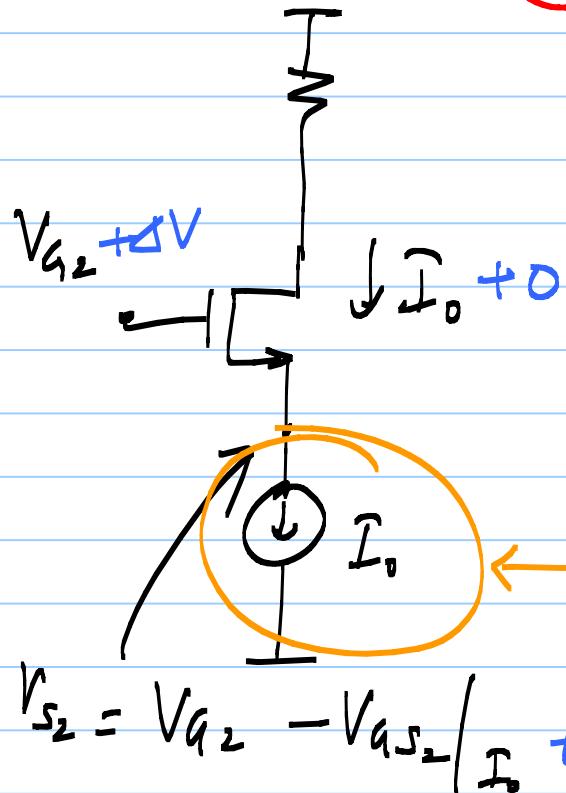
$$V_T + \sqrt{\frac{2I_0}{\mu_n C_x \left(\frac{W}{L}\right)}}$$



$$V_{S2} = V_{G2} - V_{GS2} \Big|_{I_0 + \Delta I_0}$$

open circuit for incremental signals

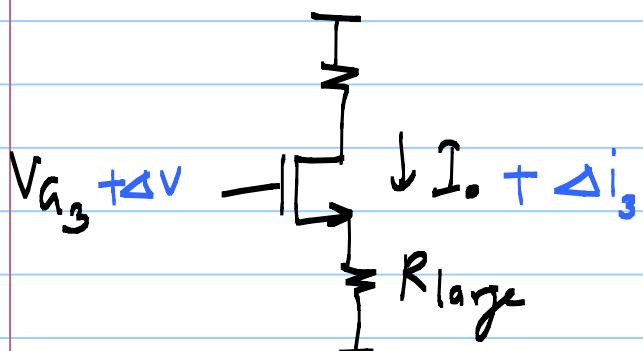


DC point:

$$V_{S3} = I_0 \cdot R_{large}$$

$$V_{G3} = V_{S3} + V_{GS} \Big|_{I_0}$$

$$\Delta i_3 = ?$$

KVL₁

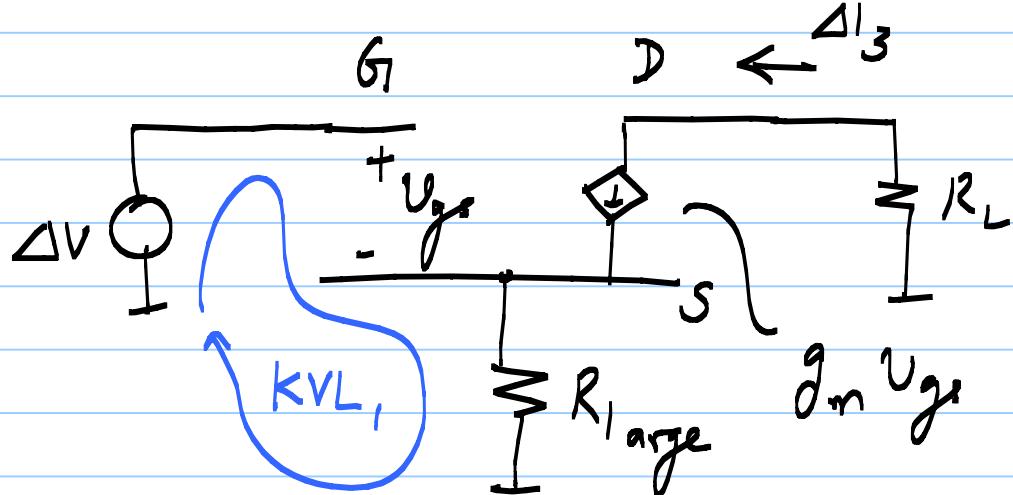

$$\Delta V = V_{gs} + \Delta i_3 \cdot R_{large}$$


$$\Delta i_3 = g_m V_{gs}$$

$$\Delta V = \frac{\Delta i_3}{g_m} + \Delta i_3 R_{large}$$


$$\boxed{\Delta i_3 = \frac{g_m}{1 + g_m R_{large}} \cdot \Delta V}$$

f.b. strength is
a function of R_{large}


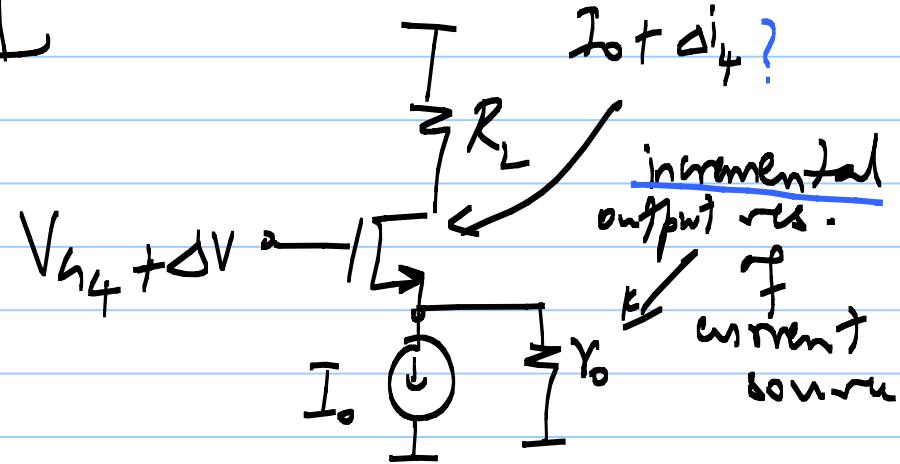
$$\Delta i_4 = \frac{g_m}{1 + g_m r_o} \cdot \Delta V$$



$$\boxed{r_{out} = r_{ds}}$$

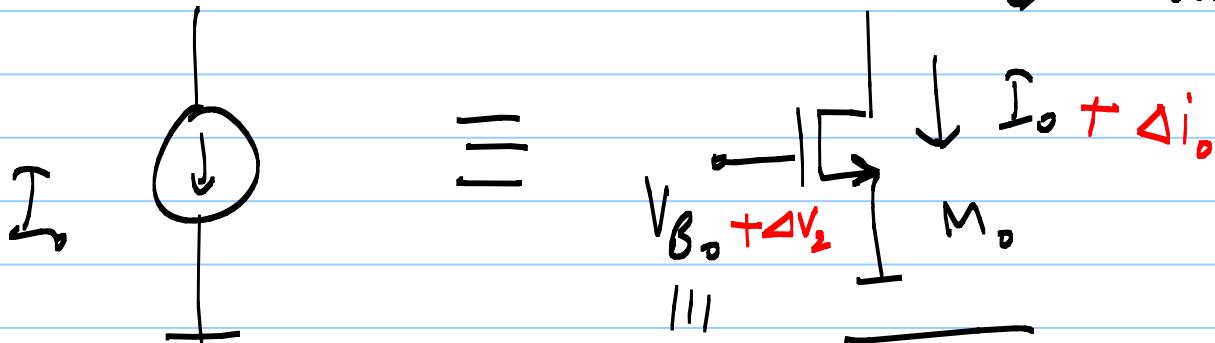
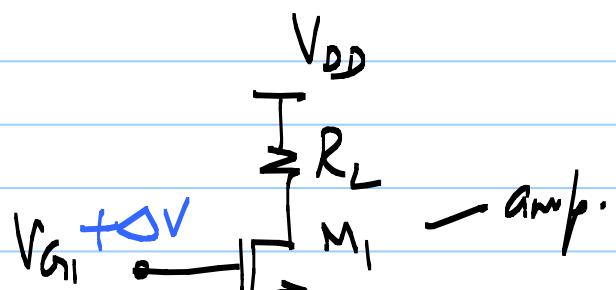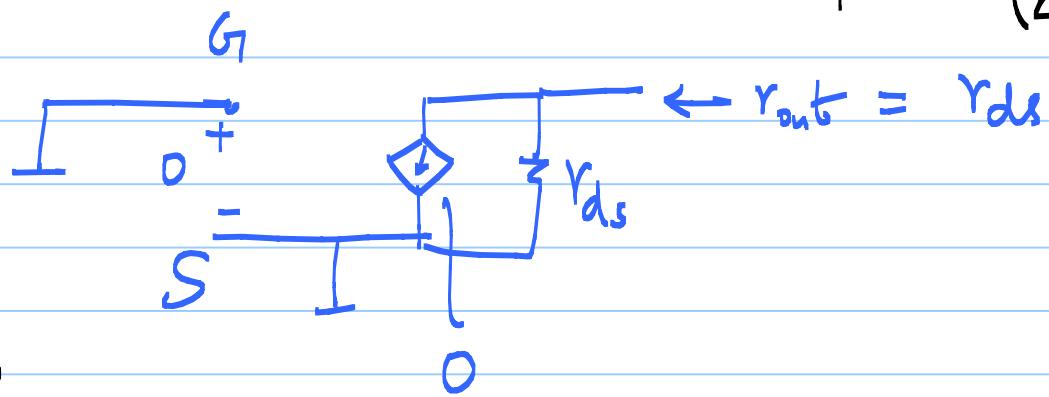
$$V_T + \sqrt{\frac{2I_0}{\mu_n C_{ox} \left(\frac{W}{L}\right)}}$$



$V_{B_0} + \Delta V_2$

M_0


I_0

C.S.

need f.b. to generate V_{B_0}

Hw 2

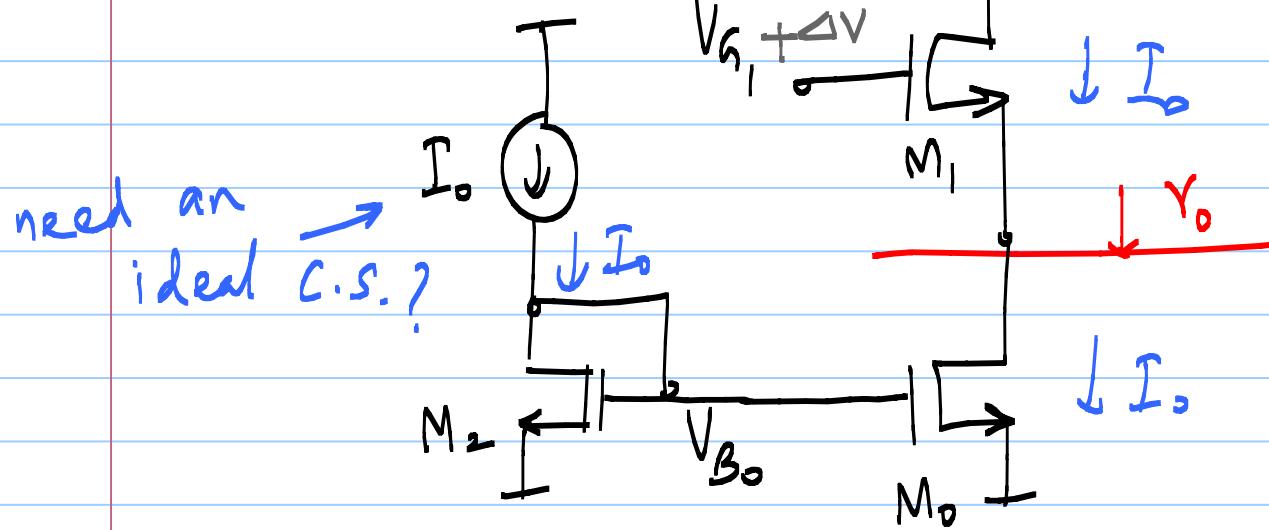draw incremental
eq. circuit and
Verify $r_o = r_{ds_0}$



* On any IC : one reference V_{ref} & I_{ref}


generated using a "Bandgap" circuit
reference

e.g. $V_{ref} = f(\delta_1 \text{ bandgap voltage})$

* often need | single ^{off-chip} Resistor \rightarrow low tolerance
low tempco

3/9/20

Lecture 18

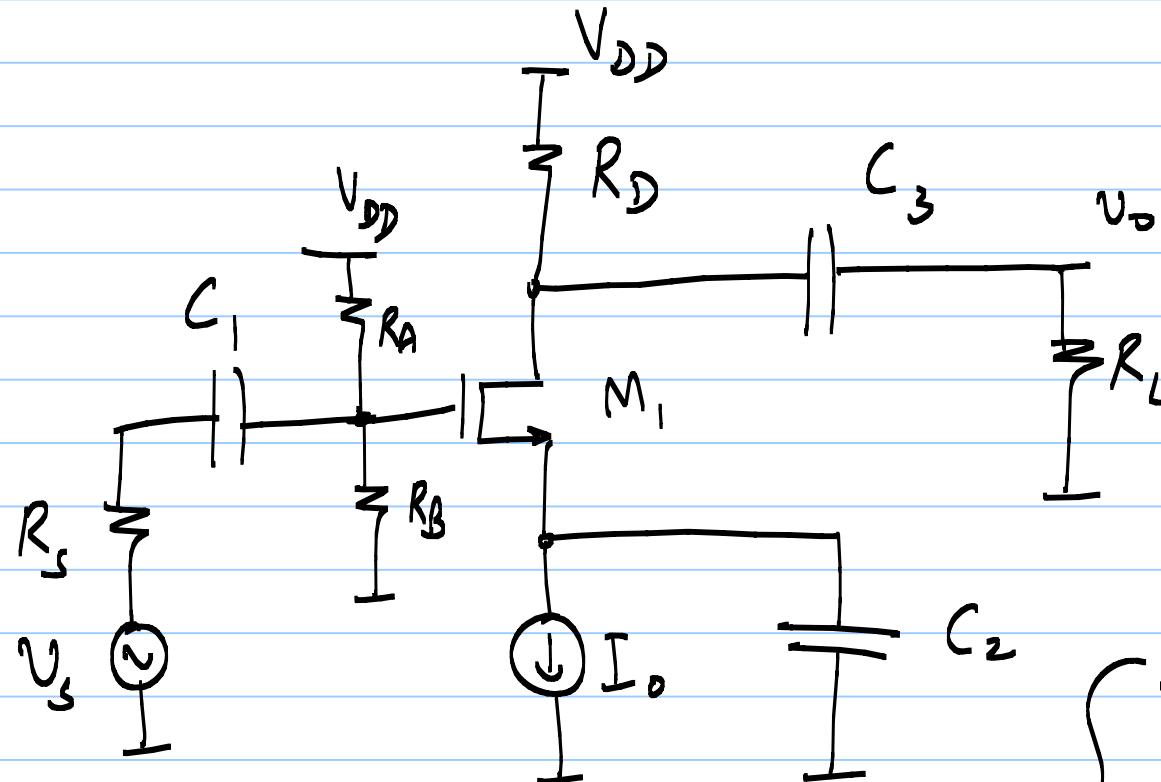

So far : $C_1, C_2, C_3 = \infty$

1) Choose C_i based

on ac resistance

① freq. f operation


⇒ small ac resistance

2) Eg. @ input, you have

HPF \rightarrow plot Bode

curves & choose based
on freq. response

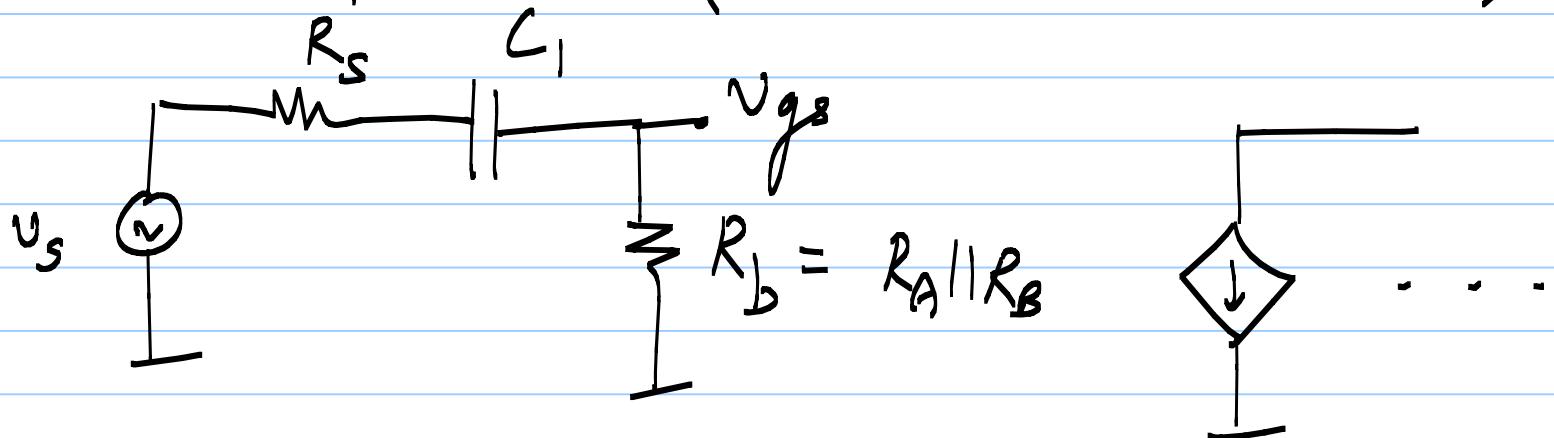SS eqn. ckt. @ input : (assume $C_2 = \infty$, $C_3 = \infty$)



want $|v_{gs}| = |v_s|$

$$|v_o| = g_m(R_D \parallel R_L) \cdot |v_s| \quad (R_b \gg R_s)$$

$$v_{gs} = \frac{R_b \cdot v_s}{R_s + R_b + \frac{1}{j\omega C_1}} = \frac{j\omega C_1 R_b \cdot v_s}{1 + j\omega C_1 (R_s + R_b)}$$


plot $\left| \frac{v_{gs}}{v_s} \right|$

$$f_{NR} C_1 : \left| \frac{2g_s}{V_s} \right|$$

$$\frac{1}{g_m(R_D || R_L || r_{ds})} \cdot \left| \frac{V_o}{V_s} \right|$$

f_{NR} C₃: HW3

f_{NR} C₂:

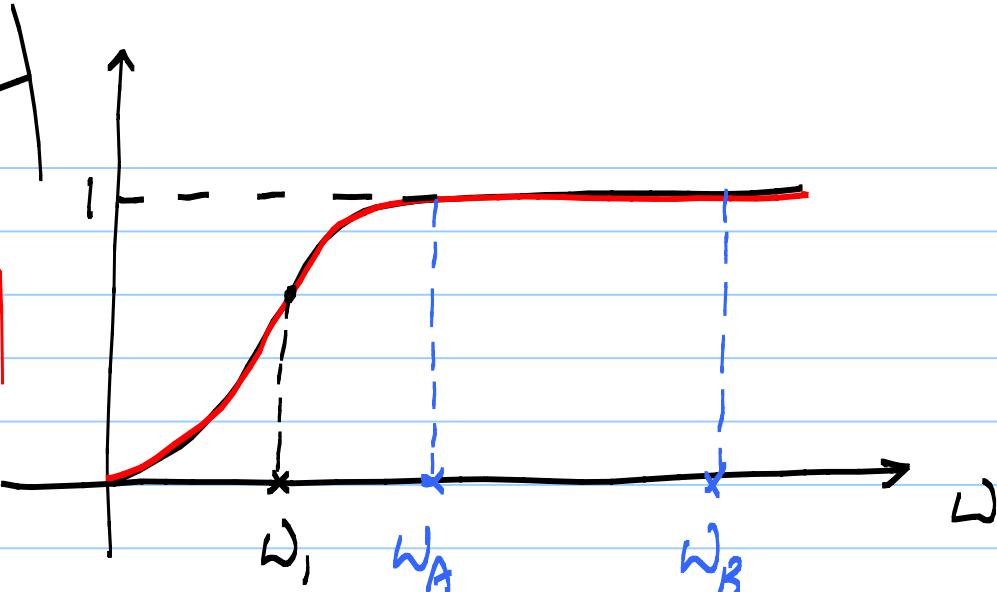

$\omega_1 = -3 \text{ dB}$ freq of

HPF $\left\{ C, \frac{R_s + R_b}{R_s} \right\}$

* choose $\omega_1 \ll \omega_A$ e.g. $\omega_1 = \frac{1}{10} \omega_A$
or $\frac{1}{20} \omega_A$ etc.


* pole for C₃ depends on R_D, R_L & r_{ds}

$$r_{ds} = f(\lambda, I_D)$$

$$\lambda = f(L)$$

* pole for C₂ depends on ?

HW3

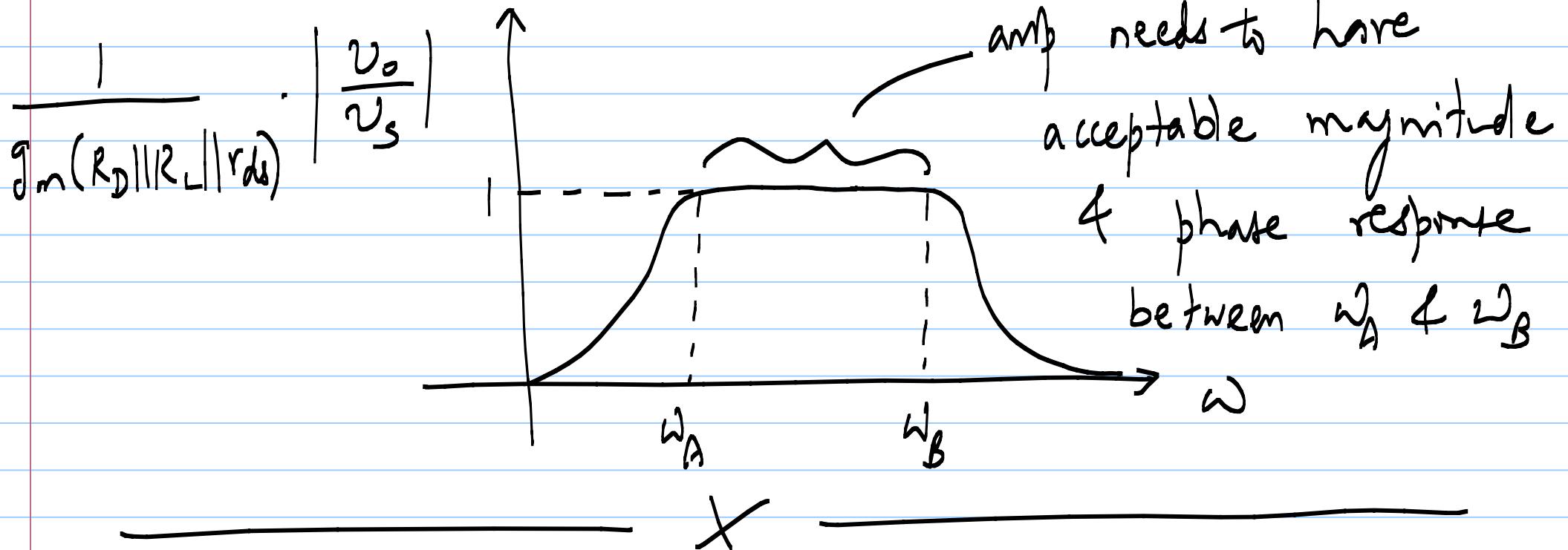


Bias
stab.


case 1 : Measure I_D , f.b. to V_O

case 2 : Measure I_S , f.b. to V_S

case 3 : Measure I_D , f.b. to V_S

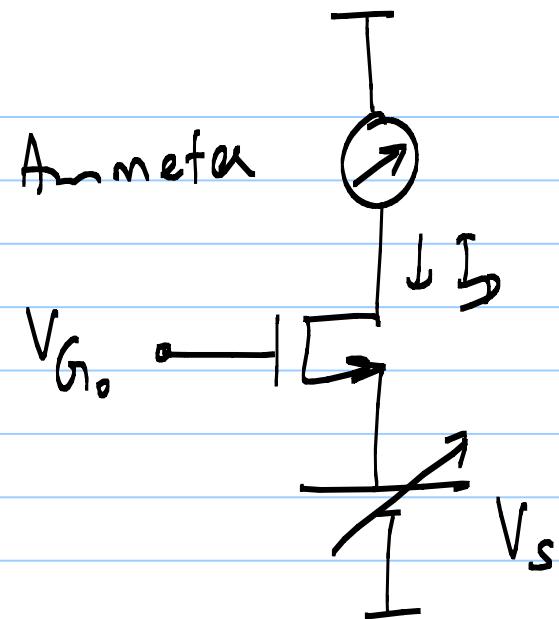

tune V_s so that $I_0 = I_D$

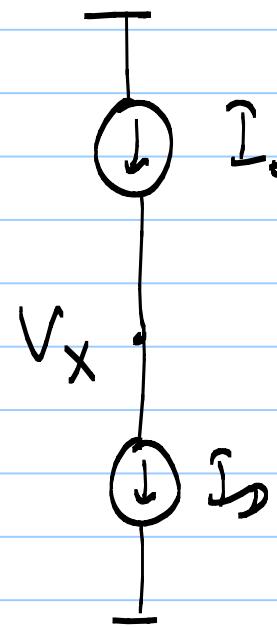

$I_0 < I_D : V_x \downarrow$

$I_0 > I_D : V_x \uparrow$


$I_0 = I_D : V_x \leftrightarrow$

e.g. $I_0 < I_D : V_x \downarrow$

We want to $\downarrow V_{GS} \Rightarrow \uparrow V_s$

} change in
direction of
current
II
inversion in polarity of f.b

DC biasing for case 3:

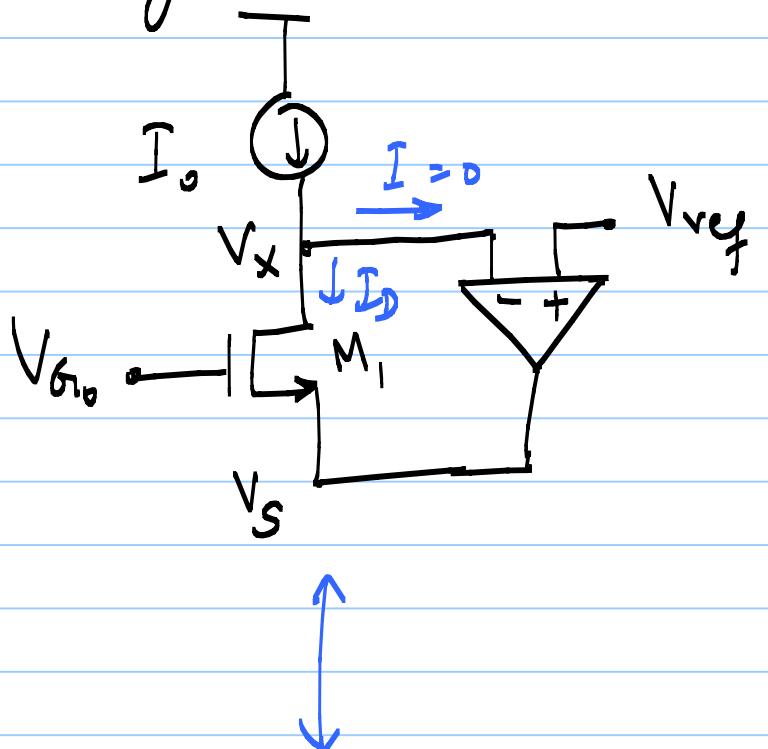


Ideal


- * opamp changes V_s to a value so that $V_x = V_{ref}$ in steady state

$$* V_s = V_{Gn_0} - V_{as}(I_D)$$


- * opamp only for DC stab.

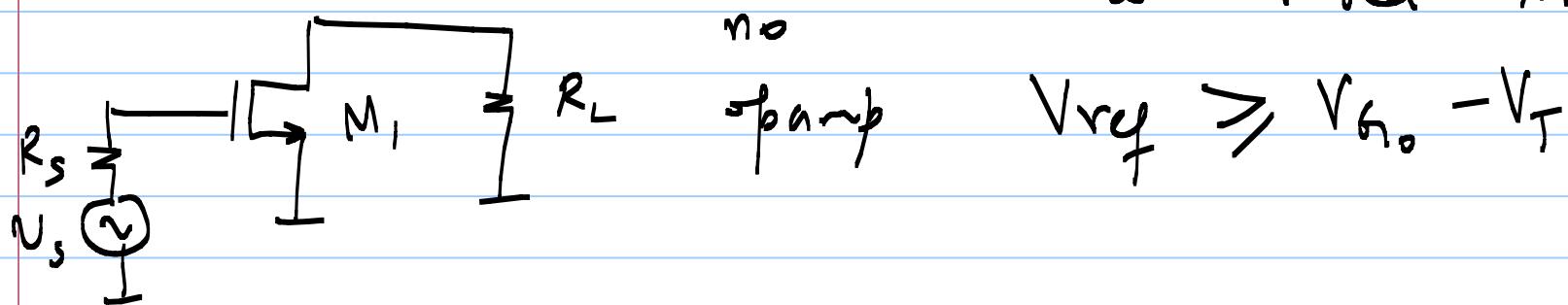- * V_{ref} chosen so that M_1 is biased in sat.





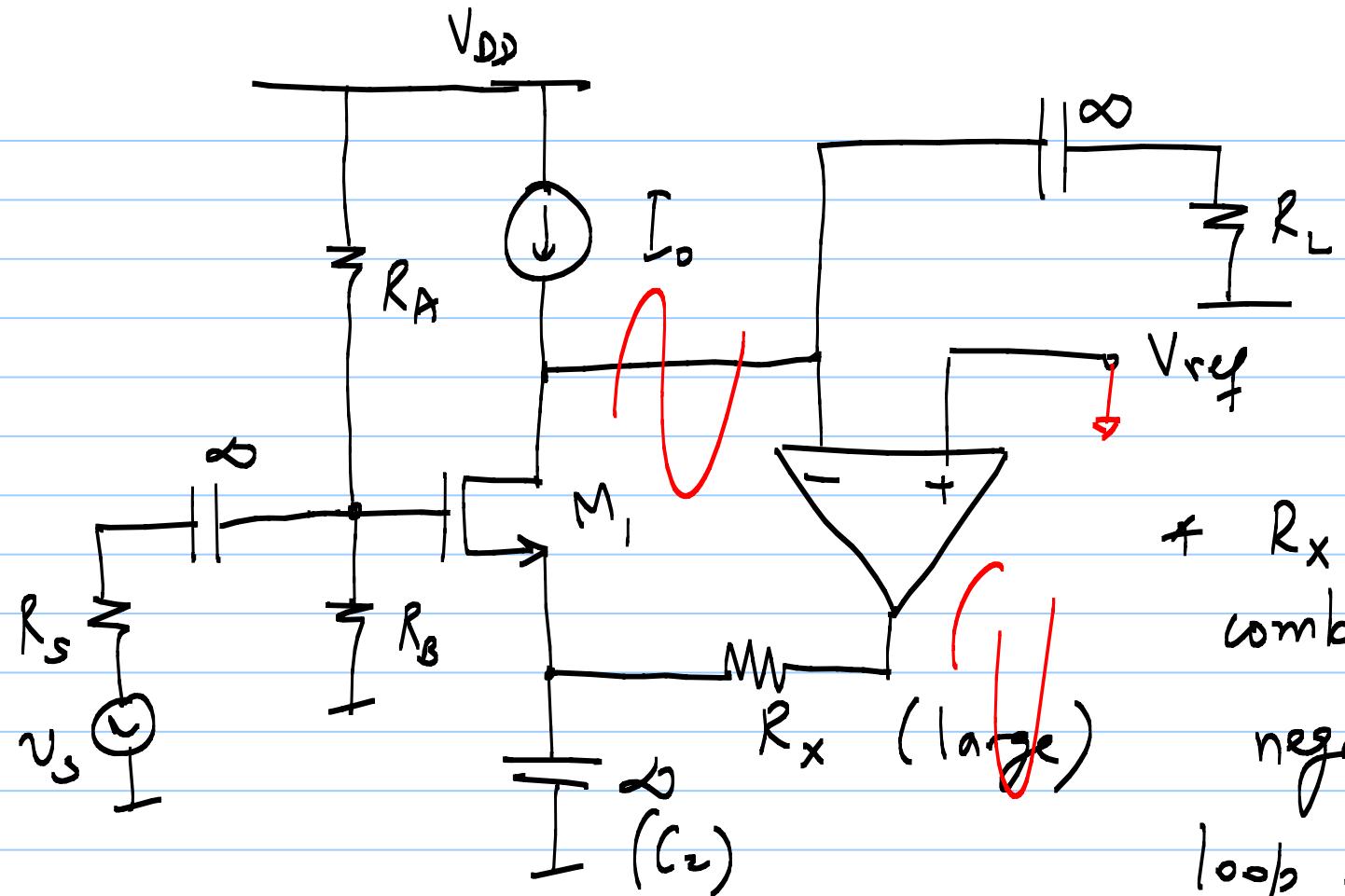


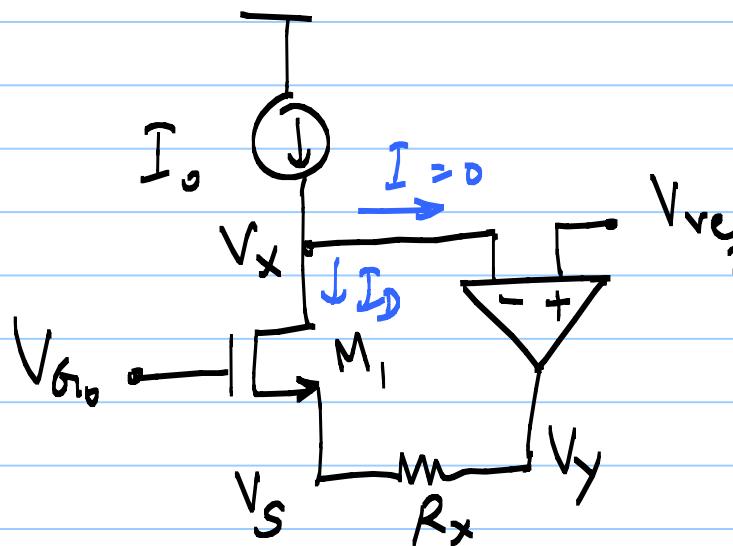+ $R_x + C_2$
combo break
negative f.b.
loop for small
signal operation



$$V_y = V_s - I_o R_x$$

as $R_x \uparrow, V_y \downarrow$

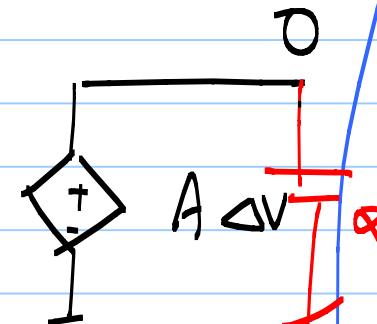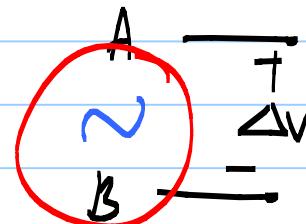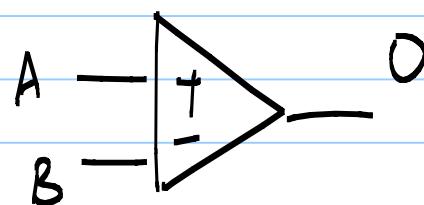

$A \rightarrow \infty$



4/9/20

Lecture 19

Bias Stab.

Sensed

no opamps required in general

I_D

I_S

Controlled

V_H


V_S

V_S


V_H

Need opamp for cases 3 & 4 because of polarity inversion in f.b.

I_S

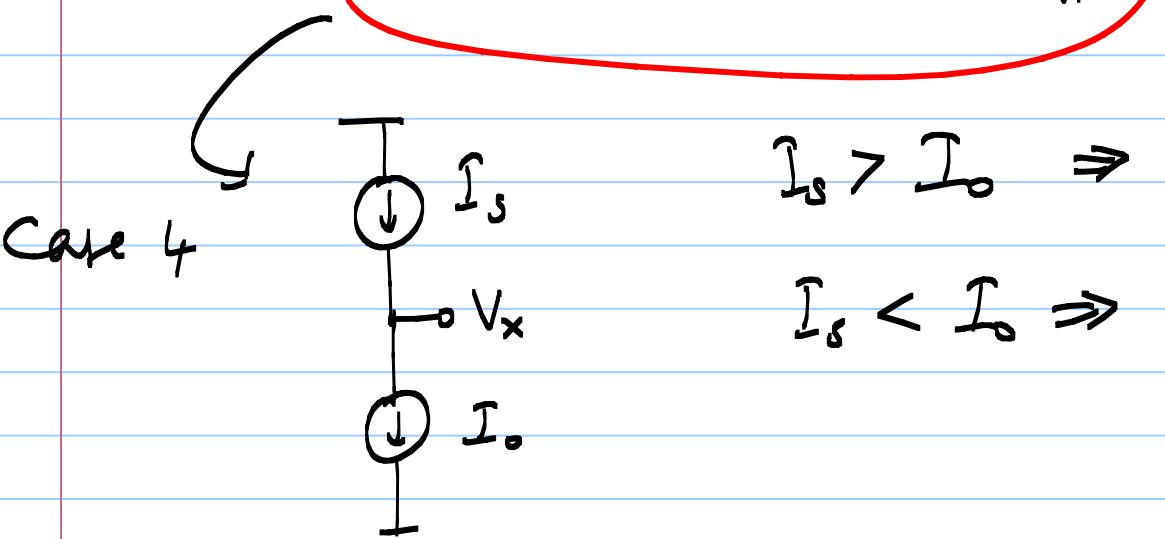
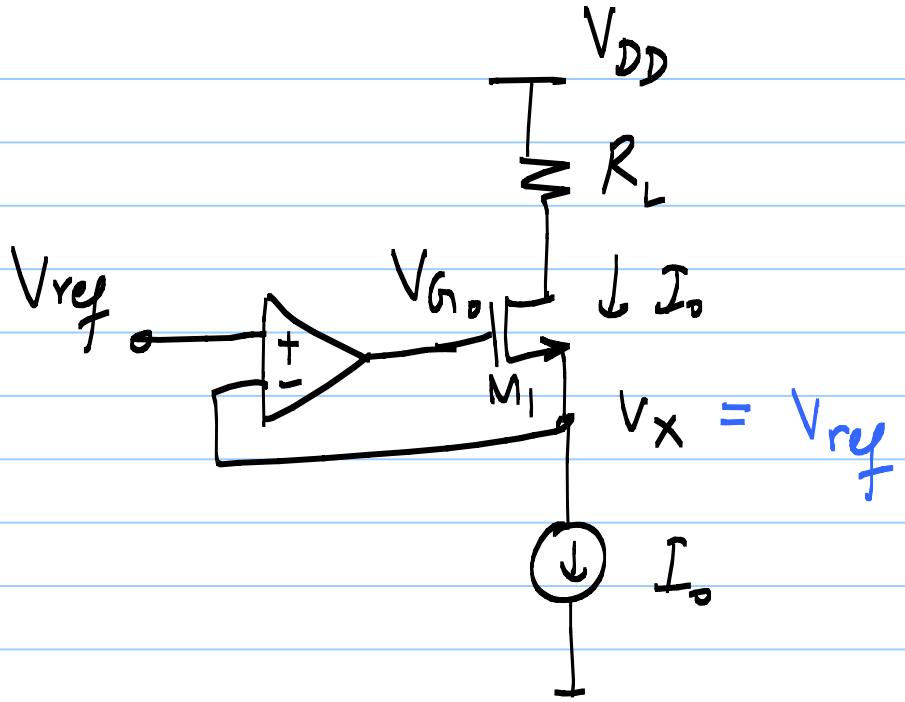
$$I_S > I_o \Rightarrow V_x \uparrow \text{ (we need to } \downarrow V_H\text{)}$$
$$I_S < I_o \Rightarrow V_x \downarrow \text{ (we need to } \uparrow V_H\text{)}$$



$$V_{G_0} = V_{ref} + \left. V_{GS} \right|_{I_0}$$

$$V_{D_0} = V_{DD} - I_0 R_L$$


$$V_{S_0} = V_{ref}$$

Choose V_{ref} so that M_1 is sat.

$$V_{D_0} \geq V_{G_0} - V_T$$


* You can use opamps in cases 1 & 2 also

e.g.
case 1

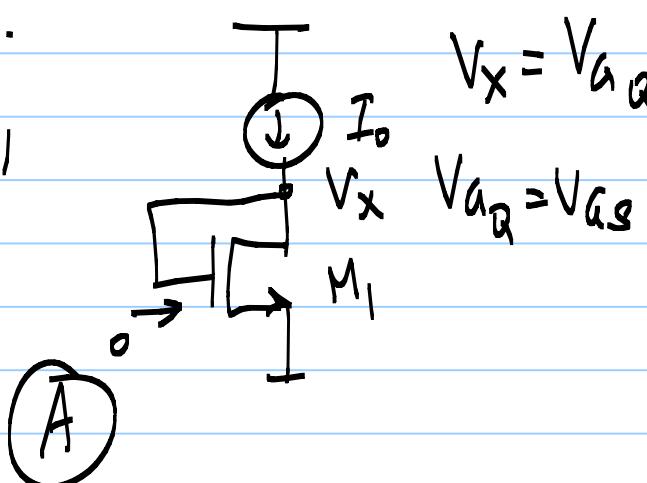

$$V_x = V_{G_Q} = V_{D_Q}$$



$$V_{G_Q} = V_{GS}$$

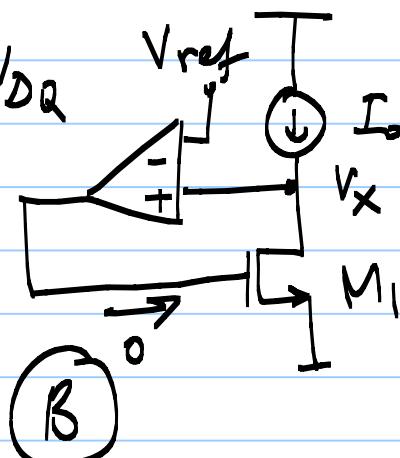


$$V_x = V_{ref} = V_{D_Q}$$

$$V_{G_Q} = V_{GS}$$

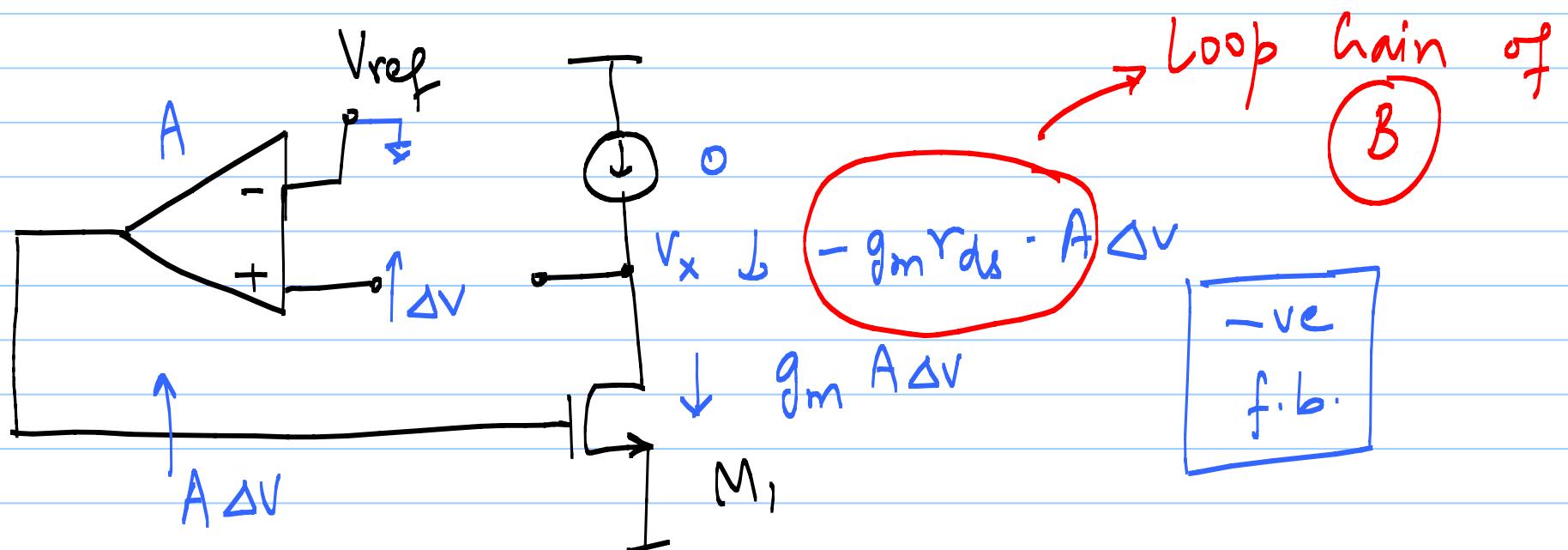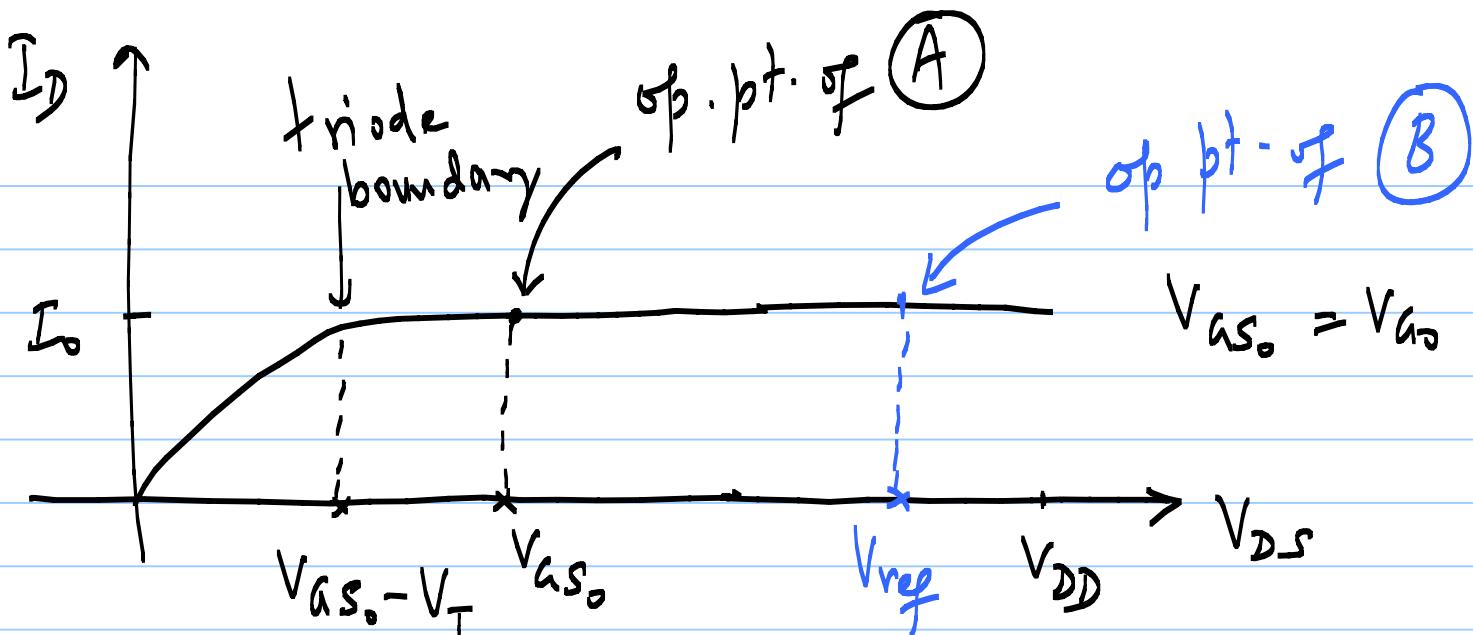can be biased further from triode boundary



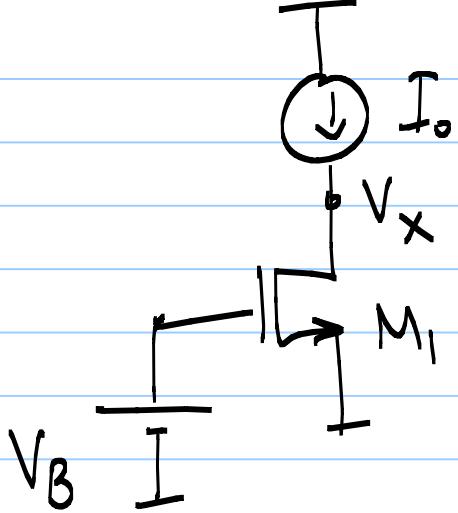
$$\text{Loop gain of } \textcircled{A} = -g_m r_d$$




$$V_B \neq V_{AS} \Big|_{I_o}$$

\textcircled{I} $V_B < V_{AS} \Big|_{I_o} \Rightarrow V_x \uparrow \xrightarrow{\text{to}} \infty$

\textcircled{II} $V_B > V_{AS} \Big|_{I_o} \Rightarrow V_x \downarrow$

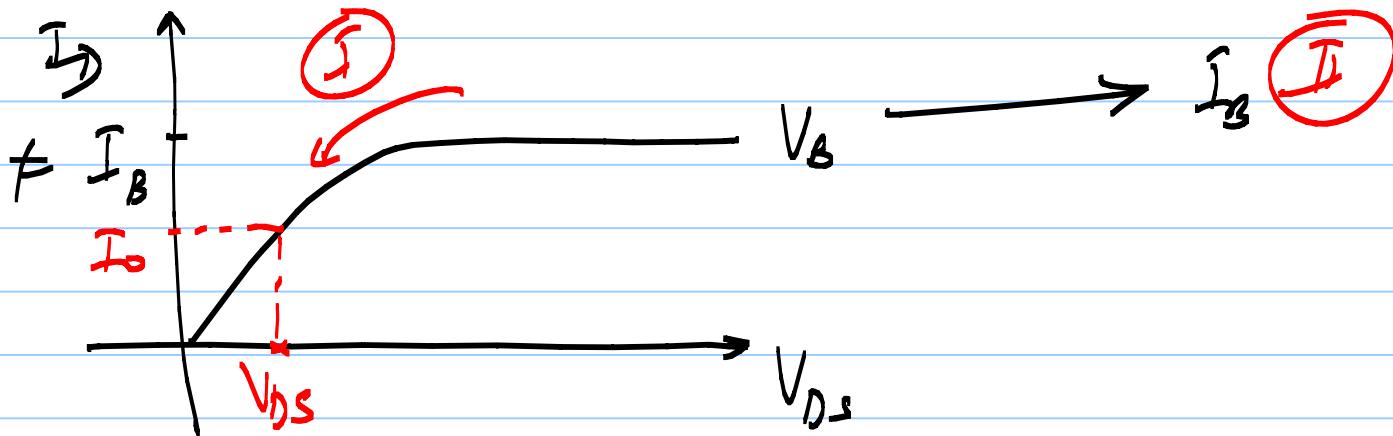



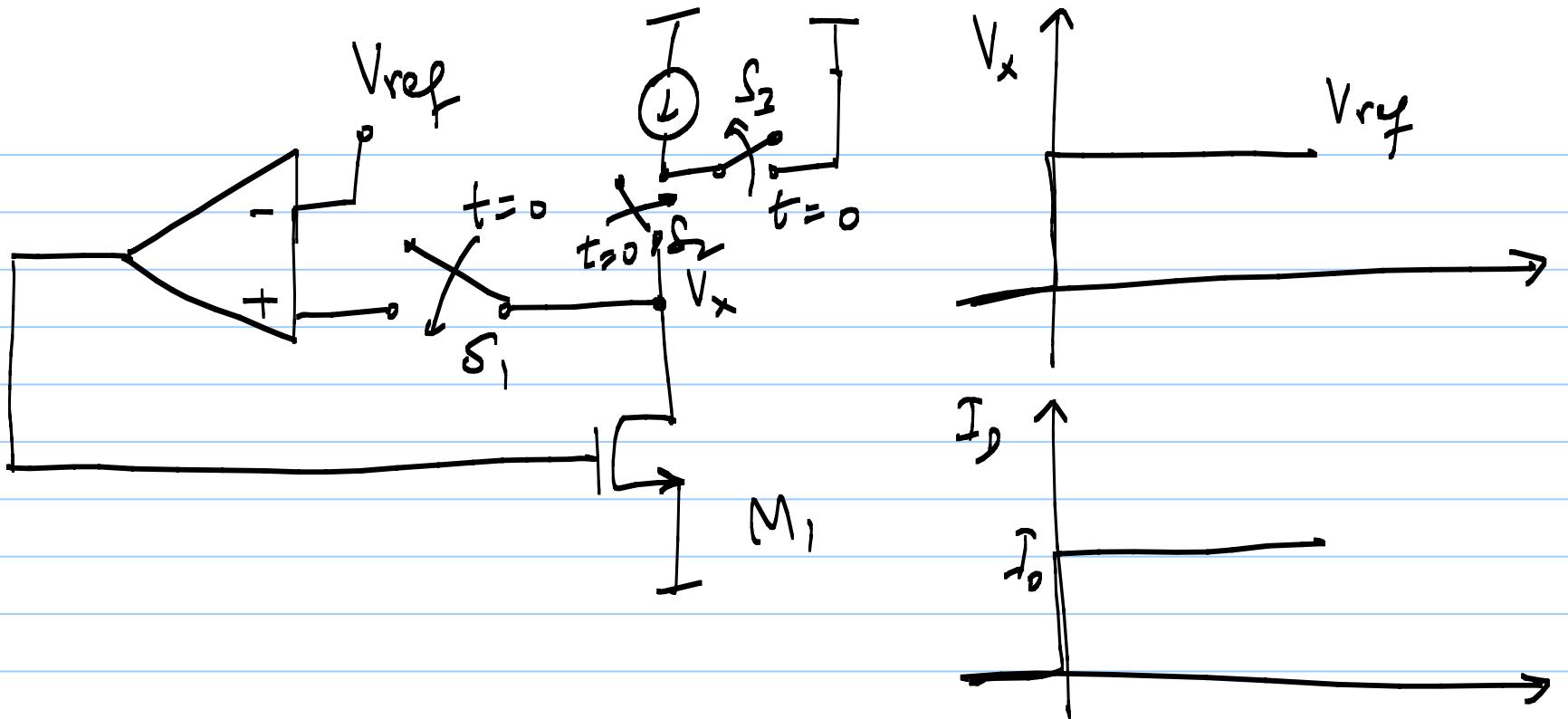


8/9/20

Lecture 20



Negative f.b. to create small signal controlled sources

VCVS using opamp

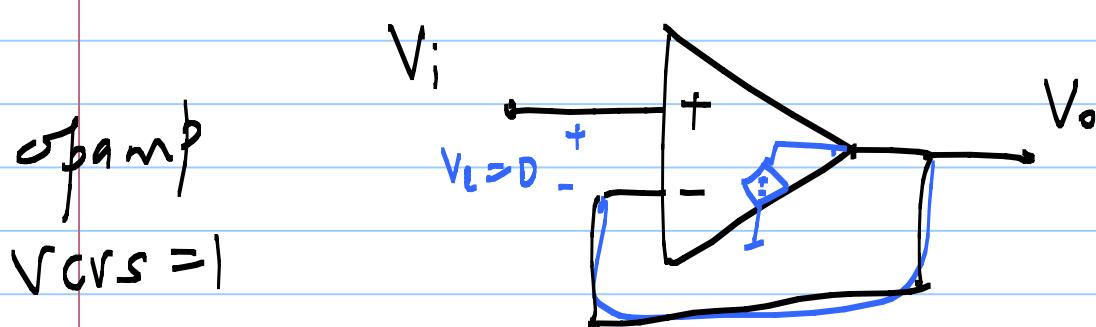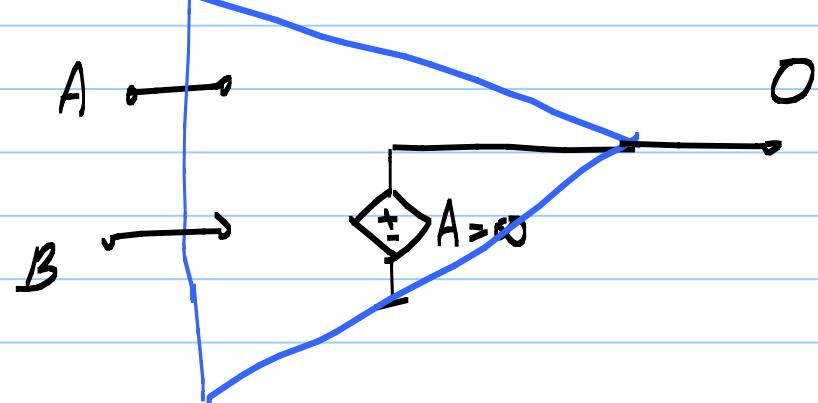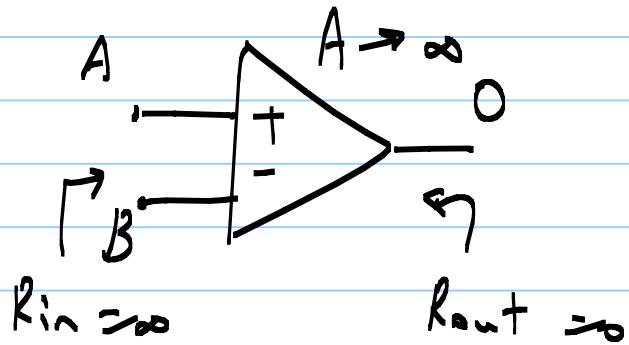


VCVS using MOSFET (Any controlled source)

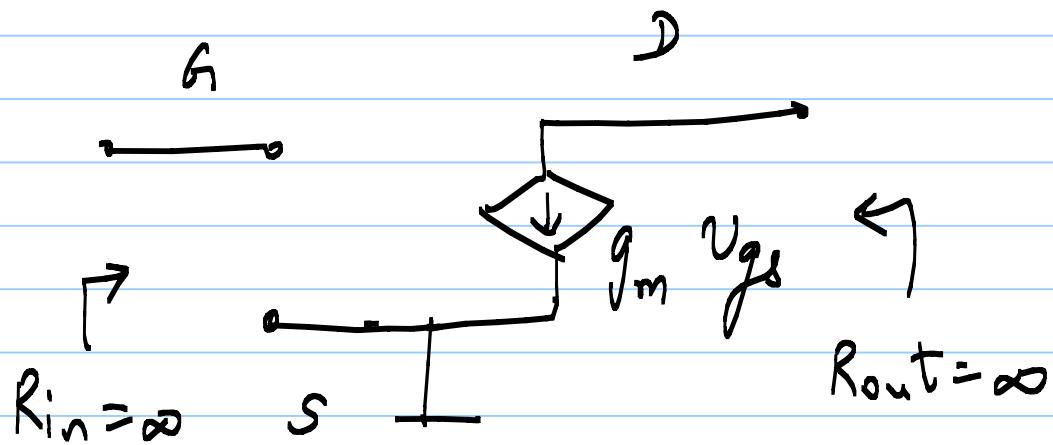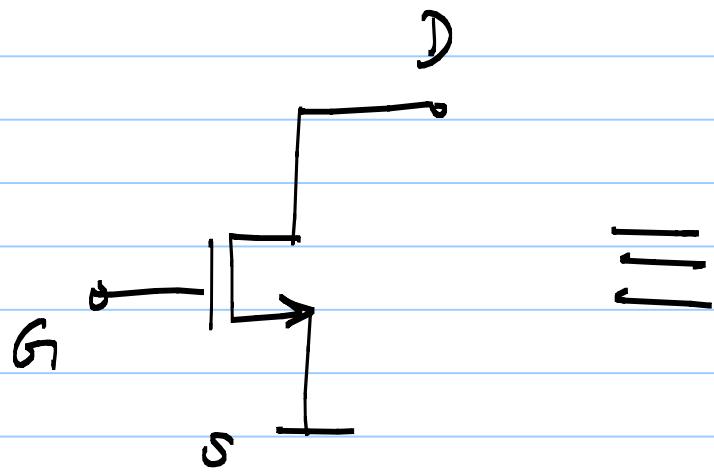- 1) Works only for small-signal
- 2) Idealized view for MOSFET :



$$G_m = g_m$$

allow $g_m \rightarrow \infty$

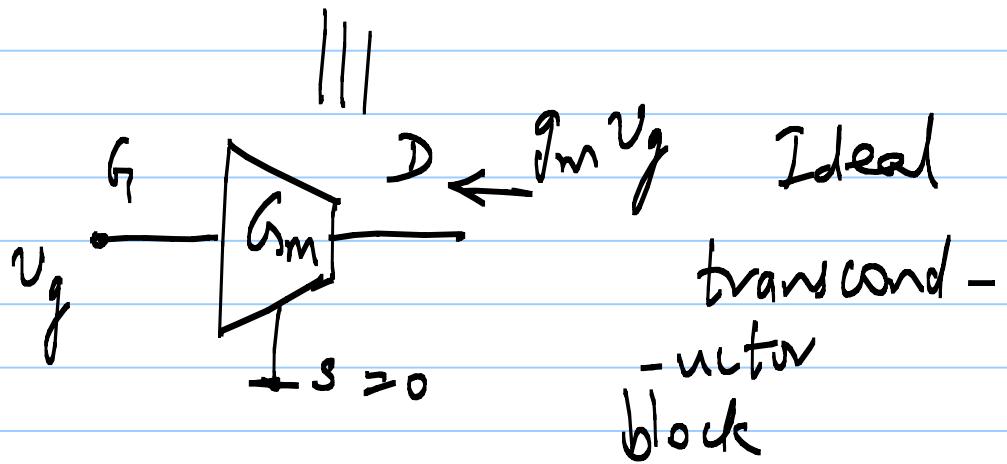

i.e. $\left(\frac{W}{L}\right)$ & I_D can be as large as required
 to set $g_m = \text{as large as required.}$


Ideal VCVS = : $V_{out} = V_{in}$ ($g_m \rightarrow \infty$)

* measure V_{in} , V_{out} ; compare

* change V_{out}


* If $V_{out} > V_{in}$, reduce i_x

If $V_{out} < V_{in}$, increase i_x

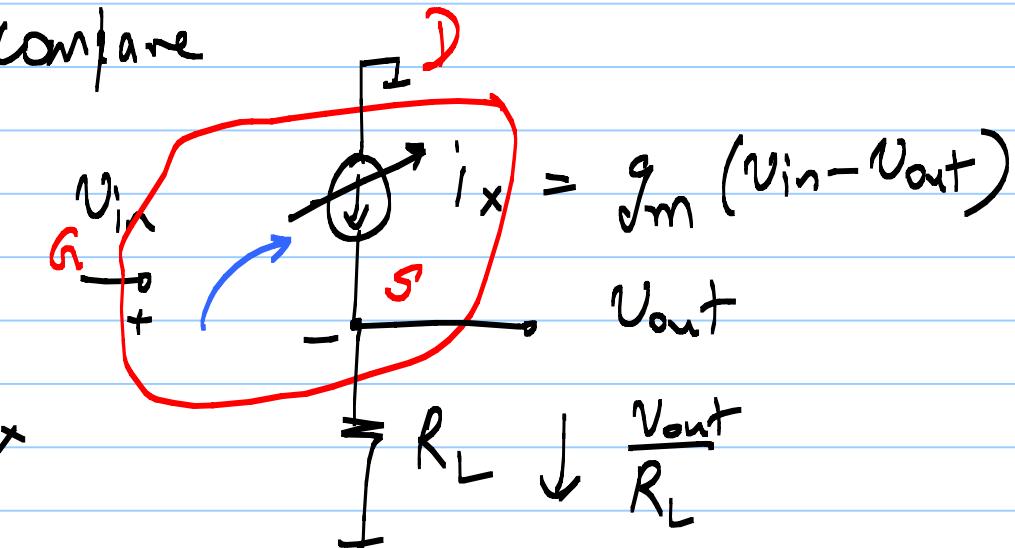


output current $\frac{V_{out}}{R_L} = g_m(V_{in} - V_{out})$ if in neg. f.b.

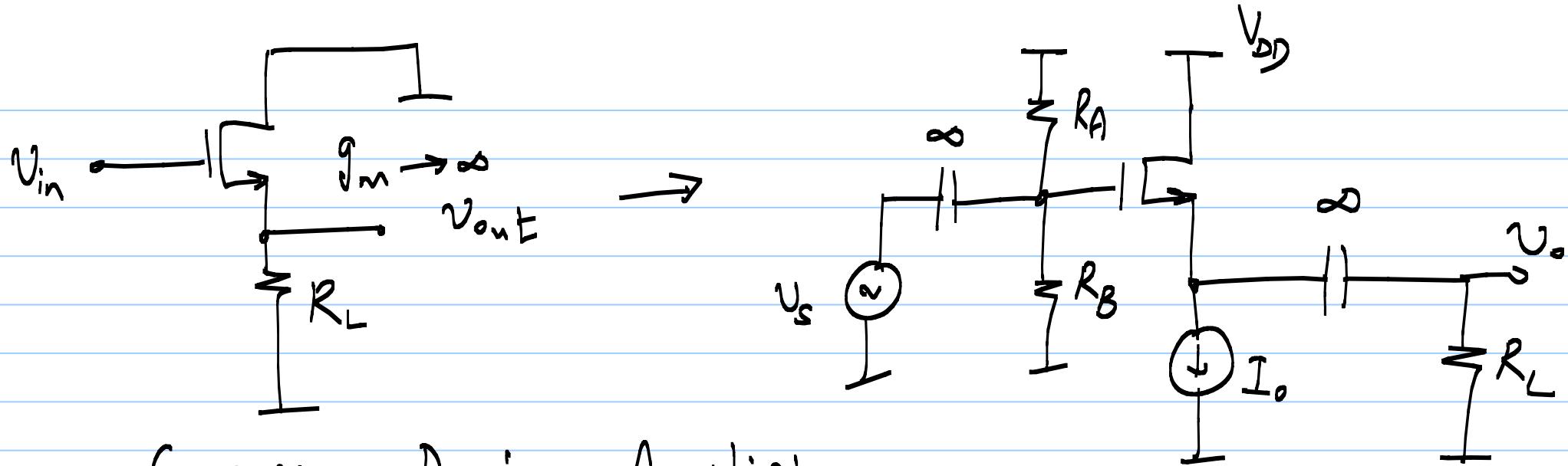we want $V_{out} = V_{in} \Rightarrow g_m \rightarrow \infty$ so that
 $V_{in} - V_{out} \rightarrow 0$





Common Drain Amplifier

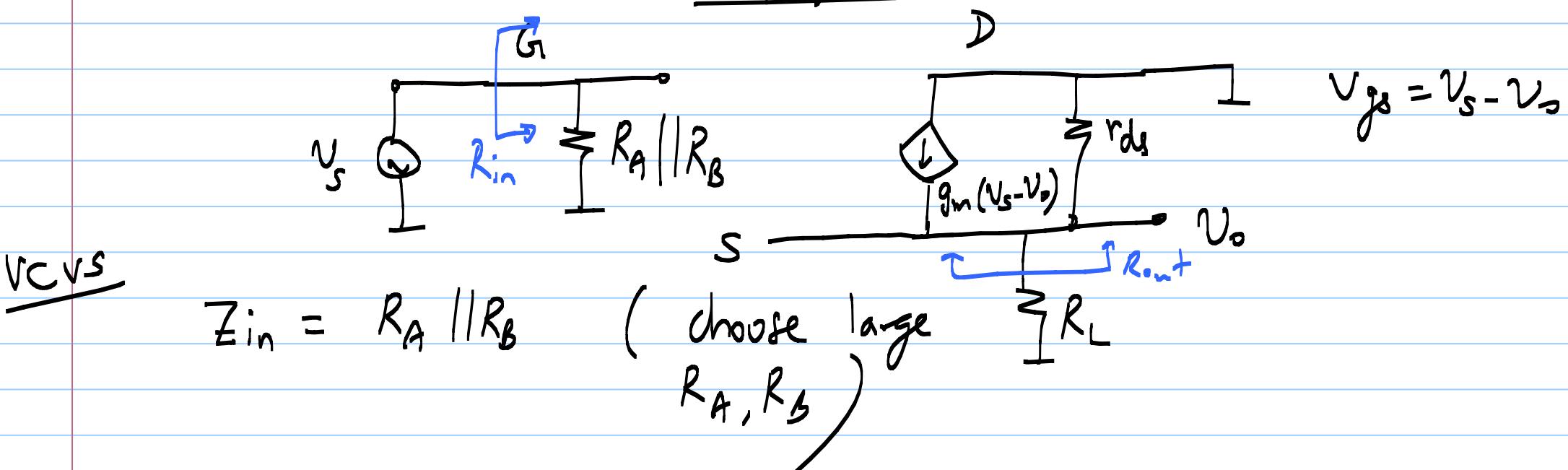

$$Z_{out} = ?$$

set

$$v_s = 0$$

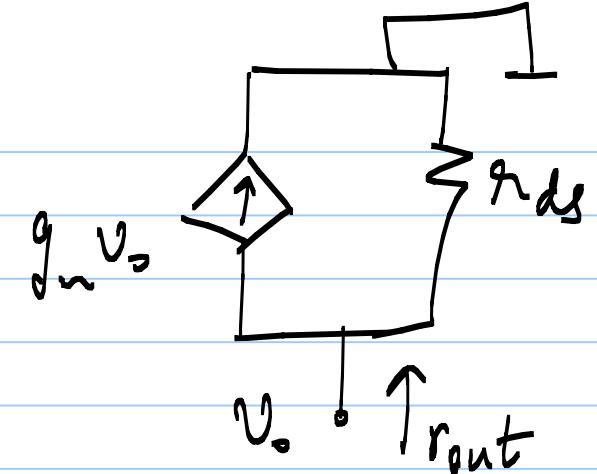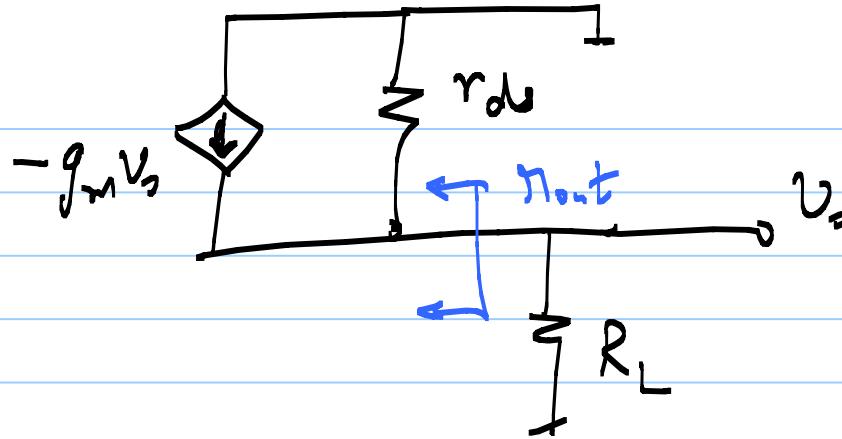

$$r_{out} = \frac{1}{g_m} \parallel r_{ds}$$

$$Z_{out} = \frac{r_{ds}}{1 + g_m r_{ds}} = \frac{1}{g_m} \cdot \frac{g_m r_{ds}}{1 + g_m r_{ds}}$$

$$\text{If } g_m r_{ds} \gg 1, \quad Z_{out} = \frac{1}{g_m}$$

KCL @ S node :


$$g_m (v_s - v_o) = v_o (G_L + g_{ds})$$

$$V_o(g_m + g_{ds} + G_L) = g_m V_s$$

$$\frac{V_o}{V_s} = \frac{g_m}{g_m + g_{ds} + G_L} < 1$$

$\rightarrow 1$ if $g_m \rightarrow \infty$



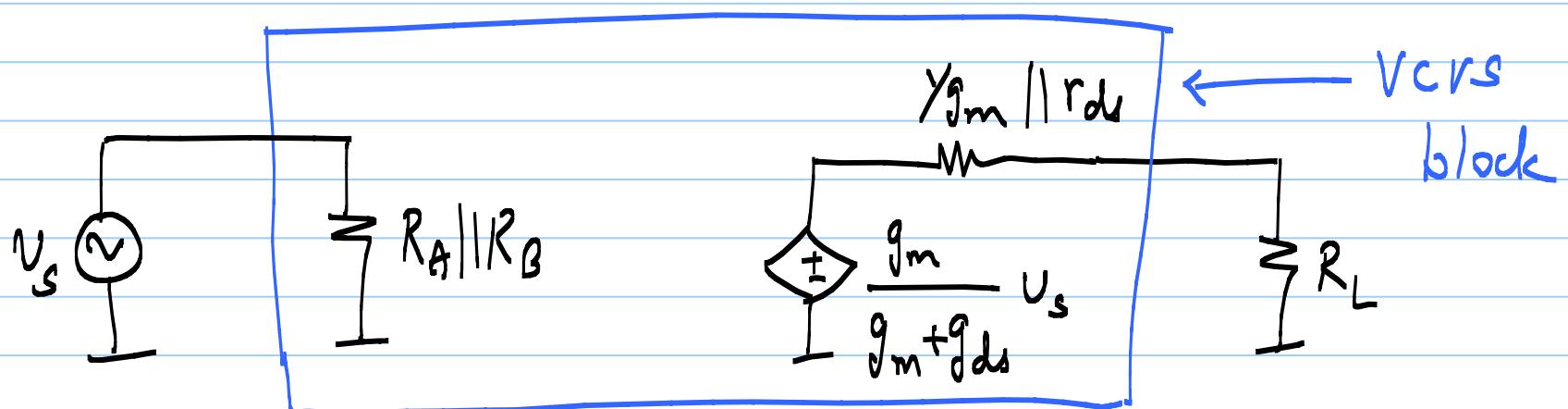
$$\hookrightarrow Z_{out} \rightarrow 0$$



9/9/20

Lecture 21

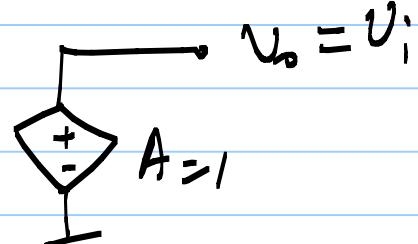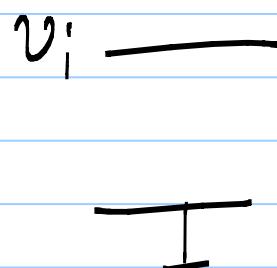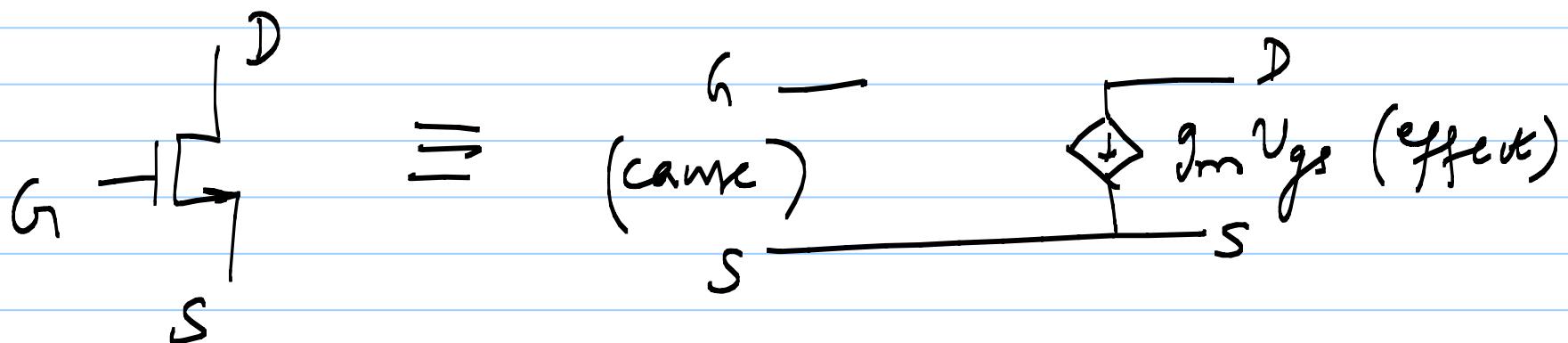MOSFET VCVS, gain = 1, $V_o = V_i$
using negative f.b.



$$V_o = V_i$$
$$\Rightarrow \underbrace{V_i - V_o}_{} = 0$$

comparison

use this $(V_i - V_o)$ ← action
to change V_o

Sense id or is (relate to v_o)

drive back to v_{gs} (relate to $v_i - v_o$)

i_d, i_s, v_g, v_s etc. are small signed quantities


$$v_i, v_o \leftrightarrow v_g, v_s \quad (\text{cause})$$

$$v_o \leftrightarrow v_d, v_s \quad (\text{effect id or is})$$

$$v_o \rightarrow v_s \quad) \quad v_i - v_o = v_{gs}$$

$$v_i \rightarrow v_g$$
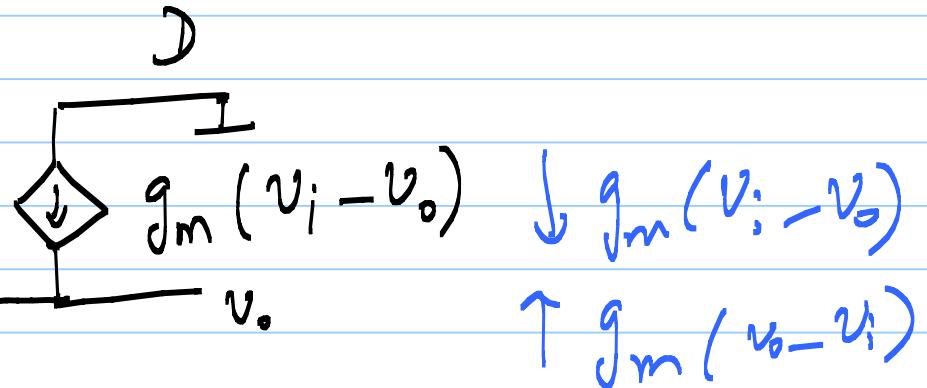
$$v_i \xrightarrow{a} \frac{+}{v_i - v_o} \xrightarrow{s}$$



Check for -ve f.b.:

If $v_o > v_i \Rightarrow g_m(v_o - v_i)$ will flow out of \textcircled{S} node $\Rightarrow v_o \downarrow$

If $v_o < v_i \Rightarrow g_m(v_i - v_o)$ will flow into \textcircled{S} node $\Rightarrow \uparrow v_o$


$$v_o = v_i \Rightarrow i_d = 0$$



Common Drain Amplifier

(or)

Source
follower

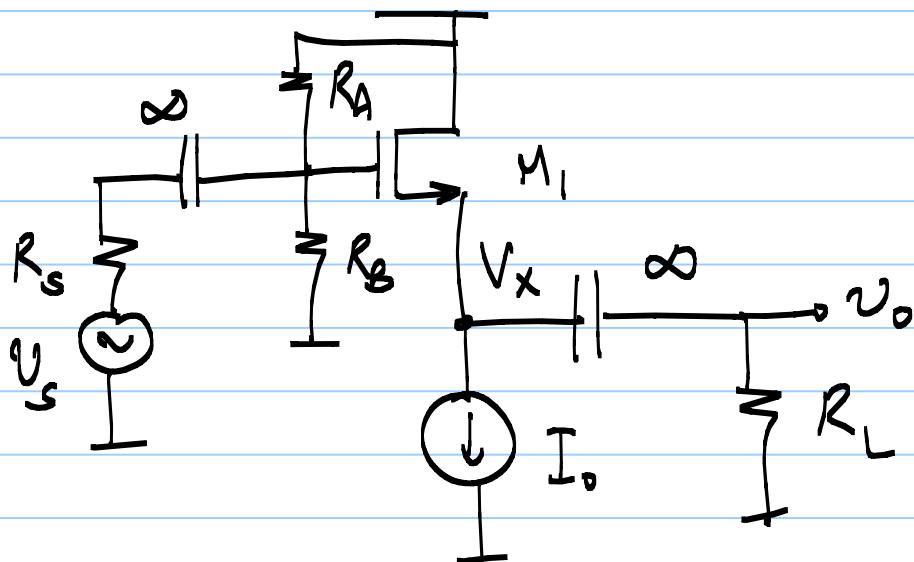

$$V_x = \frac{R_B}{R_A + R_B} V_{DD} - V_T$$

$$- \sqrt{\frac{2 I_0}{\mu_n C_{ox} \left(\frac{W}{L} \right)}}$$

- 1) choose large R_A, R_B (large Z_{in})
- 2) As $g_m \rightarrow \infty$, gain $\rightarrow 1$ (gain < 1 if R_L is significant)
- 3) As $g_m \rightarrow \infty$ $Z_{out} \rightarrow 0$

$$\frac{v_o}{v_s} = \frac{g_m}{g_m + g_{ds} + G_L}$$

$$\begin{aligned} g_m &>> G_L \\ g_m &>> g_{ds} \end{aligned}$$

Swing limits

$$v_s = V_A \sin \omega t$$

i) Cutoff limit

$$I_D = I_Q + i_d$$

$$= I_o + i_d$$

assume g_{ds} is very small

$$i_d = \frac{V_o}{R_L} = \frac{1}{R_L} \cdot \frac{g_m R_L}{1 + g_m R_L} \cdot v_s$$

$$I_D = I_o + \frac{g_m R_L}{1 + g_m R_L} \cdot \frac{V_A \sin \omega t}{R_L}$$

$$\text{Set } I_D = 0 \Rightarrow V_{A_1} = I_0 \cdot R_L \left[1 + \frac{1}{g_m R_L} \right]$$

2) Triode limit

$$V_D - V_S = V_a - V_S - V_T$$

$$V_D = V_a - V_T$$


$$V_{DD} = \frac{V_{DD} \cdot R_B}{R_A + R_B} + V_{A_2} \sin \omega t - V_T$$

$$V_{A_2} = \frac{R_A}{R_A + R_B} \cdot V_{DD} + V_T$$

$$V_{A_{\max}} = \min \{ V_{A_1}, V_{A_2} \}$$




MOSFET VCCS

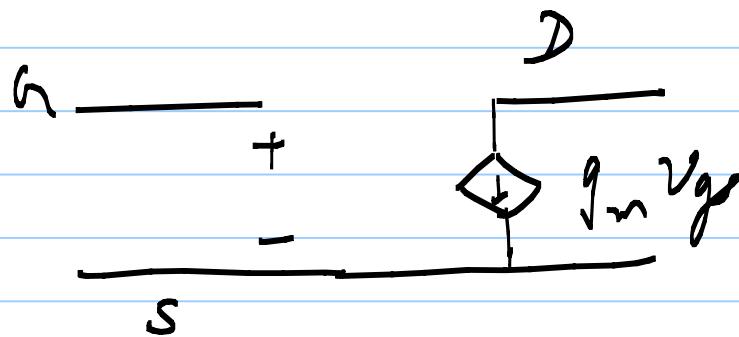
$$i_o = G \cdot v_i = \frac{v_i}{R}, Z_{in} = \infty, Z_{out} = \infty$$



controlling - v_{gs}

controlled - i_d

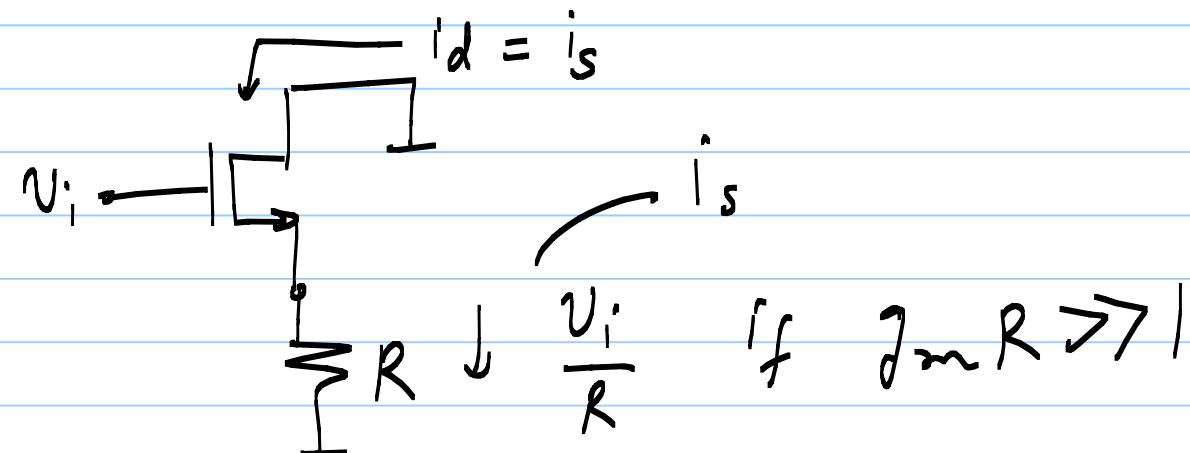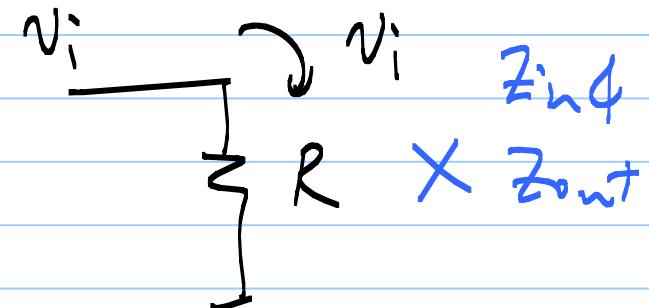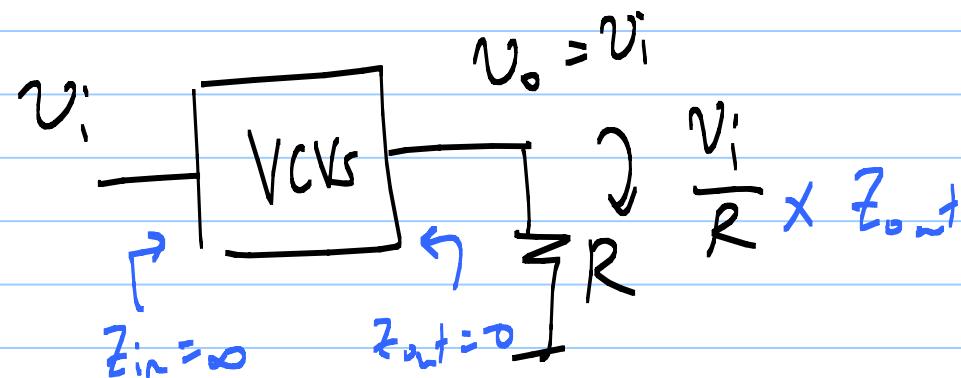

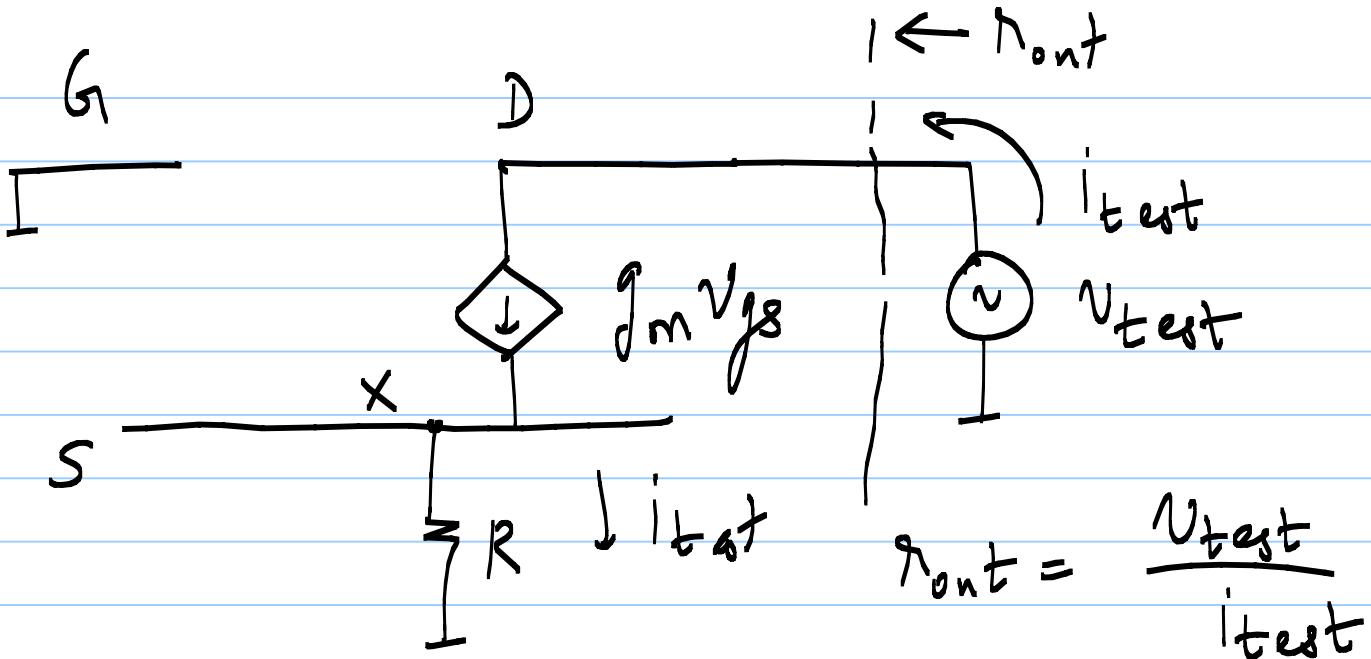

$$V_x = i_{\text{test}} \cdot R$$


$$g_m v_{ds} = - g_m V_x = - g_m R \cdot i_{\text{test}} = i_{\text{test}}$$

$$i_{\text{test}} = 0 \Rightarrow Z_{\text{out}} = \infty$$


(HW)

Calculate Z_{out} if r_{ds} is finite
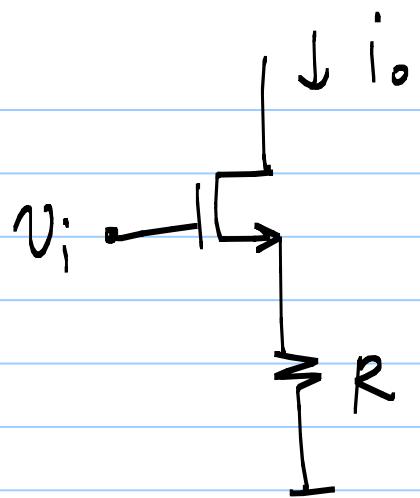
$$Z_{\text{out}} = r_{ds} + g_m R r_{ds} + R$$



Trans admittance
amplifier



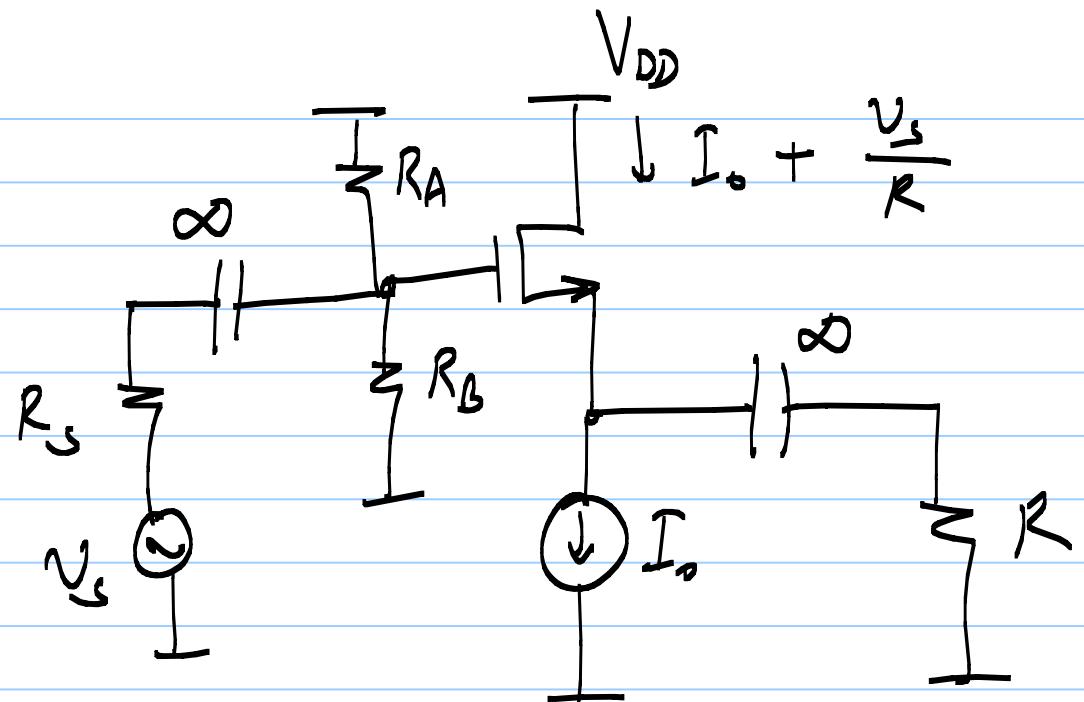


10/9/20

Lecture 21

VCCS

$$i_o = \frac{v_s}{R} = G \cdot v_s$$

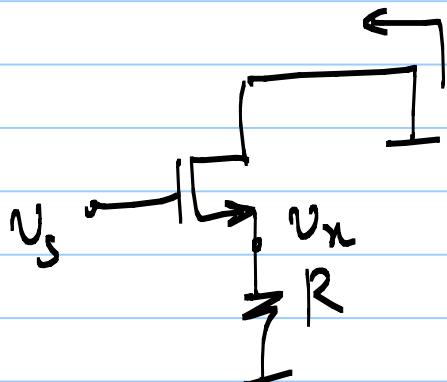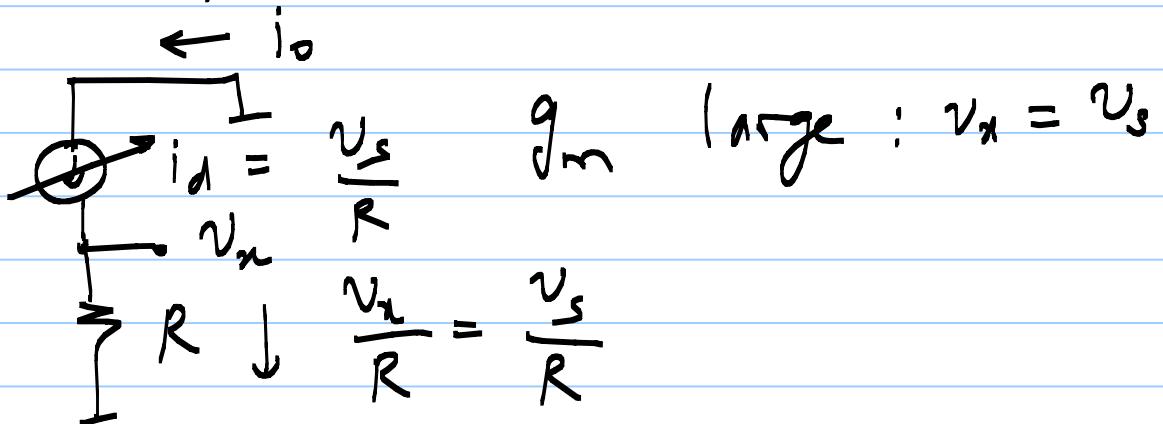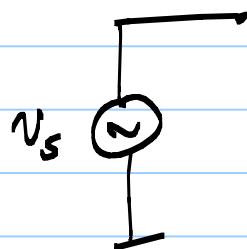

$$i_o = \frac{v_s}{R} \quad \text{if } g_m \rightarrow \infty$$


$$\text{actual } i_o = \frac{v_x}{R} = \frac{v_s}{R} \cdot \left(\frac{g_m}{g_m + G} \right)$$


$$i_o = \frac{g_m}{1 + g_m R} \cdot v_s$$

Large $g_m \Rightarrow g_m R \gg 1$ (\approx) $g_m \gg 6$


HW 7: Swing limits

Phase Splitter

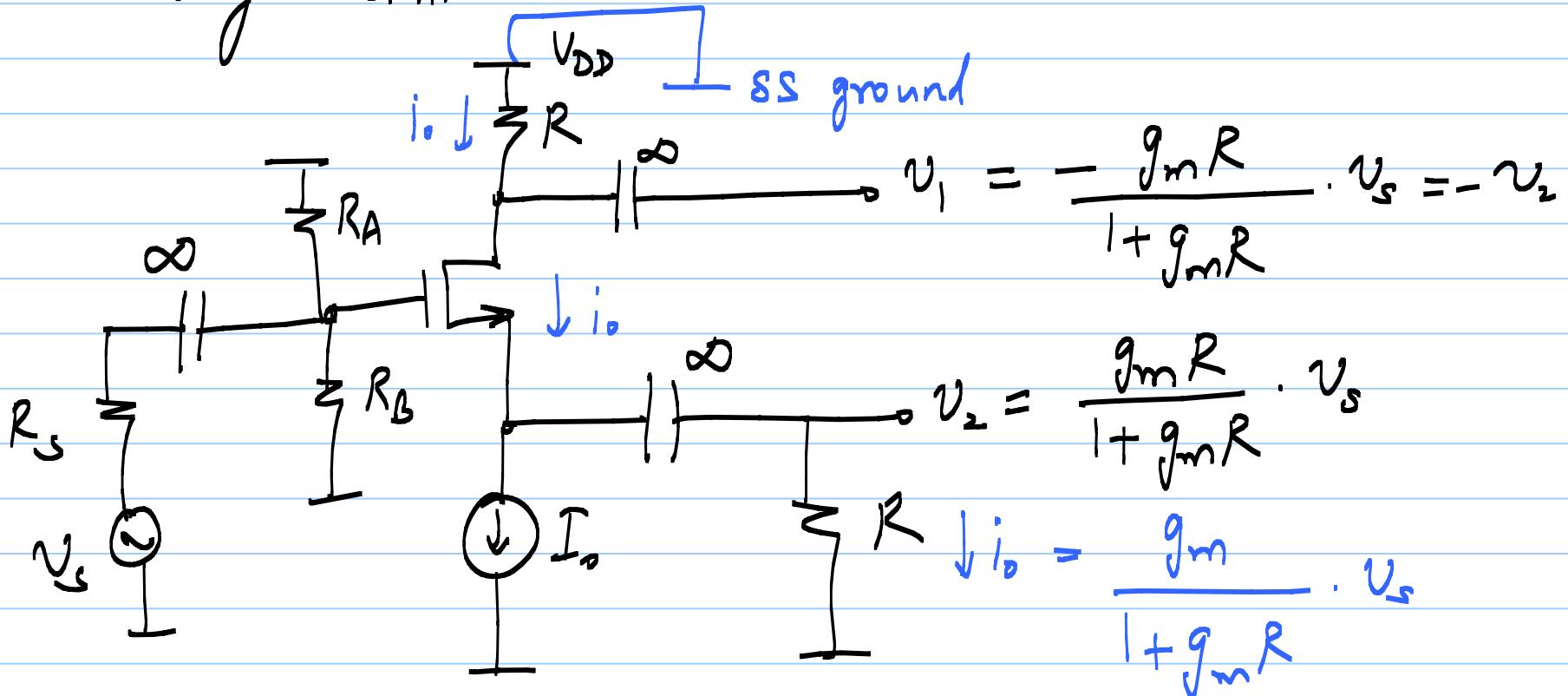

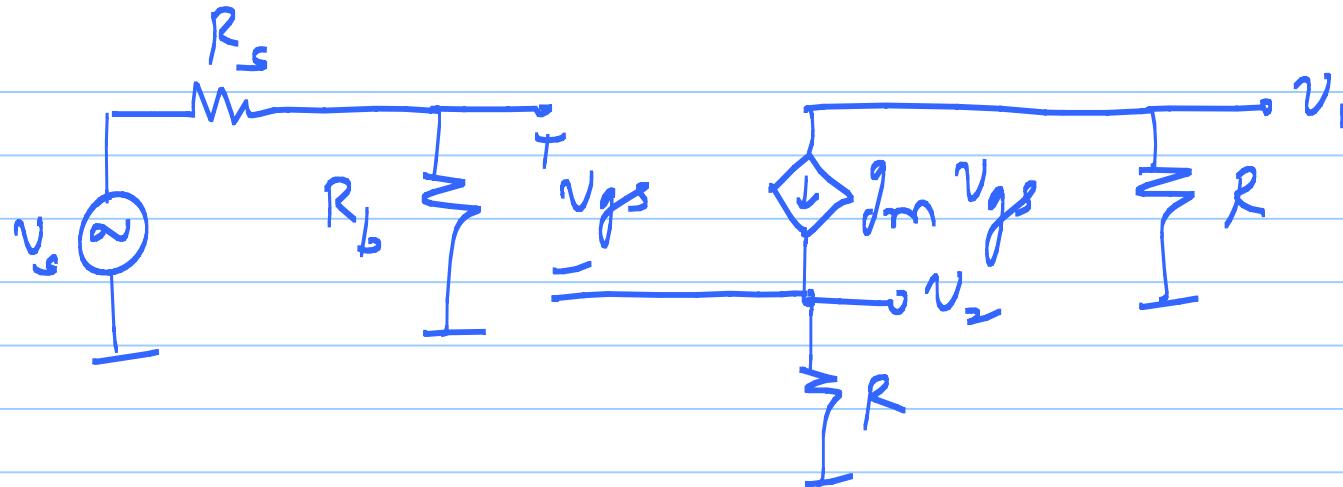

$$r_{out} \approx (g_m r_{ds}) R$$

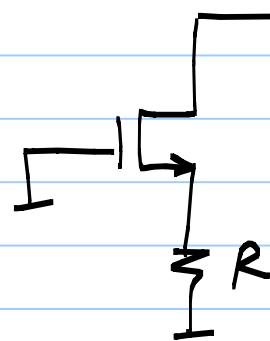


MOSFET incremental CCCS

$$i_o = i_{in}$$

$Z_{in} = 0$


$Z_{out} = \infty$

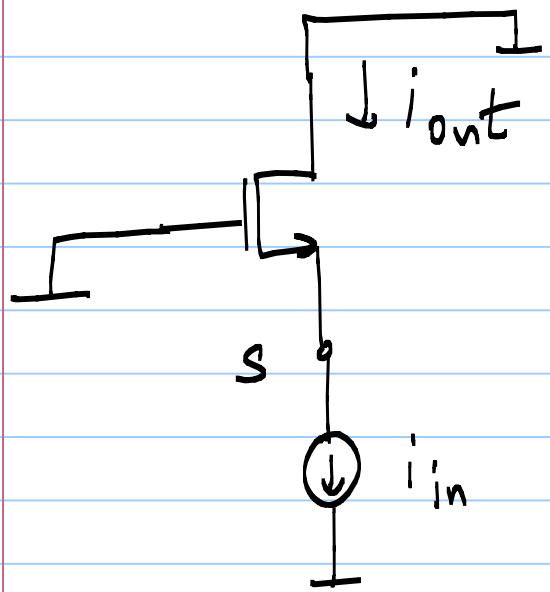


$$i_a = 0$$

$$i_d = i_s$$


v_{gs} - change

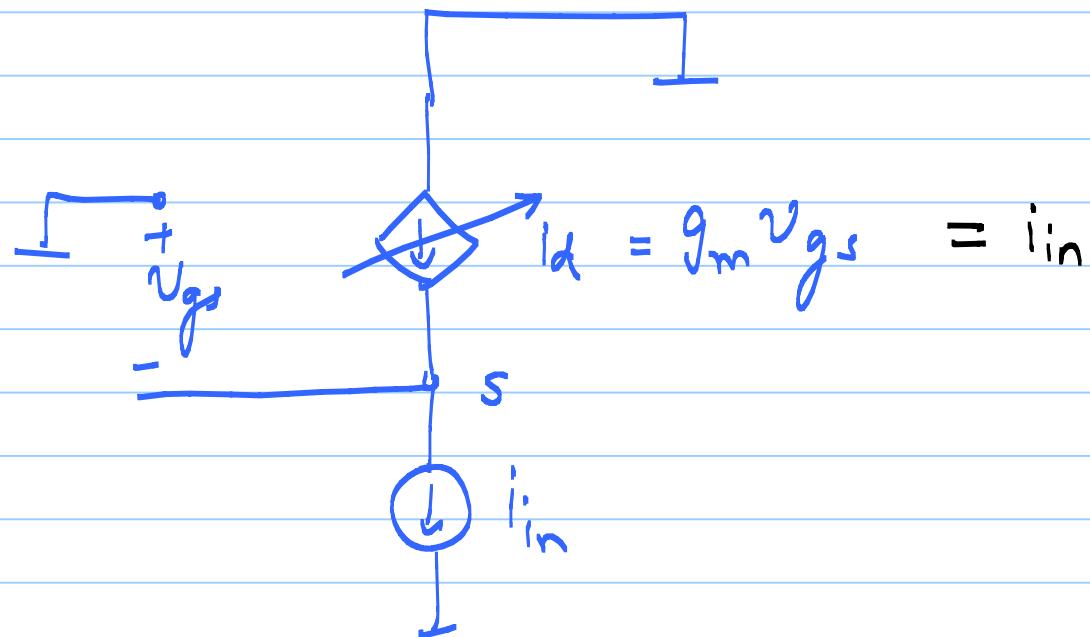


Neg. f.b. biasing : source f.b.

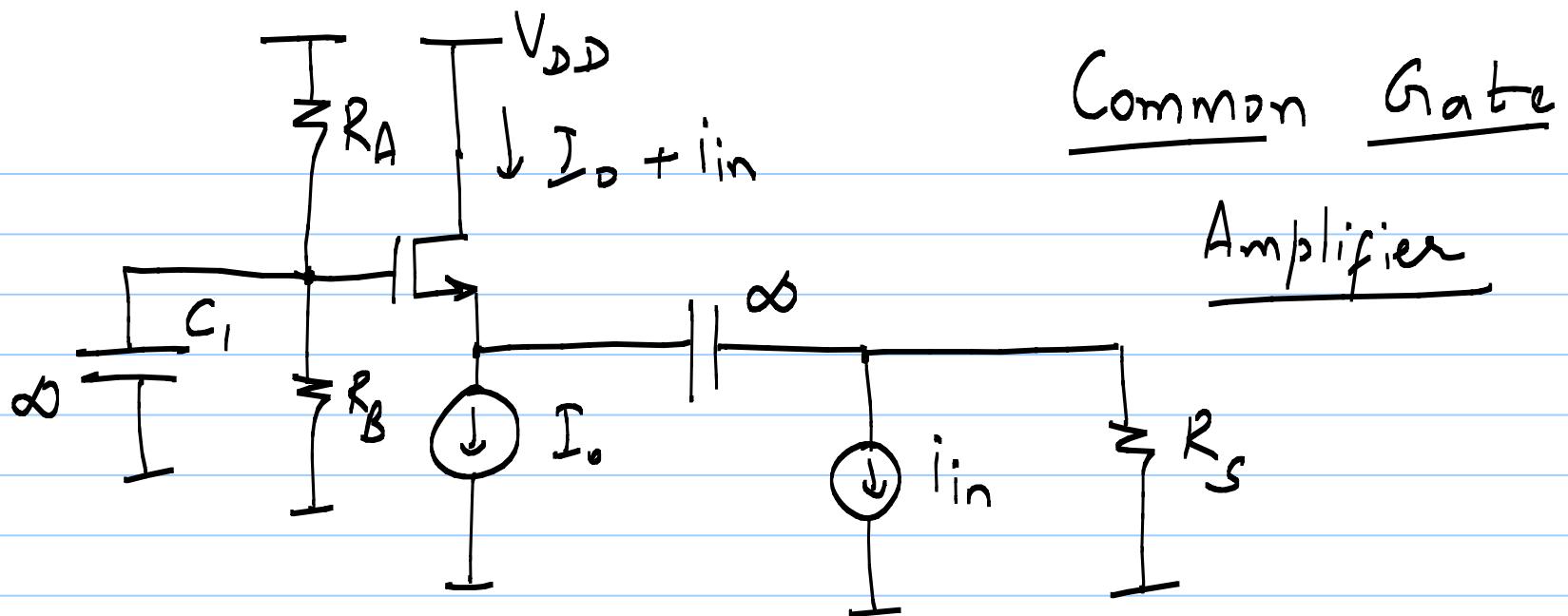

DC

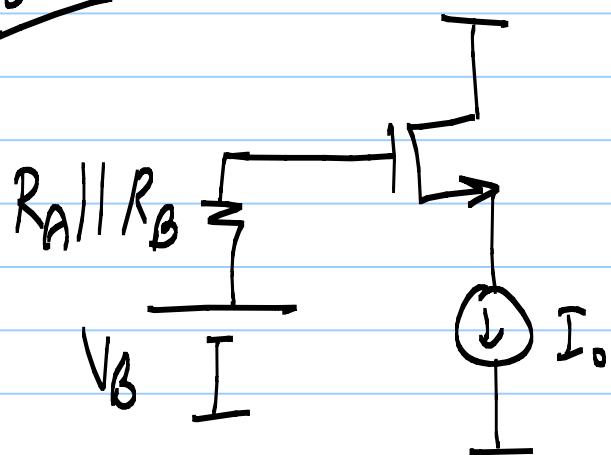

AC

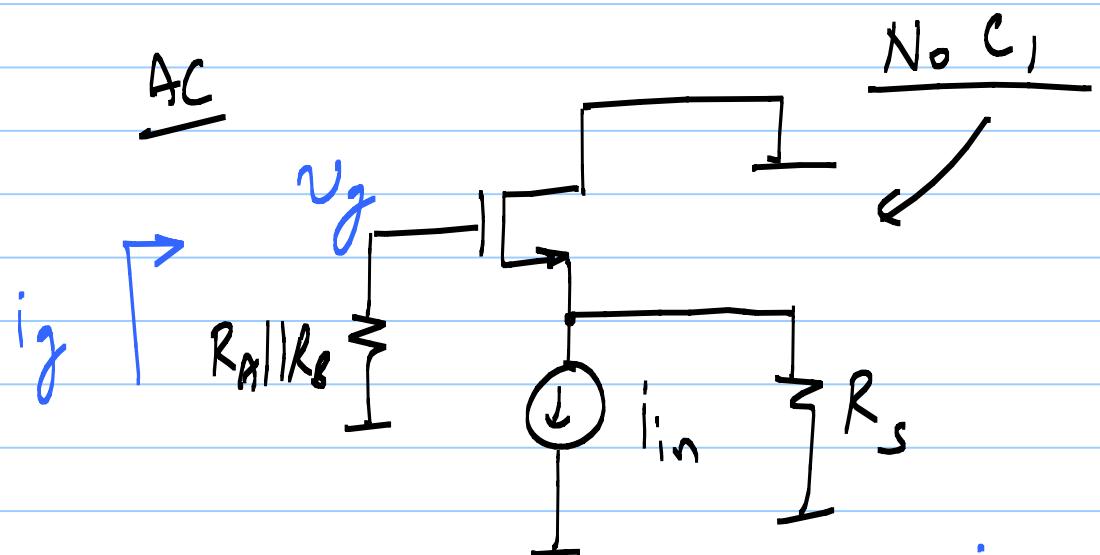


$v_g = 0$ if $i_g = 0$) C_1 is
Unfortunately AC $i_g \neq 0$) necessary


$$\frac{i_{\text{out}}}{i_{\text{in}}} = | \quad \text{independent of } g_m$$

$$Z_{\text{out}} = R_s + r_{\text{ds}} + g_m R_s r_{\text{ds}} \approx g_m R_s r_{\text{ds}}$$

(Very high)

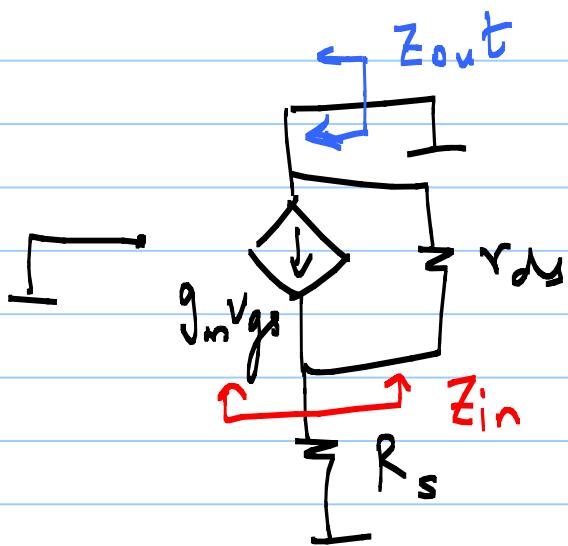

$$Z_{\text{in}} = ?$$

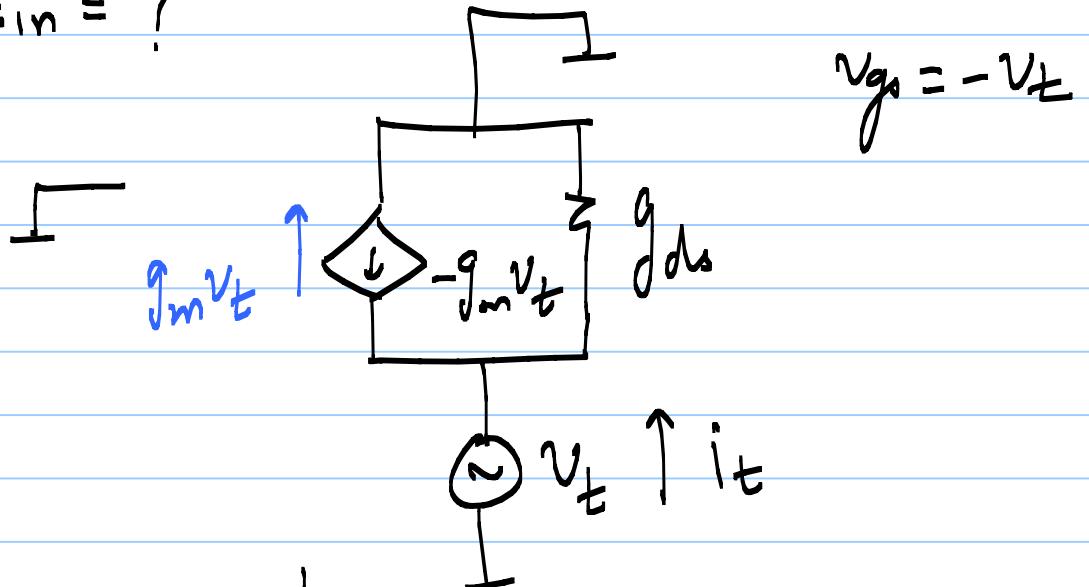

$$Z_{\text{in}} = \frac{1}{g_m + g_{\text{ds}}}$$


large intrinsic gain : $g_m r_{ds} \gg$




$$g_m \gg g_{ds}$$


$$Z_{in} \approx \frac{1}{g_m}$$

large g_m : Z_{in} as small as required
 Z_{out} as large as required.

Why do you need a cccs if gain !?

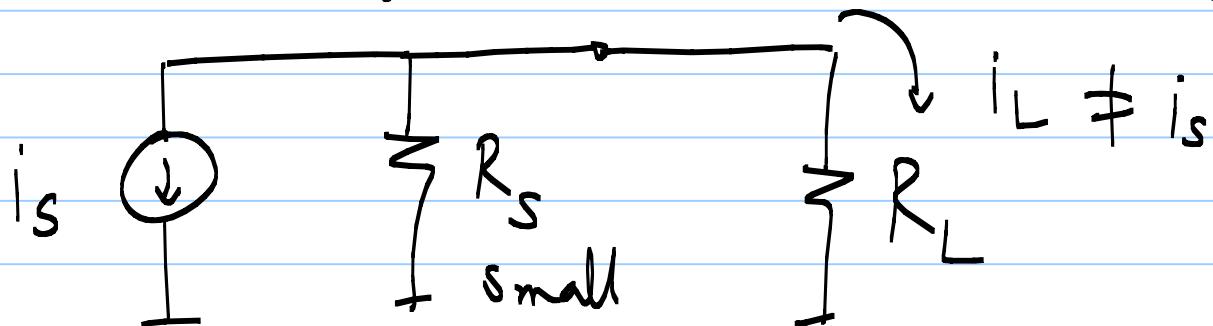



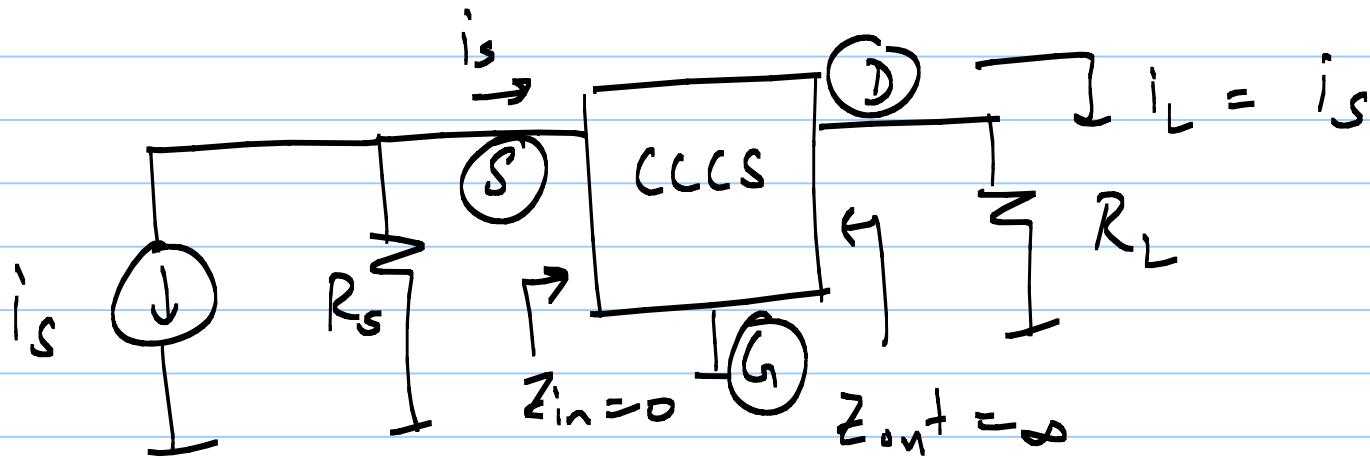
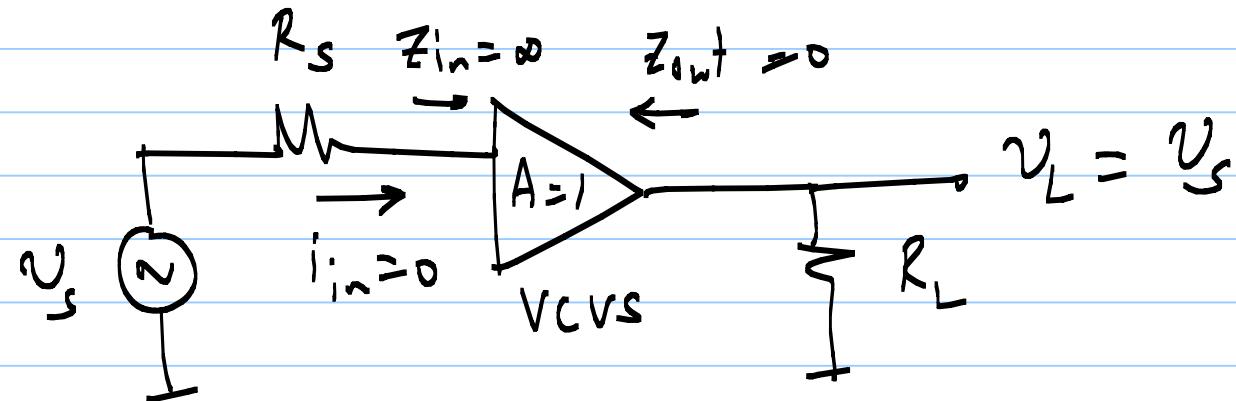
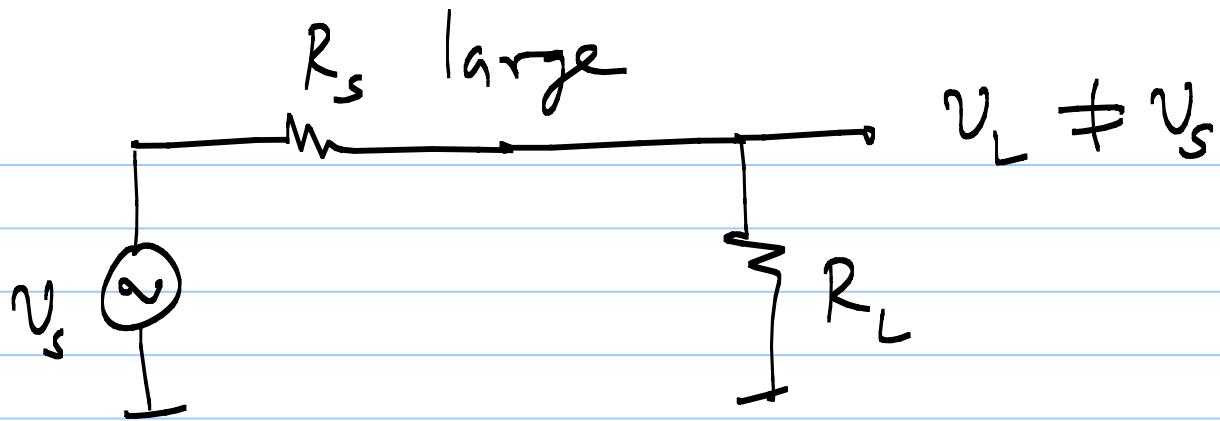



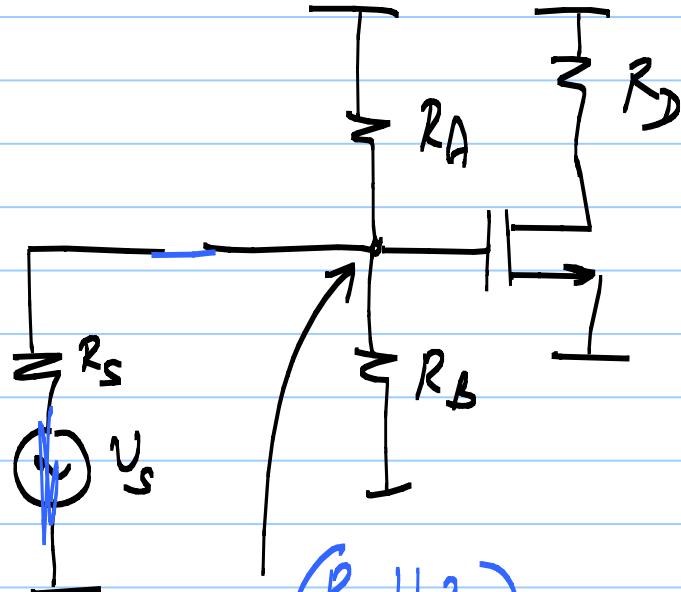




$$\frac{(R_B \parallel R_s)}{R_A + (R_B \parallel R_s)} \cdot V_{DD}$$

11/9/2020

Lecture 23

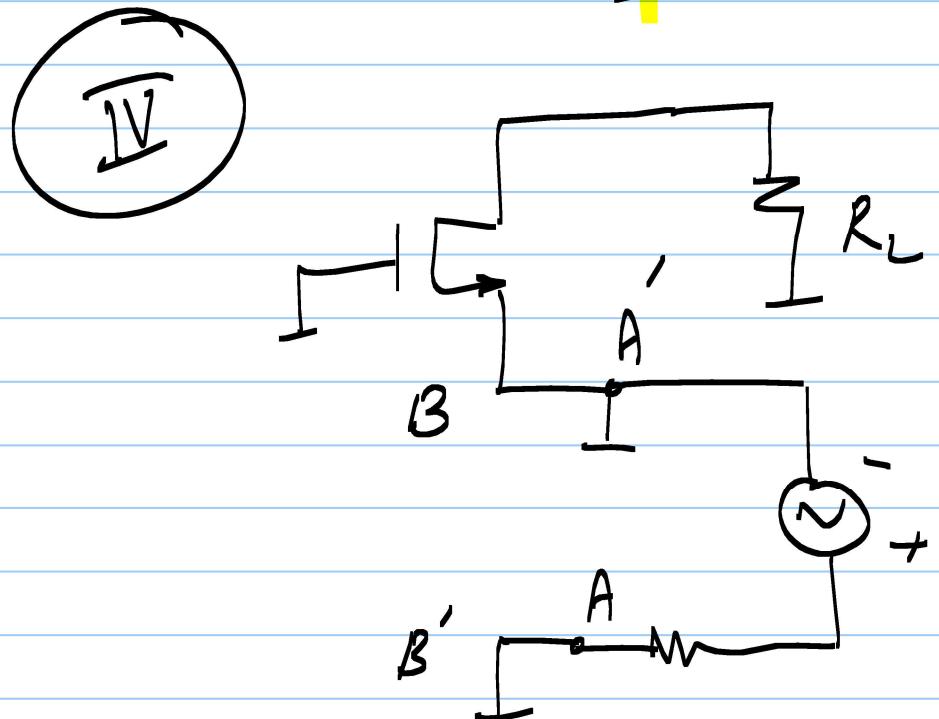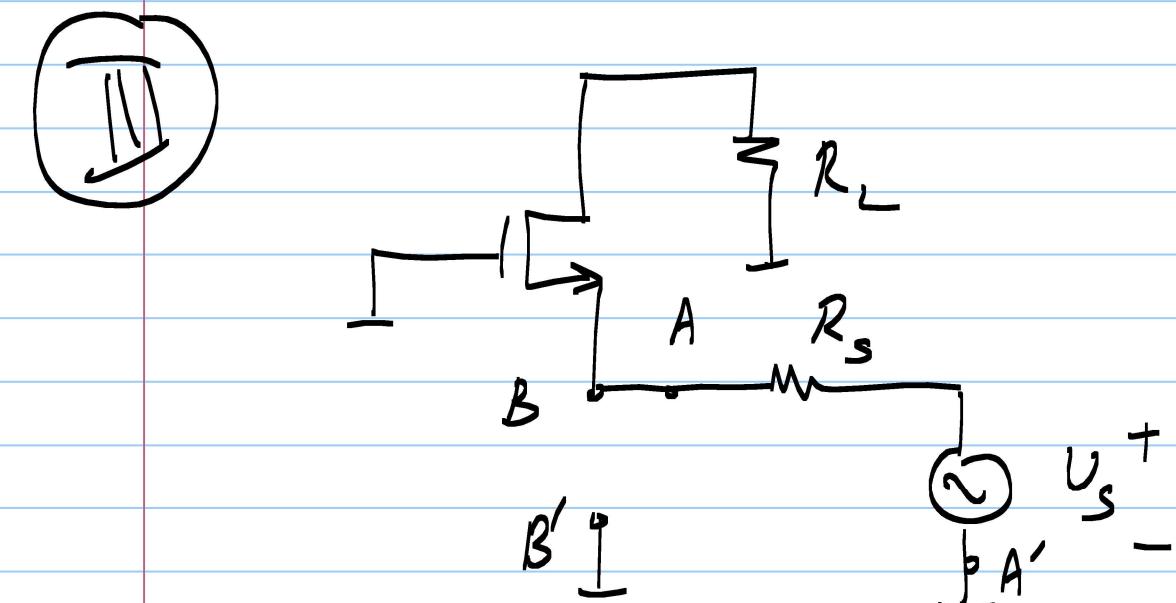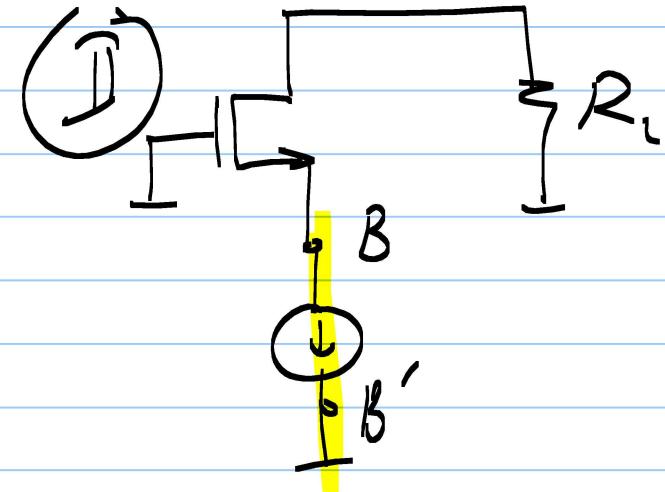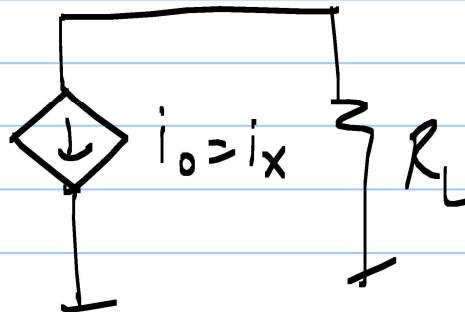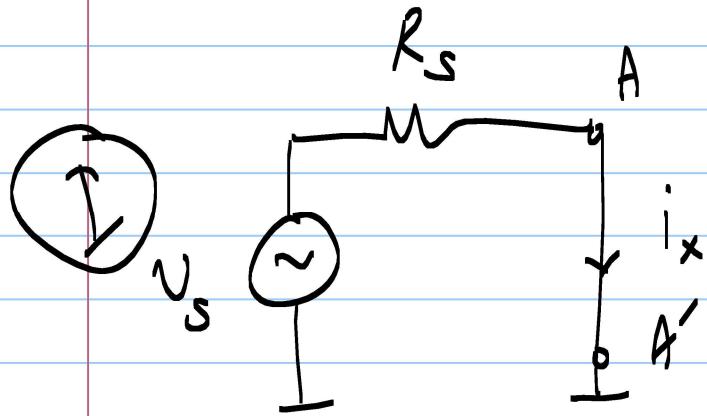

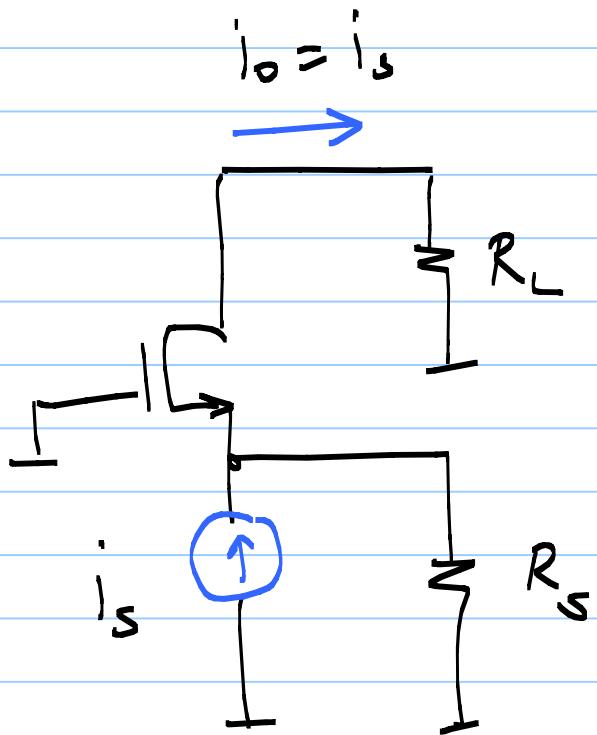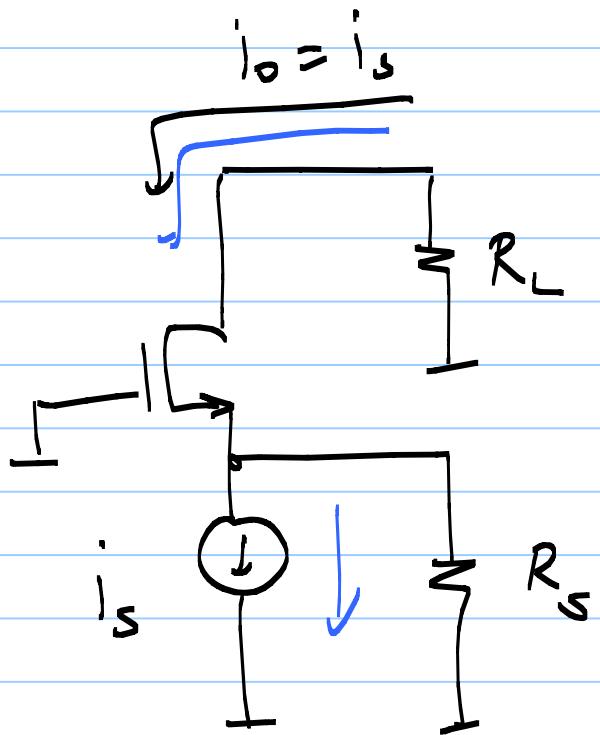


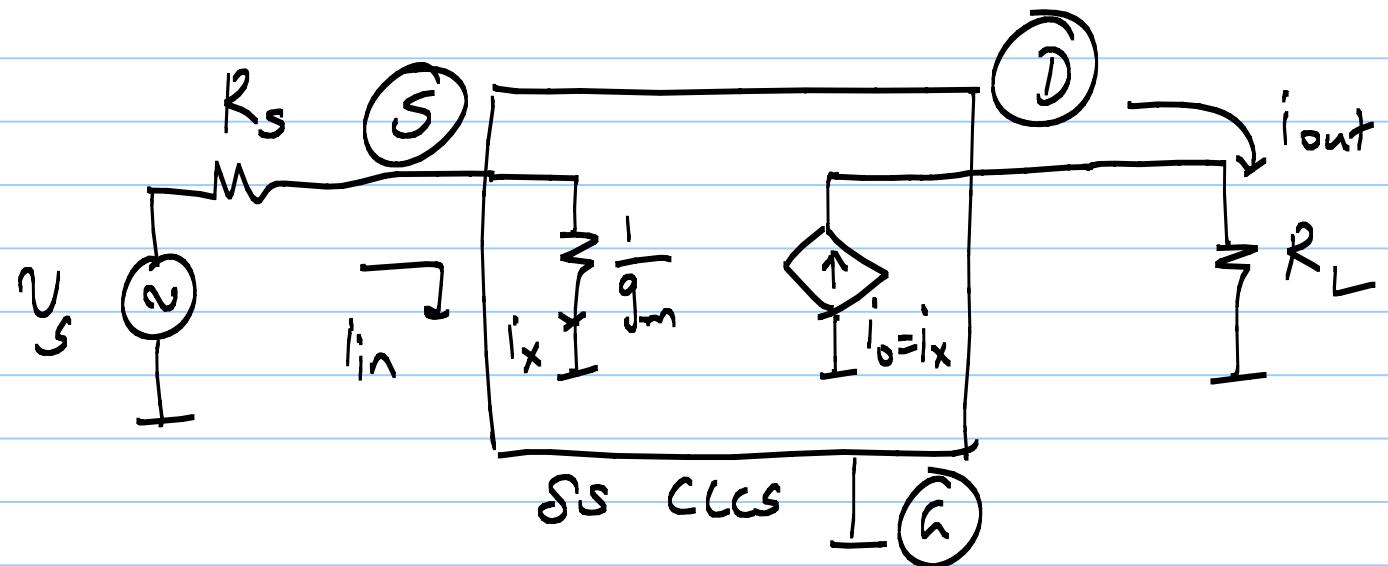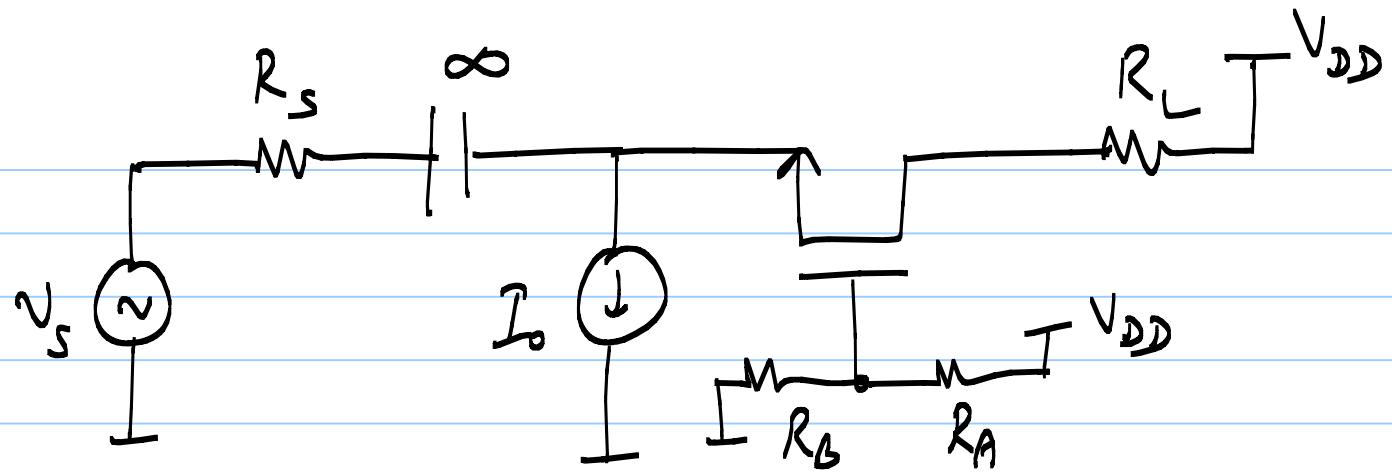

$$i_n \approx \frac{v_s}{R_s} \quad \text{if} \quad g_m \gg \frac{1}{R_s}$$

$$\frac{i_{out}}{v_s} = \frac{1}{R_s} \quad ; \quad \frac{V_{out}}{v_s} = \frac{R_L}{R_s}$$

with r_{ds} :

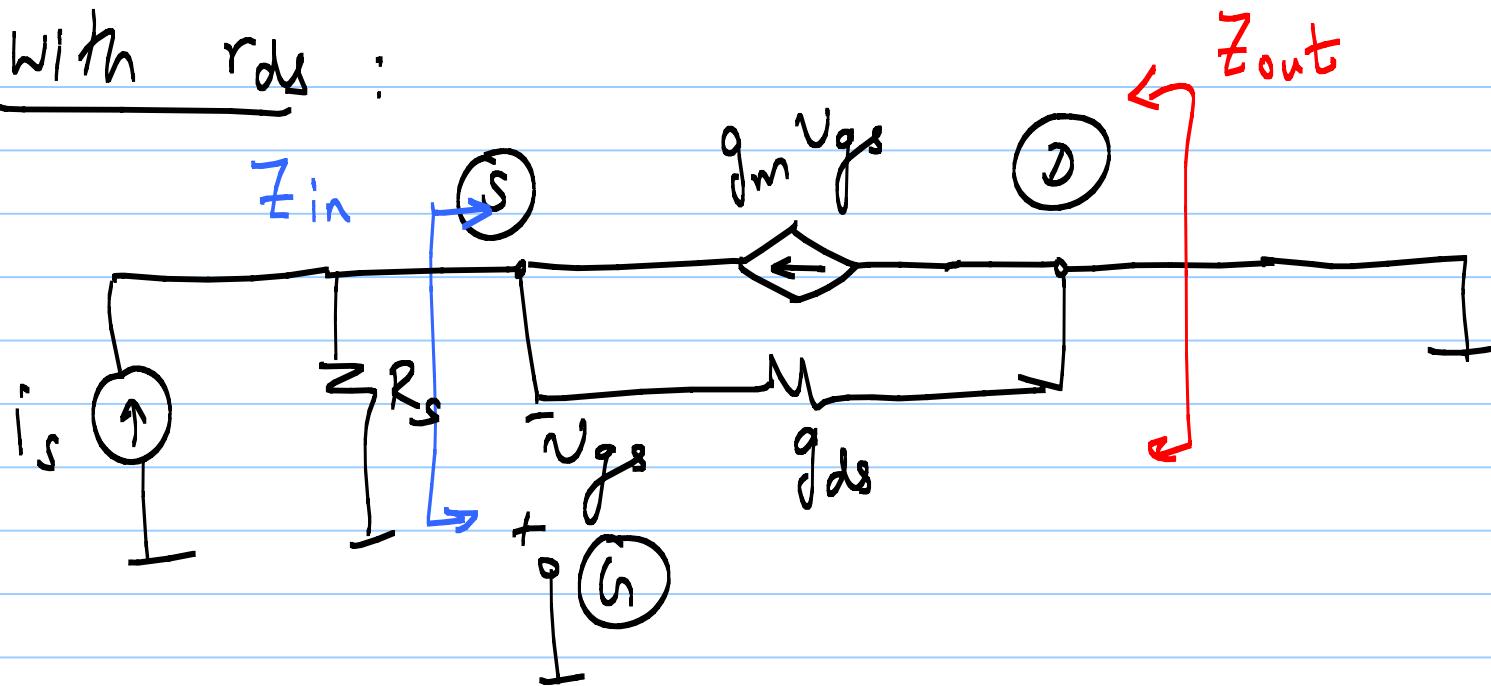

without g_{ds} : $Z_{in} = 1/g_m$


with g_{ds} , without R_L : $Z_{in} = \frac{1}{g_m + g_{ds}}$

with g_{ds} , R_L : HW 8 $Z_{in} = ?$

without g_{ds} : $Z_{out} = \infty$

with g_{ds} :

& R_s

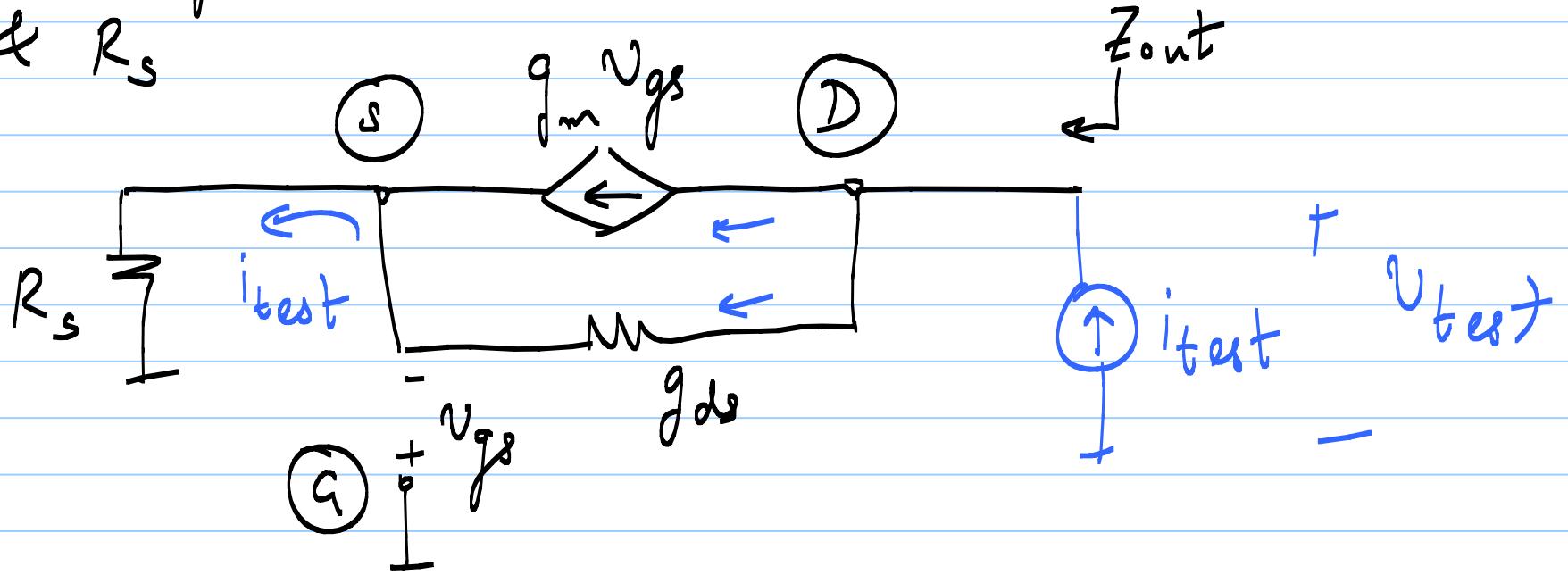


$$Z_{out} = R_s + r_{ds} + g_m r_{ds} R_s$$

$$v_S = R_s \cdot i_{test} = -v_{gs} \dots$$

HW9 : swing limits for CGA

MOSFET incremental CCVS


Trans-impedance amplifier

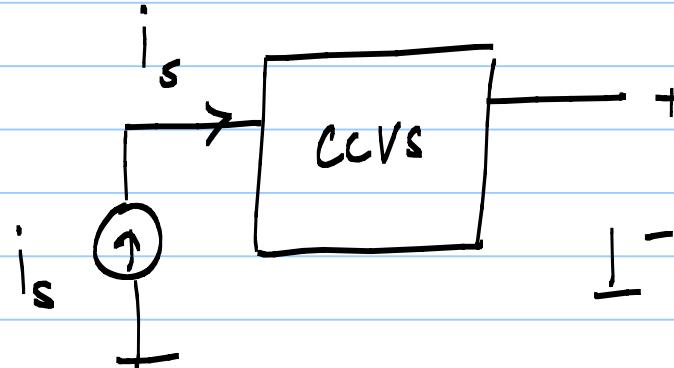



$$v_{out} = R i_s ; \quad Z_{in} = 0$$

$$Z_{out} = 0$$
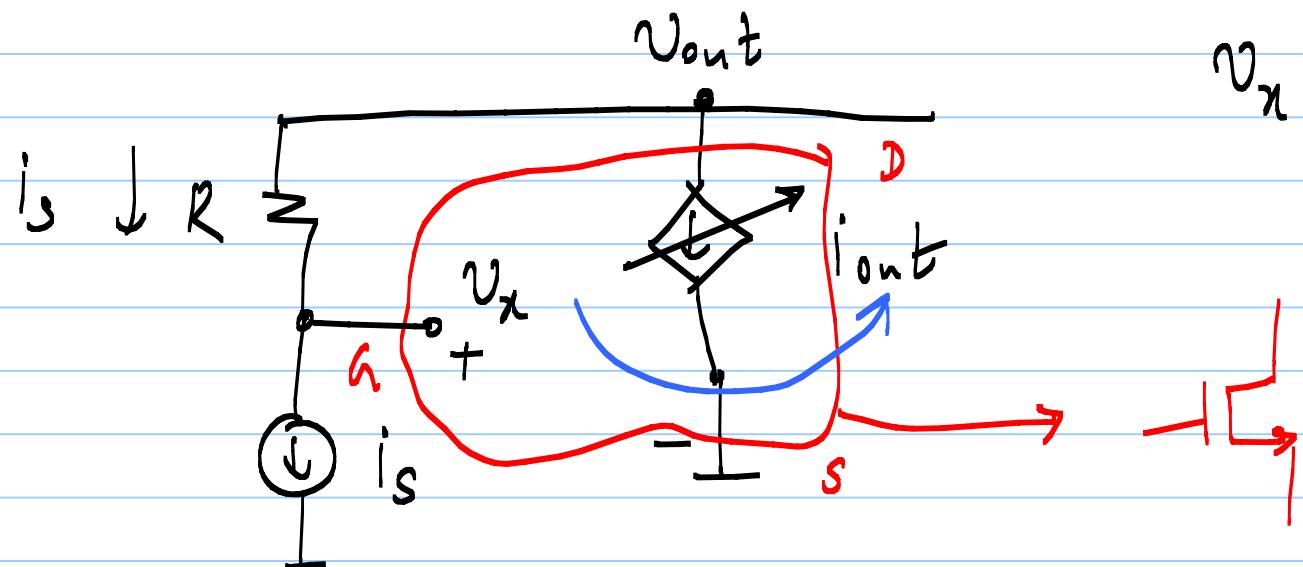
$$v_{out} = R i_s \Rightarrow v_{out} - R i_s = 0 \quad (\text{if } g_m \rightarrow \infty)$$




$$v_x = v_{out} - R i_s$$

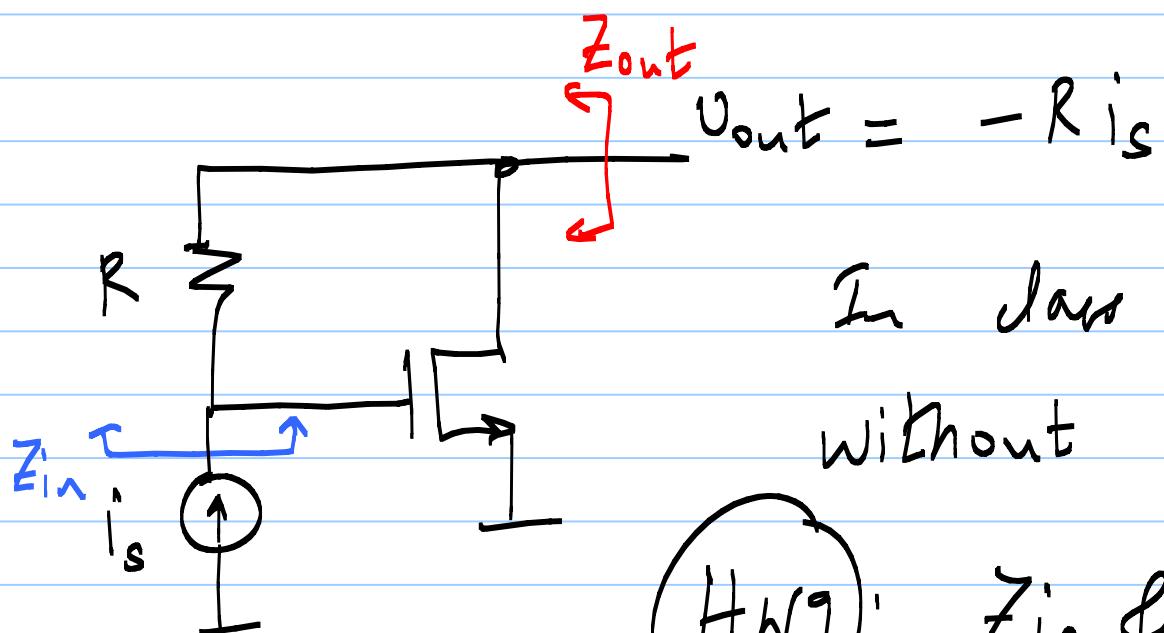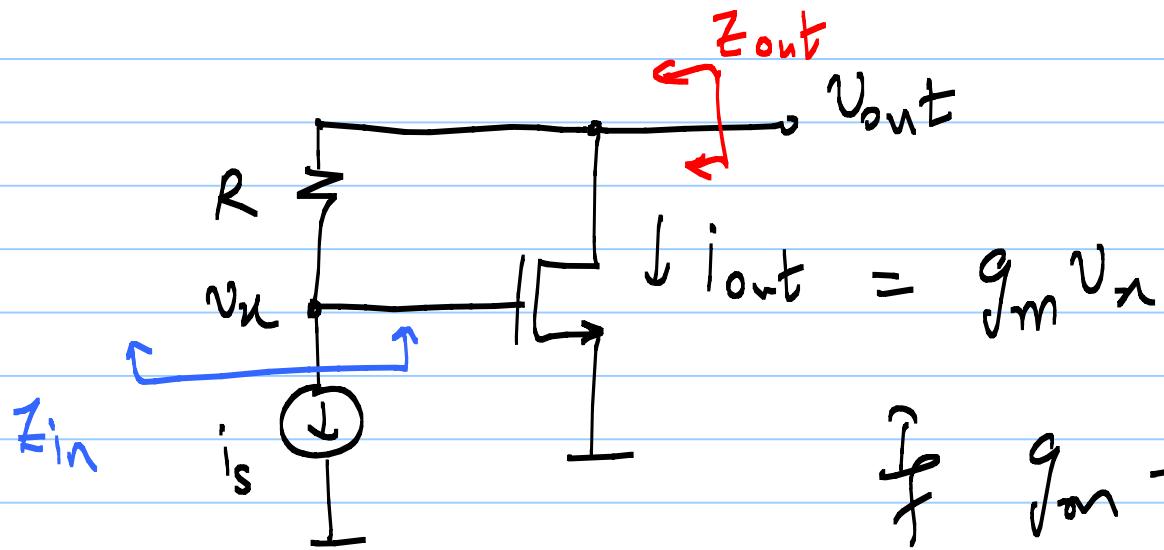



HW9:

with R_s & R_L
 Z_{in} & Z_{out}

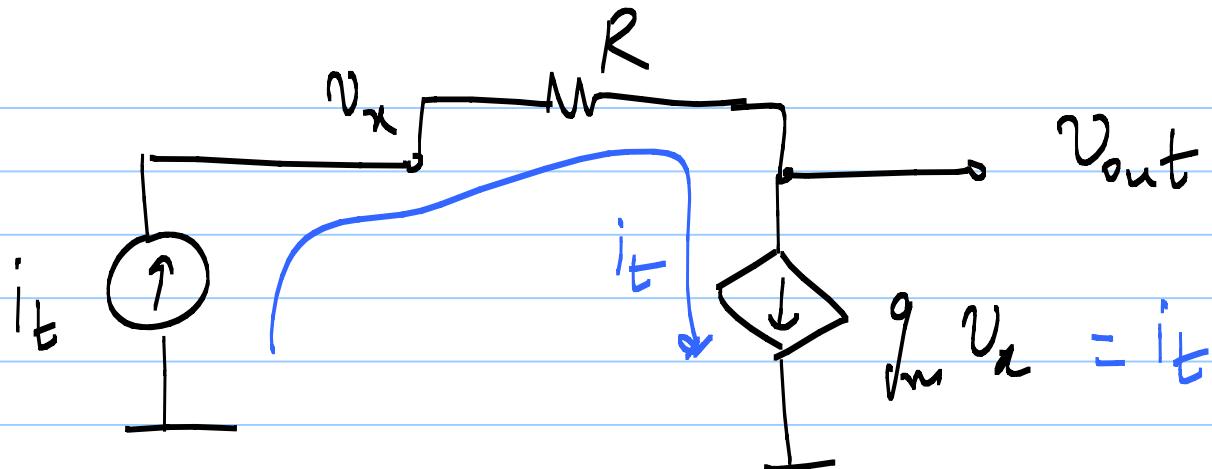
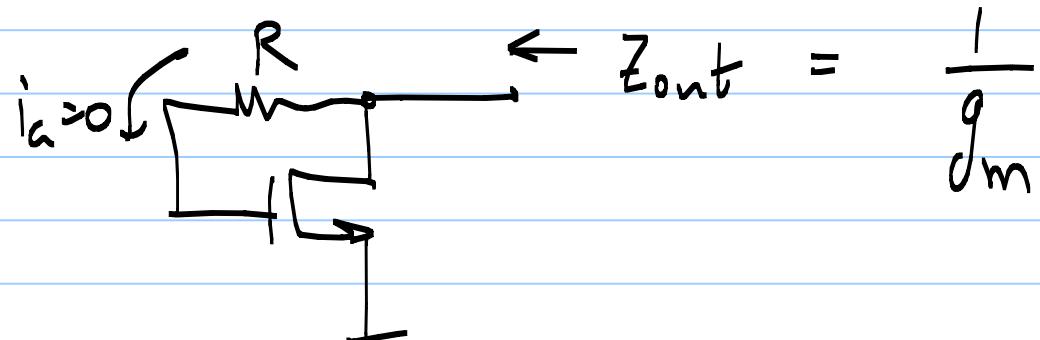
$$i_t = g_m v_x \Rightarrow Z_{in} = \frac{v_x}{i_t} = \frac{1}{g_m}$$



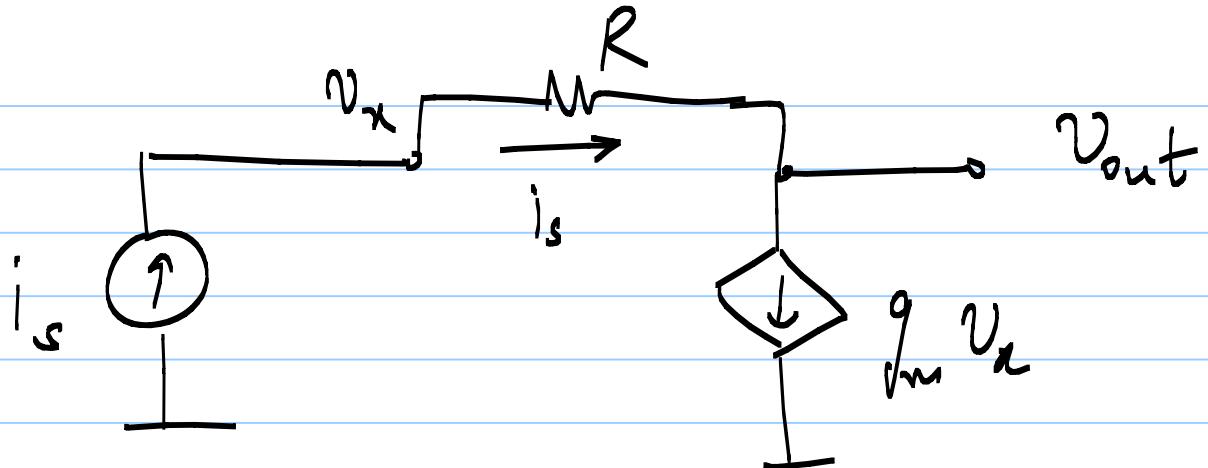

$$i_s = g_m v_x$$



$$v_{out} = v_x - i_s \cdot R$$

$$v_{out} = i_s \left[\frac{1}{g_m} - R \right]$$

$$\frac{v_{out}}{i_s} = \left[\frac{1}{g_m} - R \right] = -R \left[1 - \frac{1}{g_m R} \right]$$

If $g_m R \rightarrow \infty$, $\frac{v_{out}}{i_s} \rightarrow -R$

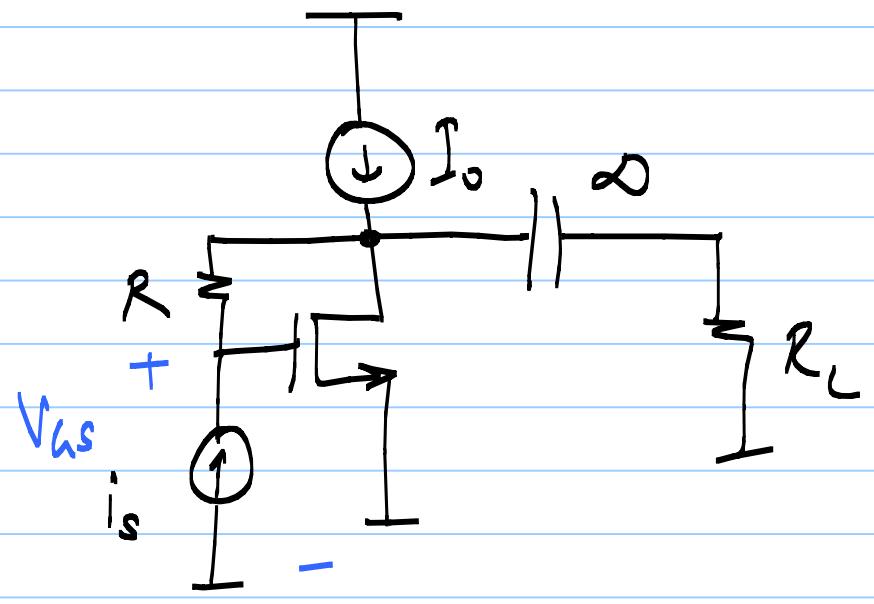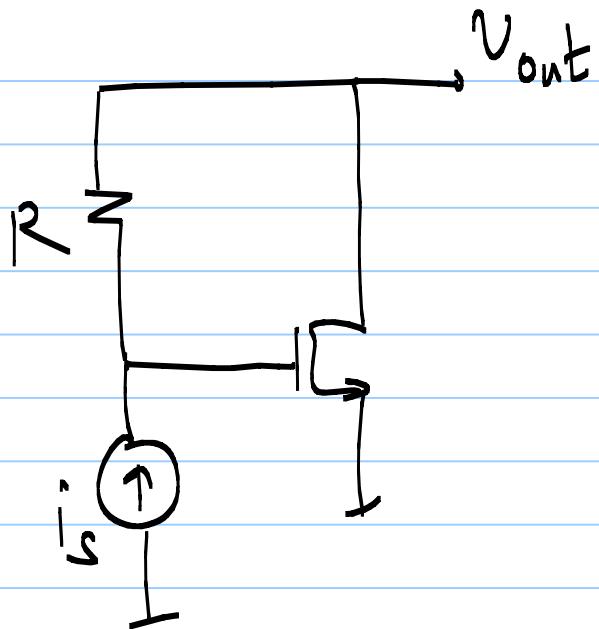
large $g_m \Rightarrow g_m R \gg 1$ (or) $g_m \gg \frac{1}{R}$




with biasing

15 | 9 | 20


Lecture 24

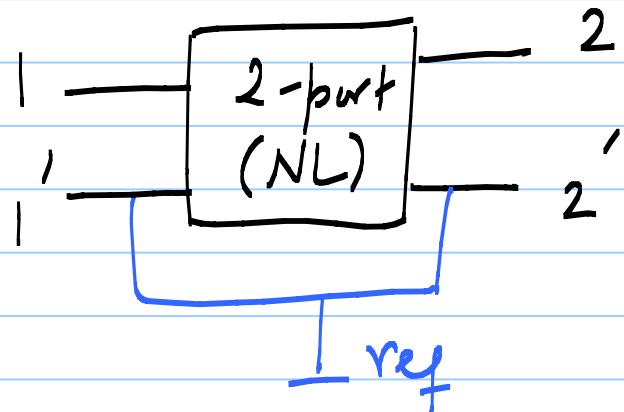


2T 2-port #1

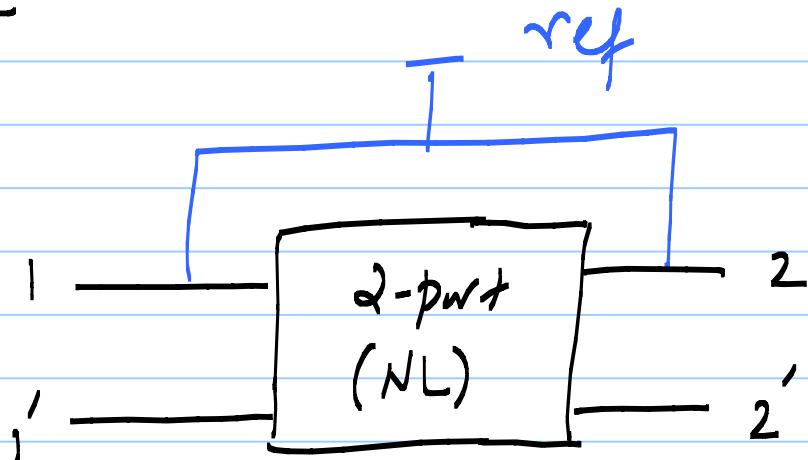


2T 2-port #2

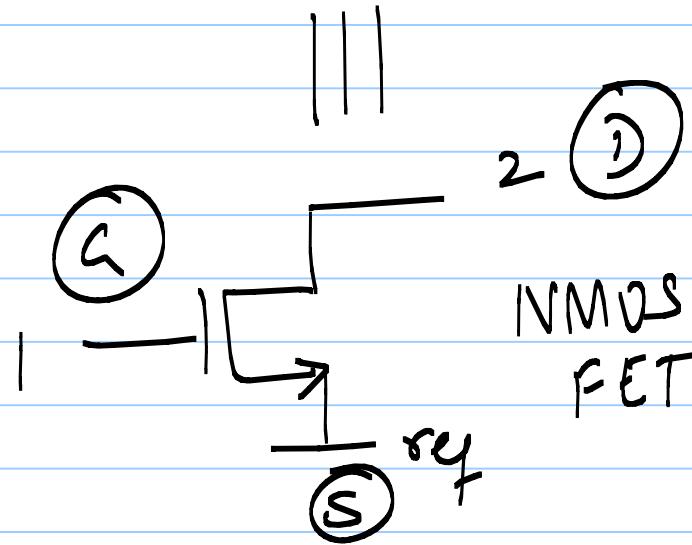



NMOS
FET


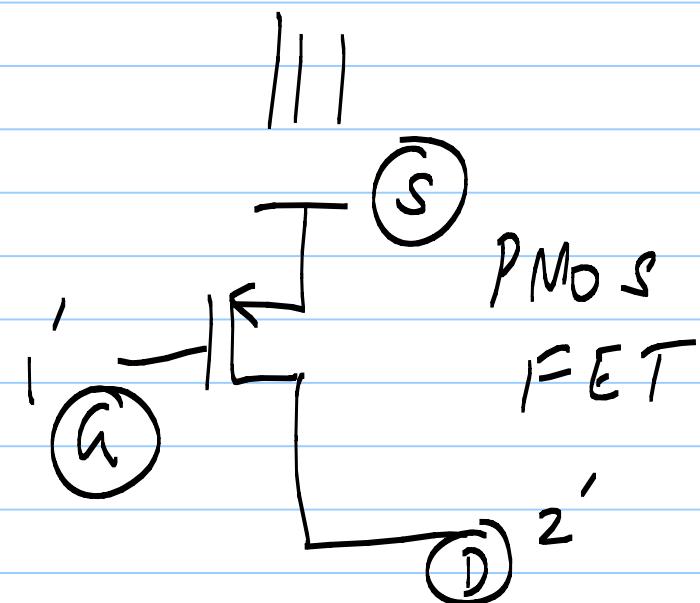


PMOS
FET

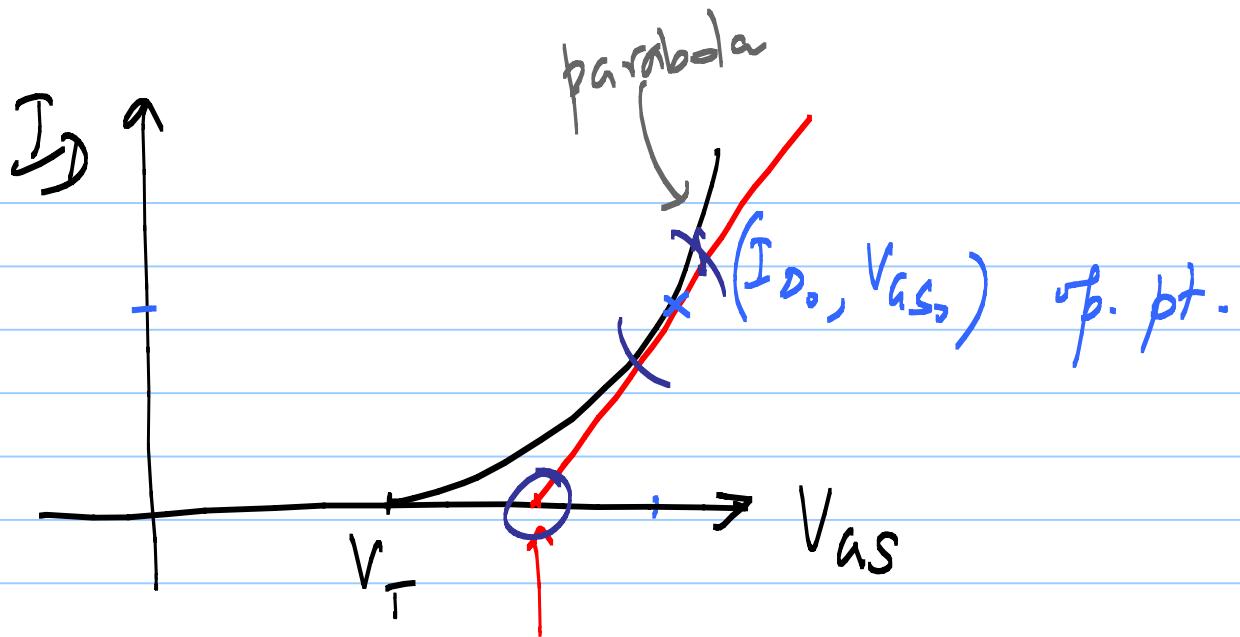

$I_D = 0$ point assuming linear approx.

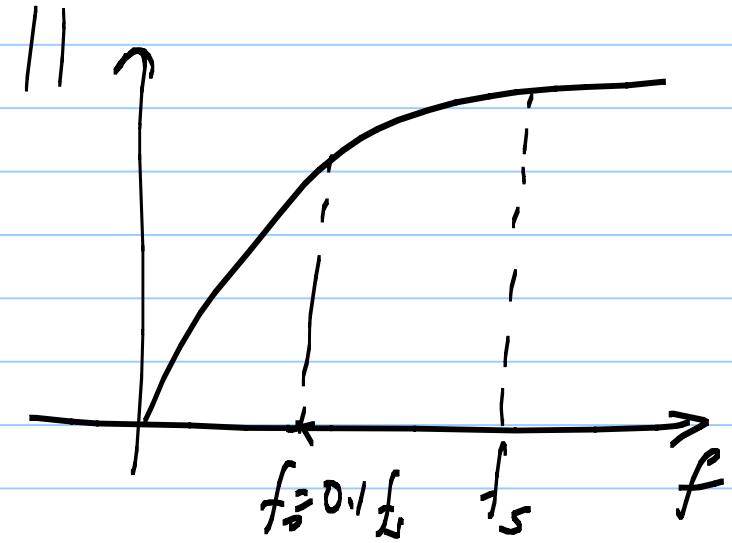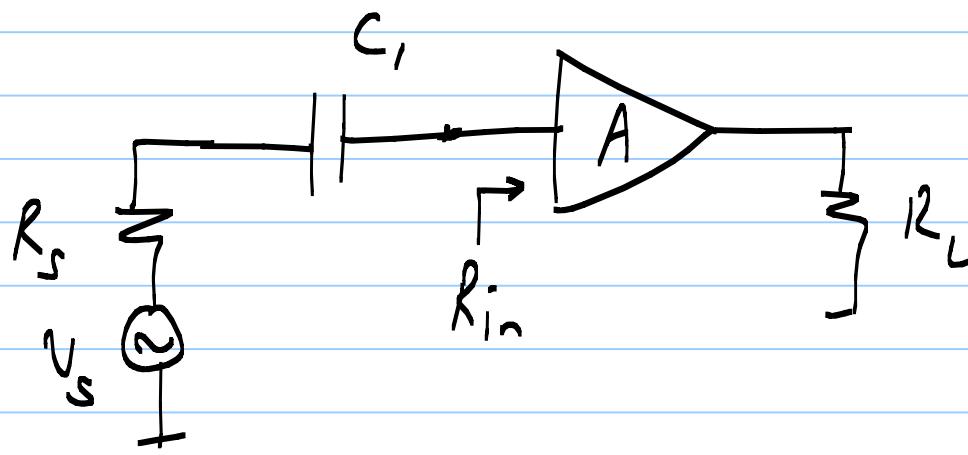

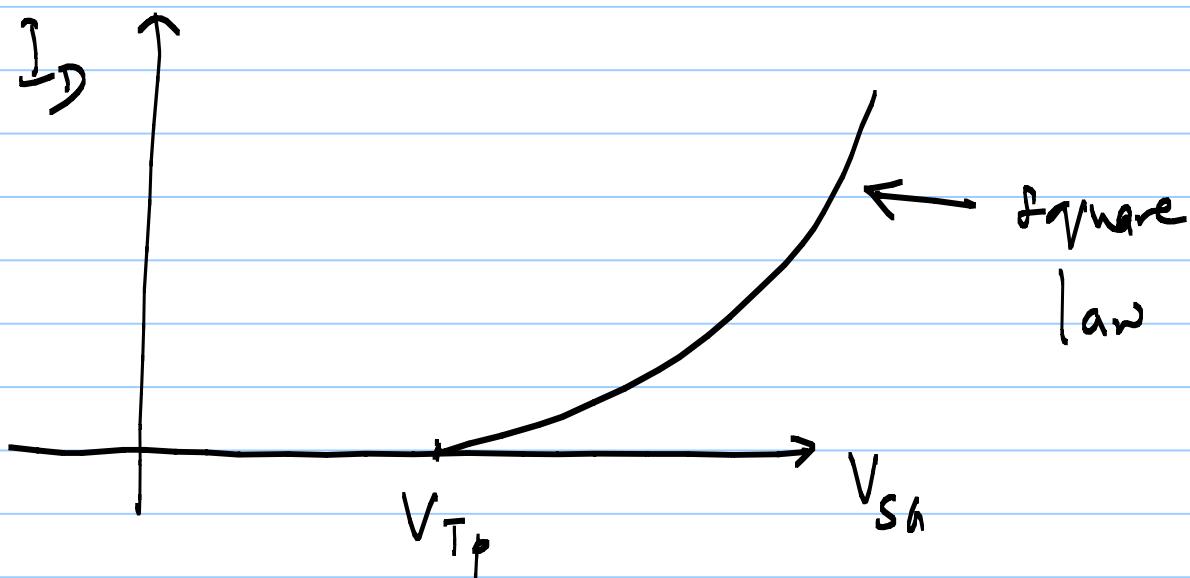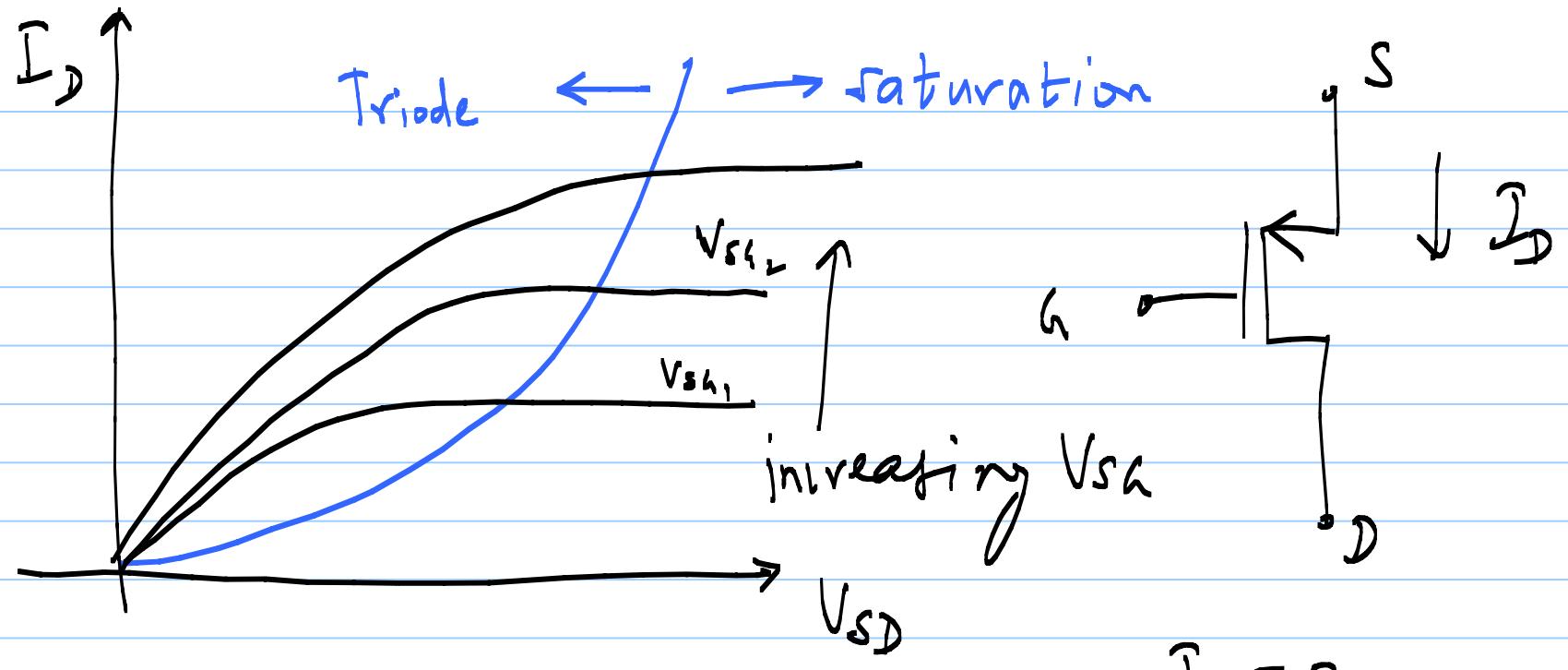

$$I_D = 0 \quad \text{if} \quad V_{SD} < V_{TP} \quad (\text{OFF})$$

$$= \frac{1}{2} \mu_p C_o \left(\frac{W}{L} \right) \left[V_{SD} - V_{TP} \right]^2 \quad \begin{matrix} (\text{SAT}) \\ \text{if } V_{SD} > V_{TP} \\ \text{and} \end{matrix}$$

$$\cdot (1 + \lambda_p V_{SD}) \quad V_{SD} \geq V_{SD} - V_{TP}$$

$$\text{i.e. } V_D \leq V_A + V_{TP}$$

$$= \mu_p C_o \left(\frac{W}{L} \right) \left[(V_{SD} - V_{TP}) V_{SD} - \frac{V_{SD}^2}{2} \right] \quad (\text{TR MODE})$$

$$\text{if } V_{SD} > V_{TP} \quad \text{and} \quad V_D > V_A + V_{TP}$$

Small-signal


$$y_{11} = 0 ; \quad y_{12} = 0$$

$$y_{21} = g_m = M_p C_x \left(\frac{w}{l} \right) (V_{SG} - V_{TP})$$

HW 10

2 other expressions for g_m

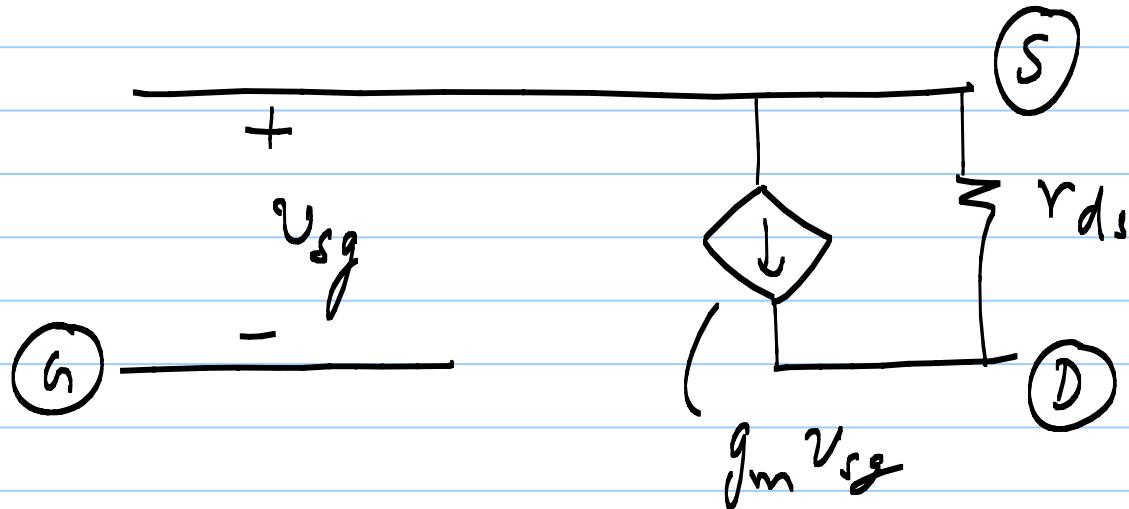
$$y_{22} = g_{ds} = \frac{1}{r_{ds}} = \lambda_p \cdot I_D$$



<p>V_{GS}</p> <p>NMOS</p> <ul style="list-style-type: none"> * DC I_D flows into D * For sat., $V_D >> V_s$ $V_D \geq V_G - V_{Tn}$ * $V_{GS} \geq V_{Tn}$ for $I_D > 0$ * $V_{Tn} > 0$ for enhancement mode device 	<p>Exactly same ss model as for NMOS</p> <p>PMOS</p> <ul style="list-style-type: none"> * DC I_D flows out of D * For sat.: $V_D \ll V_s$ $V_D \leq V_G + V_{Tp}$ * $V_{GS} \geq V_{Tp}$ for $I_D > 0$ * $V_{Tp} > 0$ for enhancement mode device
---	--


Common Source Amplifier

NMOS

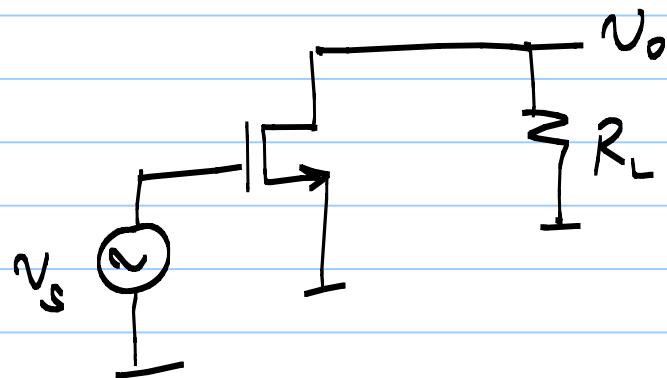


$$\frac{v_o}{v_s} = -g_m R_L$$

PMOS

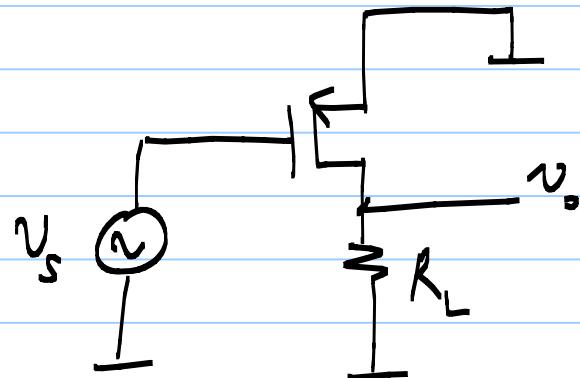


$$\frac{v_o}{v_s} = -g_{m_p} R_L$$

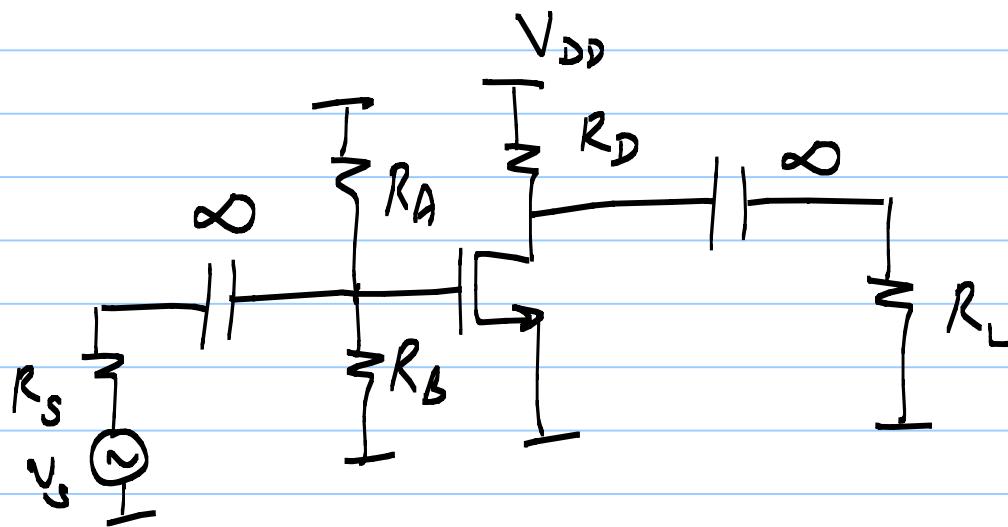

NMOS
CSA
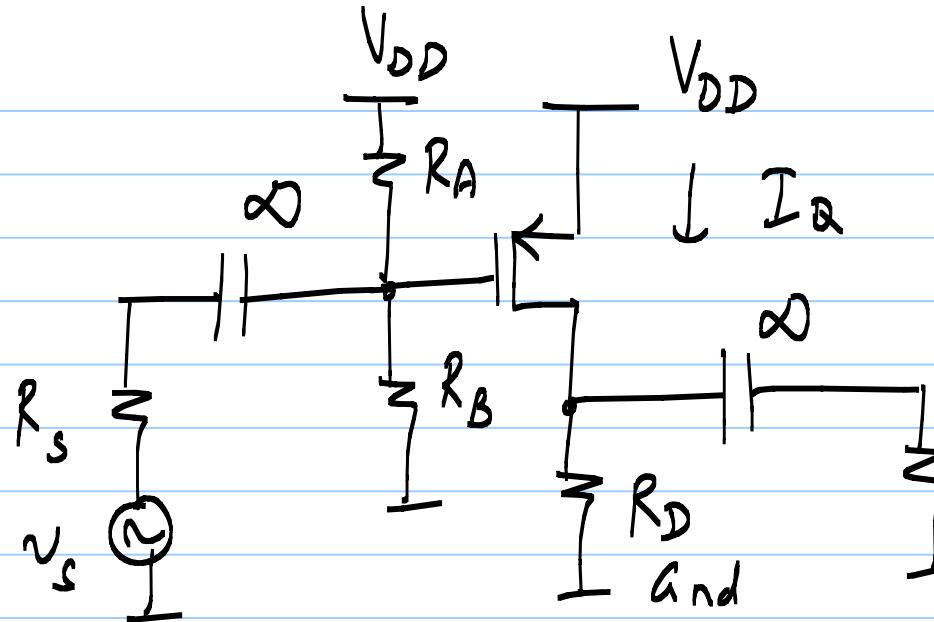
$$V_{G,S} = \frac{R_B}{R_A + R_B} V_{DD}$$



PMOS
Common-Source
amplifier

$$I_Q = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right) \left(V_{SGQ} - V_{T_P} \right)^2$$



$$V_{SGQ} = \frac{R_A}{R_A + R_S} \cdot V_{DD} ; \quad V_{SDQ} = V_{DD} - I_Q \cdot R_D$$

$$V_{S,Q} = V_{DD} ; \quad V_{A,Q} = \frac{R_S}{R_A + R_S} \cdot V_{DD}$$

$$V_{D,Q} = I_Q \cdot R_D$$

16 | 9 | 20

Lecture 25

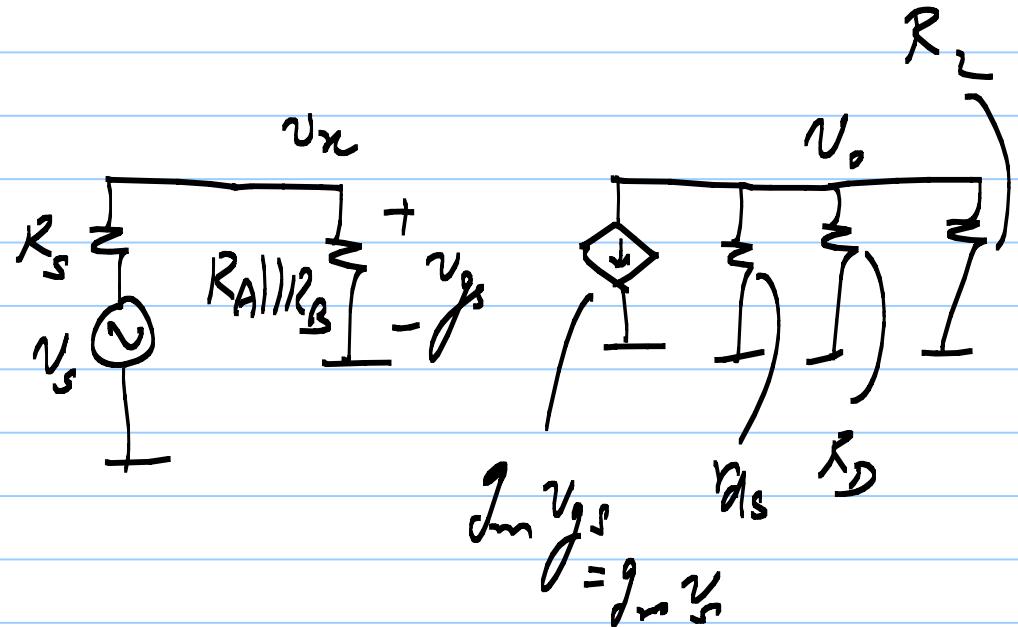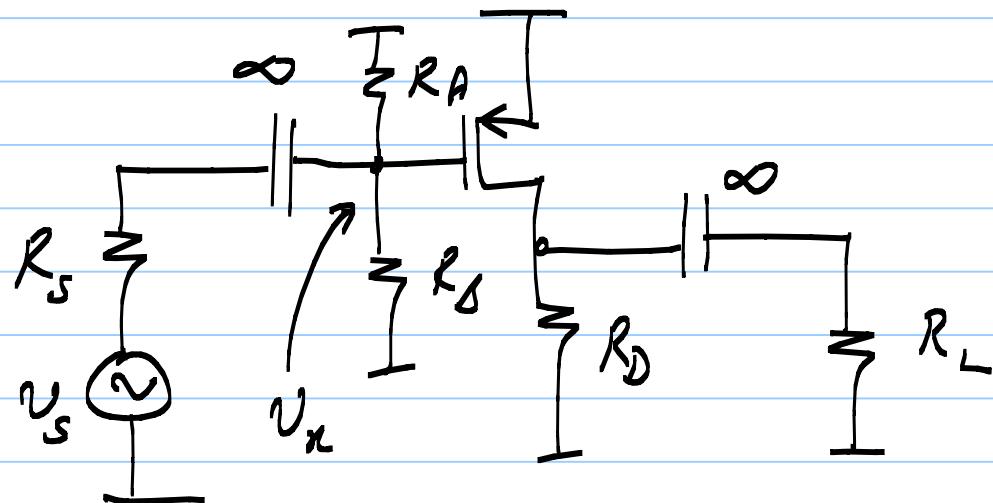

$$v_x = \frac{R_A \parallel R_B}{R_s + R_A \parallel R_B} \cdot v_s$$

choose $R_A \parallel R_B \gg R_s$

$$\Rightarrow v_x \approx v_s$$

$$v_o = -g_m (r_{ds} \parallel R_D \parallel R_L) \cdot v_s$$


HW 11

- Swing Limits :
- 1) Triode limit : $V_D > V_a + V_{TP}$
 - 2) Cutoff limit : $I_D = 0$



Bias Stabilization



(I)

Drawn to have f.b.

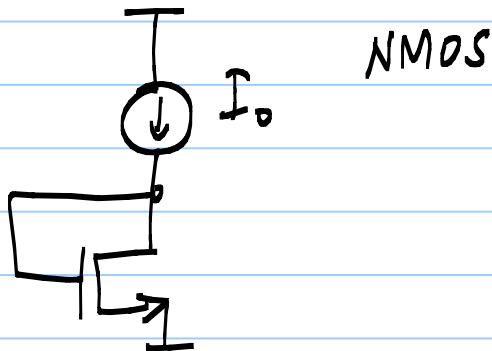


NMOS

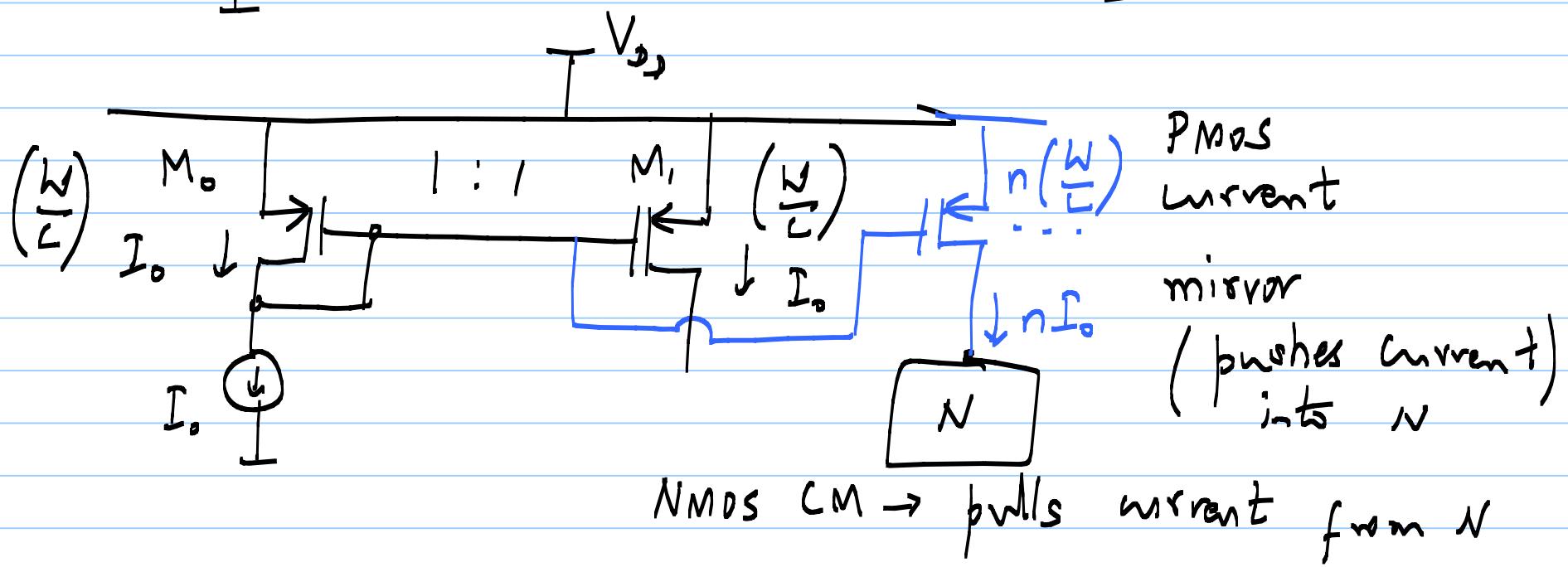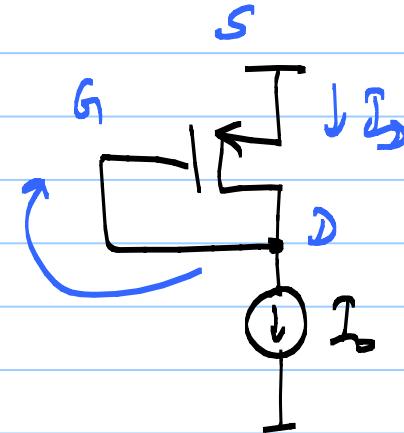

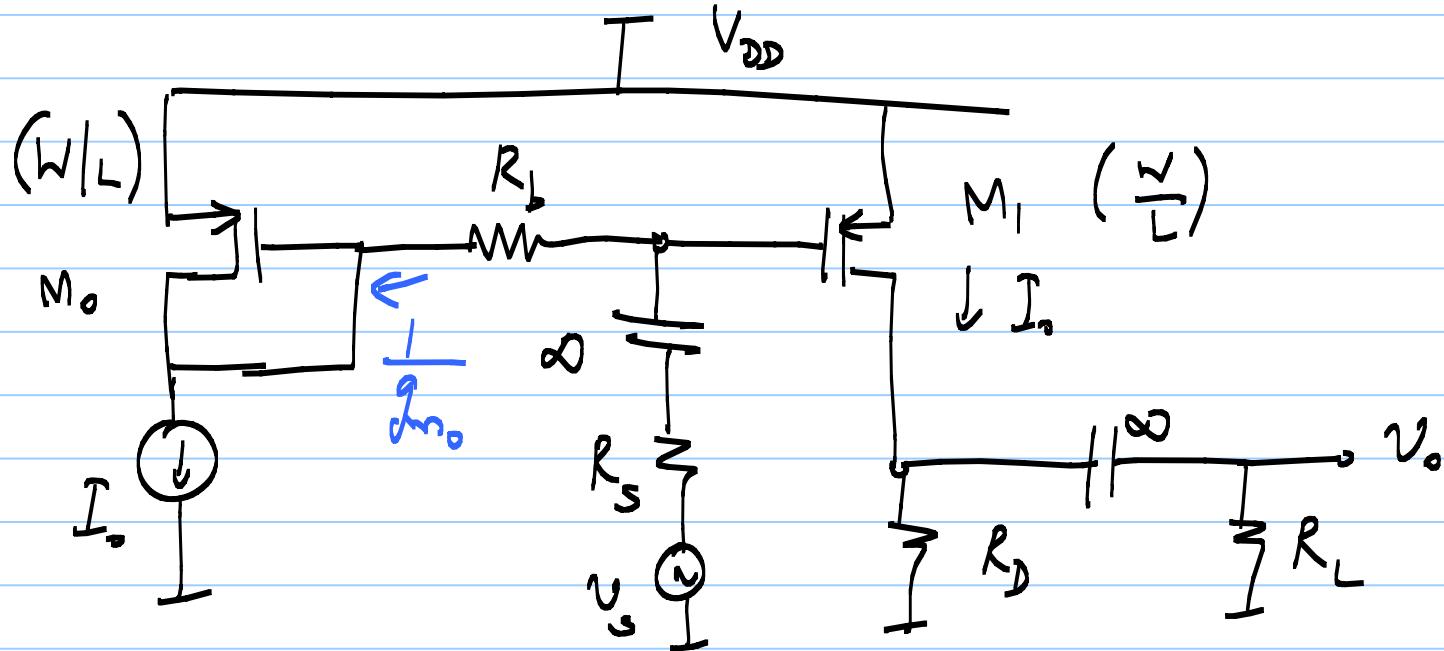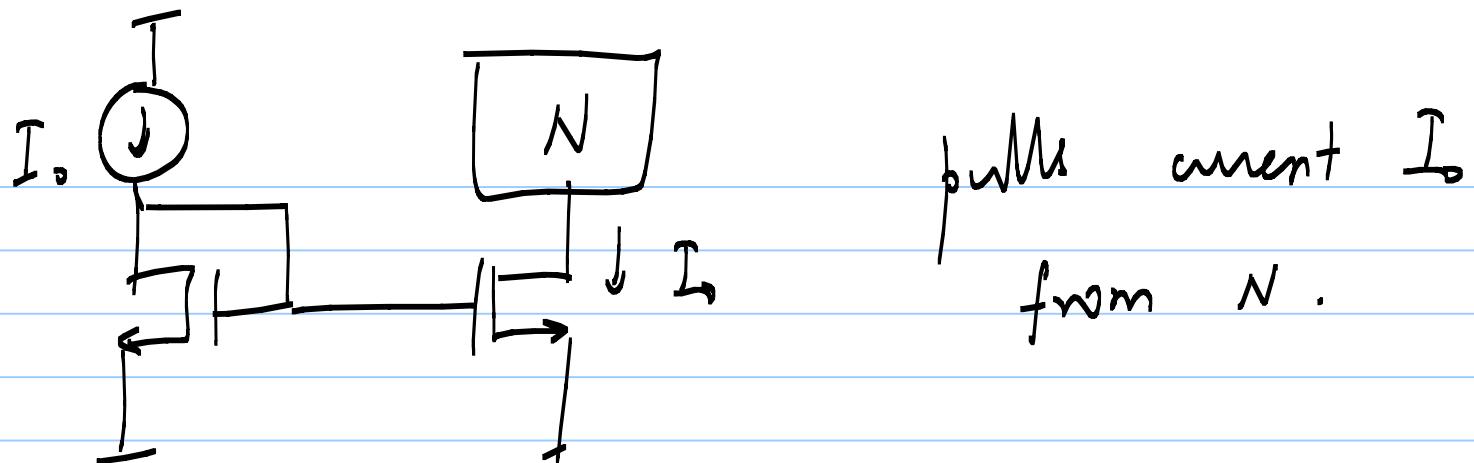


\hat{I}

NMOS

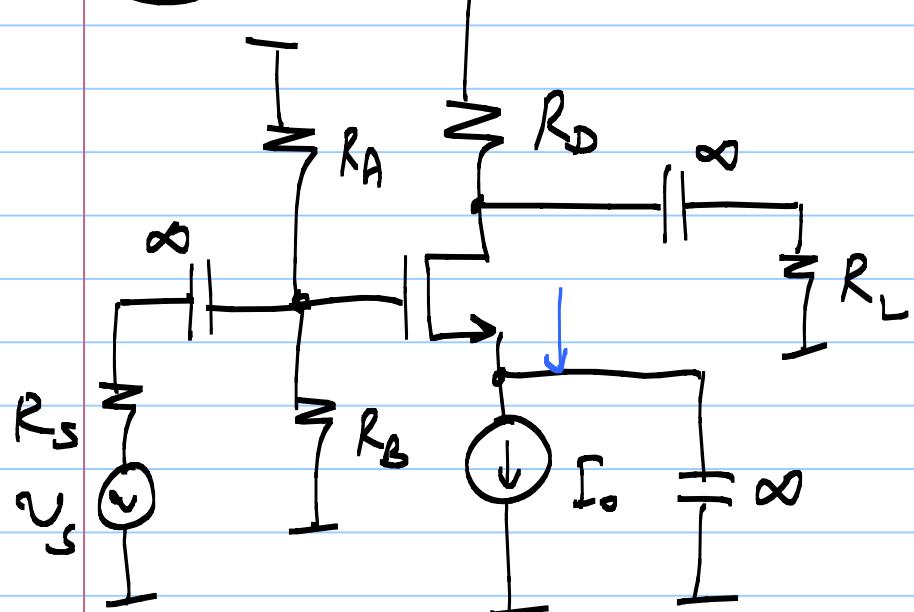

P MOS

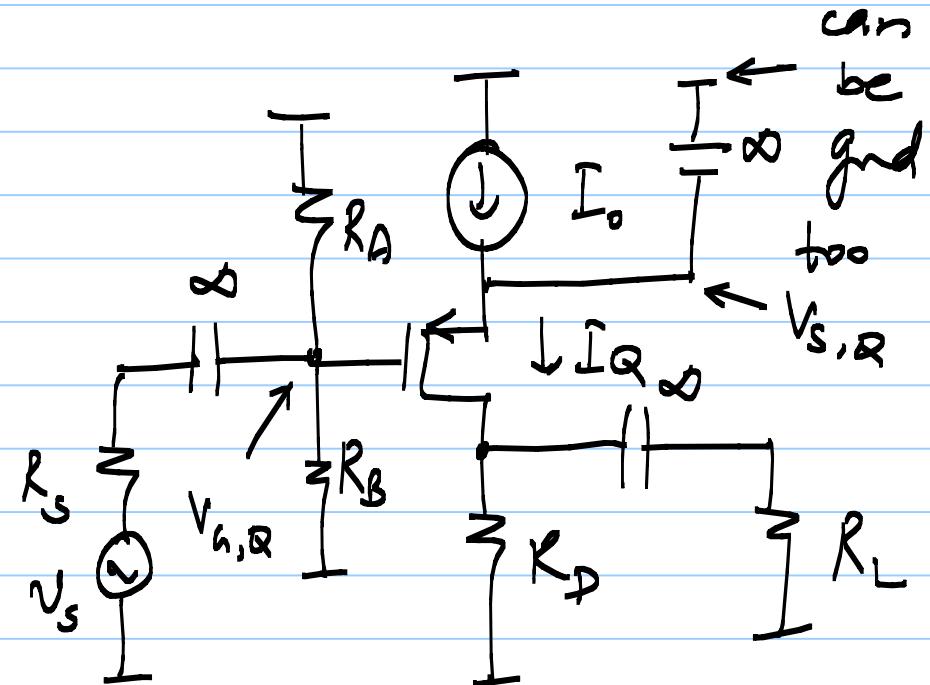

$$I_Q = I_0$$

$$V_{G,Q} = \frac{R_B}{R_A + R_B} \cdot V_{DD}$$

$$V_{D,Q} = I_0 \cdot R_D$$

$$V_{S,Q} = V_{G,Q} + V_{SG,Q}$$

$$V_{SG,Q} = V_T + \sqrt{\frac{2I_0}{\mu_p C_{ox} \left(\frac{W}{L}\right)}}$$

HW12

: SS analysis, swing limits


Case II & IV \rightarrow HW13

SS Controlled Sources



(SS eq. circuits are

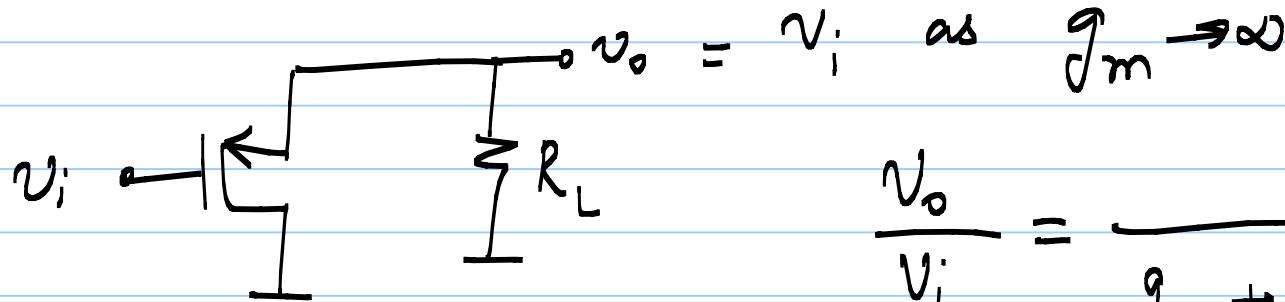i) VCVS gain = 1 i.e. $V_o = V_i$ identical)

PMOS Common Drain Amplifier or PMOS source follower



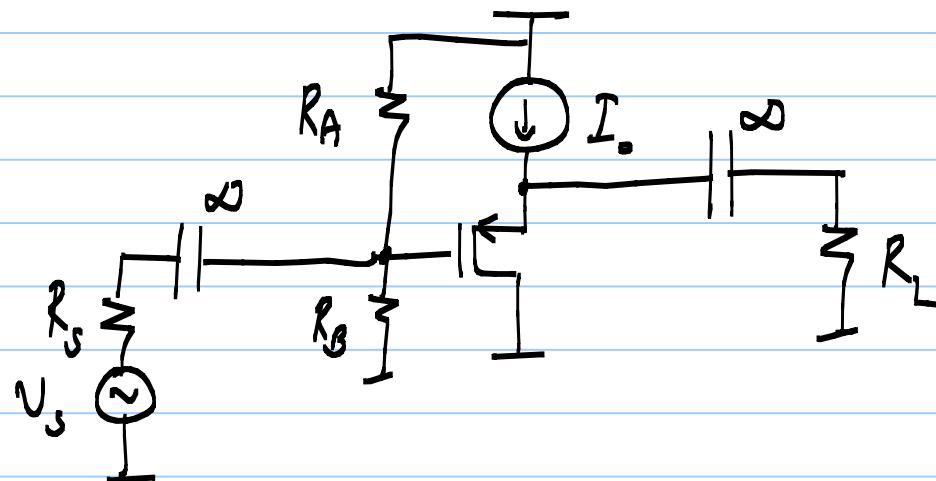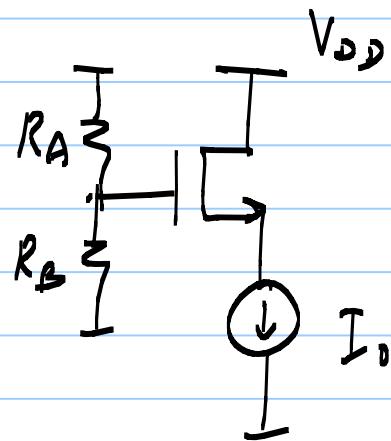
$$\frac{V_o}{V_i} = \frac{g_m}{g_m + g_{ds} + g_L}$$



PMOS
CDA
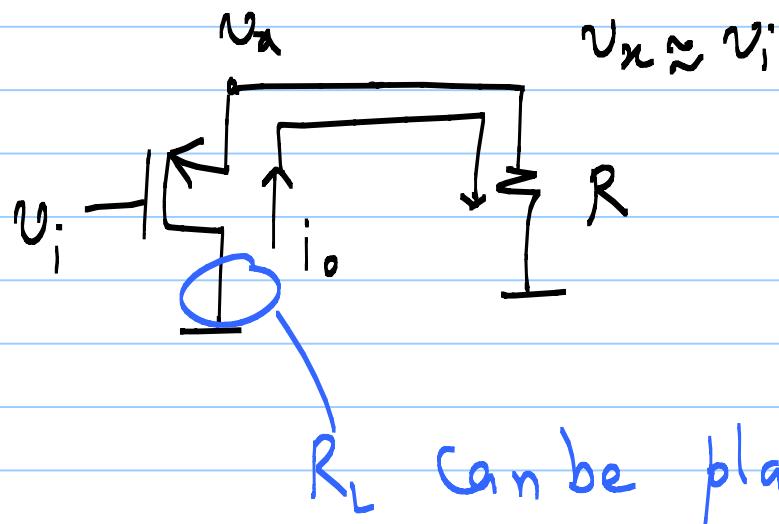
$$2) \underline{V_{CCS}} - TCA \text{ (PMOS)} \quad i_o = \frac{v_i}{R}$$



$$\text{as } g_m \rightarrow \infty, \quad v_x \approx v_i$$


$$i_o = \frac{v_i}{R}$$

17/9/2020


Lecture 2b

PMOS based controlled sources





2) VCCS

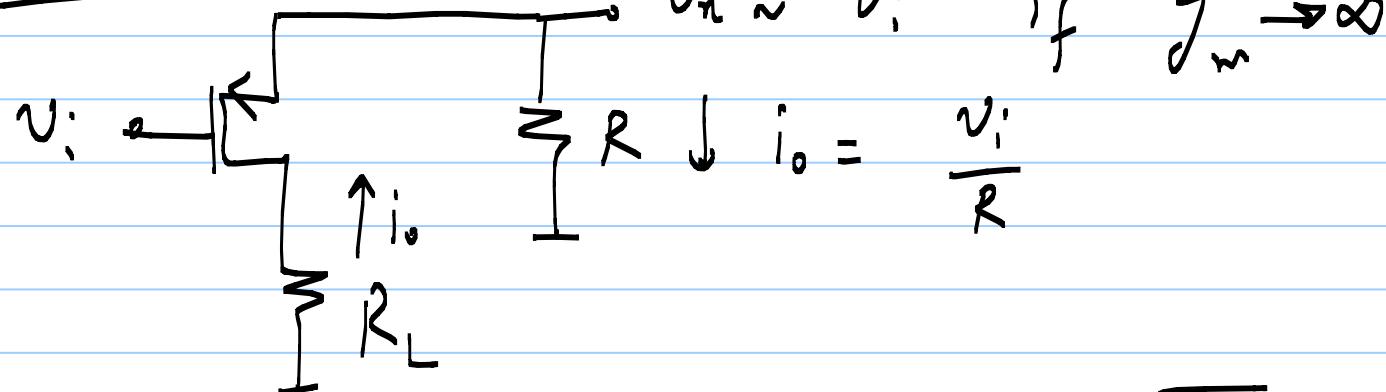

PMOS
Transadmittance
amplifier

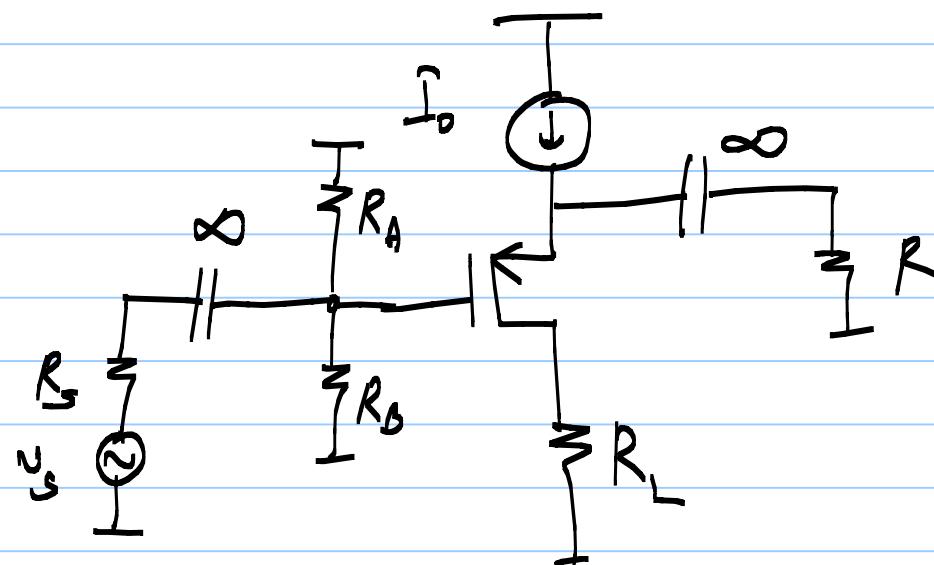

3) CCCS - Common Gate Amplifier

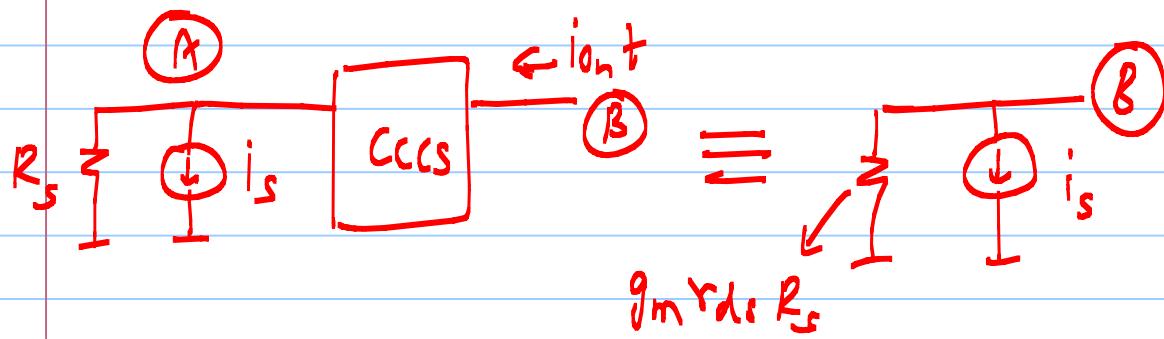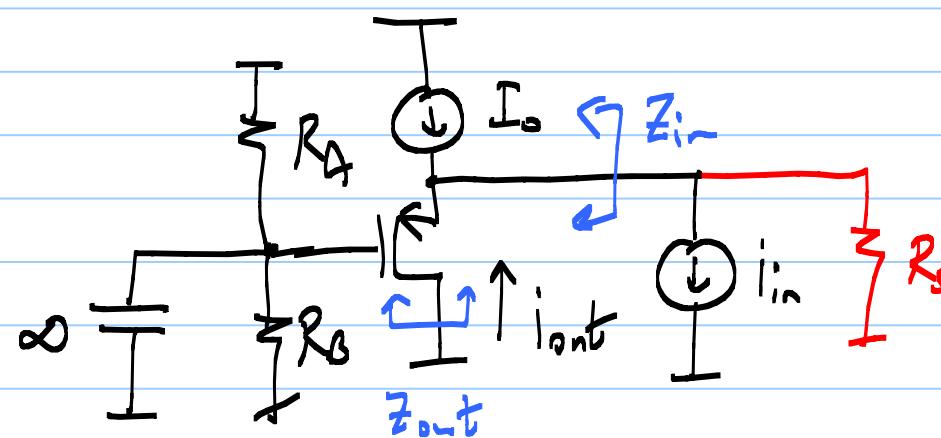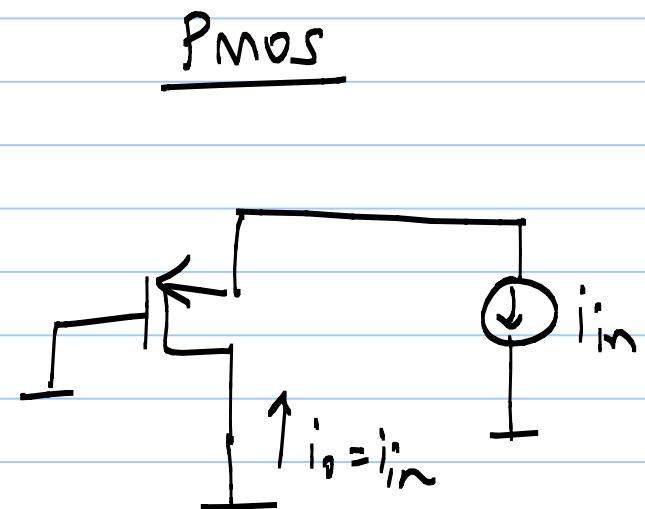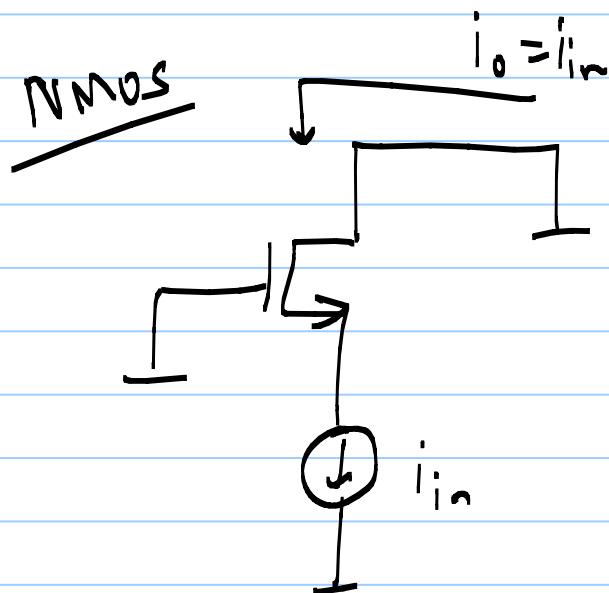


$$Z_{out} = R_s + r_{dst} +$$

$$\approx g_m r_{ds} R_s$$

$$\approx g_m r_{ds} R_g$$

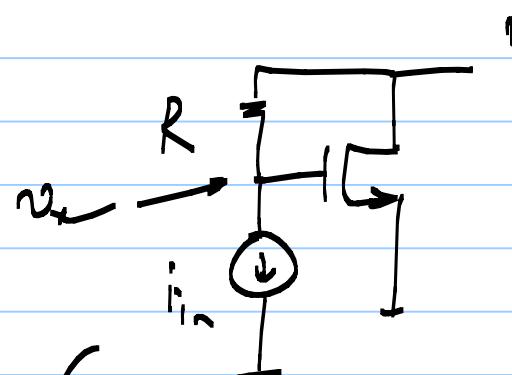
4) CCVS (Trans impedance amplifier) $v_{out} = R \cdot i_{in}$




v_{out}

$$v_n = v_{out} - i_{in} \cdot R$$

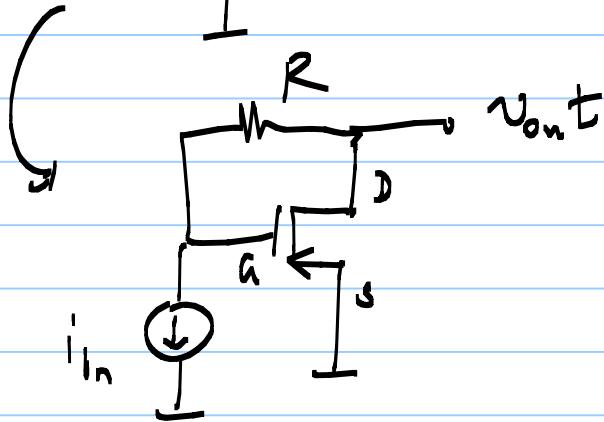at $g_m \rightarrow \infty$, $v_n \rightarrow 0$




v_{out}

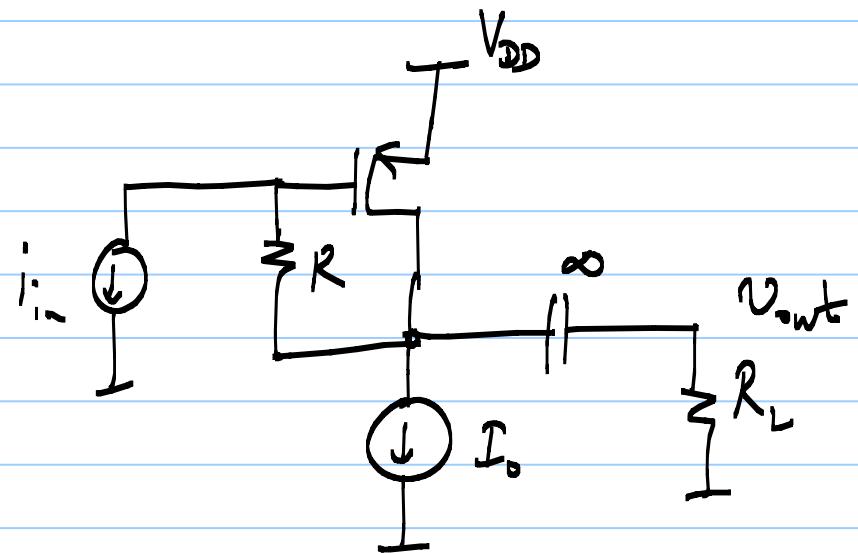

v_{out}


R_L


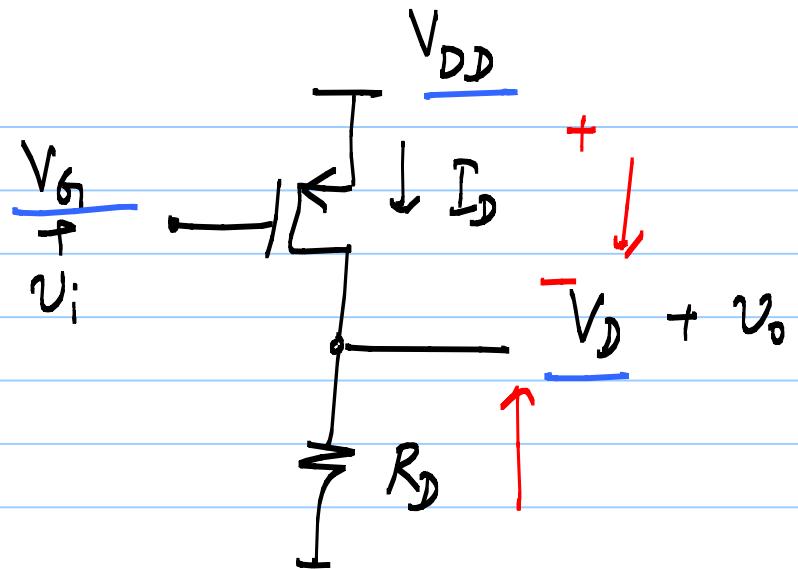




$$\frac{V_o}{V_i} = -g_m R_D$$

$$V_D = I_D R_D$$

$$V_{SD} = V_{DD} - V_D$$

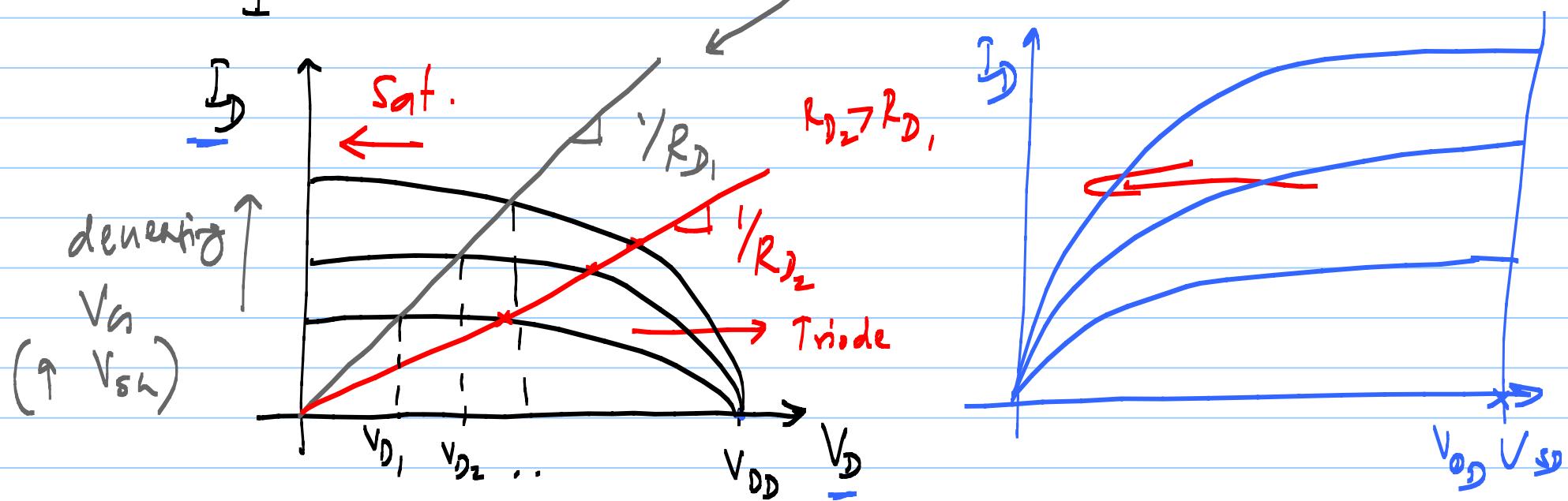


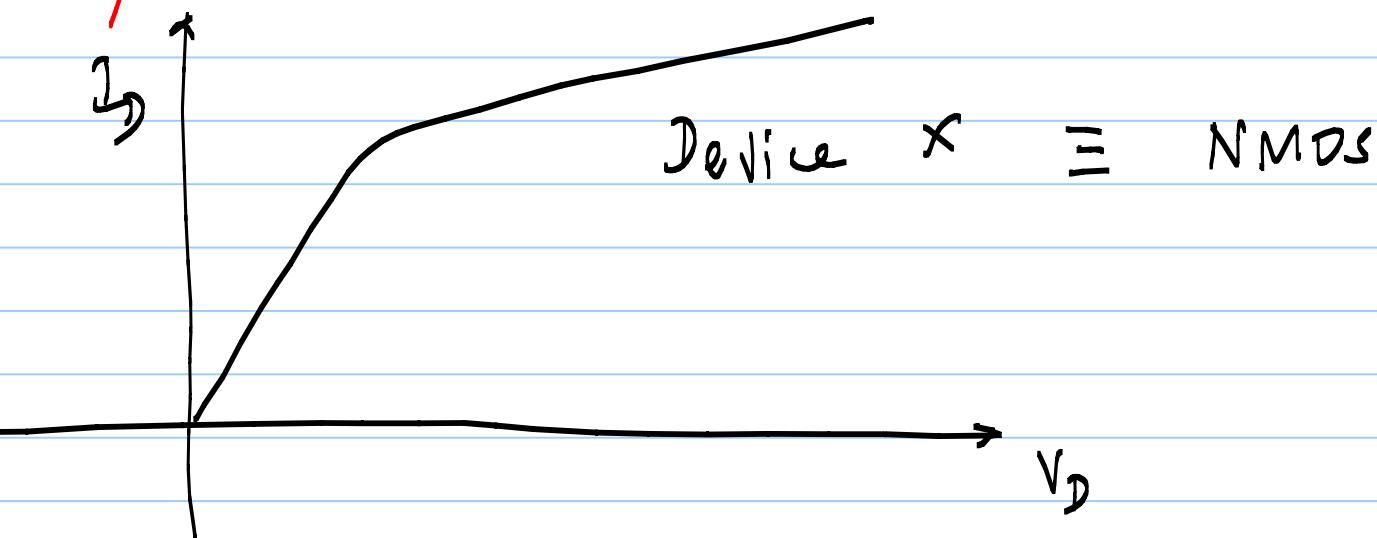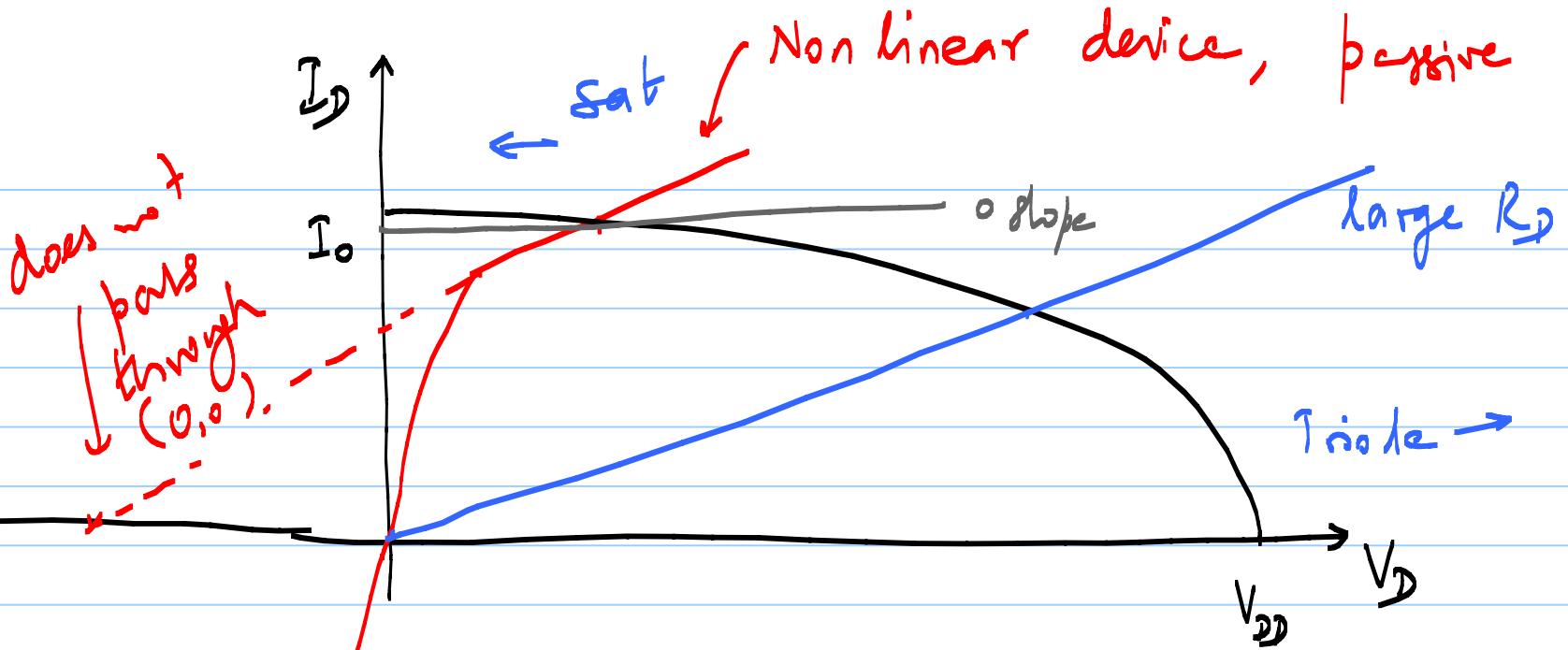

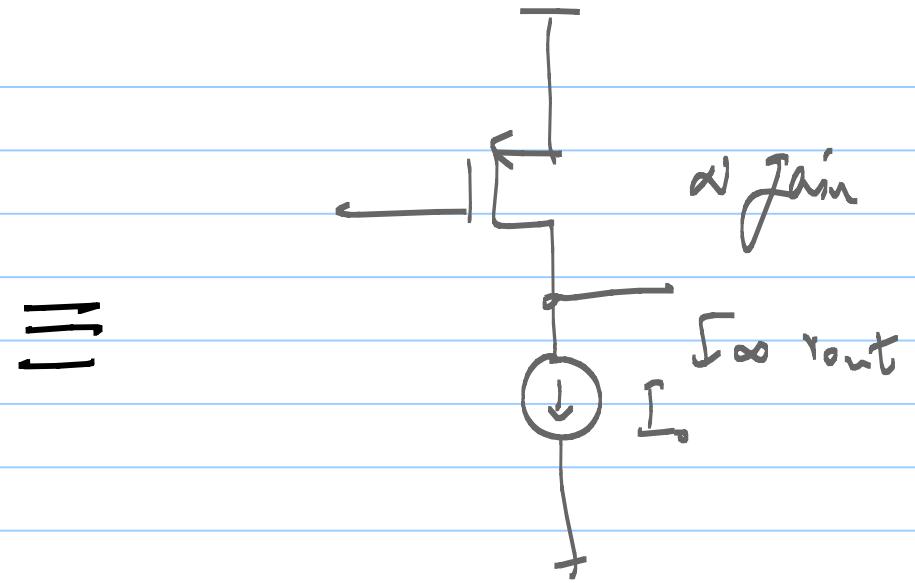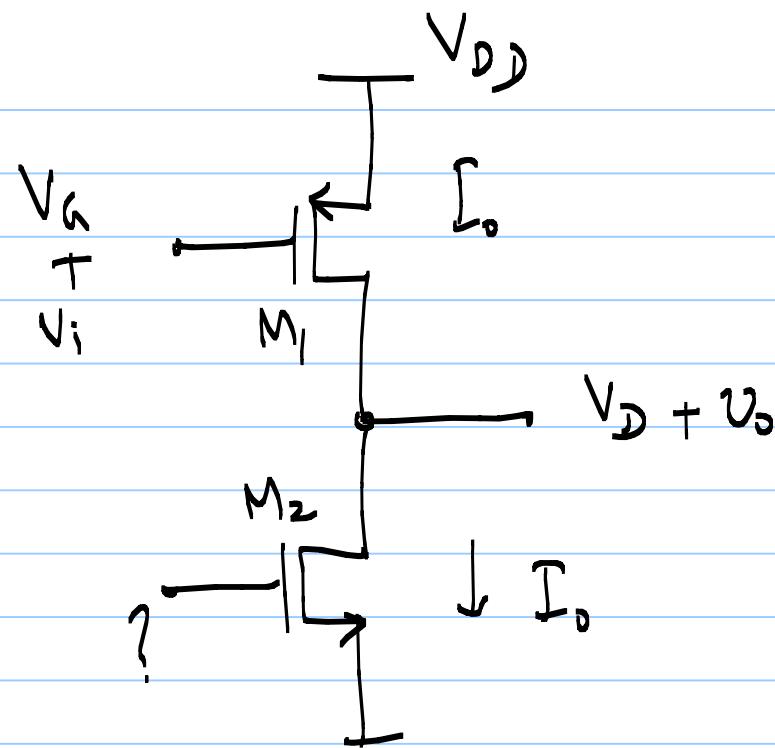


$$Z_{down} = \frac{1}{g_{m2}}$$
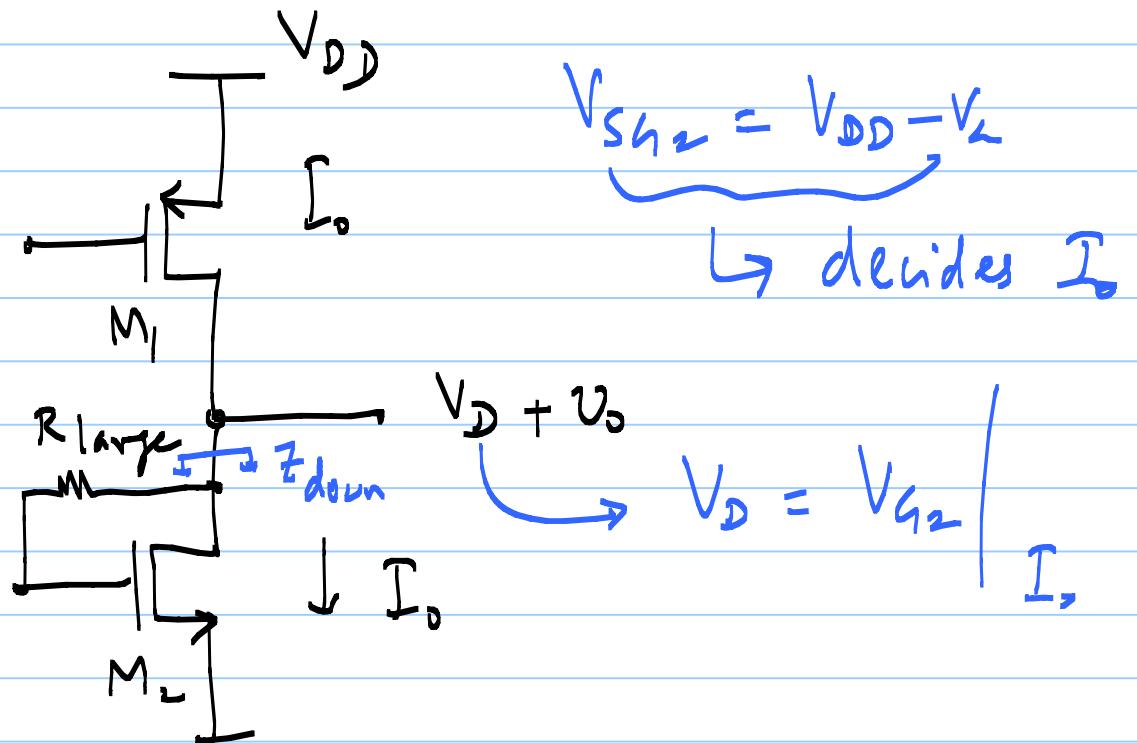
$$\text{gain} = -\frac{g_{m1}}{g_{m2}} \quad (\text{small})$$



18 | 9 | 2020

Lecture 27

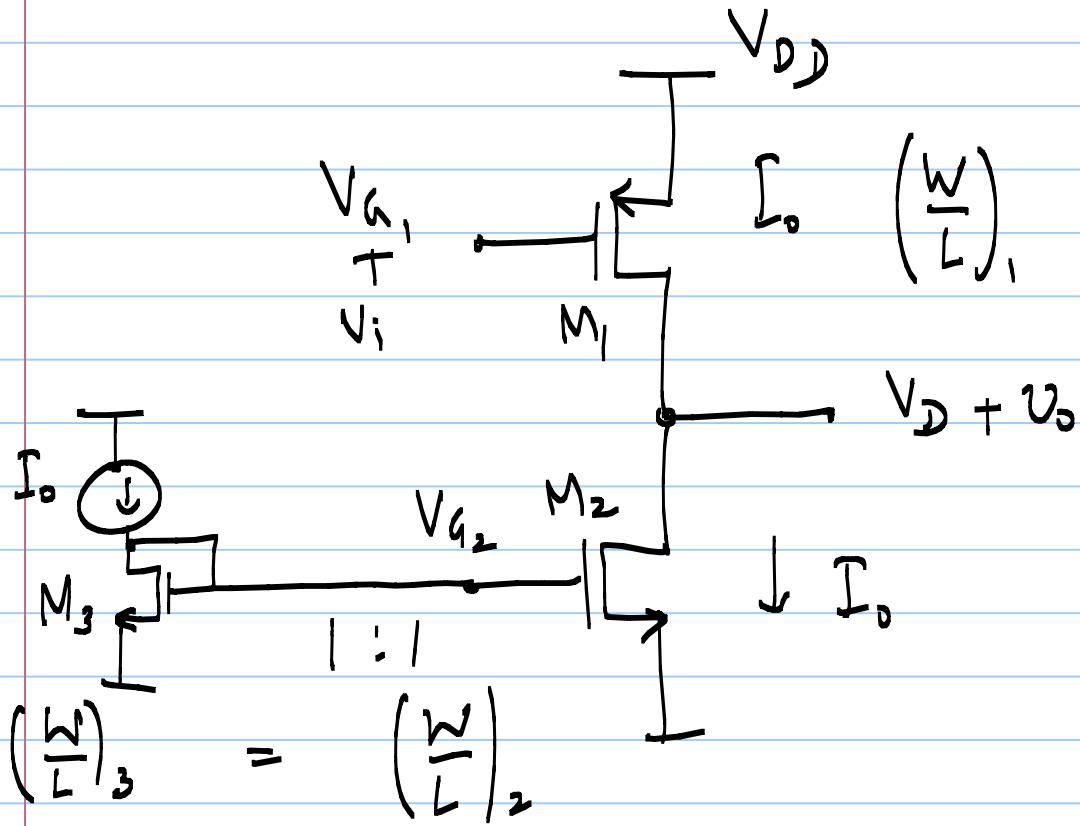

$I_o \left(\frac{W}{L}\right)_1$ - decided by gain, swing limit etc.


ideal $M_1, M_2 \& M_3$:

* all $I_D = I_o$

* ideal gain $= \infty$

* practical gain



$$= -g_m \left(r_{ds1} || r_{ds2} \right)$$

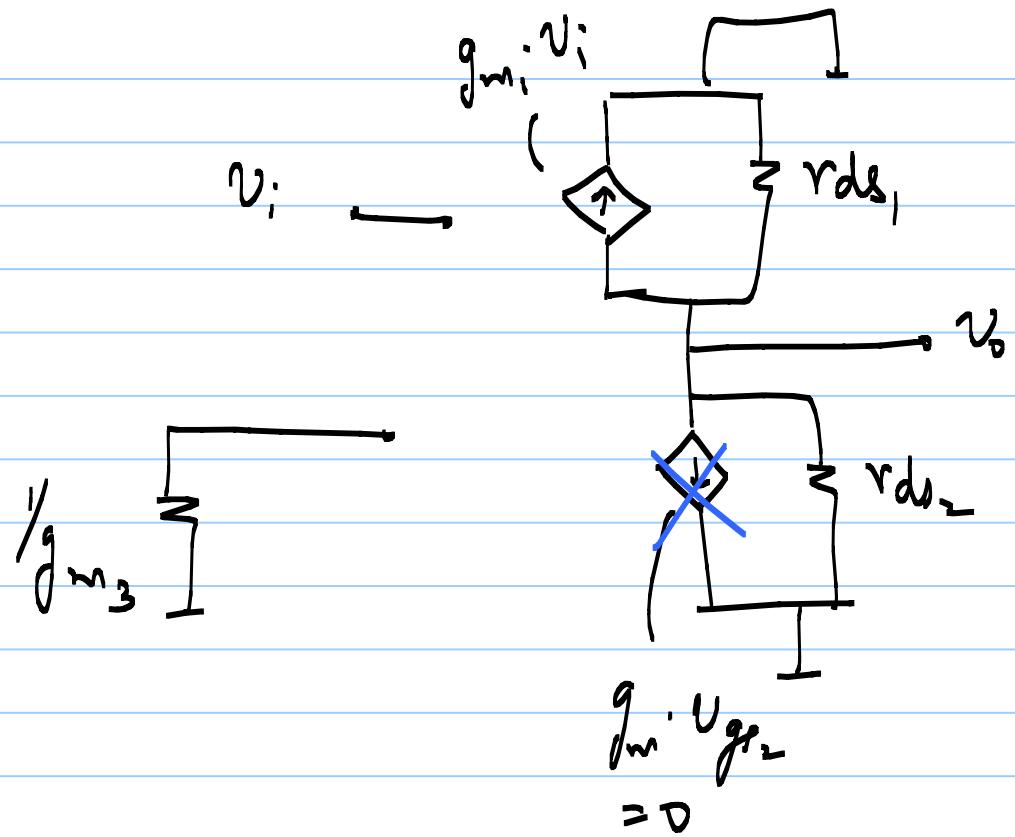


$$\frac{v_o}{v_i} = -g_m (r_{ds_1} || r_{ds_2})$$

V_{Tn} = threshold voltage of NMOS

V_{Tp} = threshold voltage of PMOS

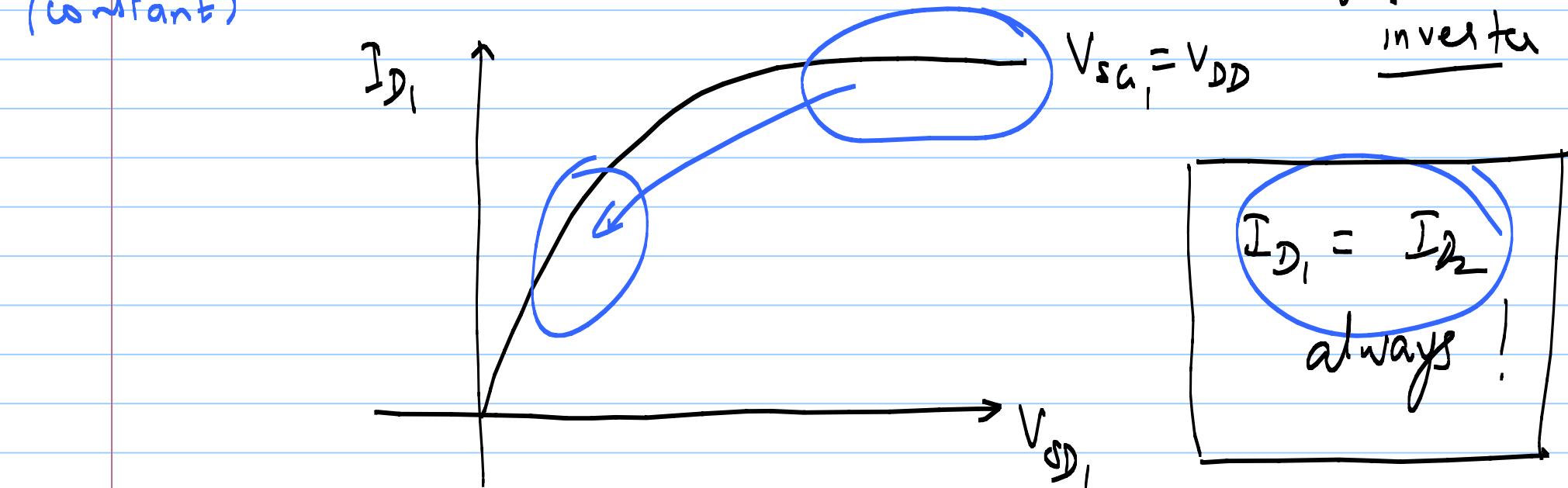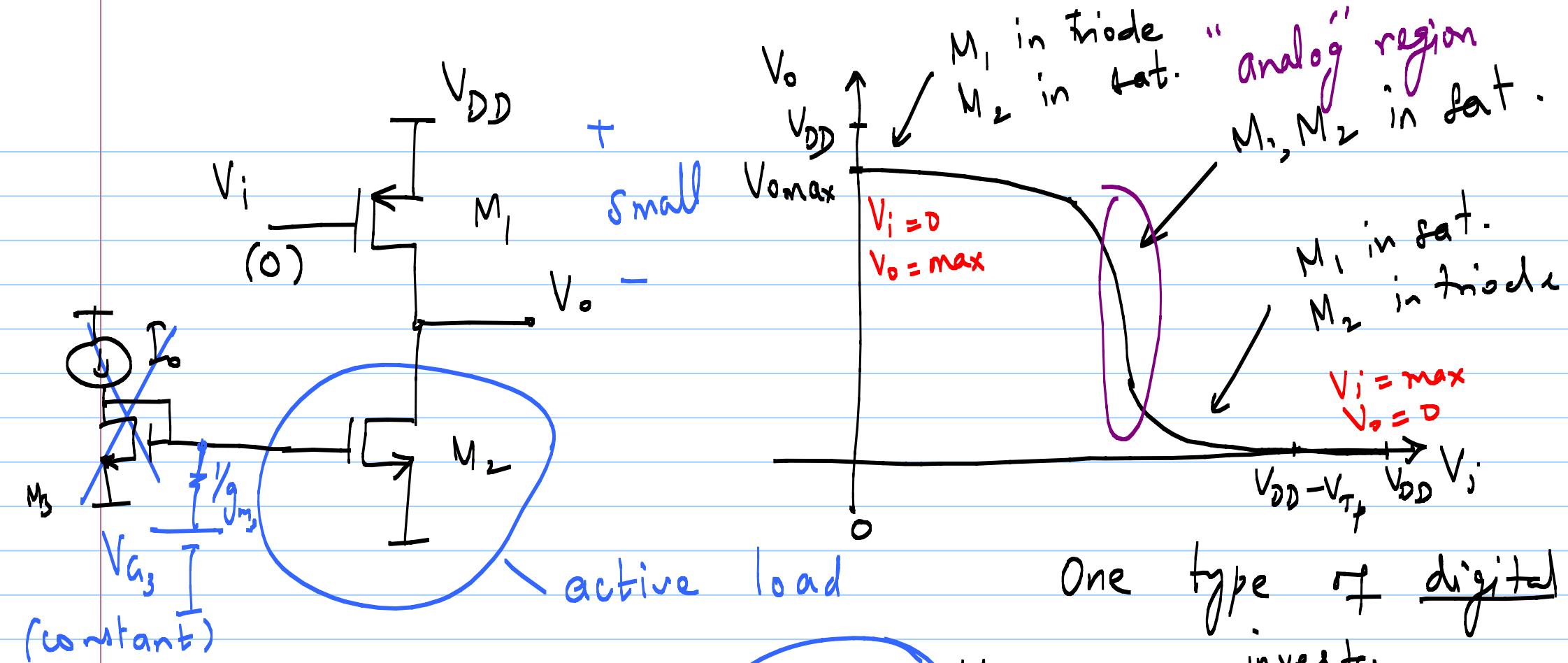


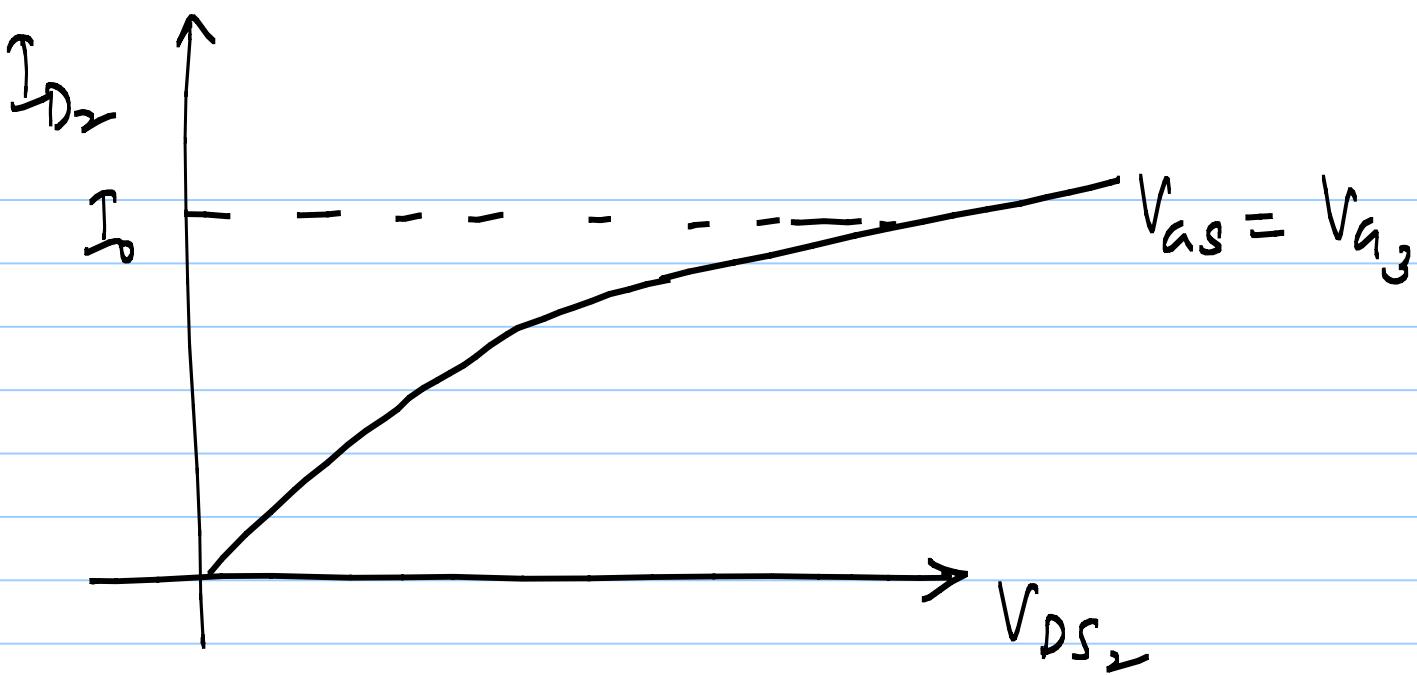

@

$$V_i = V_{DD} - V_{TP} : I_{D1} = 0$$

"inverting amplifier"

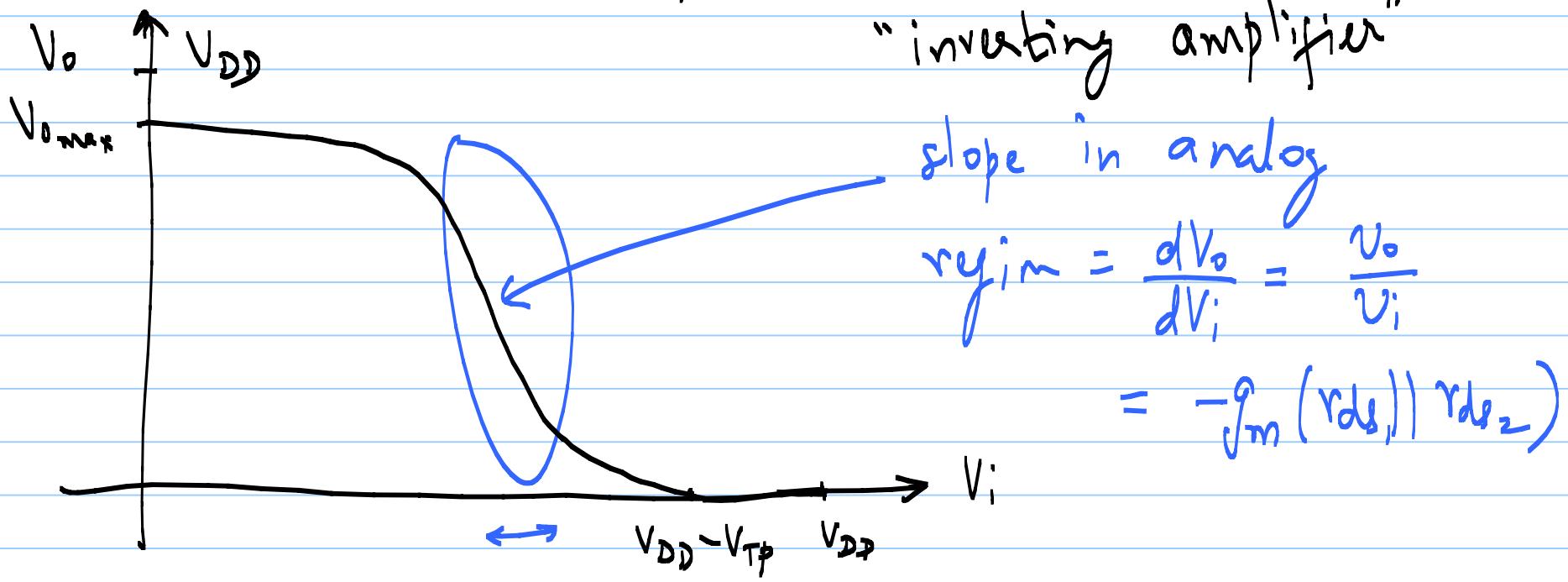


$V_{o_{max}}$

$$\text{Triode } I_D = \text{Sat. } I_{D_2}$$

In This course : normally for bias point
calculations - ignore effect of λ

22/9/2020



Lecture 28

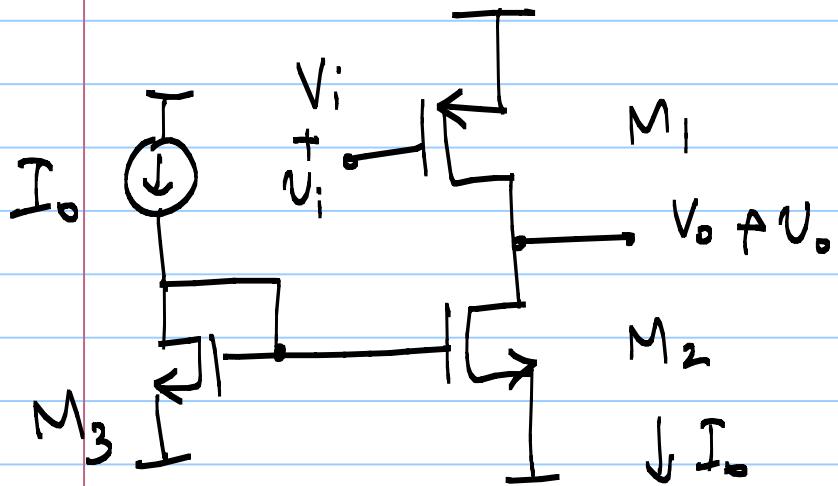


$$\frac{V_o}{V_i} = -g_{m1} \left(r_{ds1} \parallel r_{ds2} \right)$$


$$= -\frac{g_{m1}}{g_{ds1} + g_{ds2}}$$




$$r_{ds_3}$$

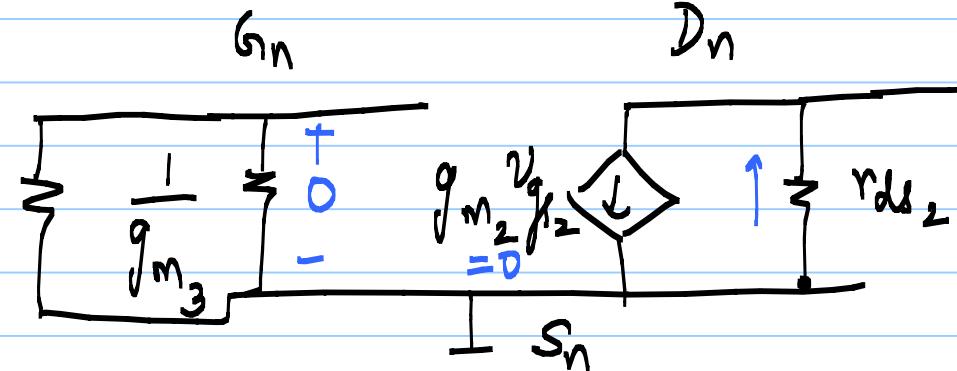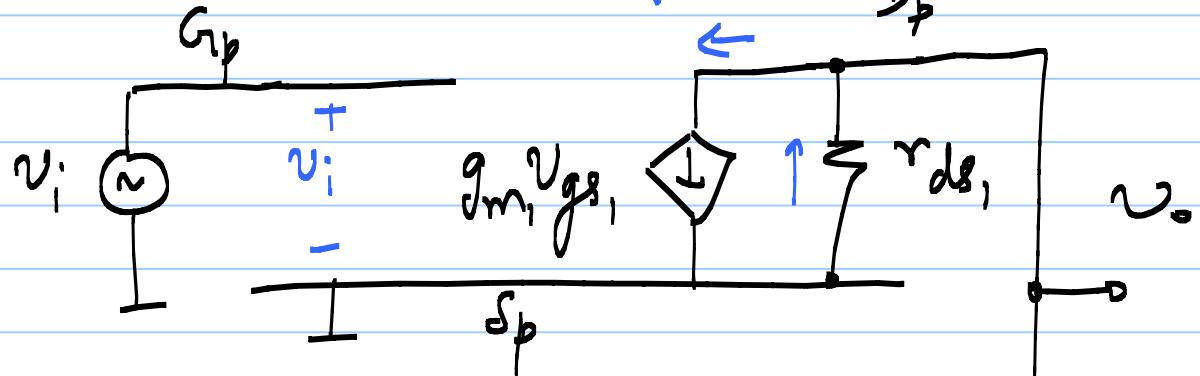

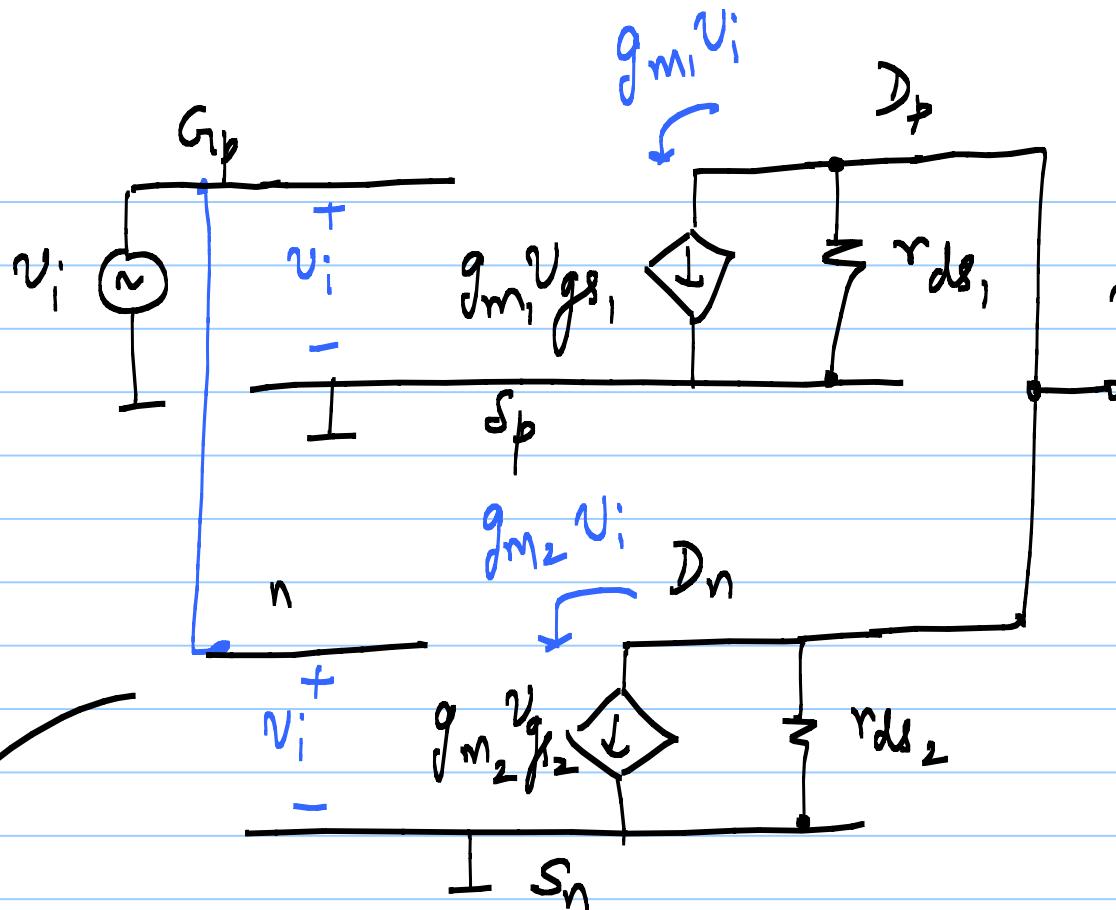

If r_{ds1} & r_{ds2} were ∞ , gain = ∞

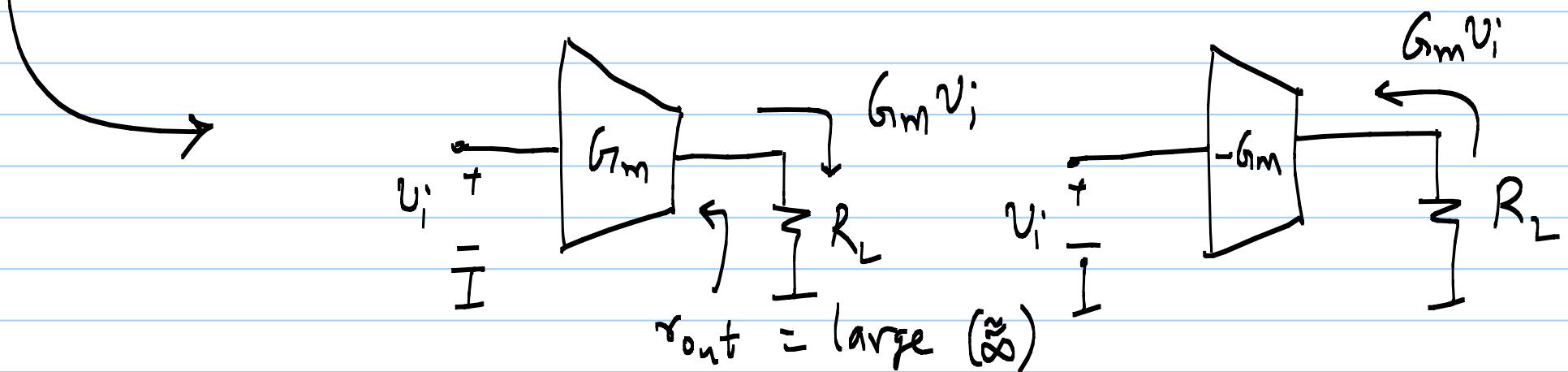

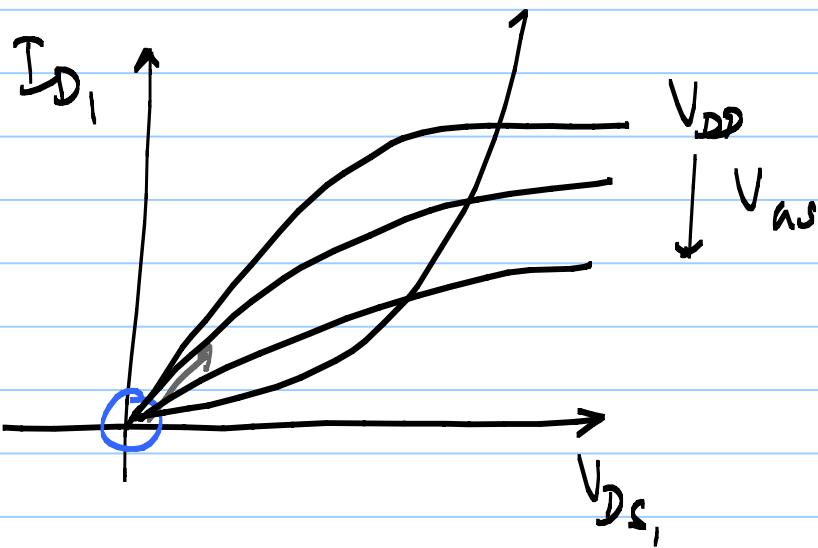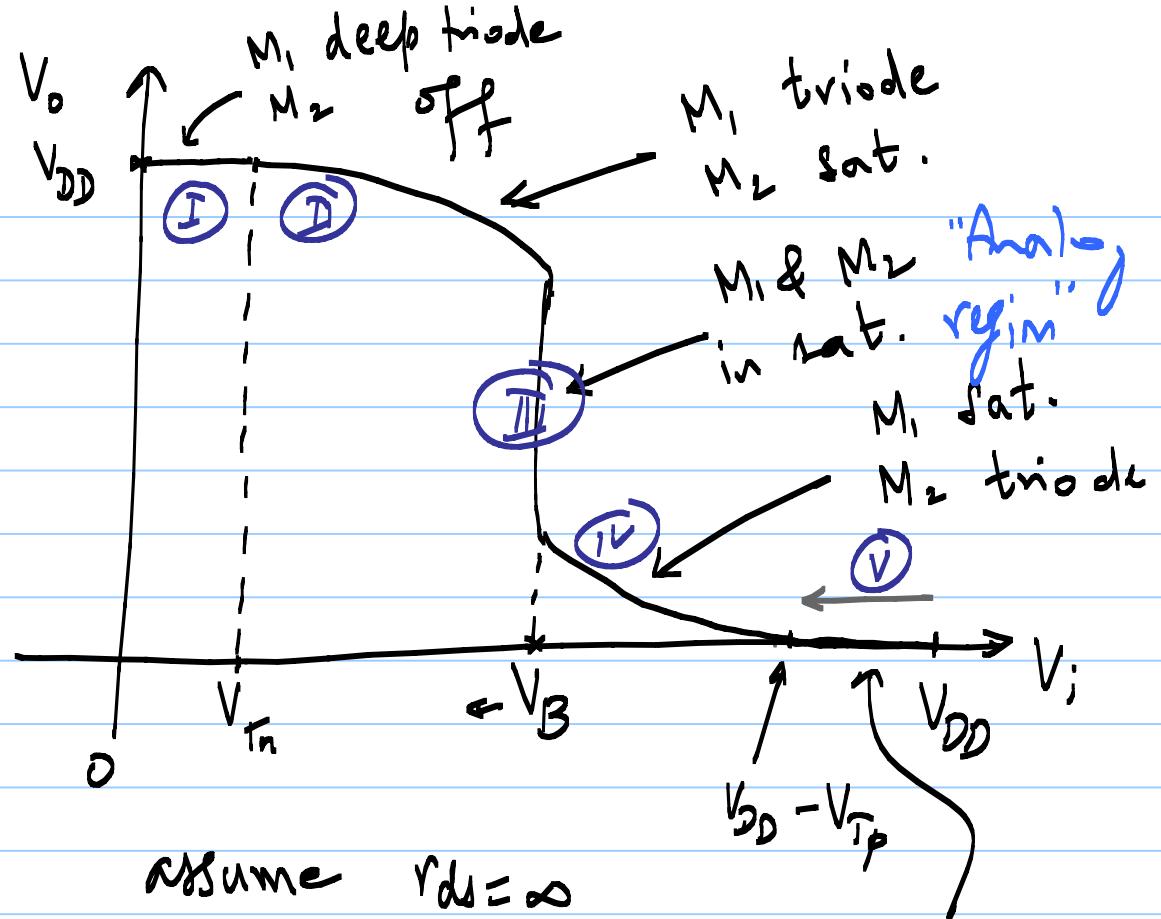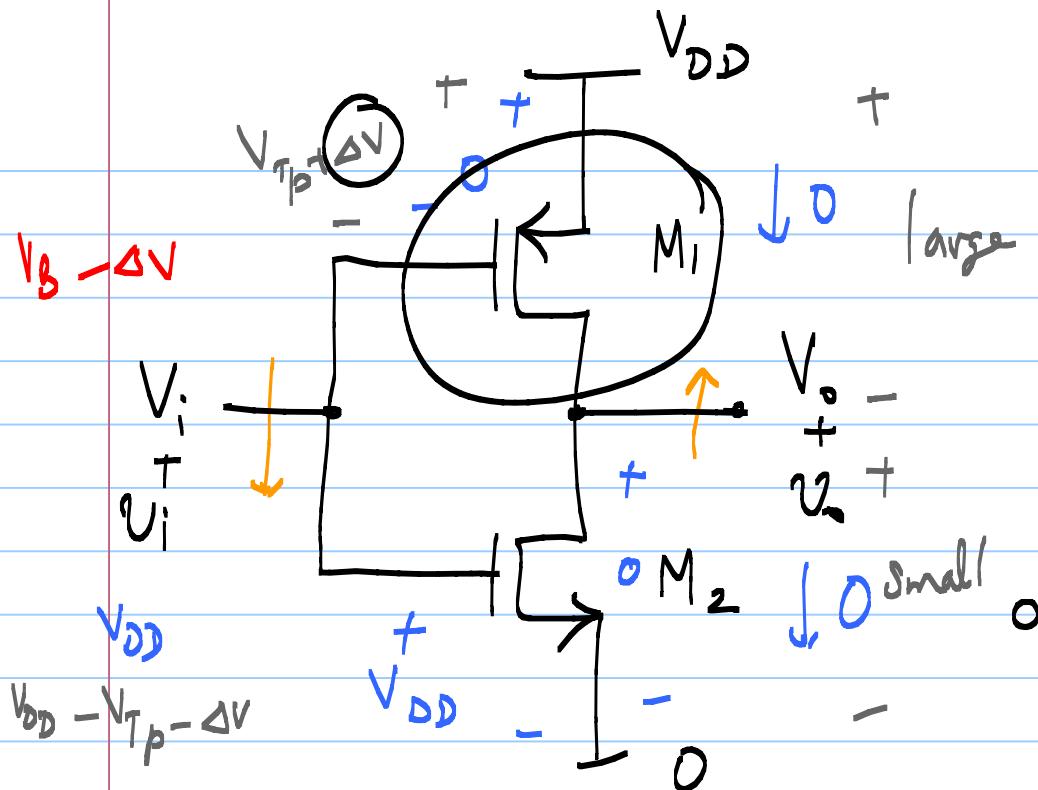

assume $r_{ds} = \infty$
 "CMOS"
 Inverter

$$V_i = V_{DD} - V_{TP} - \Delta V : I_{D1}(\text{sat.}) = I_{D2}(\text{triode})$$

Determine $\underline{V_B}$:

$$I_{D_1}(\text{sat}) = I_{D_2}(\text{sat.})$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_p \left[V_{DD} - V_B - V_{T_P} \right]^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_n \left[V_B - V_{T_n} \right]^2$$


$$k_n = \mu_n \left(\frac{W}{L} \right)_n ; \quad k_p = \mu_p \left(\frac{W}{L} \right)_p$$

$$V_B - V_{T_n} = \sqrt{\frac{k_p}{k_n}} \cdot (V_{DD} - V_B - V_{T_p})$$

$$V_B \left[1 + \sqrt{\frac{k_p}{k_n}} \right] = V_{T_n} + (V_{DD} - V_{T_p}) \left[\sqrt{\frac{k_p}{k_n}} \right]$$

$$V_B = \frac{V_{Tn} + (V_{DD} - V_{Tp}) \left[\sqrt{\frac{k_p}{k_n}} \right]}{1 + \sqrt{\frac{k_p}{k_n}}}$$

* $M_n \approx 3 M_p$

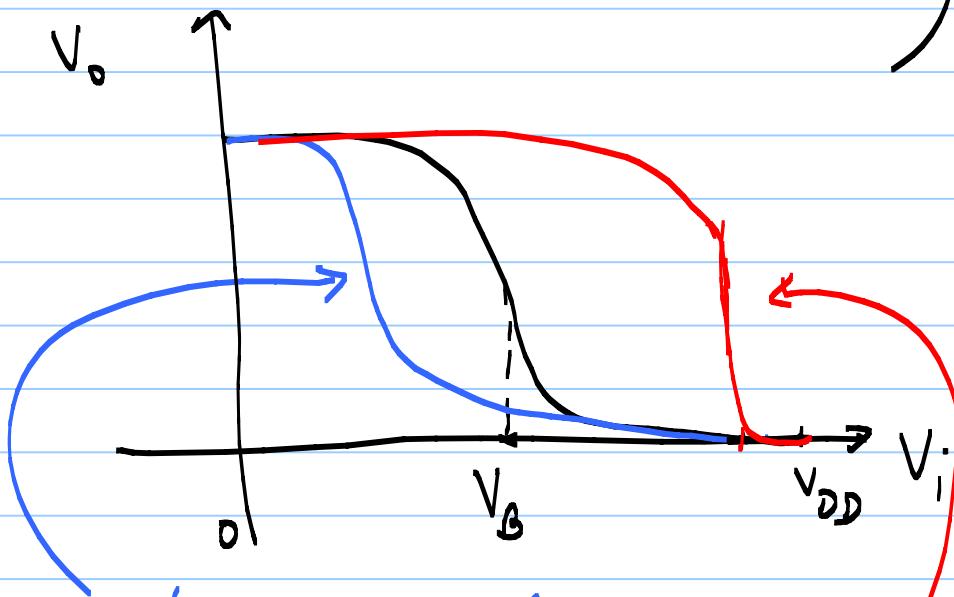

1) $V_{Tn} = V_{Tp} = V_T$

We want $V_B = V_{DD}/2$

$$\Rightarrow k_p = k_n \Rightarrow \left(\frac{W}{L} \right)_p = 3 \left(\frac{W}{L} \right)_n$$

$$\left(\frac{W}{L} \right)_p = \left(\frac{M_n}{M_p} \right) \left(\frac{W}{L} \right)_n$$

2) If $\left(\frac{W}{L} \right)_n \gg \left(\frac{W}{L} \right)_p$



$$V_B \approx V_{Tn}$$

3) If $\left(\frac{W}{L} \right)_p \gg \left(\frac{W}{L} \right)_n$

$$V_B \approx V_{DD} - V_{Tp}$$

23/9/2020



Lecture 29

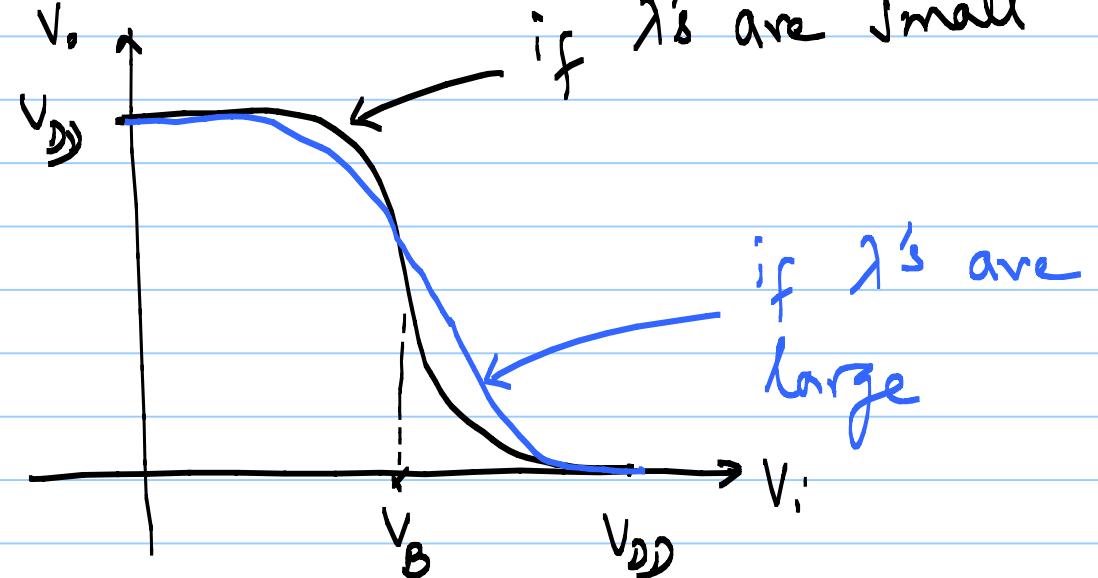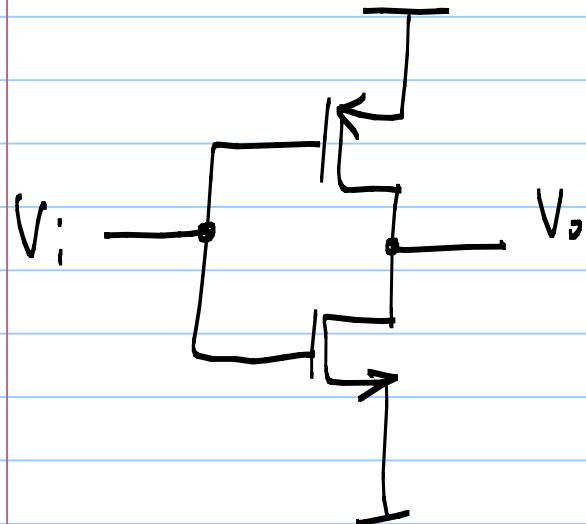

Small signal gain $\frac{V_o}{V_i} = \frac{- (g_m 1 + g_m 2)}{g_{ds1} + g_{ds2}}$

$$= - (g_m 1 + g_m 2) (r_{ds1} || r_{ds2})$$

Biasing of CMOS inv.

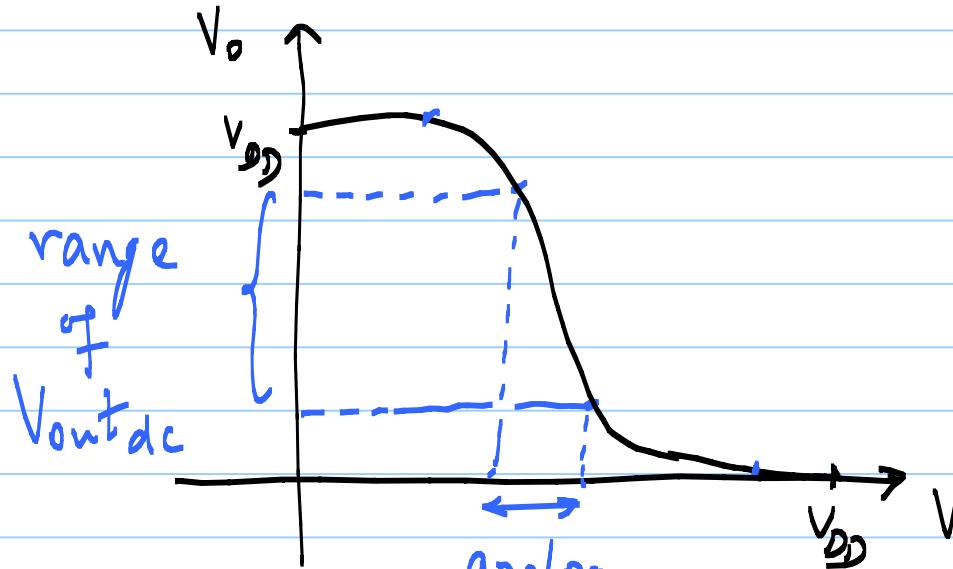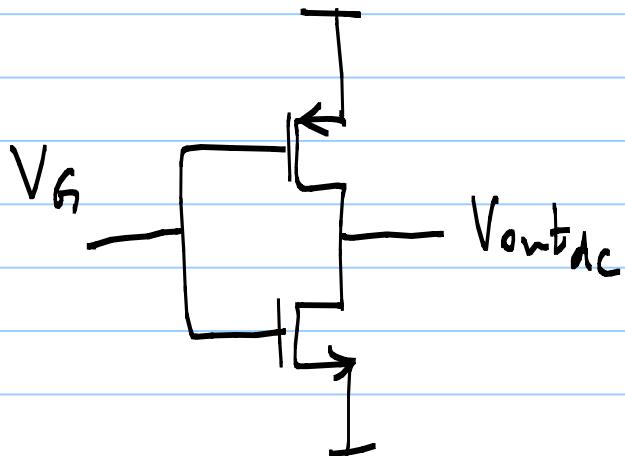




* Assume $V_B \sim V_{DD}/2$



i.e. PMOS \sim NMOS except for $M_p \sim 3 M_n$

$$\left(\frac{W}{L}\right)_p \sim 3 \left(\frac{W}{L}\right)_n$$


* Negative f.b. biasing

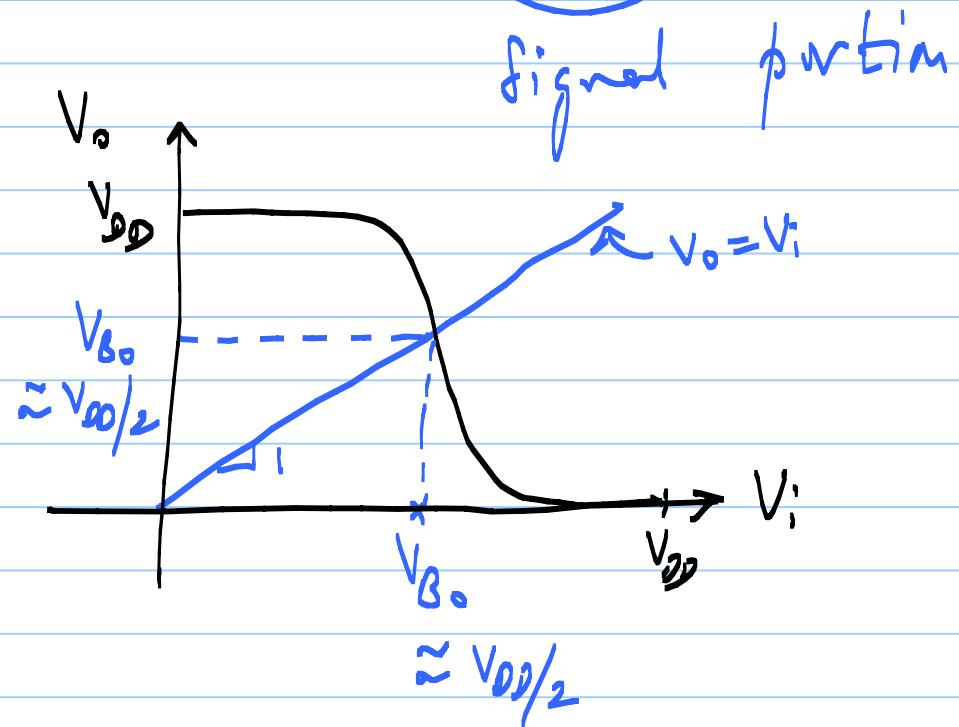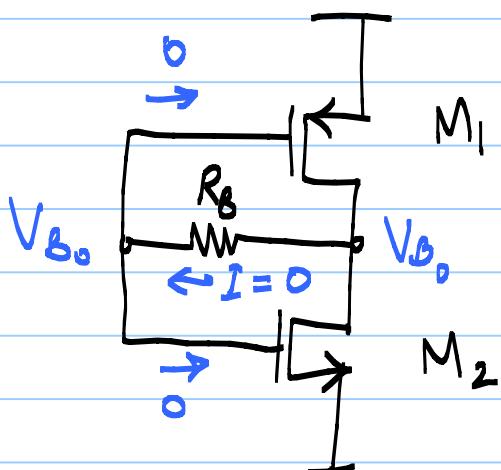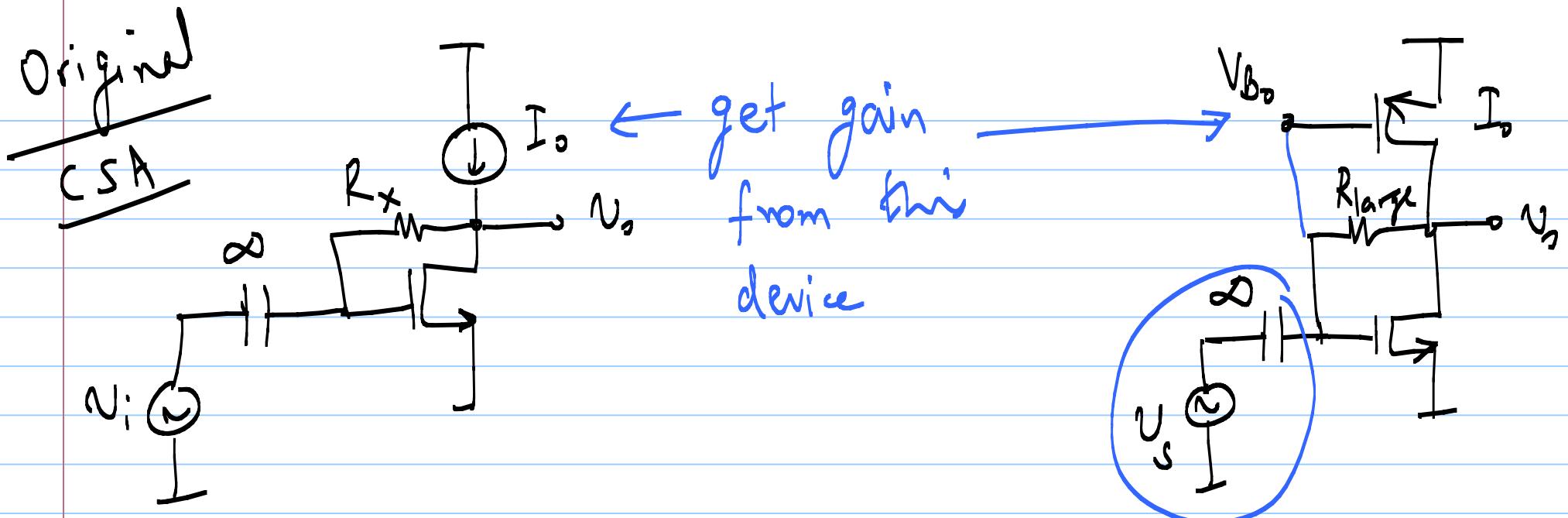→ Drain to Gate f.b. using a current source & resistor



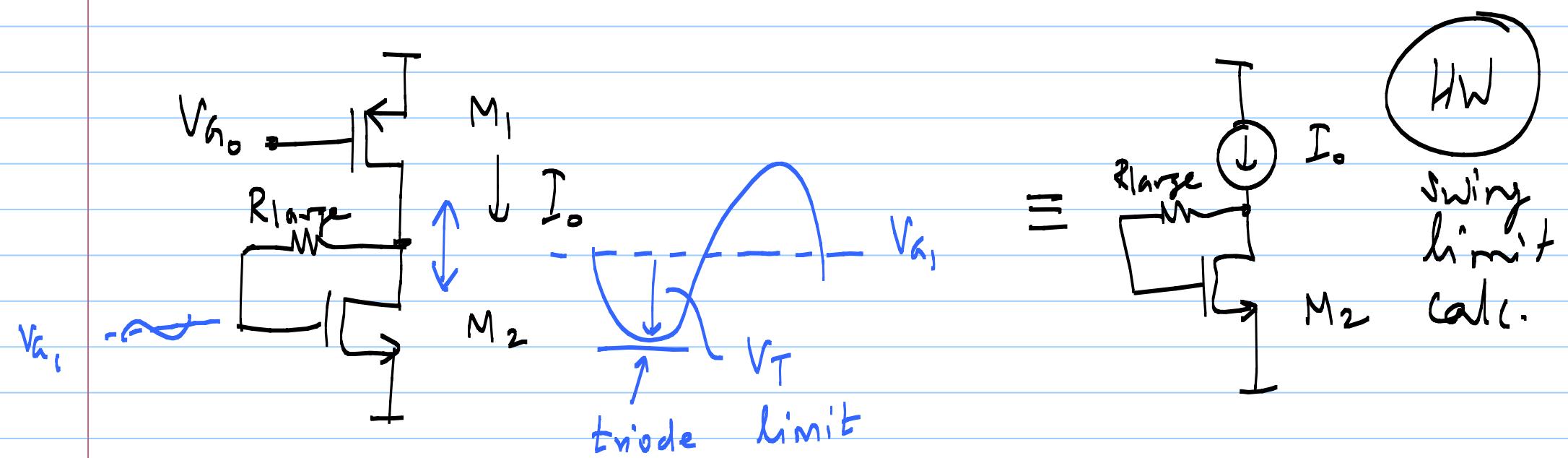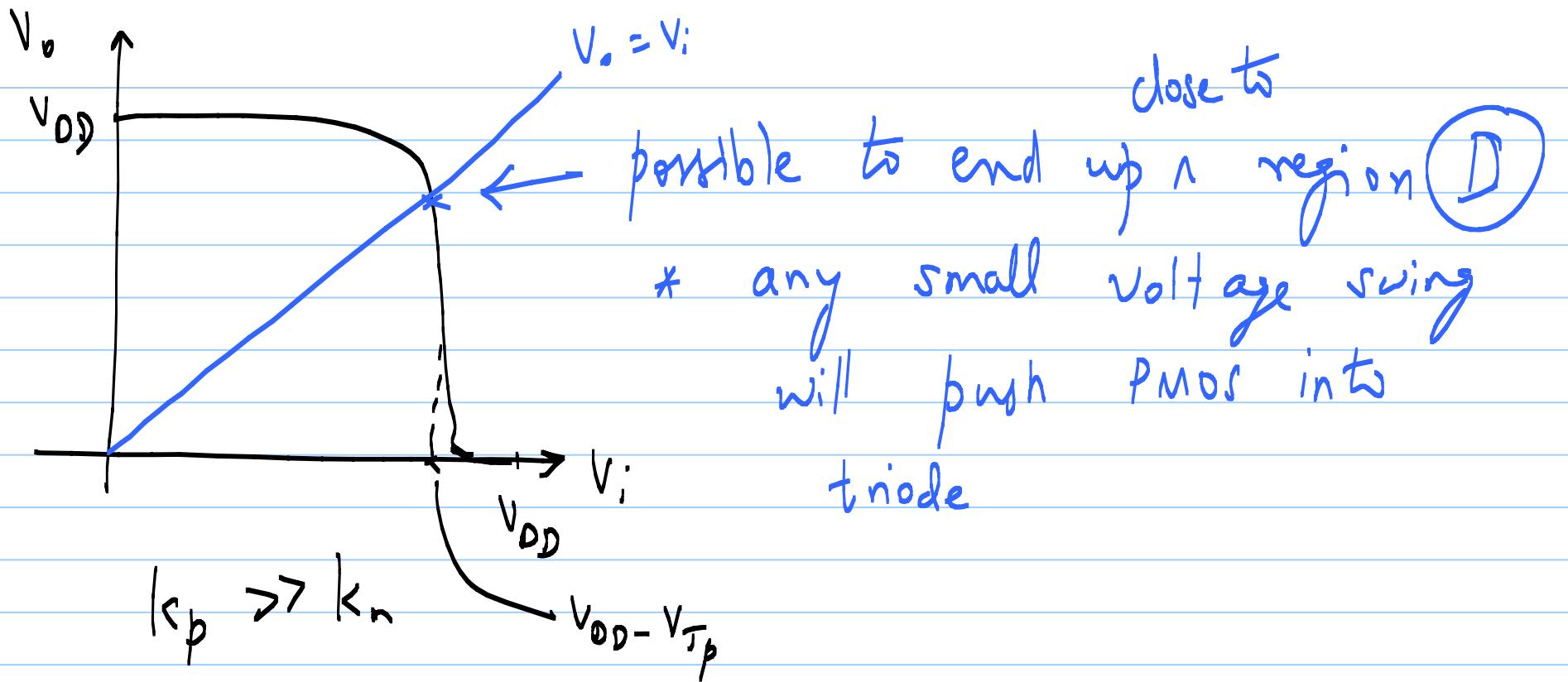

Swing limits of CMOS Inv.


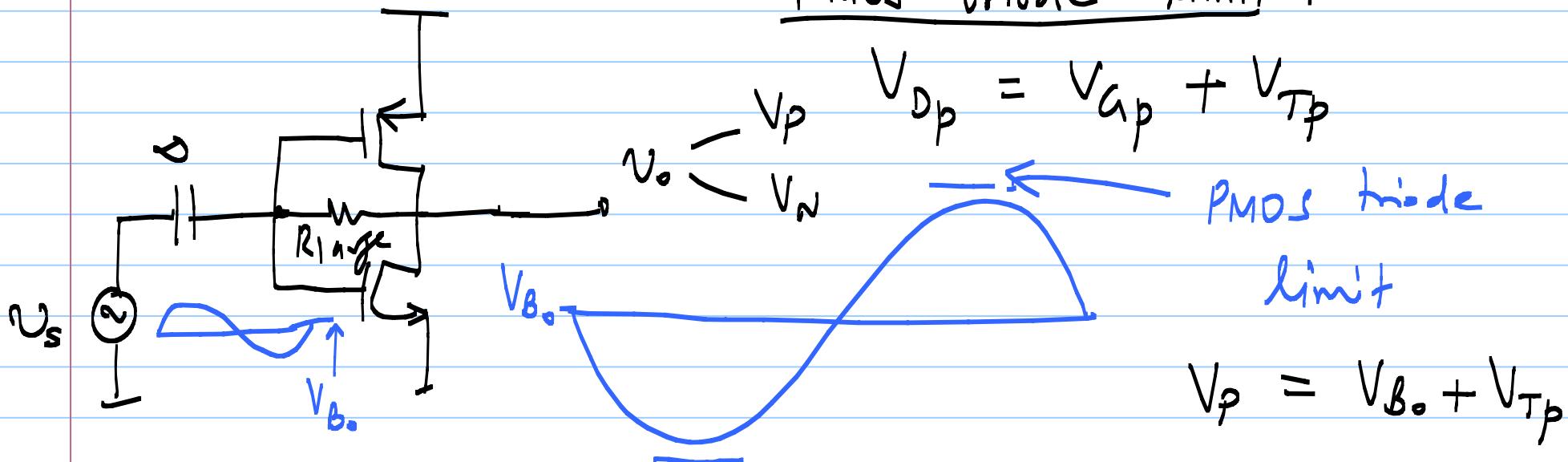


NMOS triode limit


$$V_{D_N} = V_{A_N} - V_{T_N} \Rightarrow V_N = V_{B_0} - V_{T_N}$$

IHW

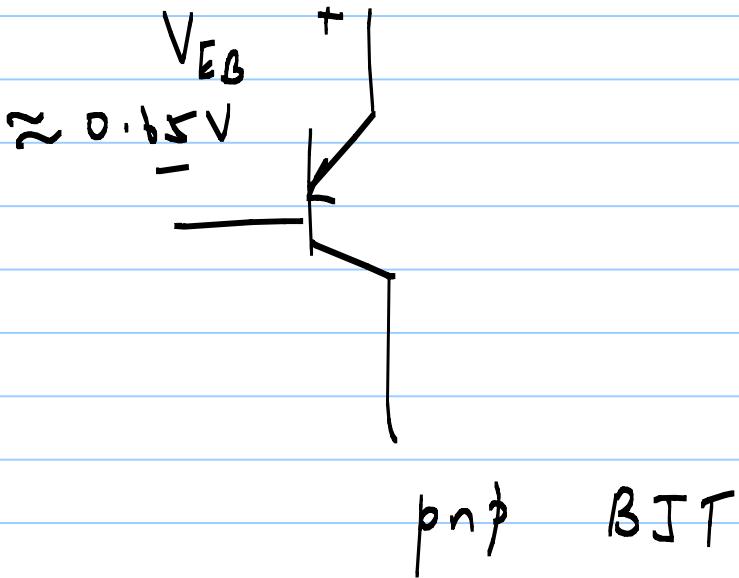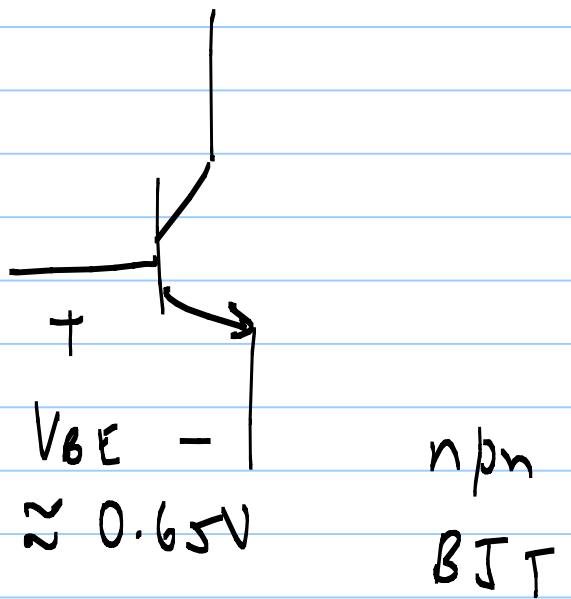- accurate swing limit calculation for inv.






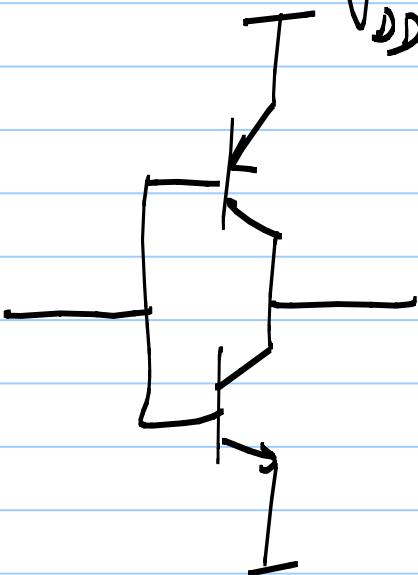
$$V_{DD} \approx V_{BE_n} + V_{EB_p} \approx 1.3V$$




24/9/2020


Lecture 30

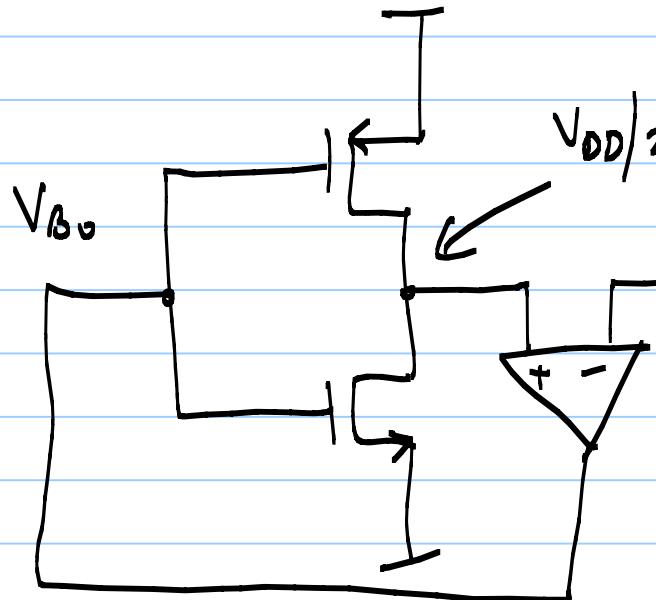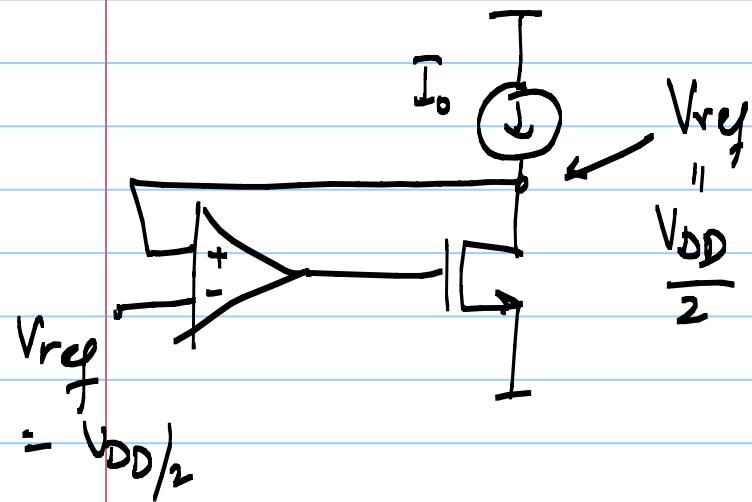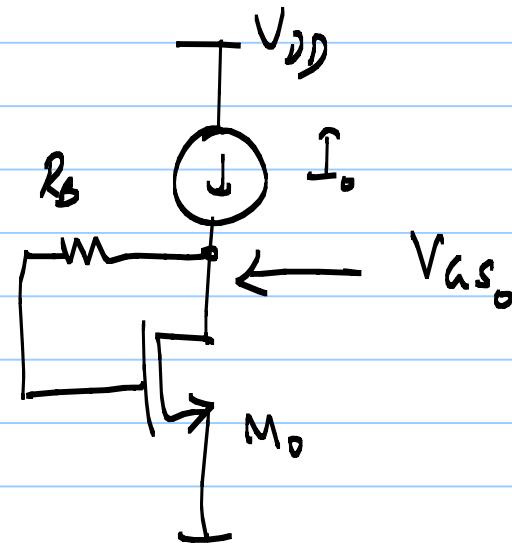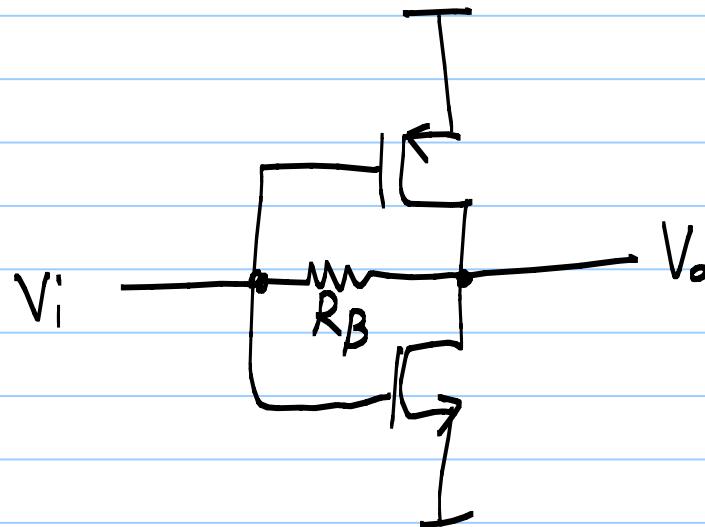

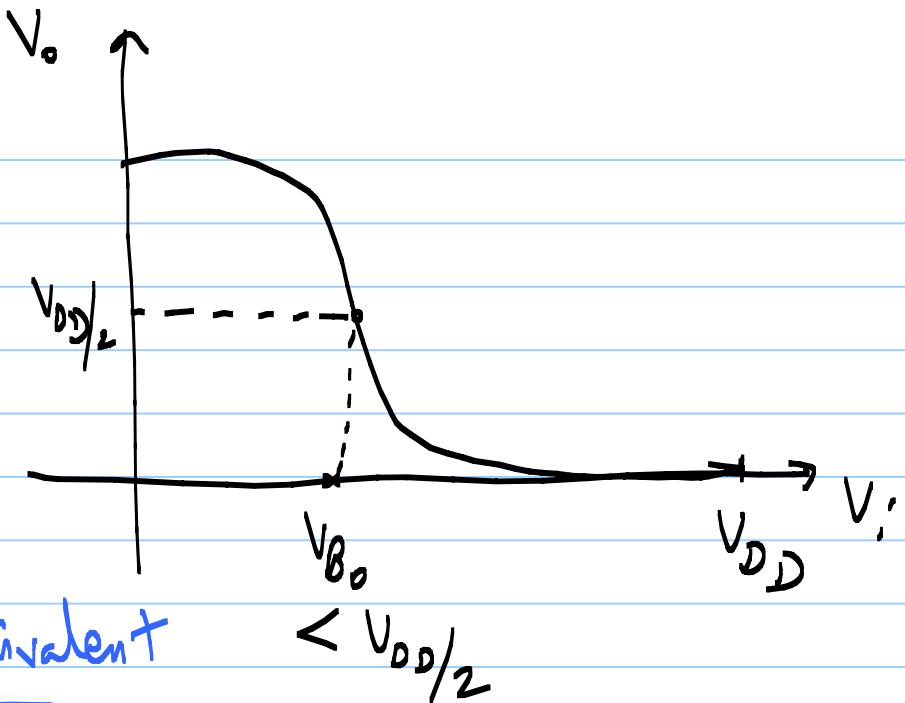Modify the circuit to break the opamp loop for AC.




Chenkin equivalent

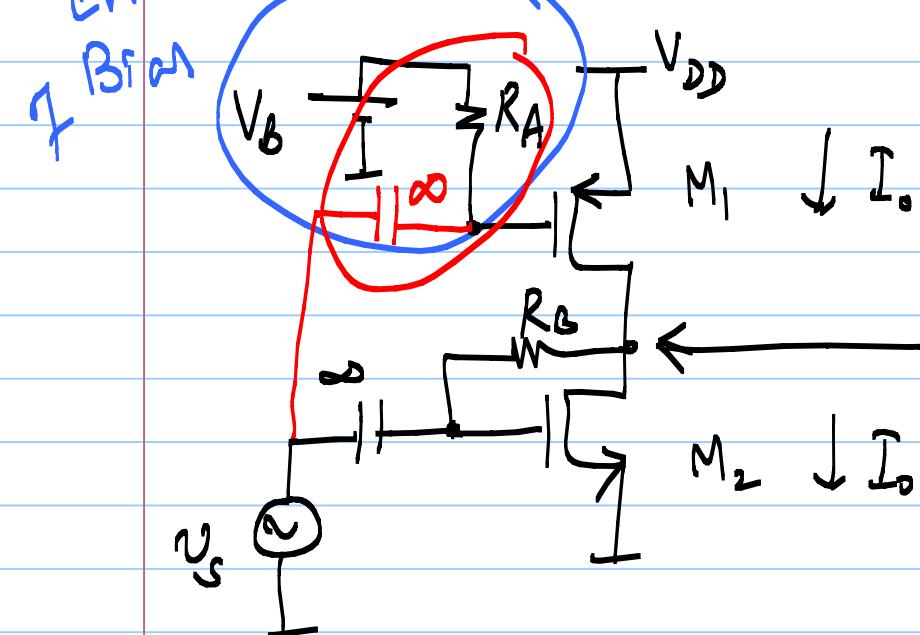

$V_{o_{dc}}$ adjusts
 $M_2 \downarrow I_D$ itself based on $I_D (V_o)$


\equiv

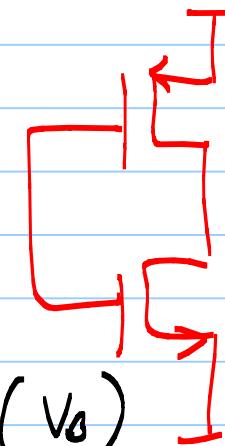

for
AC

Differential Amplifiers

σ_{amp} :

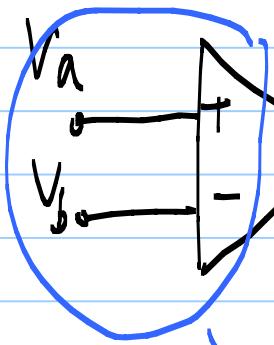

$$A(V_a - V_b) ; A \rightarrow \infty$$

↑ first half of course

σ_{amp} responds only to $V_a - V_b$

$$V_a = \left(\frac{V_a + V_b}{2} \right) + \left(\frac{V_a - V_b}{2} \right)$$

$$V_b = \left(\frac{V_a + V_b}{2} \right) - \left(\frac{V_a - V_b}{2} \right)$$

common-mode

voltage V_{CM}

differential mode

voltage V_{DM}

e.g., 1) $V_a = 1V$, $V_b = 1.1V$

$$V_{CM} = 1.05V \quad V_{DM} = -0.05V$$

$$V_a = V_{CM} + V_{DM}$$

** opamp should amplify only V_{CM}*

2) $V_a = 1.1V$, $V_b = 1V$

$$V_{CM} = 1.05V, \quad V_{DM} = 0.05V$$

3) $V_a = 0.6V$, $V_b = 0.5V$

$$V_{CM} = 0.55V, \quad V_{DM} = 0.05V$$


* Assume $V_a = v_a$ & $V_b = v_b$

$$V_a = V_{CM} + \frac{\Delta V}{2} \quad V_b = V_{CM} - \frac{\Delta V}{2}$$


We know: $v \xrightarrow{k} kv$

Circuit

(I)

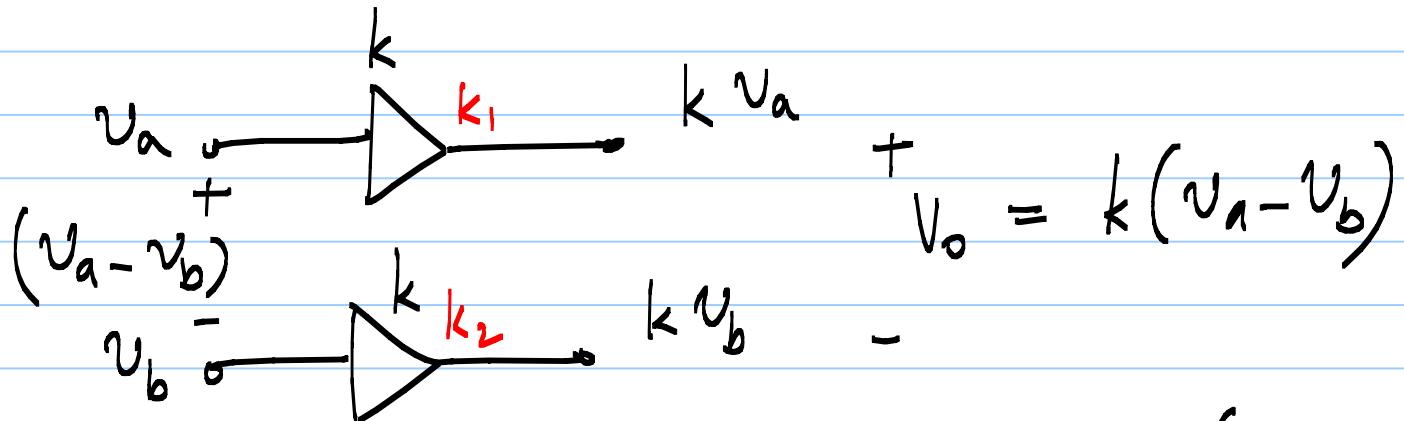

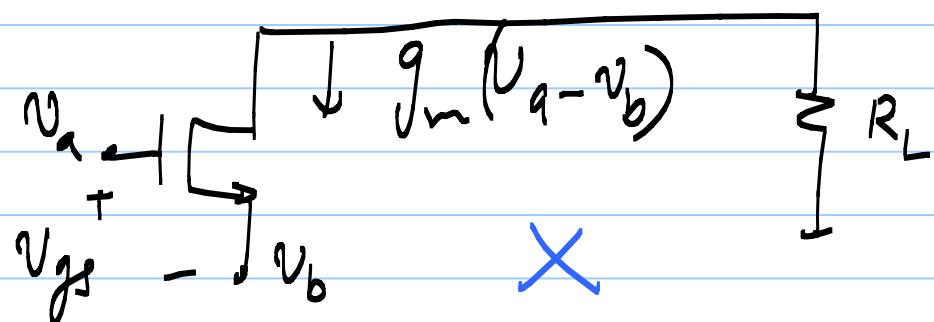* We wanted single-ended output (ignore this for now)



For circuit (I), what are V_{icm} , V_{idm} , V_{ocm} , V_{odm} ?

(1) has
equal
 A_{CM} & A_{DM}


$$V_{i_{CM}} = \frac{V_a + V_b}{2} ; \quad V_{i_{DM}} = \frac{V_a - V_b}{2}$$

bad ↓ good


$$V_{o_{CM}} = k \left(\frac{V_a + V_b}{2} \right) ; \quad V_{o_{DM}} = k \left(\frac{V_a - V_b}{2} \right)$$

we want large A_{DM} for A_{CM}

e.g.

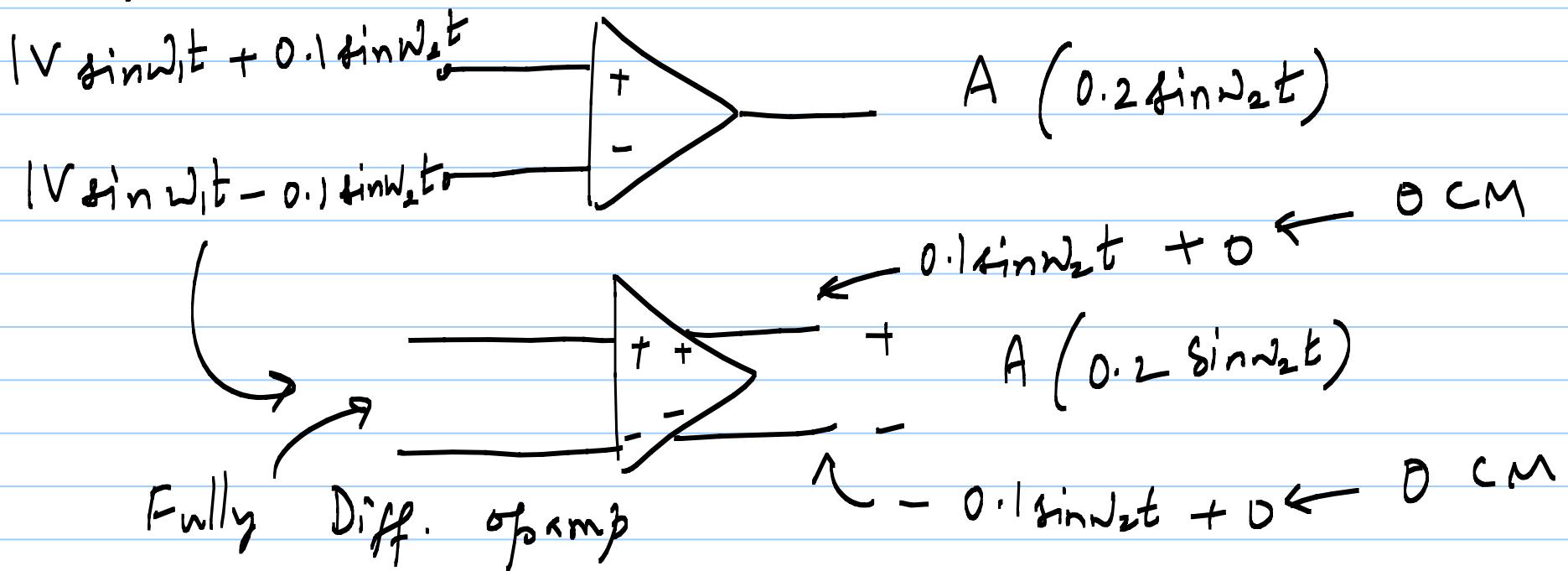

Circuit I

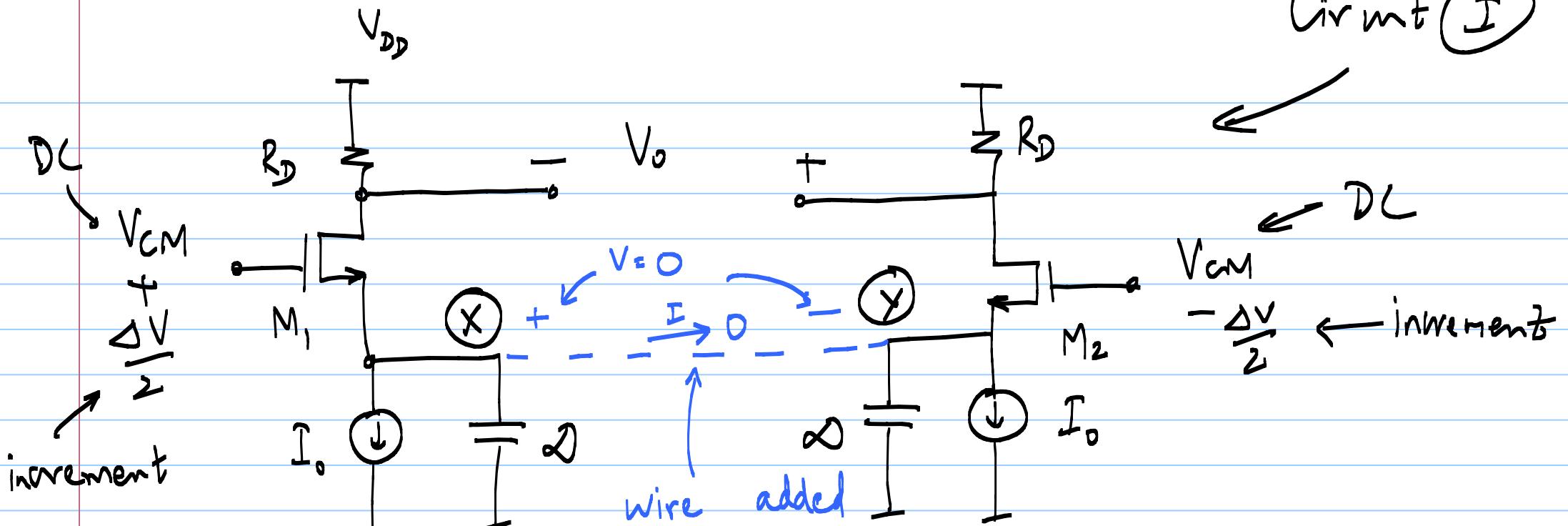


to original circuit

$$V_x = V_{CM} - V_{HS_1}; \quad V_y = V_{CM} - V_{HS_2}$$

$$V_{HS_1} = V_{HS_2} \Rightarrow V_x = V_y$$

25 | a | 2020


Lecture 31

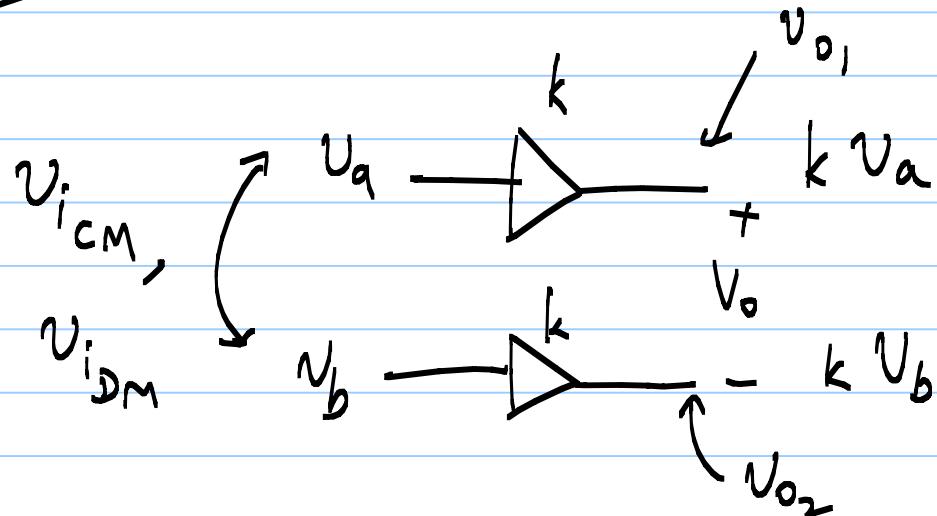


$$\begin{aligned}V_{oCM} &= \frac{V_{o1} + V_{o2}}{2} \\&= k \frac{(U_a + U_b)}{2} \\&= k V_{iCM}\end{aligned}$$

$$V_{oDM} = \frac{V_{o1} - V_{o2}}{2} = \frac{k(U_a - U_b)}{2} = k V_{iDM}$$

* We want to amplify only V_{iDM}

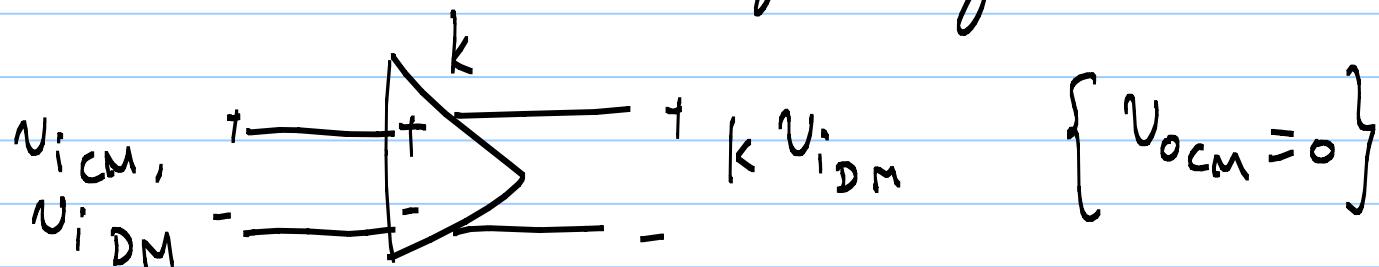

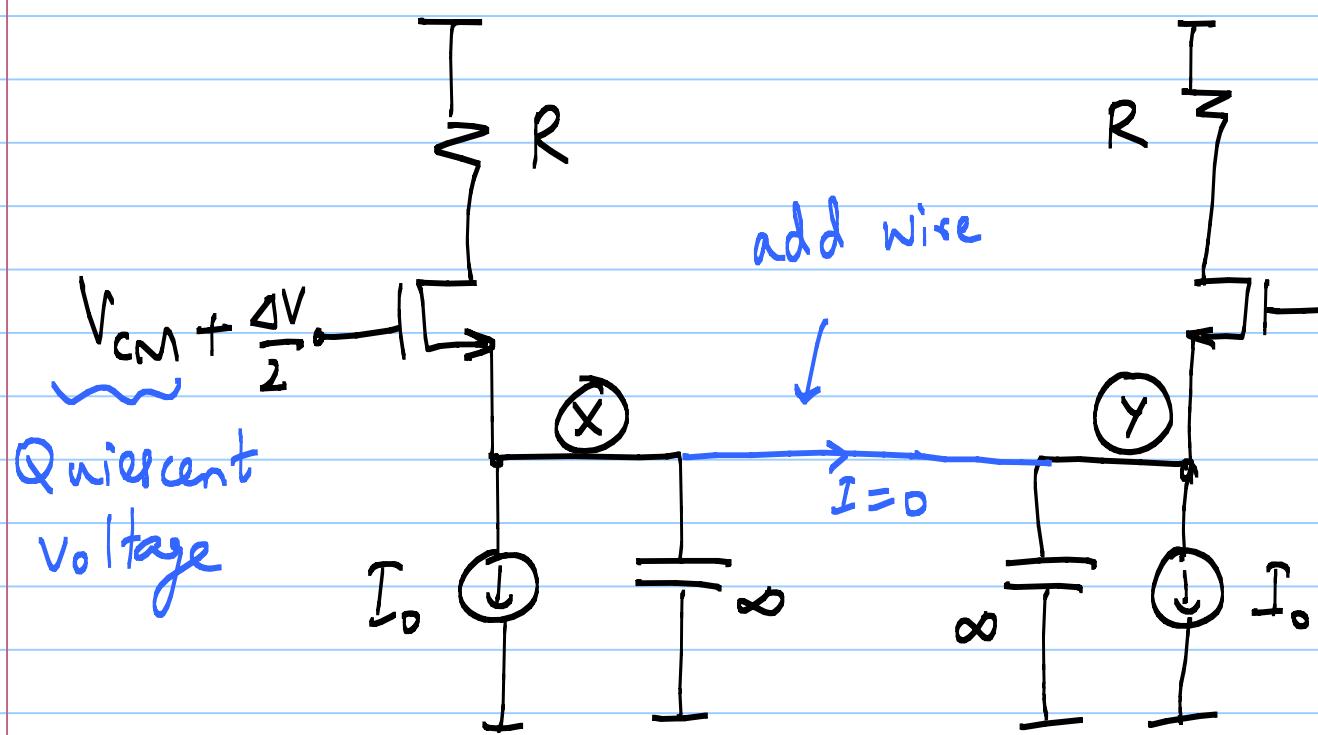


$$V_x = V_{CM} - V_{AS_1} \Big|_{I_0}$$

$$V_y = V_{CM} - V_{AS_2} \Big|_{I_0}$$

$$V_{CM} - \frac{\Delta V}{2}$$


$$V_x = V_y$$
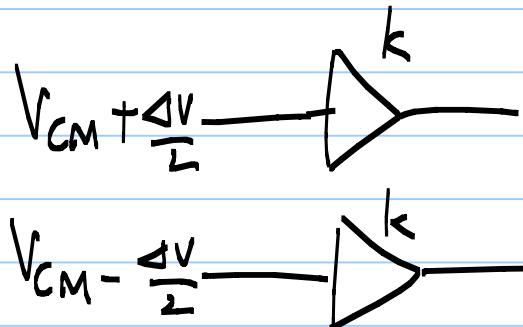
$$\Delta V_x = \Delta V_y = 0 \text{ (} \infty \text{ up) }$$





$$V_{iCM} = V_{CM}$$

$$V_{iDM} = \frac{\Delta V}{2}$$

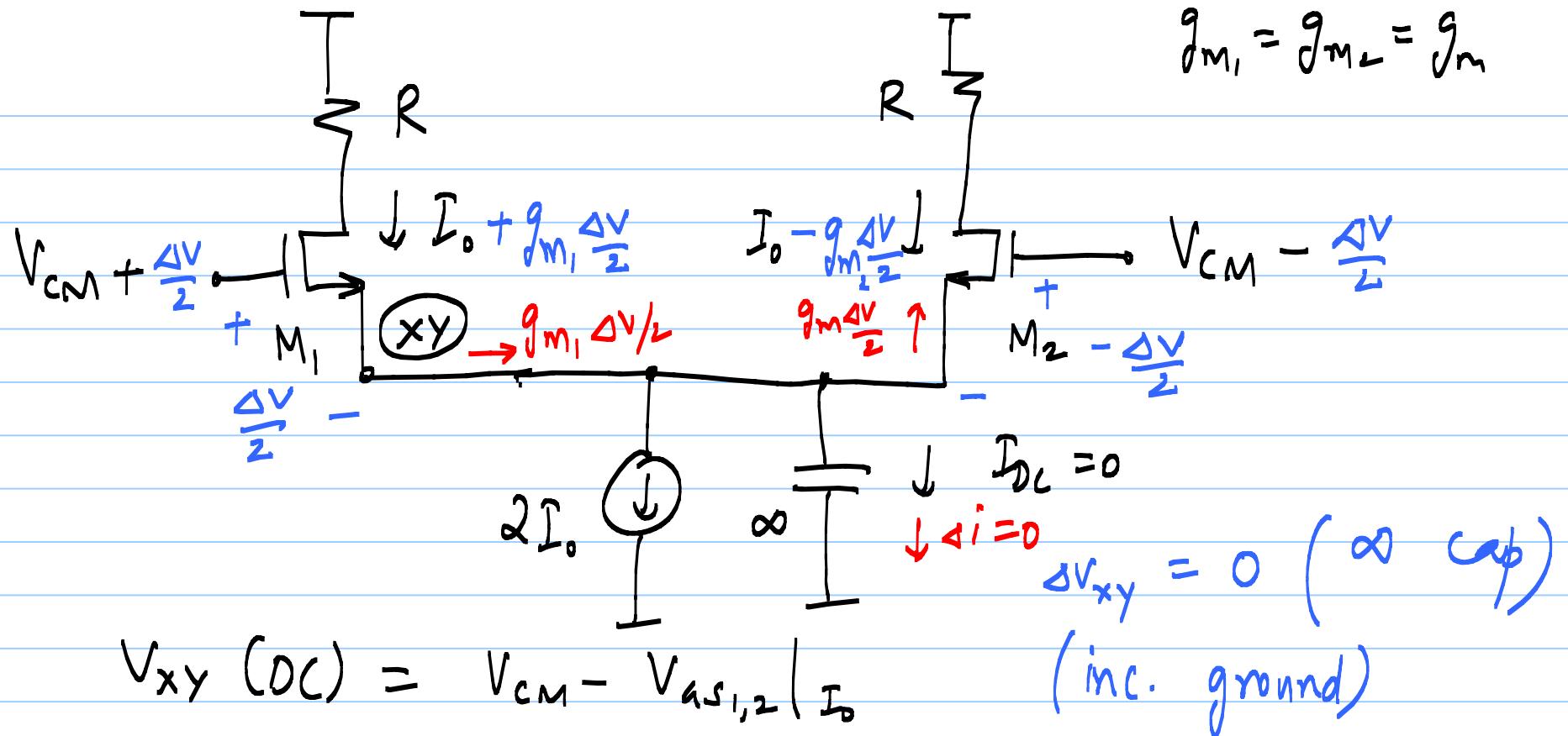


Incl. eqv. circuit

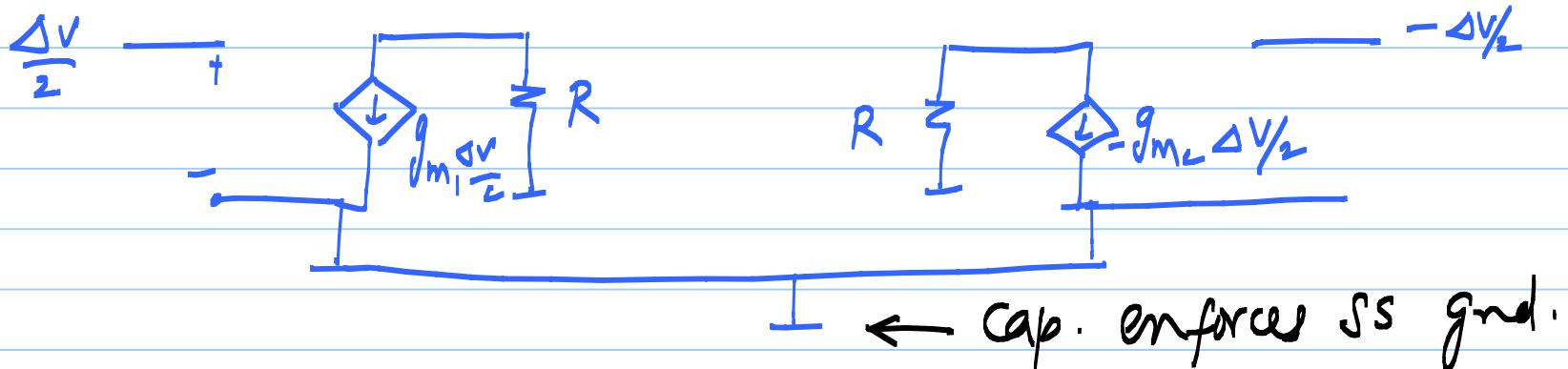

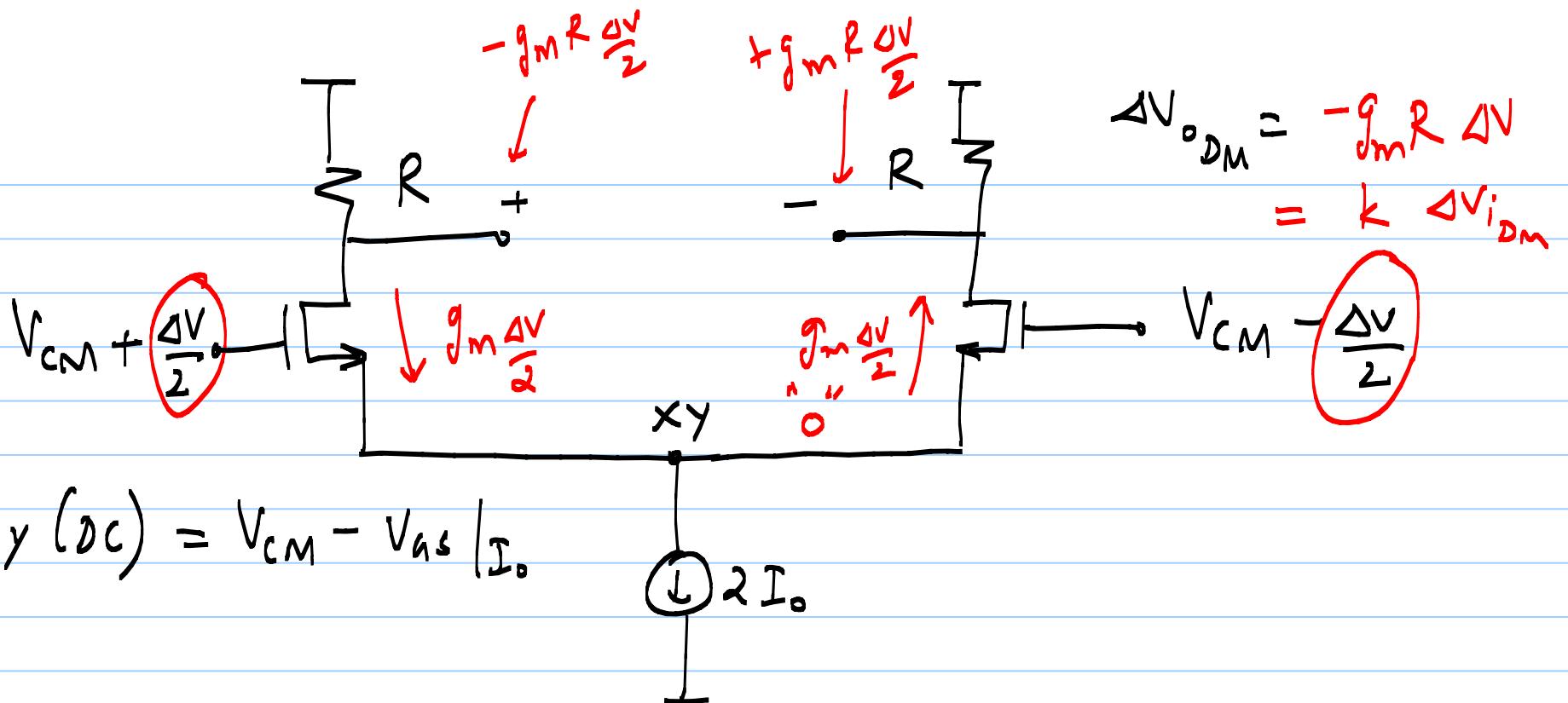

$$V_{XY(DC)} = V_{CM} - V_{GS} |_{I_o}$$

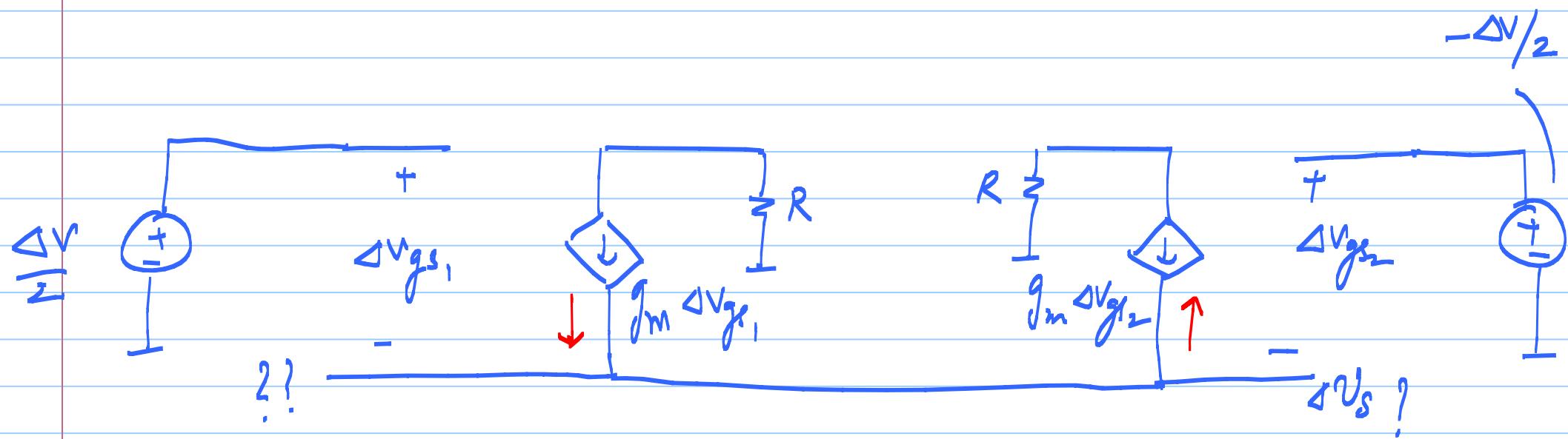

$$g_m \Delta V_{GS1} + g_m \Delta V_{GS2} = 0$$


$$g_m (\Delta V_{g_1} - \Delta V_s) + g_m (\Delta V_{g_2} - \Delta V_s) = 0$$

$$\downarrow$$


$$+ \frac{\Delta V}{2}$$

$$- \frac{\Delta V}{2}$$

$\boxed{\Delta V_s = 0}$

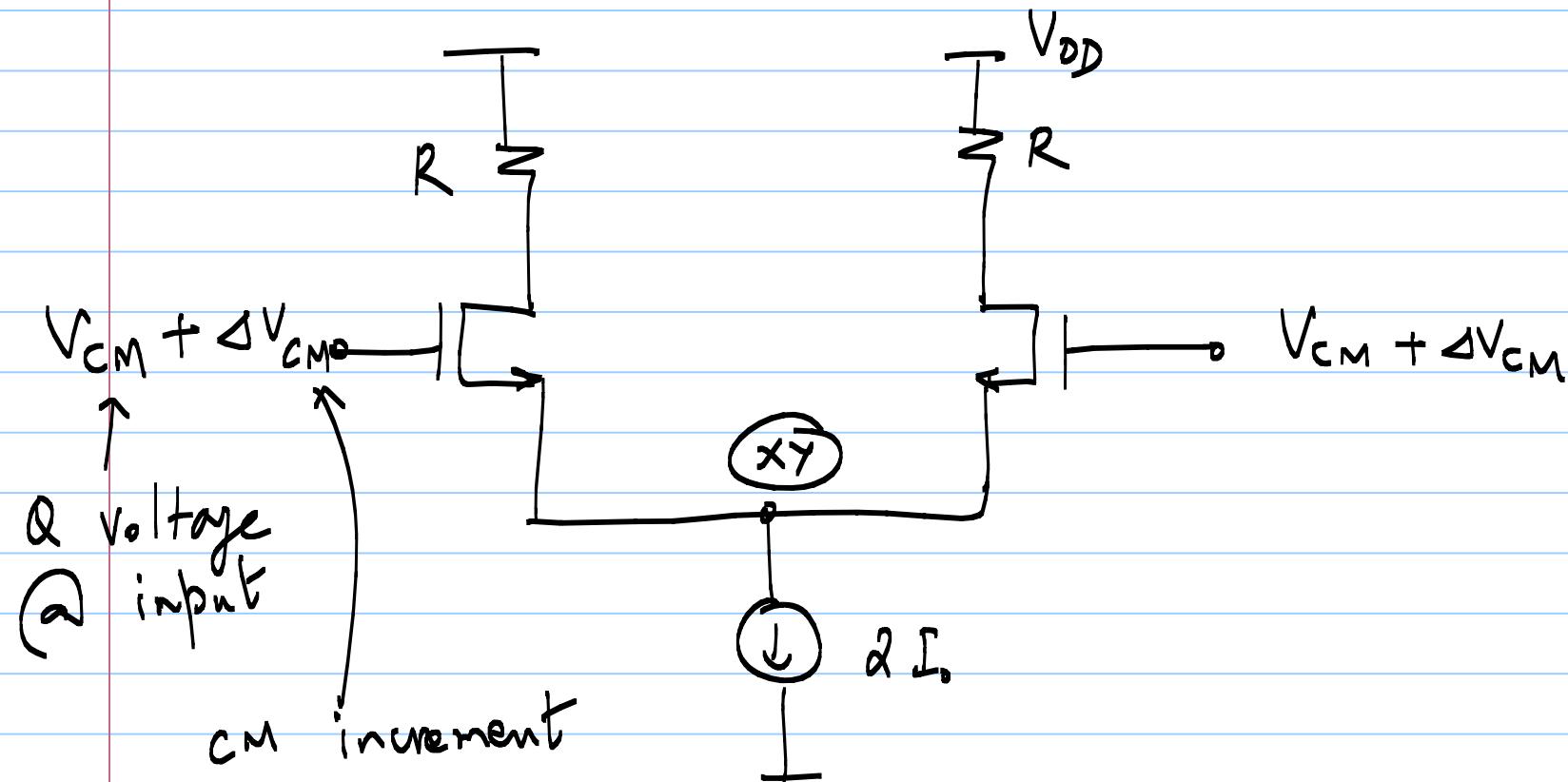

inc. eq. :

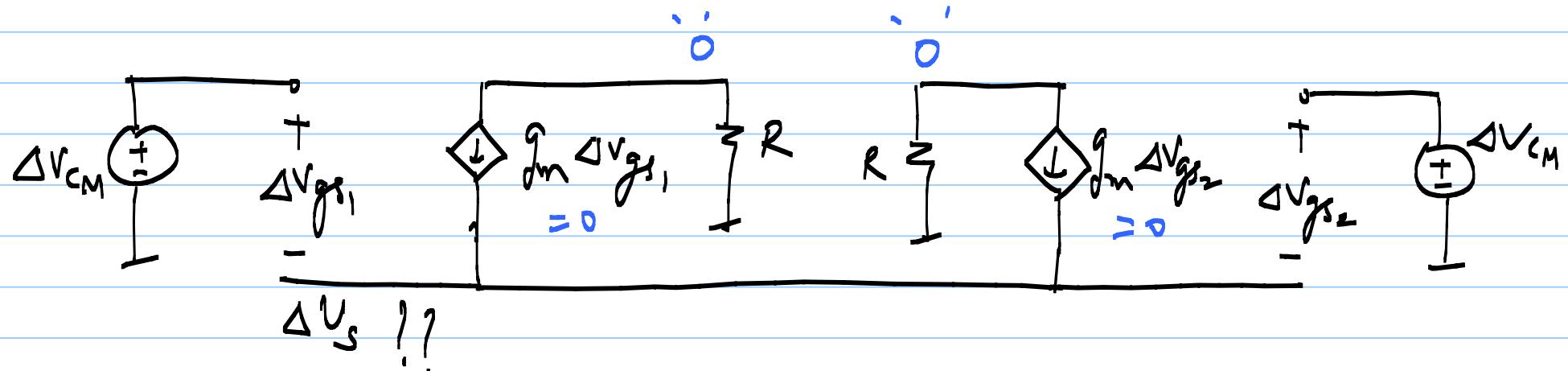

KCL @ Source : $g_m \Delta V_{gs_1} + g_m \Delta V_{gs_2} = 0$

$$g_m (\Delta V_{gs_1} - \Delta V_s) + g_m (\Delta V_{gs_2} - \Delta V_s) = 0$$

$$\Delta V_{gs_1} = \Delta V_{gs_2} = \Delta V_{CM}$$


$$2\Delta V_{CM} = 2\Delta V_s$$

$$\boxed{\Delta V_s = \Delta V_{CM}}$$

$$\Delta V_{gs_1} = \Delta V_{gs_2} = 0$$

$\Delta V_{o_{CM}} = 0 \Rightarrow$ This circuit has 0 CM gain

"Differential Amplifier" we want

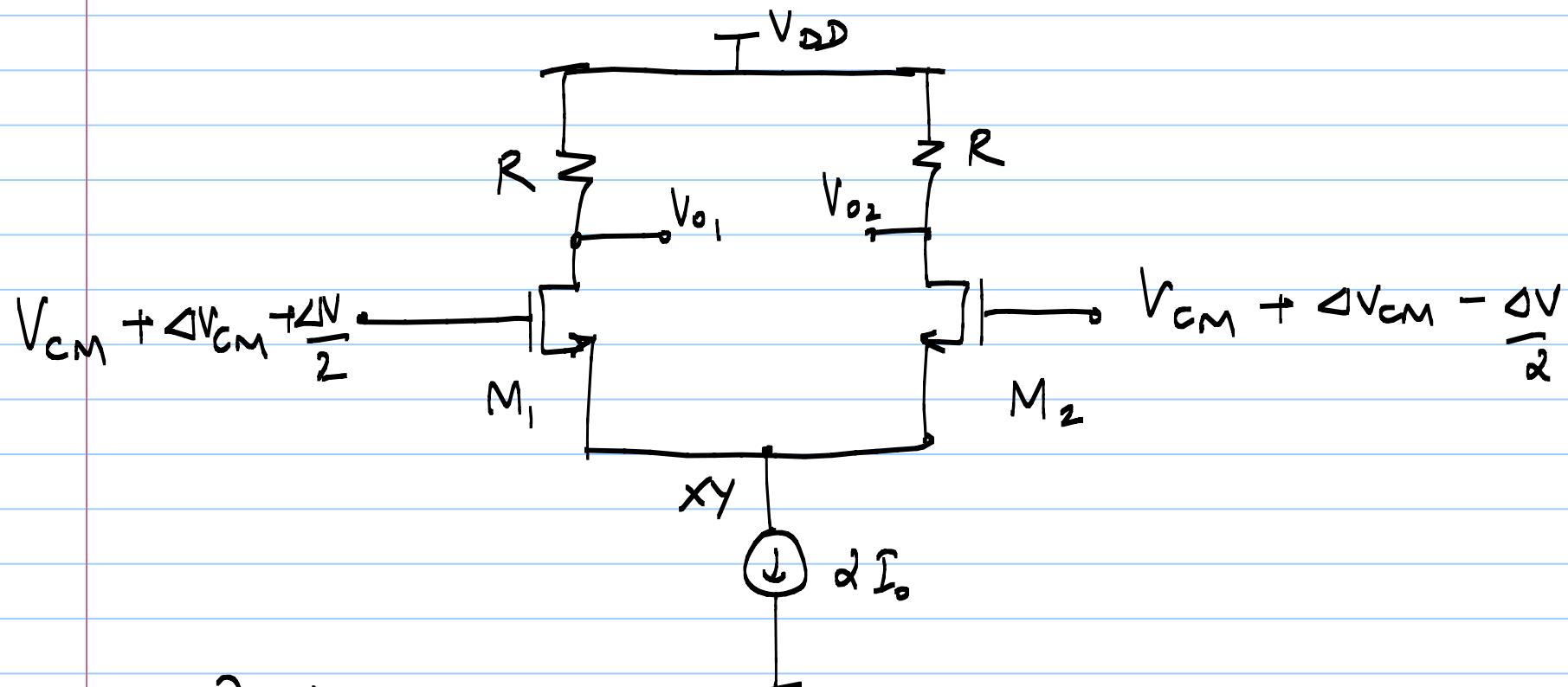

$$\left\{ DC \right\} \rightarrow V_{CM} : I_{D_1} = I_{D_2} = I_o ; \quad V_{xy} = V_{CM} - V_{hs} \Big|_{I_o}$$

$$V_{o_1} = V_{o_2} = V_{DD} - I_o R ;$$


$$2) \Delta V_{CM} : \Delta i_{d_{1CM}} = \Delta i_{d_{2CM}} = 0$$

$$\Delta V_{01_{CM}} = \Delta V_{02_{CM}} = 0$$

$$\Delta V_{xy} = \Delta V_{CM}$$


$$\begin{array}{r|l} 29 & 1 \quad 20 \\ \hline & \end{array}$$

Lecture 32

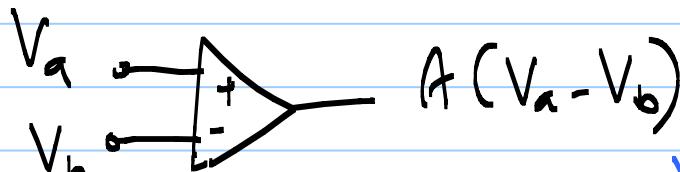


$$V_{CM} = \frac{V_a + V_b}{2}$$


$$\Delta V = V_a - V_b$$

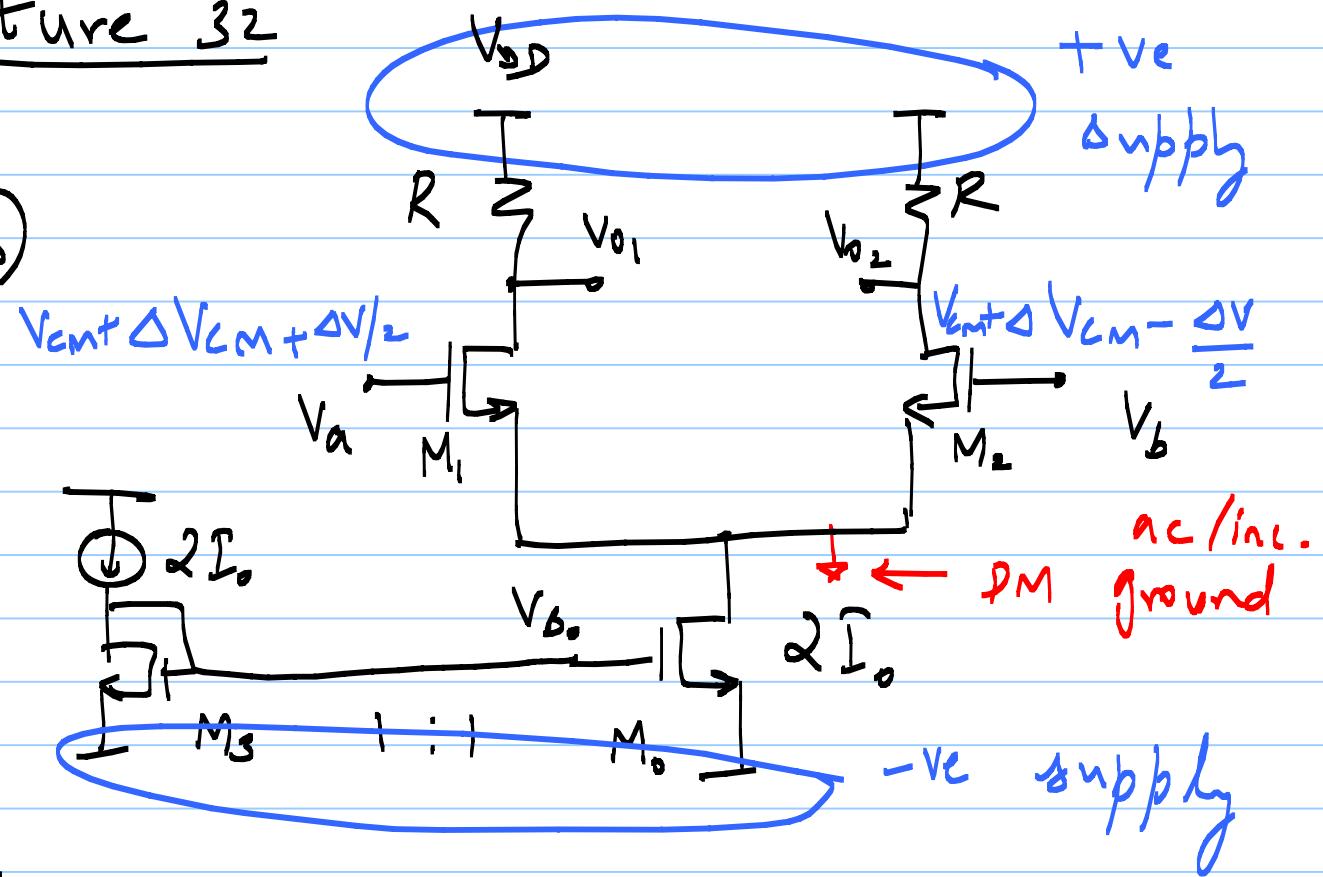


DM eq circuit

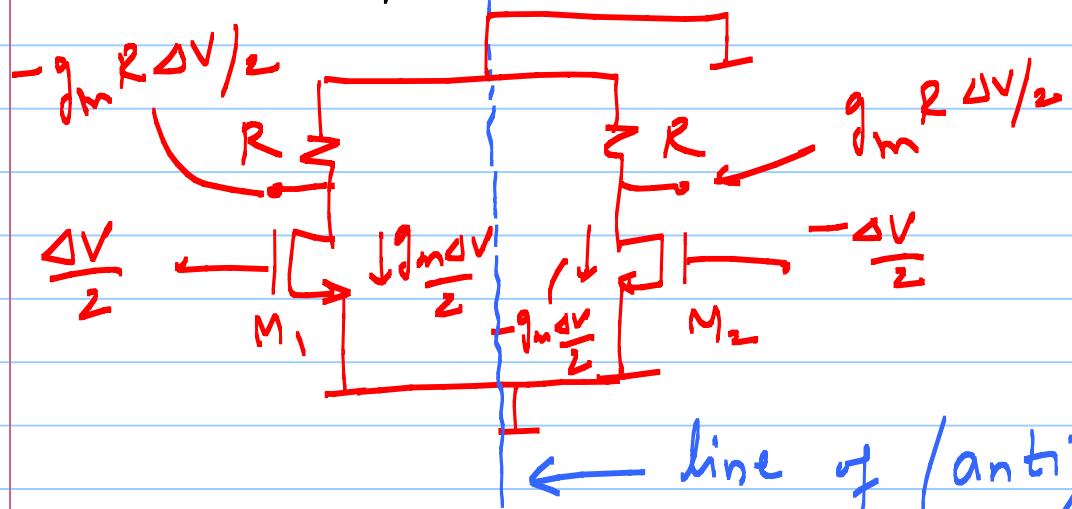

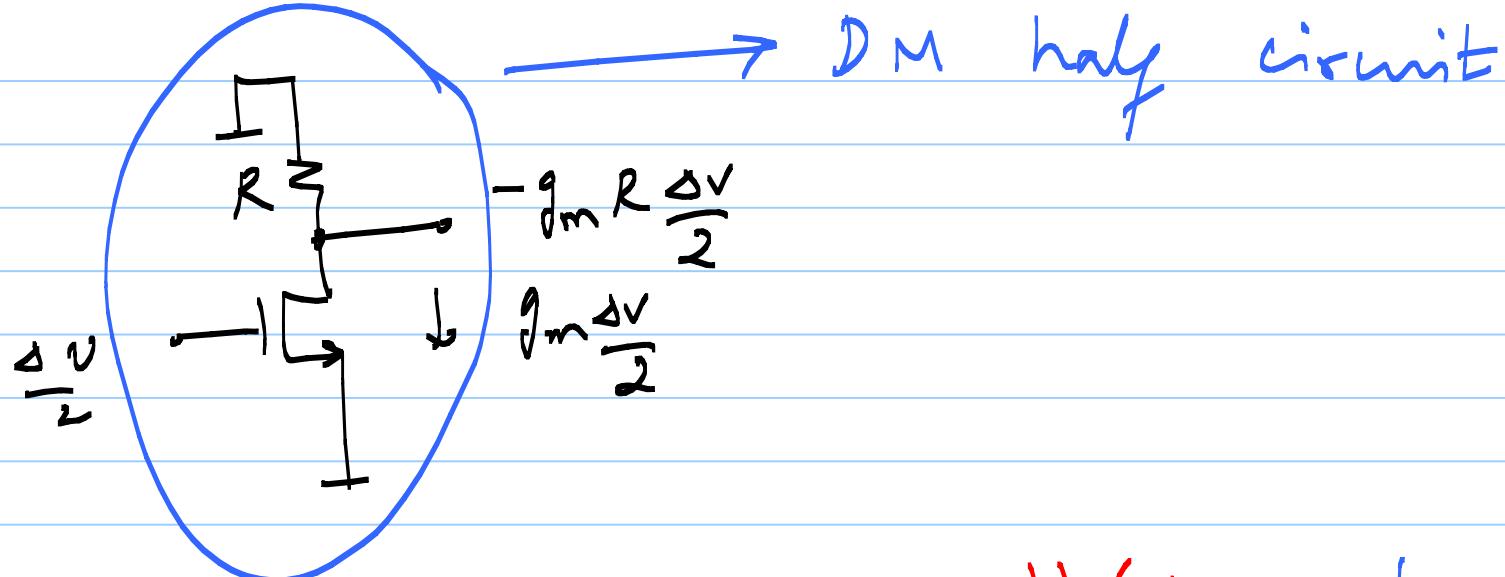
"V's and i's on each
"half-circuit" have
equal magnitude & opposite
phase




CM eq. cir.

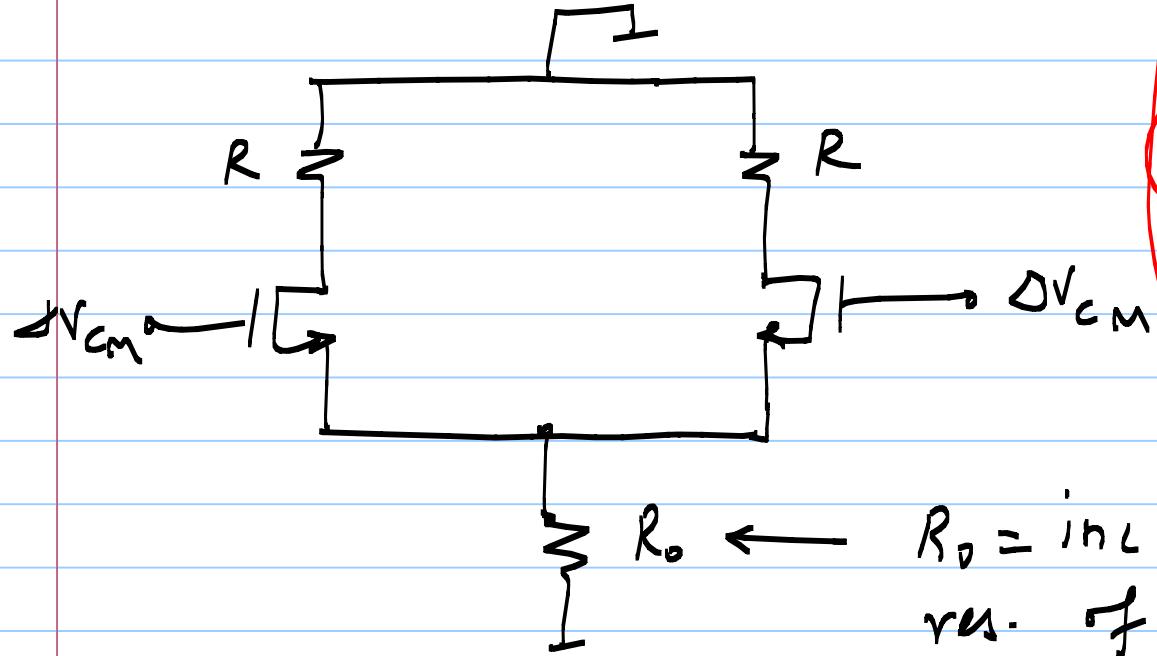


CM H.C.

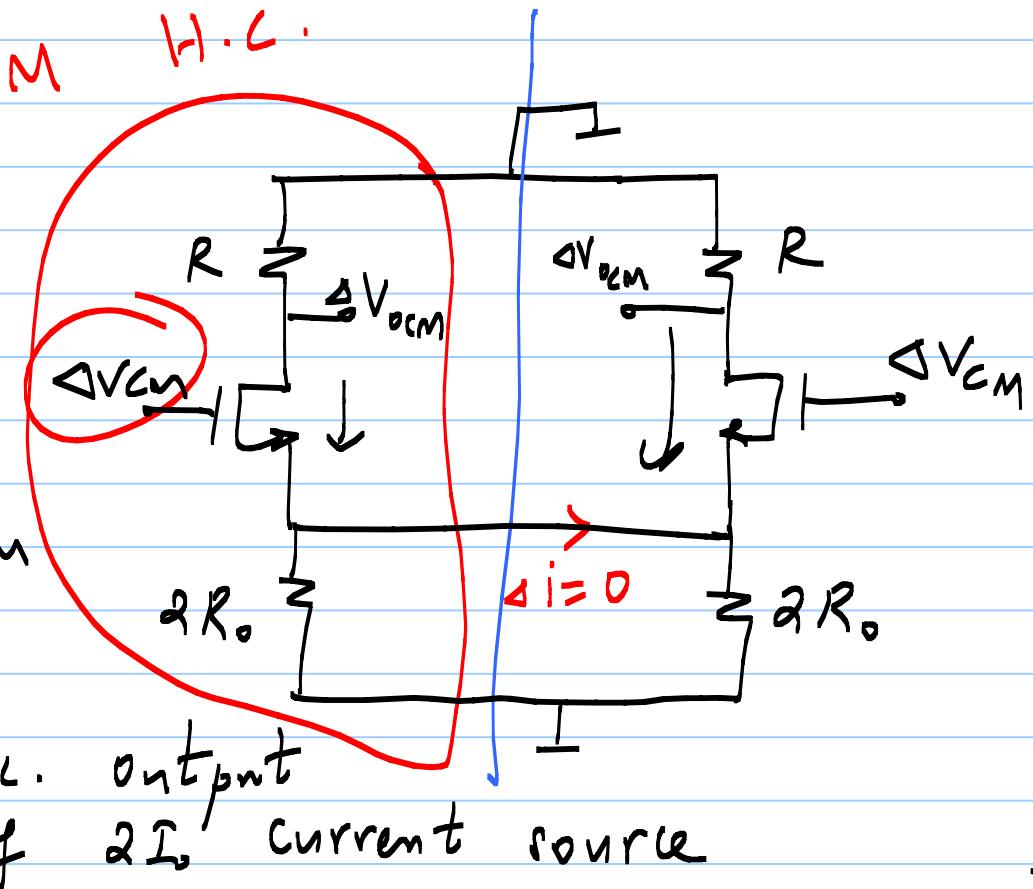


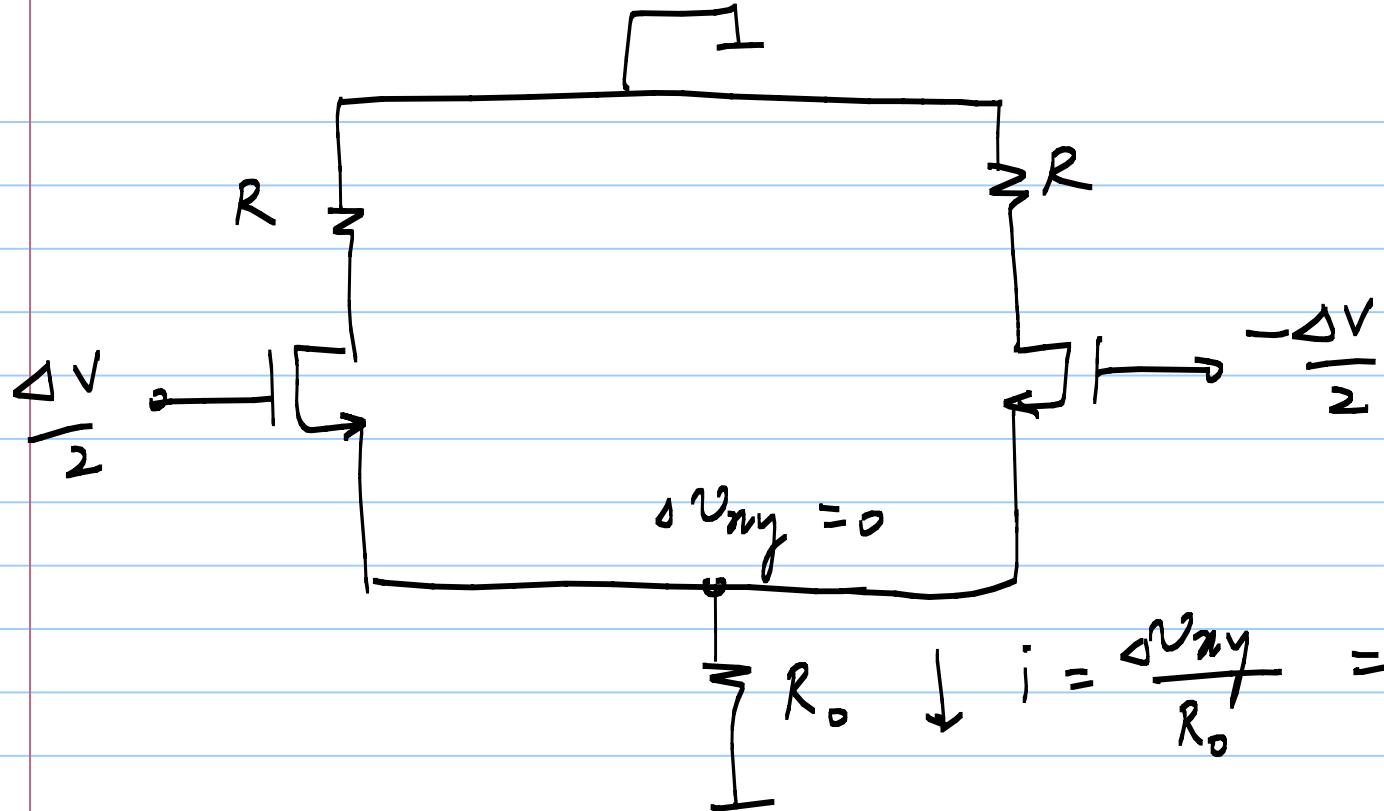

$i = \frac{\Delta V_{xy}}{R_0} = 0$ is the only possible state of the DM cir.

$$\Delta V_{CM} = ?$$

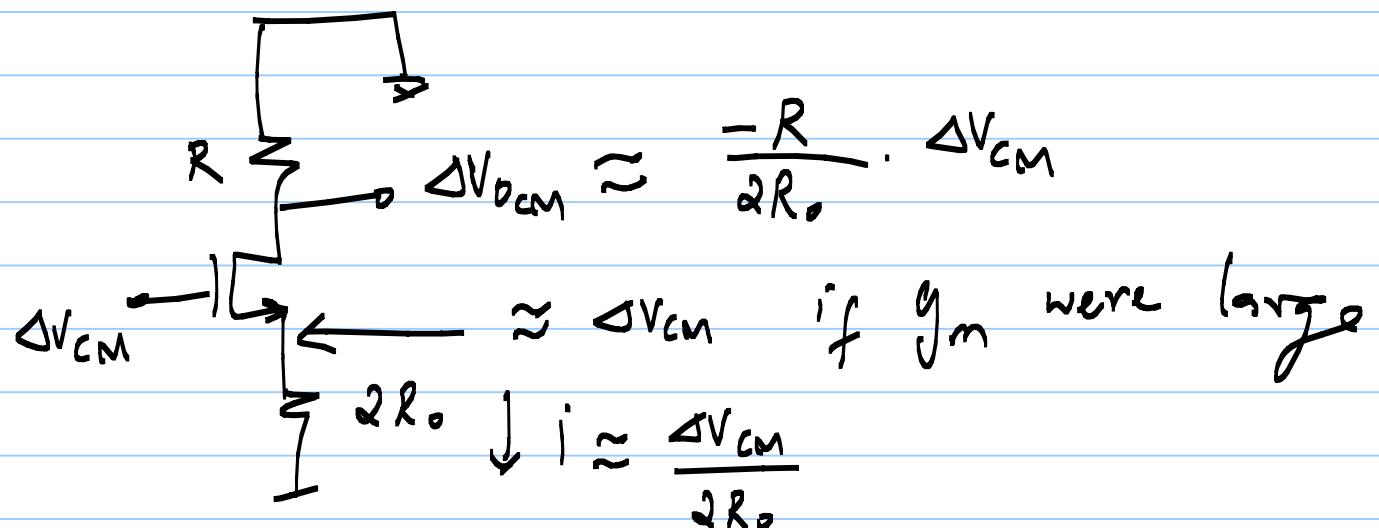

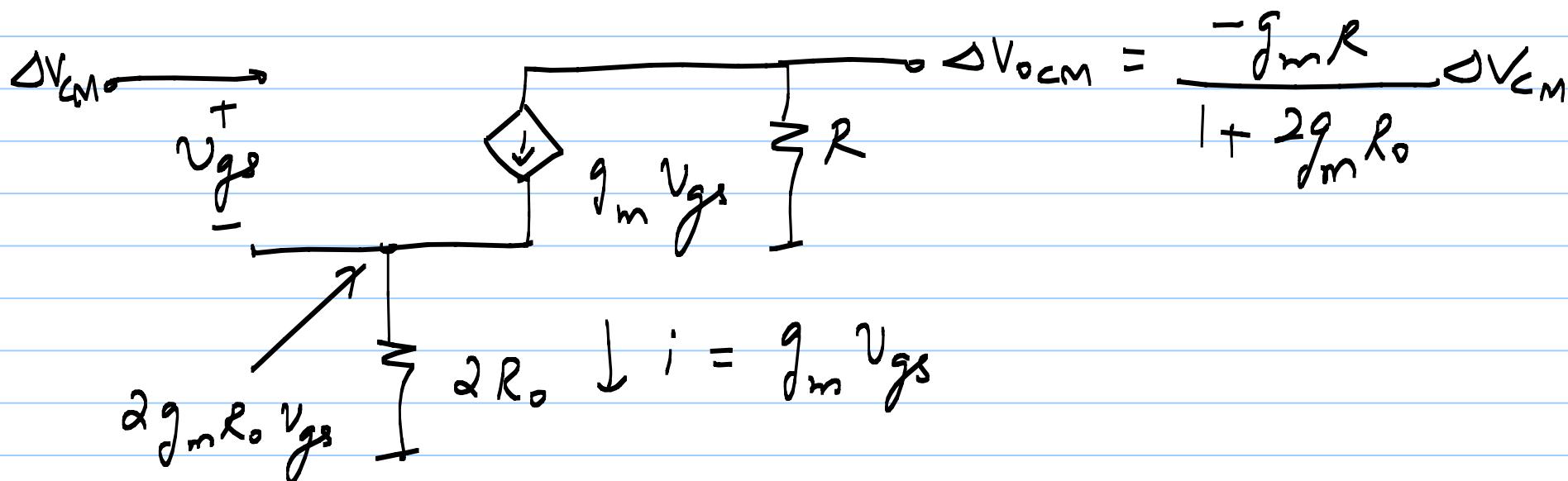

$$A_{DM} = -g_m R$$

$$A_{CM} = \frac{-g_m R}{1 + 2g_m R_0}$$


$$CMRR = \left| \frac{A_{DM}}{A_{CM}} \right|$$

Common Mode

Rejection Ratio

$$CMRR_{dB} = 20 \log \left| \frac{A_{DM}}{A_{CM}} \right|$$

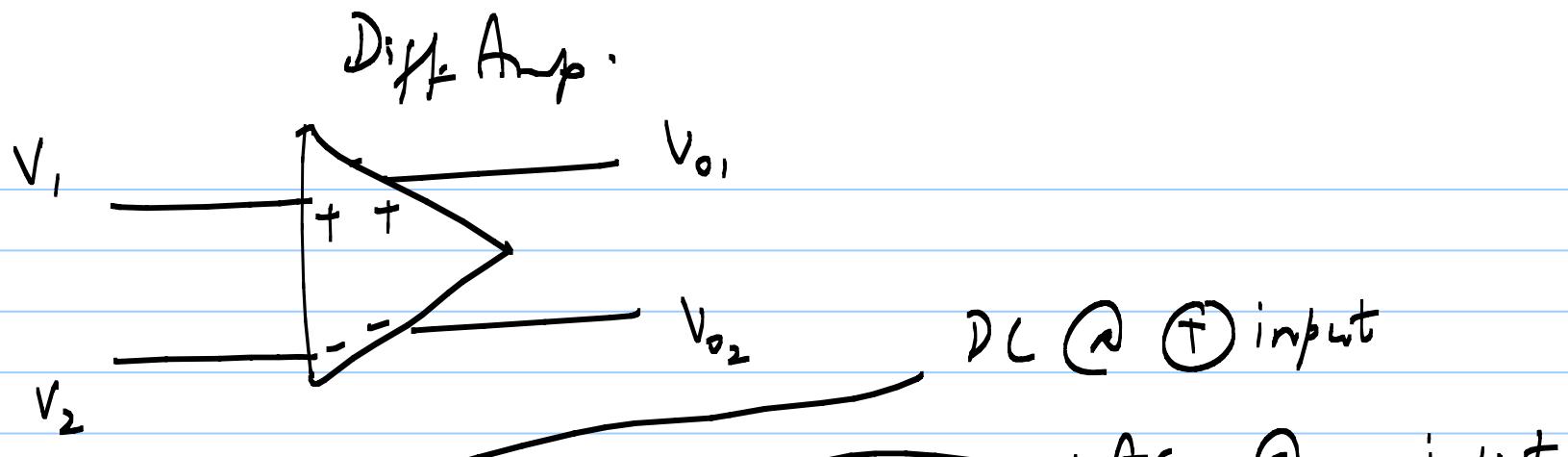large CMRR = "good" differential amplifier



e.g. $V_1 = 1V + 2mV \sin \omega t + 5mV (DC)$

$$V_2 = (.01V + 1mV \sin \omega t + 5mV (DC))$$

$$V_{iCM} = \frac{V_1 + V_2}{2} = 1.005V + 1.5mV \sin \omega t + 1\mu V \cos \omega t$$

$$V_{iDM} = \frac{V_1 - V_2}{2} = -0.005V + 0.5mV \sin \omega t + 2\mu V \cos \omega t$$

$$V_1 = V_{iCM} + V_{iDM} ; V_2 = V_{iCM} - V_{iDM}$$

$$V_{iDC} = V_{iCM} = 1.005V \rightarrow 1.01V$$


$$v_{CM} = 1.5mV \sin \omega t$$

$$\Delta V_{DM} = -0.005$$

$$v_{DM} = 0.5mV \sin \omega t$$

06/10/2020

Lecture 33

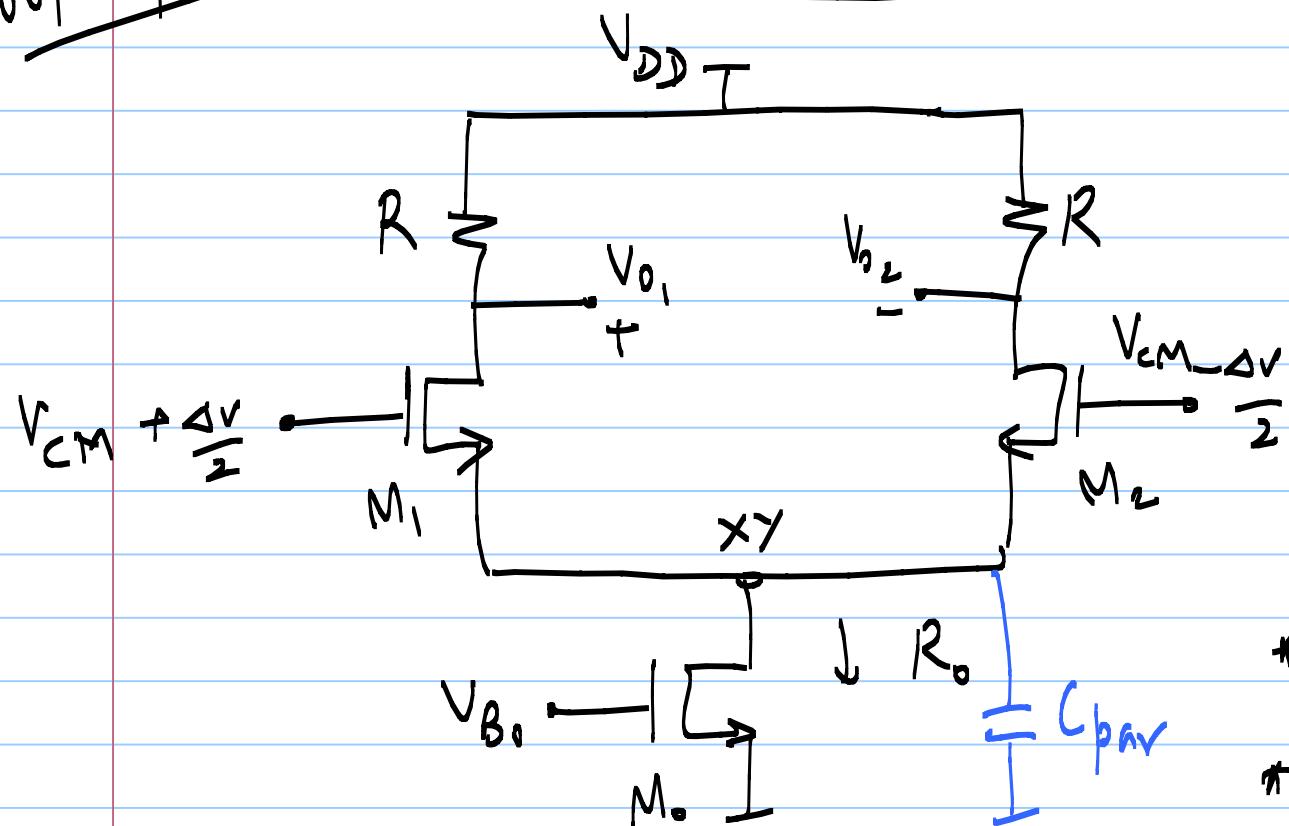

A_{DM} is large ($-g_m R$)

A_{CM} is small (dep. on R_o)

CMRR is large


We want to

- * have a single ended o/p
- * have more gain

* Ensure C_{par} is as low as possible

Possibilities

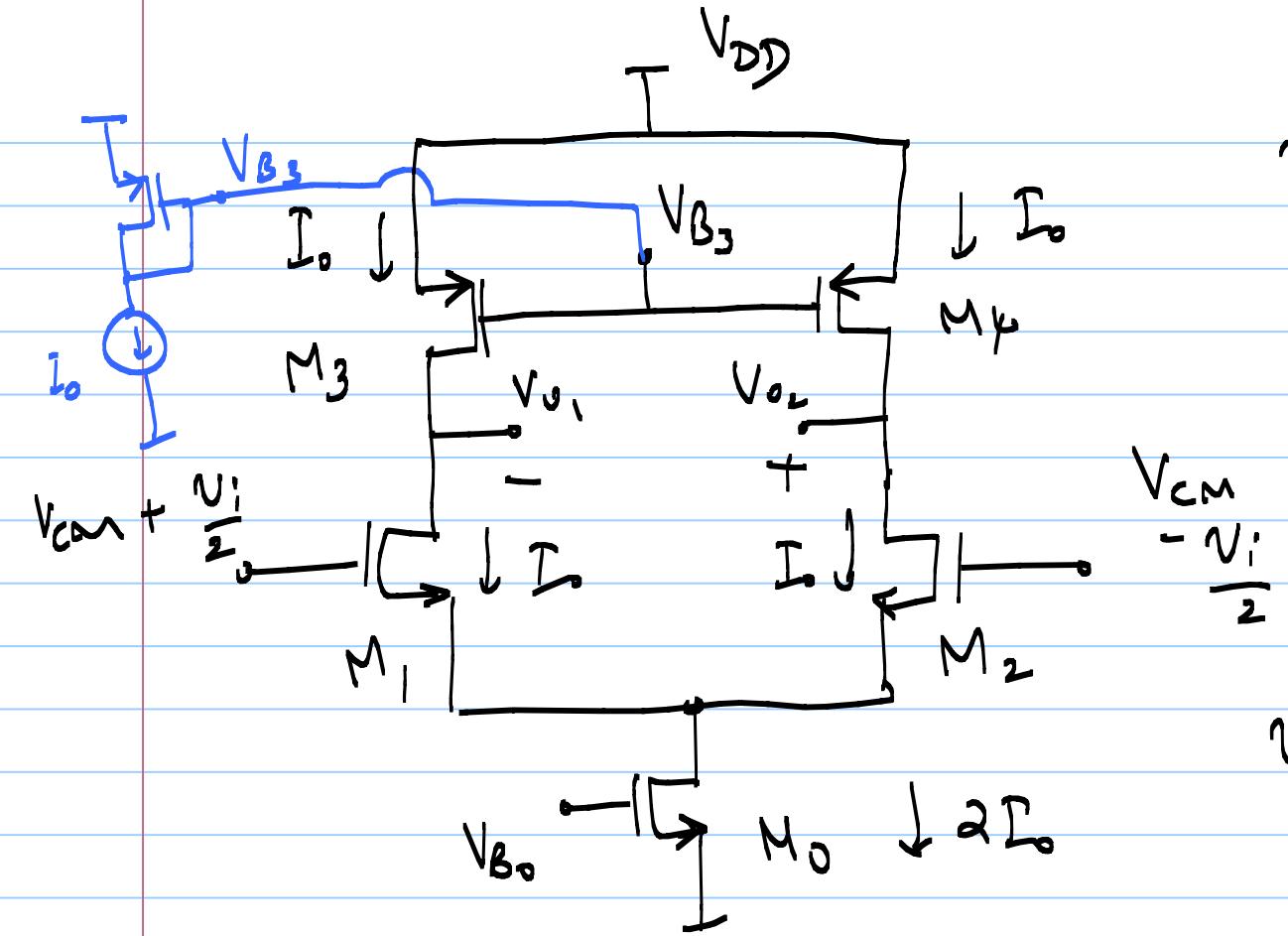- * SE o/p - discard V_{O_1} or V_{O_2} {not good}
- * More gain - active load



* Set V_{B_3} so that

$$I_{D_3} = I_{D_4} = I_o$$


$$V_{o_1} = -g_{m_1} (r_{ds_1} || r_{ds_3}) \cdot \left(\frac{V_i}{2}\right)$$

$$V_{o_2} = -g_{m_2} (r_{ds_2} || r_{ds_5}) \cdot \left(-\frac{V_i}{2}\right) \\ = +g_{m_1} (r_{ds_1} || r_{ds_3}) \cdot \frac{V_i}{2}$$

$$V_o = V_{o_2} - V_{o_1}$$

$$= +g_{m_1} (r_{ds_1} || r_{ds_3}) \cdot V_i$$

gain similar to
CSA with active load

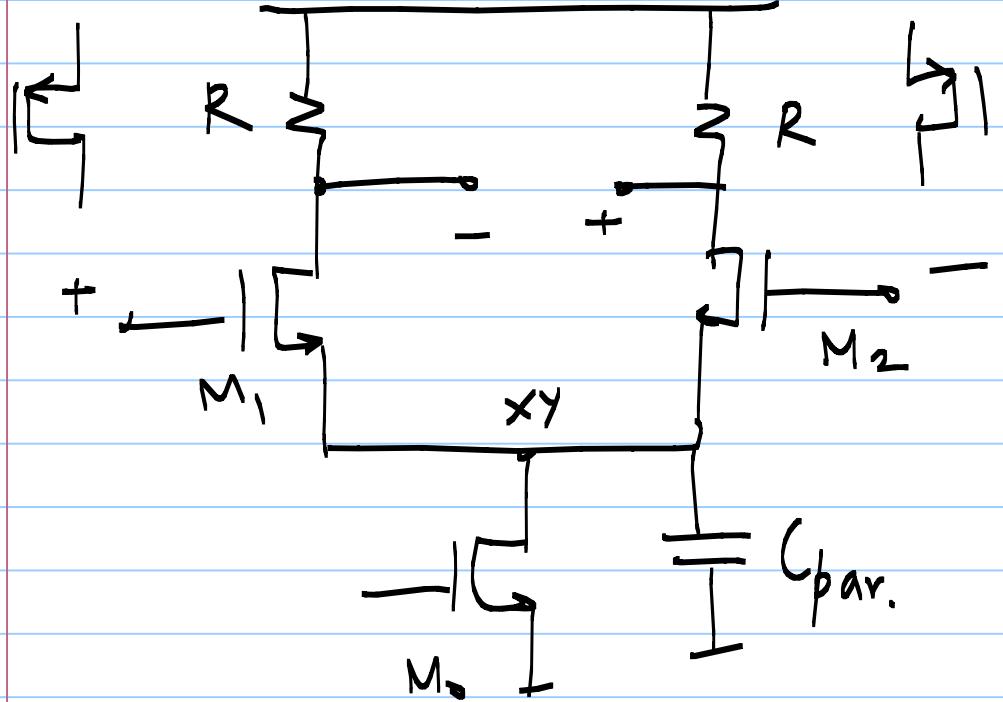

- * C_{par} = "parasitic" cap
(undesired cap)
- * Normally C_{par} @ xy
dominated by device cap.
($M_0, M_1 \& M_2$)
(Not $M_3 \& M_4$)


* C_{par} does not affect DM performance
significantly

* C_{par} affect CM performance


$$\text{e.g. } R_o \left(r_{ds} \right) = \infty$$



original $A_{CM} = 0$ (without C_{par})

With C_{par} :

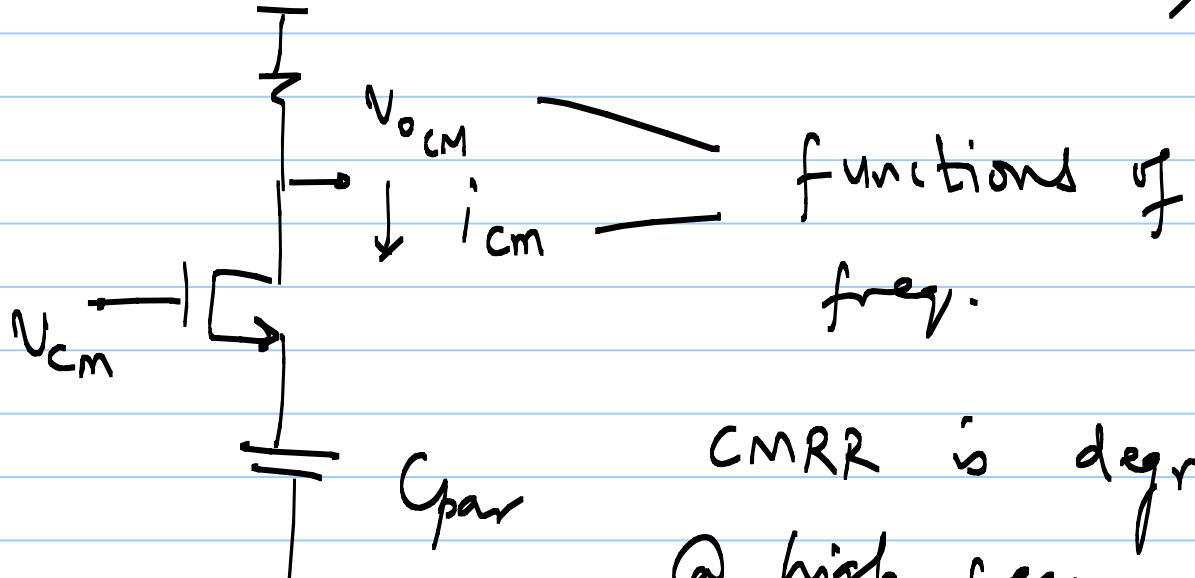

CMRR is degraded
at high freq.


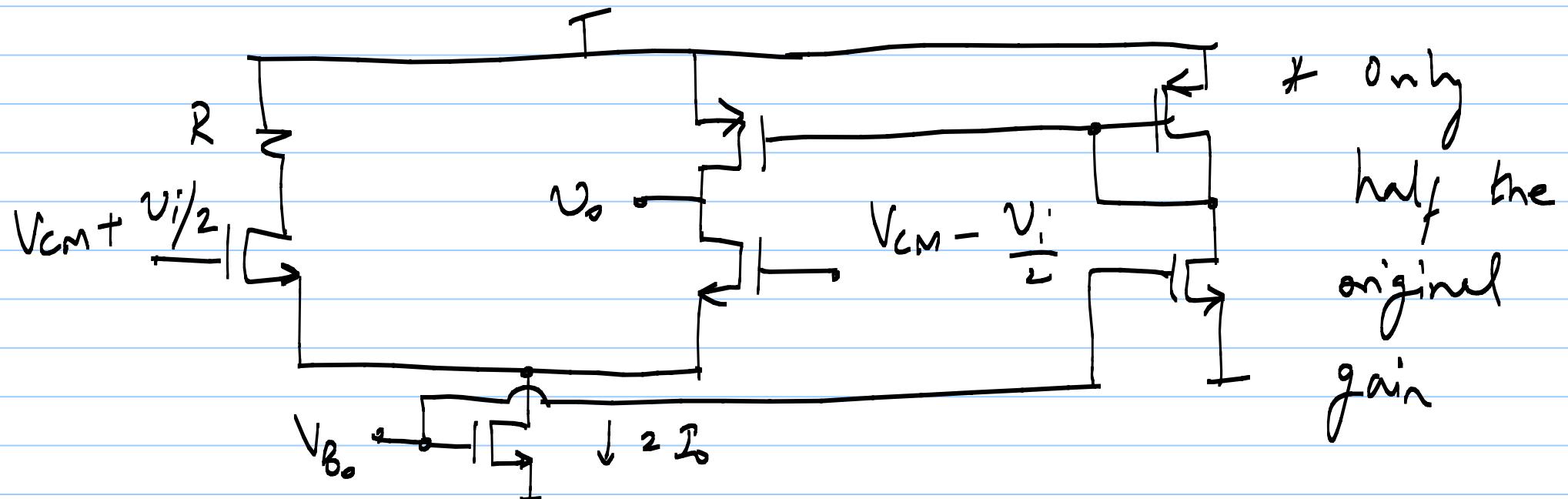


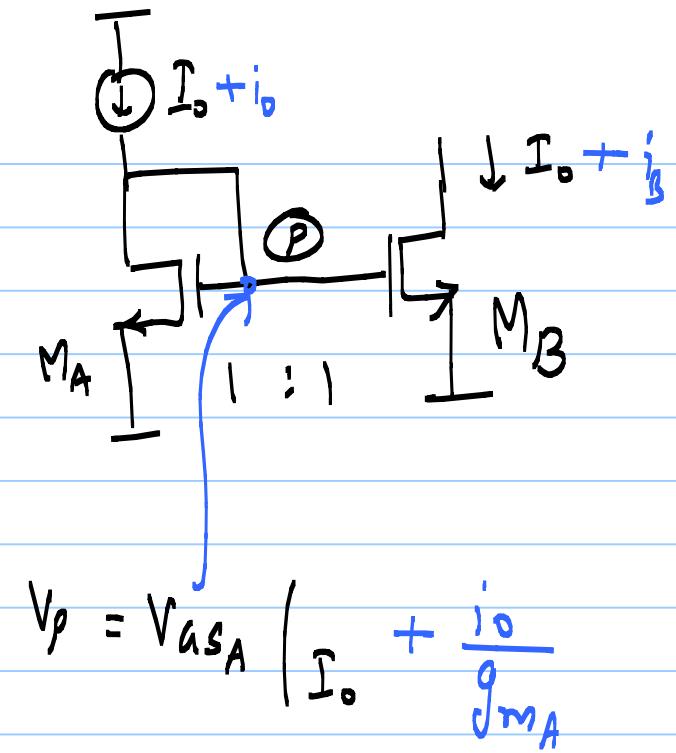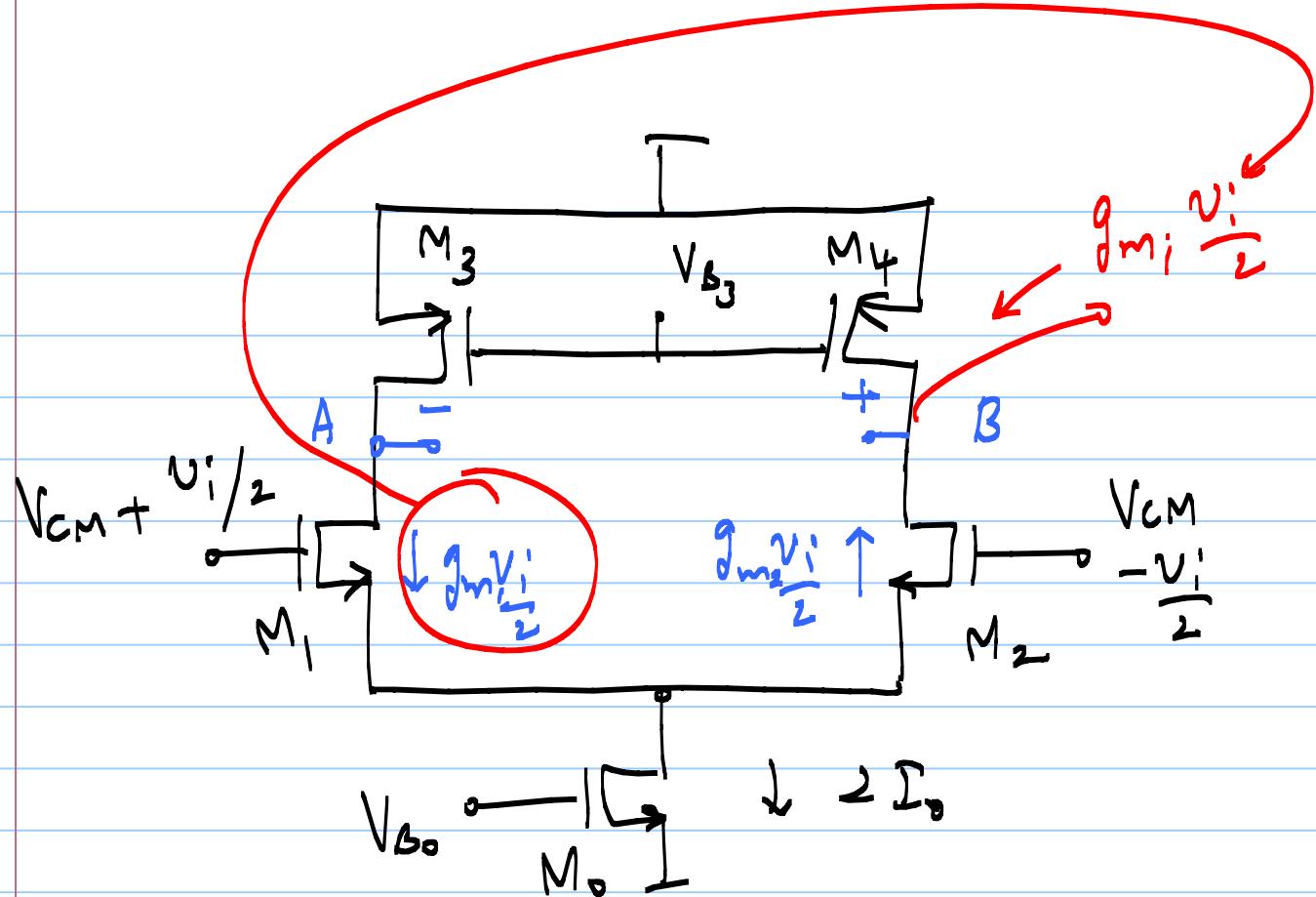


$$I_{D_B} = I_0 + \frac{i_0 \cdot g_{m_B}}{g_{m_A}}$$

$$i_3 = i_0 \text{ here } (1:1 \text{ cm})$$


C.G.A.

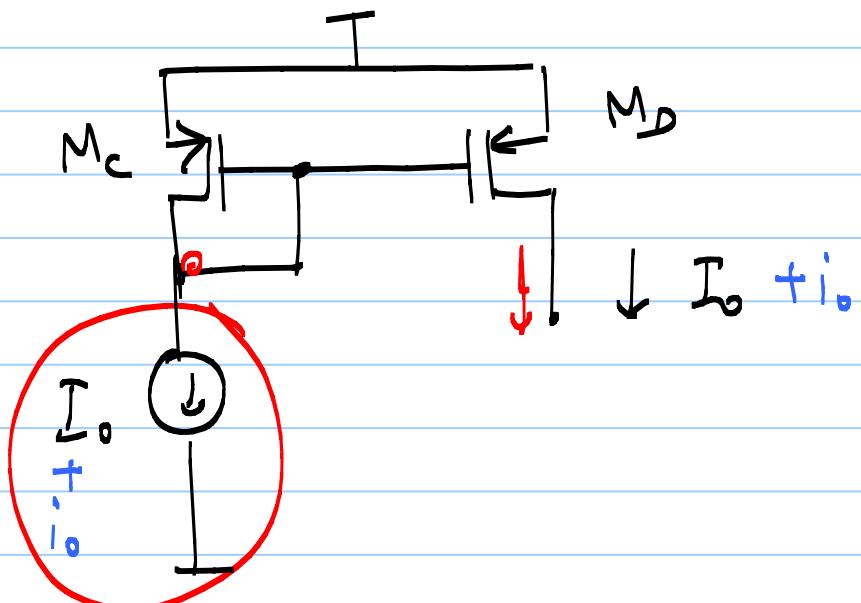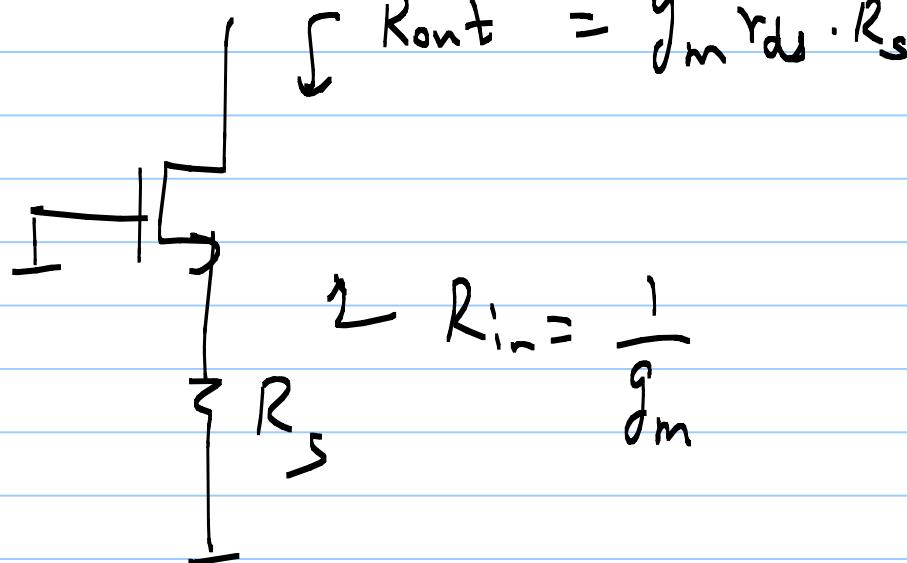

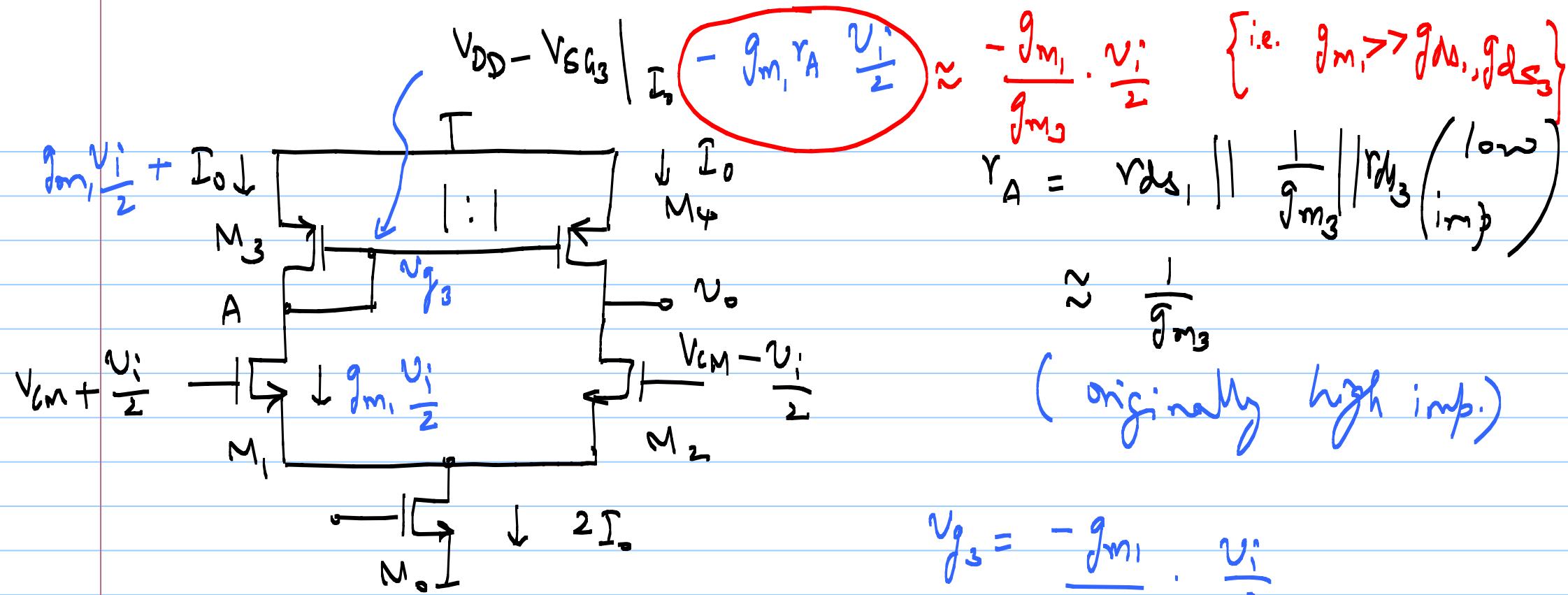* Repurpose M_3 & M_4
to form $M_c - M_d$ C.M.



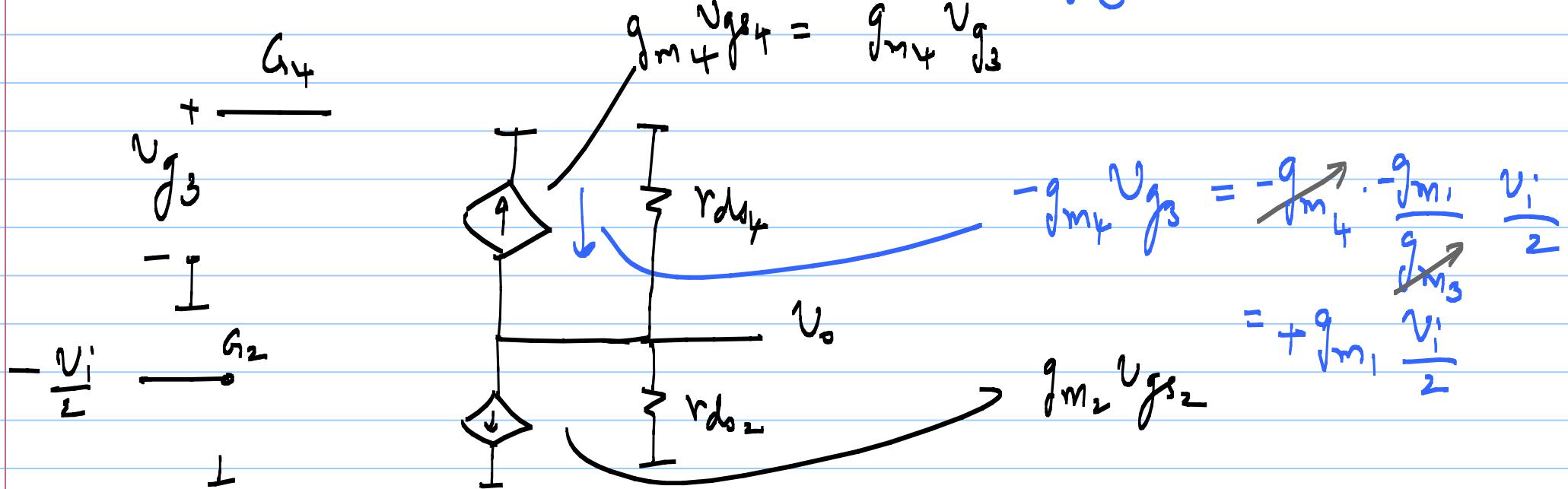
$$v_{g3} = - \frac{g_{m_1}}{g_{m_3}} \cdot \frac{V_i}{2}$$



7/10/20

Lecture 34

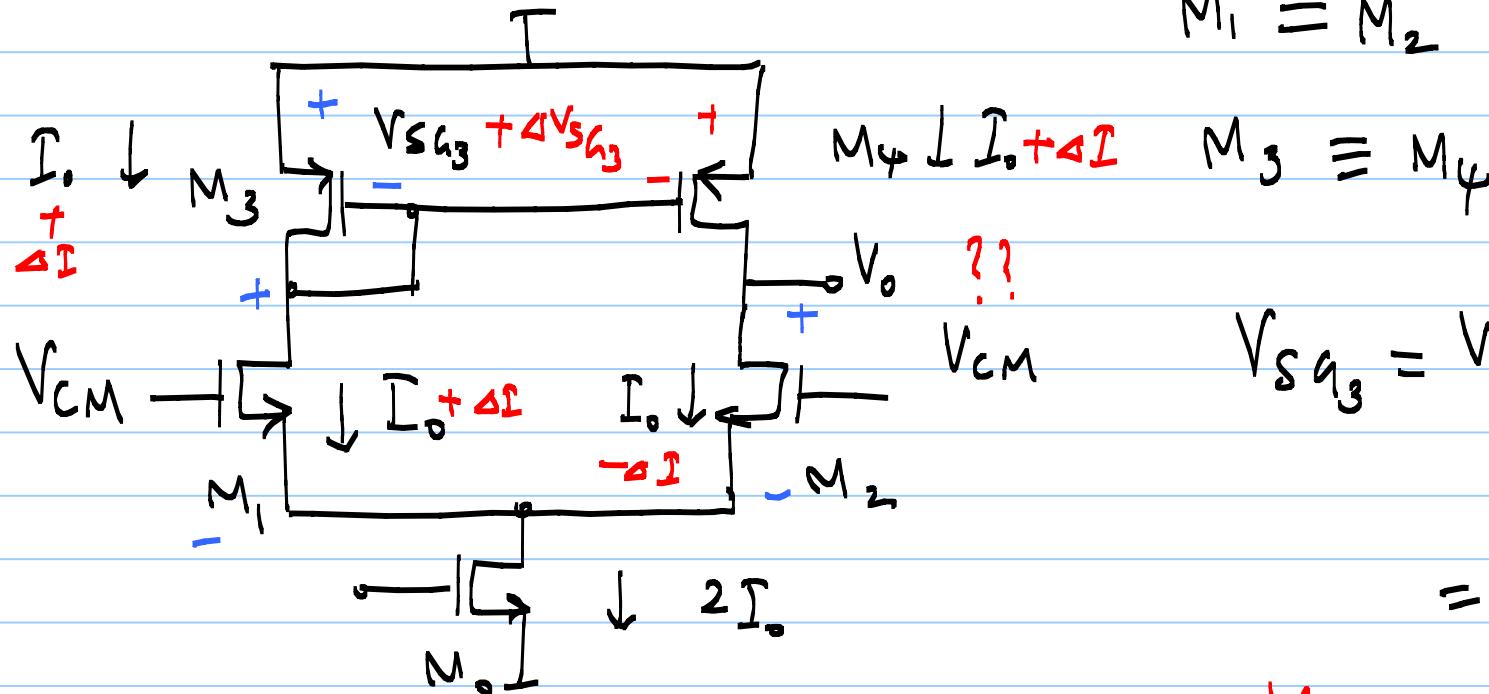

$$M_1 \equiv M_2$$

$$V_{SG_3} = V_T_3 + \sqrt{\frac{2I_0}{\mu_p C_{ox} \left(\frac{W}{L}\right)_3}}$$

$$= V_{SG_4}$$

$$V_{D_1} = V_{DD} - V_{SG_3} - \Delta V_{SG_3} \quad ?? = 0$$

$$\Delta I = 0 ; V_{O_{CM}} = V_D - V_{SG_3}$$

$$I_{D_1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS_1} - V_{Tn})^2 (1 + \lambda V_{DS_1})$$

$$I_{D_2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{GS_2} - V_{Tn})^2 (1 + \lambda V_{DS_2})$$


Case 2: λ's are non-zero

DM SS analysis


$$\frac{U_o}{U_i} = ?$$

$$\frac{U_i}{2} \xrightarrow{G_1} +$$

$$I$$

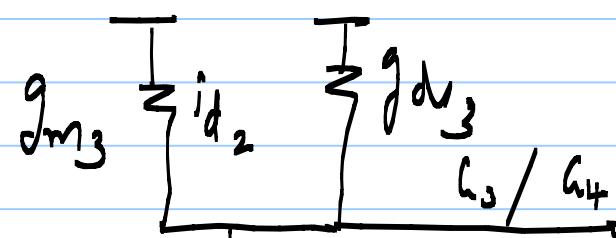


(A)

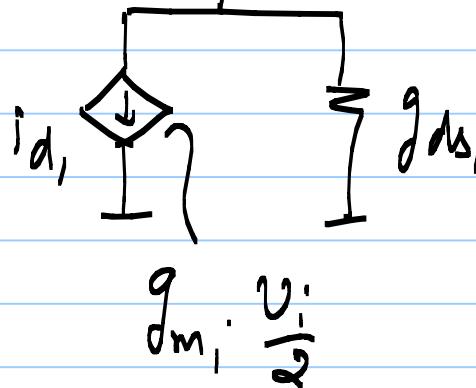


$$g_m_1 \cdot \frac{U_i}{2}$$

$$g_{m_4} \cdot U_A$$

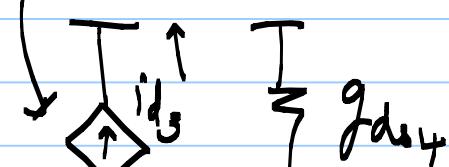

(B)

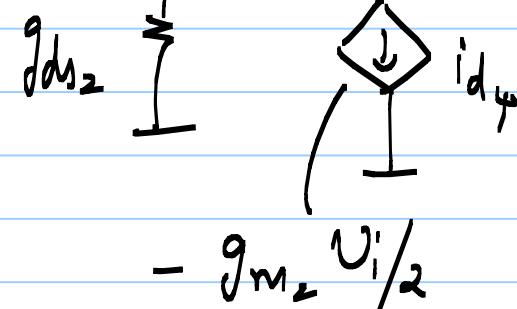

$$\frac{G_2}{T} - \frac{U_i}{2}$$

$$I$$

$$U_A = - \frac{g_{m_1}}{g_{m_3} + g_{d_{u_1}} + g_{d_{u_3}}} \cdot \frac{U_i}{2}$$

$$i_{d_3} = g_{m_4} \cdot U_A = - \frac{g_{m_4}}{g_{m_3} + g_{d_{u_1}} + g_{d_{u_3}}} \cdot g_{m_1} \cdot \frac{U_i}{2}$$

$$\approx -g_{m_1} \frac{v_i}{2} \quad \text{if } g_{m_3} > g_{ds_1} + g_{ds_3}$$


$$v_o = -\left(i_{d_3} + i_{d_4}\right) \cdot \frac{1}{g_{ds_2} + g_{ds_4}}$$

$$= -\left(-g_{m_1} \frac{v_i}{2} - g_{m_2} \frac{v_i}{2}\right) \cdot \frac{1}{g_{ds_2} + g_{ds_4}}$$


$$= \frac{g_{m_1}}{g_{ds_2} + g_{ds_4}} \cdot v_i$$

$$\frac{v_o}{v_i} = \frac{g_{m_1}}{g_{ds_2} + g_{ds_4}} = g_{m_1} (r_{ds_2} || r_{ds_4})$$

"Single-Stage Opamp"

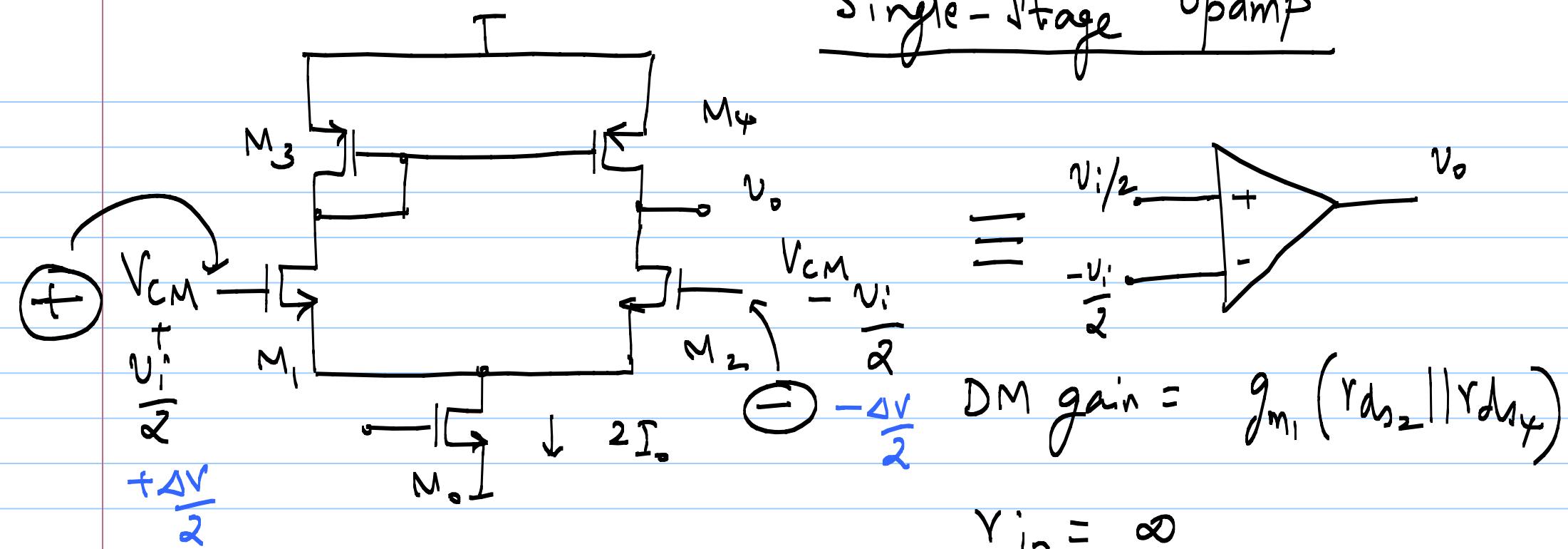

|||


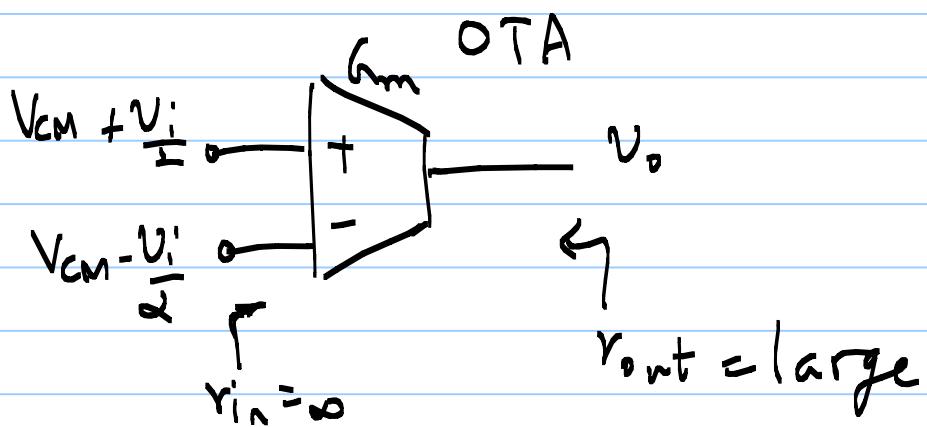


$$r_{out} = r_{ds_2} || r_{ds_4}$$

(large)

$$G_m = g_{m_1}$$

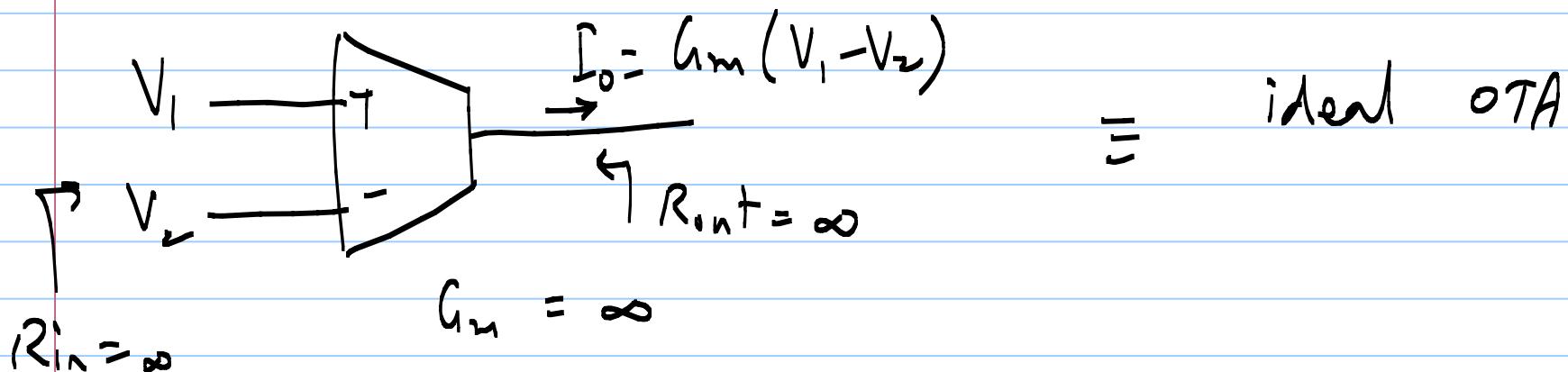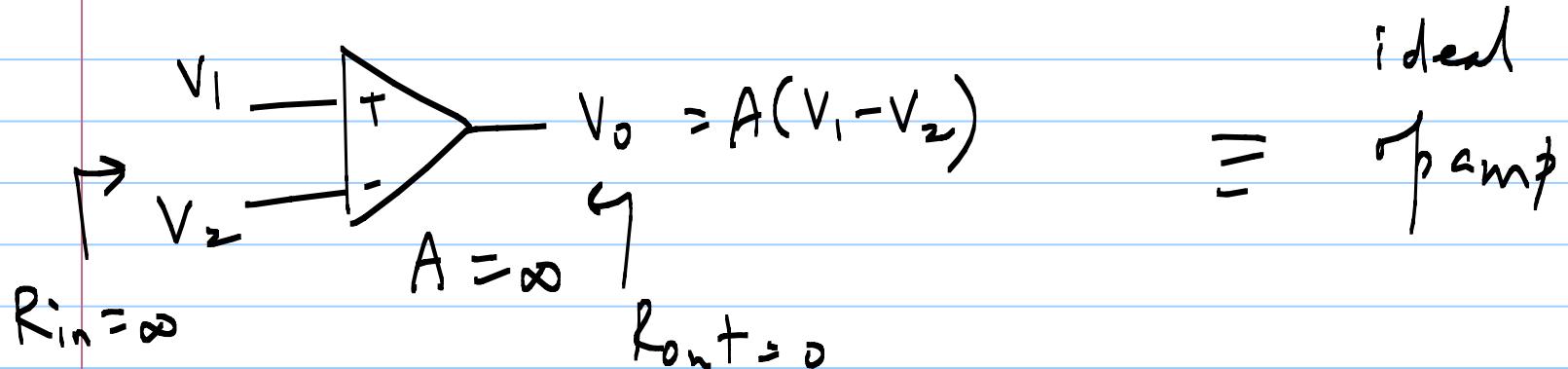OTA = operational Transconductance Amplifier




$$\text{gain} = \frac{V_o}{V_1 - V_2} = g_m R_{out} + t = \text{large}$$

8/10/2020

Lecture 35

"Single Stage 'Pamp'"

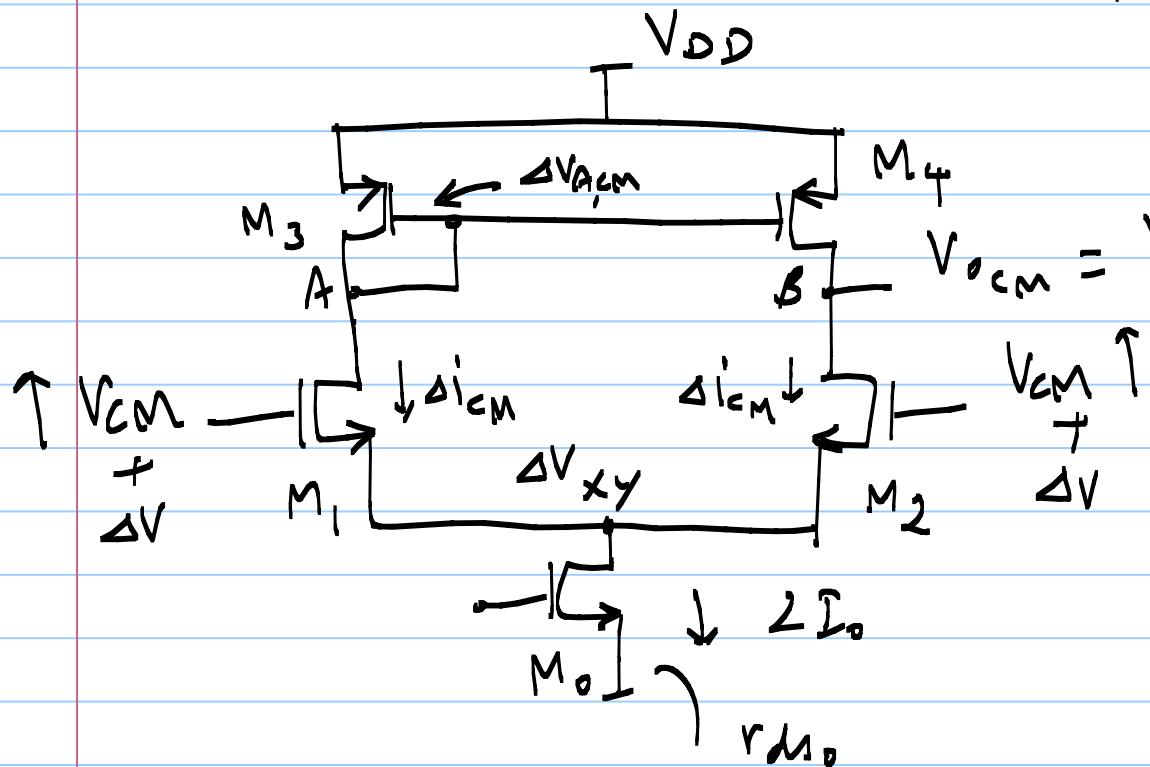

$$V_{OCM} = V_{DD} - V_{SG3} + \Delta V_{OCM}$$

$$\frac{\Delta V_{OCM}}{\Delta V} = A_{CM} \left\{ HW \right\}$$


V_{CM} = Input CM level \rightarrow range?

V_{OCM} = Output CM level \rightarrow range?

I_{CMR} - input CM range

O_{CMR} - output CM range

I_{CMR} : 1) keep $\downarrow V_{CM}$

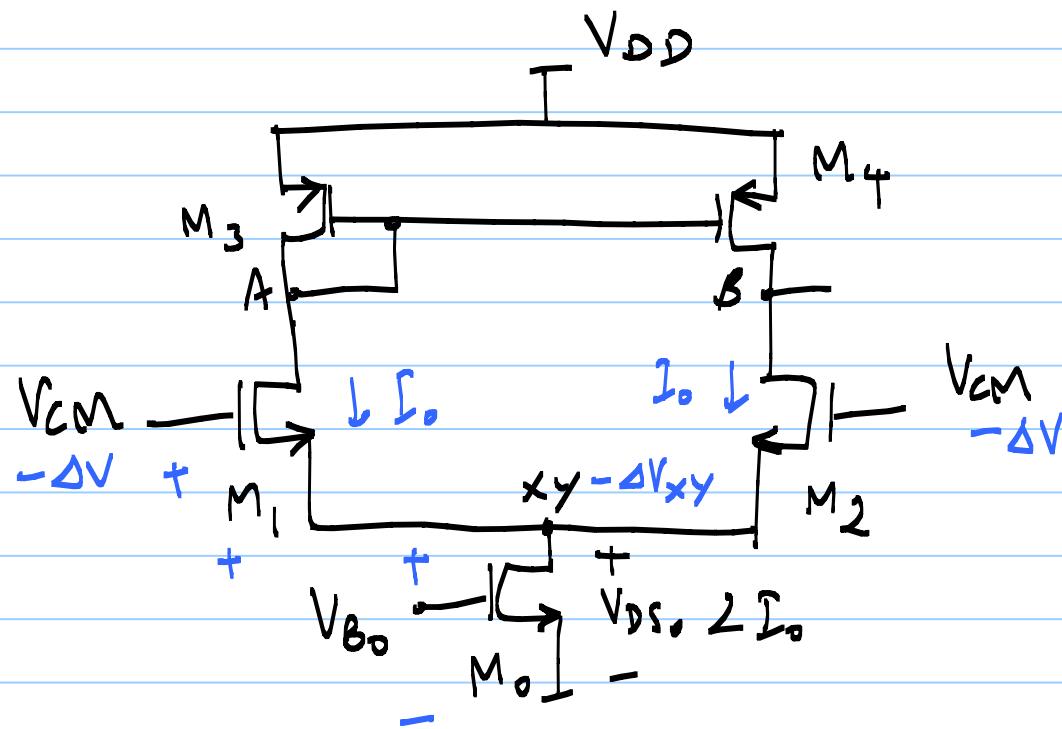

$\Delta V_{xy} = \Delta V$ if M_0 current does not change

ΔV_{xy} slightly less than ΔV if M_0 has large r_{ds}

$$\left\{ V_{DS} \downarrow \right\}$$

Eventually M_0 will go into triode region


$$\text{When } V_{DS} = V_{BS} - V_{T_0} = V_{DSat_0}$$

2) $V_{CM} \uparrow \rightarrow V_{CMmax}$

M_0 moves away from triode boundary


$$V_{CMmin.} = V_{DSat_0} \Big|_{2I_0} + V_{DS1} \Big|_{I_0}$$
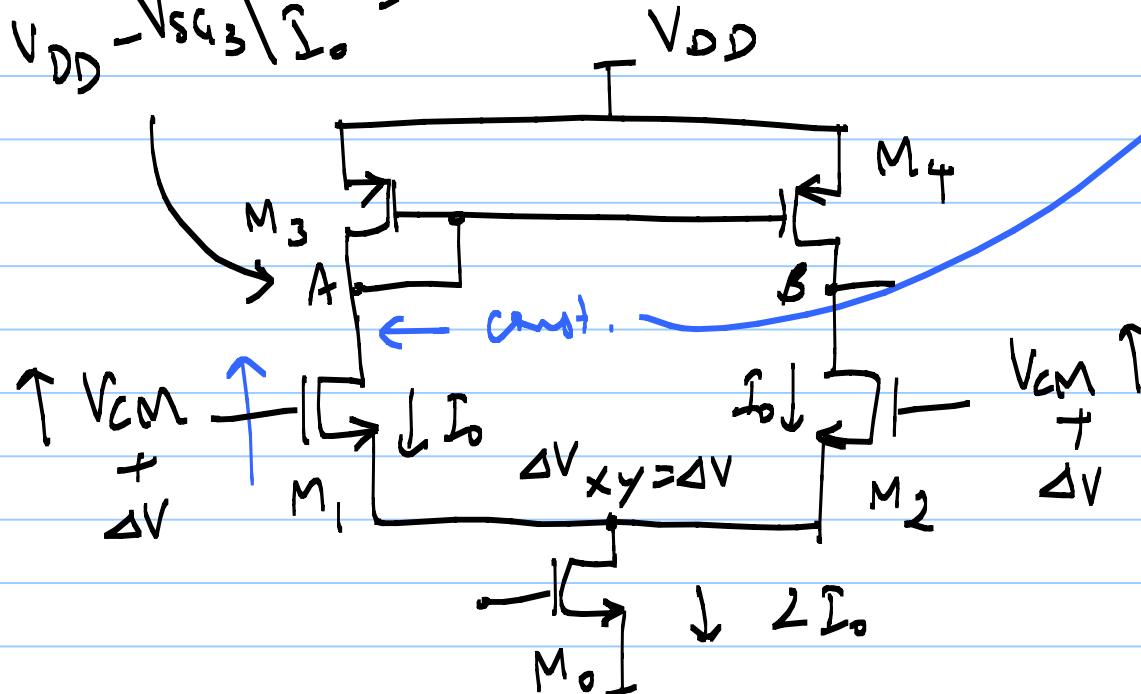
$$V_A = V_{DD} - \frac{V_{SG_3}}{I_o} = \text{constant}$$



$$V_{D_1} = V_A - V_{T_1}$$
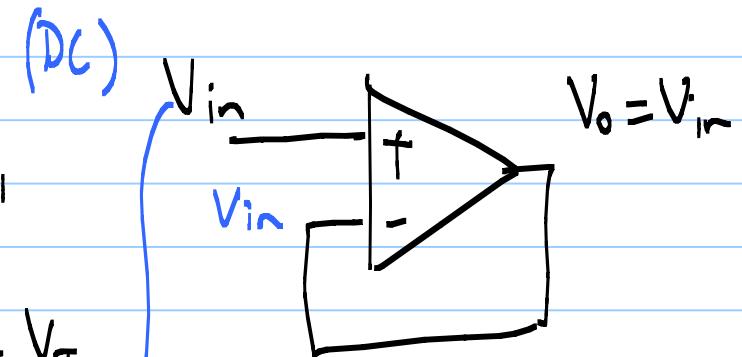
$$V_{DD} - \frac{V_{SG_3}}{I_o} = V_{CM_{max}} - V_{T_1}$$




$$V_{CM_{max}} = V_{DD} - \frac{V_{SG_3}}{I_o} + V_{T_1}$$

$$ICMR = \{ V_{CM_{min}}, V_{CM_{max}} \}$$

OCMR

constant

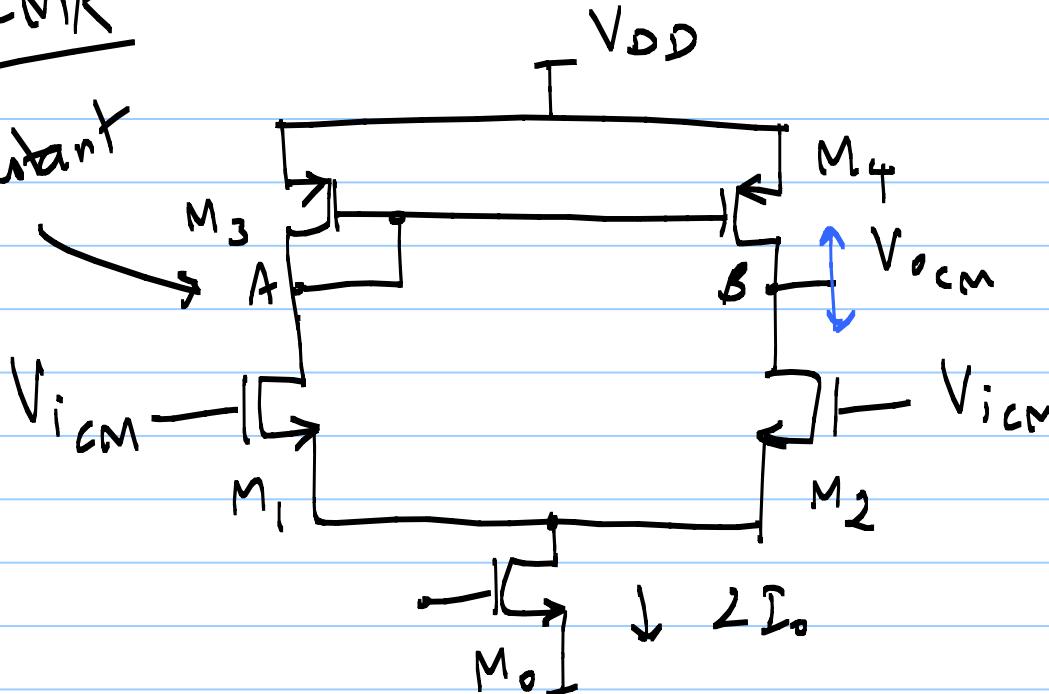

* V_{oCM} is set by

f.b.

1) $V_{oCM\ max} = \text{Voltage at which } M_4 \text{ goes into triode}$

$$V_A = V_{DD} - V_{SG_3} \Big|_{I_o}$$

$$V_{D4} = V_{g4} + V_{T4}$$

$$V_{oCM\ max} = V_A + V_{T4}$$

$$V_{oCM\ max} = V_{DD} - V_{SG_3} \Big|_{I_o} + V_{T4}$$

$$V_{oCM\ max} = V_{DD} - V_{SD_{sat4}}$$


2) $\downarrow V_{oCM} \rightarrow V_{oCM\ min.} = \text{Voltage at which } M_2 \text{ goes into triode}$

$$V_{D_2} = V_{A_2} - V_{T_2}$$



$$V_{OCM\min.} = \underbrace{V_{ICM}}_{\text{range of values within ICMR}} - V_{T_2}$$

range of values within ICMR

$$DCMR = \{ V_{CM\min.}, V_{CM\max} \}$$


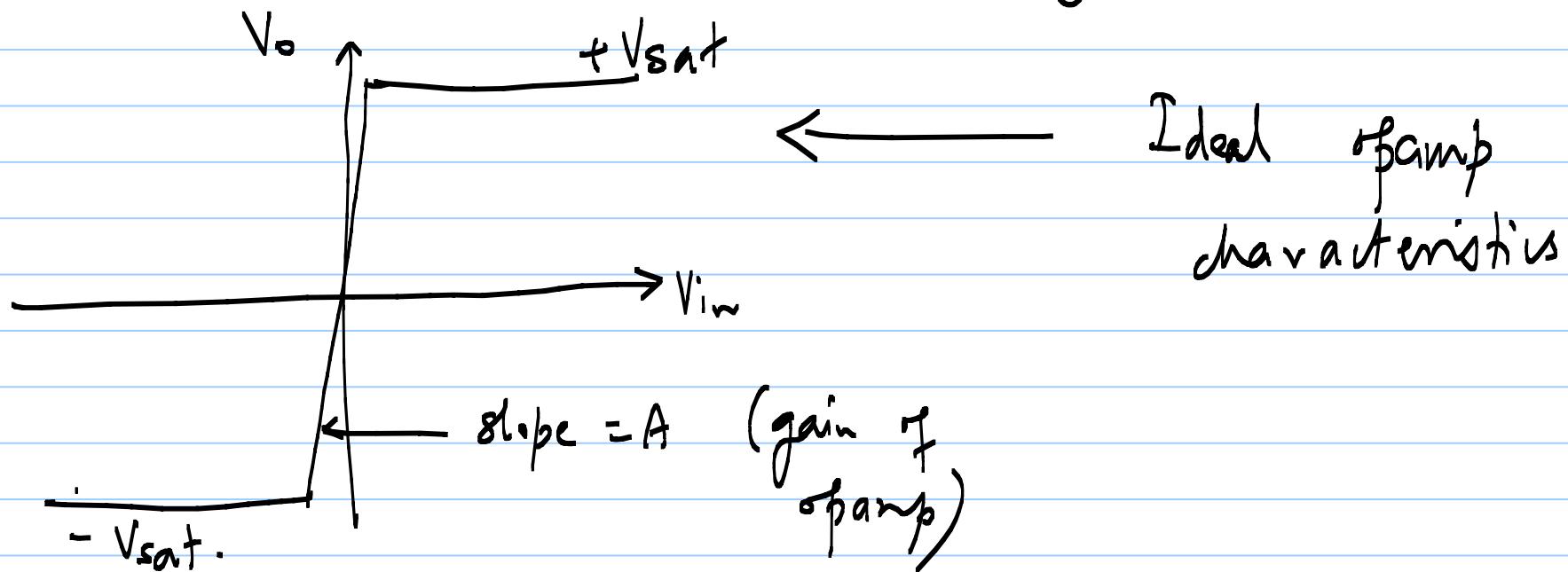


One stage of amp :

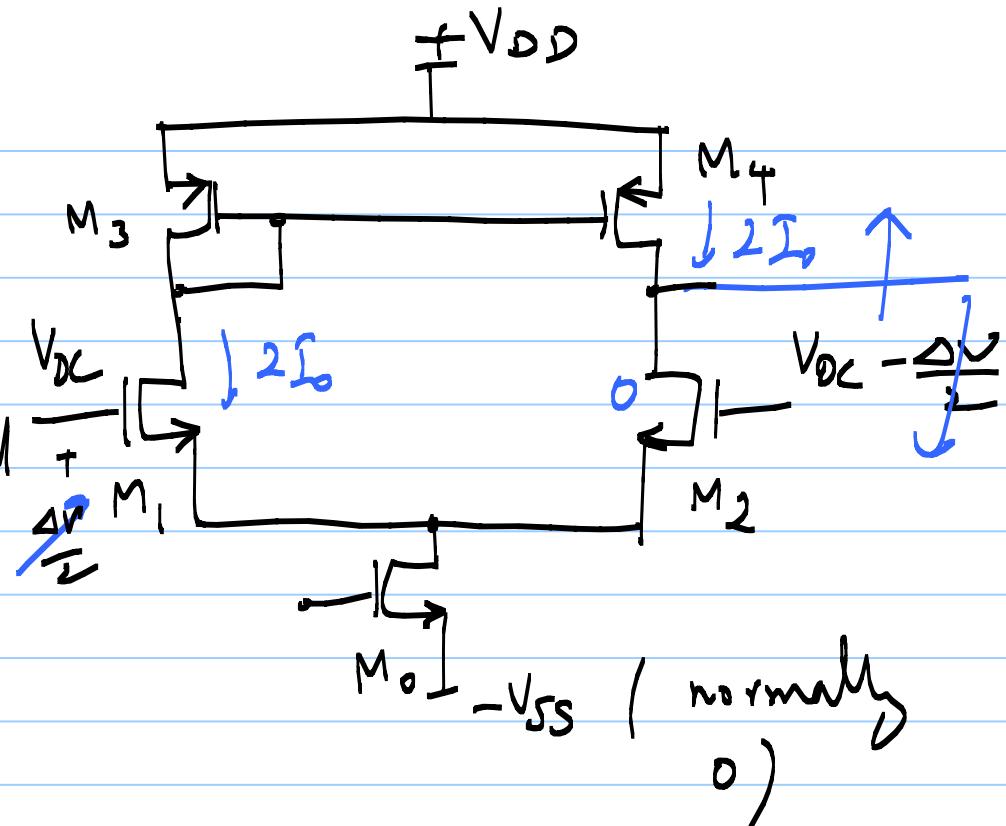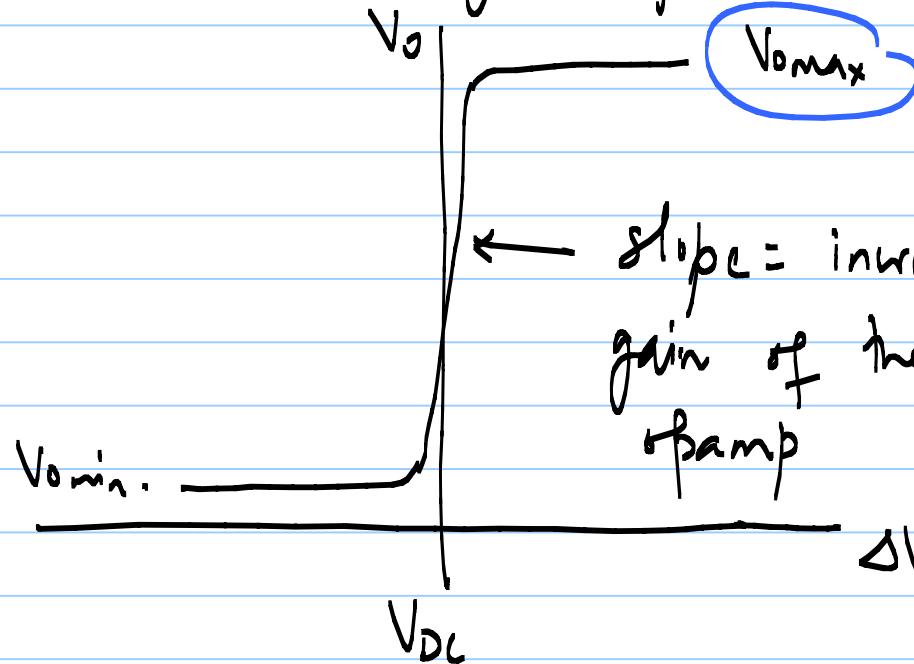

9/10/2020

Lecture 36

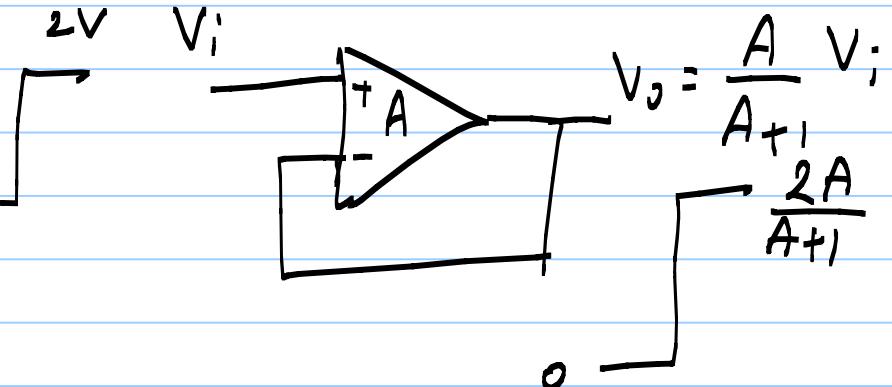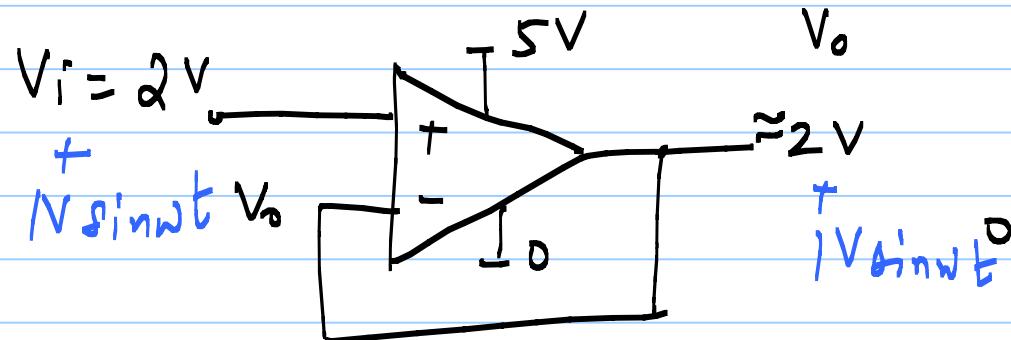

$$A = 100$$

$$\text{here } V_o = \frac{100}{101} \cdot 2V$$

$$V_{CM} = \frac{V_+ + V_-}{2} = \frac{V_i + V_o}{2} = \frac{1}{2} \left[V_i + \frac{100}{101} V_i \right]$$


$$= \frac{201}{202} \cdot V_i \approx V_i$$


$$V_{DM} = \frac{V_+ - V_-}{2} = \frac{V_i - V_o}{2} = \frac{1}{2} \left[V_i - \frac{100}{101} V_i \right]$$

$$V_{DM} = \frac{V_i}{2} \cdot \frac{1}{101} = \frac{V_i}{202}$$


$$V_+ = V_{CM} + V_{DM} = \frac{201}{202} V_i + \frac{V_i}{202} = V_i$$

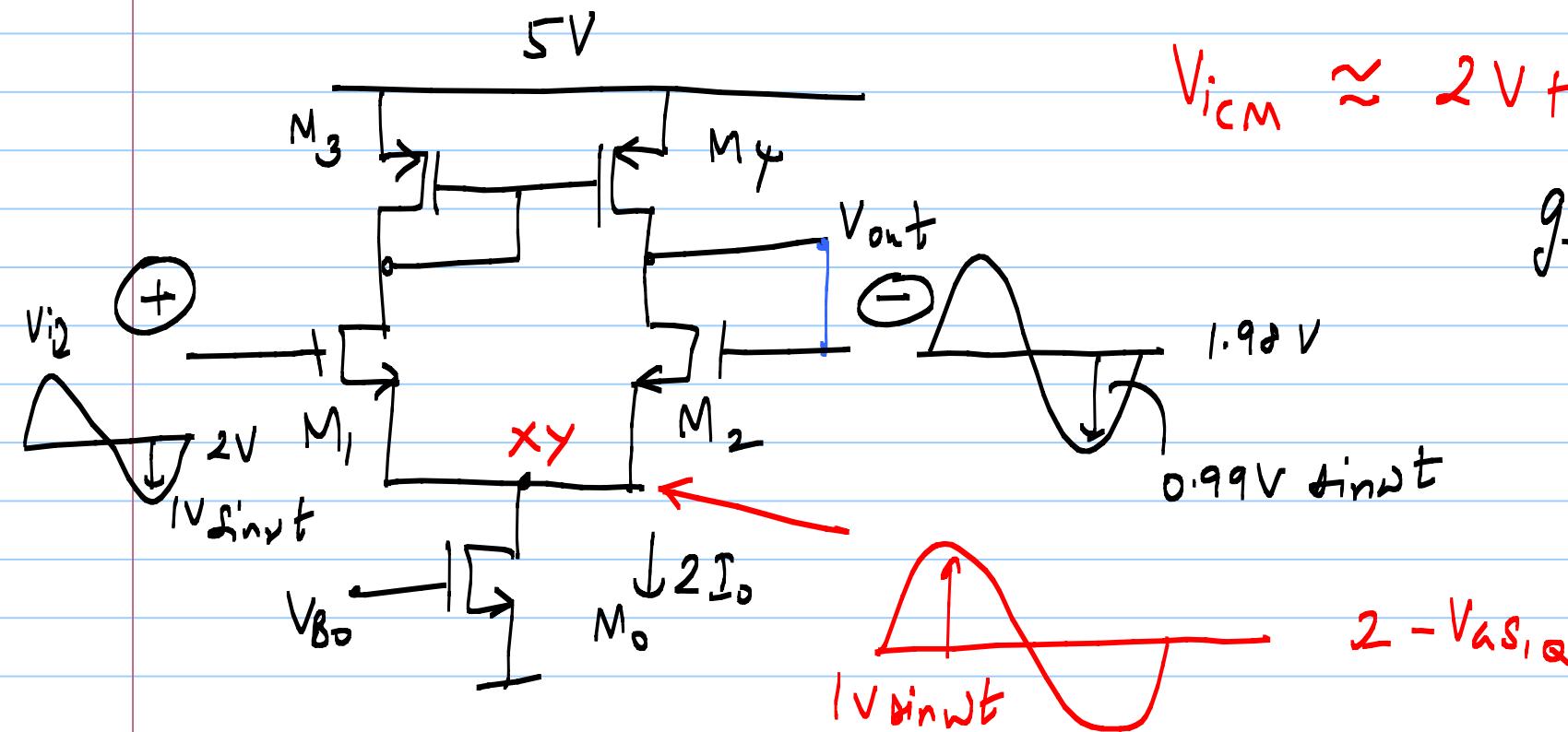
$$V_- = V_{CM} - V_{DM} = \frac{100}{101} V_i$$



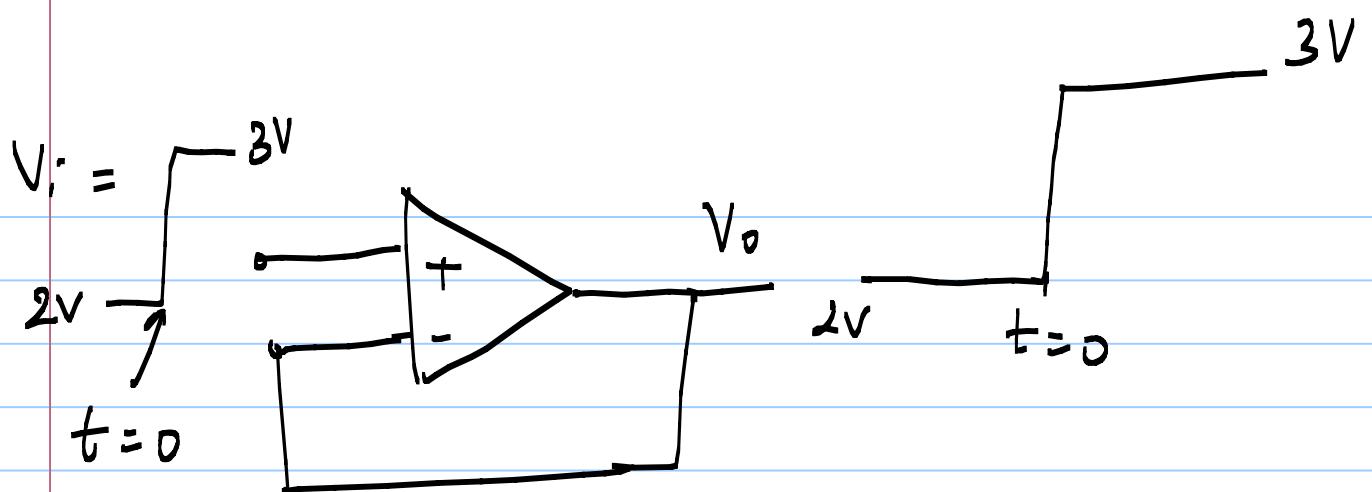

No f.b.i. yet

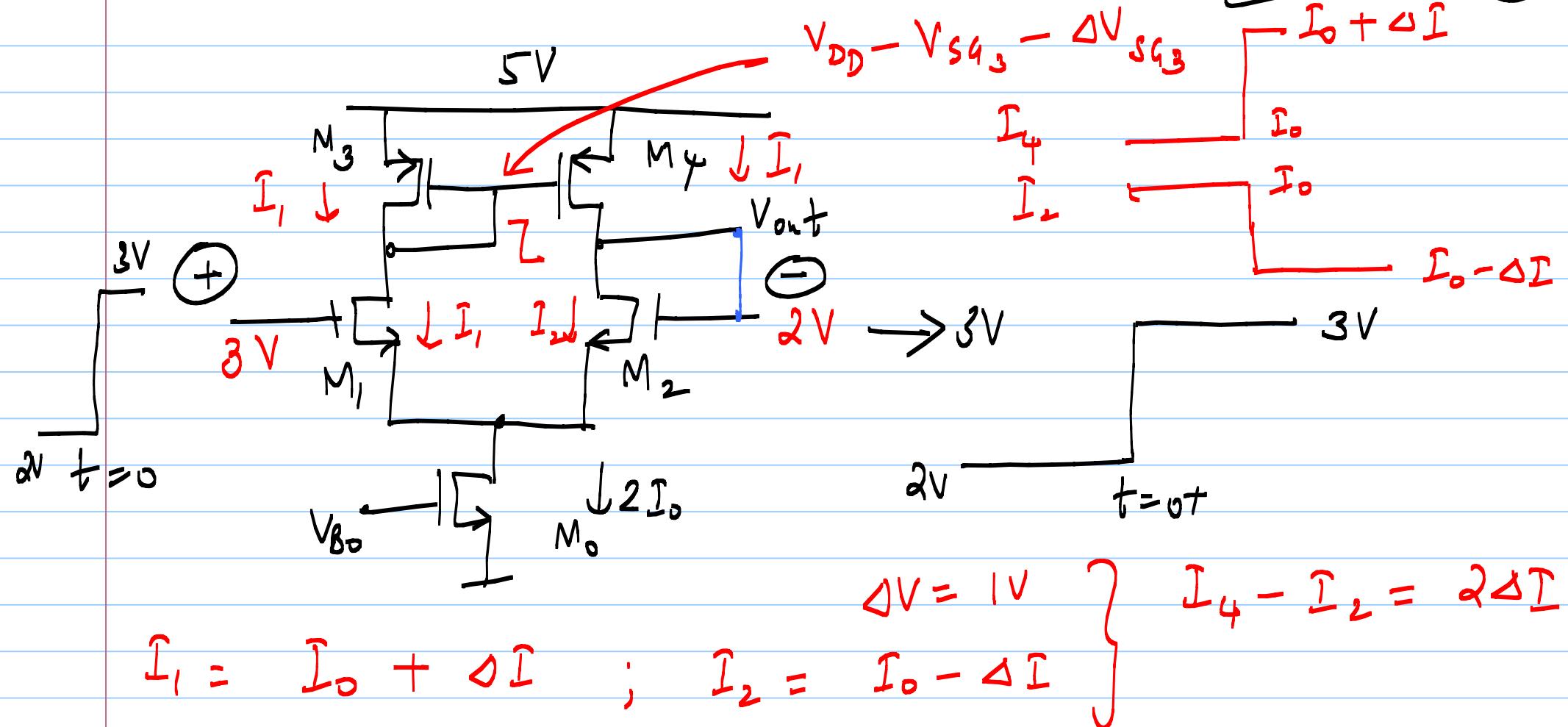

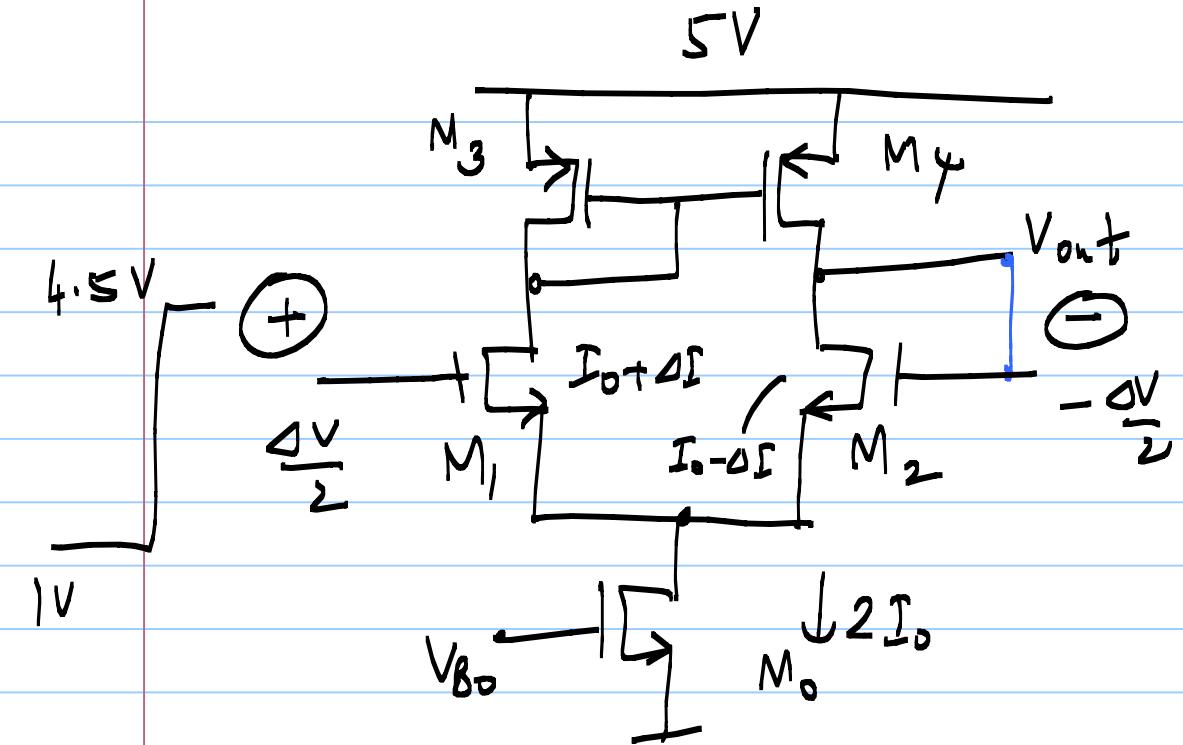

ΔI depends on $\frac{\Delta V}{2}$

larger $\frac{\Delta V}{2} \rightarrow$ larger ΔI

small signals: $\Delta I = g_m \frac{\Delta V}{2}$

large signals (large ΔV)


larger $\frac{\Delta V}{2} \rightarrow$ larger ΔI

still true


$$M_2 = 0$$

(largest possible $\Delta I = I_0$, $\{ I_1 = 2I_0, I_2 = 0 \}$)

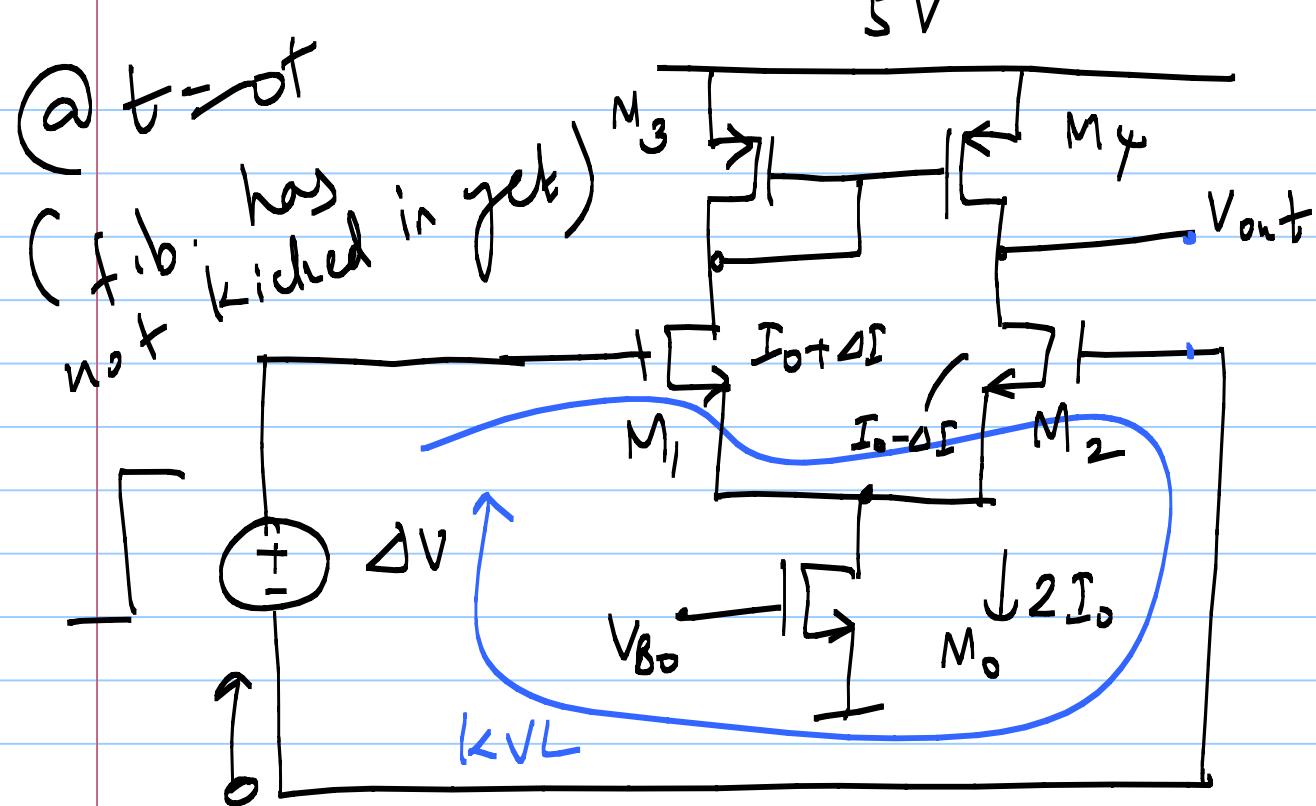Beyond this: larger $\Delta V \not\Rightarrow$ larger ΔI



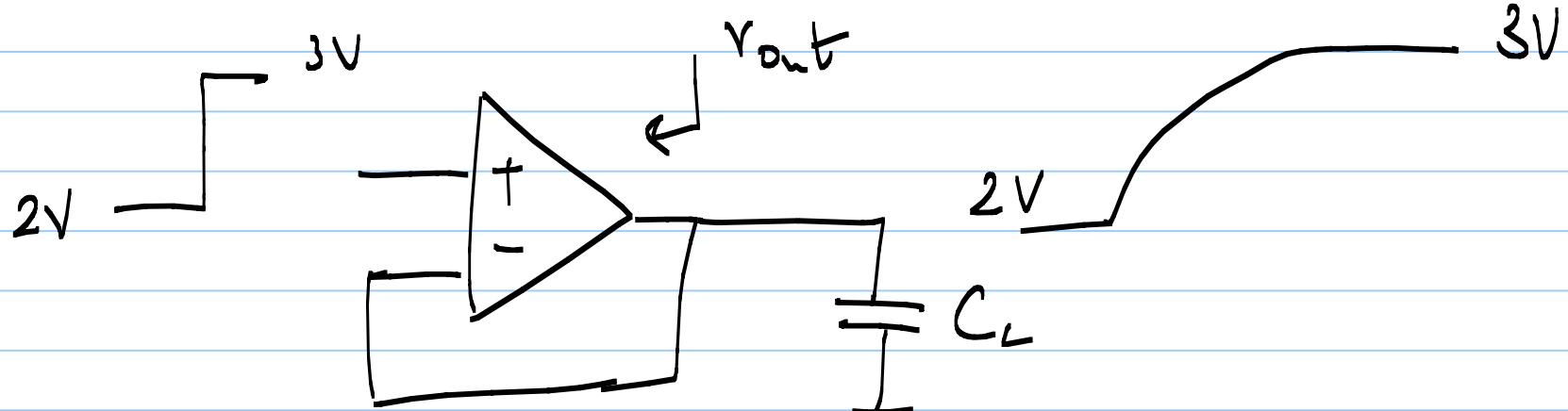
$$\begin{aligned}
 & +\Delta V - V_{GS_1} + V_{GS_2} = 0 \\
 \Delta V &= V_{GS_1} - V_{GS_2}
 \end{aligned}$$



13 | 10 | 2020

Lecture 37

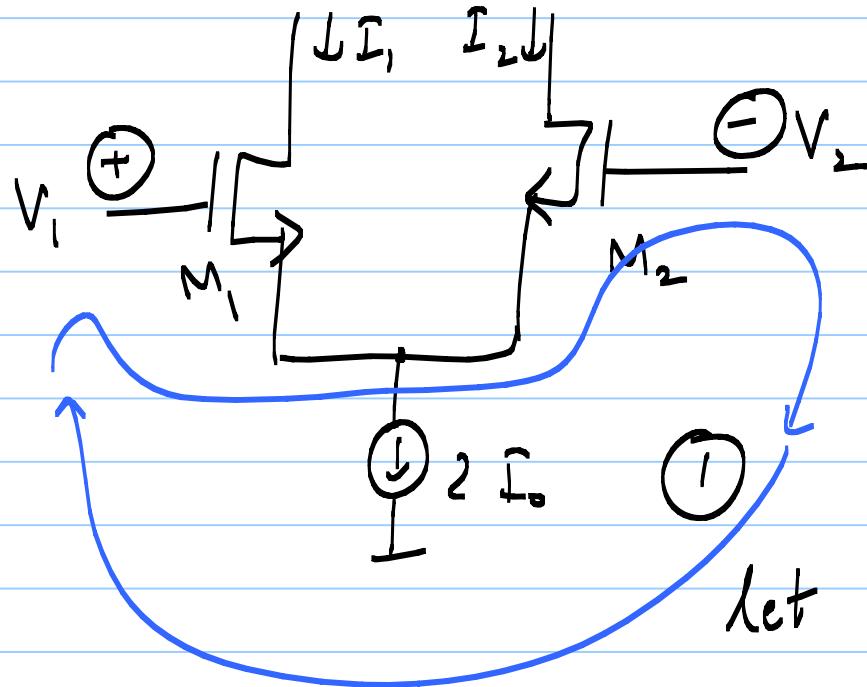

$$V_{id} = V_1 - V_2$$

$$V_{id} = 0 \Rightarrow I_1 = I_2 = I_0$$

$$I_{od} = I_1 - I_2$$

$= g_m V_{id}$ for small
signals / increments

$$\text{let } k' = \mu_n C_{ox}$$

KVL around ① : $V_1 - V_{as_1} + V_{as_2} - V_2 = 0$

$$V_{id} = V_1 - V_2 = V_{as_1} - V_{as_2}$$

$$= \left[V_{T_1} + \sqrt{\frac{2I_1}{k' \left(\frac{W}{L}\right)_1}} \right] - \left[V_{T_2} + \sqrt{\frac{2I_2}{k' \left(\frac{W}{L}\right)_2}} \right]$$


$$V_{id} = \sqrt{\frac{2}{k'(\frac{w}{L})}} \left[\sqrt{I_1} - \sqrt{I_2} \right] \quad \text{--- } A$$

$$I_1 + I_2 = 2I_0 \quad \text{--- } B$$

Use A & B to get $I_1 = f(V_{id})$

HW

$$I_2 = g(V_{id})$$

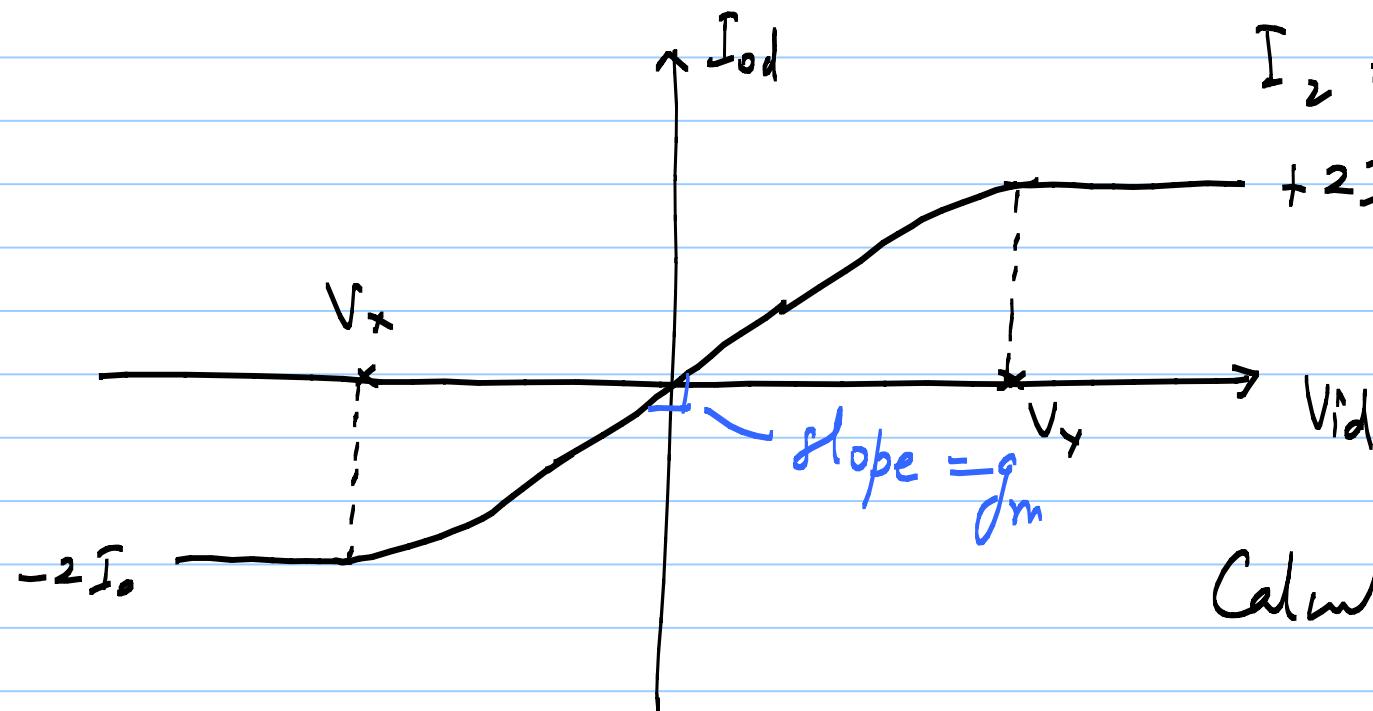



slope = g_m

Calculate V_x & V_y

HW

V_x & V_y : currents become $\neq I_0$ & 0

One stage opamp gain $\approx g_m (r_{ds2} || r_{ds4})$

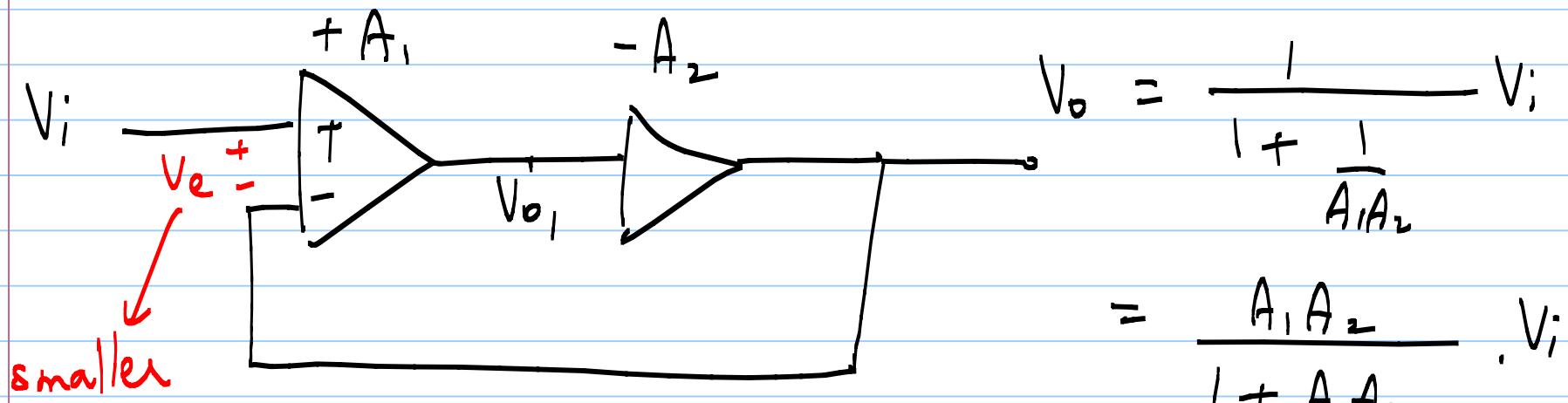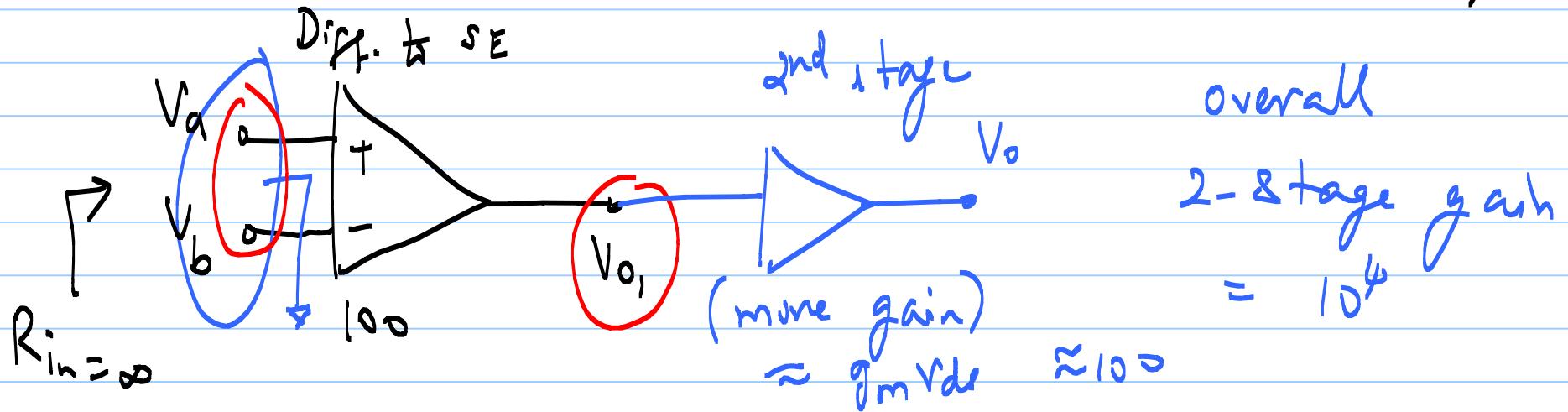

$$V_e = \frac{V_i}{1 + A_1 A_2} ; V_{o1} = \frac{A_1 V_i}{1 + A_1 A_2} = \frac{V_i}{A_2 + \frac{1}{A_1}}$$

A circuit diagram showing a voltage-controlled voltage source (VCCS). The input voltage V_i is applied to the non-inverting terminal (+). The output voltage V_o is controlled by the inverting terminal (-), which is connected to ground through a resistor. The gain is labeled $A_3 = A_1$.

$$V_{e_s} = \frac{V_i}{1 + A_3}$$

$$= \frac{V_i}{1 + A_1}$$

$$V_o = \frac{A_3}{1 + A_3} V_i$$

A circuit diagram of a common-emitter amplifier stage. The input voltage $V_Q + \Delta V$ is applied to the base. The collector is connected to a DC voltage source V_{DD} through a resistor R . The output voltage is given by the equation:


$$V_{DD} - I_Q R - g_m R \Delta V$$

The output current is:

$$I_Q + g_m \Delta V$$

$$g_m = f(V_Q \text{ or } I_Q)$$

2 - stage opamp:

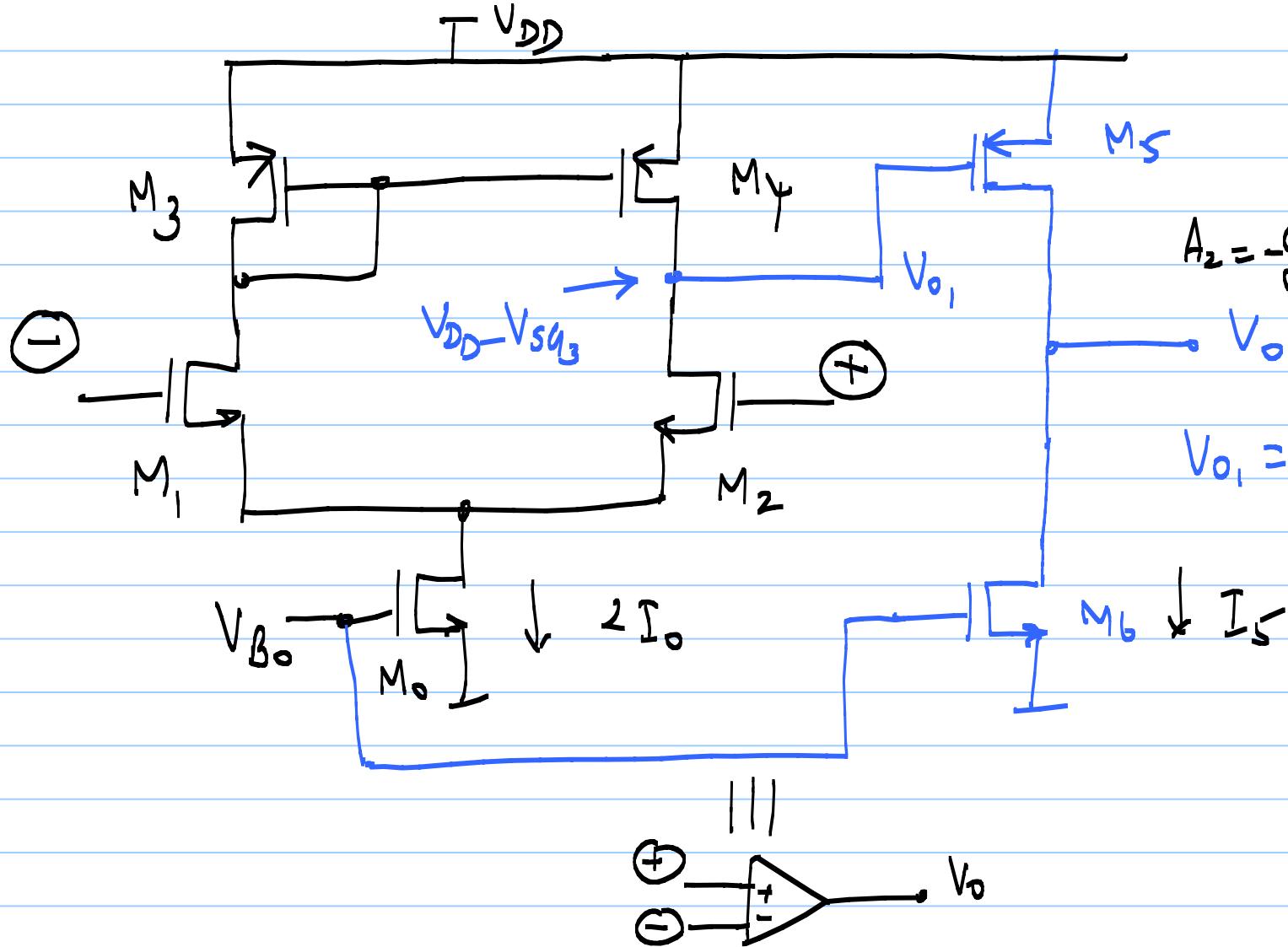


$$A_1 = g_{m_1} (r_{ds_2} || r_{ds_4})$$

$$A_2 = -g_{m_5} (r_{ds_5} || r_{ds_6})$$

$$V_{o1} = -g_{m_1} (r_{ds_2} || r_{ds_4})$$

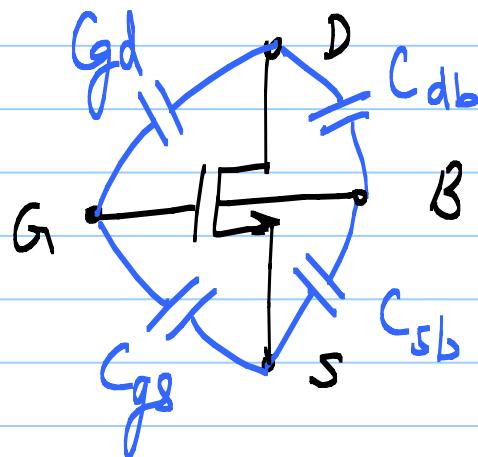* Every MOSFET has a speed limitation / delay




bulk / substrate

terminal { normally signal ground }

$B = \text{gnd}$ for NMOS

$B = V_{dd}$ for PMOS

AC small signal eq. cir.:

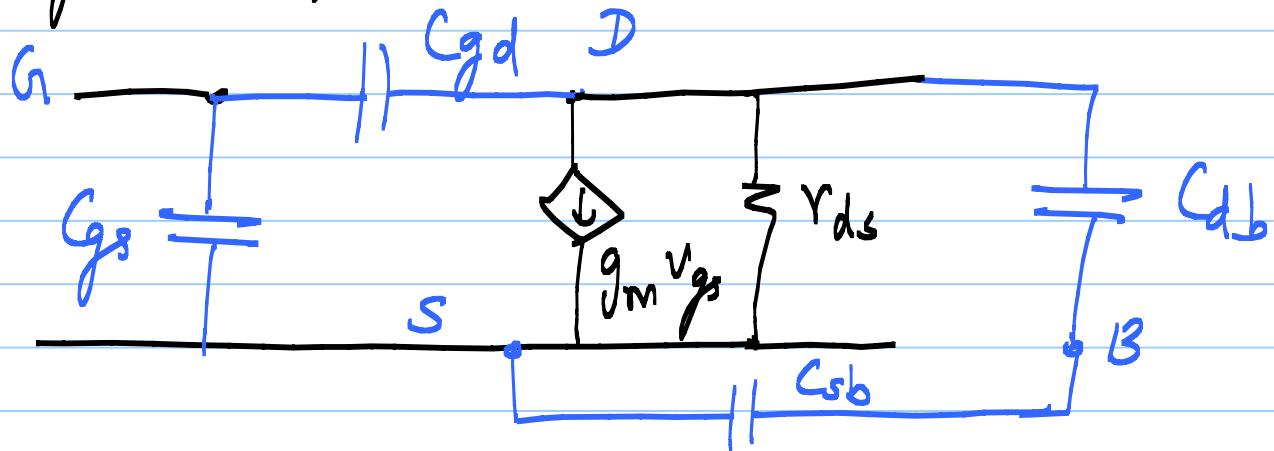

* In sat.: $C_{GS} \gg C_{GD}, C_{DB}, C_{SB}$

smallest cap.

(largest cap.)

* $C_{GS} \approx \frac{2}{3} W \cdot L \cdot C_{OX}$ in saturation

\downarrow \downarrow

f_F μ_m

f_F/m^2

$$V_1 = 3V \quad V_2 = 4V$$

$$V_{CM} = 3.5V$$

$$V_{DM} = -0.5V$$

14/10/2020


Lecture 38

* MOSFET caps - C_{gs} , C_{gd} , C_{db} , C_{sb}


$\frac{2}{3} WL C_{ox}$

largest smallest


i) Assume C_{gd} is negligible

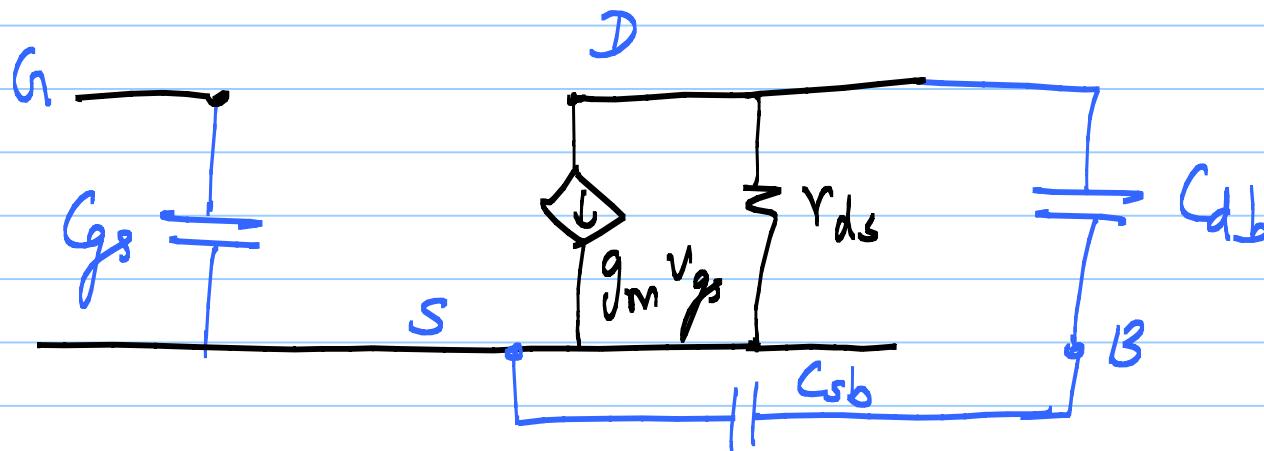

CSA

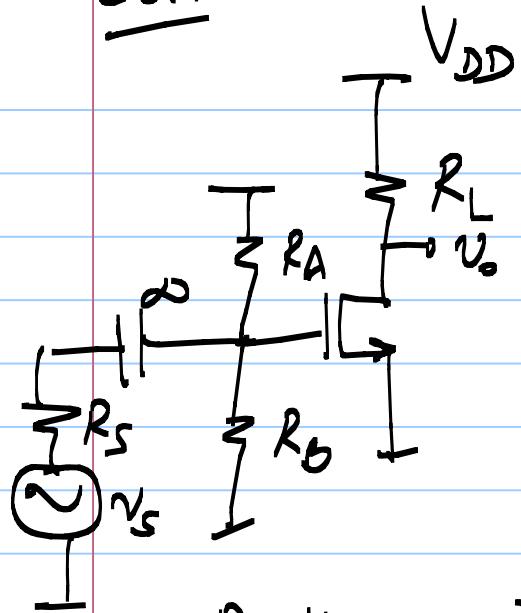

$$R_A \parallel R_b \gg R_s$$

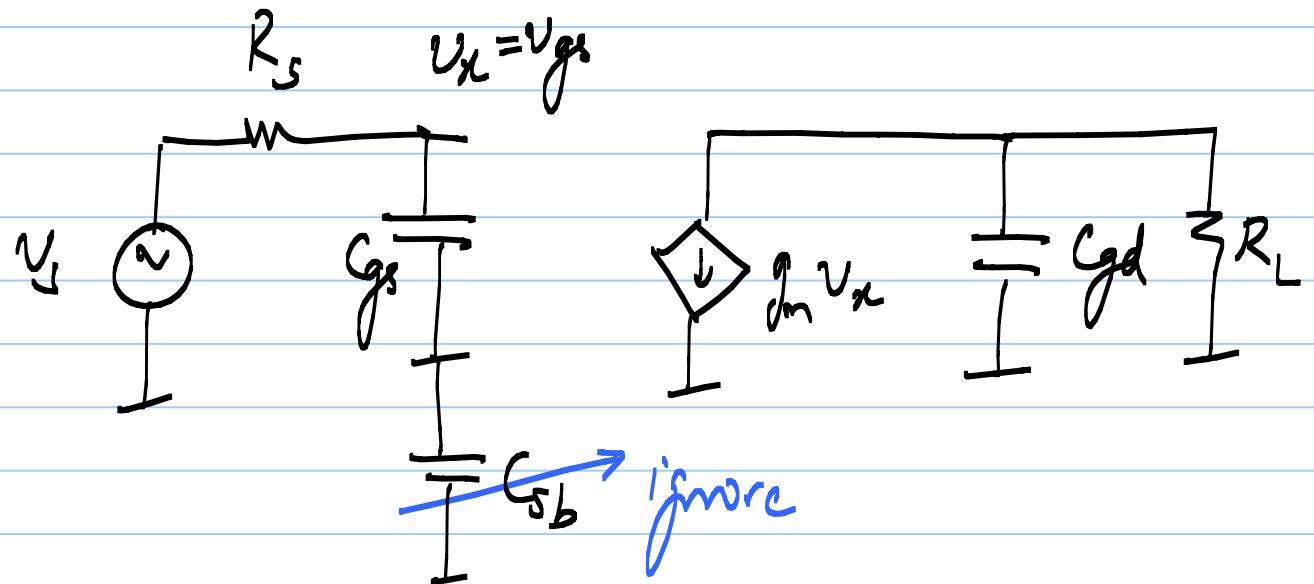

$$v_x(s) = \frac{1/s C_{gs}}{R_s + 1/s C_{gs}} \cdot v_s(s)$$

$$v_o(s) = -g_m \cdot \frac{1}{G_L + s C_{db}} \cdot v_x(s)$$


$$\frac{v_o}{v_s}(s) = \frac{1}{1 + s C_{gs} R_s} \cdot \frac{R_L}{1 + s C_{db} R_L} \cdot -g_m$$

$$\frac{v_o}{v_s}(s) = (-g_m R_L) \cdot \frac{1}{(1 + \zeta_1 g_s R_s)(1 + \zeta_2 g_{db} R_L)}$$

input pole $\beta_1 = -\frac{1}{R_s g_s}$




output pole $\beta_2 = -\frac{1}{R_L g_{db}}$

2) With C_{gd} :

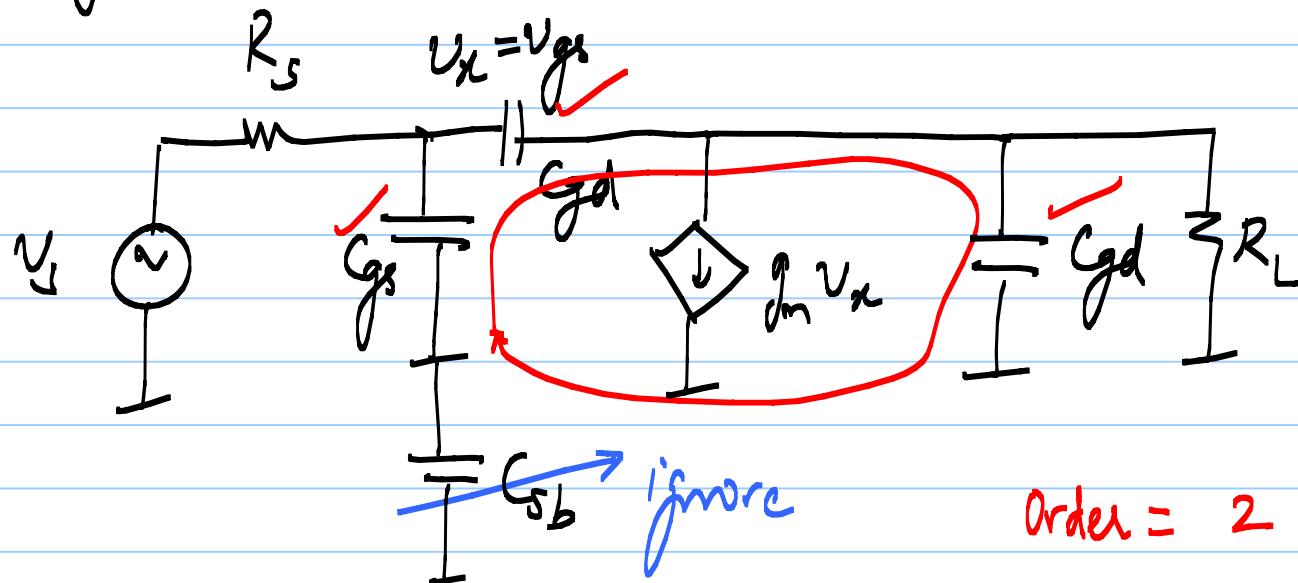

quadratic
Order = 2 {D(s)}


2 poles + 1 zero

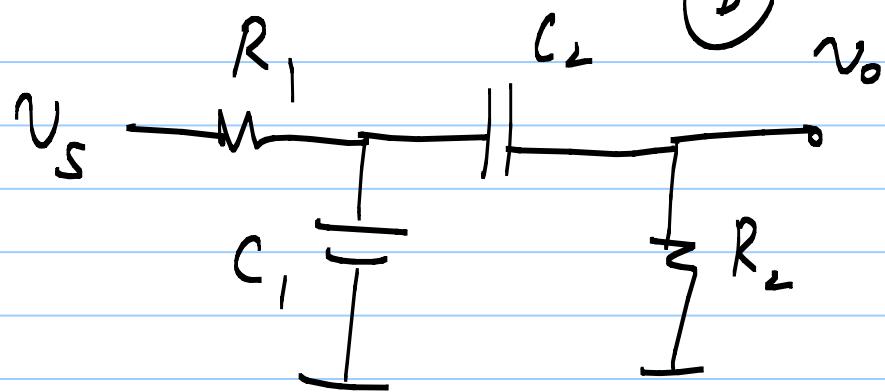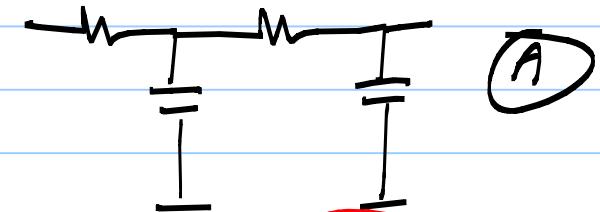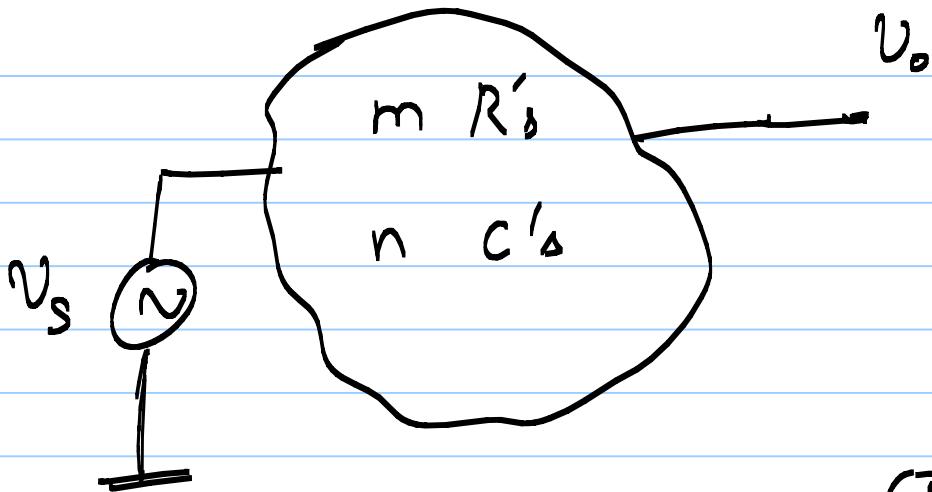

$$\frac{v_o}{v_s} = \frac{N(s)}{D(s)}$$




order = degree of $D(s)$

1 cap. \Rightarrow order = 1

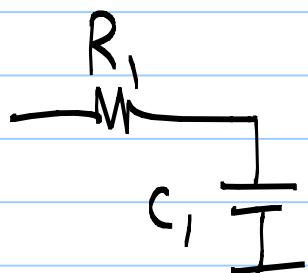

v_i
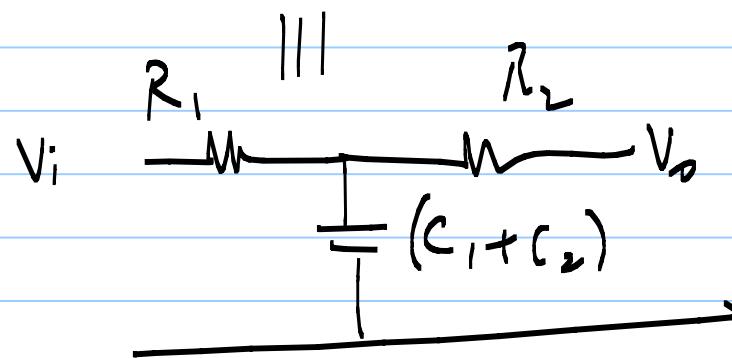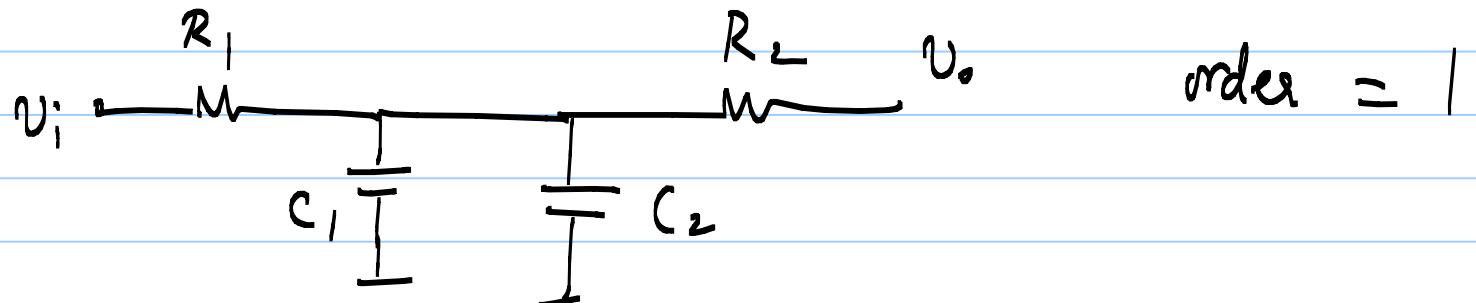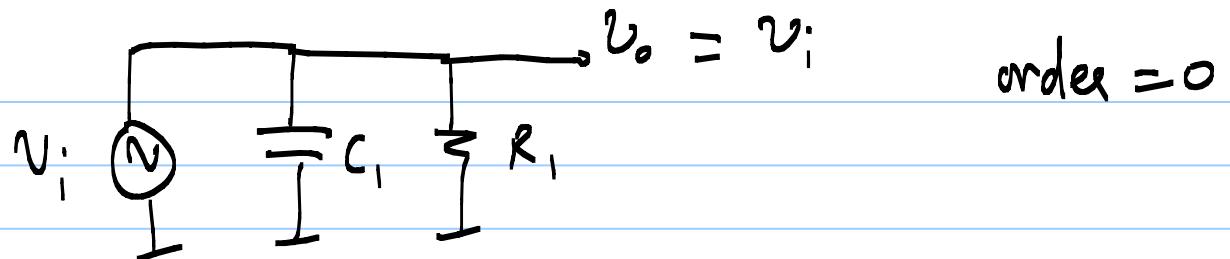
$$v_o = \frac{s C_1 R_1}{1 + s C_1 R_1}$$




$N(s)$ degree = # of zeroes



$$\frac{v_o(s)}{v_s} = \frac{N(s)}{D(s)}$$

@ zero frequency (s), $v_o(s) = 0$

independent of v_s

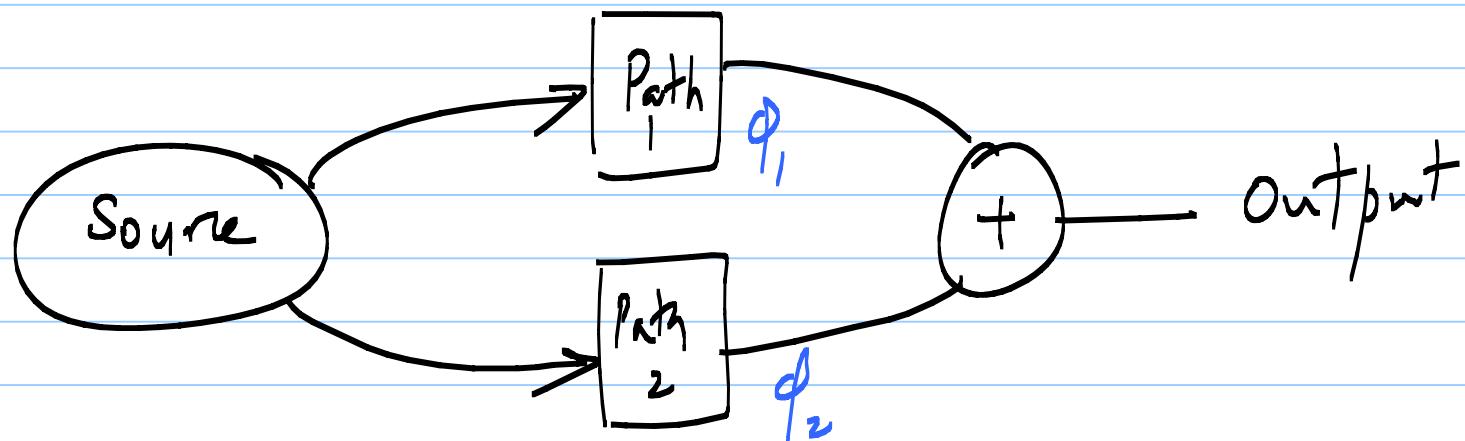

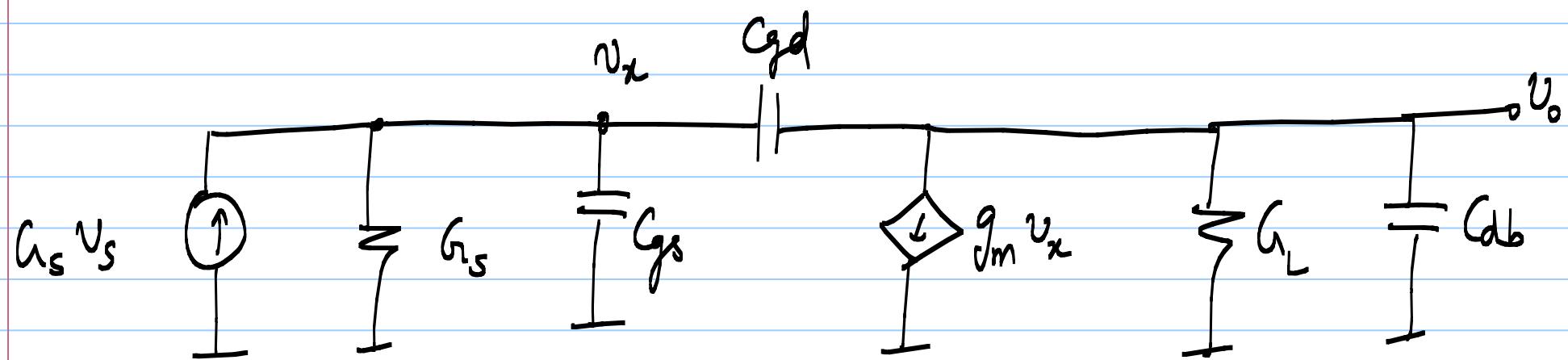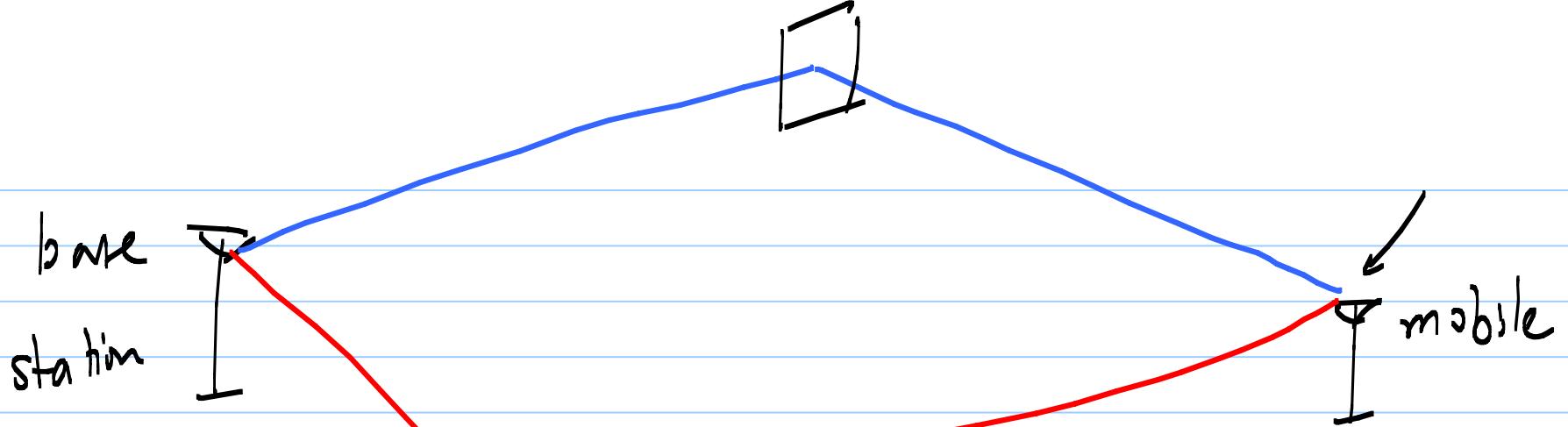zero \Rightarrow * multiple paths from input to output
and * phase shifts along paths are different



KCL @ input :

$$v_x sG_s + v_x G_s + (v_x - v_o) sC_{gd} = v_s G_s$$

$$\Rightarrow v_x \left[g_s + s(g_s + g_d) \right] = v_s g_s + v_o s g_d$$

$$v_x = \frac{v_s g_s + v_o s g_d}{g_s + s(g_s + g_d)}$$

KCL @ output :

$$(v_o - v_x) s g_d + v_o (g_L + s(d_b)) + g_m v_x = 0$$

 $\rightarrow \frac{v_o(s)}{v_s} = ?$

$$\frac{V_o}{V_s} = \frac{\text{(low freq.)}}{\text{j} \omega n}$$

Zeros $(N(s))$
poles $(D(s))$

$$= \left(-\frac{g_m}{G_L} \right)$$

1st order $N(s)$
2nd order $D(s)$


IS/10/2020

Lecture 39

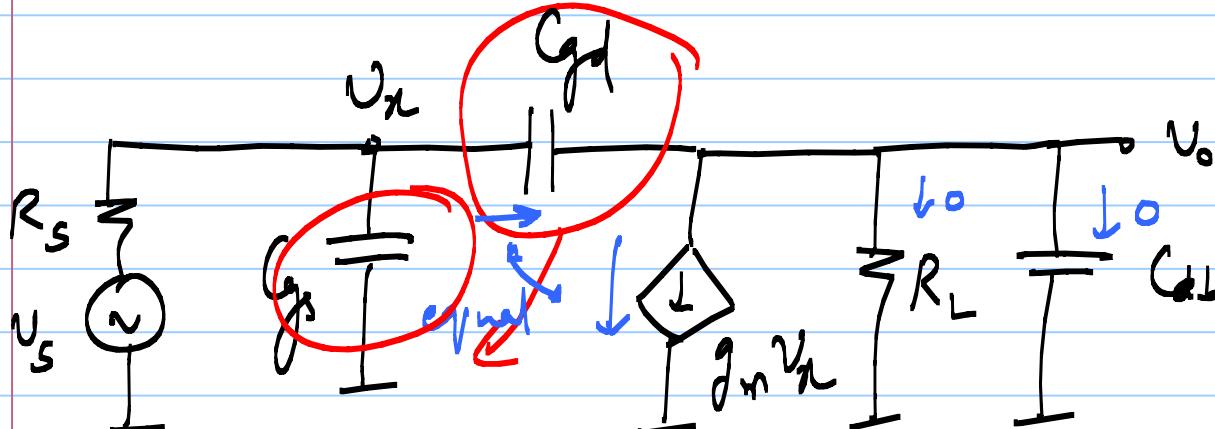2) CSA with C_{gd} considered :

$$\frac{V_o}{V_s}(s) = \left(-\frac{g_m}{G_L} \right) \frac{\left[1 - \frac{s C_{gd}}{g_m} \right]}{\left[\frac{s^2}{G_L G_S} (C_{gs} C_{gd} + G_S C_{db} + C_{gd} C_{db}) \right] + }$$

$$\frac{s}{G_L G_S} \left[G_L (G_S + G_d) + G_S (G_d + G_b) + g_m G_d \right] + 1$$



@ zero freq.
⇒ $V_o = 0$

$$D(s) = \frac{s^2}{G_L G_S} \left[G_L ((g_d + C_{d,b}) \right]$$

(ignore G_d ($C_{d,b}$))

$$+ \frac{s}{G_L G_S} \left[G_L G_S + G_S (G_d + C_{d,b}) \right.$$

(ignore G_d)

$$\left. + g_m G_d \right]$$


+

|

$$D(s) = \frac{s^2}{G_L h_s} \left[C_{gs} (C_{gd} + C_{fb}) \right] + \frac{s}{G_s} \left[C_{gs} + \frac{g_m}{G_L} C_{gd} + \frac{h_s}{G_L} (C_{gd} + C_{fb}) \right]$$

due to Miller effect ignore

+ 1

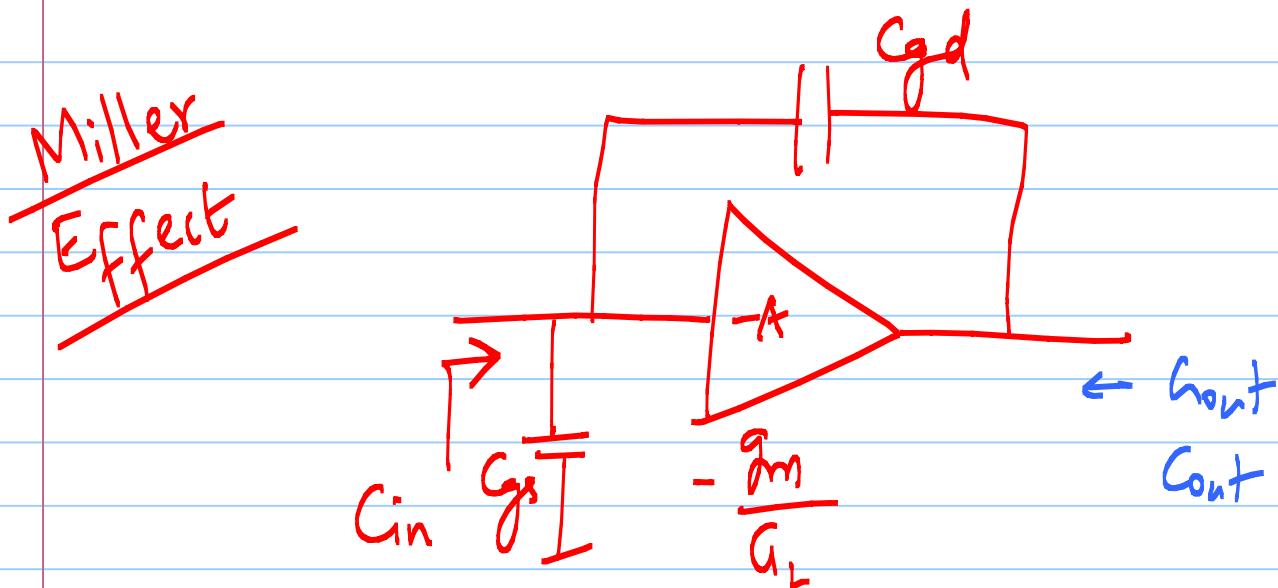

$$C_{in} \approx (1+A) C_{gd} + C_{gs}$$

$$\approx \frac{g_m}{G_L} C_{gd} + C_{gs}$$

$$I_f \quad D(s) = \left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right)$$

$$= \frac{s^2}{p_1 p_2} + s\left(\frac{1}{p_1} + \frac{1}{p_2}\right) + 1$$

$$p_1 \gg p_2 \Rightarrow \frac{1}{p_2} \gg \frac{1}{p_1}$$

$$D(s) \approx \frac{s^2}{p_1 p_2} + \frac{s}{p_2} + 1$$

$$p_2 = \frac{G_s s}{C_{gs} + C_{gd} \cdot \frac{g_m}{R_L}}$$

Compare this
with case without G_d


$$p_{20} = \frac{G_s}{C_{gs}}$$



$$\begin{aligned} b_1 &= b_1 b_2 \cdot \frac{1}{b_2} \\ &= \frac{g_L h_s}{g_s (g_d + g_b)} \cdot \frac{g_s + g_d \cdot \frac{g_m}{g_L}}{h_s} \end{aligned}$$

$$b_1 = \frac{g_L \left(g_s + g_d \cdot \frac{g_m}{g_L} \right)}{g_s (g_d + g_b)}$$

Compare with
case without g_d

$$b_{10} = \frac{g_L}{g_b}$$

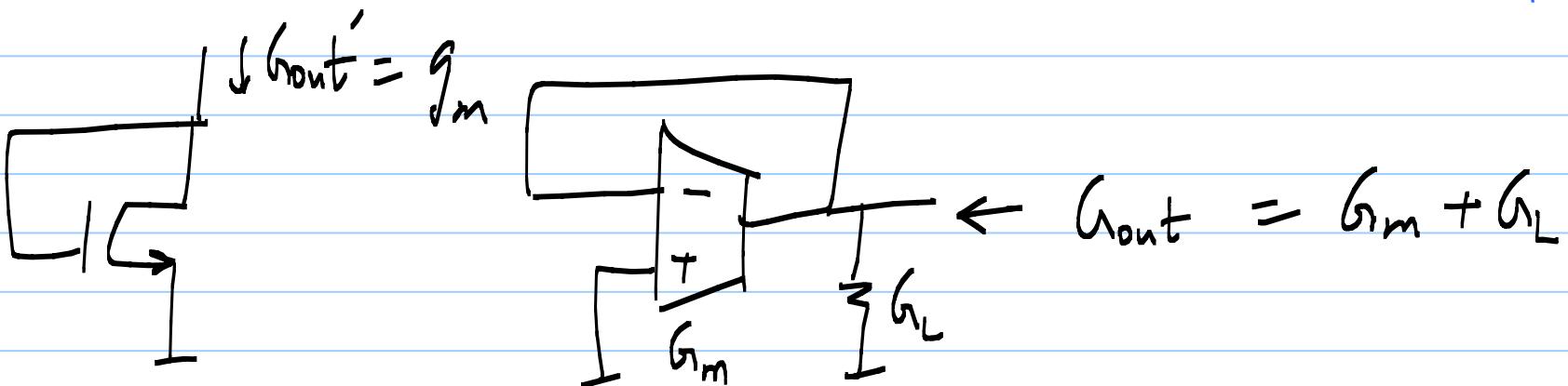

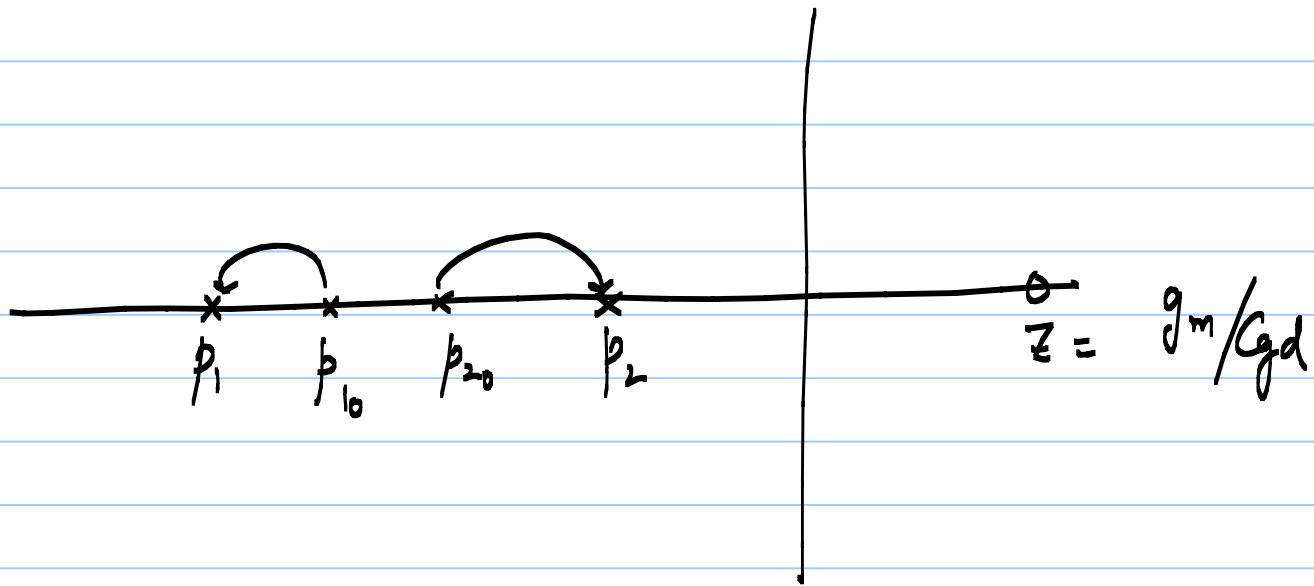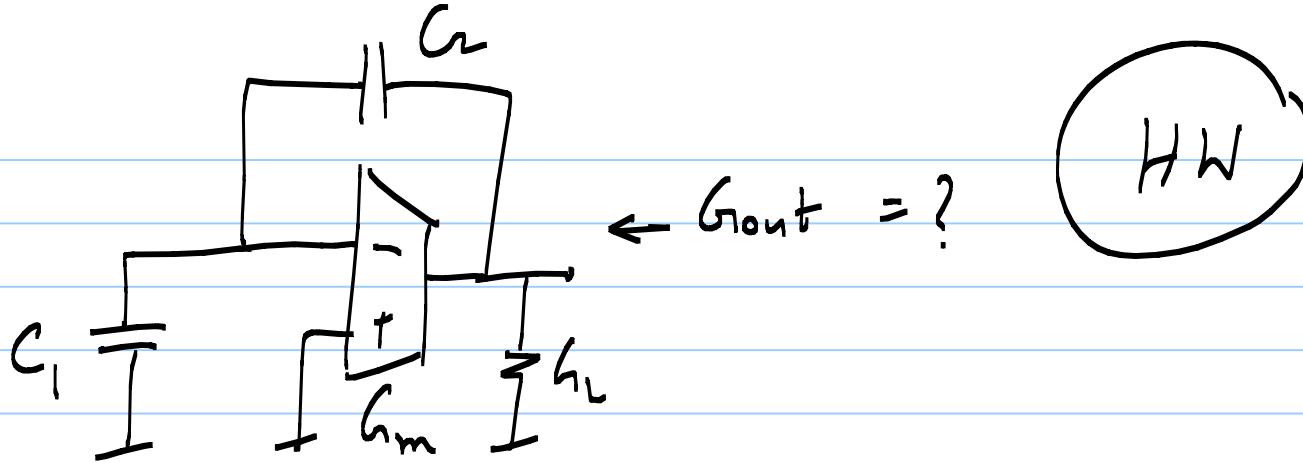


* Every node in an amplifier will have some parasitic cap.
 → made up of device cap. of transistors unconnected to that node

* pole associated with each node


e.g.
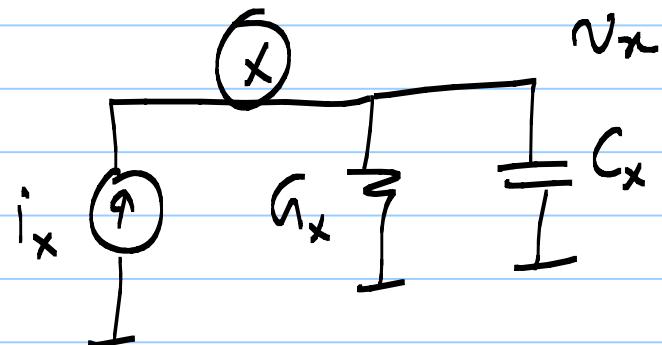
$$v_x = \frac{i_x}{y_x} = \frac{i_x}{g_x + j\omega C_x}$$



pole
at
 $\frac{g_x}{C_x}$

v_x has no freq. response

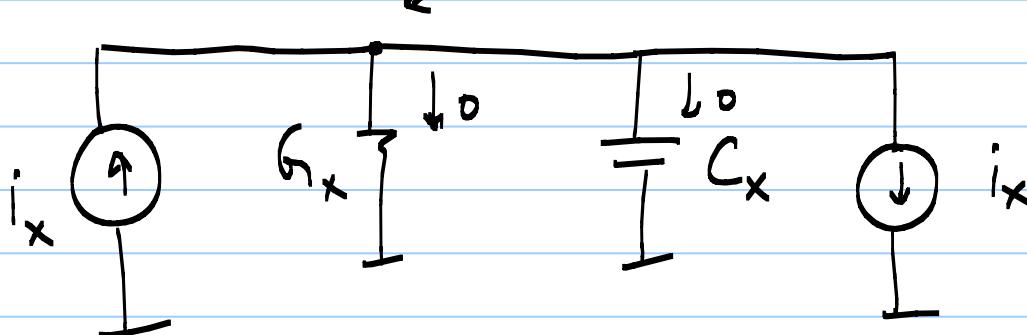


- * More gain \rightarrow cascade amplifier stages
 \rightarrow more # of nodes \rightarrow more # of poles
(and maybe zeroes)
- * More # of poles \rightarrow possibility of instability
when placed in feedback.

16/10/2020

Lecture 40

Feedback Systems

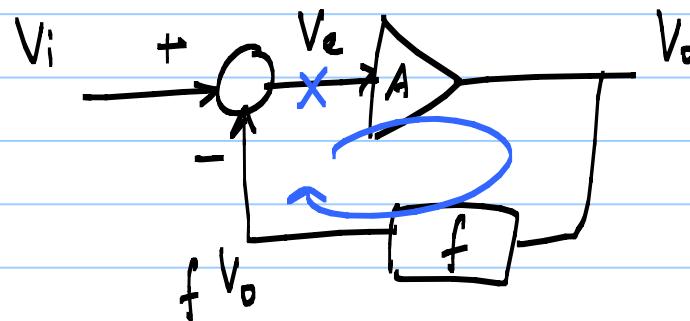

$$CLG = \frac{V_o}{V_i} = \frac{1}{f} \frac{Af}{1+Af}$$

$\approx \frac{1}{f}$ if A_f is large
loop gain (LG)

If $A = A(s)$, f is freq. indep.

$$CLG = \frac{1}{f} \frac{A(s) \cdot f}{1 + A(s)f} = CLG(s)$$

) 1st order : $A(s) = \frac{A_0}{1 + s/\omega_p}$ "DC" gain
(single pole amp.)

@ low freq. $A(s) \approx A_0 \Rightarrow LG \approx A_0 f \Rightarrow CLG \approx \frac{1}{f}$

Assume $CL_A \approx \frac{1}{f}$ is valid till $|LA| \sim 1$


$$CL_H(s) = \frac{1}{f} \frac{A(s) \cdot f}{(1 + A(s) \cdot f)}$$

$$= \frac{1}{f} \frac{\frac{A_0 f}{1 + s/\omega_p}}{\left(1 + \frac{A_0 f}{1 + s/\omega_p}\right)}$$

$$= \frac{1}{f} \frac{A_0 f}{(1 + A_0 f + s/\omega_p)}$$

$$= \frac{1}{f} \cdot \frac{A_0 f}{1 + A_0 f} \cdot \frac{1}{1 + \frac{s}{\omega_p (1 + A_0 f)}} \quad \begin{matrix} CL_H \text{ pole is} \\ @ \omega_p (1 + A_0 f) \end{matrix}$$
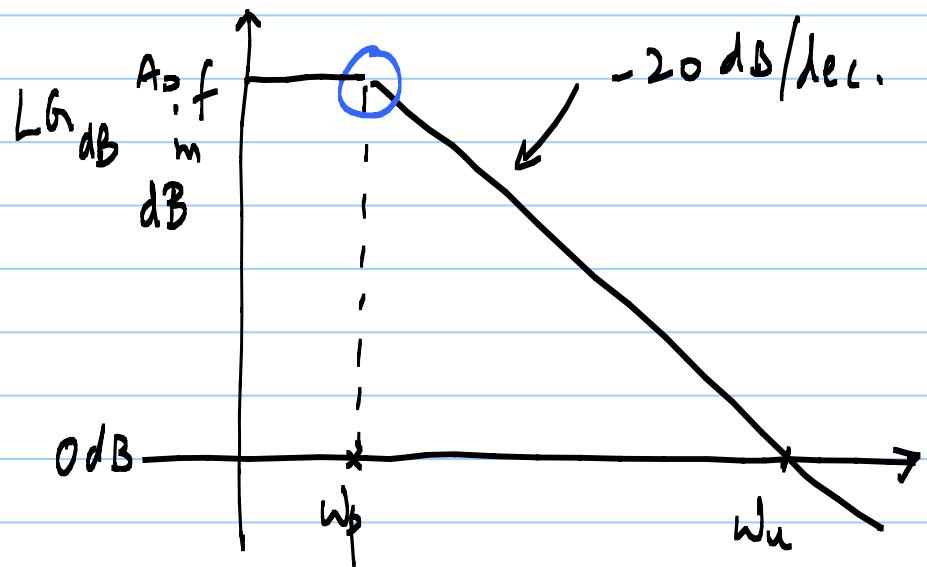
$$CLG \quad BW = \omega_p (1 + A_{of}) \approx \omega_p A_{of}$$



$$= A_{of} \cdot \omega_p \approx CLG \quad BW$$

- Note :
- 1) Single-pole system in closed loop has LHP poles
 - 2) Unconditionally stable

2) 2nd order system : $A(s) = \frac{A_0}{\left(1 + \frac{s}{\omega_p}\right)^2}$

$$CL_A(s) = \frac{1}{f} \cdot \frac{A_{of}}{1+A_{of}} \cdot \frac{1}{1 + \frac{2s}{A_{of}\omega_p} + \frac{s^2}{A_{of}\omega_p^2}}$$

* LHP poles
* Unconditionally stable
general 2nd order system has compare

$$D(s) = 1 + \frac{s}{Q \cdot \omega_0} + \frac{s^2}{\omega_0^2}$$

Quality factor $\longrightarrow Q \cdot \omega_0$

$$(n) D(s) = s^2 + 2 \zeta \omega_n s + \omega_n^2$$

damping factor

roots are $\frac{s}{\omega_0} = -\frac{1}{2Q} \pm j \sqrt{1 - \frac{1}{4Q^2}}$


Small $Q \rightarrow$ 2 real LHP poles

$Q = \frac{1}{2} \rightarrow$ 2 equal poles

$Q > \frac{1}{2} \rightarrow$ pair of complex conjugate poles

$Q = \infty \rightarrow$ poles on $j\omega$ axis

step
responce
for $CLh(s)$

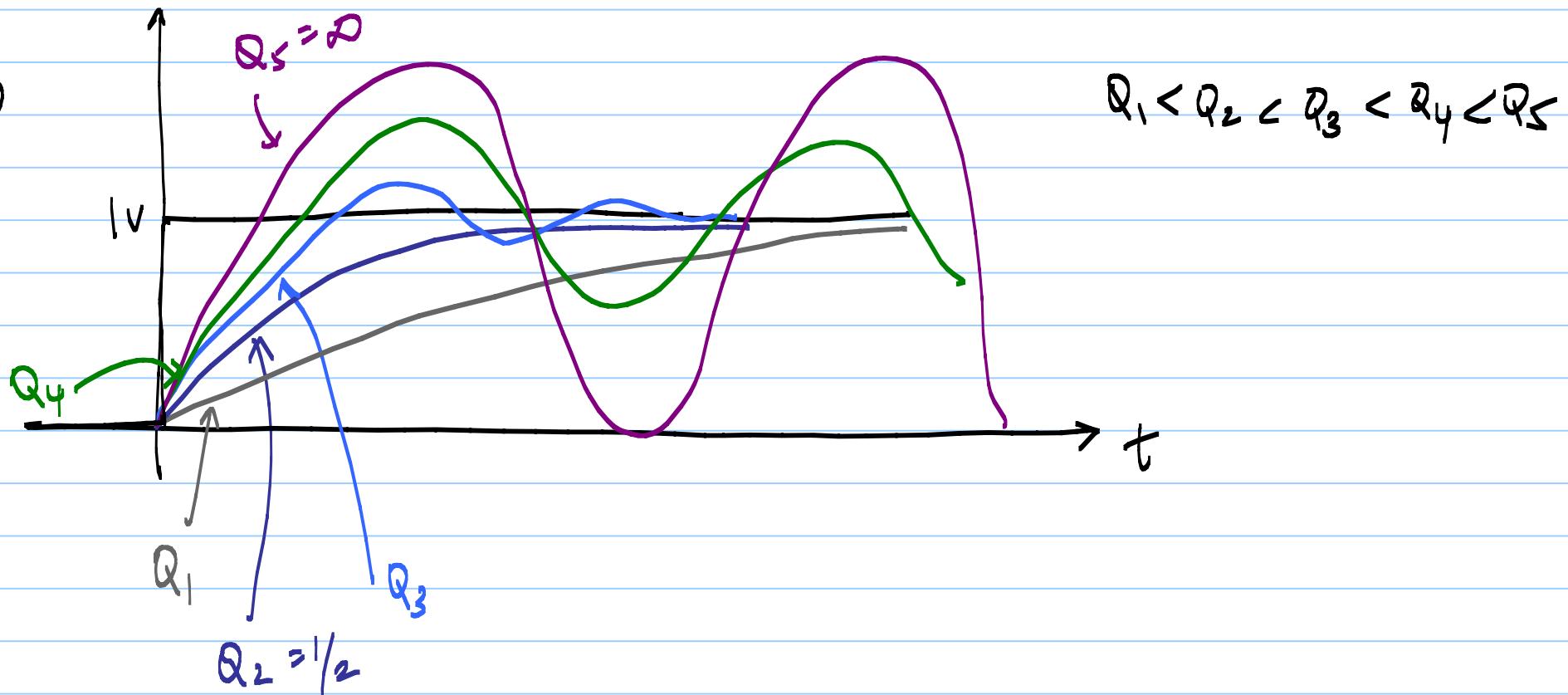

Here : $\omega_p = \omega_p \sqrt{A_0 f}$

$$Q = \frac{\sqrt{A_0 f}}{2}$$

No ringing $\Rightarrow Q \leq 1/2$

But : $A_{of} = \text{large}$ due to large La
requirement

3) 3rd order system : $A(s) = \frac{A_0}{\left(1 + \frac{s}{\omega_p}\right)^3}$

$$= \frac{A_0}{1 + \frac{3s}{\omega_p} + \frac{3s^2}{\omega_p^2} + \frac{s^3}{\omega_p^3}}$$

$$CLG(s) = \frac{1}{f} \cdot \frac{A_{of}}{1 + A_{of}} \cdot \frac{1}{1 + \left(\frac{1}{1 + A_{of}}\right) \left[\frac{3s}{\omega_p} + \frac{3s^2}{\omega_p^2} + \frac{s^3}{\omega_p^3} \right]} \quad \leftarrow \text{Eq (J)}$$

$$D(s) = 1 + \frac{3s}{\omega_p(1+A_{of})} + \frac{3s^2}{\omega_p^2(1+A_{of})} + \frac{s^3}{\omega_p^3(1+A_{of})}$$

$$x = \frac{s}{\omega_p}$$

$$D(x) = 1 + \frac{3x}{1+A_{of}} + \frac{3x^2}{1+A_{of}} + \frac{x^3}{1+A_{of}}$$

$$= \left(\frac{1}{1+A_{of}} \right) \left[(1+A_{of}) + 3x + 3x^2 + x^3 \right]$$

we want roots if

$$(1+x)^3 = -A_{of}$$


$$x = -1 + (-A_{of})^{1/3}$$

3 roots

e.g. 1) $A_{of} = 0 \rightarrow$ all 3 roots @ -1

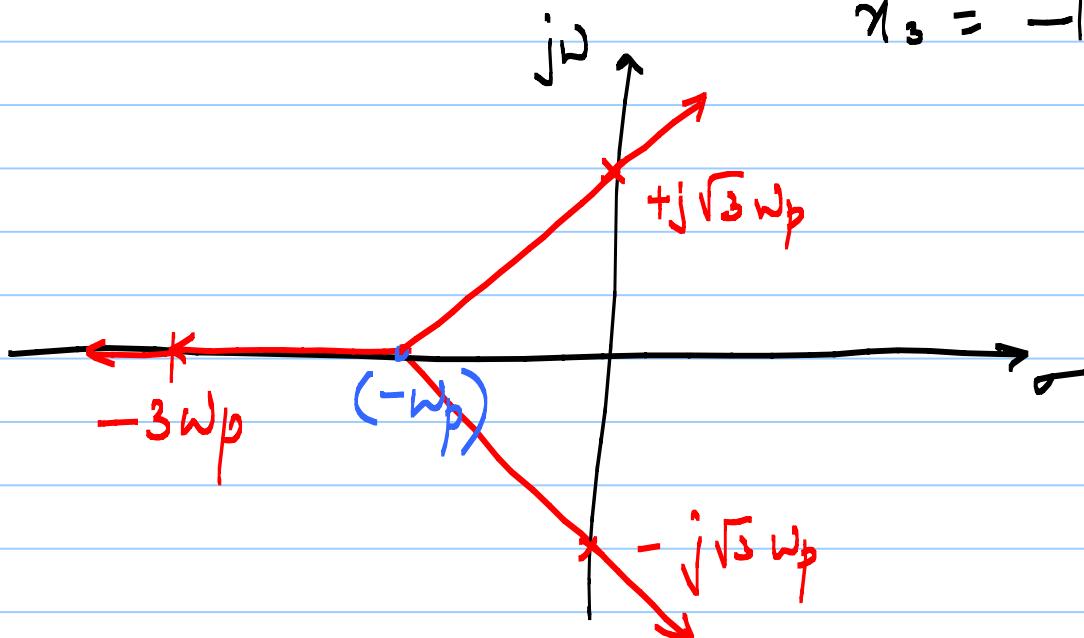2) $A_{of} = 8 \rightarrow$

$$\begin{aligned}\gamma_1 &= -1 - 2 = -3 \\ \gamma_2 &= -1 - 2e^{-j\frac{2\pi}{3}} \\ \gamma_3 &= -1 - 2e^{+j\frac{2\pi}{3}}\end{aligned}$$
$$\left. \begin{aligned}s_1 &= -3\omega_p \\ s_2 &= +j\sqrt{3}\omega_p \\ s_3 &= -j\sqrt{3}\omega_p\end{aligned} \right\}$$



If $A_{of} > 8$

↳ complex conjugate
roots move into
RHP

Unstable for $A_{of} > 8$

20/10/2020

Lecture 4

Summary:

1st order → low gain

→ unconditionally stable

2nd order → larger gain

→ technically stable, but ringing in
step response

3rd order → very large gain

→ unstable even for small LG_{dc}

4th order → very very large gain

→ highly unstable (guess)

Solution : Make a higher order system look like
 a 1st order system from the point of
 view of stability.


Take 3rd order system as an example

$$\frac{A_0}{(1 + s/\omega_p)^3} \xrightarrow[\text{pole } \omega_d]{\text{add a}} \frac{A_0}{\left(1 + \frac{s}{\omega_d}\right) \left(1 + \frac{s}{\omega_p}\right)^3}$$

* In reality, you may choose to move one ω_p
 pole to ω_d .

$$\omega_d \ll \omega_p$$

$$\omega_d = \text{"dominant" pole}$$

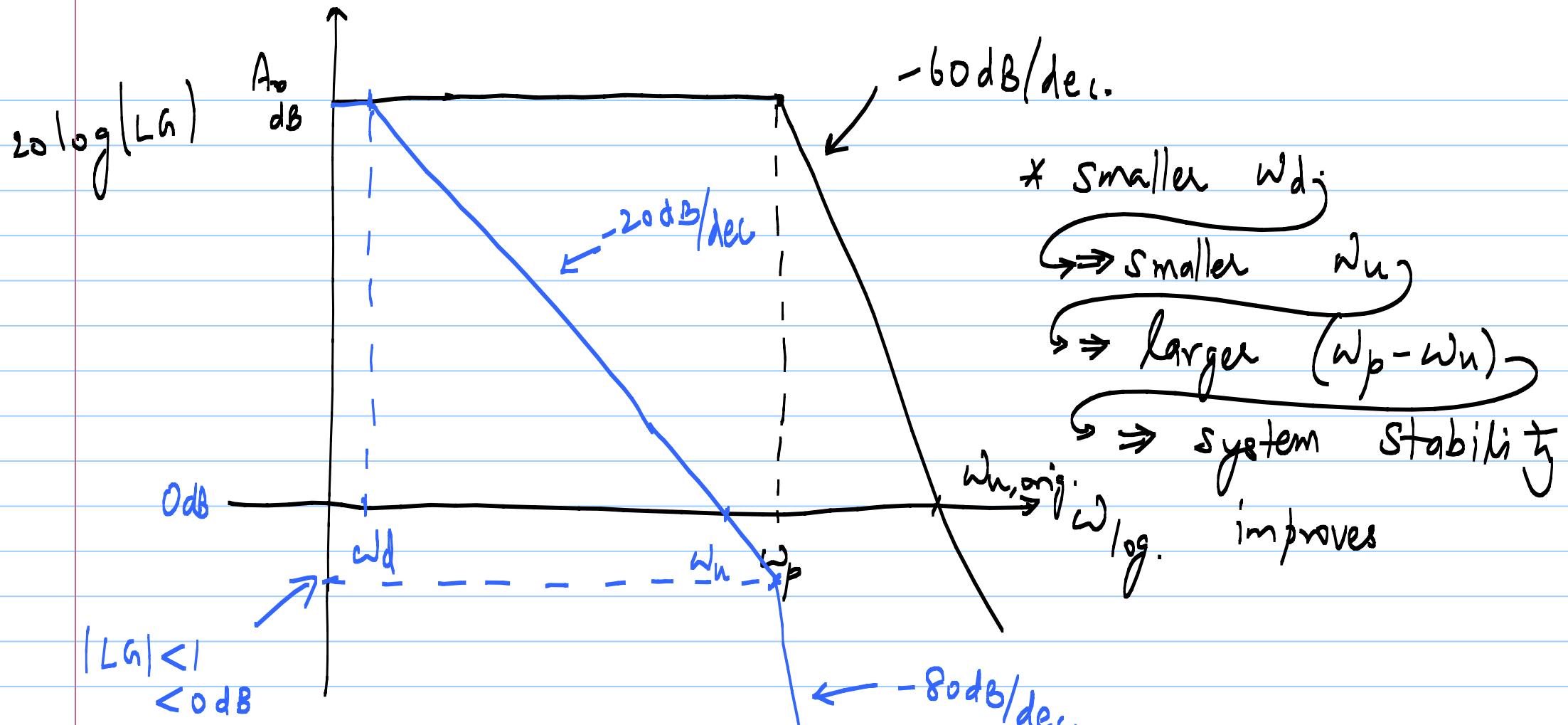

Improving stability = "Frequency Compensation"
 This technique = "Dominant-pole Compensation"

* $L_G = -1$

$$|L_G| = 1 \quad \& \quad \angle L_G = -180^\circ$$

* Avoid $|L_G| > 1$ when $\angle L_G = -180^\circ$

* Measures of Stability :

1) Gain Margin = $0\text{dB} - |L_G(j\omega)| \Bigg| \angle L_G(j\omega) = -180^\circ$

2) Phase Margin = $\angle L_G(j\omega) \Bigg| - (-180^\circ)$
 $|L_G| = 0\text{dB}$

$$= 180^\circ + \angle L_G(j\omega) \Bigg| |L_G| > 0\text{dB}$$

* We normally want high
GM & PM

21/10/2020

Lecture 42

Example :

$$\omega_d = \frac{\omega_p}{1000}$$

original limit for
stability : $A_{of} = 8$

$$L_G(s) = \frac{A_{of}}{\left(1 + \frac{s}{\omega_p}\right)^3 \left(1 + \frac{1000s}{\omega_p}\right)}$$

we need to
find new limit
on A_{of}

$$L_G(s) = \frac{X(s)}{Y(s)}$$

$$CLG(s) = \frac{1}{f} \cdot \frac{L_G(s)}{1 + L_G(s)} = \frac{1}{f} \cdot \frac{X(s)/Y(s)}{1 + X(j)/Y(j)} = \frac{N(s)}{D(j)}$$

roots of $L_G(s) = -1$

$$|L_G(j\omega_0)| = 1 \quad \varphi \quad \angle L_G(j\omega_0) = -\pi \quad \leftarrow$$

apply bin
first

$$-3 \tan^{-1} \left(\frac{\omega_0}{\omega_p} \right) - \underbrace{\tan^{-1} \left(\frac{1000 \omega_0}{\omega_p} \right)}_{\text{phase shift}} = -\pi$$

(a) $\omega_0 \rightarrow \omega_d$ give $-\pi/2$ phase shift

$$\Rightarrow -3 \tan^{-1} \left(\frac{\omega_0}{\omega_p} \right) = -\pi/2$$

each ω_p pole gives $-\pi/6$ (-30°)

$$\frac{\omega_0}{\omega_p} \approx \frac{1}{\sqrt{3}}$$

$$\boxed{\omega_0 = \frac{\omega_p}{\sqrt{3}}}$$

* Apply magnitude condition: $|LH(j\omega_0)| = 1$

$$\left| \frac{A_0 f}{(1 + j\frac{1}{f_2})^3 \left(1 + j\frac{1000}{\sqrt{3}}\right)} \right| = 1$$


$$\frac{A_0 f}{\left(\sqrt{1 + \frac{1}{3}}\right)^3 \left(\frac{1000}{\sqrt{3}}\right)} = 1 \Rightarrow A_0 f \approx 890$$


for stability

* Worst-case scenario: largest possible $A_0 f$

\Rightarrow largest possible f

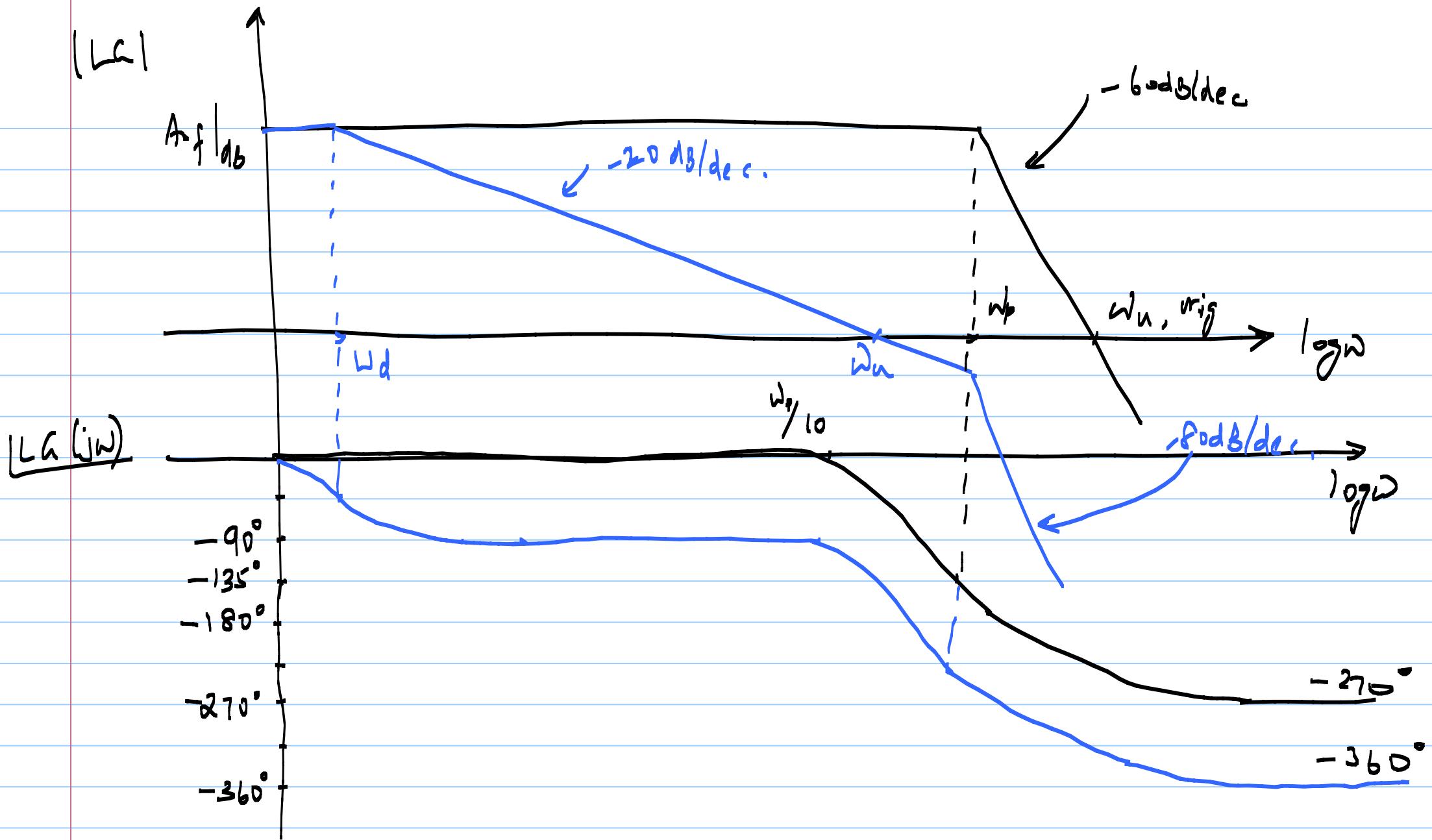$\Rightarrow f_{max} = 1$ i.e. unit gain amplifier



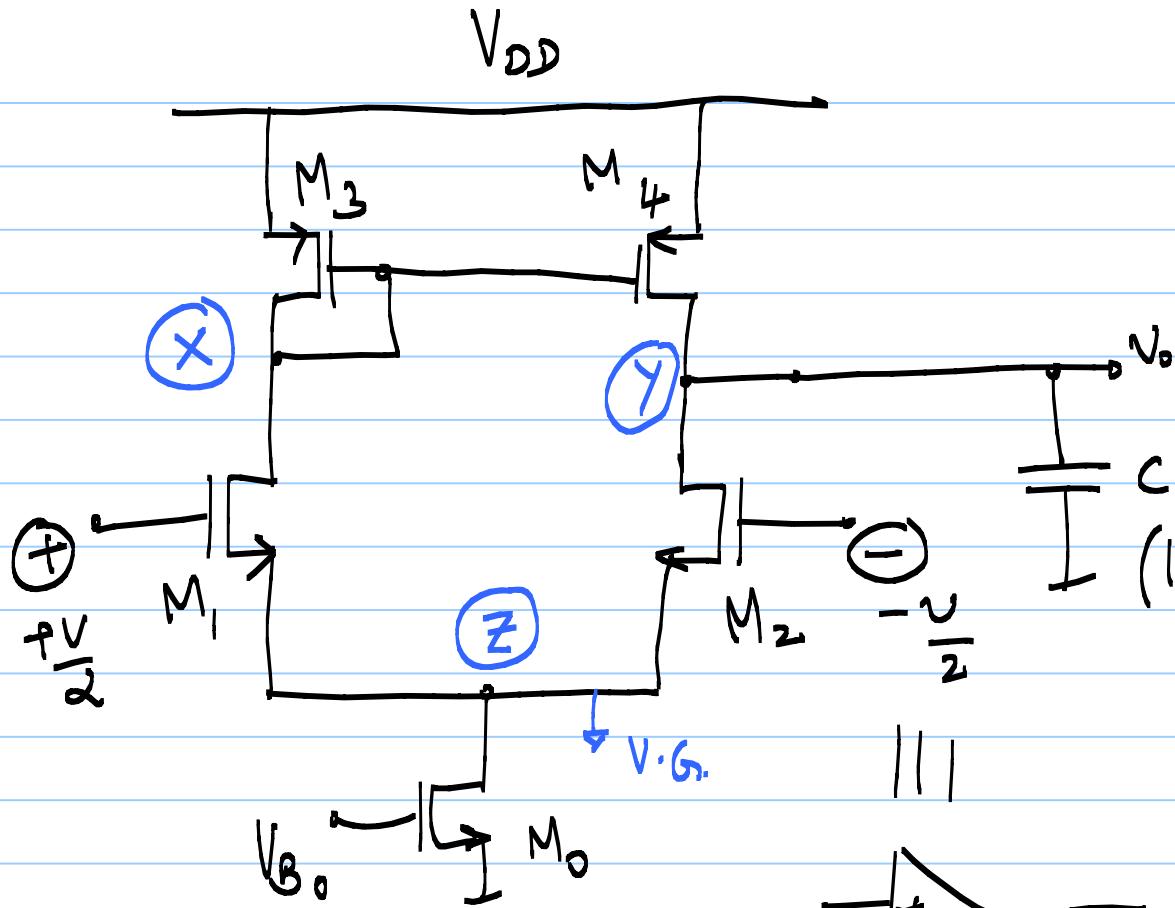


$$A_0 = g_{m_1} \left(r_{ds_2} || r_{ds_4} \right)$$

$$A(s) = g_{m_1} \left(r_{ds_2} || r_{ds_4} || \frac{1}{sC_L} \right)$$

$$= A_0 \frac{1}{1 + \frac{s}{\omega_p}}$$

\times 1-pole system

without parasitics

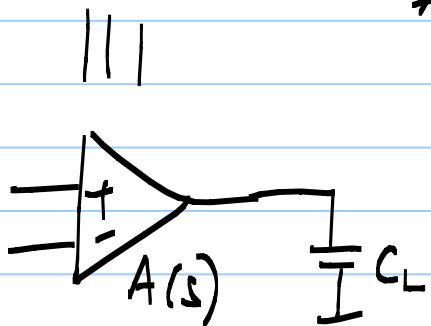

$$A(s) = \frac{g_{m_1}}{g_{ds_2} + g_{ds_4} + sC_L} = \left[\frac{\frac{g_{m_1}}{(g_{ds_2} + g_{ds_4})}}{1 + \frac{sC_L}{g_{ds_2} + g_{ds_4}}} \right] \cdot \frac{1}{1 + \frac{sC_L}{g_{ds_2} + g_{ds_4}}}$$

$$\omega_b = \frac{g_{ds_2} + g_{ds_4}}{C_L} = \frac{1}{(r_{ds_2} || r_{ds_4}) \cdot C_L}$$

* Ignore G_d


$$C_x = C_{gs_3} + C_{gs_4} + C_{db_3} + C_{db_1} \approx 2 C_{gs}$$

$$C_y = C_L + C_{db_2} + C_{db_4} \approx C_L$$

$$C_z = C_{db_0} + C_{gs_1} + C_{gs_2} \leftarrow \text{No DM current}$$

$$+ C_{sb_1} + C_{sb_2} \quad \text{through } C_z$$

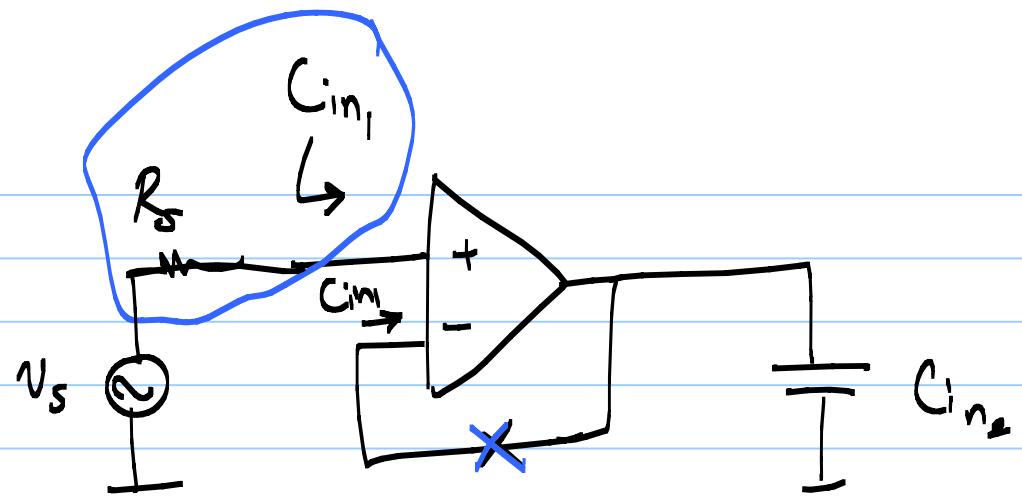* 2-pole system when parasitic caps are taken into account




$$C_L = C_{in_1} + C_{in_2}$$


22/10/2020

Lecture 43

parasitic cap. @ x & y

2 poles in A(s)

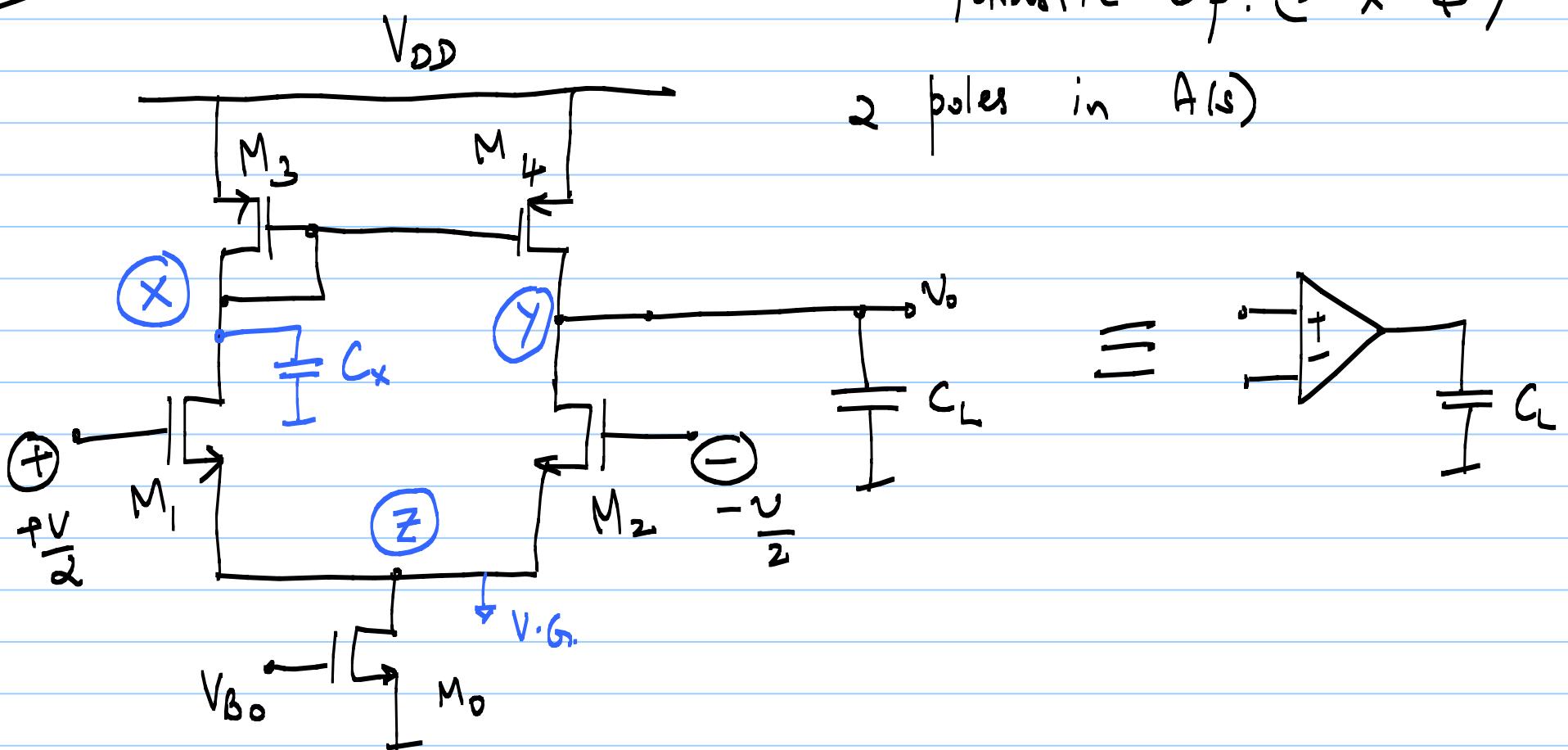

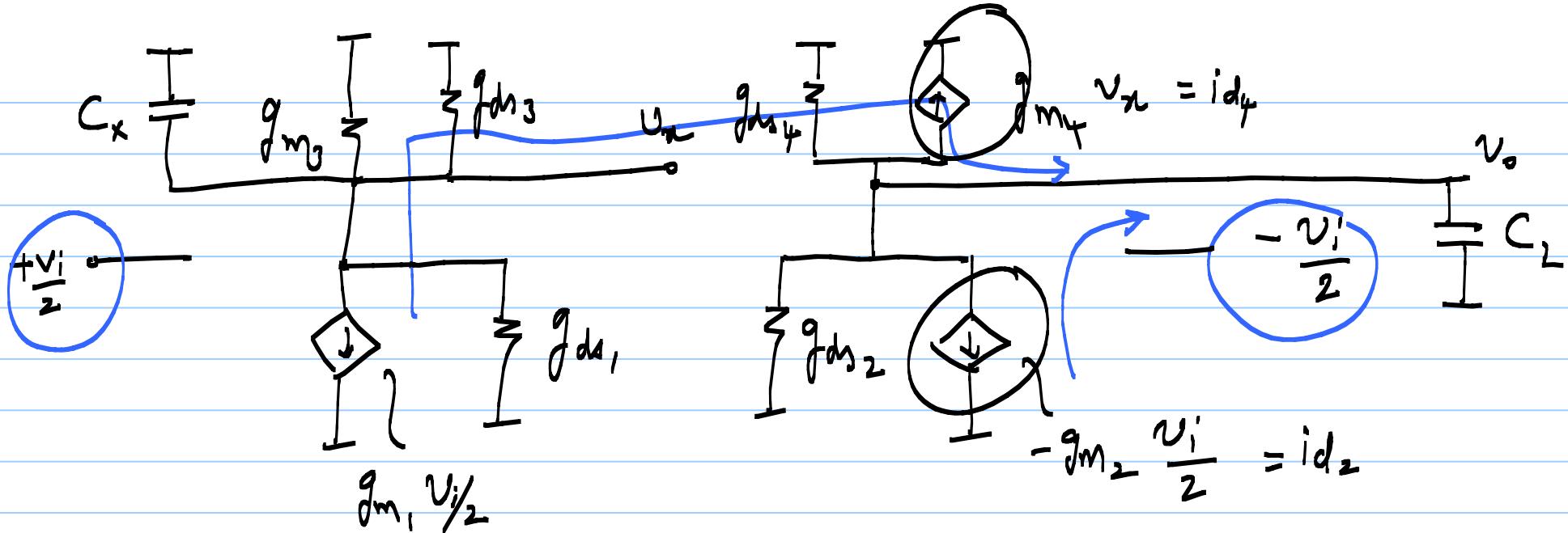

* all g_m 's \gg all g_{ds} 's

$$v_x = - \frac{+g_{m_1} v_i / 2}{g_{m_3} + g_{ds_3} + g_{ds_1} + sC_x} \approx \frac{-g_{m_1} v_i / 2}{g_{m_3} + sC_x}$$

$$v_x \approx \frac{-g_{m_1}}{g_{m_3}} \cdot \frac{1}{1 + \frac{sC_x}{g_{m_3}}} \cdot \frac{v_i}{2}$$

$$id_4 = g_{m_4} \cdot v_x$$

$$= \frac{-g_{m_1}}{1 + \frac{\delta c_x}{g_{m_3}}} \cdot \frac{v_i}{2}$$

$$id_2 = -g_{m_2} v_i/2$$

$$(id_2 + id_4)$$

$$v_o = -\frac{g_{ds_2} + g_{ds_4} + \delta c_L}{g_{ds_2} + g_{ds_4} + \delta c_L}$$

$$v_o = -\frac{-g_{m_2} v_i/2 - \frac{g_{m_1}}{1 + \delta c_x/g_{m_3}} \cdot v_i/2}{g_{ds_2} + g_{ds_4} + \delta c_L}$$

$$= \frac{\frac{g_{m_1} v_i}{g_{d_2} + g_{d_4}} - \frac{\frac{1}{2} + \frac{\frac{1}{2}}{1 + \frac{\delta C_x / g_{m_3}}{1 + \frac{\delta C_L}{g_{d_2} + g_{d_4}}}}{1 + \frac{\delta C_L}{g_{d_2} + g_{d_4}}}}$$

$$\boxed{\frac{v_o}{v_i} = \frac{g_{m_1}}{g_{d_2} + g_{d_4}} \cdot \frac{\left(1 + \frac{\delta C_x / 2 g_{m_3}}{1 + \delta C_x / g_{m_3}}\right)}{\left(1 + \frac{\delta C_L}{g_{d_2} + g_{d_4}}\right) \left(1 + \frac{\delta C_L / (g_{d_2} + g_{d_4})}{1 + \delta C_x / g_{m_3}}\right)}}$$

* $A_o = \frac{g_{m_1}}{g_{d_2} + g_{d_4}}$

* 2 poles $\rightarrow @ \textcircled{x}, \textcircled{y}$



* 1 zero $@ 2 g_{m_3} / C_x$

$$p_1 = \frac{g_{ds2} + g_{ds3}}{C_L}$$

$$p_2 = \frac{g_{m3}}{C_X}$$


$$z = 2p_2 = \frac{2g_{m3}}{C_X}$$

Ideal 1-stage opamp :

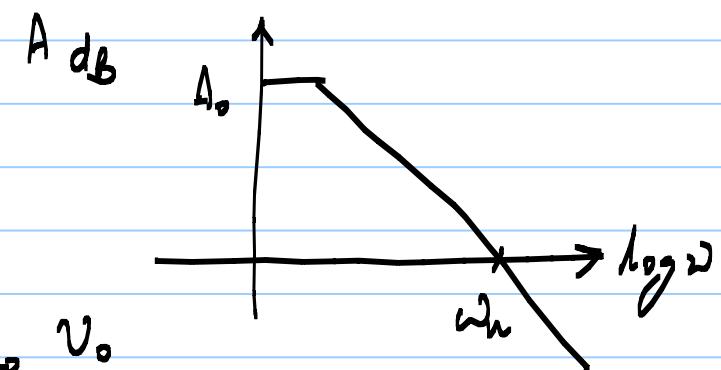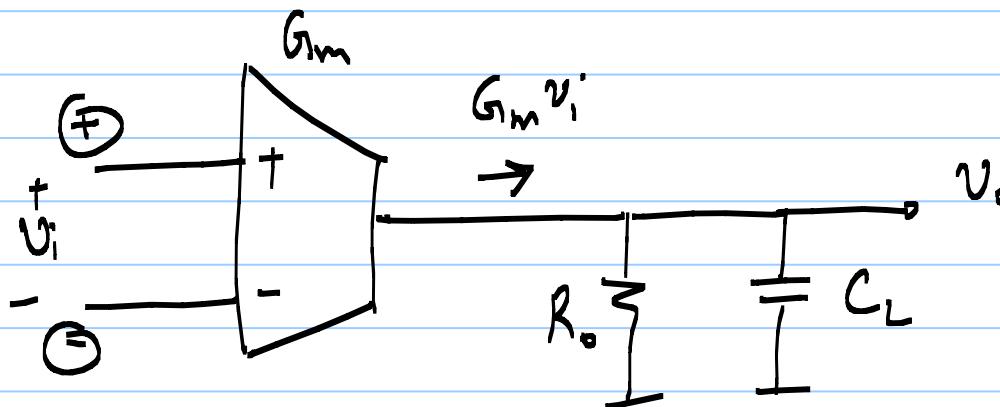


$$\omega_n = \frac{G_m}{C_L} = \frac{g_{m1}}{C_L}$$
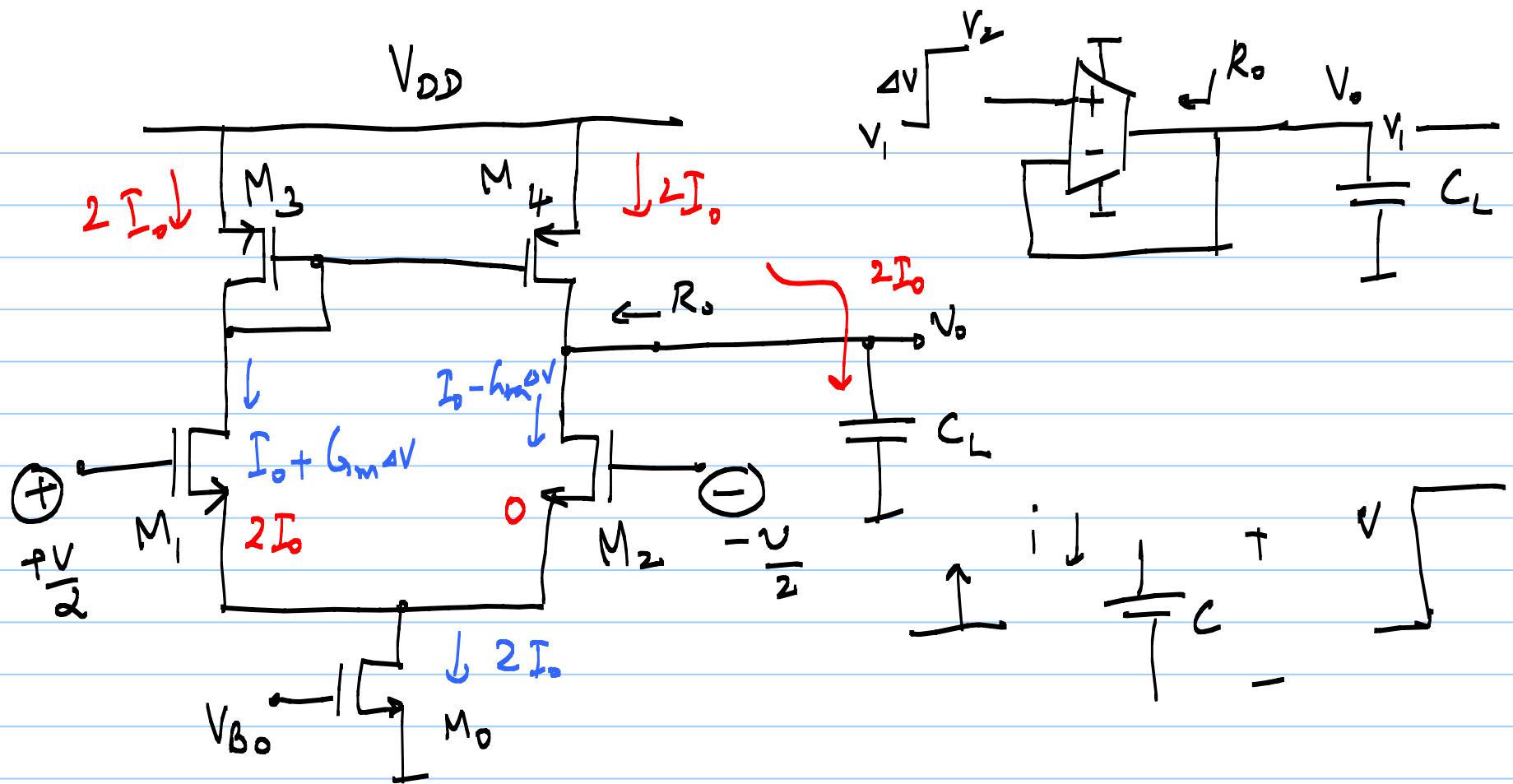
$$G_m = g_m; \quad R_o = r_{ds2} \parallel r_{ds4}; \quad A_o = G_m R_o = g_{m1} (r_{ds2} \parallel r_{ds4})$$



@ $t = 0^+$:


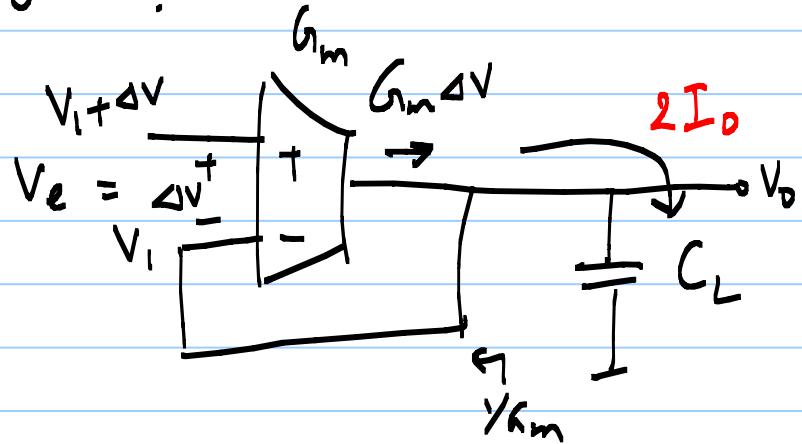


$V_o(t)$ approaches 0


as C_L charges towards

$$V_i + \Delta V$$

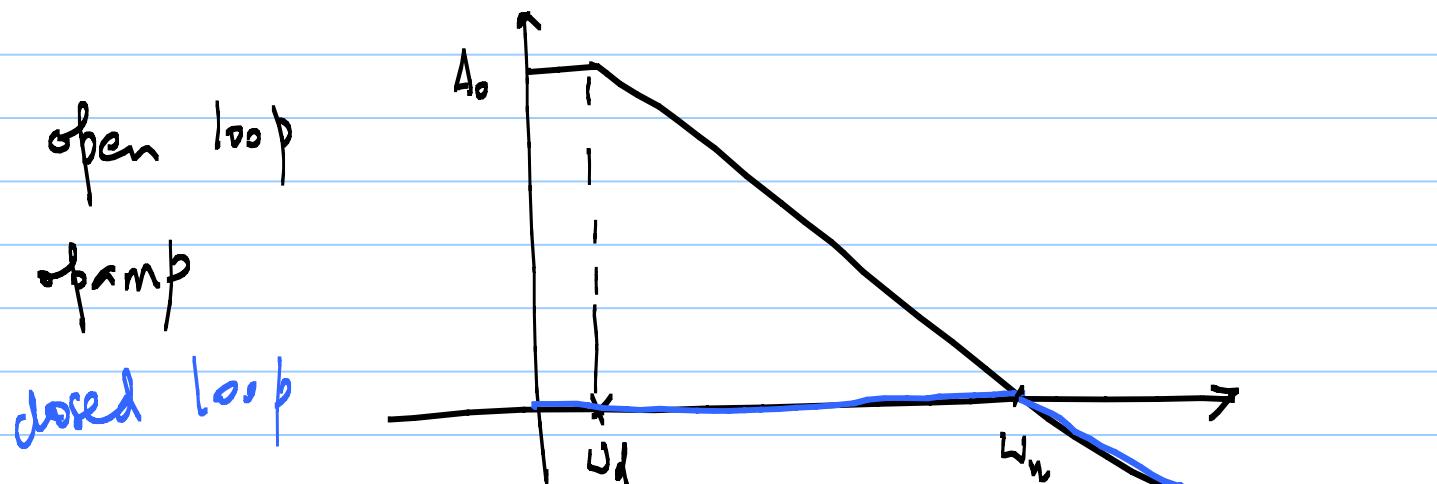
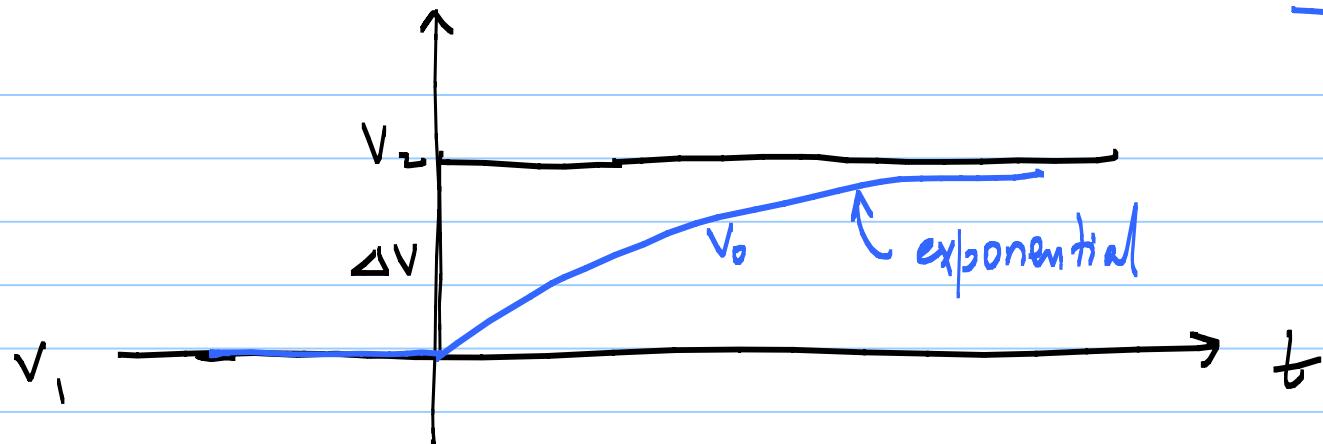
$$\bar{T} = \frac{1}{\omega_m} = \frac{C_L}{G_m}$$



No ω Start ↑ ΔV


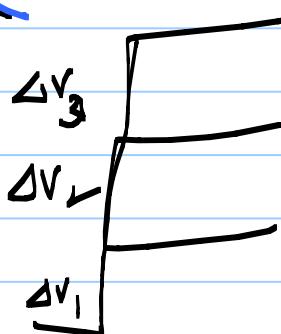


$$i_o \Big|_{t=0^+} = G_m \cdot \Delta V$$

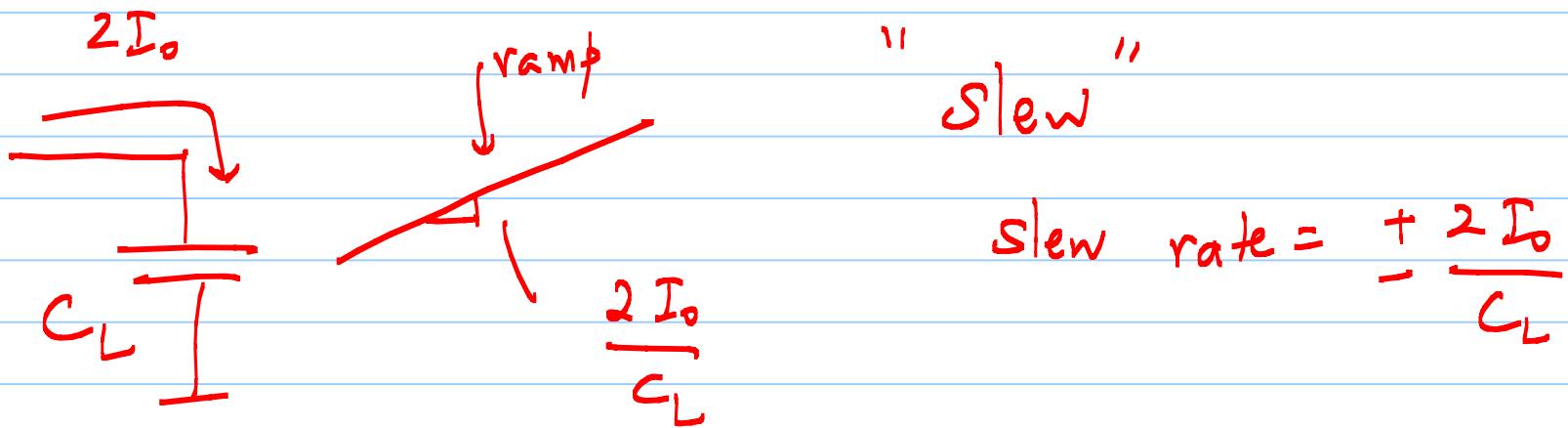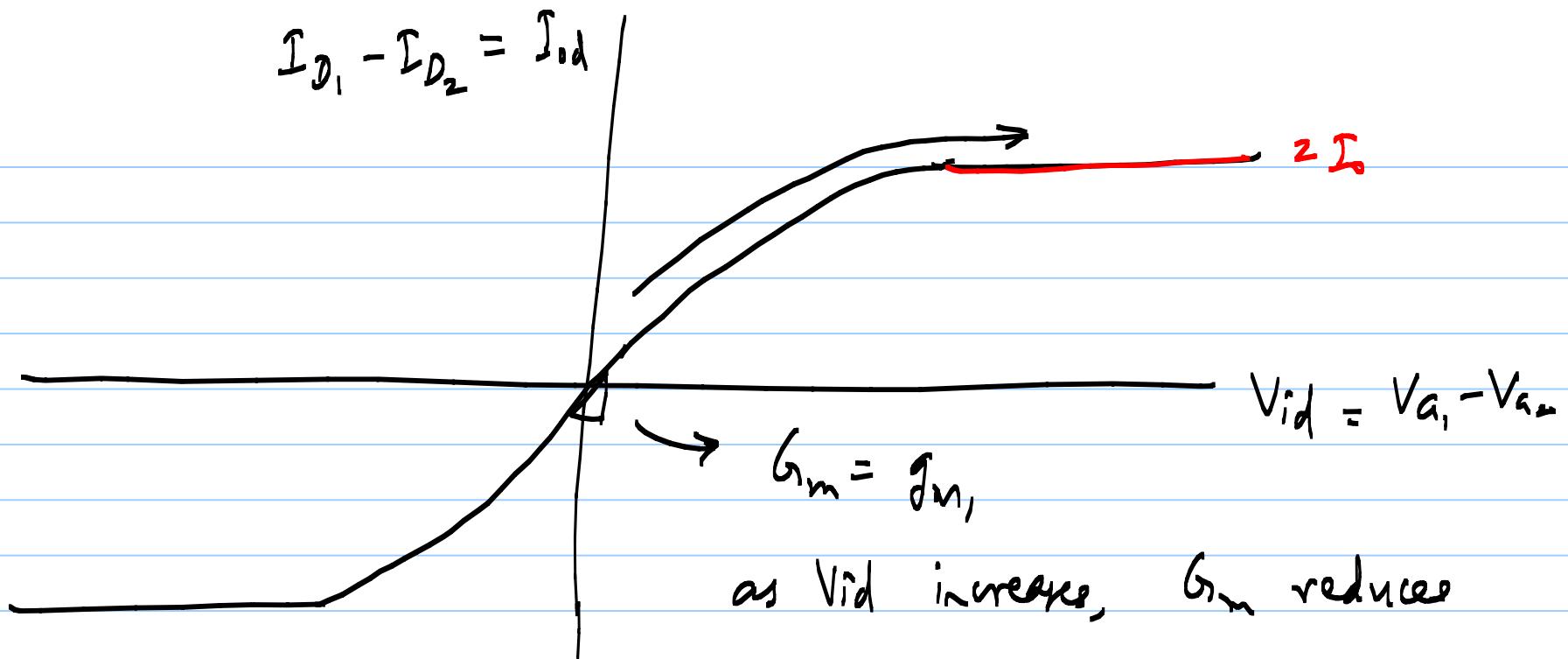

23 | 10 | 20 20

Lecture 44

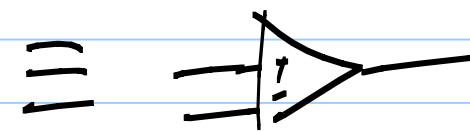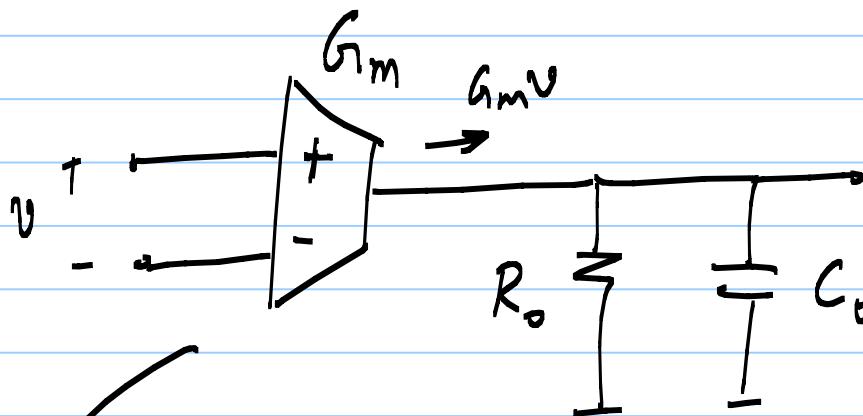


$$R_o = (r_{d1} \parallel r_{d2})$$

$$A_o = G_m R_o$$

$$\omega_d = \frac{1}{R_o C_o}$$

$$\omega_u = \frac{G_m}{C_o}$$

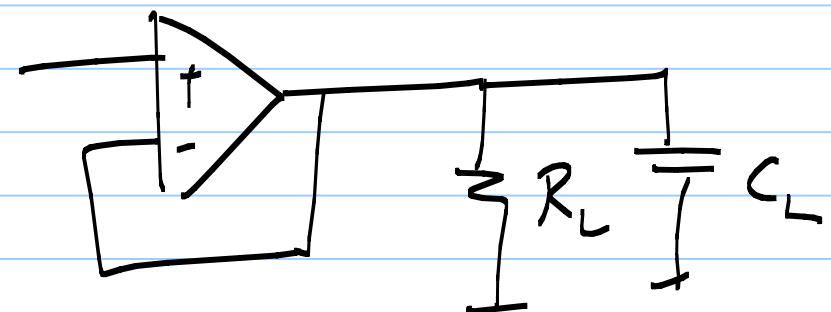

$$A_o' = G_m (R_o \parallel R_L) ; \quad \omega_d' = \frac{1}{(R_o \parallel R_L)(C_o + C_L)}$$

$$\omega_u = \frac{G_m}{(C_o + C_L)} \quad \checkmark$$


$$R_o \parallel R_L = R_L \parallel r_{ds_2} \parallel r_{ds_4} \approx R_L$$

$$A = g_m, (r_{ds_2} \parallel r_{ds_4})$$

$A_o' = g_m, R_L$ extremely small compared to A_o

steady state V_o can be large


→ need a 2-stage opamp

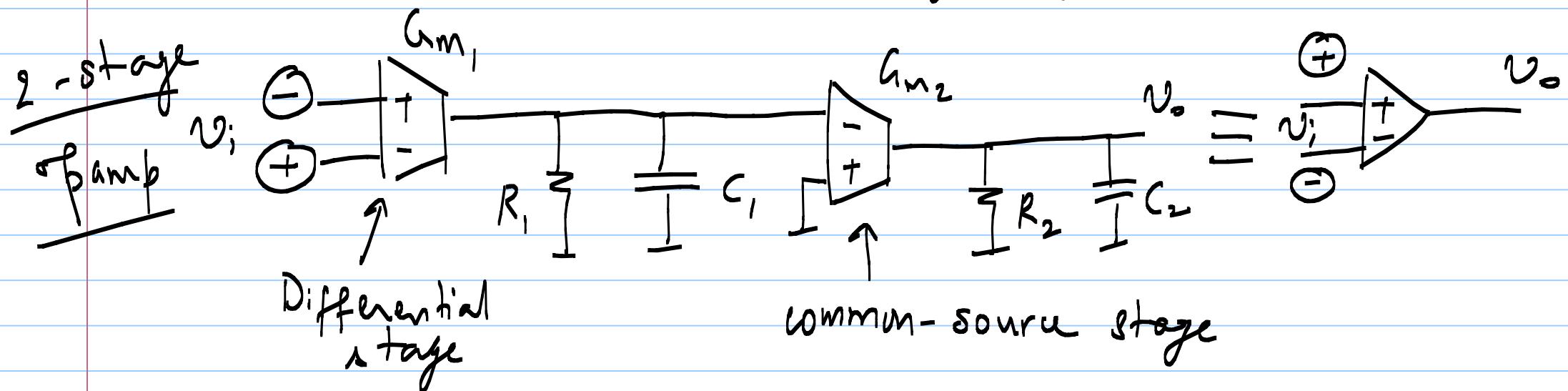

$$A_o = A_1 \cdot A_2$$

$$= g_{m1} R_1 \cdot g_{m2} R_2$$

~~resistive load~~

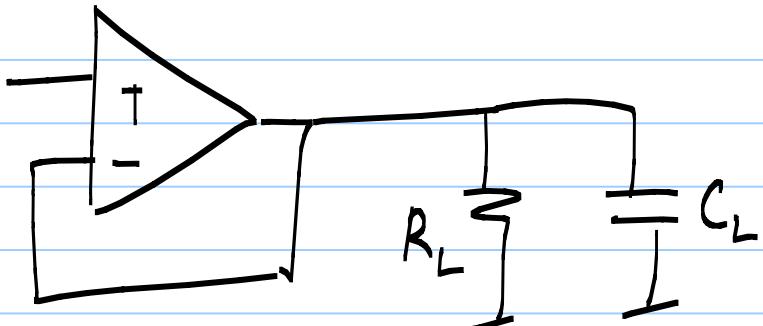

$$A'_o = g_{m1} R_1 \cdot g_{m2} (R_2 || R_L)$$

$$\approx \underbrace{g_{m1} R_1}_{\text{DC gain from 1st stage}} \cdot g_{m2} R_L$$


DC gain from
1st stage is preserved

$$g_{m1} = g_{m1}$$

$$g_{m2} = g_{m2}$$

$$R_1 = r_{ds2} || r_{ds4}$$

$$R_2 = r_{ds5} || r_{ds6}$$

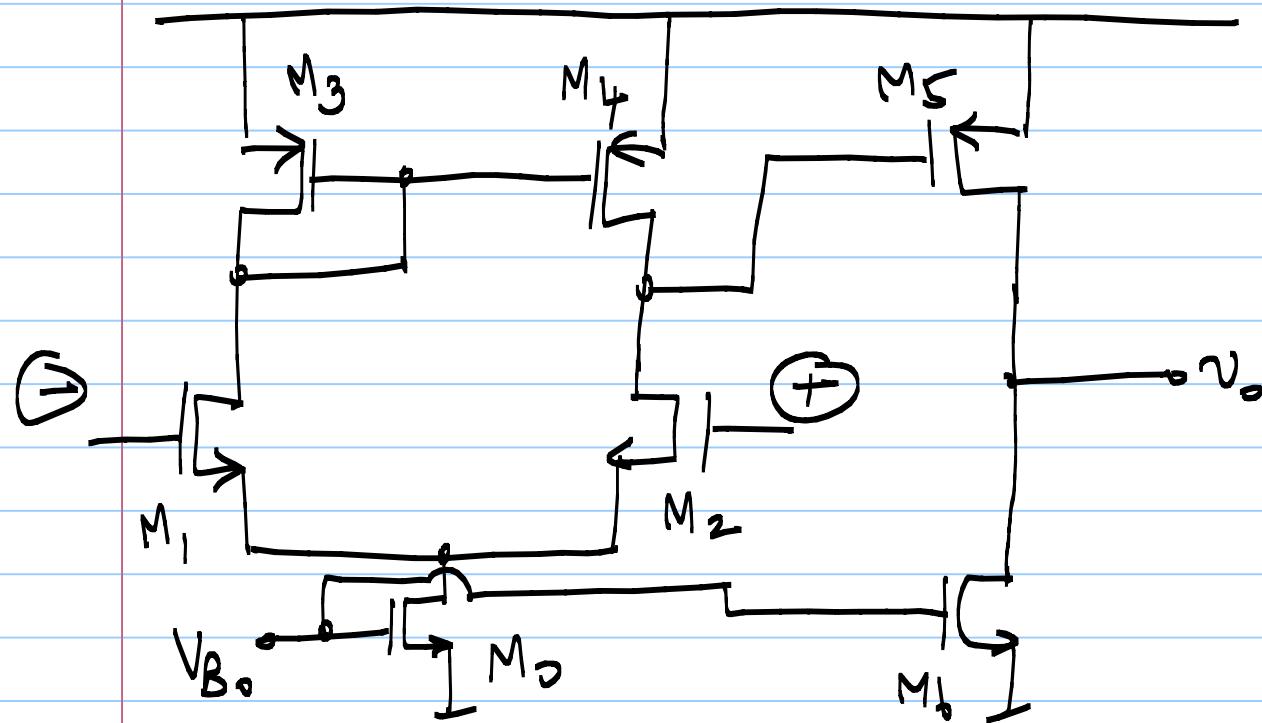


$$C_1 = C_{g_{1s}} + C_{db_4} + C_{db_2} \approx C_{g_{5s}}$$

$$C_2 = C_{db_5} + C_{db_1}$$

A If opamp is driving C_L

check to see
if these are
valid
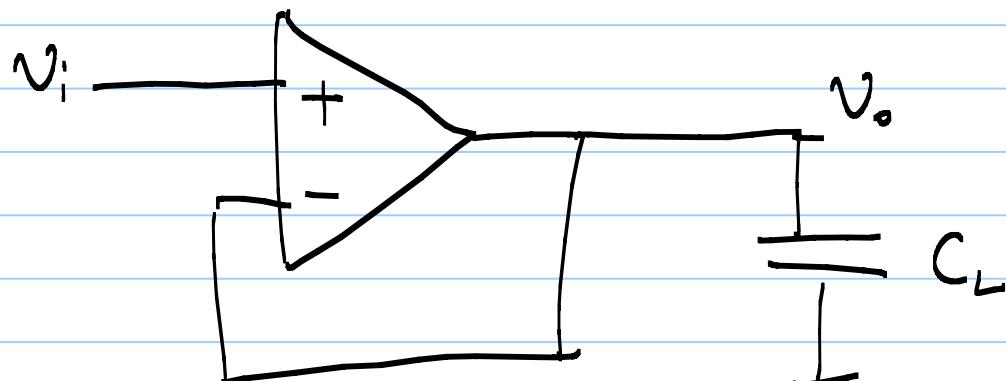
$$C_2 = C_L + C_{db_5} + C_{1b_6} \approx C_L$$



$$A_1 = A_1(s)$$

$$A_2 = A_2(s)$$

$$A(s) = A_1(s) A_2(s)$$

→ 2 poles

* How to choose ω_d ?

use P_M , but: $P_M \geq 60^\circ$

$P_{M_{\min.}} = 50^\circ$ etc.



↳ sets $\omega_{d_{\max}}$

* As $\omega_d \downarrow \Rightarrow \omega_n \downarrow$

→ we BW spec. in doted loop amplifier

27/10/2020

Lecture 45

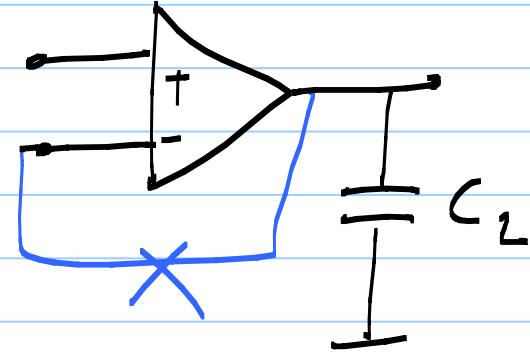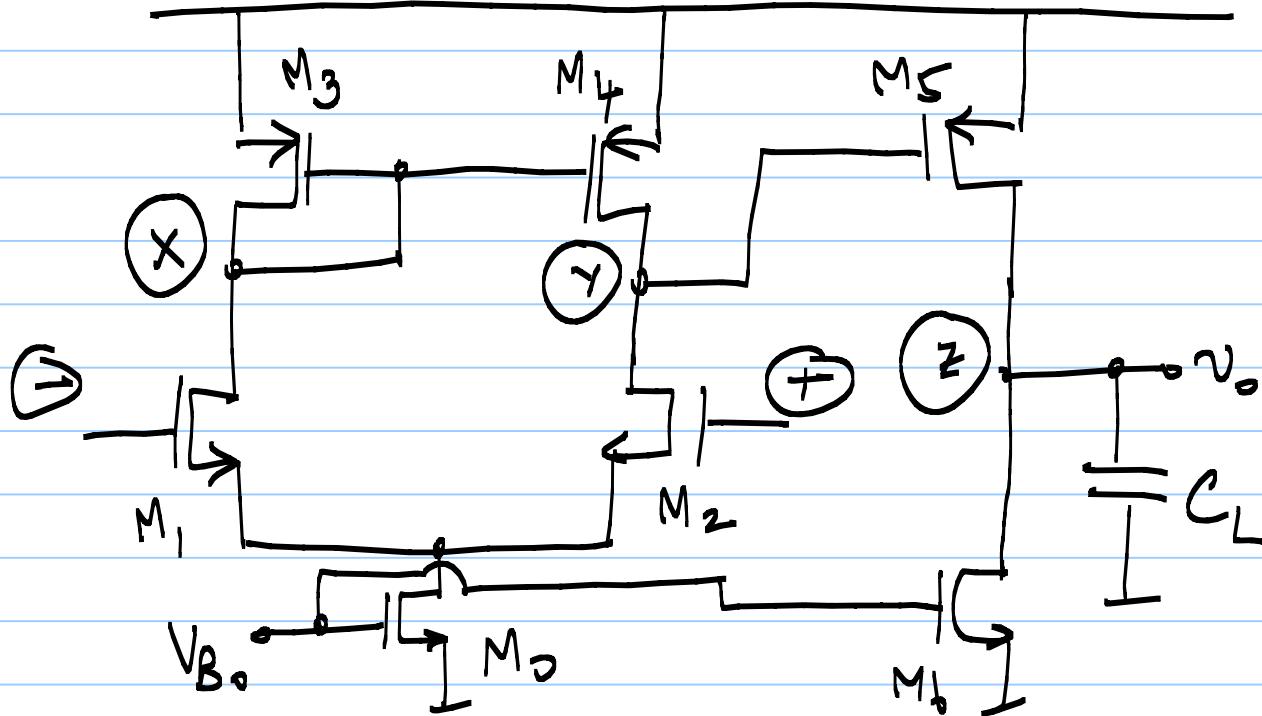

3 poles @ x, y, z

1 zero @ $2p_x (z)$

$$C_x \approx 2(g_{ds_3}) ; \quad C_y \approx (g_{ds_5}) ; \quad C_z \approx C_L$$


$$G_x \approx g_{m_3} ; \quad G_y = g_{ds_2} + g_{ds_4} ; \quad G_z = g_{ds_5} + g_{ds_1}$$

(FLW)

$$p_x \approx \frac{g_{m_3}}{2(g_{ds_3})} ; \quad p_y \approx \frac{g_{ds_2} + g_{ds_4}}{g_{ds_5}} ; \quad p_z \approx \frac{g_{ds_5} + g_{ds_1}}{C_L}$$


$p_x \gg p_y, p_z$; so, ignore p_x & $z_x = 2p_x$

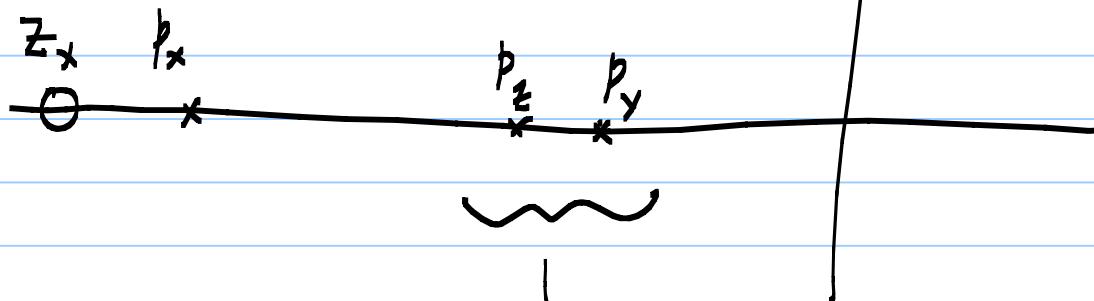so \rightarrow effectively a 2-pole system (p_y & p_z) with high DC gain



high Q , low ω , ringing in step response

problem

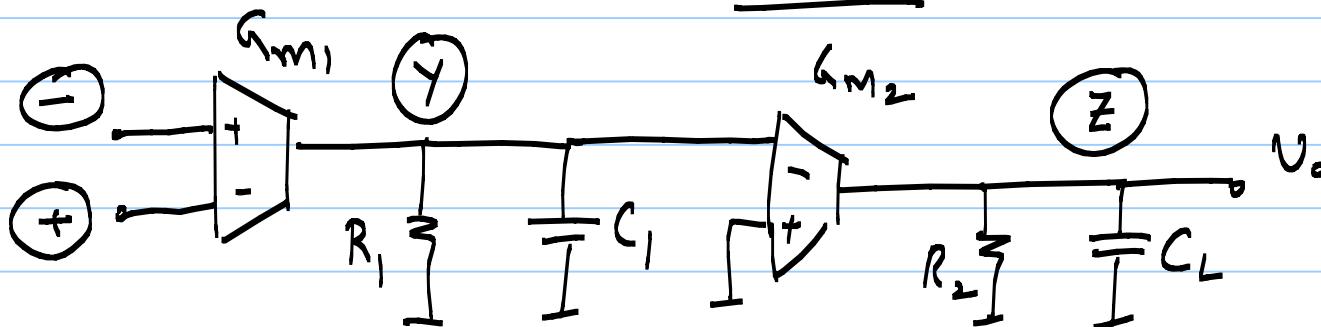


Block level view of
2-stage opamp

$$G_{m_1} = g_{m_1}; \quad G_{m_2} = g_{m_5}$$

$$R_1 = \frac{1}{g_{ds_2} + g_{ds_4}}; \quad R_2 = \frac{1}{g_{ds_5} + g_{ds_6}}$$

$$C_1 = C_{g_{ss5}}; \quad C_2 = C_L$$

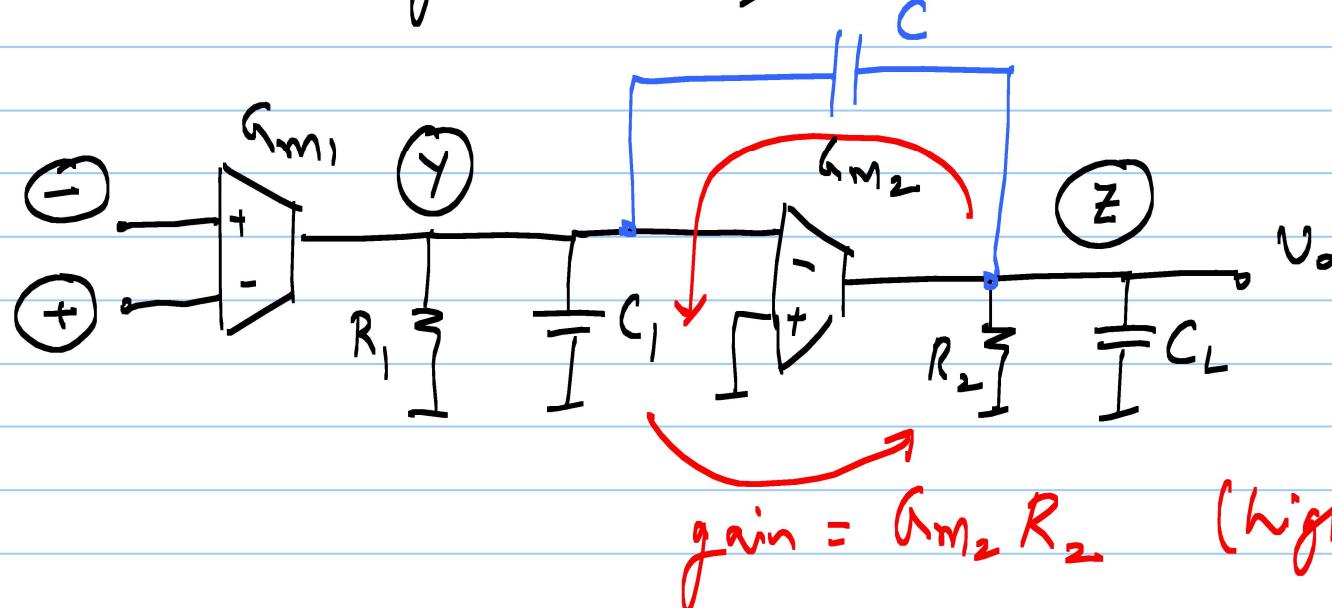


G_2 reduces
due to AC
feedback
through C_f

$$C'_1 \approx C_1 + \underbrace{G_{m_2} R_2 C}_\text{"Miller Capacitance"}$$

$$|p_y'| \approx \frac{1}{R_1 C_1'} \ll |p_y|$$

Dominant pole

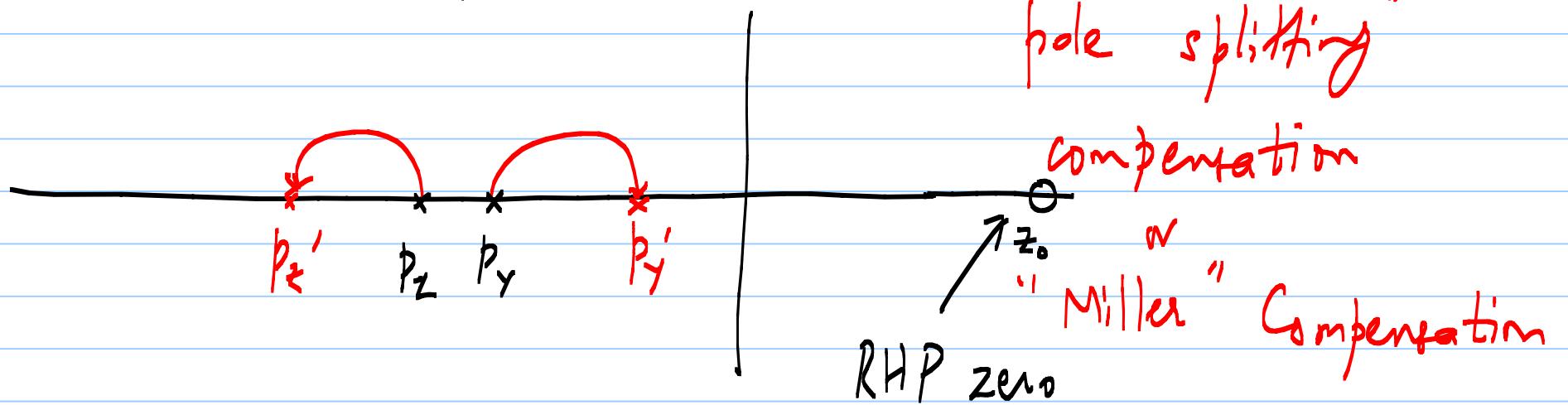



required value of C is small due to

Miller multiplication

HW



G_{out} of \rightarrow

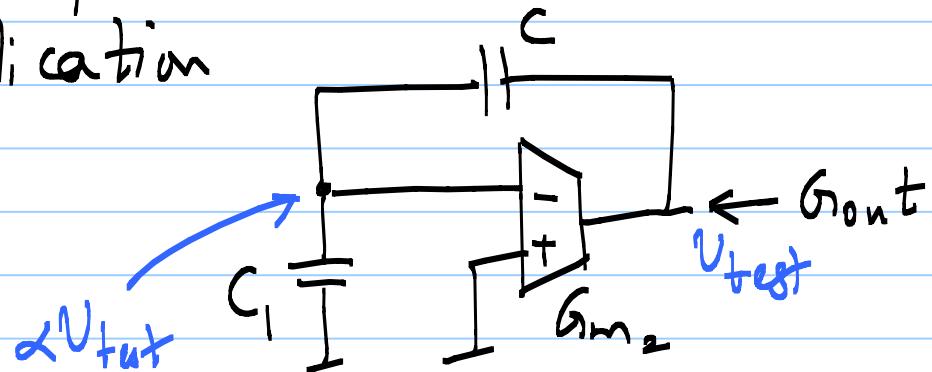

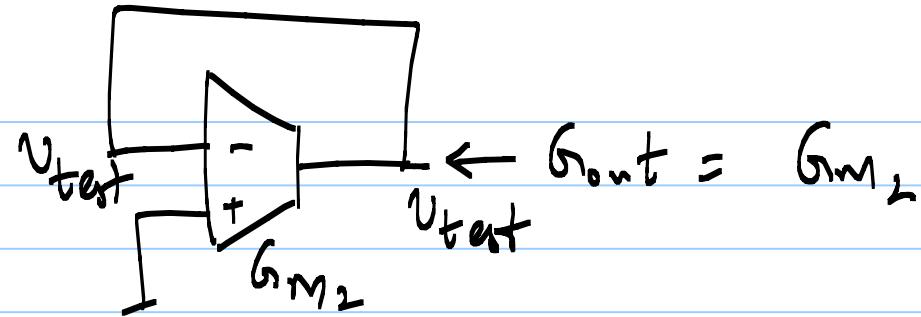

28/10/2020

Lecture 4b

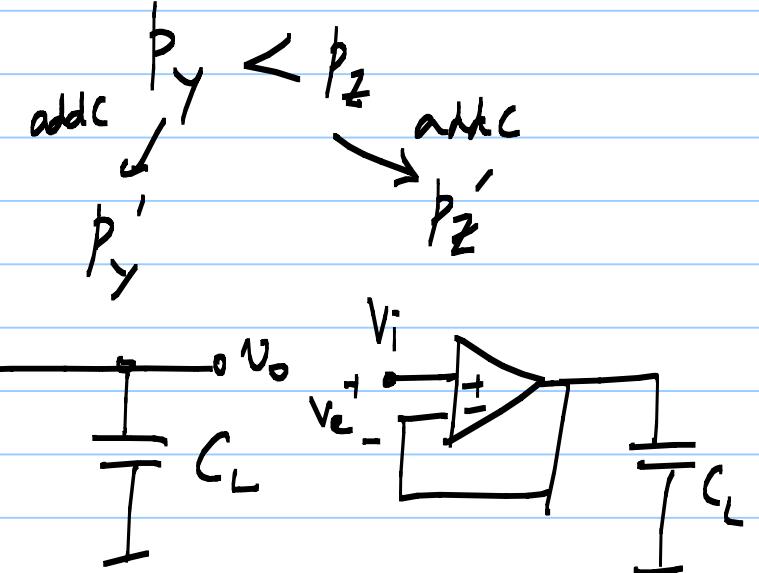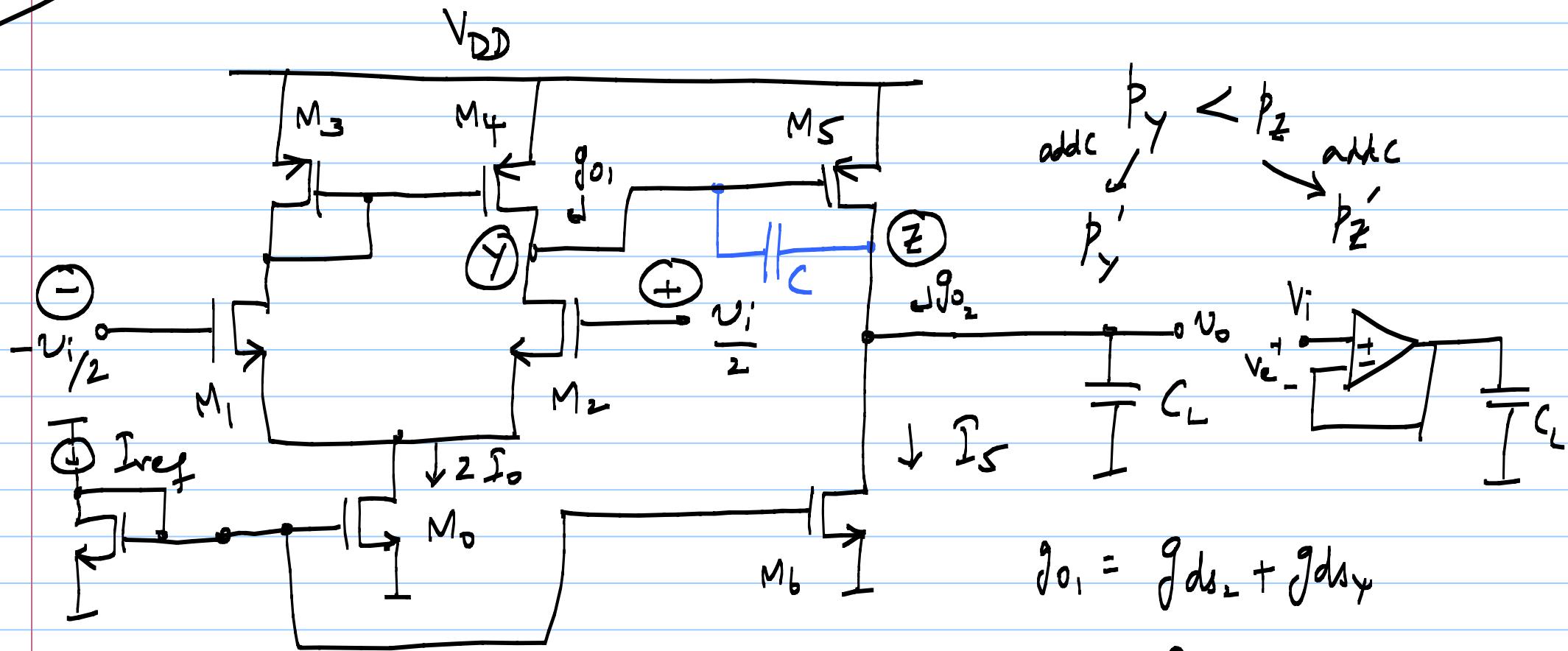

$$g_{o1} = g_{ds2} + g_{ds4}$$

$$g_{o2} = g_{ds5} + g_{ds6}$$

$$A_1 = \frac{g_{m1}}{g_{o1}} ; \quad A_2 = \frac{g_{m5}}{g_{o2}}$$

$$p_y' \approx \frac{g_{o1}}{A_2 \cdot C} \quad \text{dominant pole}$$

$$\underline{DC} \quad V_y = V_{DD} - V_{SG_3} \Big|_{I_o} = V_{DD} - V_{SG_5} \Big|_{I_s}$$

$$V_{SG_3} \Big|_{I_o} = V_{SG_5} \Big|_{I_s}$$

$$V_{SG} = V_T + \underbrace{\sqrt{\frac{2 I_D}{\mu_p C_{ox} \left(\frac{W}{L}\right)}}}_{V_{DSat}}$$

$$L_3 \equiv L_4 \equiv L_5$$


Entire by Design:

$$V_{DSat_3} \Big|_{I_o} = V_{DSat_5} \Big|_{I_s}$$


$$\sqrt{\frac{2 I_o}{\mu_p C_{ox} \left(\frac{W}{L}\right)_S}} = \sqrt{\frac{2 I_s}{\mu_p C_{ox} \left(\frac{W}{L}\right)_S}} \Rightarrow$$

$$\boxed{\frac{I_{D3}}{\left(\frac{W}{L}\right)_3} = \frac{I_{D5}}{\left(\frac{W}{L}\right)_5}}$$

Same "Current Density"

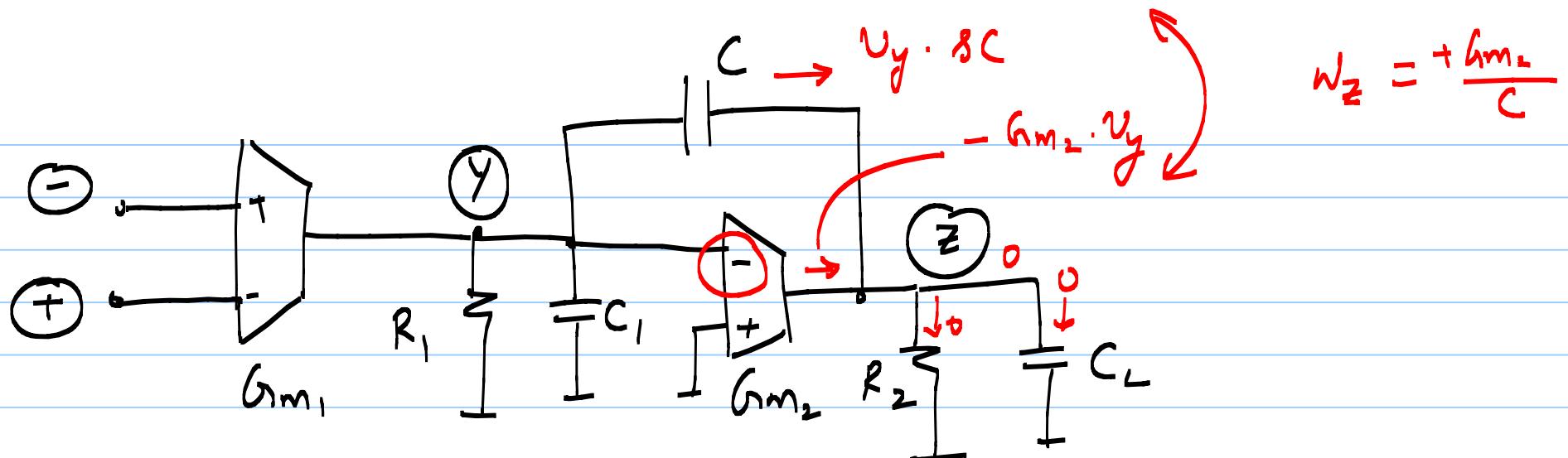
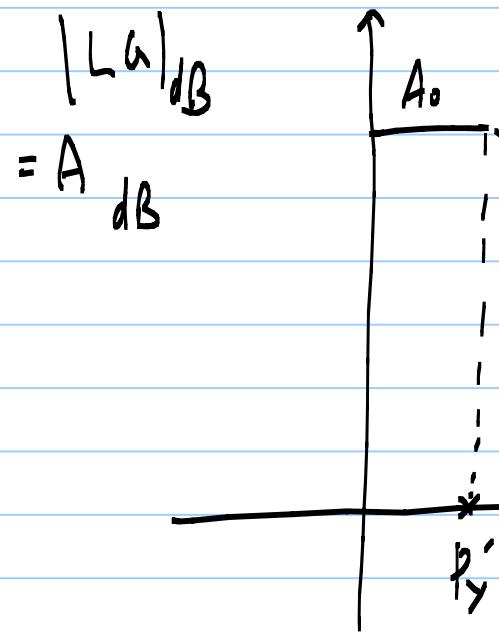
$$p'_y \approx \frac{1}{R_1(G_m_2 R_2 C)} ; \quad p'_z \approx \frac{()}{()}$$



$$\omega_n = A_0 p_y'$$

$$= (G_m_1 R_1) (G_m_2 R_2) \cdot \frac{1}{R_1 G_m_2 R_2 C}$$


$$\boxed{\omega_n = \frac{G_m_1}{C}}$$

$$\omega_z = + \frac{Gm_2}{C} \quad (\text{RHP zero})$$

* Design condition: $Gm_2 > Gm_1$, i.e. $g_{m_2} \gg g_{m_1}$
 so that $\omega_z > \omega_n$

RC - pole splitting compensation

* want to move

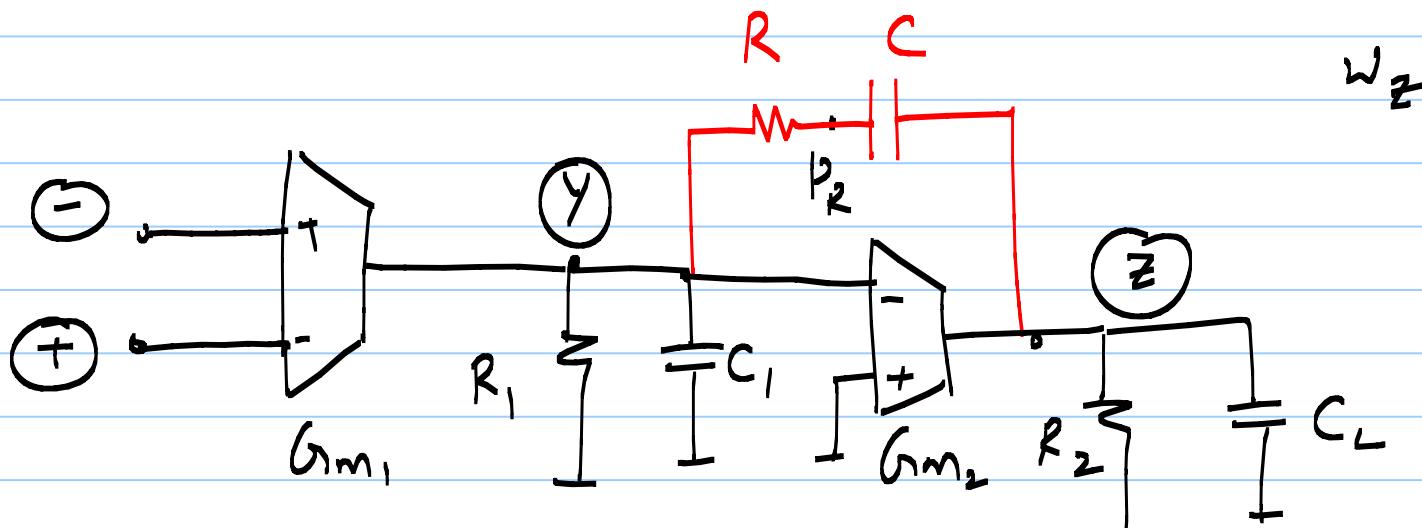


* poles will
move slightly

* 3rd pole
added p_R

$$\omega_z = \frac{1}{\left(\frac{C}{Gm_2} - RC \right)} = \frac{1}{C \left(\frac{1}{Gm_2} - R \right)}$$

1) set $R = \frac{1}{Gm_2}$

$$\Rightarrow \omega_z' = \infty$$

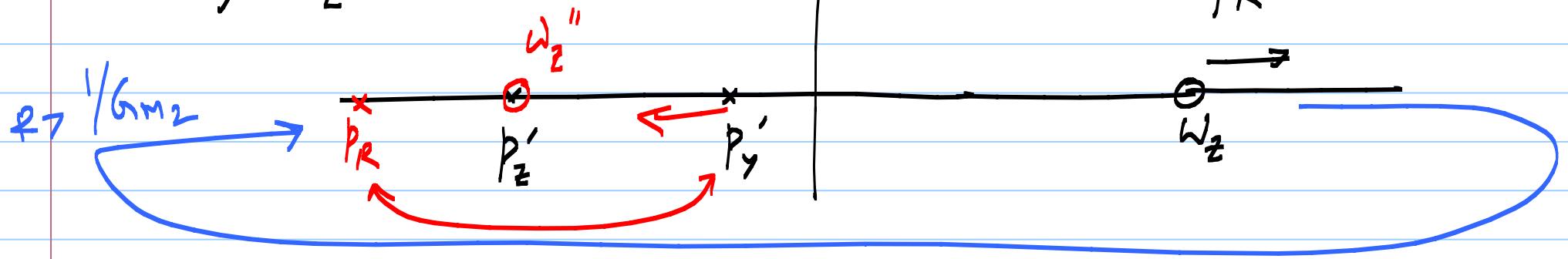


2) $R > \frac{1}{Gm_2} \Rightarrow LHP_{zero}$

choose R to set $\omega_z'' = p_z'$

29/10/2020

Lecture 47


Bipolar Junction Transistor (BJT)

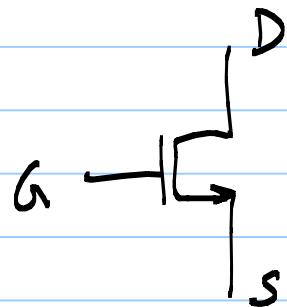

N MOS

Corte - V_{GS}


efect - I_D

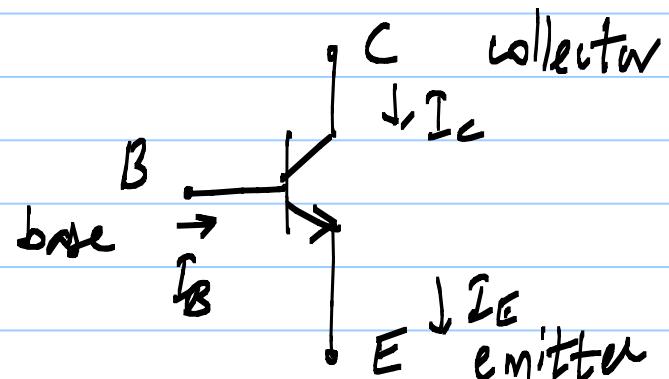

NPN transistor

Corte - V_{BE}

efect - I_c

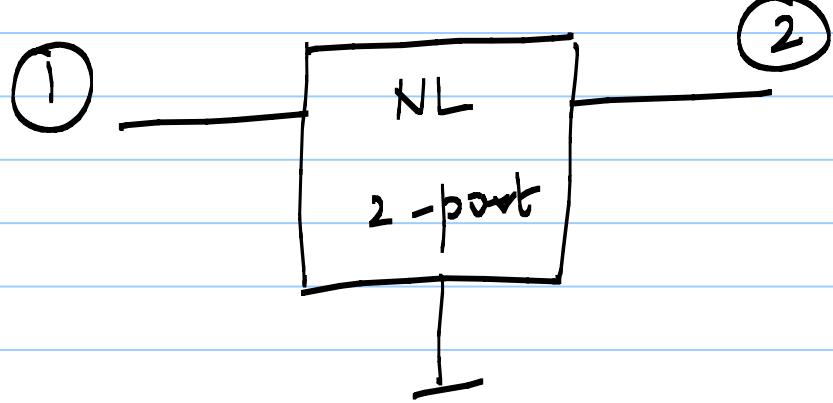

$$[y] = \begin{bmatrix} 0 & 0 \\ y_{21} & 0 \end{bmatrix}$$


as large as possible


$$I_1 = \text{constant}$$

$$I_2 = g(V_1)$$

BJT also

shares these characteristics

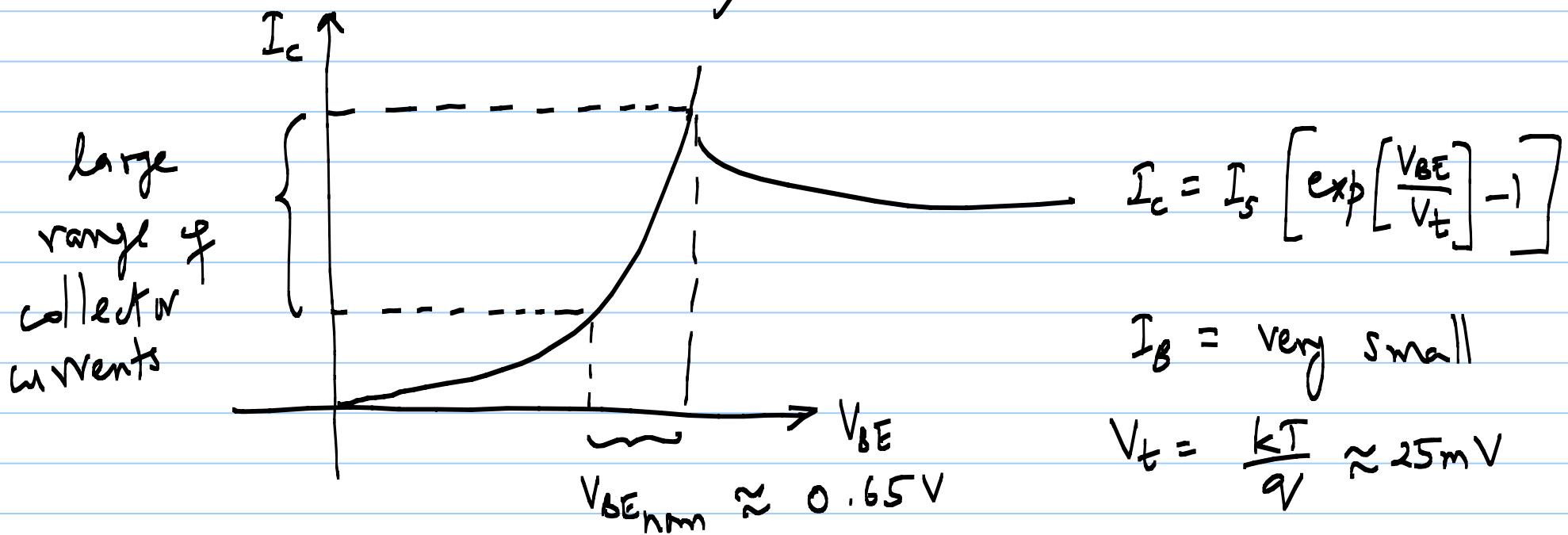

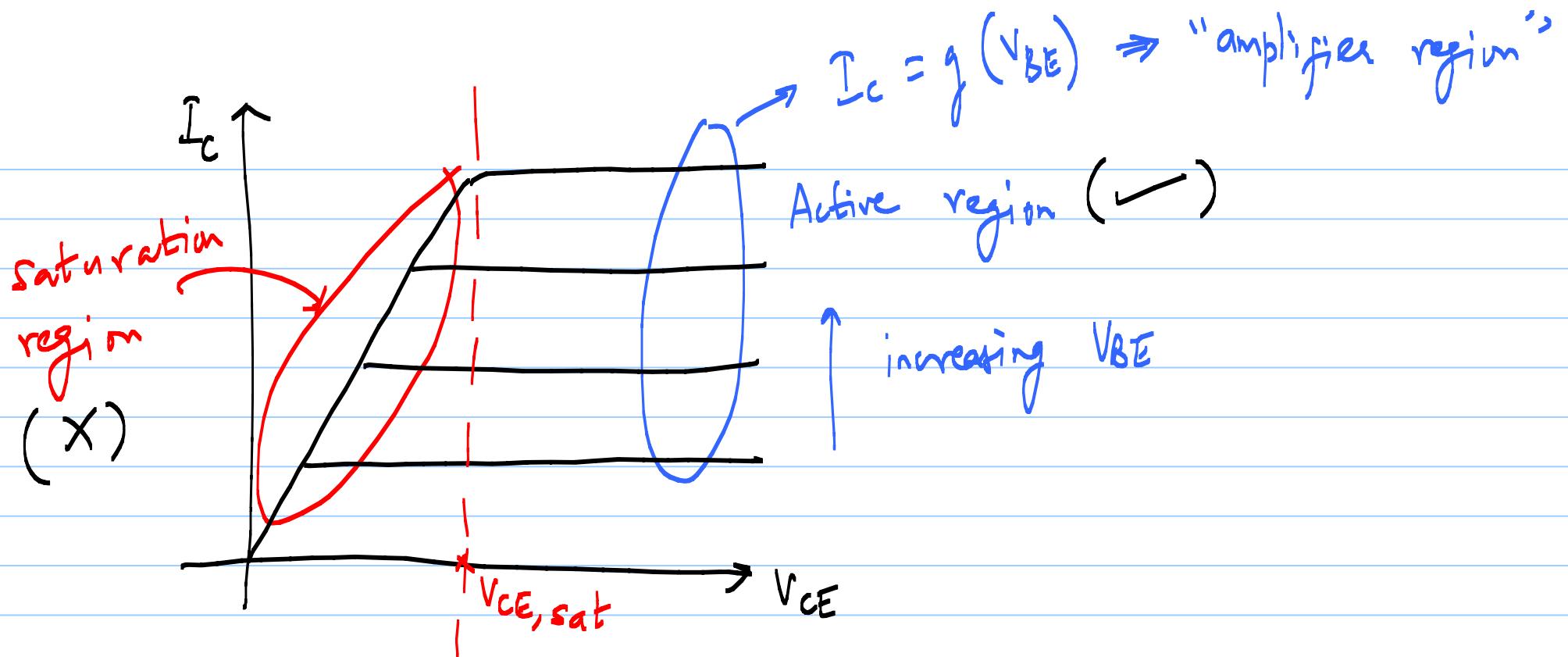

When $V_{CE} > V_{CE,sat} \Rightarrow$ good amplifier

$$V_{BE,om} \approx 0.65V, \quad V_t \approx 25mV$$

* $I_c \approx I_s \exp\left(\frac{V_{BE}}{V_t}\right)$

* $V_{BE} = V_t \ln\left(\frac{I_c}{I_s}\right)$

$$* \quad I_B = \frac{I_C}{\beta}$$

β = current gain of BJT


$\sim 50 - 200$, typically

$$* \quad I_E = I_C + I_B = (\beta + 1) I_B = \left(\frac{\beta + 1}{\beta} \right) I_C$$


* Small signal parameters:

$$y_{11} = \frac{\partial I_B}{\partial V_{BE}} = \frac{1}{\beta} \frac{\partial I_C}{\partial V_{BE}} = \frac{I_C}{\beta V_t} = \frac{g_m}{\beta}$$

$$y_{12} = \frac{\partial I_B}{\partial V_{CE}} = 0$$
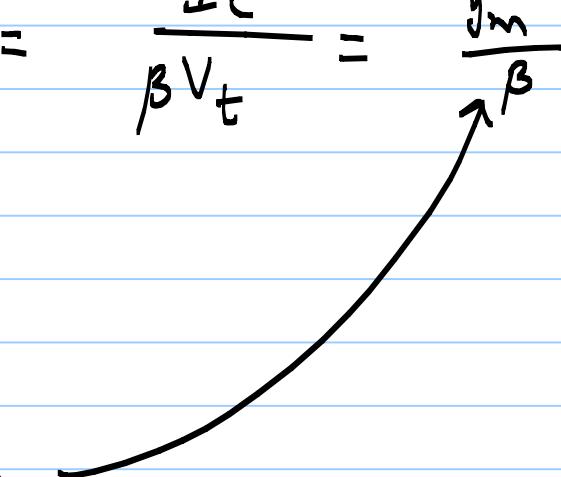
$$y_{21} = \frac{\partial I_C}{\partial V_{BE}} = \frac{I_C}{V_t} = g_m$$

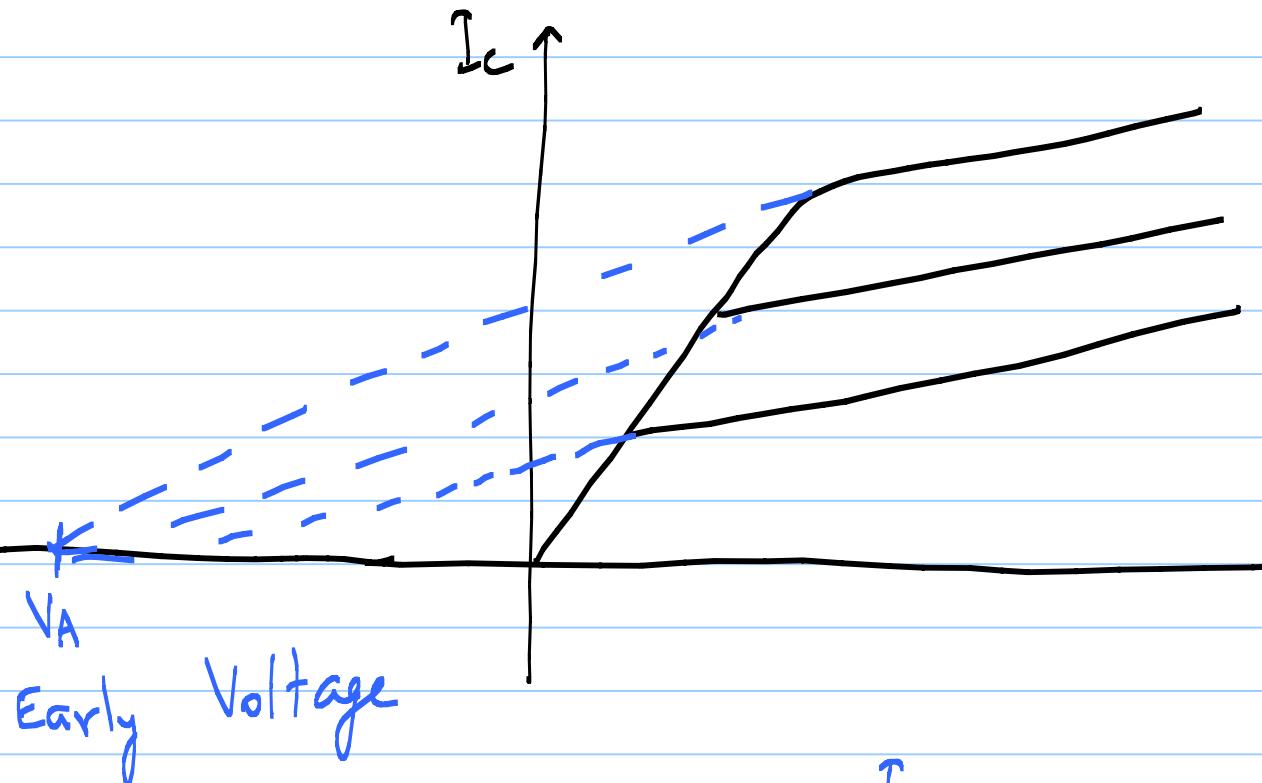
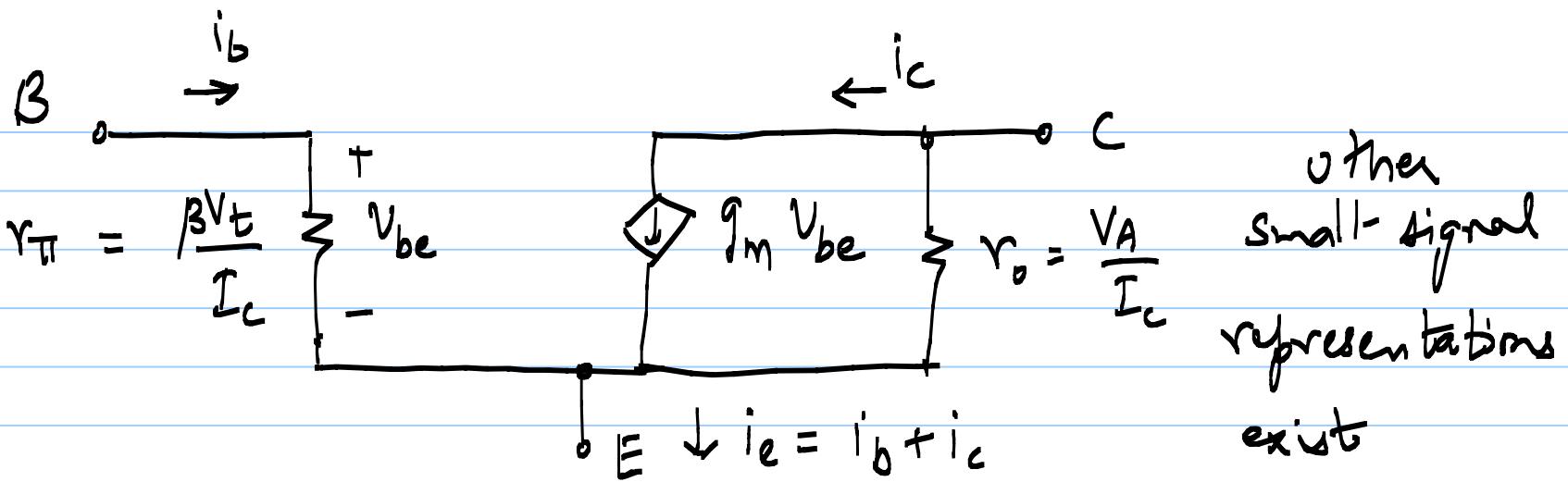
$$y_{22} = \frac{\partial I_C}{\partial V_{CE}} = 0 \quad \left. \begin{array}{l} \text{very small in a} \\ \text{real device} \end{array} \right\}$$




$$I_C = I_s \exp\left(\frac{V_{BE}}{V_t}\right) \left[1 + \frac{V_{CE}}{V_A}\right]$$

$V_A = -\infty$ for an ideal device with $y_{22} = 0$

$$\text{actual } y_{22} = \frac{I_C}{V_A}$$




BJT Amplifiers

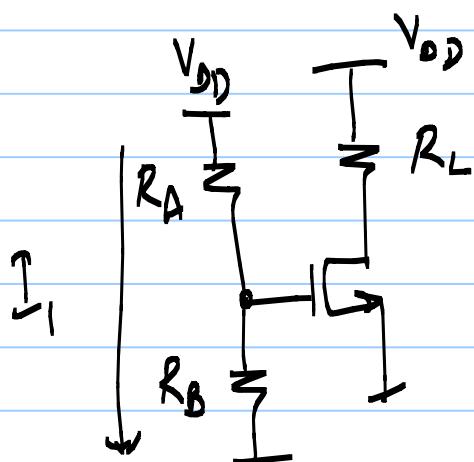


choose R_A, R_B so that

$$R_A \parallel R_B \gg R_s$$

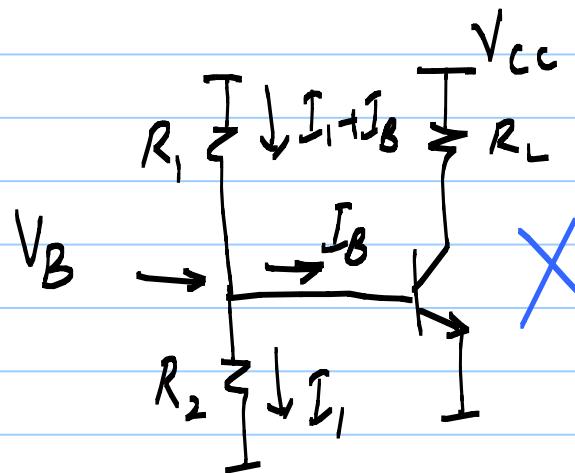

V_B will not be equal to desired bias value due to additional

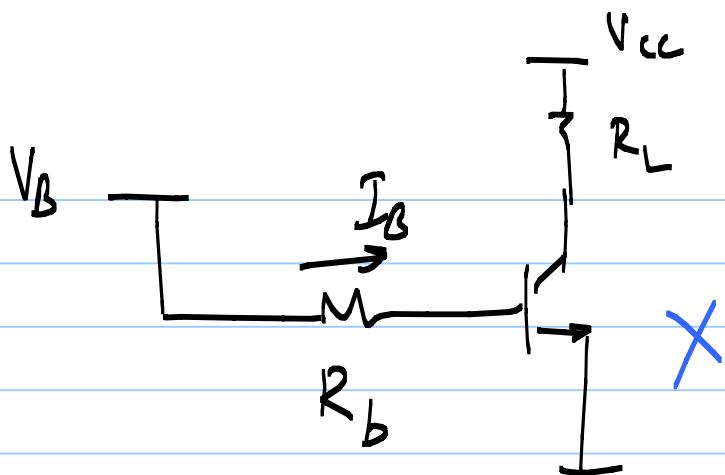
$$\text{i.e. } V_B = f(I_B) \text{ drop across } R_1 = f(I_c)$$



BJT current mirror

o)

$$Q_1 = Q_2$$

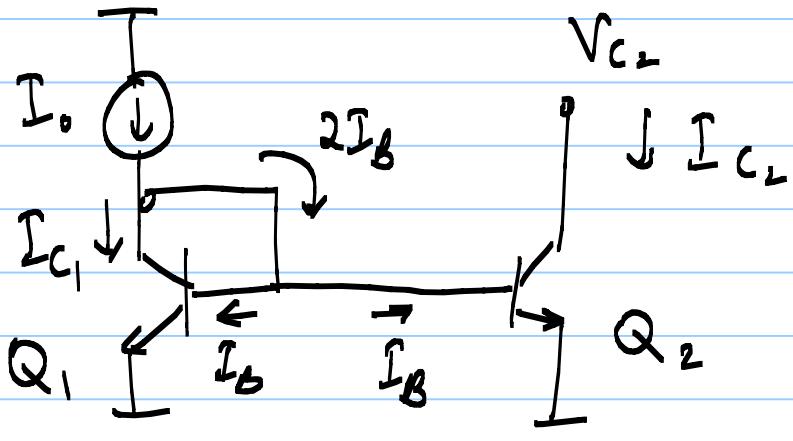

$$I_{C1} = I_o - 2I_B$$

$$I_B = \frac{I_{C1}}{\beta}$$


$$I_{C1} = \frac{I_o \cdot \beta}{\beta + 2}$$

$$V_{BE1} = V_{BE2} \Rightarrow I_{C1} = I_{C2} \Rightarrow I_{B1} = I_{B2} = I_B$$


when $V_{C2} > V_{CEsat}$

3/11/20


Lecture 48

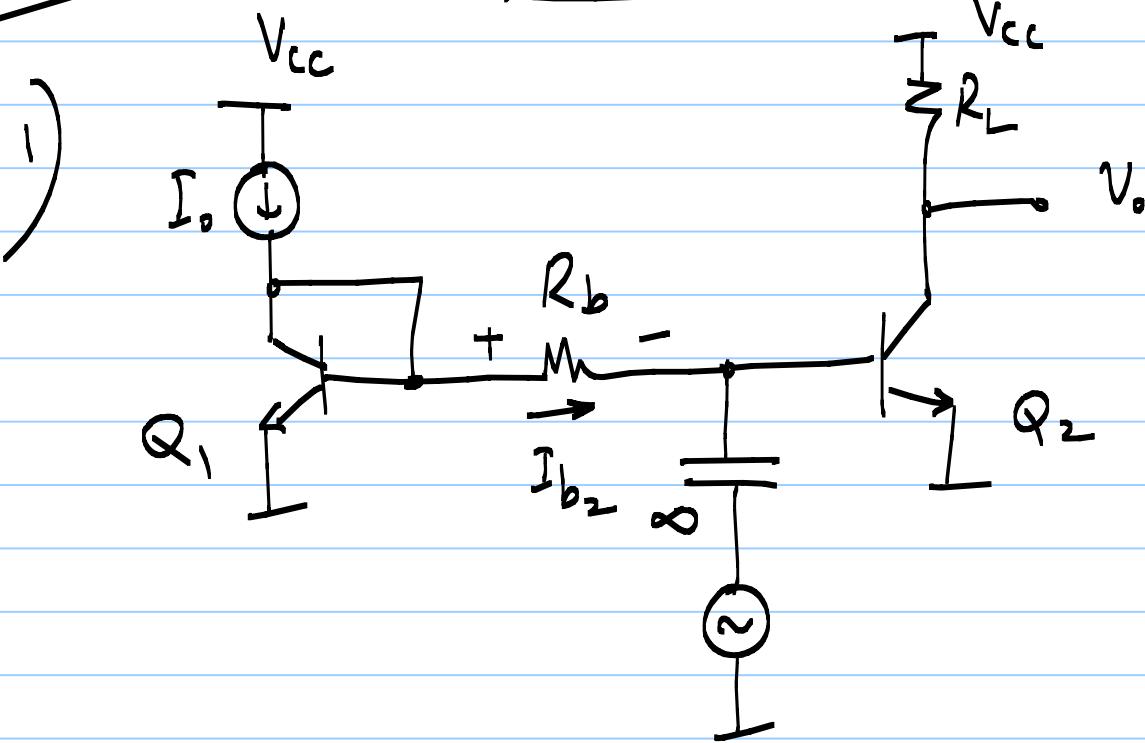

Not a good
way of biasing.

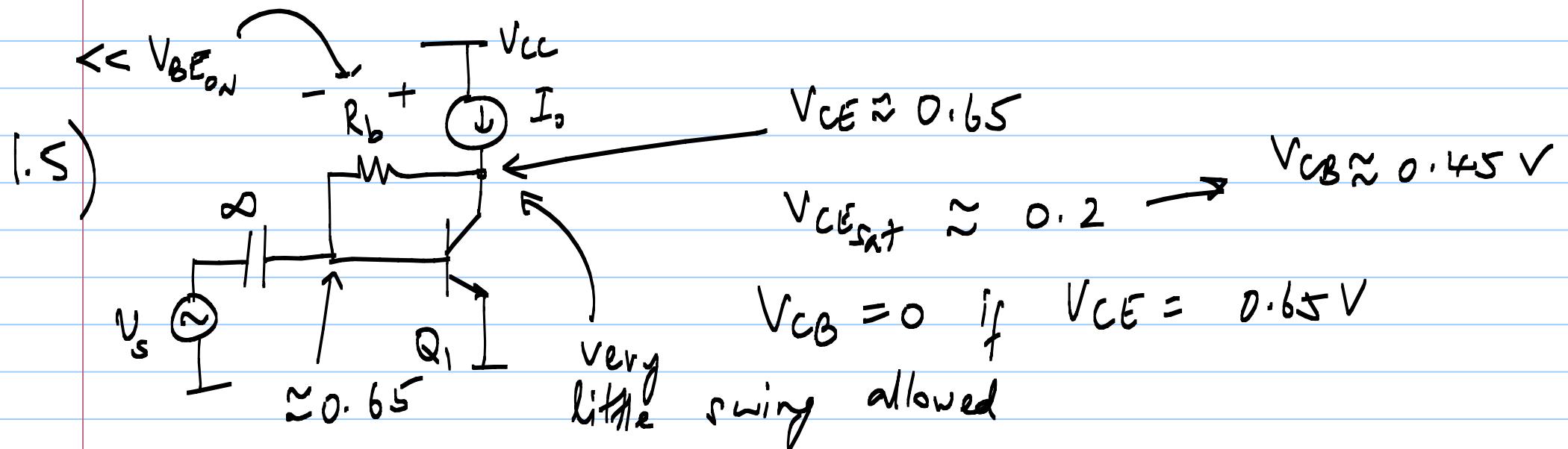


2)

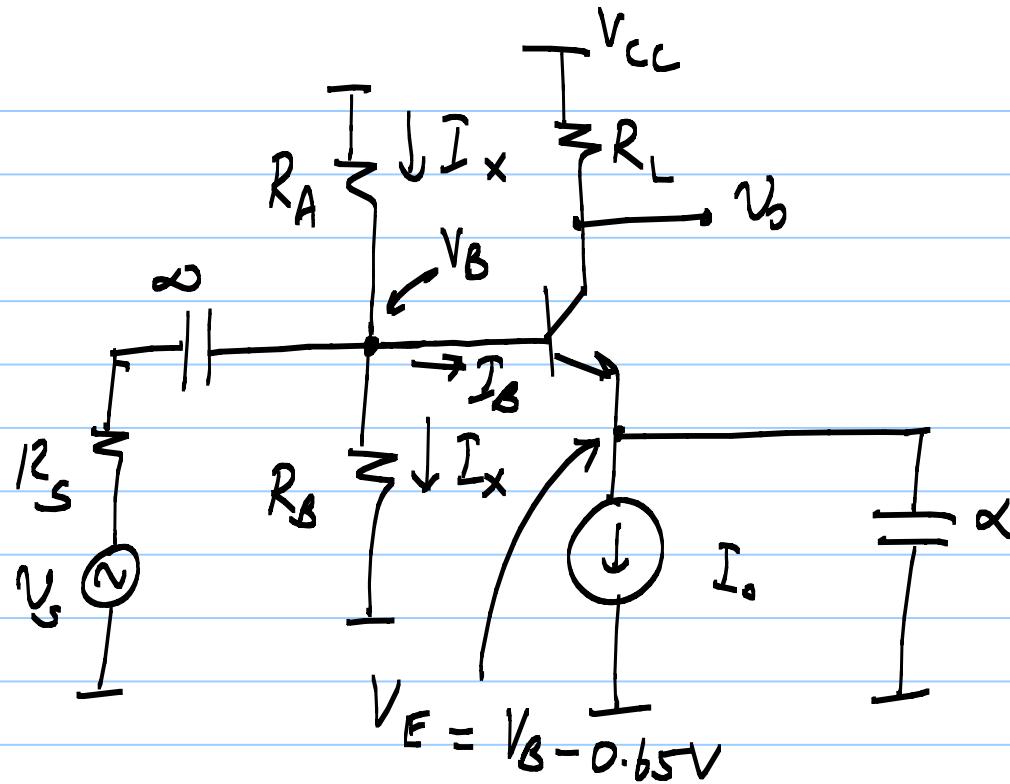

$$I_x > I_B$$

"Common Emitter
Amplifier"


2.5)

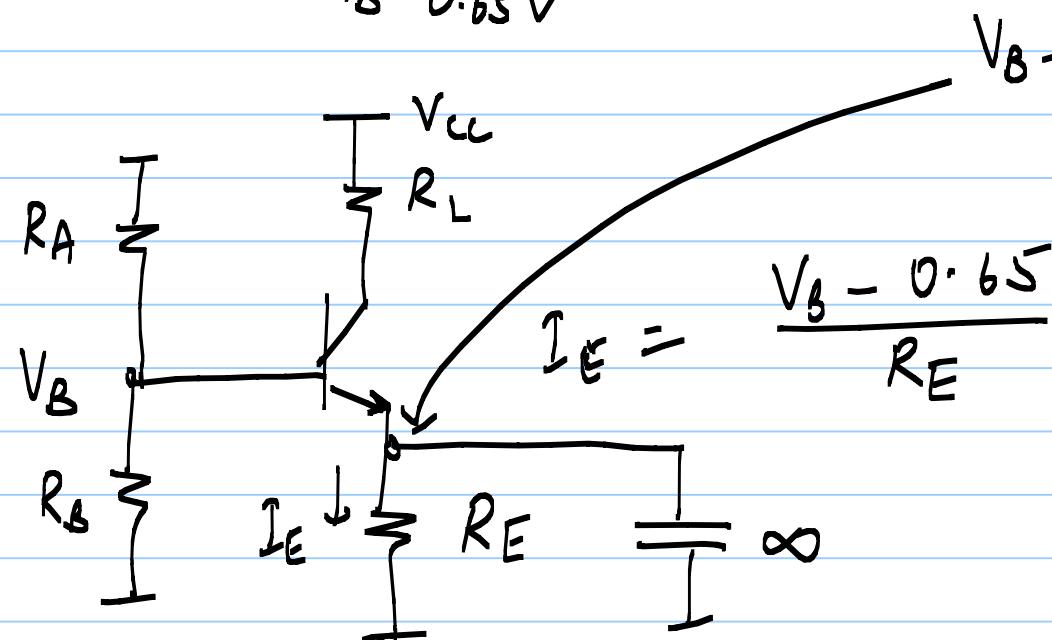

$$V_B - 0.65V$$

Circuits (3) & (4) - HW { require opamps}

4)

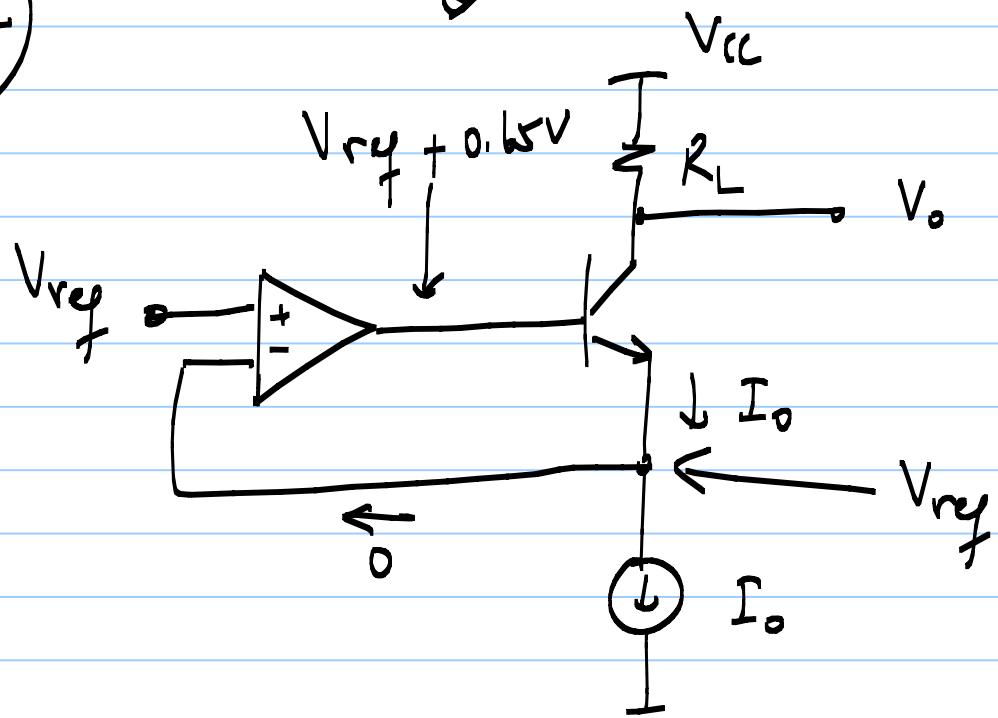

Swing Limits

i) Saturation limit


$$V_{CE_{sat}} = 0.2 \text{ V}$$

e.g. for circuit (2):

$$V_C - V_E = 0.2 \text{ V}$$

$$V_{CC} - I_o R_L + A \underbrace{V_A \sin \omega t}_{-g_m R_L} - (V_B - 0.65 \text{ V}) = 0.2 \text{ V}$$

A = gain of CE amplifier

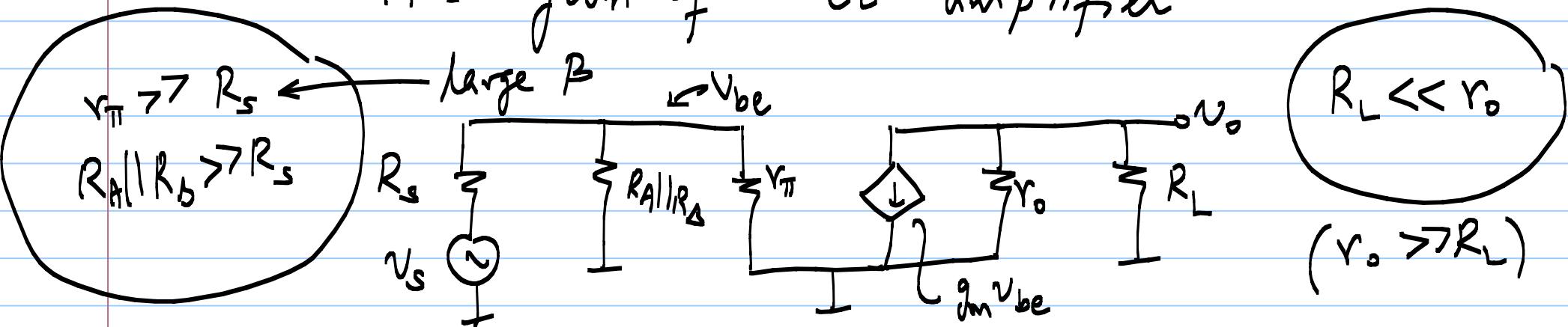

$$V_{be} \approx V_s$$


$$V_o = -g_m R_L V_s$$

$$A = \frac{V_o}{V_s} = -g_m R_L$$

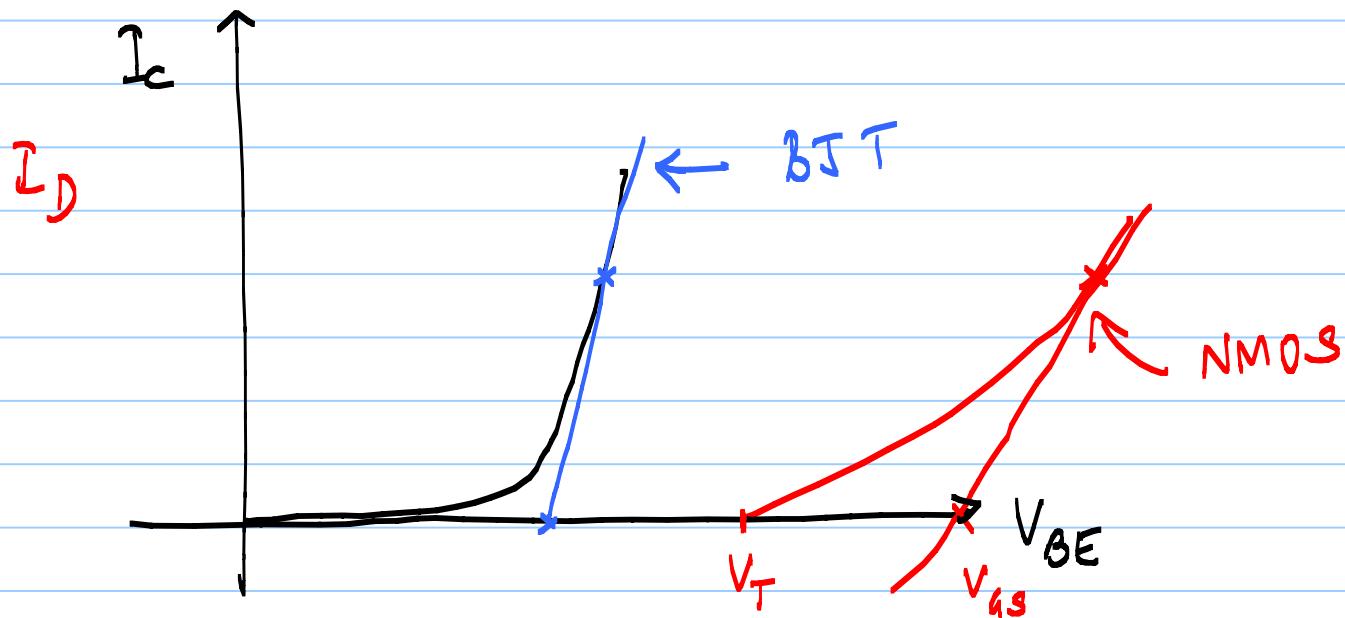2) Cut off limit

$$I_c = 0$$

$$I_o + g_m V_A \sin \omega t = 0 \Rightarrow V_A = \frac{I_o}{g_m}$$




4/11/20


Lecture 49

Band gap Reference

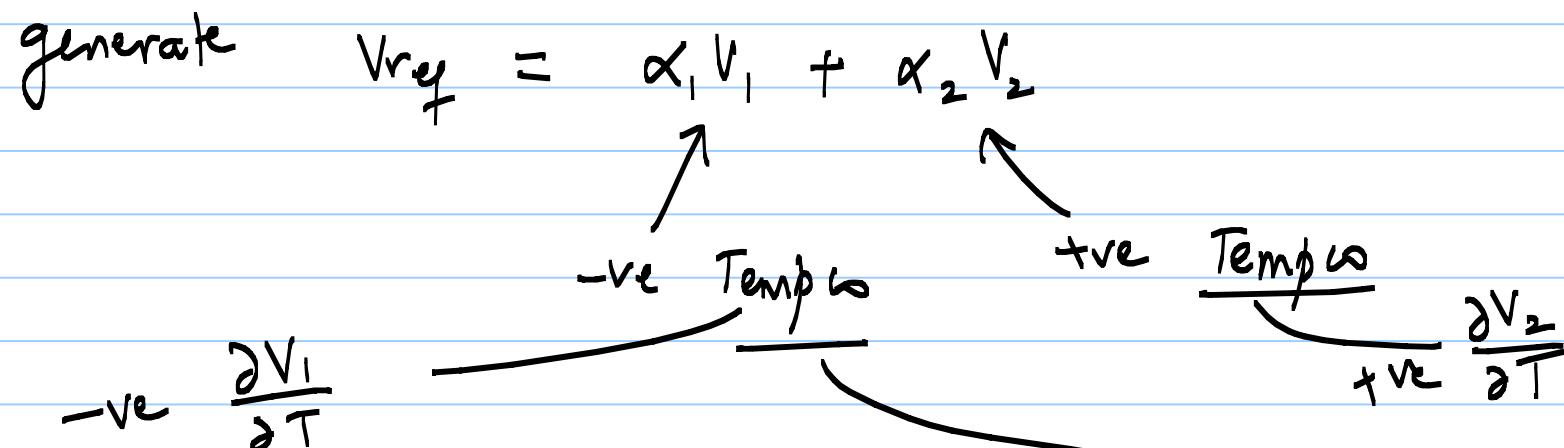- * Create V_{ref} that is independent of temperature
- * $C, R, M, V_T, V_b \rightarrow$ all vary with temp.
- * At least at one temp. $T_0 \rightarrow$ make $\frac{dV_{ref}}{dT} = 0$



@ R_T : set $\left. \frac{\partial V_{ref}}{\partial T} \right|_{R_T} = 0$ temperature coefficient

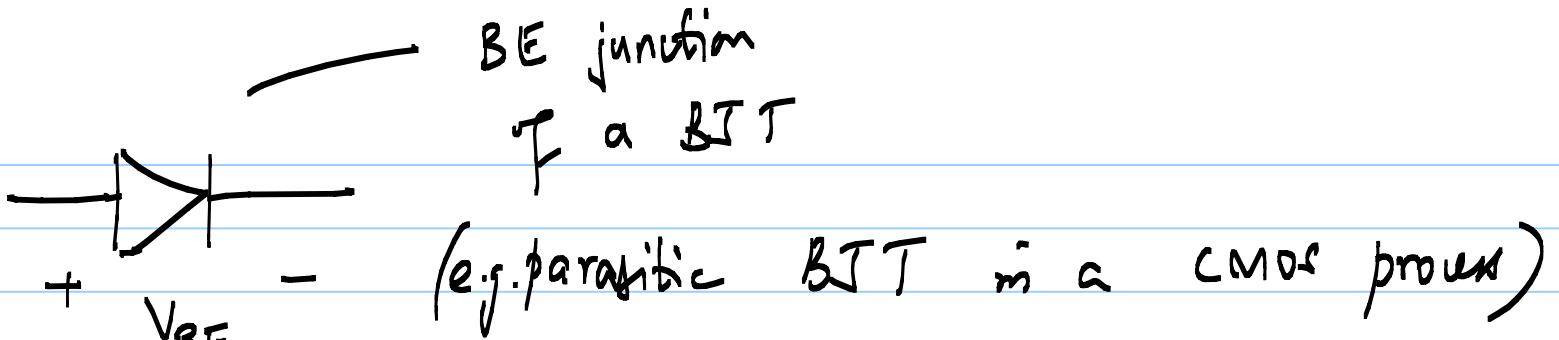


CTAT
Complementary
to
absolute
temp.


$$\approx 0.65V$$

$$\left| \frac{\partial V_{BE}}{\partial T} \right|_{RT} \approx -1.5 \text{ to } -2 \text{ mV/K}$$

use to
create V_1
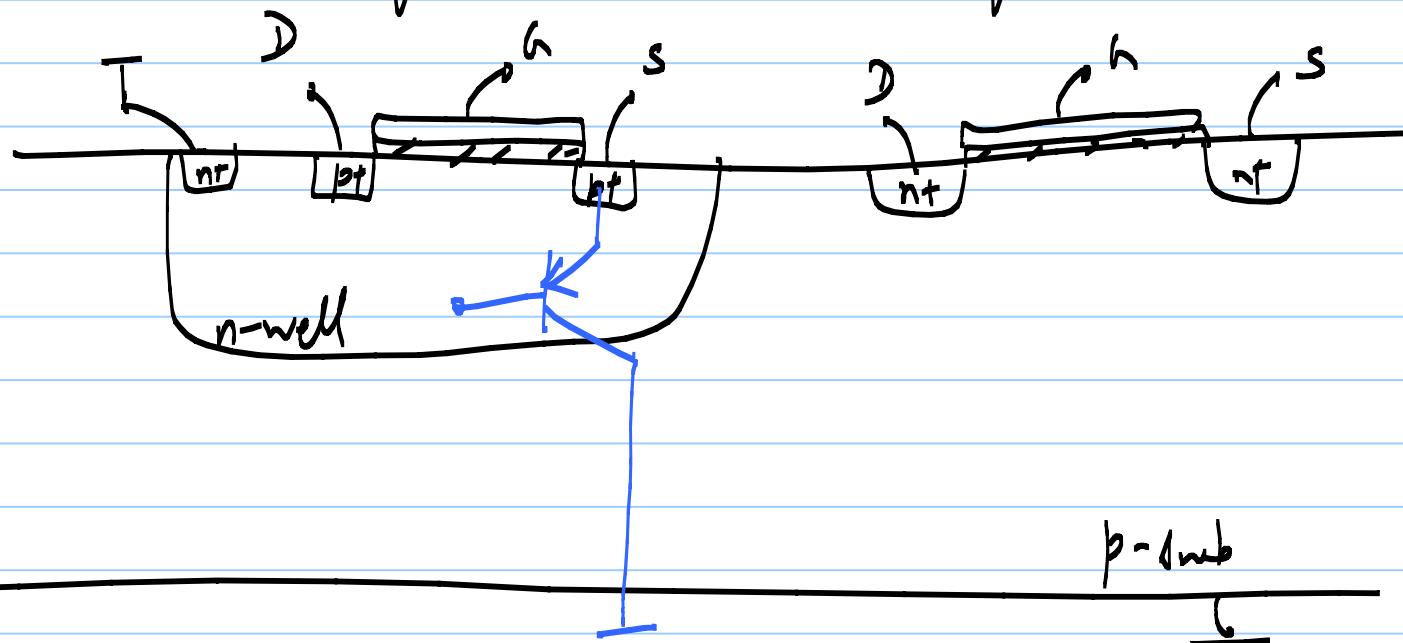
$$V_t = \frac{kT}{q} \rightarrow \frac{\partial V_t}{\partial T} = \frac{k}{q} \rightarrow \text{use to create } V_2$$



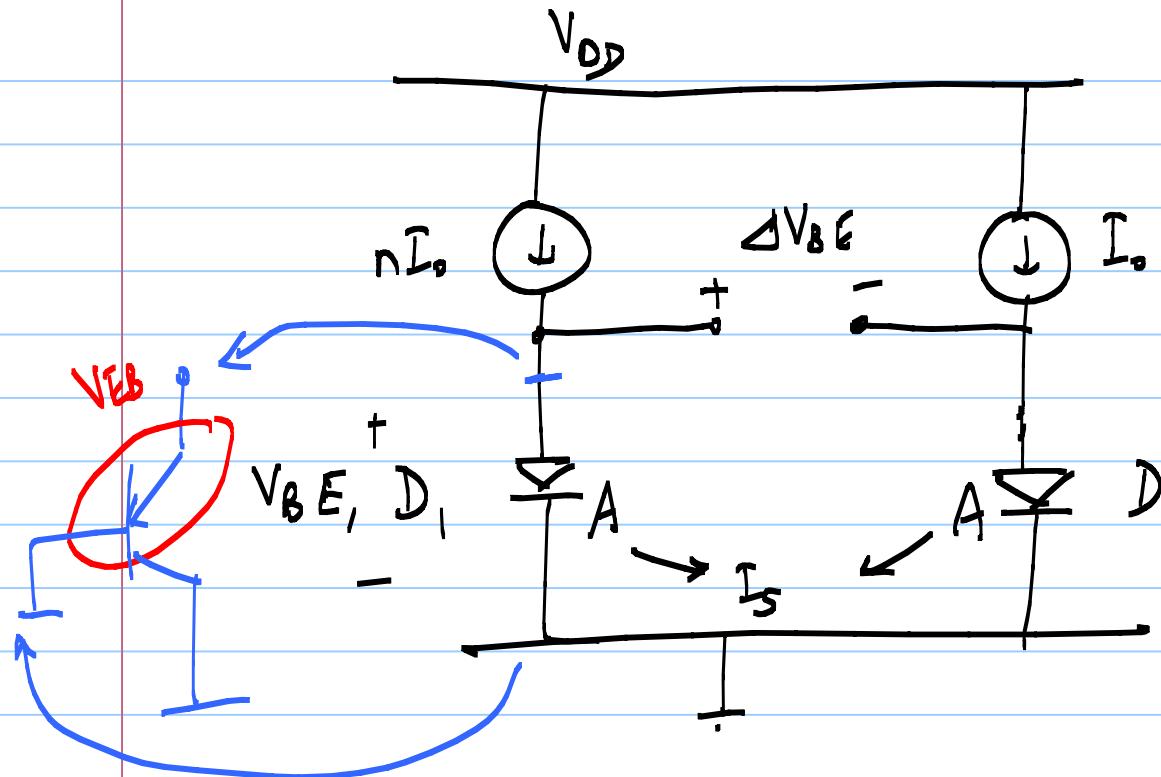

$$\Delta V_{BE} = V_{BE_1} - V_{BE_2}$$

$$= V_t \ln\left(\frac{I_c}{I_s}\right) - V_t \ln\left(\frac{I_{c_1}}{I_s}\right)$$

$$= V_t \ln\left(\frac{nI_s}{I_s}\right) - V_t \ln\left(\frac{I_s}{I_s}\right)$$

$$\Delta V_{BE} = V_t \ln(n)$$

$$= \frac{kT}{q} \ln(n)$$

$\propto T$

V_T with +ve T.C.


ΔV_{BE} is called a "PTAT" voltage

↳ proportional to absolute temperature


* exact value of I_s does
not matter

$$\Delta V_{BE} =$$
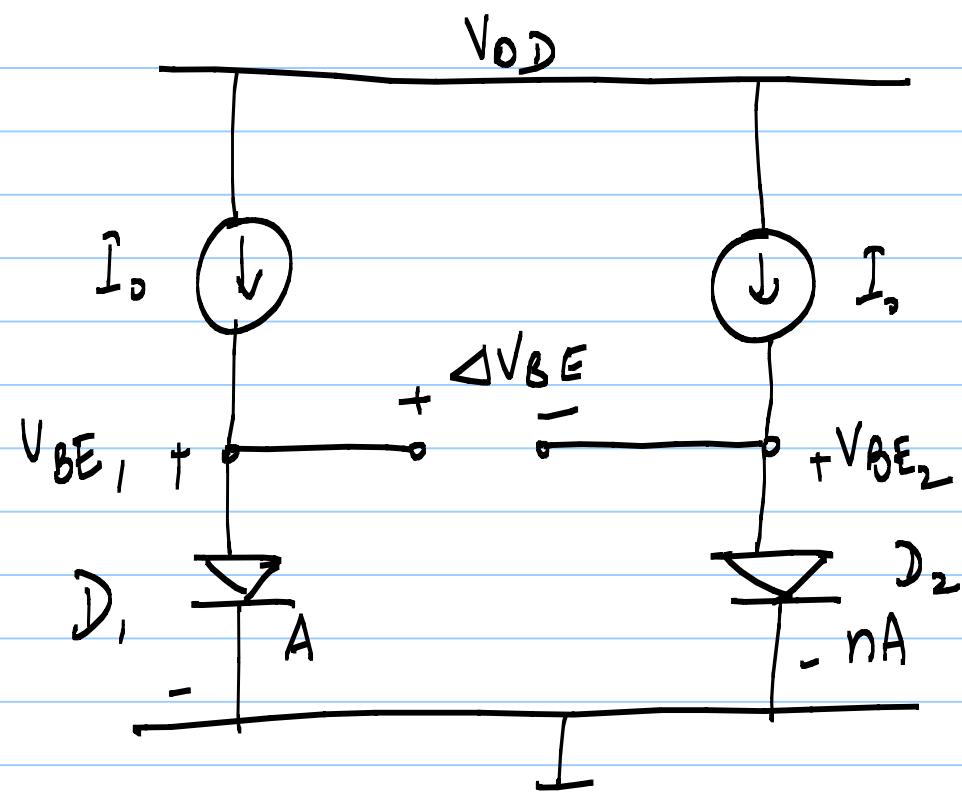
$$V_t \ln \left(\frac{I_o}{I_s/n} \right) - V_t \ln \left(\frac{I_o}{I_s} \right)$$



$$\Delta V_{BE} = V_t \ln(n)$$

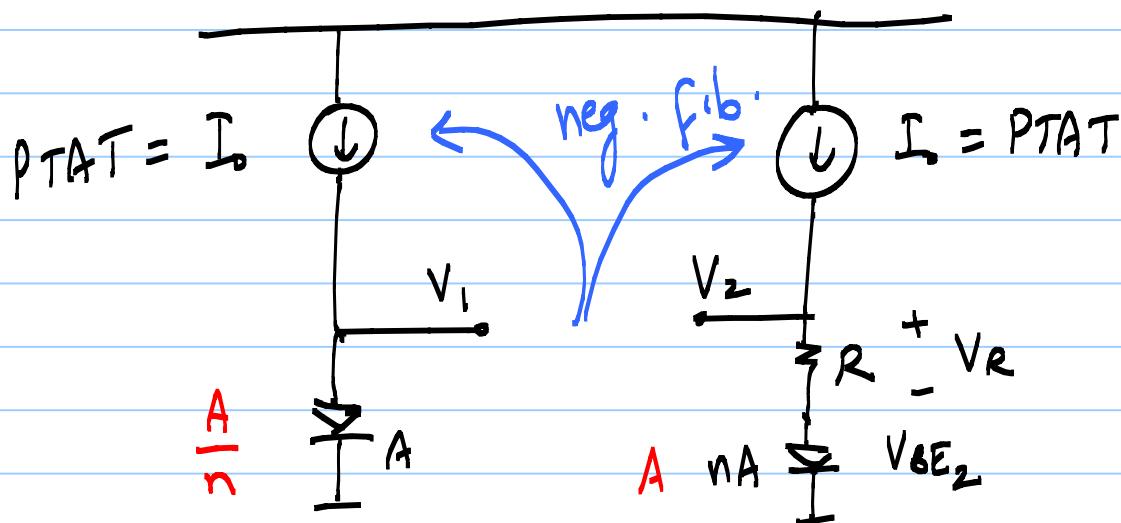

$$\text{force } V_1 = V_2$$

$$\Rightarrow V_R = \Delta V_{BE_1} = V_t \ln(n)$$

Use an opamp

in negative f.b.

$$V_{ref} : V_z = V_{BE_2} + V_R = V_{BE_2} + \Delta V_{BE} \leftarrow \text{set eqn to } V_{ref}$$

Set temp. coeff. @ RT if V_z to be zero

$$\frac{\partial V_{ref}}{\partial T} \Big|_{300K} = 0$$


$$\frac{\partial}{\partial T} \left(V_{BE_2} + \frac{kT}{q} \ln(n) \right) \Big|_{RT} = 0$$

$$\frac{\partial V_{BE_2}}{\partial T} \Big|_{RT} + \frac{k}{q} \ln(n) = 0$$

$$-1.5mV/k \quad \rightarrow +1.5mV/k$$

$$\ln(n) = 1.5 \times \frac{q}{k} \approx 17.4$$



$$V_{ref} \approx 1.2V$$


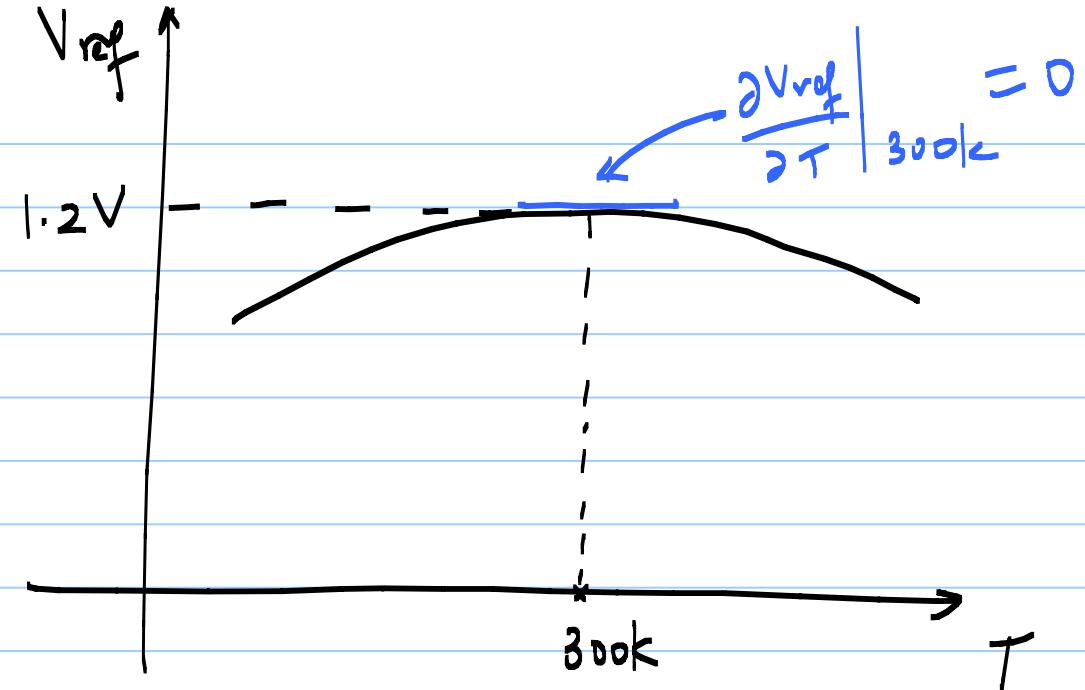


5/11/20

Lecture 50

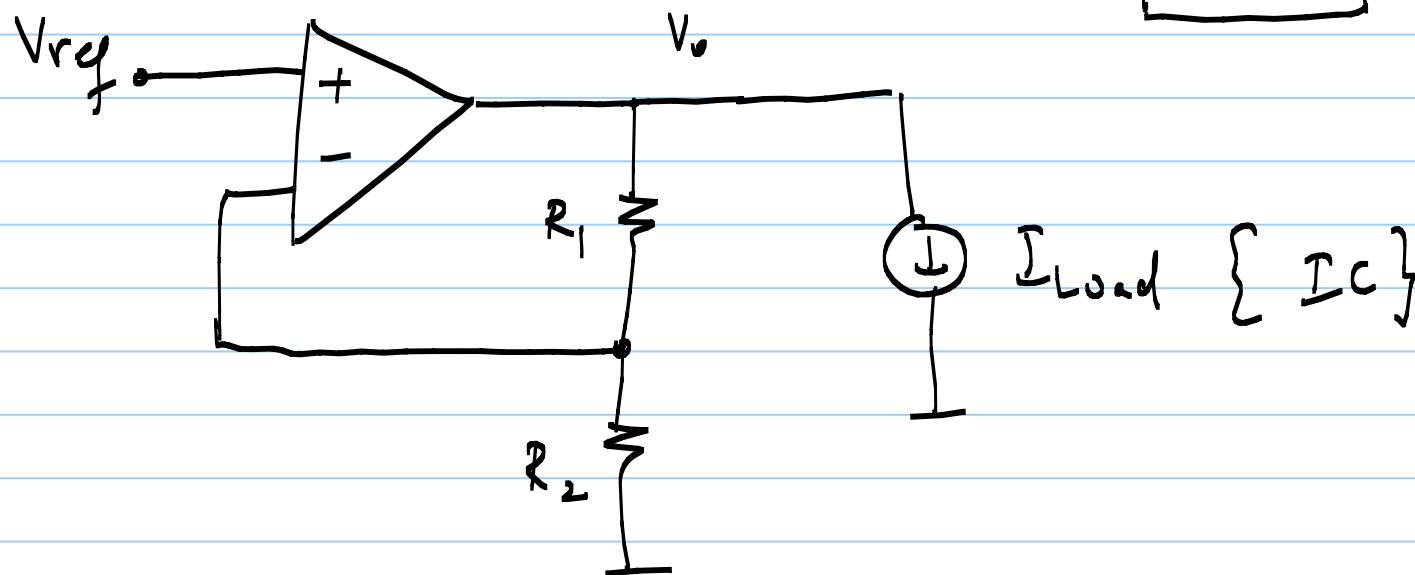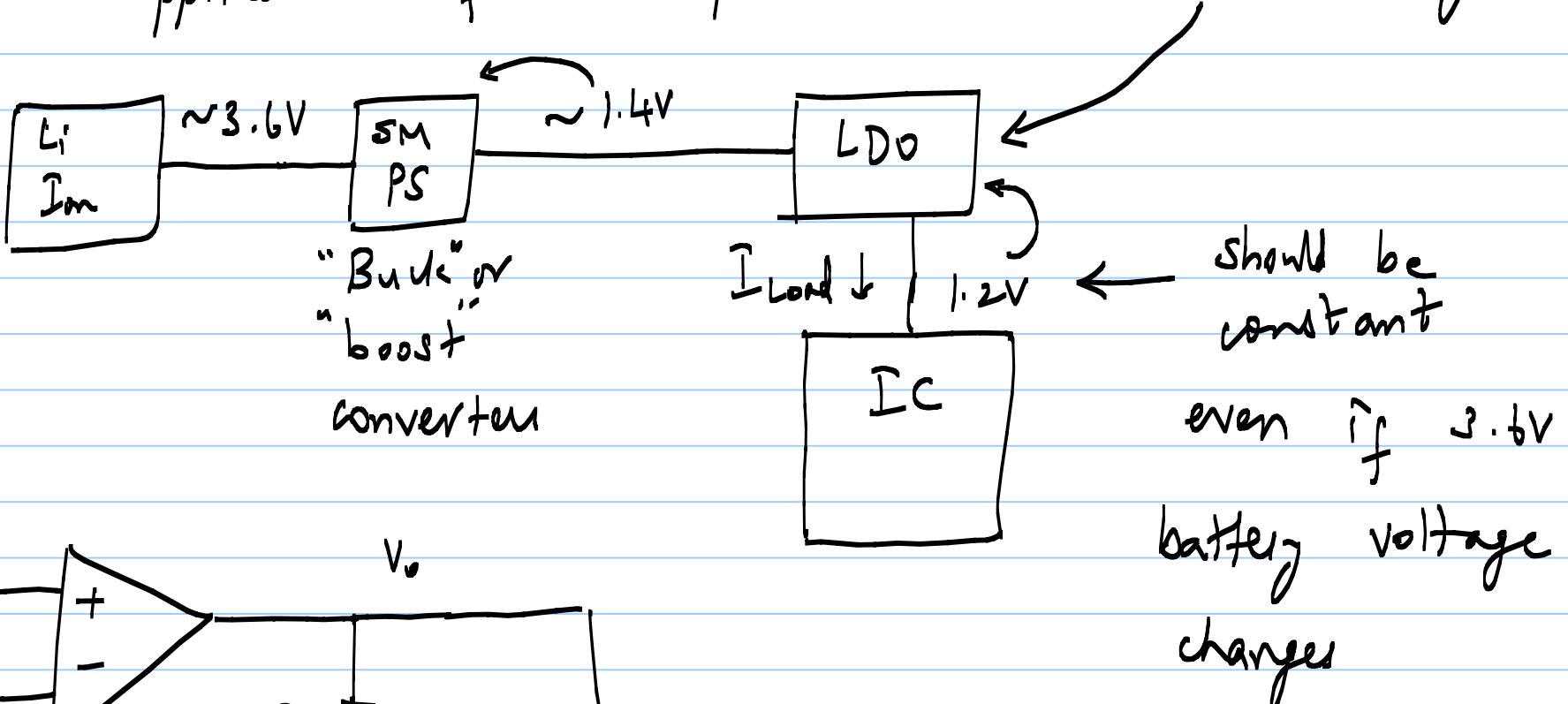One application of Bh reference - low Dropout regulator



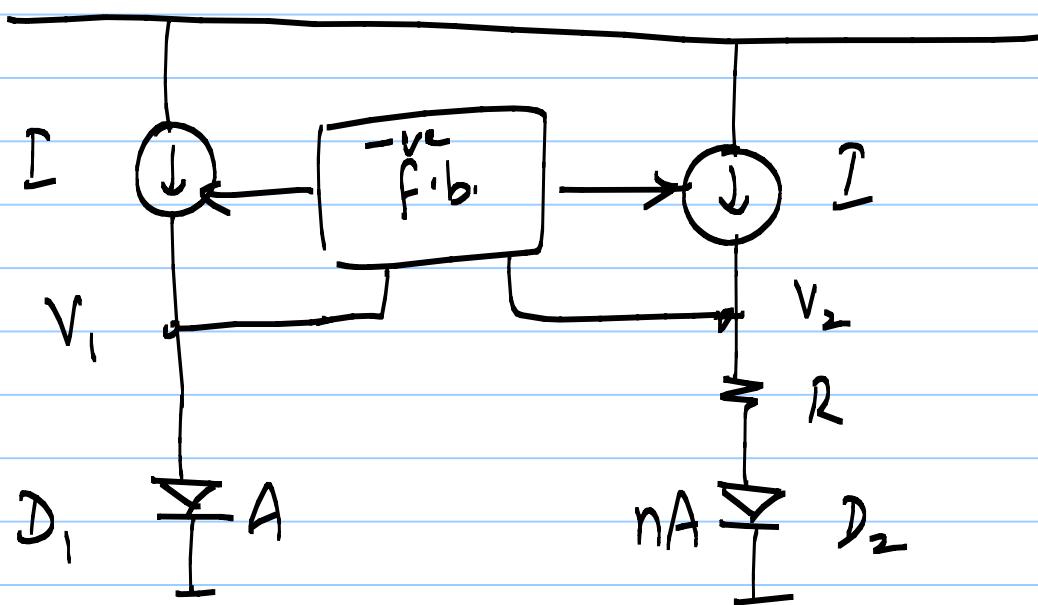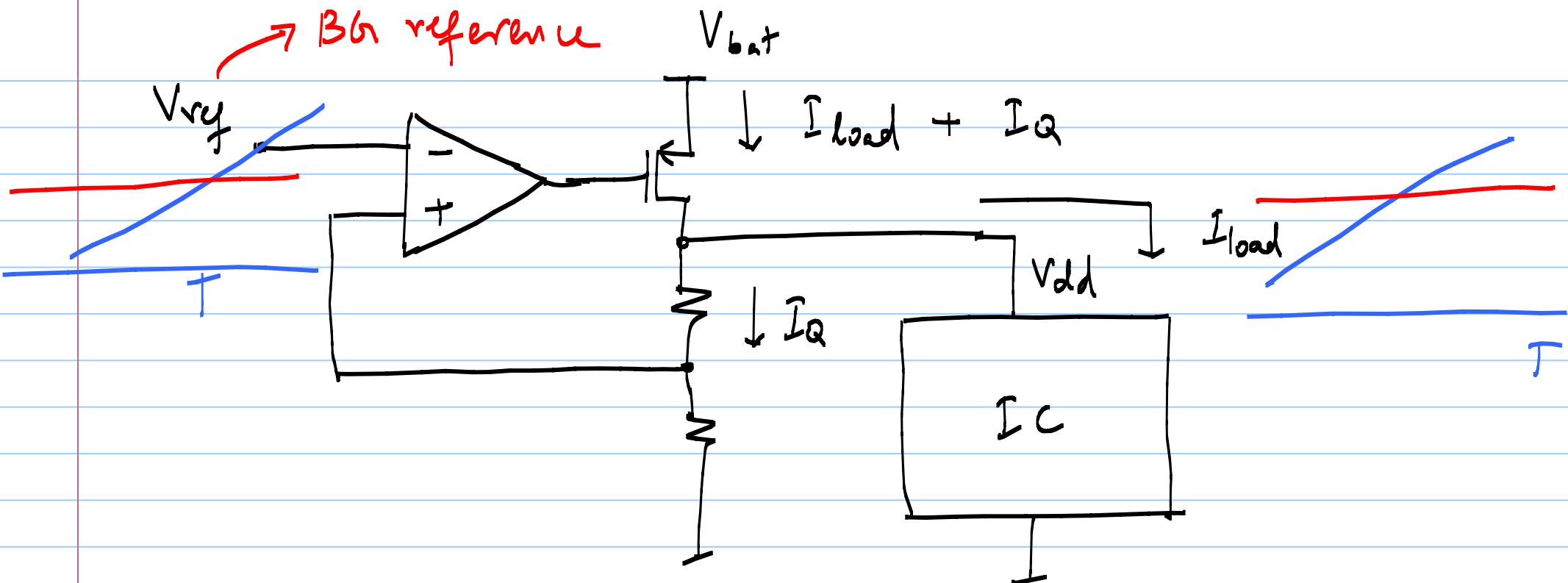

$$V_1 = V_2 = V_{ref} \sim 1.2V$$

$$\hookrightarrow V_1 = V_{BE1} \sim 0.65V$$


normally

$$V_{BE1} \sim 0.65V$$

$$V_{BE_1} = V_T \ln \left(\frac{I_{C_1}}{I_{S_1}} \right) \approx \frac{0.65V}{0.026V} \approx 20. \times x$$

I_{C_1} large
 I_{S_1} small



$-V_{BE}$
 $\sim 1.2V$

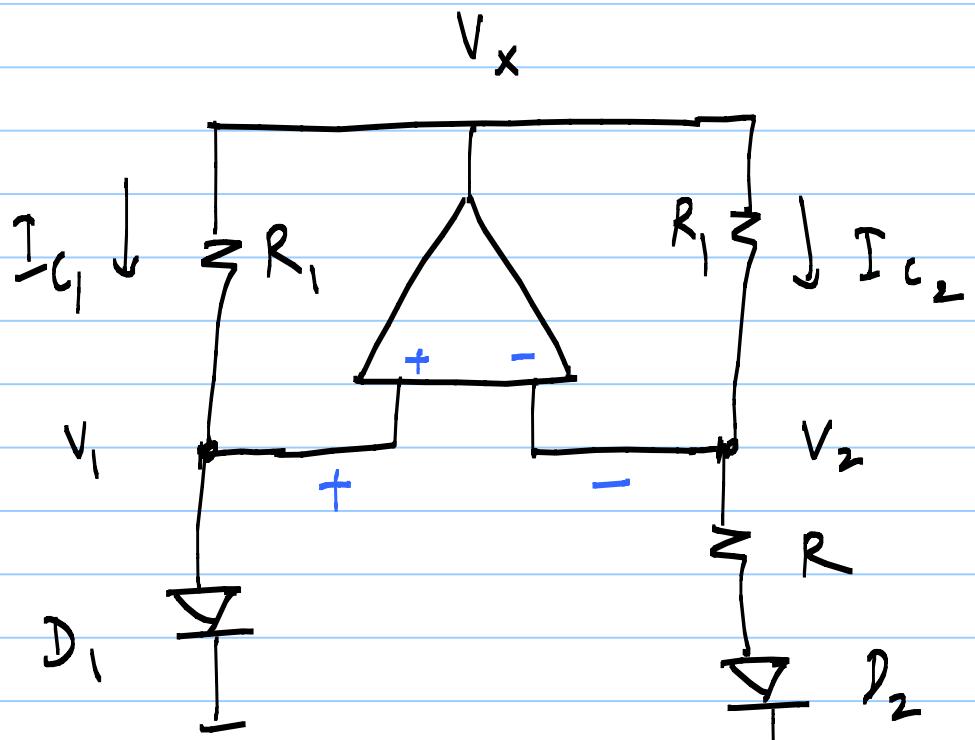



$$I_{C_1} = \frac{V_x - V_1}{R_1}$$

$$I_{C_2} = \frac{V_x - V_2}{R_1} = I_{C_1}$$

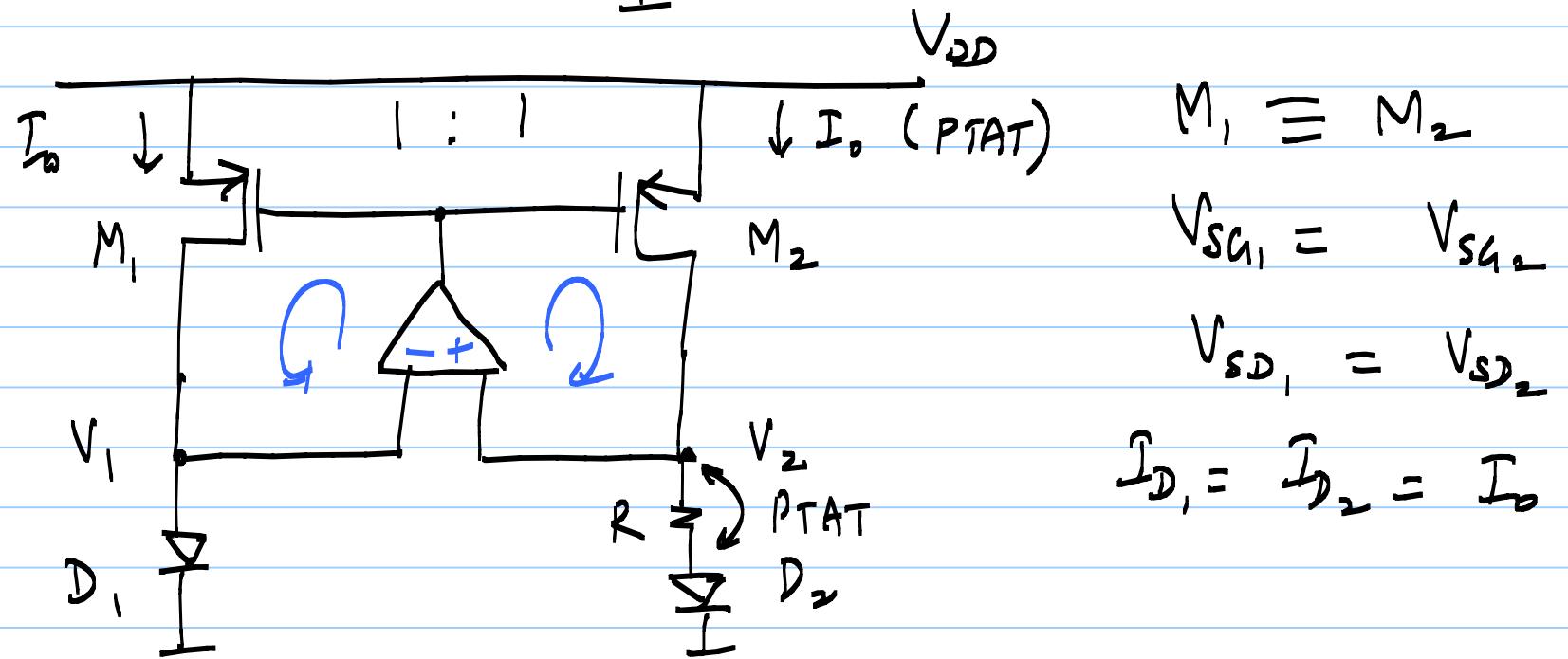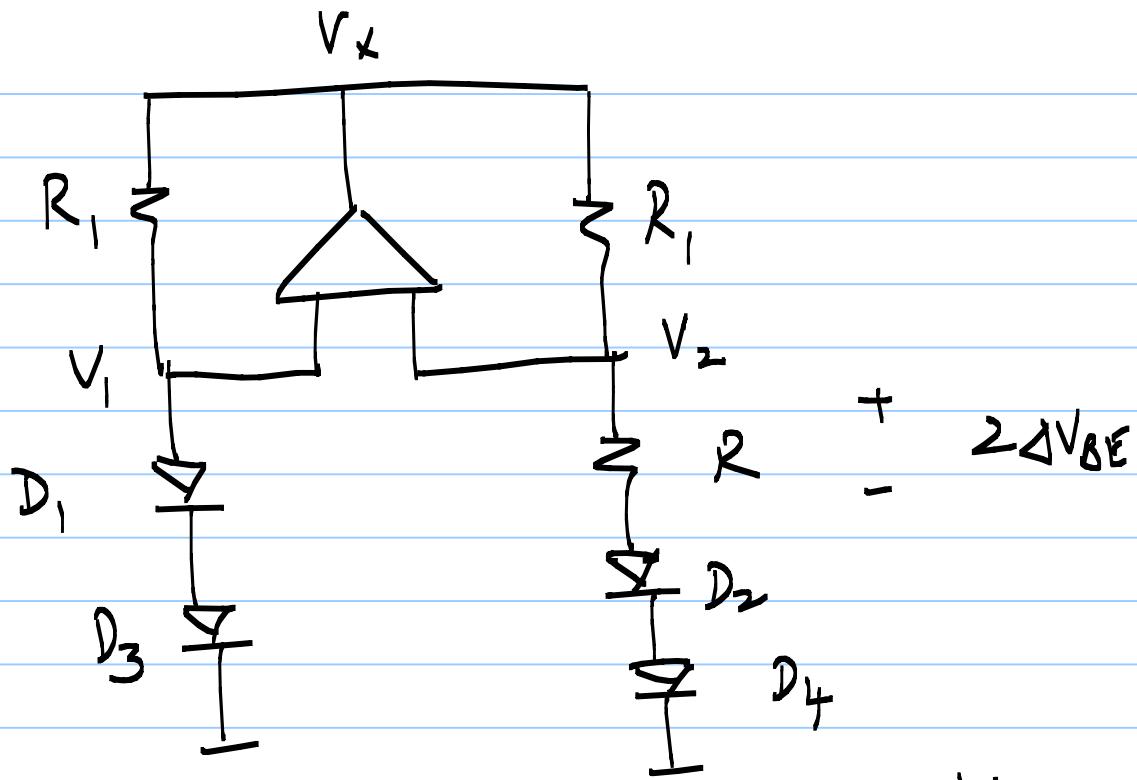* choose signs of opamp so that strength of -ve f.b. > strength of +ve f.b.



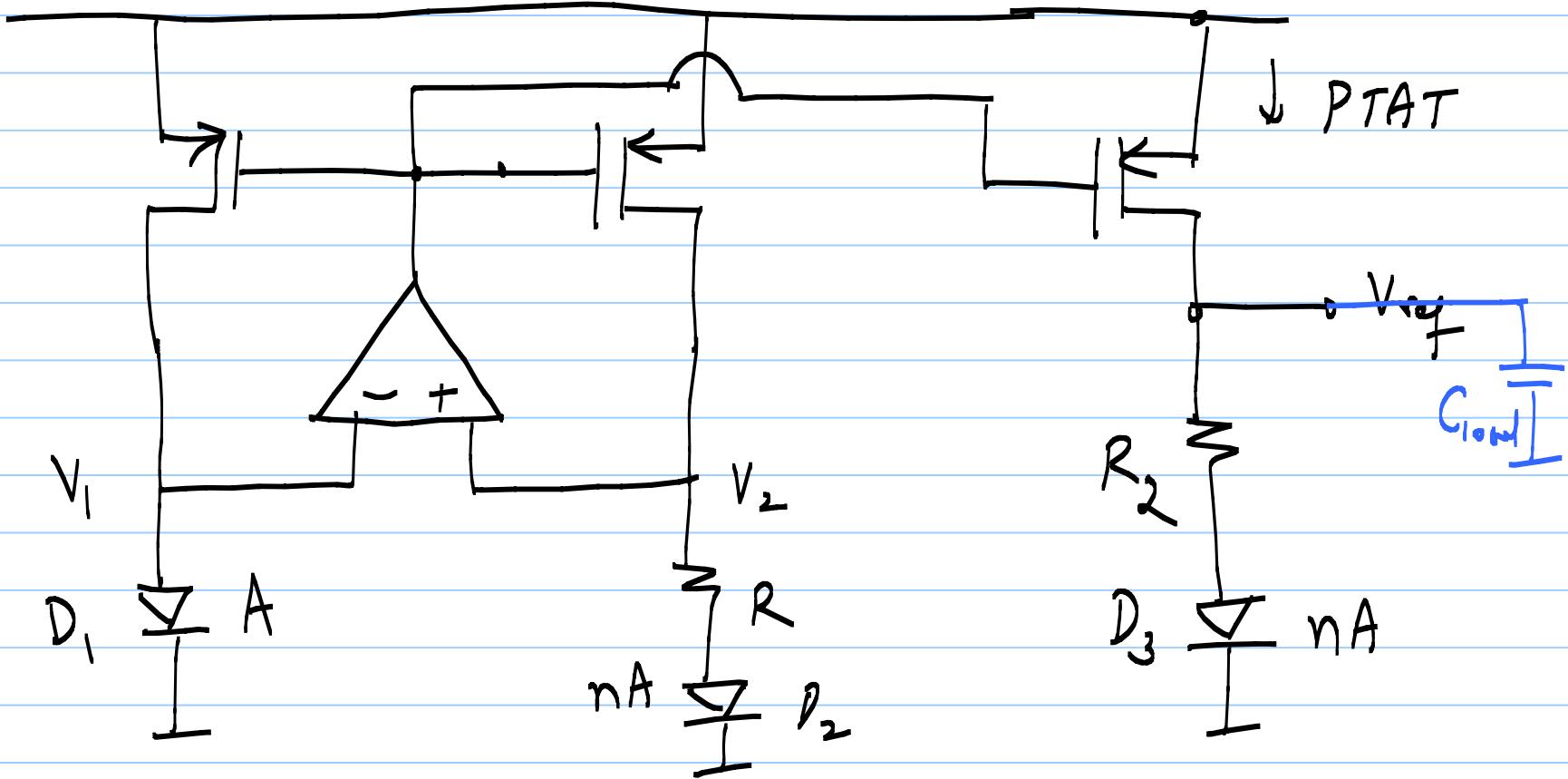

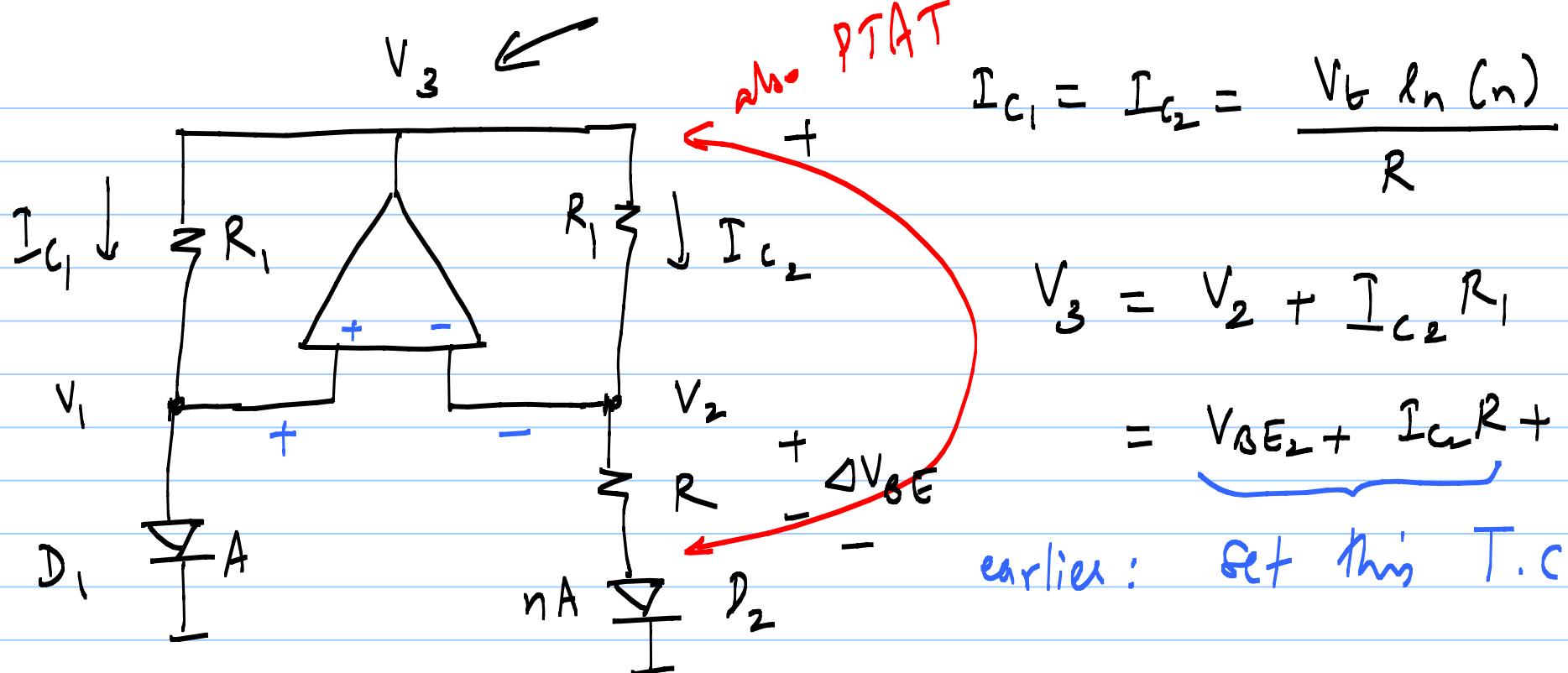

$$I_{C_1} = I_{C_2} = \frac{V_b \ln(n)}{R}$$

$$\begin{aligned} V_3 &= V_2 + I_{C_2} R_1 \\ &= V_{BE_2} + \underbrace{I_{C_2} R + I_{RL} R}_{\Delta V_{BE}} \end{aligned}$$

earlier: Set this T.C. = 0

Now : Set T.C. of $V_3 = 0$ i.e. $\left. \frac{\partial V_3}{\partial T} \right|_{300K} = 0$

$$V_3 = V_{BE_2} + I_{C_2} (R + R_1)$$

$$= V_{BE_2} + \frac{V_b \ln(n)}{R} (R + R_1)$$

$$V_3 = V_{BE2} + \left[V_T \ln(n) \right] \left[1 + \frac{R_1}{R} \right]$$

$$\left. \frac{\partial V_3}{\partial T} \right|_{300K} = 0 \Rightarrow \left[1 + \frac{R_1}{R} \right] \ln(n) = 17.2$$

* choose $\frac{R_1}{R}$ so that n is small

* $V_3 = V_{ref}$ {Bh ref. voltage)

* V_{ref} depends on $\underbrace{(R_1/R)}$
well controlled
over "PVT"
variations