

Analog Circuits (EE3002/EE5310) : Problem Set 7

shanthi@ee.iitm.ac.in

For all transistors, use $\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 50 \mu\text{A}/\text{V}^2$, $V_{TN} = V_{TP} = 1 \text{ V}$. Use $\lambda = 0$ unless otherwise mentioned. The (W/L)s of the devices are marked next to them.

Problem 1

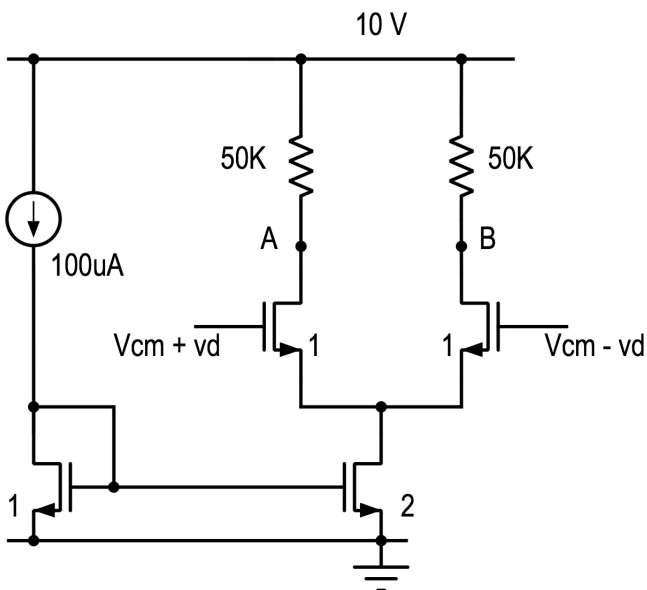


Figure 1: Circuit for problem 1.

In the amplifier of Fig. 1, $V_{cm} = 6 \text{ V}$, and v_d is a small signal.

- Determine the operating points of all the devices in the circuit.
- Determine the incremental voltages at A and B.
- What is the range over which V_{cm} can vary, while keeping all devices in saturation?
- It is desired to increase the incremental gain by increasing the resistors, and by using the lowest V_{cm} possible. Determine the maximum achievable incremental gain at node B.

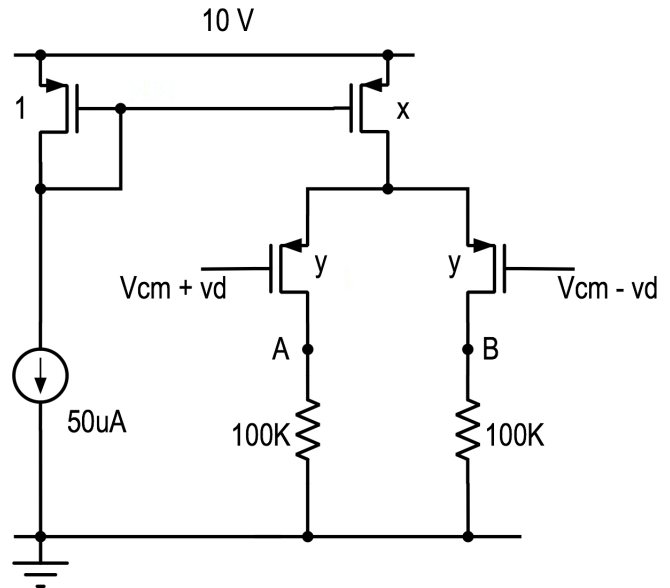


Figure 2: Circuit for problem 2.

Problem 2

In the circuit of Fig. 2, $V_{cm} = 6 \text{ V}$ and v_d is a small signal. Determine the aspect ratios x and y so that

- the quiescent voltages at A and B are the same as in the previous problem, and
- the incremental gain is the same as that in the previous problem.
- With the calculated x and y , find the input common-mode range.

Problem 3

In the circuit of Fig. 3, $V_{cm} = 6 \text{ V}$ and v_d is a small signal. Determine the aspect ratio x , so that the incremental voltage between A and B is $4 v_d$. For this value of x , determine the quiescent voltage at A.

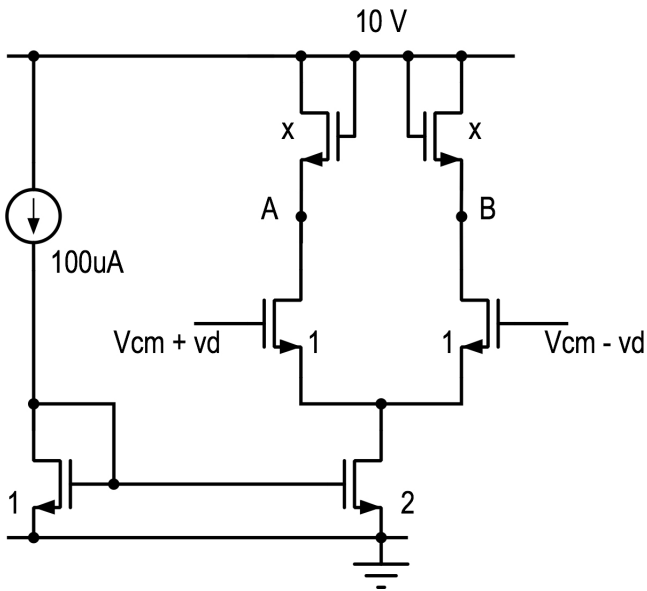


Figure 3: Circuit for problem 3.

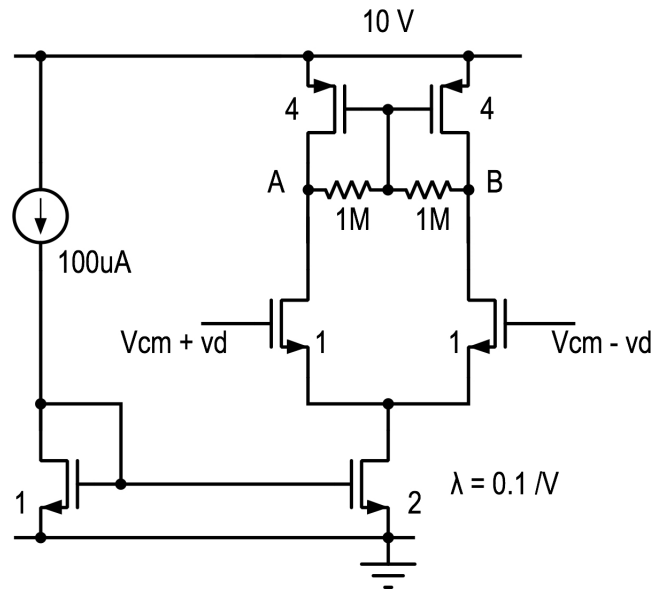


Figure 5: Circuit for problem 5.

Problem 4

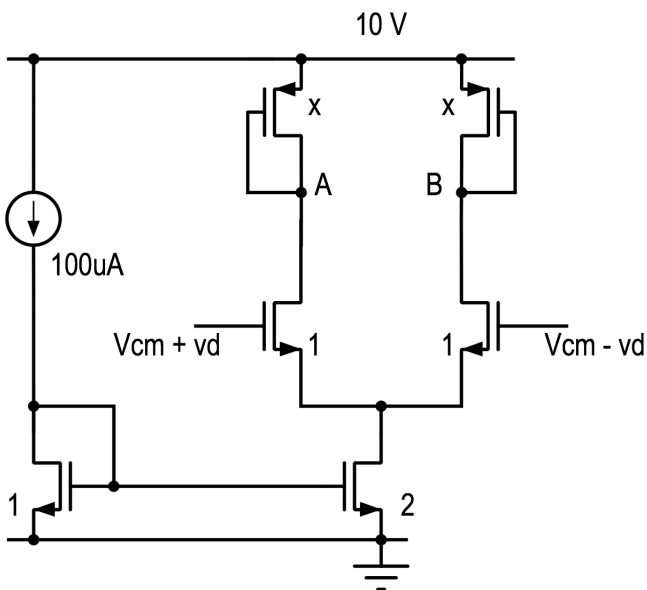


Figure 4: Circuit for problem 4.

Repeat problem 3 for the circuit of Fig. 4.

Problem 5

For this problem, use $V_{cm} = 5\text{ V}$. Though not shown, the common-mode portion of the input has a small signal component denoted by v_{cm} . Determine the quiescent voltages at A and B. Determine the incremental voltage at node B, and the common-mode rejection

ratio. What is the common-mode range?

Problem 6

For this problem, use $V_{cm} = 5\text{ V}$. Determine x so that the quiescent voltage at A and B is 5 V. Next, for the value of x you just determined, find the range of V_M over which all devices remain in saturation.

For $V_M = 3\text{ V}$, determine the range of V_{cm} that will keep all devices in saturation.

Finally, determine the incremental gain, which we define in this case to be $v_{AB}/2v_d$.

Problem 7

For this problem, use $V_{cm} = 5\text{ V}$. Determine the incremental gain from the input to the output at node A. Over what range of V_{cm} is this gain maintained?

Problem 8

For this problem and the next, use $V_{cm} = 5\text{ V}$, $\lambda_p = 0$ and $\lambda_n = 0.1/V$.

Determine the quiescent operating point at the output node. What is the incremental voltage at the output?

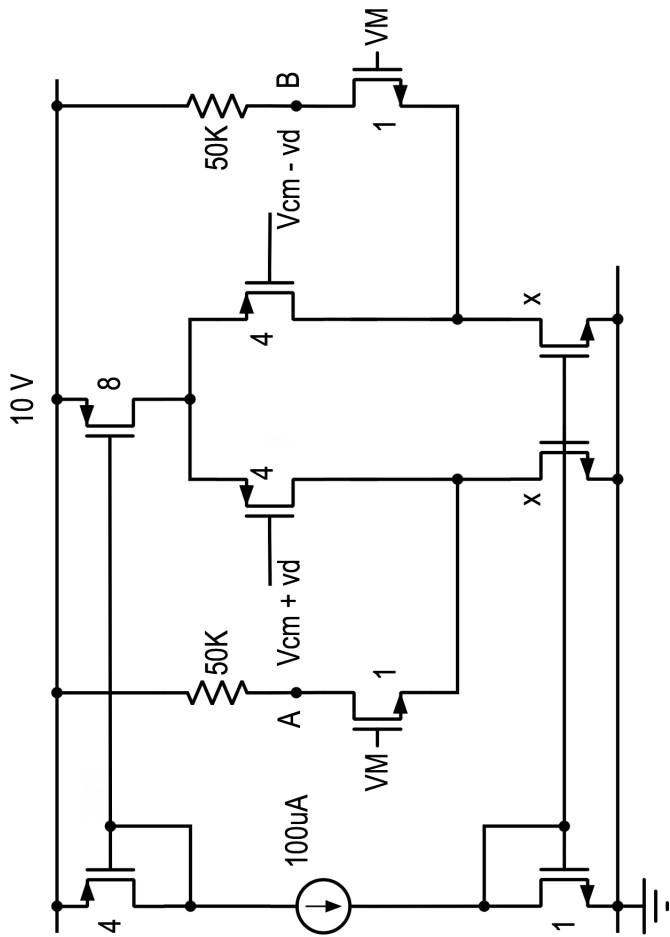


Figure 6: Circuit for problem 6.

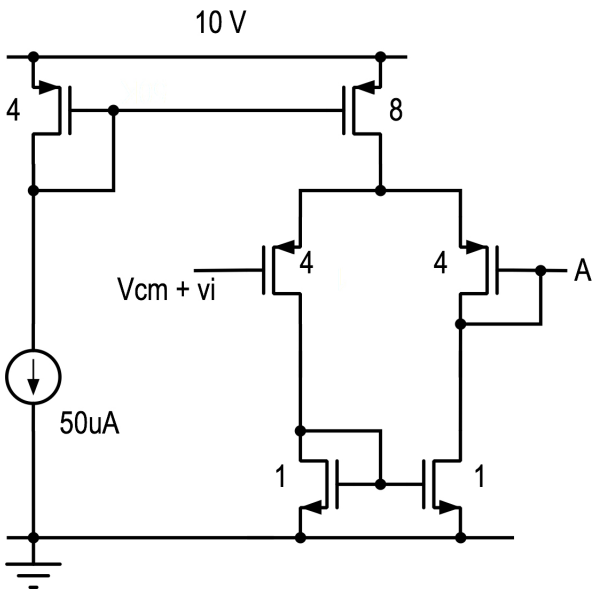


Figure 7: Circuit for problem 7.

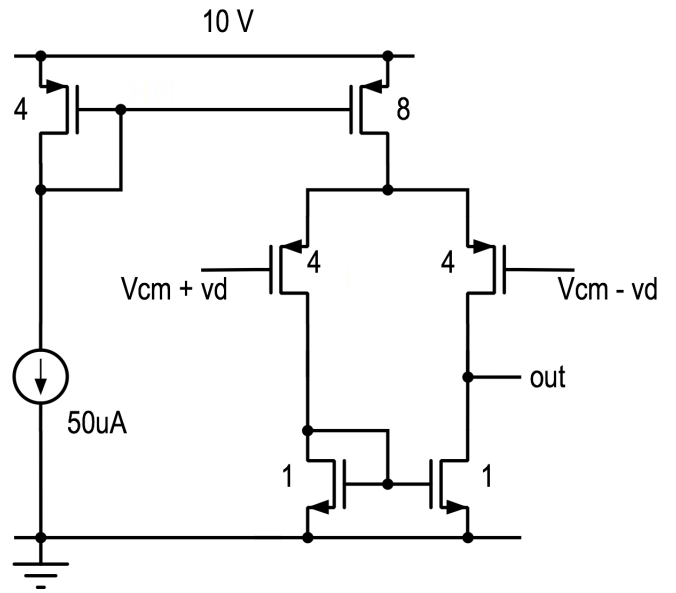


Figure 8: Circuit for problem 8.

Problem 9

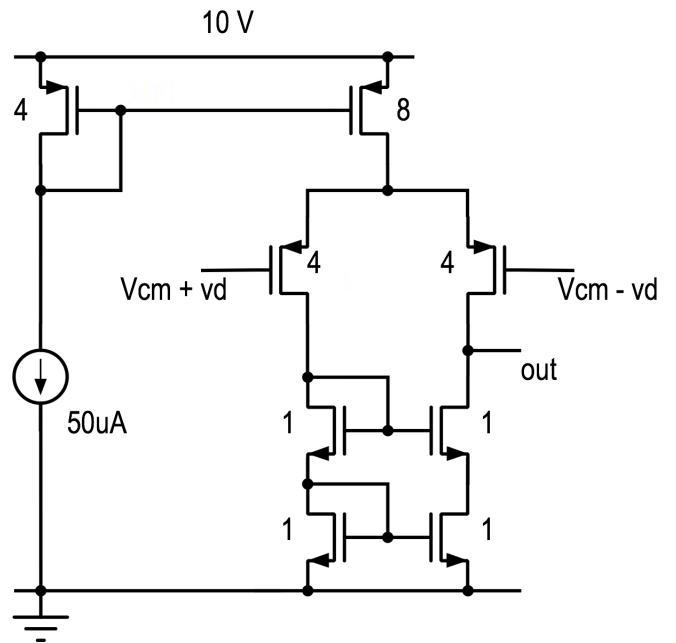


Figure 9: Circuit for problem 9.

Repeat problem 8 for the circuit of Fig. 9.