

# Analog Integrated Circuit Design

Nagendra Krishnapura (nagendra@ee.iitm.ac.in)

## Assignment 5

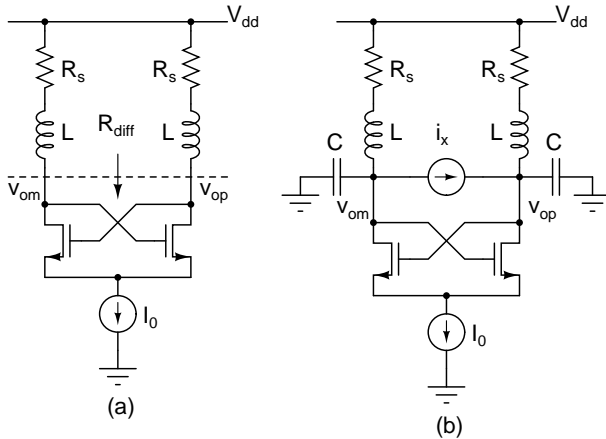


Figure 1: Problem 1

1. Calculate the current flowing in each transistor in Fig. 1(a) in the quiescent condition. Calculate the small signal differential resistance  $R_{out}$  looking into the drains of the two transistors.

In Fig. 1(b), calculate  $(v_{op} - v_{om})/i_x$ . What is the condition for this to be infinity? What is the frequency at which this happens?

 


Figure 2: Problem 2

2. Calculate the input impedance  $Z_{in}$  in Fig. 2. Is there anything special about it? Model the transistor using only its  $g_m$ .

 


Figure 3: Problem 3

3. Calculate the input impedance  $Z_{in}(s)$  in Fig. 3. Do you see anything special? What is the input impedance with  $g_m = 0$ ?

Express  $Z_{in}(s)|_{g_m \neq 0}$  as a parallel combination of  $Z_{in}(s)|_{g_m=0}$  and another branch  $Z_1(s)$ . What does  $Z_1(s)$  consist of?

 


Figure 4: Problem 4

4. Calculate the input impedance  $Z_{in}(s)$  in Fig. 4. Do you see anything special? Derive an equivalent circuit with passive elements that has an impedance  $Z_{in}$ .
5. Calculate the small signal impedance  $v_x/i_x$ . What is the condition for this to be infinity? What is the frequency at which this happens? Model the transistor

 


Figure 5: Problem 5

using only its  $g_m$ .


 


Figure 6: Problem 6


- In Fig. 6, assume that all nodes are at the self bias voltage of the inverter. Model the small signal gain of each inverter as  $A_0/(1 + s/p_1)$  and calculate the condition for instability (i.e. when the loop gain becomes  $-1$ ). Hint: Among the roots of  $-1$ , pick the one which satisfies the above for the lowest value of  $A_0$ .
- What is the function of the circuits in Fig. 1(b), Fig. 5, and Fig. 6?
- Fig. 7(a) shows a phase-locked loop which multiplies a 10 MHz reference up to 1 GHz. The charge pump details are shown in Fig. 7(b).  $K_{VCO} = 100 \text{ MHz/V}$ ;  $I_{CP} = 100 \mu\text{A}$ ;  $R = 10 \text{ k}\Omega$ ;  $C_1 = 10 \text{ nF}$ ;  $C_2 = 0$ ;

Determine the loop bandwidth and the location of the loop-gain zero.

 Determine  $C_2$  such that the phase margin is degraded by no more than  $5^\circ$  compared to the original. Determine the extra attenuation (in  $\phi_{out}(s)/\phi_{ref}(s)$ ) at the reference frequency due to the addition of this value of  $C_2$ .



(a)

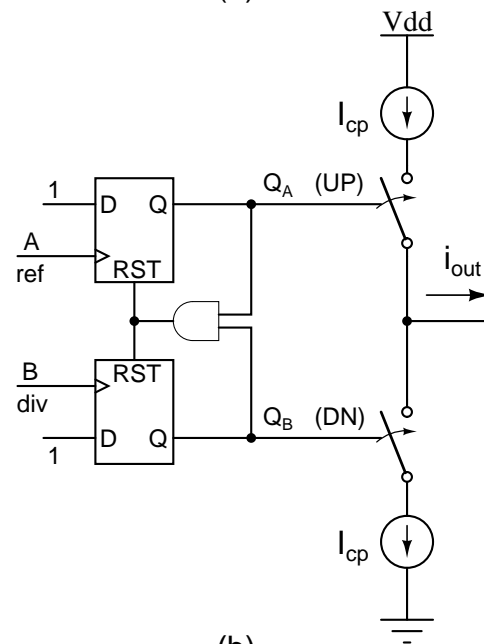

(b)

Figure 7: Problem 1