
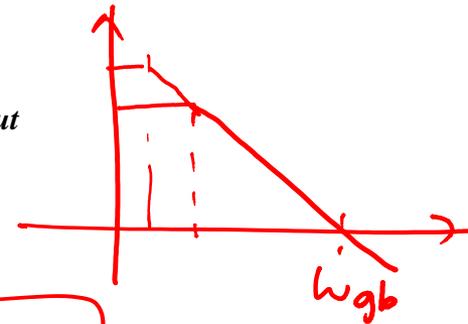
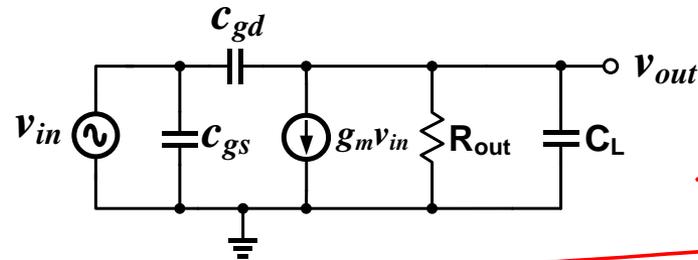


Gain-Bandwidth (GBW) Product

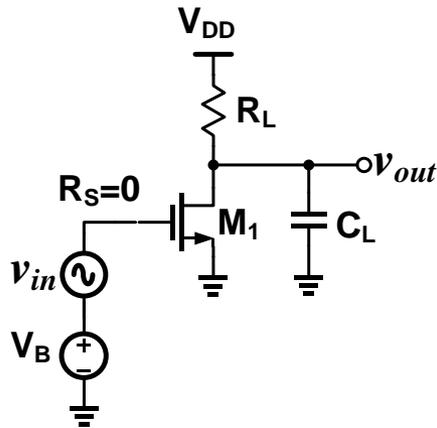

$$A_v(s) = -g_m R_{out} \frac{1 - sC_{gd}/g_m}{1 + s(C_{gd} + C_L)R_{out}}$$

DC gain $A_0 = g_m R_{out}$ ✓

Bandwidth (BW) $\omega_{-3dB} = \omega_p = \frac{1}{(C_{gd} + C_L)R_{out}}$ ✓

Gain \times Bandwidth (GBW product) $= \frac{g_m}{C_{gd} + C_L} = \omega_{ugb}$

Need: Large DC gain and large GBW product

Technology Limitation

$$\text{DC gain } A_0 = \underbrace{g_m(R_L \parallel r_{ds})}_{\checkmark \uparrow}$$

$$\text{Max DC gain } A_{0_{\max}} = \underbrace{g_m r_{ds}} = \frac{2}{\lambda V_{ov}}$$


$$\omega_{\text{ugb}} = \frac{\mu_n C_{\text{ox}} (W/L) V_{ov}}{C_{\text{gd}} + C_L} = \frac{g_m}{C_{\text{gd}} + C_L} \checkmark$$

$$\checkmark A_0 \cdot \checkmark \omega_{\text{ugb}} = \frac{2\mu_n C_{\text{ox}} (W/L)}{\lambda (C_{\text{gd}} + C_L)}$$

$$C_{\text{gd}} = \underbrace{k_c W} \quad C_L = \underbrace{0}$$


$$\underbrace{A_0 \cdot \omega_{\text{ugb}}}_{\checkmark} \Big|_{\max} = \frac{2\mu_n C_{\text{ox}}}{\lambda k_c L} = \underline{\text{constant}}$$

Graphical Illustration

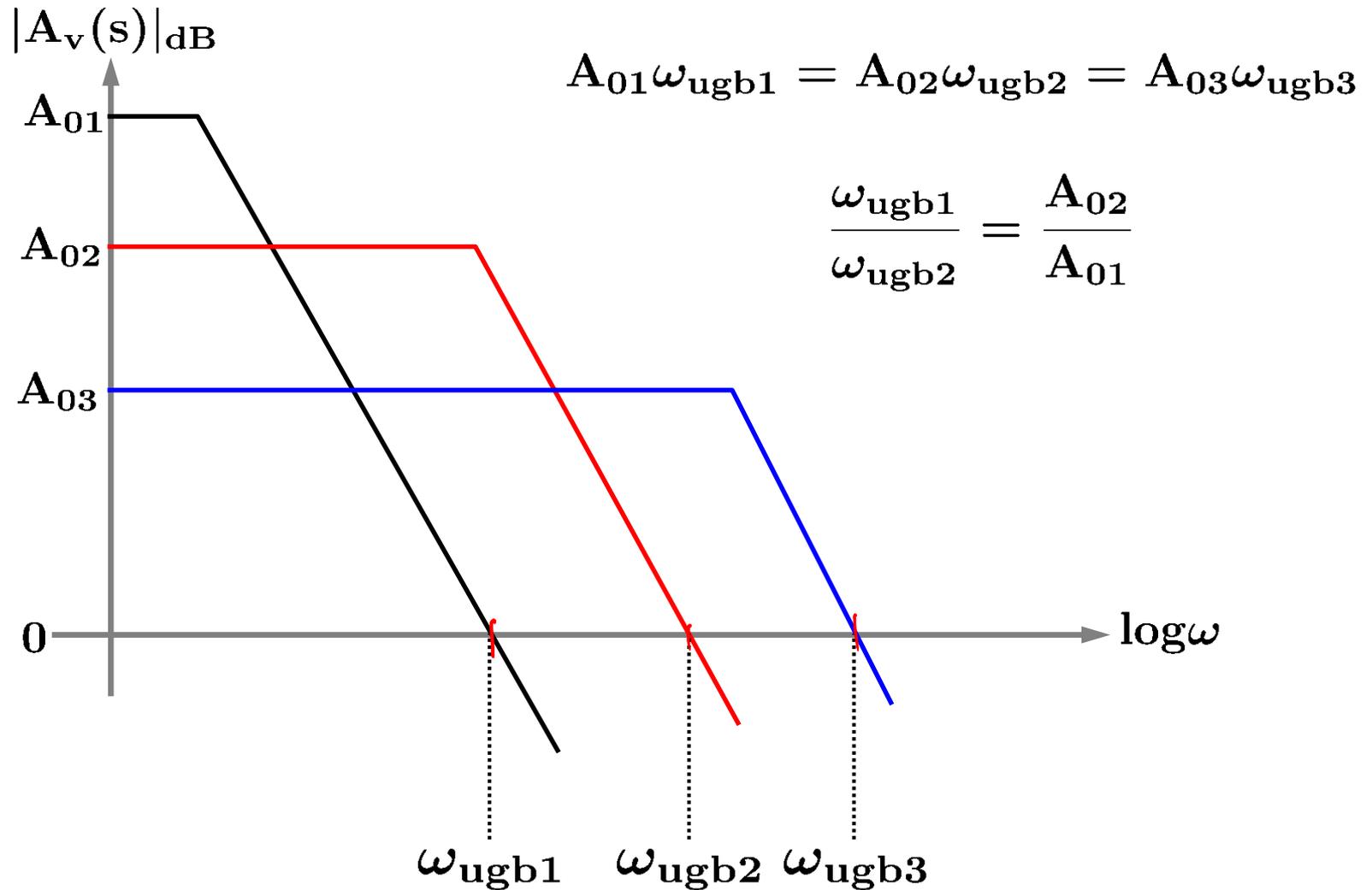

Cascoded CS (CCS) Amplifier

Common source + Common gate = Cascode

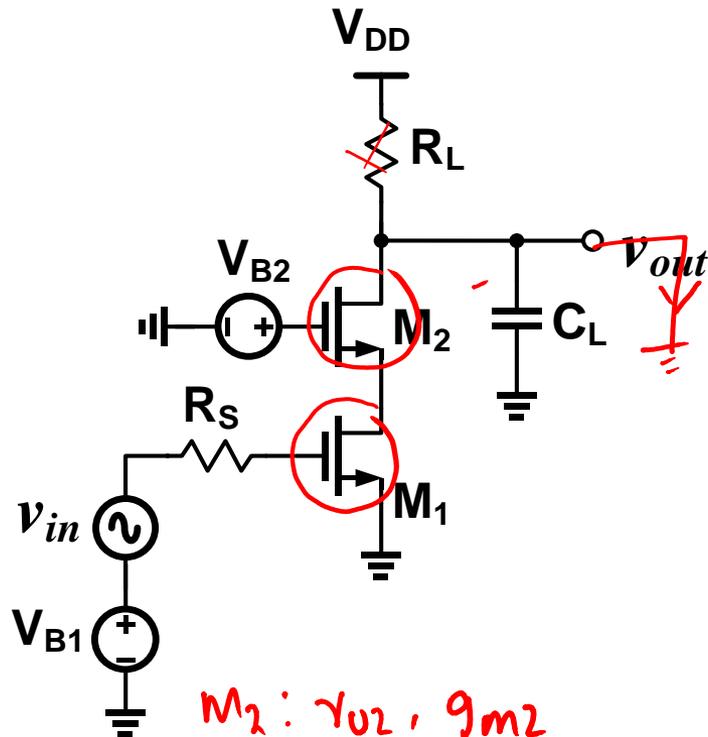

$M_2: r_{o2}, g_{m2}$

$M_1: r_{o1}, g_{m1}$

$$R_{out} = R_L \parallel (r_{o2} + r_{o1} + g_{m2}r_{o2}r_{o1})$$

$$G_m = g_{m1} \frac{r_{o1}}{r_{o1} + 1/g'_{m2}} \approx g_{m1}$$

$G_m V_{in} = i_{out}$


$$DC \text{ gain } A_v = -G_m R_{out}$$

$$A_v \approx -(\underbrace{g_{m1}r_{o1}})(\underbrace{g_{m2}r_{o2}}) \text{ for large } R_L$$

$$A_v \propto (\underbrace{g_m r_o})^2$$

Gain is boosted by $g_m r_o$

Bandwidth Extension

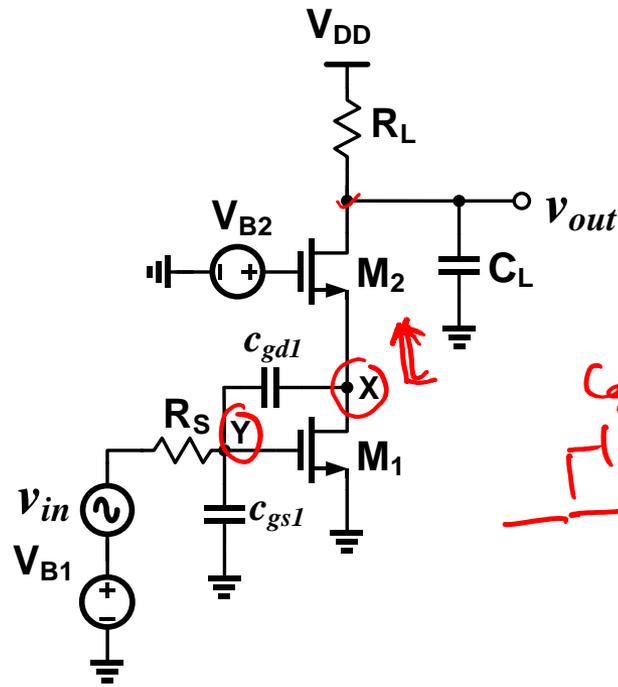


$$g'_{m2} = g_{m2} + g_{mb2}$$

$$\omega_{in} \approx \frac{1}{R_S \left[C_{gs1} + \left(1 + \frac{g_{m1}}{g'_{m2}} \right) C_{gd1} \right]}$$


$(1 + g_{m1} R_L) C_{gd1}$

$$\frac{g_{m1}}{g'_{m2}} \leq 1$$

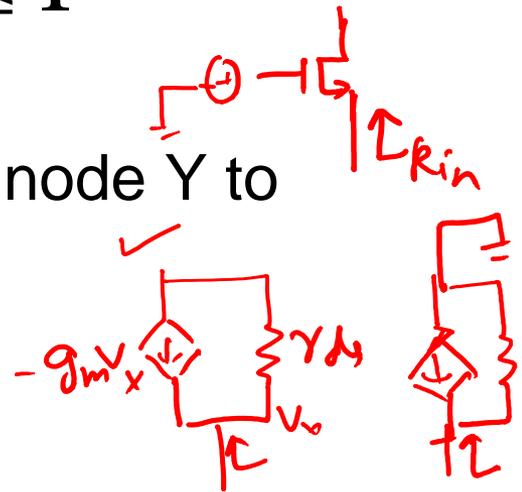- Cascode transistor reduces the gain from node Y to node X → suppresses miller effect
- Negligible impact of R_L on this benefit




CCS Amplifier Frequency Response

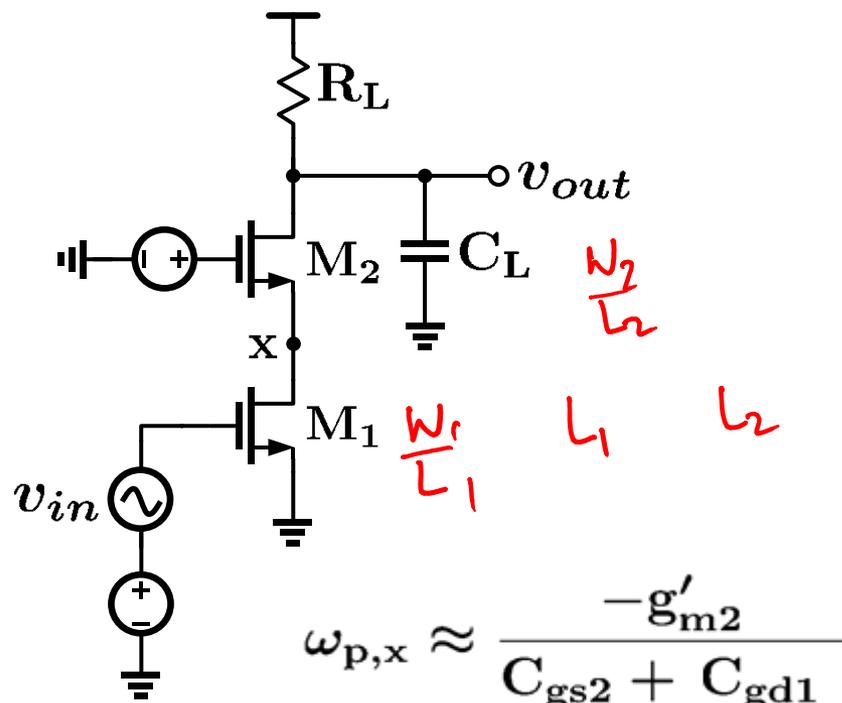

$$\omega_{p,x} \approx \frac{-g'_{m2}}{C_{gs2} + C_{gd1}}$$


$$\omega_{p,out} \approx \frac{-1}{R_{out} C_L}$$
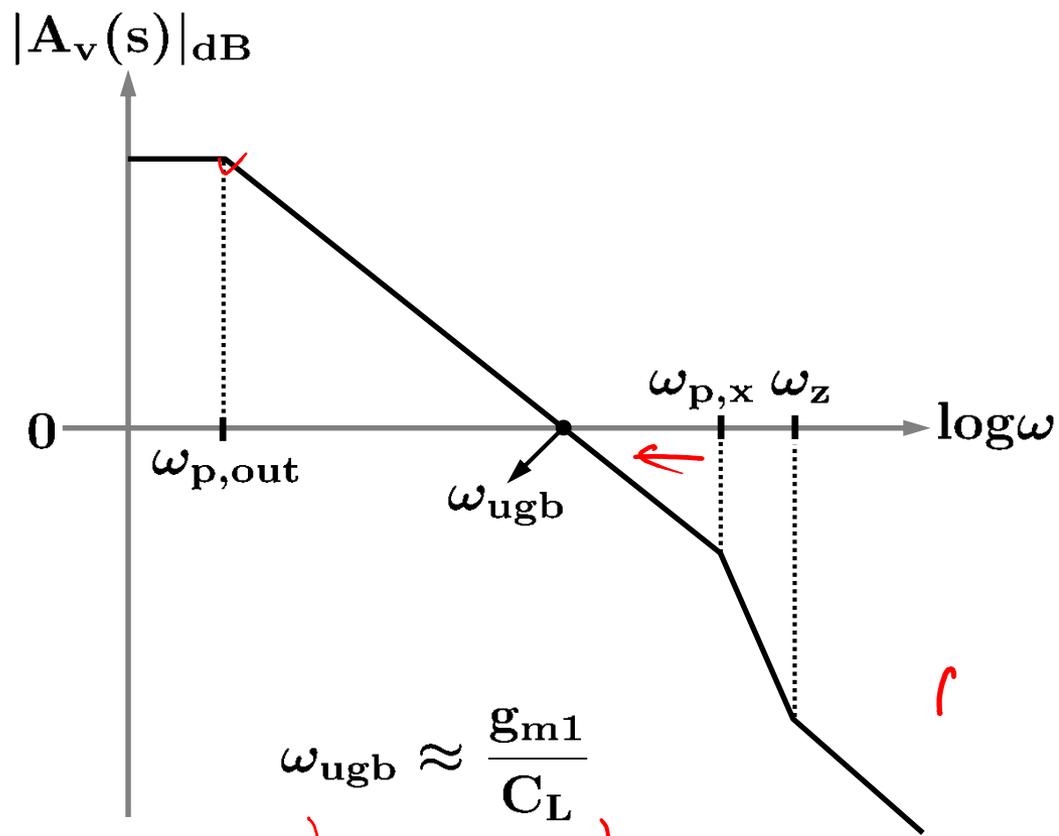
$$\omega_z \approx \frac{g_{m1}}{C_{gd1}}$$





$$\omega_{ugb} \approx \frac{g_{m1}}{C_L}$$

CS Vs. CCS Amplifier

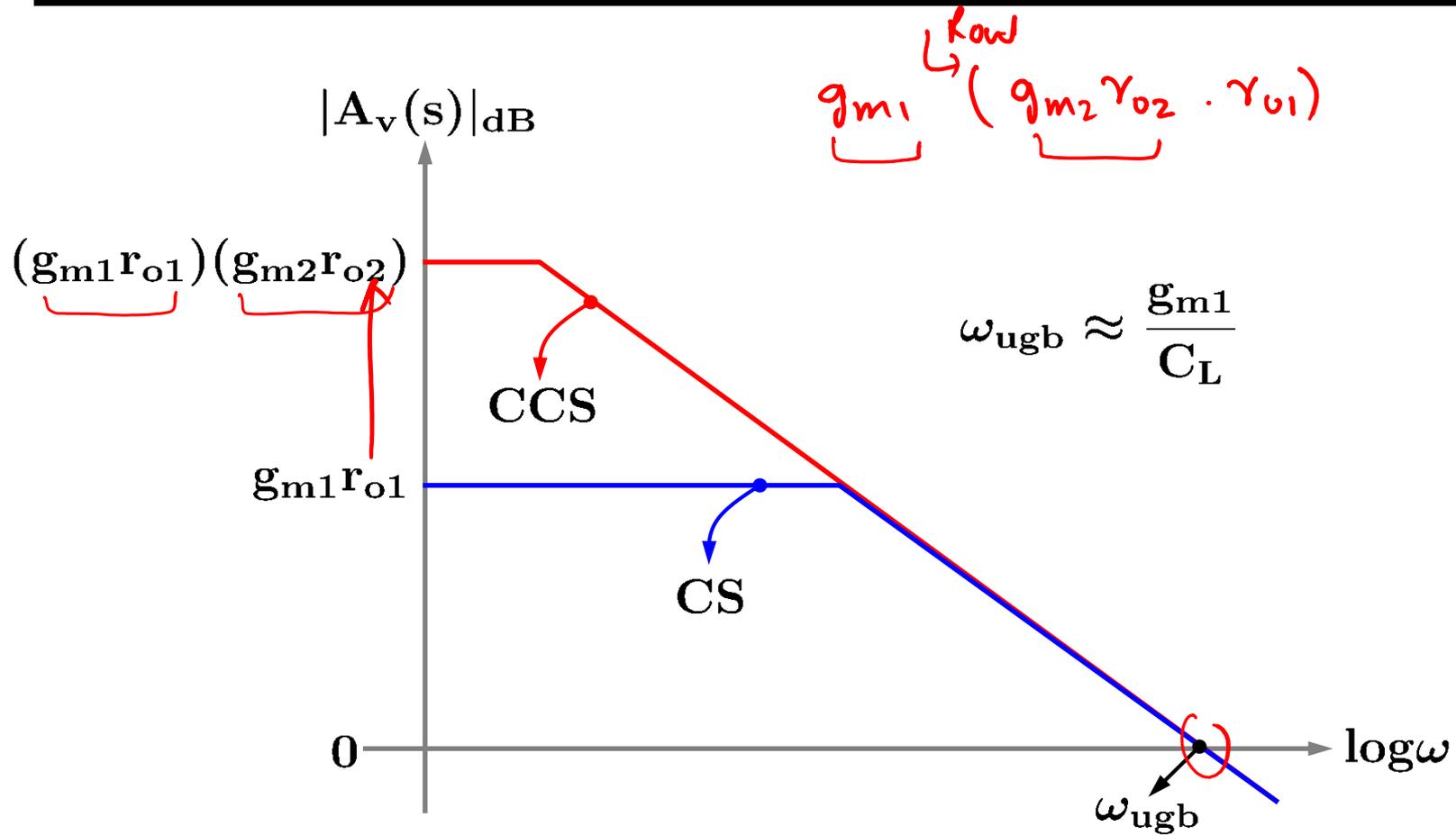

Common-Gate Amplifier

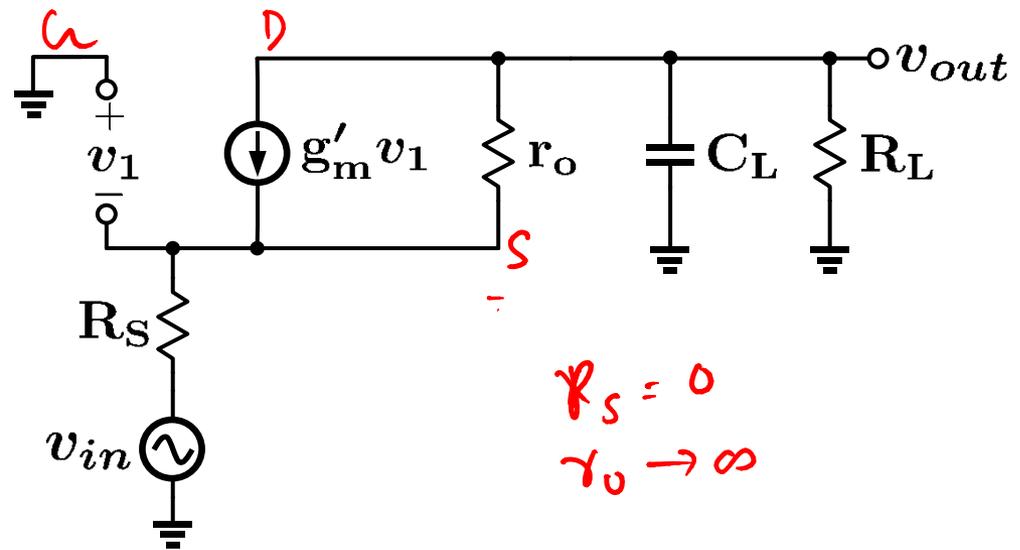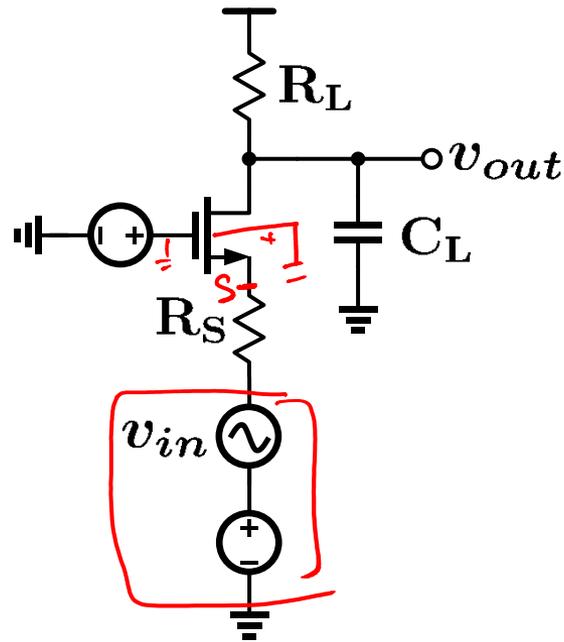

$$R_S = 0$$

$$r_o \rightarrow \infty$$


$$g'_m = g_m + g_{mb}$$

$$v_{out} = g'_m v_{in} \cdot R_L$$

$$\frac{v_{out}(s)}{v_{in}(s)} = \frac{1 + g'_m r_o}{r_o + R_S + g'_m r_o R_S + R_L} R_L$$

∴

CG Amplifier Input Impedance

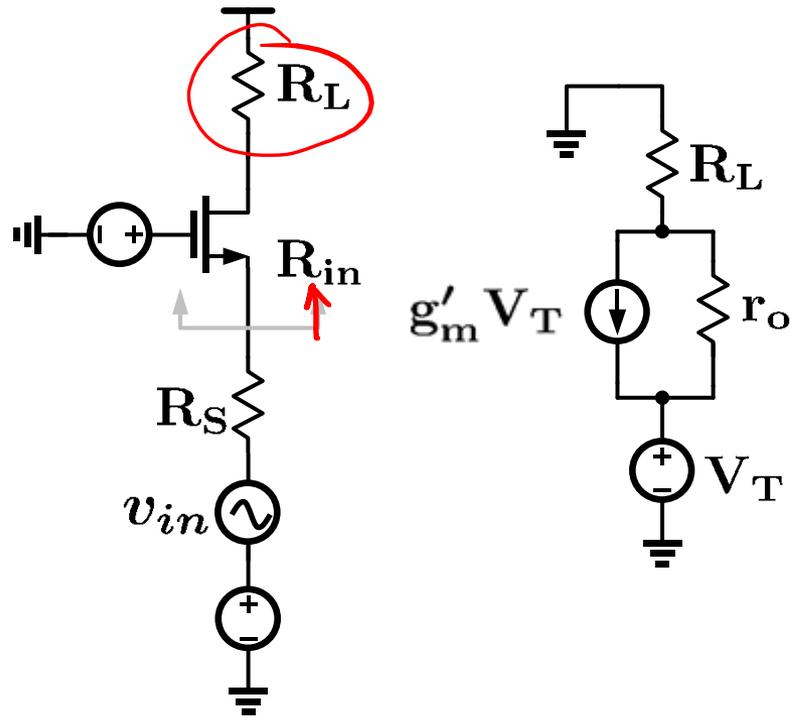

$$R_L I_T + r_o (I_T - g'_m V_T) = V_T$$


$$R_{in} = \frac{V_T}{I_T} = \frac{R_L + r_o}{1 + g'_m r_o}$$

$$R_{in} \approx \frac{1}{g'_m} \left(1 + \frac{R_L}{r_o} \right) \text{ if } g'_m r_o \gg 1$$


$$R_{in} \approx \frac{1}{g'_m} \text{ if } R_L \ll r_o \text{ and } g'_m r_o \gg 1$$

$$R_{in} \approx \frac{R_L}{g'_m r_o} \text{ if } R_L \gg r_o \text{ and } g'_m r_o \gg 1$$

CG Amplifier Output Impedance

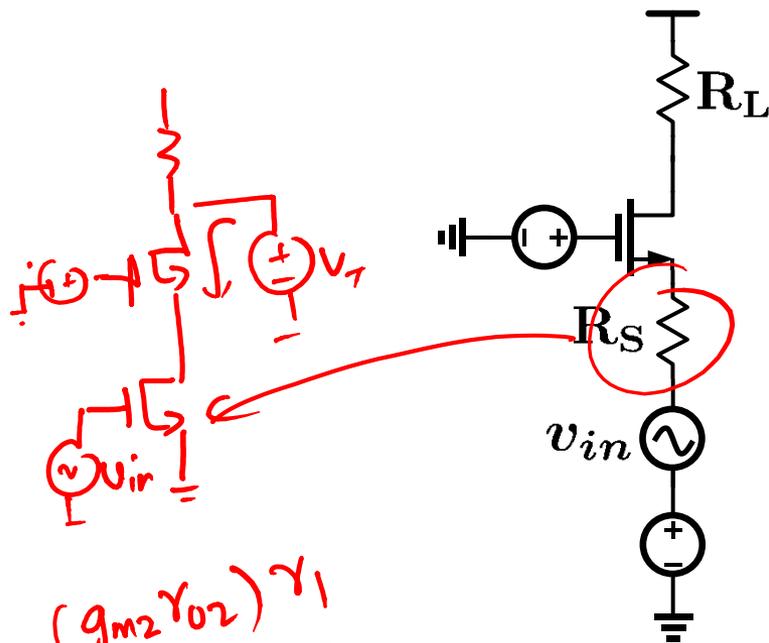

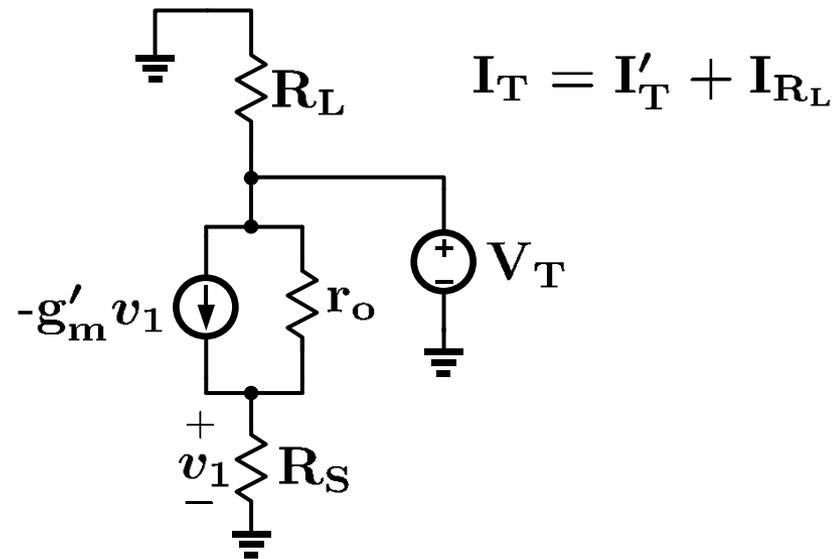$(g_{m2} r_{o2}) r_1$
 $(g_{m2} r_{o2}) R_S$





$$I_T = I'_T + I_{R_L}$$

$$V_T = r_o (I'_T + g'_m R_S I'_T) + I'_T R_S$$

$$R_{out} = \frac{V_T}{I_T} = R_L \parallel (r_o + R_S + g'_m r_o R_S)$$

$$R_{out} \approx R_L \parallel r_o (1 + g'_m R_S)$$


CG Amplifier Frequency Response

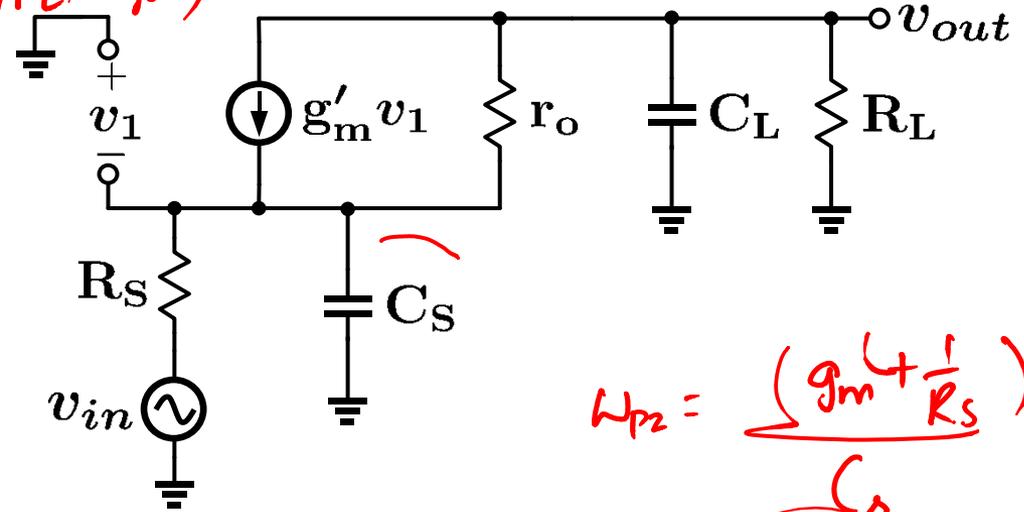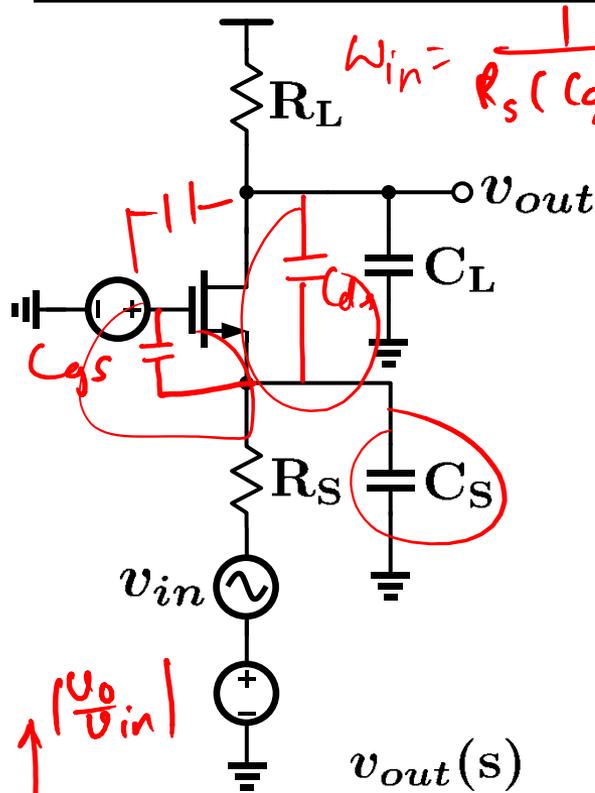

if $r_o = \infty$


$$\omega_{p2} = \frac{g'_m + \frac{1}{R_S}}{C_S}$$

$$\approx \frac{1}{R_S C_S}$$

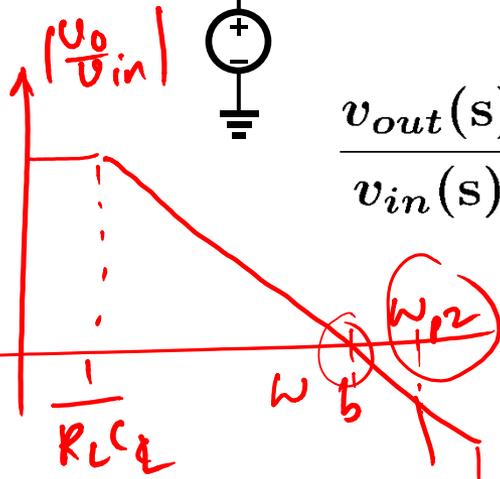

$$\frac{v_{out}(s)}{v_{in}(s)} = \frac{g'_m R_L}{1 + g'_m R_S} \frac{1}{\left(1 + \frac{C_S}{\left(g'_m + \frac{1}{R_S}\right)} s\right) (1 + R_L C_L s)}$$


Source Follower

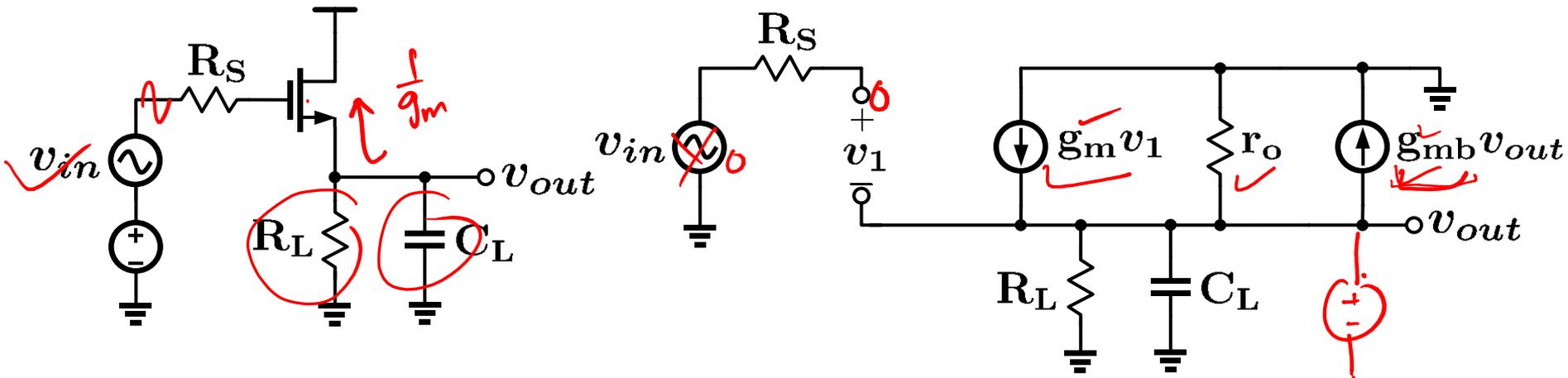

$$R'_L = r_o \parallel \frac{1}{g_{mb}} \parallel R_L$$

$$\frac{v_{out}(s)}{v_{in}(s)} = \frac{R'_L}{R'_L + \frac{1}{g_m}} = \frac{g_m}{g_m + \frac{1}{R'_L}} = \frac{g_m R'_L}{1 + g_m R'_L}$$

Source Follower Frequency Response

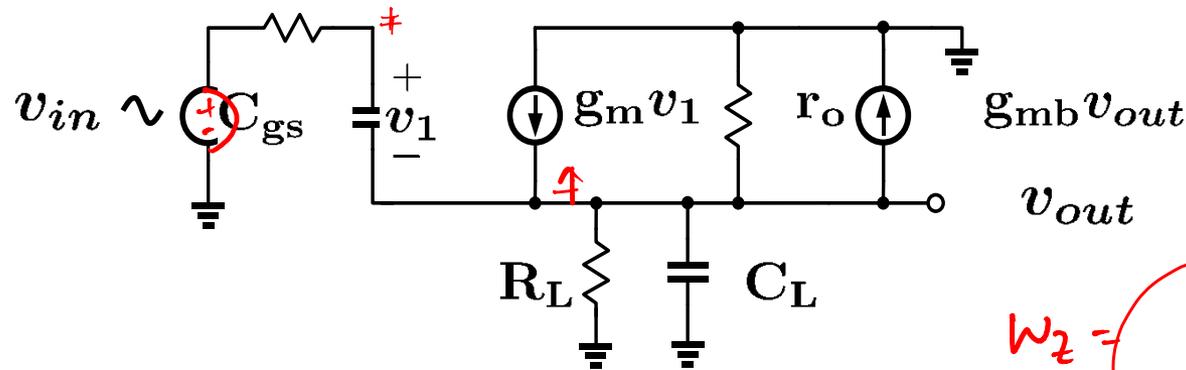


if $R_S = 0$ and $C_{gd} = 0$

$$\frac{v_{out}(s)}{v_{in}(s)} = \frac{g_m}{g_m + \frac{1}{R'_L}} \frac{1 + sC_{gs}/g_m}{1 + \frac{s(C_{gs} + C_L)}{g_m + \frac{1}{R'_L}}}$$

$\omega_z = \frac{g_m}{C_{gs}}$ ✓
 $\omega_p = \frac{g_m + \frac{1}{R'_L}}{C_{gs} + C_L}$ ✓
 $\approx \frac{g_m}{C_{gs} + C_L} = \frac{g_m}{C_{gs}}$ ✓

Source Follower Input Impedance

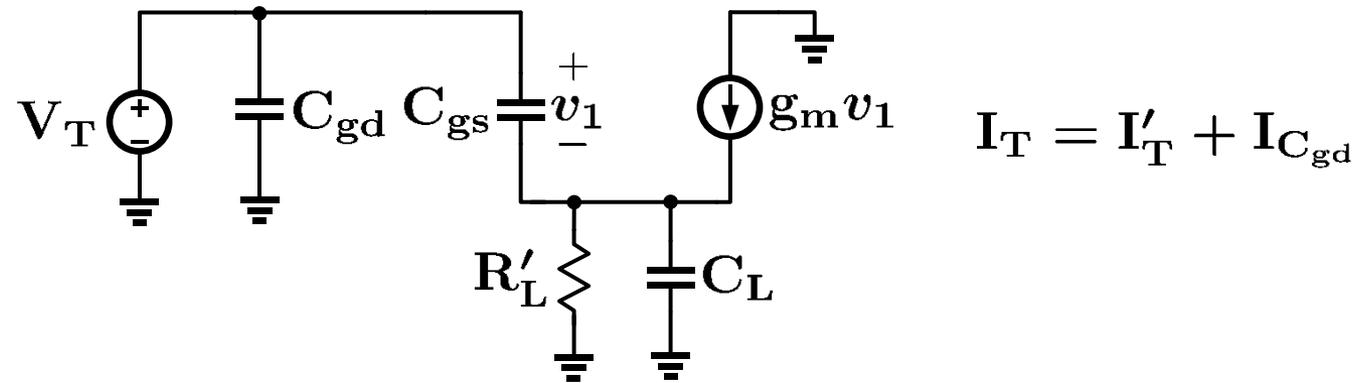

$$V_T = \frac{I'_T}{sC_{gs}} + (I'_T + \frac{g_m I_T}{C_{gs} s})(R'_L \parallel \frac{1}{C_L s})$$

$$Z_{in}(s) = \left[\frac{1}{C_{gs} s} + \left(1 + \frac{g_m}{C_{gs} s}\right) \left(\frac{R'_L}{1 + R'_L C_L s}\right) \right] \parallel \frac{1}{C_{gd} s}$$

Source Follower Input Capacitance


for $|R'_L C_L s| \ll 1$

$$Z_{in}(s) \approx \left[\frac{1}{C_{gs}s} + \left(1 + \frac{g_m}{C_{gs}s}\right) R'_L \right] \parallel \frac{1}{C_{gd}s}$$

$$C_{in}(s) \approx C_{gd} + C_{gs} \left(\frac{g_{mb}}{g_m + g_{mb}} \right)$$

A very small input capacitance until moderate frequencies

Source Follower Output Impedance

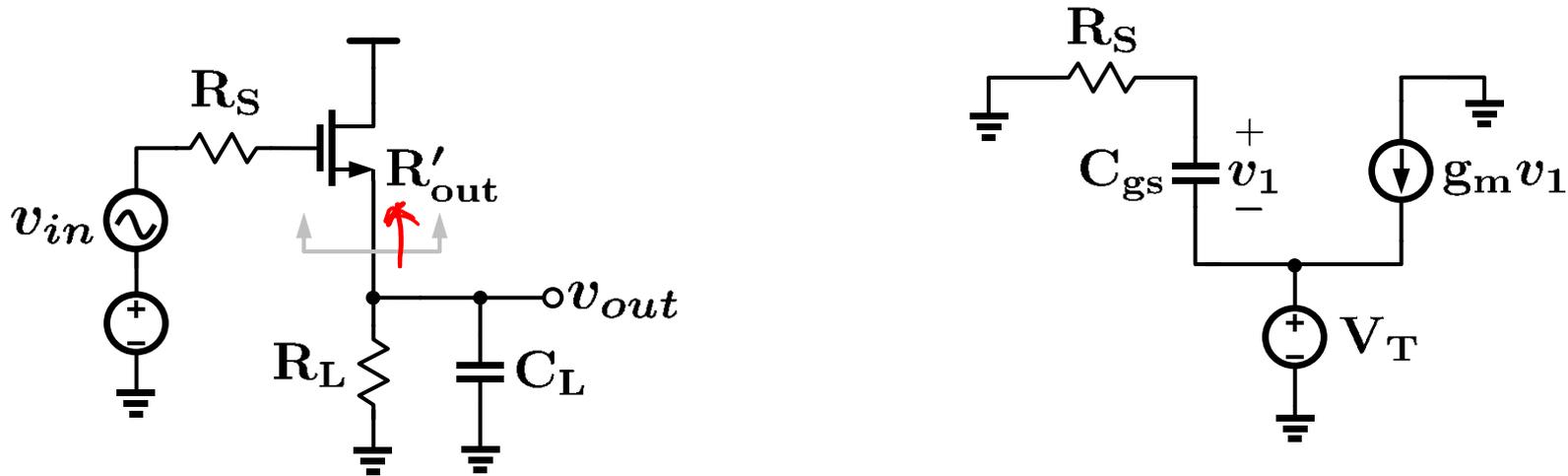

$$v_1 C_{gs} s + g_m v_1 = -I_T$$

$$v_1 C_{gs} R_S s + v_1 = -V_T$$

$$Z_{out}(s) = \frac{R_S C_{gs} s + 1}{g_m + C_{gs} s} \parallel \frac{1}{s C_L} \parallel R'_L$$

A closer look at SF Output Impedance

$|Z(\omega)| = 1 \quad R$
 $|Z(\omega)| \propto \frac{1}{\omega} \quad C$
 $\propto \omega \quad L$

$Z_{out}(s) \approx \frac{1 + R_S C_{gs} s}{g_m + C_{gs} s}$

$\omega_z = \frac{1}{R_S C_{gs}}$

$\omega_p = \frac{g_m}{C_{gs}}$

