
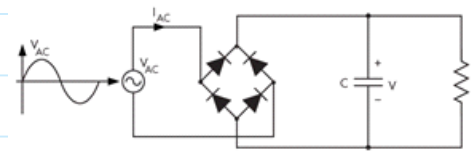

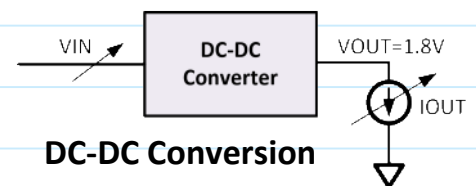
# What is Power Management?

- Efficient and reliable means of power delivery to a system.
- AC-DC / DC-AC
- DC-DC (Voltage Regulator)




AC-DC/DC-AC Conversion



DC-DC Conversion

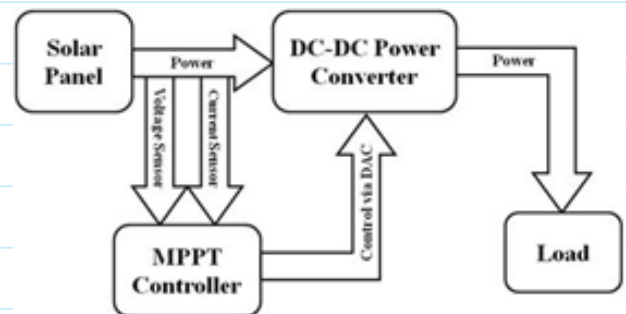
- Generating / Supply Power from freely available resources.



Energy Harvesting

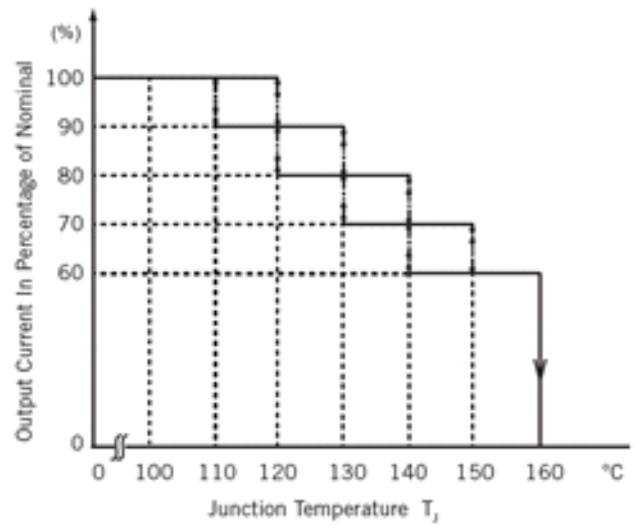
## What is Power Management (Contd.)

Thermal management  
→ manage heat or losses



Current/Power derating

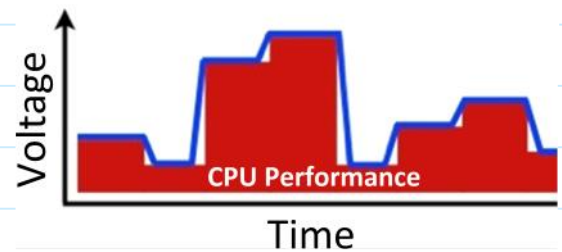Voltage is controlled based  
on CPU performance



Dynamic Voltage Scaling (DVS)

# PMIC Vs Power Electronics



High Power - Power Electronics  
(Discrete Solution)

Source: ST Microelectronics



Low/Mid Power - Power Management IC  
(Integrated Solution)


## Power Electronics

- Large solution mainly due to discrete components
- Deals with high power  $\rightarrow 100s\ W \rightarrow kW$

## PMIC


- Smaller solution
- Single chip PMIC with off-chip passive components
- Low/mid power  $\mu W \rightarrow 10s\ W$

## Why do we need PMIC?

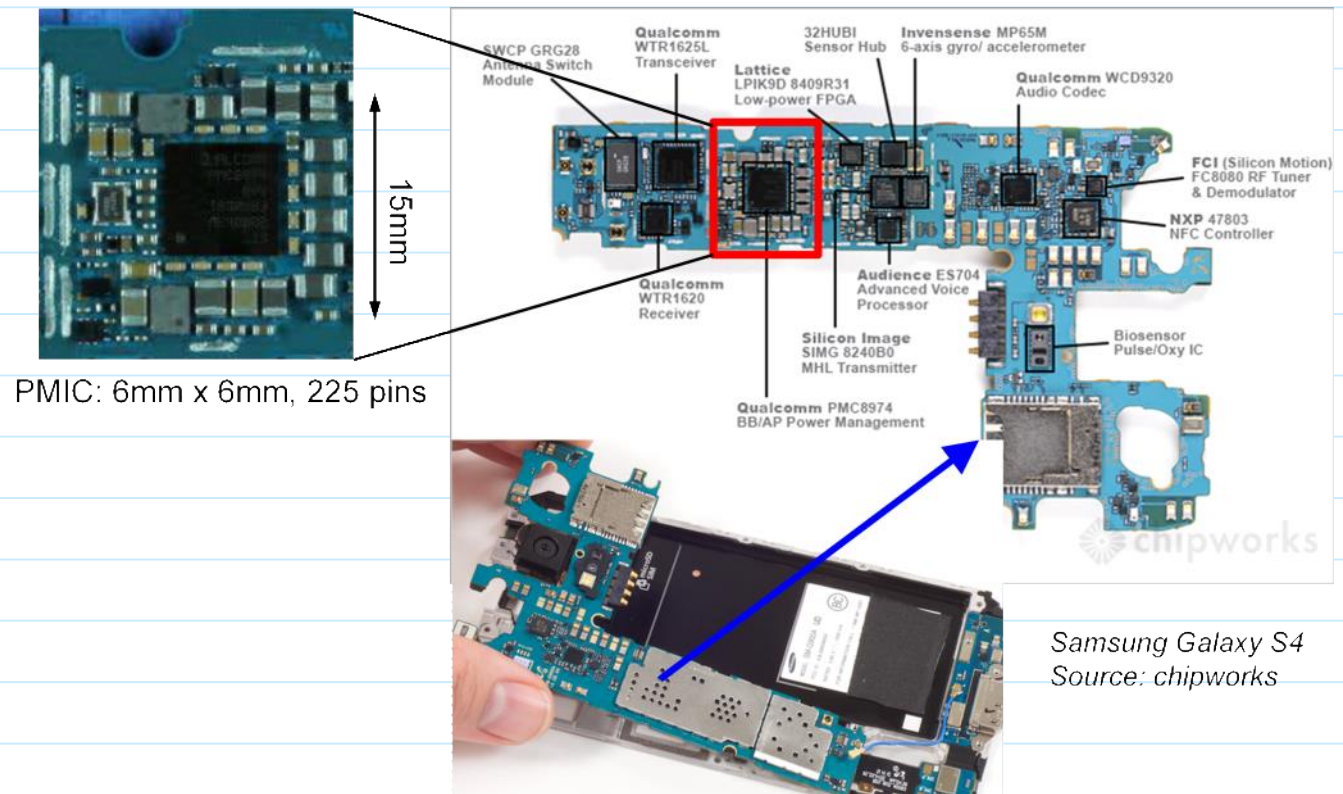


Need higher power in smaller area  
→ Higher power density  
→ PMIC integrates most of the components on-chip hence reduces overall size.

# Applications of PMIC

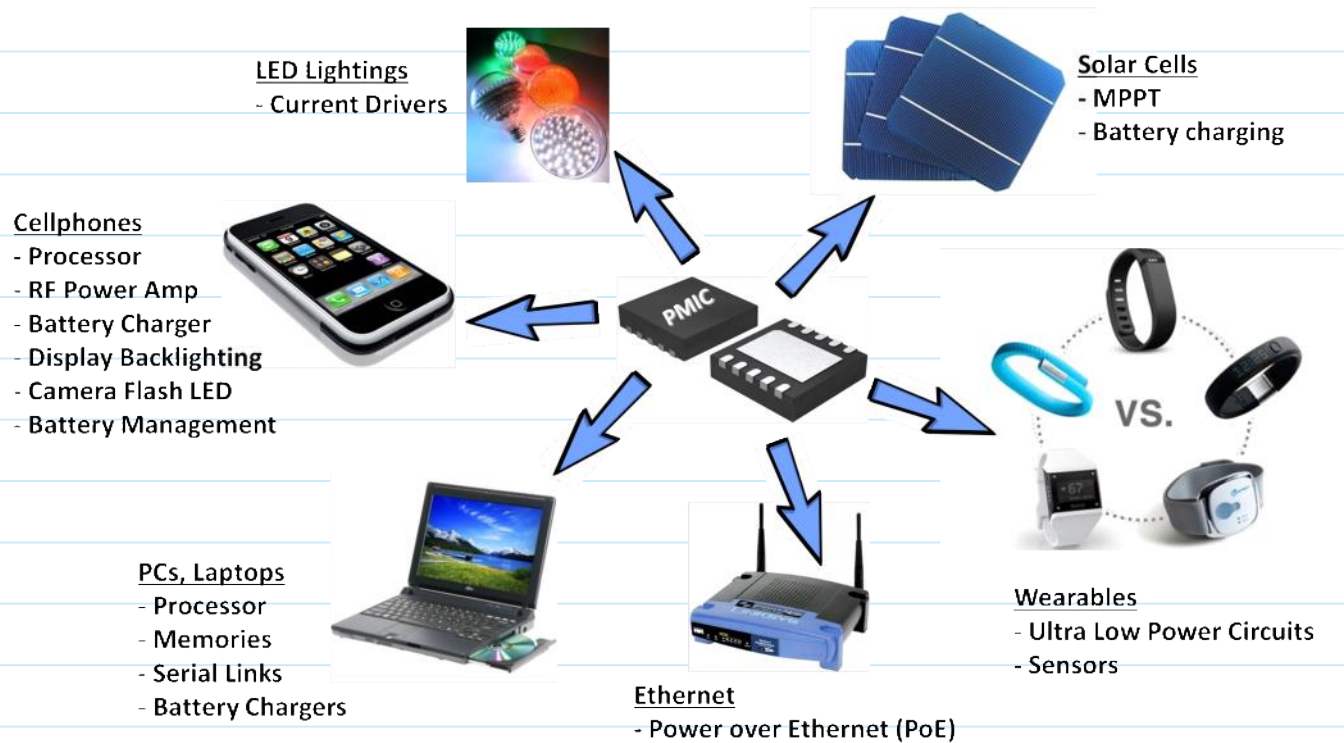


## DC - DC converter (Voltage Regulator)

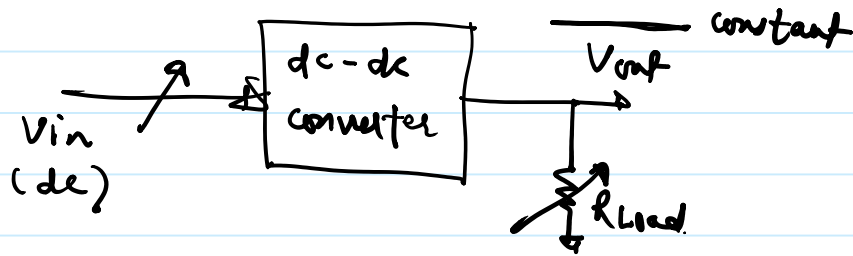


- converts voltage from one power domain to other
- constant  $V_{out}$
  - $V_{out} > V_{in}$
  - $V_{out} < V_{in}$
  - $V_{out} = V_{in}$

## Types of dc-dc converter

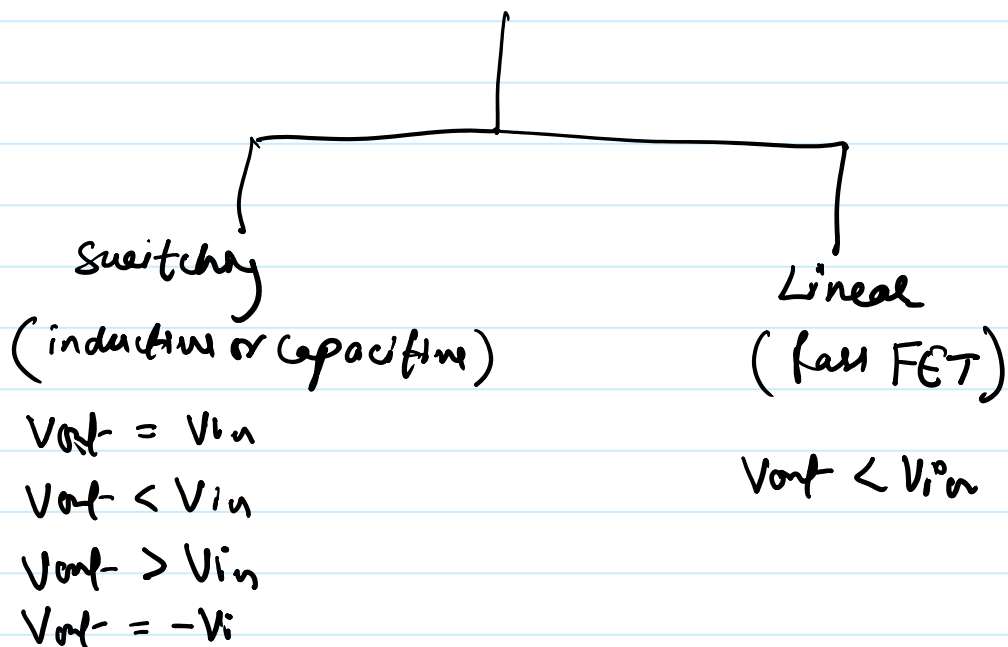


# Switching Vs Linear Regulators

Switching

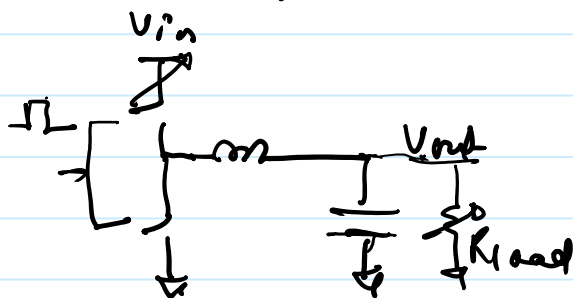


PWM based

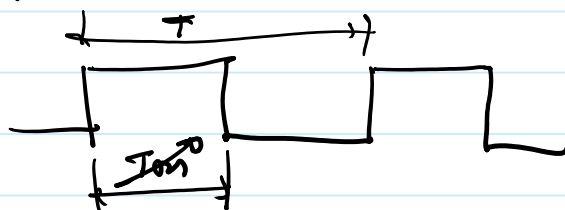

$$V_{out} = D \cdot V_{in}$$

$$D = \frac{T_{on}}{T}$$

Linear

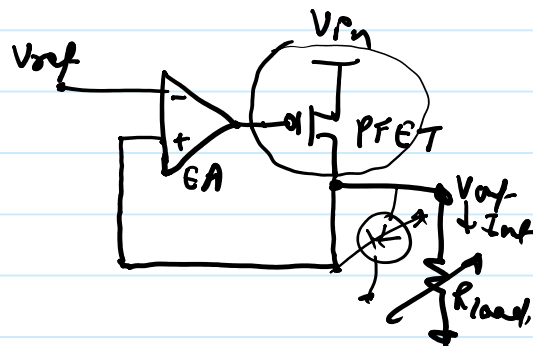

$$V_{drop} = V_{in} - V_{out}$$

$$P_{loss} = V_{drop} \times I_{out}$$

$$V_{in} = 5V$$

$$V_{out} = 1V$$

$$I_{out} = 1A$$

$$V_{drop} = 5 - 1 = 4V$$

## Switching Vs Linear Regulators - Contd.

Switching

$$V_{out} = 1V$$

$$I_{out} = 1A$$

$$R_{ds-on} = 100m\Omega$$

$$P_{out} = V_{out} \times I_{out} \\ = 1W$$

switch losses

$$= I_{out}^2 R_{ds-on} = (1)^2 \times 0.1 \\ = 100mW$$

$$\eta \approx 90\%$$

Linear

$$P_{loss} = V_{drop} \times I_{out} \\ = 4W$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{out} + P_{loss}}$$

$$= \frac{1W}{5W} = 20\%$$

$$V_{out} = 4V$$

$$I_{out} = 1A$$

$$V_{drop} = 5 - 4 = 1V$$

$$P_{loss} = 1W$$

$$\eta = \frac{4W}{5W} = 80\%$$

