

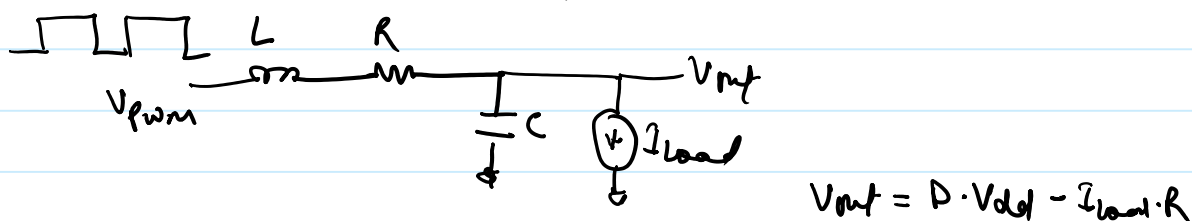
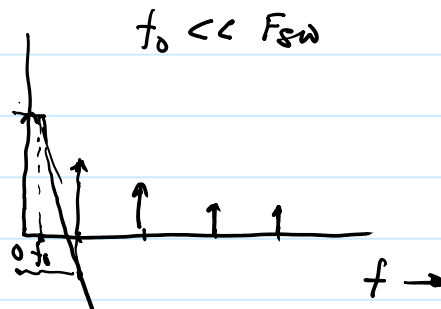


Switching Regulator - Basic Concept

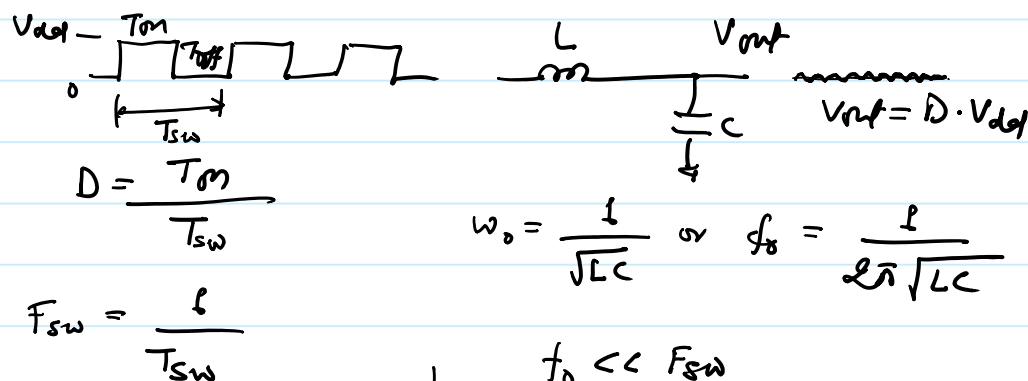
- # works on the principle of PWM
- # preferred for higher power applications due to better efficiency
- # switching converters can be step-up, step-down, inverting
- # dc-dc converter
- # buck \rightarrow step-down $V_{in} > V_{out}$
- # boost \rightarrow step-up $V_{in} < V_{out}$
- # Buck-boost \rightarrow buck + boost & $V_{in} = V_{out}$
- # Inverting $\rightarrow V_{out} < 0$



Switching Regulator - Closed Loop

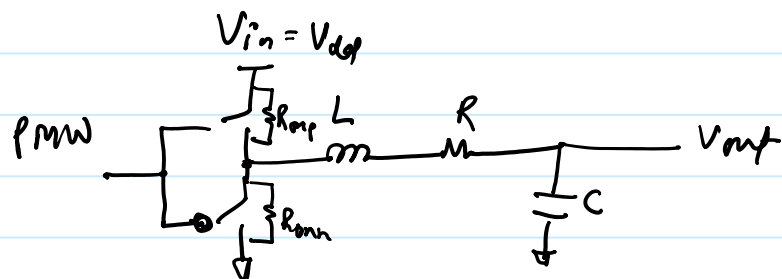
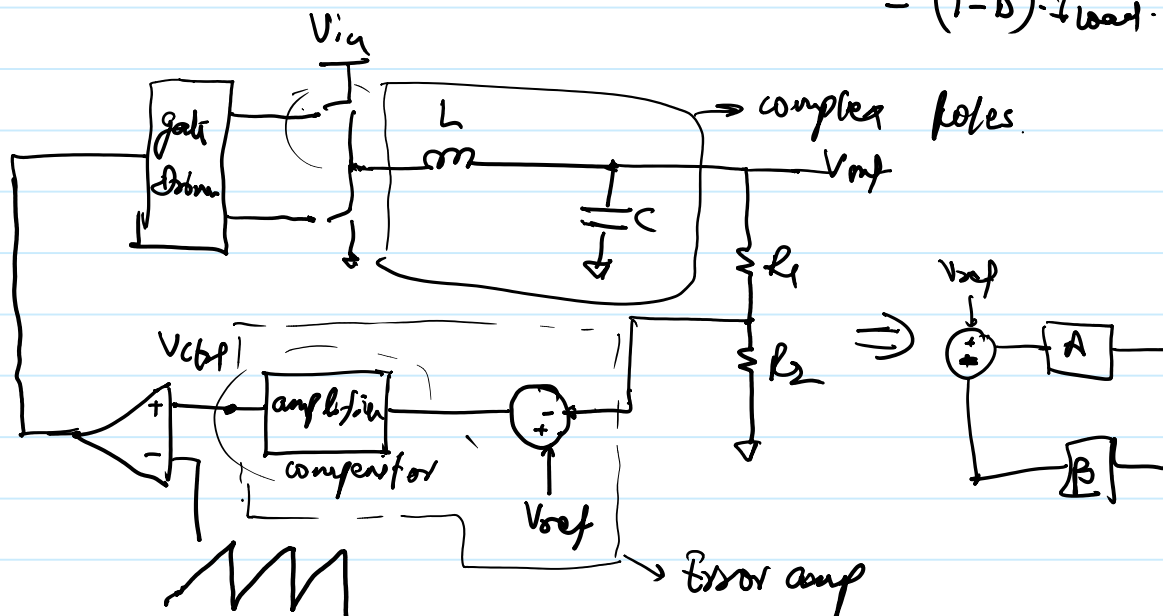
$$V_{out} = D \cdot V_{in} - I_{load} \cdot R - D \cdot I_{load} \cdot R_{DS(on)} - (1-D) \cdot I_{load} \cdot R_{DS(on)}$$



type-no \rightarrow no. of integrators in a system.

compensators

type-1 \rightarrow Integral compensation (I)

type-2 \rightarrow Proportional & Integral (PI)

type-3 \rightarrow Proportional-Integral-Derivative (PID)