
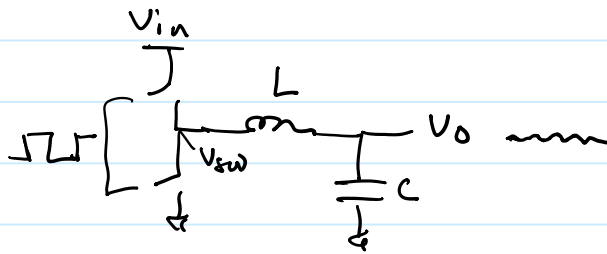


Inductor Volt-Second Balance

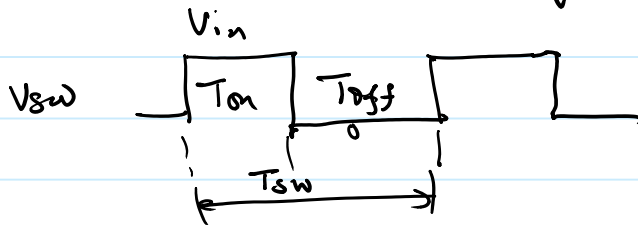

Inductor $\rightarrow$

$$V_L = L \frac{di}{dt} \Rightarrow i = \frac{1}{L} \int V_L dt$$




$$V_L \cdot D \cdot T_{sw} + V_L (1-D) T_{sw} = 0$$

Volt-second balance

$$(V_{in} - V_o) D + (-V_o) (1-D) = 0$$

$$D \cdot V_{in} - D \cdot V_o - V_o + V_o D = 0$$
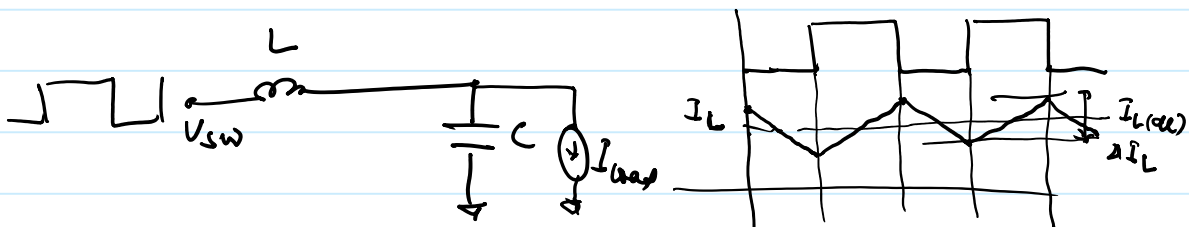
$$\Rightarrow \boxed{V_o = D \cdot V_{in}}$$



$$i_L = \bar{i}_L(dc) + \Delta i_L$$

$$\bar{i}_L(dc) = I_{load}$$

Output Ripple

$$V_L = L \frac{di}{dt}$$

$$\frac{(V_{in} - V_o)}{L} \times T_{on} = \Delta I_L$$



during T_{off}

$$-\frac{V_o}{L} \times T_{off} = -\Delta I_L$$

$$= -\frac{D \cdot V_{in} (1-D) T_{sw}}{L} = -\frac{D(1-D)}{L} V_{in} T_{sw}$$

..
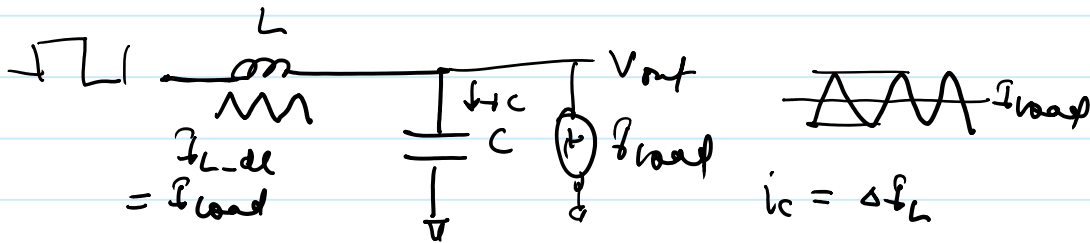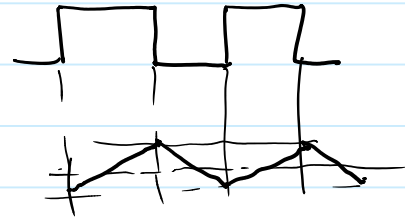
$$\frac{(V_{in} - D \cdot V_{in})}{L} D \cdot T_{sw} = \frac{D(1-D)}{L} \cdot V_{in} T_{sw}$$




Average current through Cap = 0

if $V_{out} = \text{constant}$

$$i = C \frac{dV}{dt}$$

$$V = \frac{1}{C} \int i dt$$

Output Ripple (contd.)

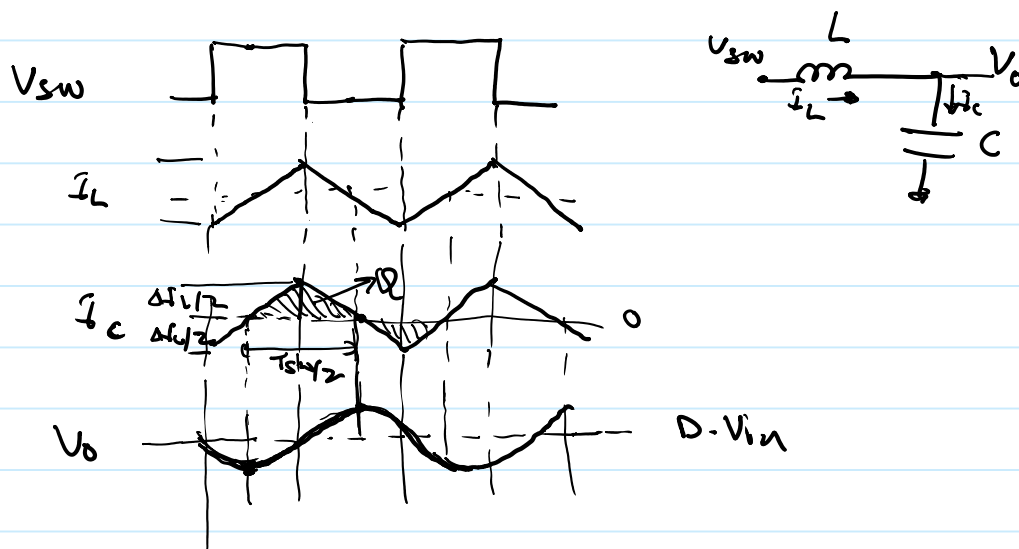

$$\Delta I_L = \frac{V_{in} D(1-D)}{L} T_{sw}$$

$$\text{Area of } \Delta = Q = \frac{1}{2} \text{ base} \times \text{ht}$$

$$= \frac{1}{2} \times \frac{T_{sw}}{2} \times \frac{\Delta I_L}{2}$$

$$= \frac{1}{8} T_{sw} \times \Delta I_L = \frac{\Delta I_L}{8 \cdot F_{sw}}$$

$$Q = CV \Rightarrow \Delta V = \frac{Q}{C}$$

$$\Delta V = \frac{\Delta I_L}{8 \cdot F_{sw} \cdot C} = \frac{V_{in} D(1-D)}{8 \cdot F_{sw}^2 \cdot CL}$$

output ripple.

$$\Delta V = \frac{D(1-D)}{8 \cdot F_{sw}^2 \cdot CL} V_{in}$$

by specification

by design