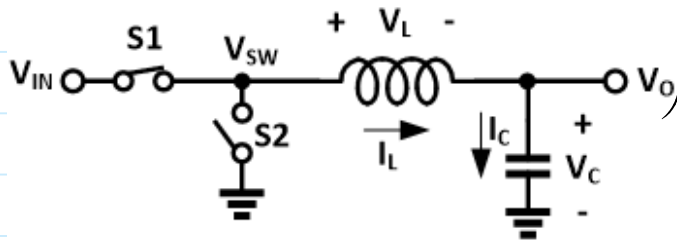


Inductor Ripple Current vs. D



$$\Delta I_L = \frac{V_{IN} D \cdot (1-D)}{L} T_{SW} = \frac{V_{IN} D \cdot (1-D)}{L} \frac{1}{F_{SW}} \quad \text{--- (1)}$$

$$\Delta I_L = \frac{V_O (1-D)}{L} \cdot \frac{1}{F_{SW}} \quad \text{--- (2)}$$



From (1)

$$\frac{\partial \Delta I_L}{\partial D} = \frac{V_{in} (1-2D)}{L} \times \frac{1}{F_{SW}} = 0 \quad (V_{in} = \text{constant})$$

$$\Rightarrow D = 0.5$$

From (2) $V_O = \text{constant}$

$$\Delta I_L \propto (1-D)$$

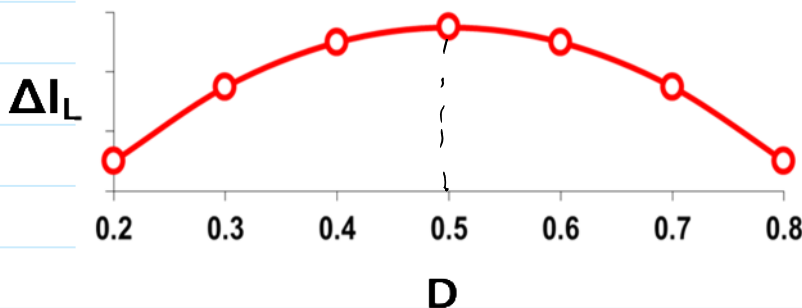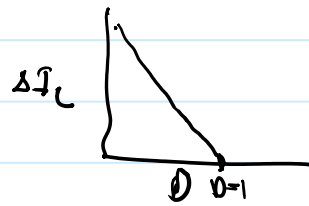

Example

$$\Delta I_L = \frac{V_o (1-D)}{L} \times \frac{1}{f_{sw}}$$

$$L = 1 \mu\text{H}, \quad f_{sw} = 1 \text{ MHz}$$


$$V_o = 1 \text{ V}$$

$$V_{in} = 5 \text{ V} \Rightarrow D = \frac{1}{5} = 0.2$$

$$\Delta I_L = \frac{(1 - 0.2)}{L} = 0.8 \text{ A}$$


$$V_{in} = 2 \text{ V} \Rightarrow D = 0.5$$

$$\Delta I_L = 0.5 \text{ A}$$


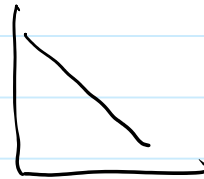


Output Voltage Ripple vs. D
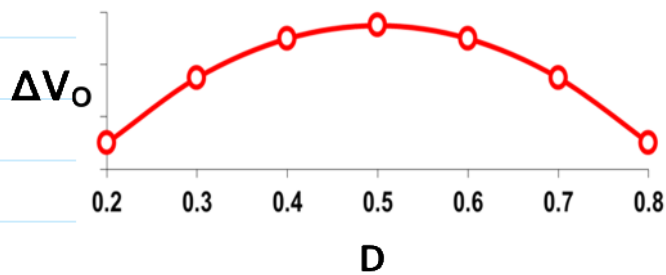
$$\Delta V_o = \frac{V_{IN} \cdot D \cdot (1 - D)}{8 \cdot L \cdot C \cdot F_{SW}^2}$$




Fsw vs. L & C size

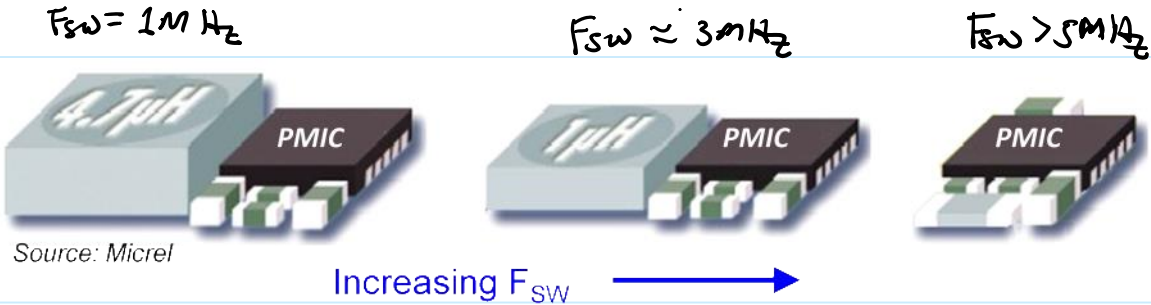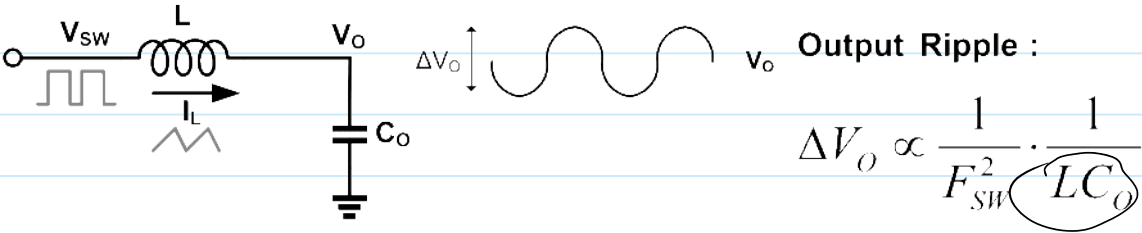

Choosing L & C
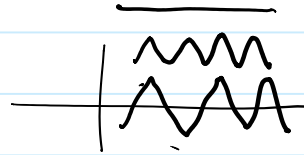
$$\Delta V_o \propto \frac{I}{f_{sw}^2} \times \frac{I}{L \times C}$$




Higher L & lower C

ΔI_L is small \rightarrow RMS losses are reduced. (good)

current slew rate is reduced (poor transient response - Bad)
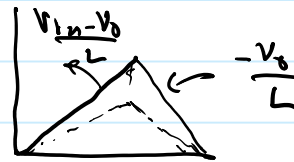
$$\Delta I_L \propto \frac{V_{in} - V_o}{L}$$



smaller Cap \rightarrow poor transient response.

$$\Delta V_{uv/ov} \propto I_{load}^2$$

Lower L & Higher C

ΔI_L is large \rightarrow higher RMS losses (bad)

Inductor current slew rate is increased.
 \rightarrow better transient response (good)

larger Cap \rightarrow improved transient response.

Inductor peak current is large
 \Rightarrow high saturation current

