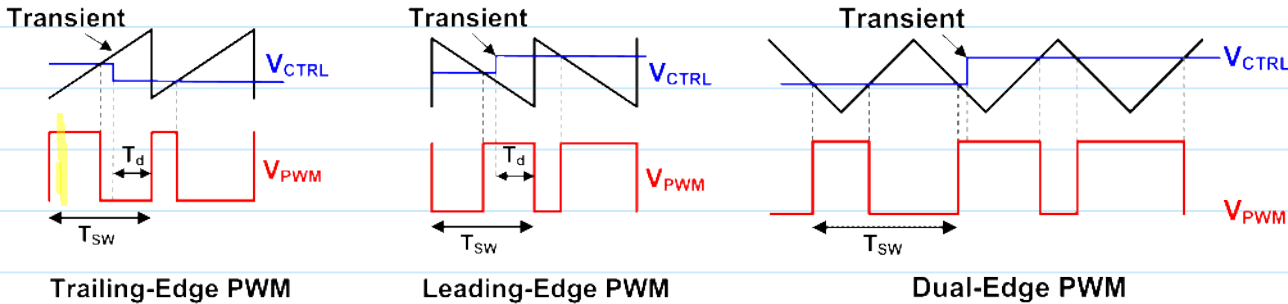


Single Edge vs. Dual Edge PWM



Trailing-Edge PWM

$$T_{d(max)} = T_{OFF} = (1 - D) \cdot T_{SW}$$

$$T_{d(max)} \approx T_{SW} \text{ for } D \approx 0$$


Leading-Edge PWM

$$T_{d(max)} = T_{ON} = D \cdot T_{SW}$$


$$T_{d(max)} = T_{SW} \text{ for } D \approx 1$$

Dual-Edge PWM


$$T_{d(max)} = \frac{T_{SW}}{2}$$

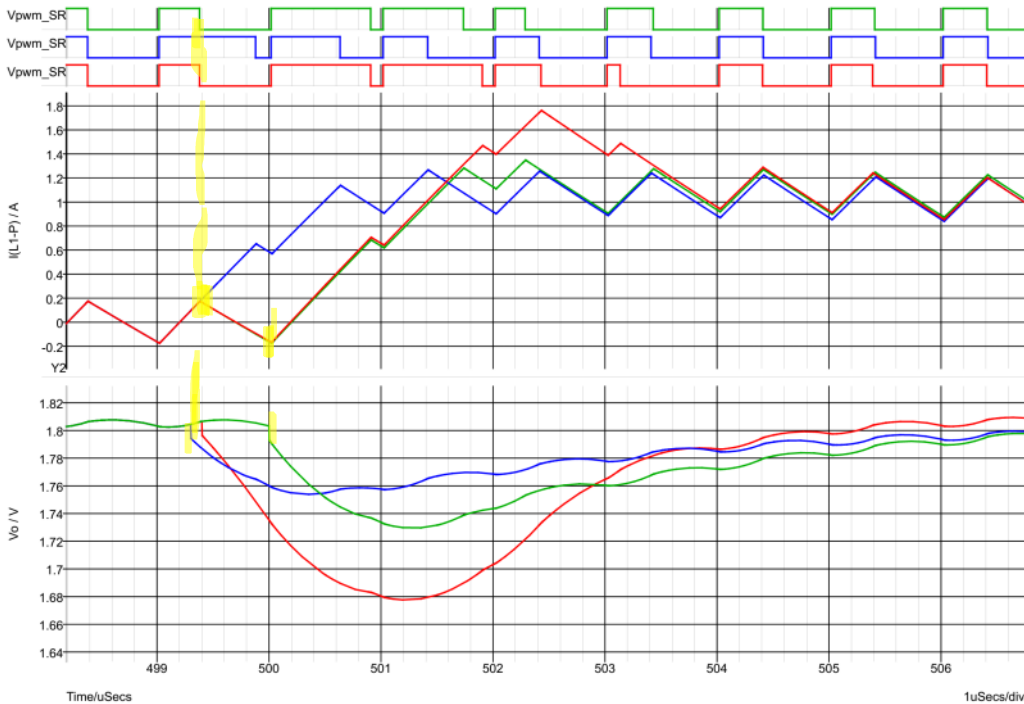

Transformer Model of Buck Converter
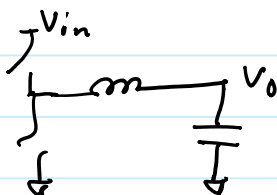
$$V_o = D \cdot V_{in}$$

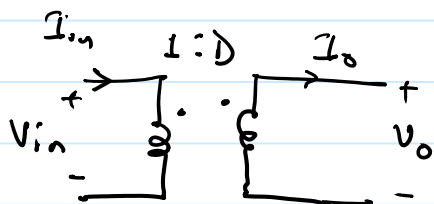
$P_{out} = P_{in}$ under ideal condition ($\eta = 100\%$)



$$V_o \cdot I_o = V_{in} \cdot I_{in}$$

$$\frac{V_o}{V_{in}} = \frac{I_{in}}{I_o}$$

$$\frac{V_o}{V_{in}} = D \Rightarrow I_{in} = D \cdot I_o$$

$$V_{in} = 5V, \quad V_o = 2.5V$$

$$D = 0.5, \quad I_o = 1A$$

$$I_{in} = 0.5A$$

Efficiency and Losses

$$\% \eta = \frac{P_{out}}{P_{in}} \times 100$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{V_o I_o}{V_{in} I_{in}} \quad \text{--- (1)}$$

$$V_o = D \cdot V_{in}$$

$$\frac{V_o}{V_{in}} = D$$

under conduction loss


$$V_o = D \cdot V_{in} - V_{loss}$$

$$\eta = \frac{\text{from (1)} \quad (D \cdot V_{in} - V_{loss}) I_o}{V_{in} \times I_{in}} = \frac{D \cdot V_{in} I_o - V_{loss} I_o}{V_{in} \times I_{in}}$$

$$I_{in} = D \cdot I_o$$

$$\frac{D \cdot V_{in} I_o - V_{loss} I_o}{I_o \times D \times V_{in}} = \boxed{\eta = 1 - \frac{V_{loss}}{D \cdot V_{in}}}$$

Losses

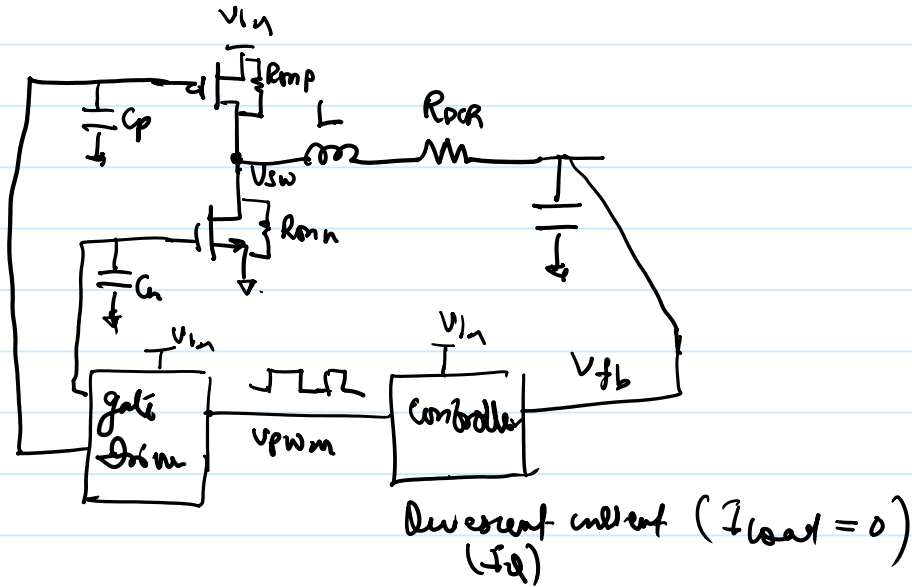

$P_{loss} =$ conduction or RMS loss or resistive loss (P_{cond}) (I^2R)

- Inductor DR losses
- switches R_{on} losses


 $+$
 Switching losses

- gate driver losses (C_{vgs})
- powerfet-switching losses
- dead time losses
- magnetic losses

 $+$
 Quiescent losses (I_Q)


$$P_{loss} = P_{cond} + P_{sw} + P_Q$$

Conduction or RMS Loss

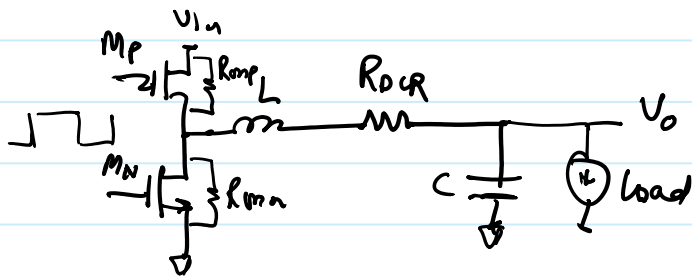

During Ton, $M_p \rightarrow ON$ & $M_n \rightarrow OFF$


$$I_{mp} = I_{load}$$

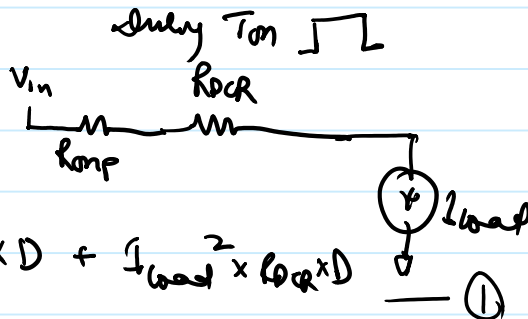

$$P_{loss-Ton} = I_{load}^2 \times R_{onp} \times D + I_{load}^2 \times R_{OD} \times D \quad \text{--- ①}$$

$P_{loss-Toff}$
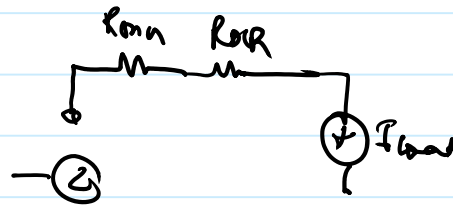
$$= I_{load}^2 \times R_{onn} (1-D) + I_{load}^2 \times R_{OD} (1-D)$$



$$P_{loss-cond} = \text{①} + \text{②}$$

$$= I_{load}^2 R_{onp} \cdot D + I_{load}^2 R_{onn} (1-D) + I_{load}^2 R_{OD}$$

$$= I_{load}^2 (D \cdot R_{onp} + (1-D) R_{onn} + R_{OD})$$

Assuming $R_{onp} = R_{onn} = R_{on}$

$$V_{loss} = I_{load} \times R_{total}$$

$$R_{total} = R_{on} + R_{OD}$$

Conduction Loss

$$V_o = D \cdot V_{in}$$

under losses

$$V_o = D \cdot V_{in} - V_{loss}$$

\Rightarrow D has to be increased to regulate \rightarrow V_o

$$R_{on} = 30 \text{ m}\Omega, R_{DCR} = 50 \text{ m}\Omega, I_{load} = 1 \text{ A}$$

$$V_{loss} = 100 \text{ mV}$$

$$V_{in} = 5 \text{ V}, V_{out} = 2.5 \text{ V}$$

$$D = 0.5$$

$$V_o = 2.5 - 0.1 = 2.4 \text{ V}$$

$$D_{new} = D + \Delta D$$

$$V_o = (D + \Delta D) V_{in} - V_{loss}$$

$$\Rightarrow V_o = D V_{in} + \Delta D \cdot V_{in} - V_{loss}$$


$$D \cdot V_{in} = V_o$$

$$\Rightarrow \boxed{V_{loss} = \Delta D \cdot V_{in}}$$

$$I_{in_new} = I_o (D + \Delta D) = \underline{I_o \cdot D} + \Delta D I_o$$

Calculating Ron and RdcR Losses

Calculating Ron & RdcR losses

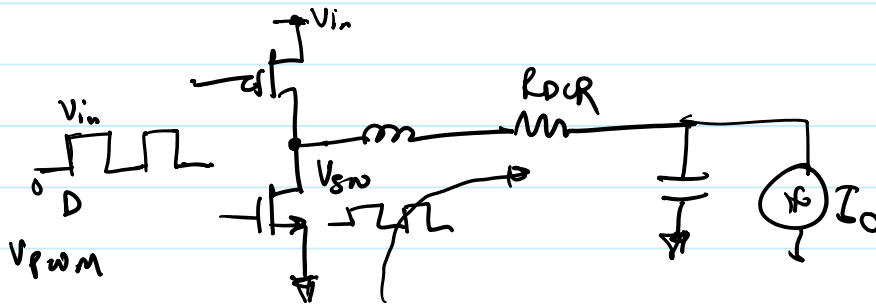


$$\text{Avg}(V_{pwm}) = D \cdot V_{in}$$

$$V_p = I_o \cdot R_{onp}$$

$$V_n = I_o \cdot R_{onn}$$

$$\text{Avg}(V_{sw})$$

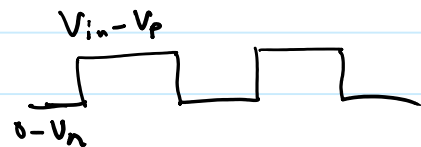

$$= D \cdot (V_{in} - V_p) + (1 - D) \cdot (-V_n)$$

$$= D \cdot V_{in} - D \cdot I_o R_{onp} - (1 - D) I_o R_{onn}$$

$$D \cdot V_{in} = \text{Avg}(V_{pwm}) \quad \text{Loss-FET}$$

$$P_{\text{loss-FET}} = \text{Avg}(V_{pwm}) - \text{Avg}(V_{sw})$$

$$P_{\text{loss-dcr}} = \text{Avg}(V_{sw}) - V_o$$