

Conduction Efficiency

$$\eta = \frac{V_o I_o}{V_{in} I_{in}} \quad \text{--- (1)}$$

$$\frac{V_o}{V_{in}} = D_{no-loss}$$

$$I_{in} = D_{load} \cdot I_o$$


substitute in (1)

$$\eta_{cond} = \frac{D_{no-loss}}{D_{load}}$$

in CCM mode

and $V_{in} \text{ at } D_{no-loss} = V_{in} \text{ at } D_{load}$


Switching Losses - Gate Drive Loss

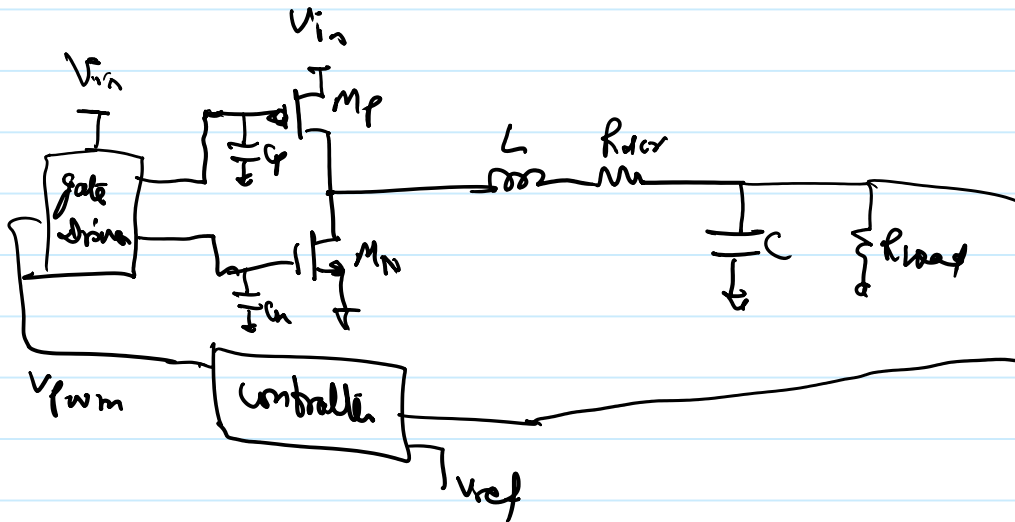


$$P_{sw-gate} = C_p V_{in}^2 F_{sw} + C_n V_{in}^2 F_{sw}$$

$$C_p + C_n = C_{gate}$$

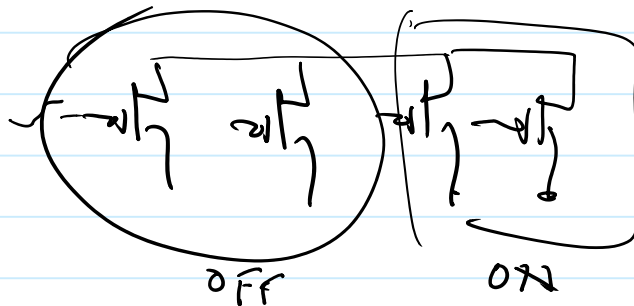
$$P_{sw-gate} = C_{gate} V_{in}^2 \cdot F_{sw}$$




Switching Losses - Dead Time Loss

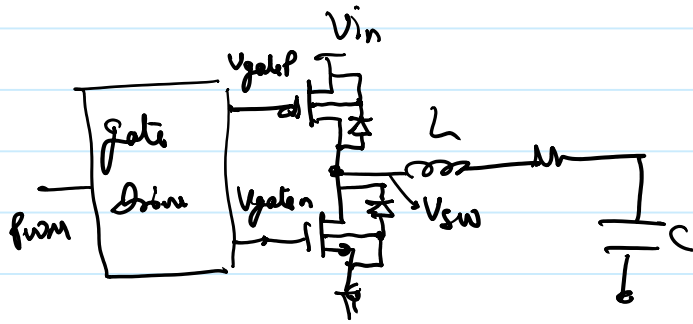

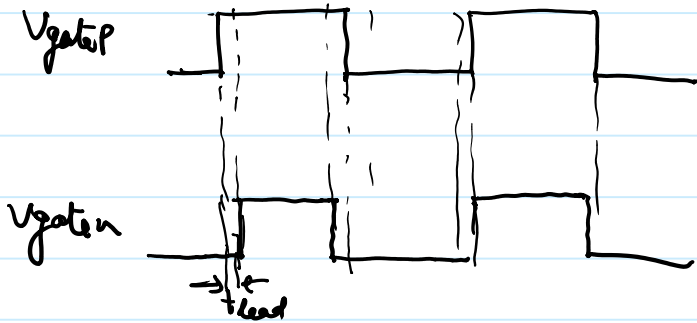non-overlap gate drive
(Break before Make)




$t_{dead} \rightarrow$ non-overlap time.

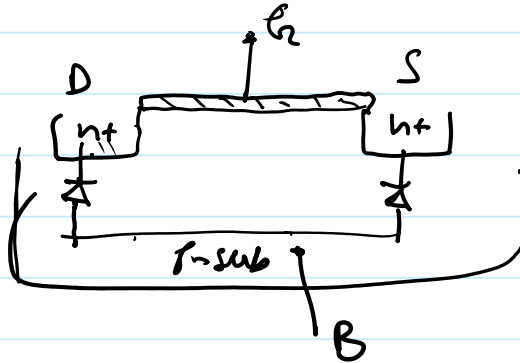

during t_{dead} current conducts through body diode of NFET.

Switching Losses - Dead Time Loss

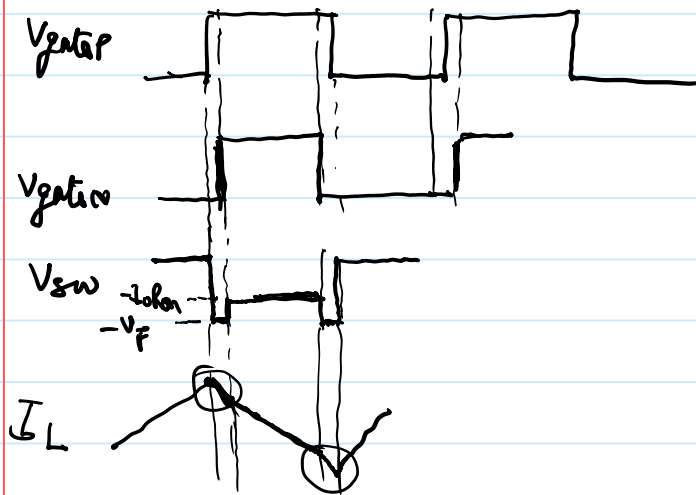

Dead time loss

$$P_{\text{dead}} = V_F \times I_0 \times \frac{t_{\text{dead}}}{T_{\text{sw}}} \times 2$$

$$P_{\text{dead}} = 2 V_F \cdot I_0 \cdot t_{\text{dead}} \times F_{\text{sw}}$$



$\frac{t_{\text{dead}}}{T_{\text{sw}}}$ should be very small for higher eff.

$$t_{\text{dead}} = 10 \text{ ns}, \quad T_{\text{sw}} = 1 \mu\text{s}$$

$$V_F = 0.7 \text{ V} \quad \& \quad I_0 = 1 \text{ A}$$

$$\frac{10 \text{ ns}}{1 \mu\text{s}} \times 0.7 \times 1 \times 2 = \frac{1.4}{100} = \boxed{14 \text{ mW}}$$

Power FETs Switching Loss

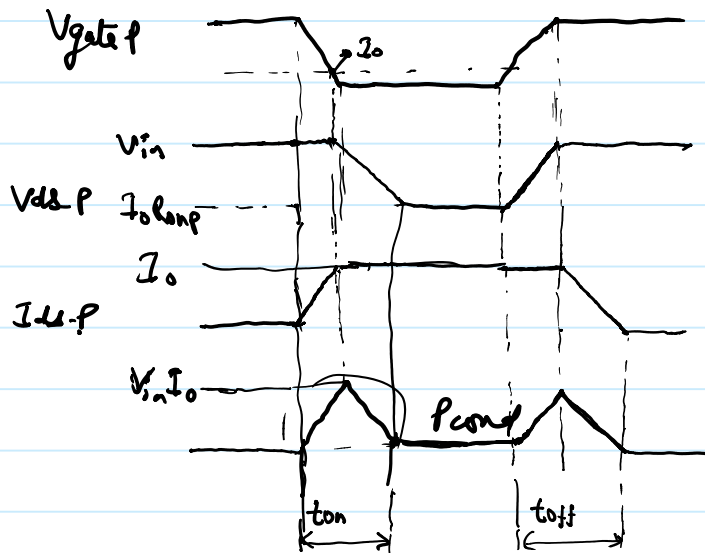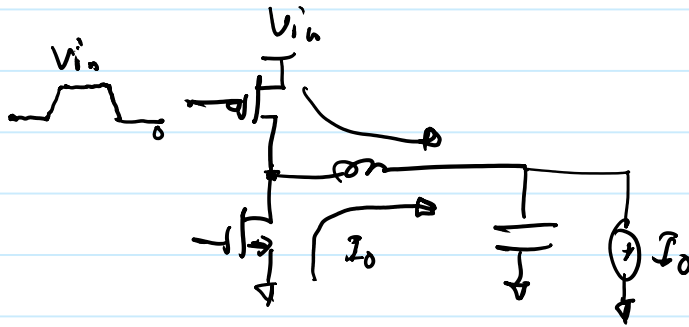

$$P_{sw_loss} = \frac{1}{2} V_{in} \cdot I_o (t_{on} + t_{off}) F_{sw}$$