



DC-DC Control Techniques

① linear └─→ voltage mode control (VMC) PWM based
└─→ current mode control (CMC)



② Non-linear └─→ Hysteretic control or bang-bang control
└─→ constant on or off time control (COT)

Voltage vs. Current Mode Control

VOLTAGE MODE

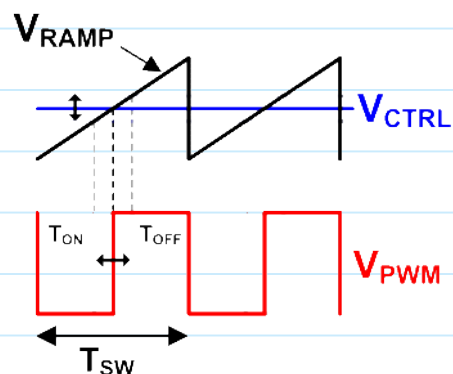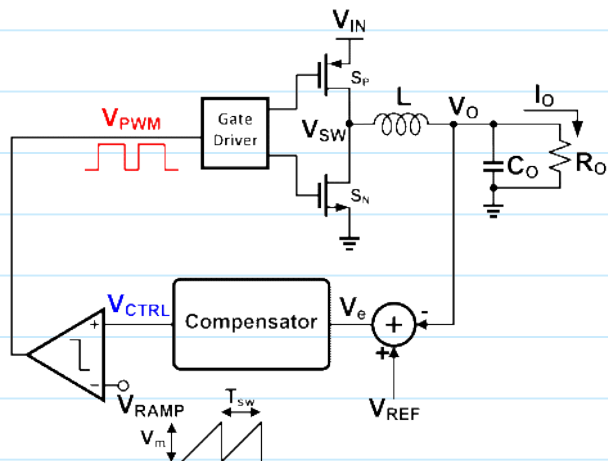

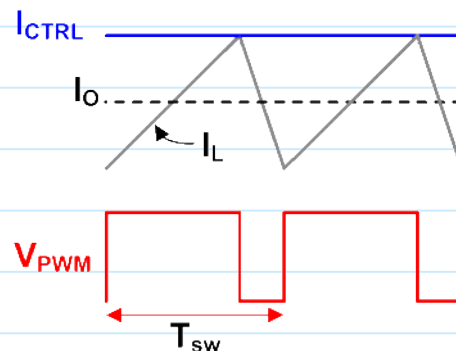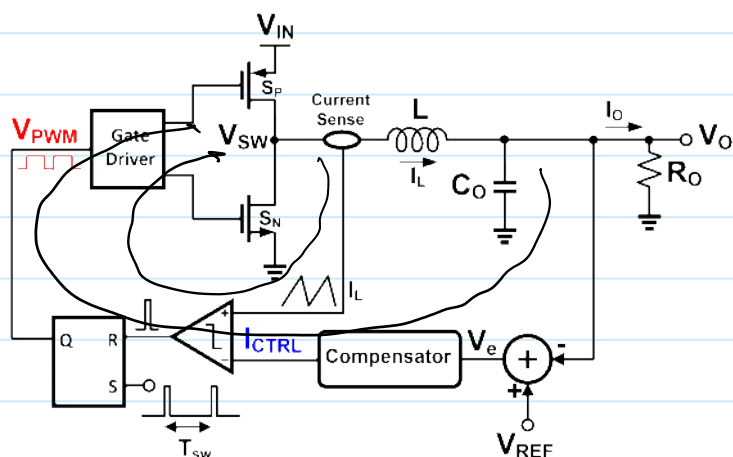- # D is controlled by voltage
- # Uses ramp signal



- # D is controlled by current
- # does not use ramp signal for PWM
- # has built-in current limiting


Sampling Delay

$$f(t) \xrightarrow{\mathcal{L}(s)} f(s)$$

$$f(t-T) \xrightarrow{\mathcal{L}(s)} e^{-sT} f(s)$$

$$|e^{-sT}| = 1$$

$$\angle e^{-sT} = -\omega T$$

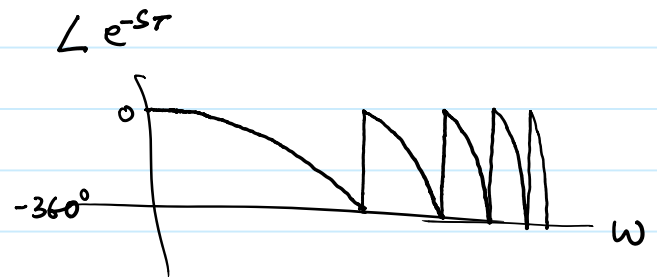

$$T = T_{sw}$$

$$\phi_{mo} = PM \text{ w/o delay } T_{sw}$$

$$\phi_{md} = PM \text{ with delay}$$

$$\phi_{md} = \phi_{mo} - \omega T_{sw}$$

$$\phi = -2\pi \text{ at } \omega = \frac{2\pi}{T_{sw}} = 2\pi f_{sw}$$

Phase wraps to 0 if $\omega = N \cdot 2\pi f_{sw}$
($N = 1, 2, 3, \dots$)

$$T_{sw} = \frac{1}{f_{sw}}$$

$$\phi_{md} = \phi_{mo} - \frac{2\pi f}{f_{sw}}$$

$$\text{assume } f = \frac{1}{10} f_{sw}$$

$$= \phi_{mo} - \frac{180}{5} = \phi_{mo} - 36^\circ$$

delay in PWM (trailing edge)

$$T_d = (1-D)T_{sw}$$

Sampling Delay

using Taylor series with 1st order approximation

$$e^{-sT} = 1 - sT \quad - (1) \Rightarrow \text{R.H.P. Zero}$$

$$\text{or } \frac{1}{1+sT} \quad - (2) \Rightarrow \text{L.H.P. pole}$$

magnitude $\neq 1$


$$e^{-sT} = e^{-sT/2} \times e^{-sT/2}$$

$$= \frac{\frac{2}{T} - s}{\frac{2}{T} + s} \quad - (3) \Rightarrow \text{R.H.P. Zero \& L.H.P. pole}$$


magnitude = 1 & phase same as (1) & (2)

(1), (2) & (3) work well only for $\frac{f}{f_{sw}} \ll 1$

Continuous Time Model

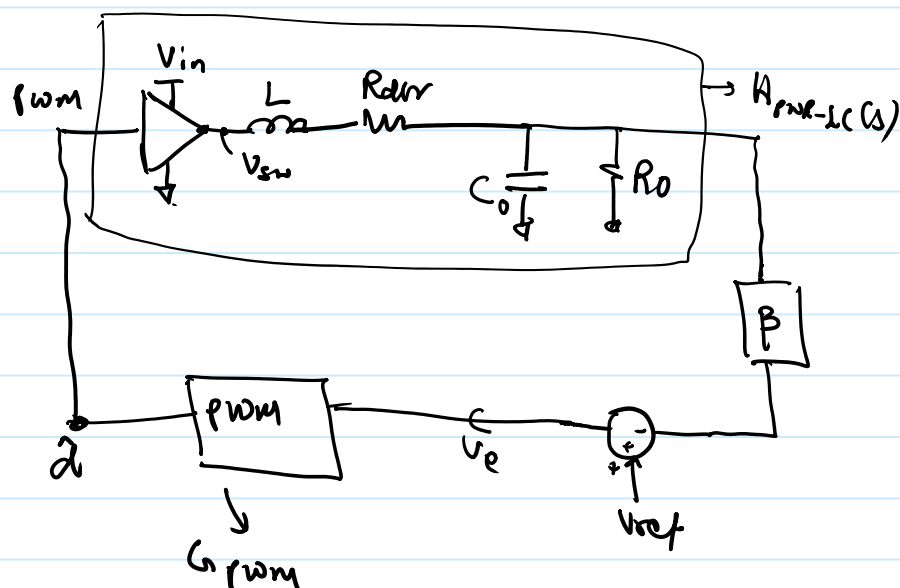

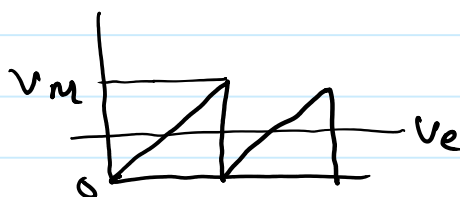
$$G_{pwm} = \frac{\partial \hat{d}}{\partial V_e} = \frac{1}{V_m}$$



$$V_o = \frac{D V_{in} \left(\frac{1}{L C_o} \right)}{s^2 + \left(\frac{1}{R_o C_o} + \frac{R_{drv}}{L} \right) s + \frac{1}{L C_o}}$$

$$\frac{\partial V_o}{\partial \hat{d}} = V_{in} \left[\frac{\frac{1}{L C_o}}{s^2 + \frac{\omega_o}{Q_s} s + \frac{1}{L C_o}} \right]$$


Loop Gain of Un-Compensated Buck

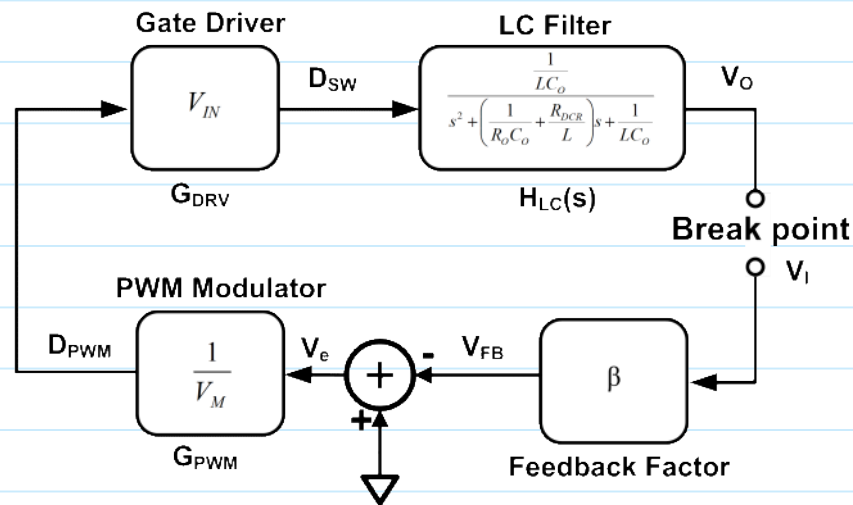


$$LG_u(s) = -\frac{R_2}{R_1 + R_2} \cdot \frac{V_{IN}}{V_M} \cdot \frac{1}{s^2 + \left(\frac{1}{R_O C_O} + \frac{R_{DCR}}{L} \right) s + \frac{1}{LC_O}}$$

$$f_o = \frac{1}{2\pi\sqrt{LC_O}}$$
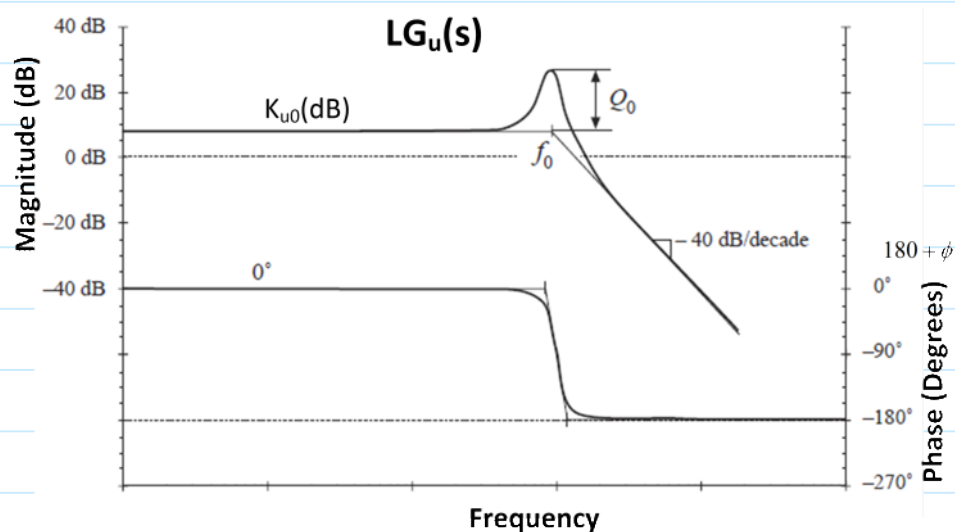
$$K_{u0} = \frac{R_2}{R_1 + R_2} \cdot \frac{V_{IN}}{V_M}$$




Compensation

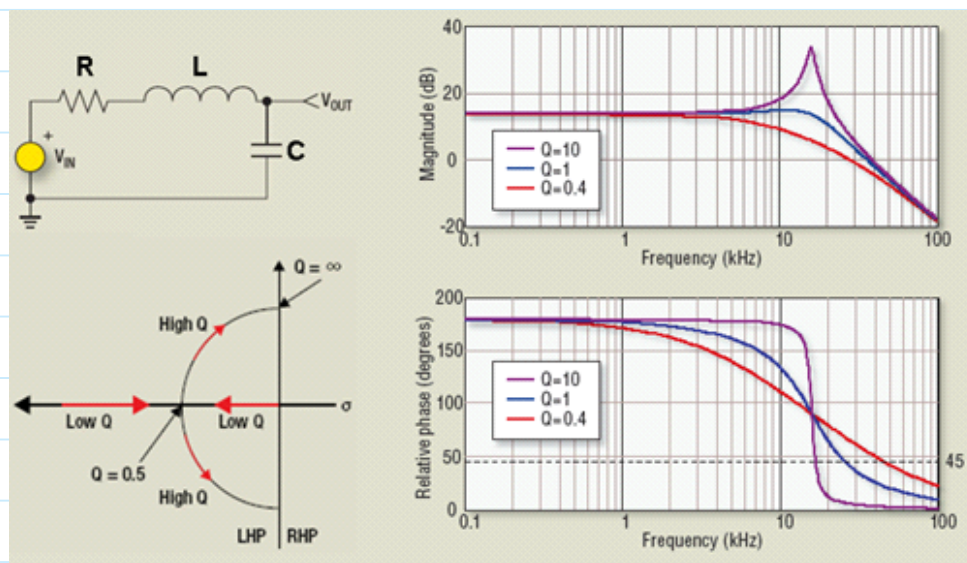

complex poles due to LC filter may cause $90^\circ - 180^\circ$ phase shift around f_0 (resonance freq.) and making system unstable.

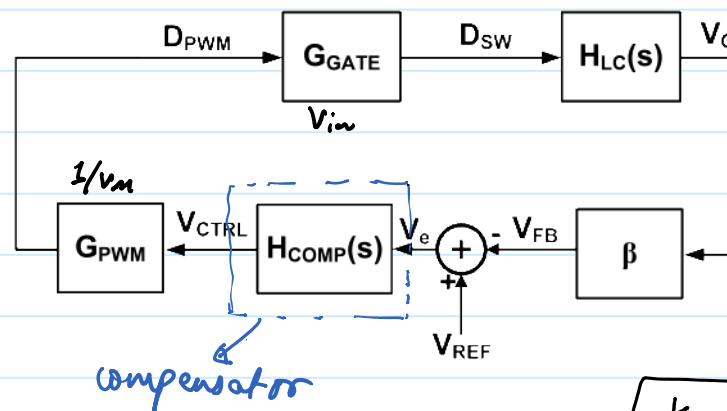we need a compensator to stabilize the loop.



Loop Gain Y.F.

$$K_{uo} = \beta \frac{V_{in}}{V_m}$$

$$L_G(s) = K_{uo} \cdot H_{comp}(s) \cdot H_{LC}(s)$$

Compensation - Cancelling Complex Poles


$H_{comp}(s) \rightarrow$ T.F. of the compensator
if we design

$$H_{comp}(s) = \frac{1}{H_{LC}(s)} \times \frac{K_i}{s}$$

complex poles due to LC are perfectly cancelled
Integrator $\frac{K_i}{s}$ is needed for high
DC gain (good regulation) and to control BW.

Loop gain T.F. after compensation

$$LG(s) = K_{uo} \frac{K_i}{s}$$

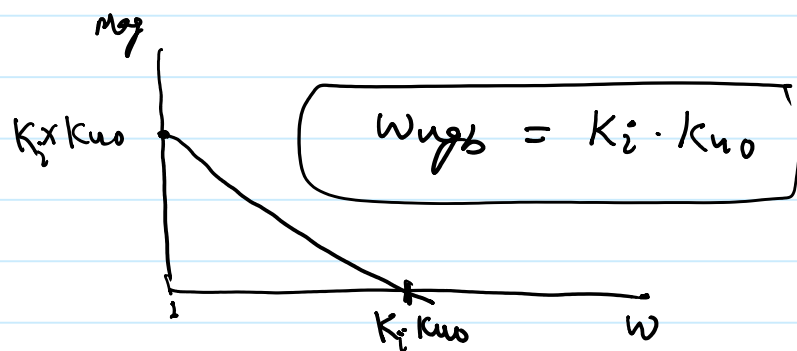

Provides an ideal compensation but not practical
to realize as compensation zeroes can't be
exactly placed at ω due to variation in parameters
and component across varying operating conditions.
Hence this type of compensation is not used.


Type-I Compensation

Also called Integral compensation

$$H_{comp}(s) = \frac{K_i}{s}$$

$$L_G(s) = K_{uo} \cdot \frac{K_i}{s} H_{LC}(s)$$

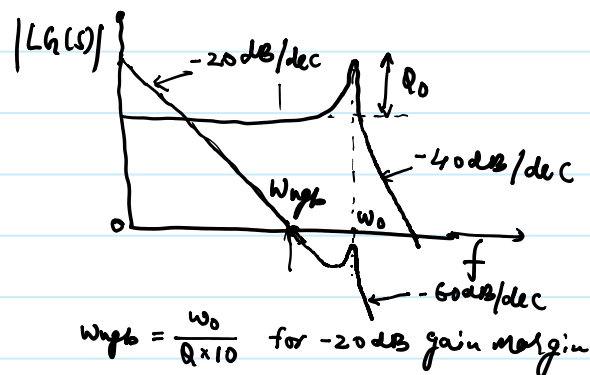If $K_{uo} \cdot K_i \ll \omega_0$ then complex poles are pushed outside ω_{gh}
Peaking due to high Q_0 should be taken into account for enough gain margin.



assume $Q = 10$

$$\omega_{gh} = \frac{\omega_0}{10} \Rightarrow \text{very low B.W.}$$

Type-I compensation is mainly used if B.W. is not a concern.

+ Transient response is poor due to low B.W. hence can't be used for fast changing load currents or line voltages.