


Variation in Loop Gain

$$k_{uo} = \beta \frac{V_{in}}{V_m}$$

Loop gain varies with V_{in} if β & V_m are constant.

Make V_m a function of V_{in} to keep V_{in}/V_m constant
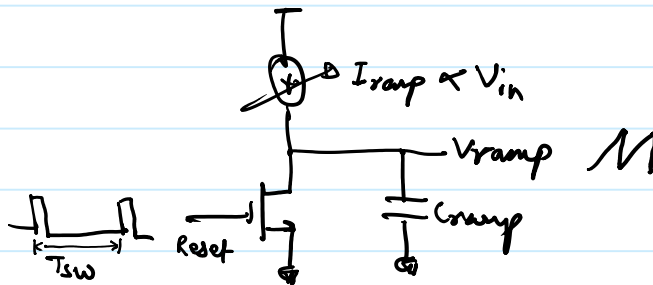
$$V_m \propto V_{in} \Rightarrow V_m = K V_{in} \text{ (feed-forward compensation)}$$



$V_m \propto V_{in} \rightarrow k_{uo}$ remains constant
& line transient is improved.

Variation in Loop Gain

Variation in k_{uo} due to β can be cancelled by programming V_o directly through V_{ref} instead of changing feedback factor (β).


$$k_{uo} = \frac{V_{ref}}{V_o} \times \frac{V_{in}}{V_m} \quad \beta = \frac{V_{ref}}{V_o}$$

However, if V_{ref} is constant then above equation can be written as:




$$k_{uo} = \frac{V_{ref}}{V_m} \cdot \frac{1}{D} \quad \left(\frac{V_{in}}{V_o} = \frac{1}{D} \right)$$

we can cancel variation in loop gain due to β and V_{in} by making the gain proportional to D while keeping V_{ref} and V_m constant.

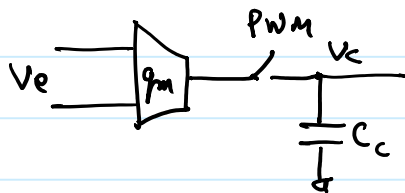Following example shows how integrator gain in type-I converter can be made constant by modulating g_m with PWM.


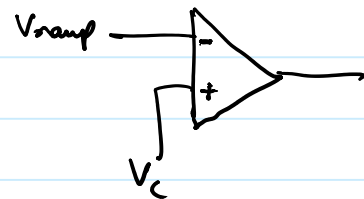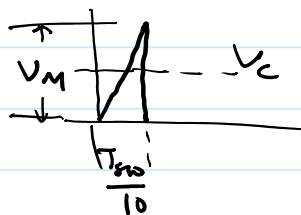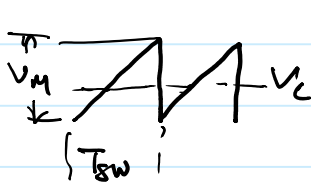
$$\frac{V_c(s)}{V_e(s)} = \frac{g_m}{C_c s} \cdot D$$



same duty cycle (we can switch g_m at higher frequency to reduce ripple in V_c)
at $10 \times f_{sw}$

Type-III Compensation

Also called PID (Proportional - Integral - Derivative)

$$\text{type-II} = \text{type-I} + \text{Prop.}$$

$$\text{type-III} = \text{type-II} + \text{deriv}$$

$$H_{\text{comp}}(s) = \left(k_p + \frac{k_i}{s}\right) \left(1 + s/\omega_{z2}\right)$$
$$= \frac{k_i}{s} \left(1 + \frac{k_p}{k_i} s\right) \left(1 + s/\omega_{z2}\right)$$
$$\omega_{z1} = \frac{k_i}{k_p}$$

$$\equiv k_p + \frac{k_p}{\omega_{z2}} s + \frac{k_i}{s} + \frac{k_i}{\omega_{z2}}$$
$$= \underbrace{\left(k_p + \frac{k_i}{\omega_{z2}}\right)}_P + \underbrace{\frac{k_i}{s}}_I + \underbrace{\frac{k_p}{\omega_{z2}} s}_D$$

$$k_p' = k_p \left(1 + \frac{\omega_{z1}}{\omega_{z2}}\right)$$
$$k_p' = k_p \text{ if } \omega_{z1} \ll \omega_{z2}$$



Rules of PID Compensation


Rule-1

$$\omega_{ngb} > \omega_0$$



$$\omega_0 = \omega_{ngb}$$

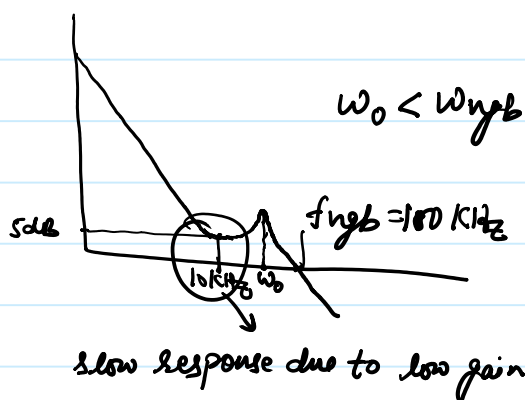gain also crosses at $w < w_0$
due to high Q



$$\omega_0 < \omega_{ngb}$$

ω_0 should be significantly
lower than ω_{ngb} to ensure
enough gain in mid-band
(between ω_z , and ω_0).

Keeping ω_0 closer to ω_{ngb} reduces
mid-band gain and degrades the
transient response.

Rules of PID Compensation

Rule-2

$$\omega_{z_1} < \omega_0$$

phase lag due to integrator must be cancelled before ω_0 to ensure stability.

ω_{z_1} controls ω_{ngb}

Rule-3


ω_{z_2} should be placed around ω_0 based on Q

high $Q \rightarrow \omega_{z_2} \leq \omega_0$

low $Q \rightarrow \omega_{z_2} \geq \omega_0$

ω_{z_2} controls phase margin

Implementing Type-III Compensator

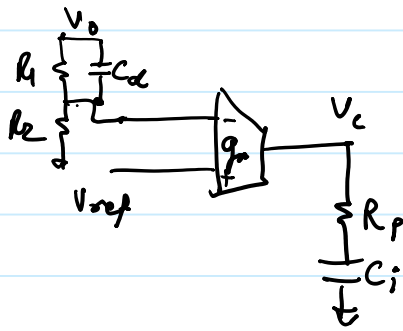


$$H_{comp}(s) = -\beta \frac{(1 + R_1 C_d s)}{(1 + \beta R_1 C_d s)} \left(g_m R_p + \frac{g_m}{C_i s} \right)$$

$$= -\beta \frac{g_m}{C_i s} \frac{(1 + R_1 C_d s)(1 + R_p C_i s)}{(1 + \beta R_1 C_d s)}$$

$$\omega_{z_1} = \frac{1}{R_p C_i}, \quad \omega_{z_2} = \frac{1}{R_1 C_d}, \quad \omega_p = \frac{1}{\beta R_1 C_d}$$

ω_{z_2} and ω_p are close to each other for $\beta \approx 1$.
hence only works if $\beta \ll 1$ which is quite
unusual as V_{ref} is usually 0.6 to 1.2V.

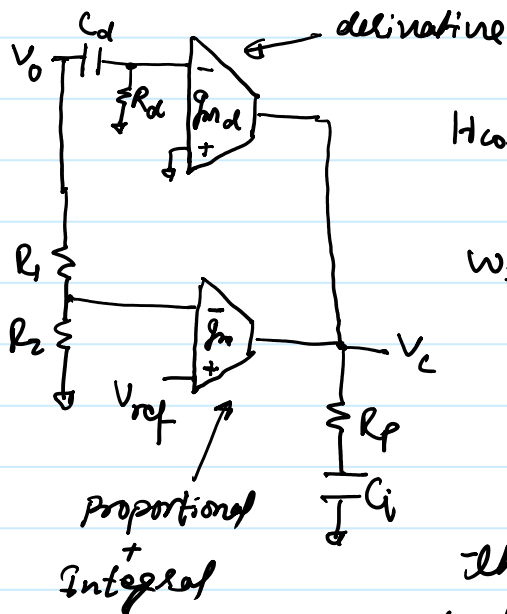derivative portion can be implemented using another g_m .




$$H_{comp}(s) = -\beta R_p \frac{g_m}{C_i} \frac{(1 + s/\omega_{z_1})(1 + s/\omega_{z_2})}{s(1 + s/\omega_p)}$$

$$\omega_{z_1} = \frac{1}{R_p C_i}; \quad \omega_{z_2} = \frac{1}{R_d C_d} \beta \frac{g_m}{g_{md}}$$

$$\omega_p = \frac{1}{R_d C_d}$$

if $R_d C_d$ is chosen low enough such
that $\omega_p \gg \omega_{ngb}$ then ω_{z_2} can be
controlled by g_m/g_{md} ratio.

Implementing Type-III Compensator

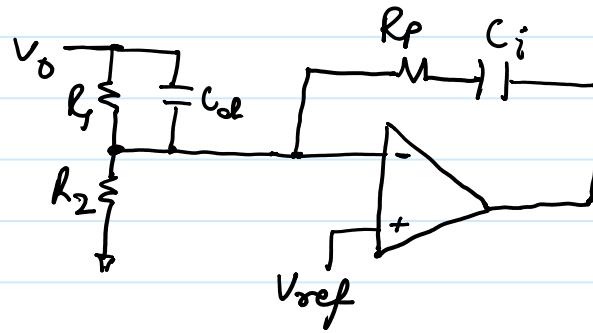

$$H_{comp}(s) = -Z_2 \times Y_1$$

$$-\left(R_p + \frac{1}{sC_i}\right) \left(\frac{1}{R_1} + sC_d\right)$$

$$= -\frac{1}{R_1 C_i s} (1 + R_p C_i s) (1 + R_1 C_d s)$$

$$\omega_{z_1} = \frac{1}{R_p C_i} \quad ; \quad \omega_{z_2} = \frac{1}{R_1 C_d}$$