
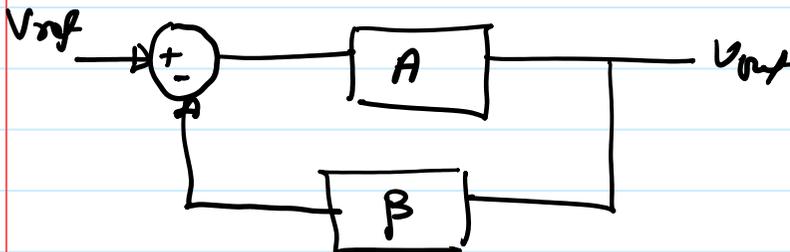


## Regulator's Performance Parameters

1. Voltage Accuracy
2. Efficiency ( $\eta$ )
3. Quiescent Current ( $I_Q$ )
4. Line Regulation
5. Load Regulation
6. Transient Performance
  - a) Load Transient
  - b) Line Transient
  - c) Settling Time
7. Output Ripple

# Voltage Accuracy/DC Regulation

→ Error in the output Voltage

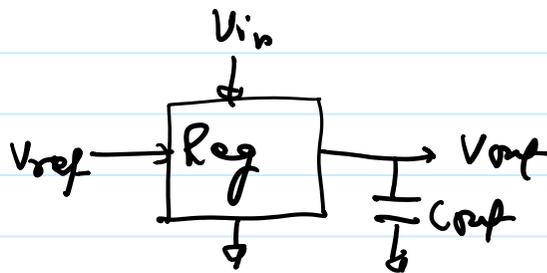

$$H = \frac{A}{1 + A\beta}$$

Assume  $\beta = 1$

$$H = \frac{A}{1 + A} \quad A \rightarrow \infty$$

$$H \approx 1$$

$$V_{out} = V_{ref}$$

Practically  $A \rightarrow 100 \rightarrow 1000$   
 $40\text{dB} \rightarrow 60\text{dB}$

$$A = 100$$

$$\Delta V_{out} (\text{error}) \rightarrow 1\%$$

$$A = 1000$$

$$\Delta V_{out} \rightarrow 0.1\%$$




## Voltage Accuracy/DC Regulation (Contd.)

$V_{out} \propto V_{ref}$

Any error in  $V_{ref}$  is directly reflected at  $V_{out}$

offset

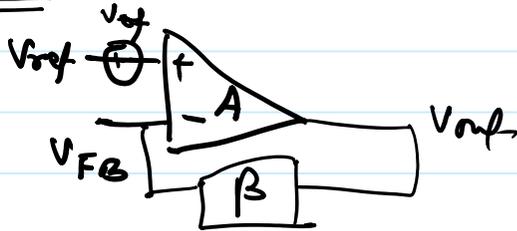

$$V_{out} = V_{ref} \pm V_{og}$$

- Gain
- $V_{ref}$
- offset

## Power Conversion Efficiency

$$\eta = \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{out} + P_{loss}}$$

$$\eta < 1 \text{ or } 100\%$$

$$\frac{P_{in} - P_{loss}}{P_{in}}$$

## Quiescent Current


Internal current

⇒ Regulator's current consumption  
at no load

⇒ minimize  $I_Q$

at no load

$$P_{out} = 0$$

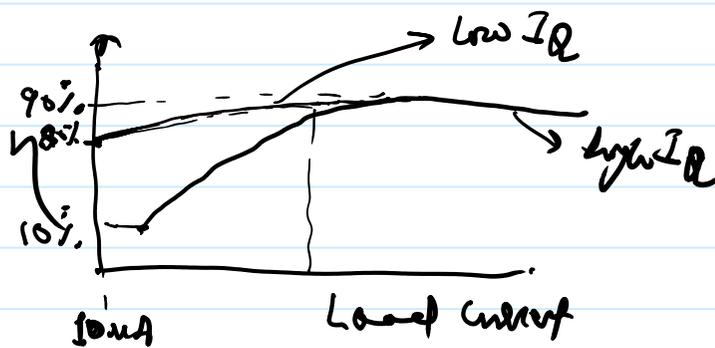

## Line Regulation

Line  $\rightarrow$  Input supply ( $V_{in}$ )

$$\Delta V_{out\_line} = \frac{\Delta V_{out}}{\Delta V_{in}}$$
$$= \frac{V_{out\_max} - V_{out\_min}}{V_{in\_max} - V_{in\_min}}$$

$$\Rightarrow \% \Delta V_{out} / V \text{ unit}$$

$$\approx \Delta V_{out} / V$$

# Load Regulation

$$\Delta V_{\text{ref-load}} = \frac{\Delta V_{\text{ref}}}{\Delta I_{\text{load}}}$$



# Transient Response

## Line Transient

$$\Delta V_{out, \text{line-tran}} = \frac{\Delta V_{out}}{\Delta V_{in}(\text{step})}$$

