

---

# ***Lecture-32***


## ***EE5325 Power Management Integrated Circuits***

**Dr. Qadeer Ahmad Khan**

**Integrated Circuits and Systems Group  
Department of Electrical Engineering  
IIT Madras**



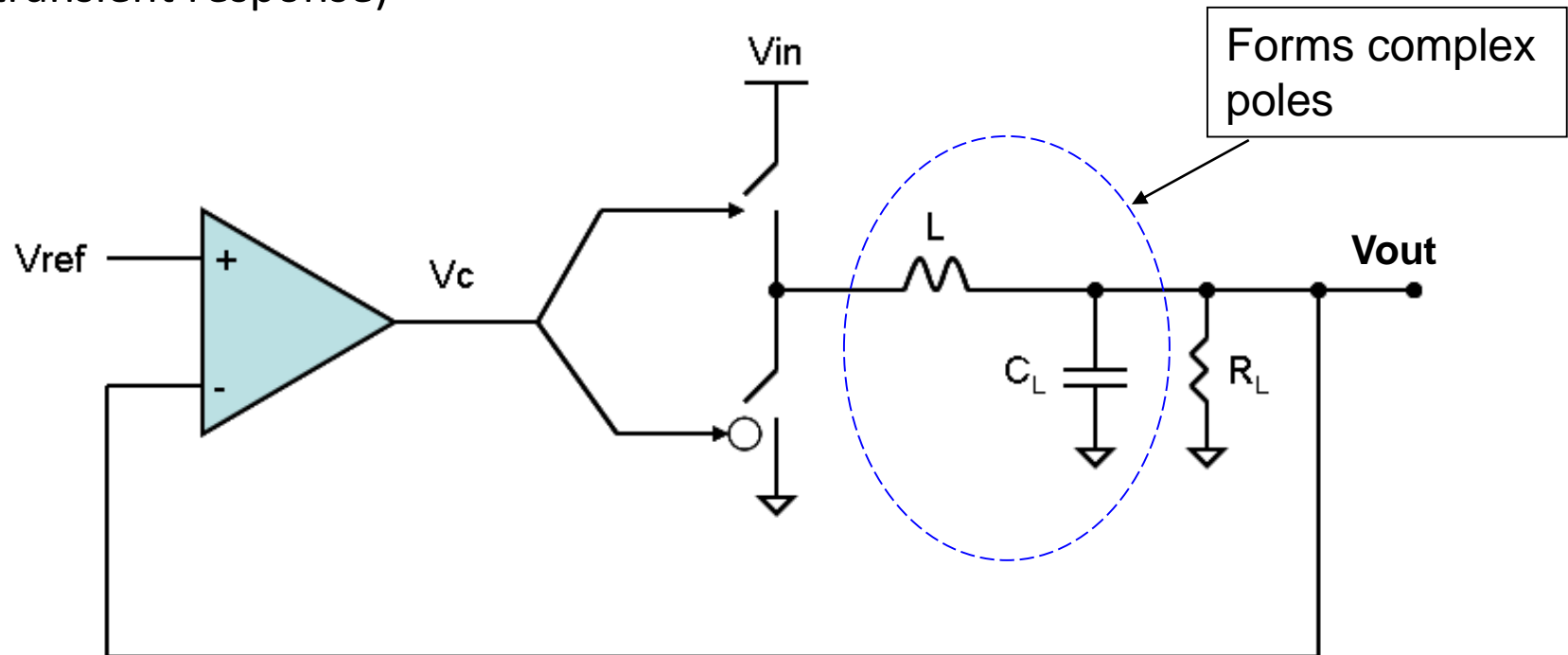
# Voltage Mode Control

- Switch duty cycle controlled by the error voltage between output and reference
- L and C forms a pair of complex poles which makes the system inherently unstable
- Requires complex PID compensation to achieve high loop BW (good transient response)


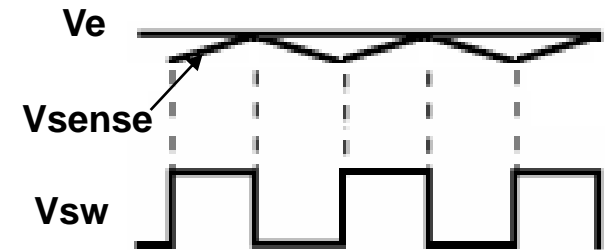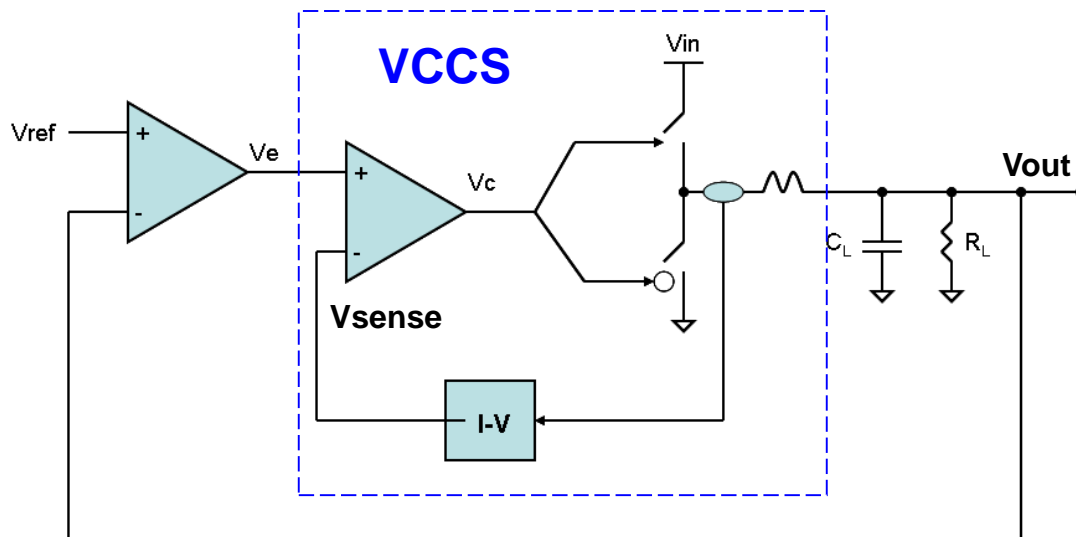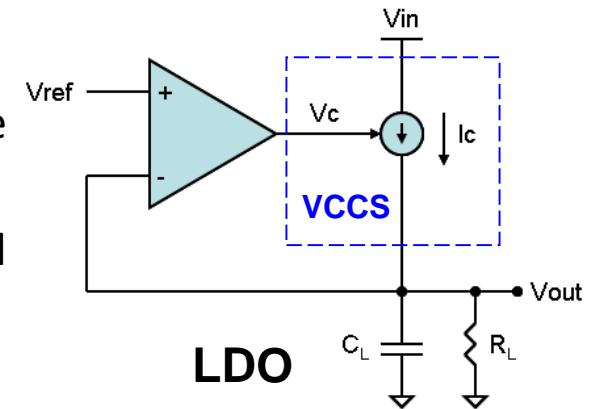
# Current Mode Control


- Uses concept of LDO Regulator where output voltage is by controlling the output current using VCVS
- In case of LDO, pass transistor acts as a lossy VCCS hence exhibits poor efficiency
- In case of current controlled dc-dc, Inductor is converted into a lossless VCCS



## Current Mode Controlled DC-DC
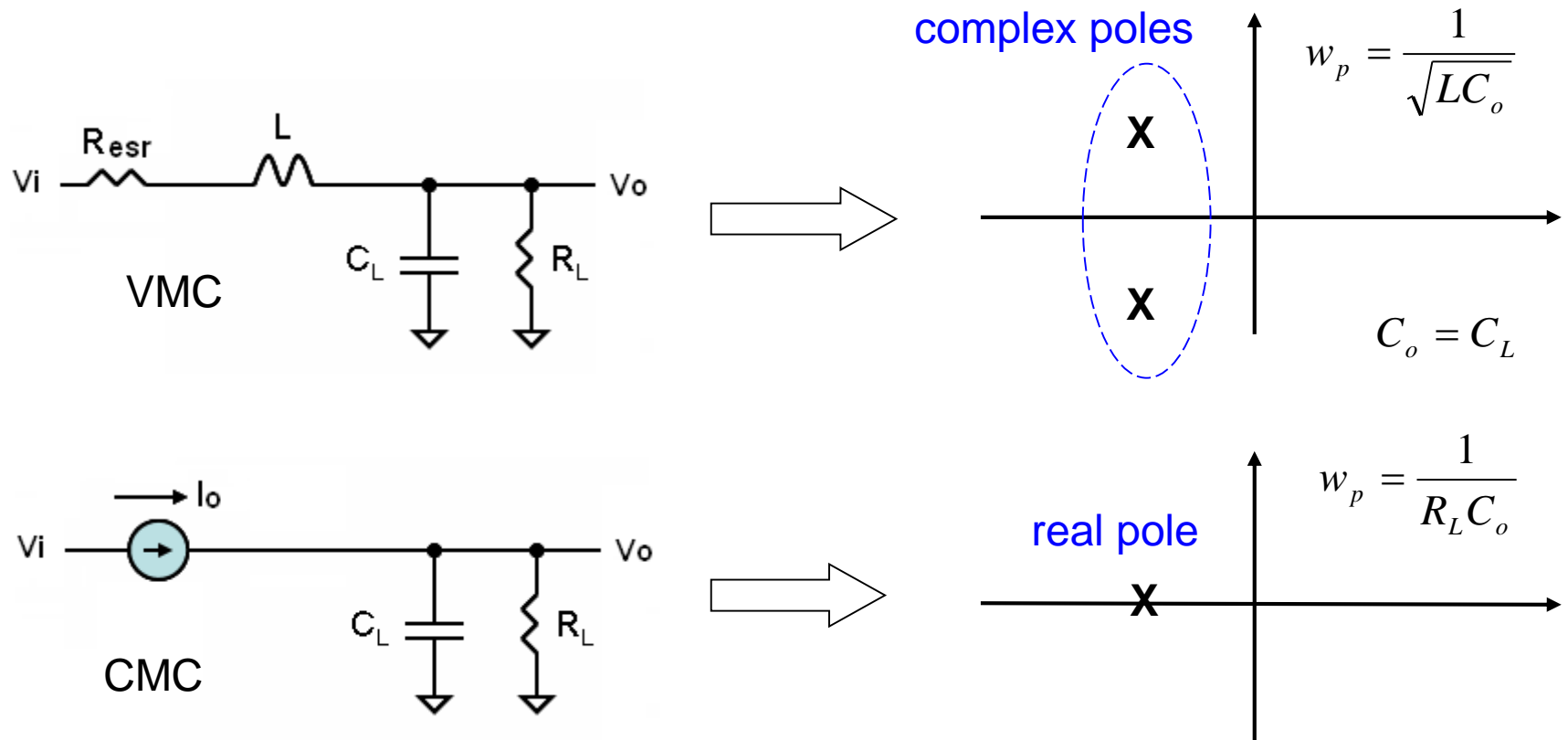
# Complex – Real Pole Transformation


- Unlike the Voltage Mode controlled, the complex poles due to L & C is converted into real pole because of the inner current loop



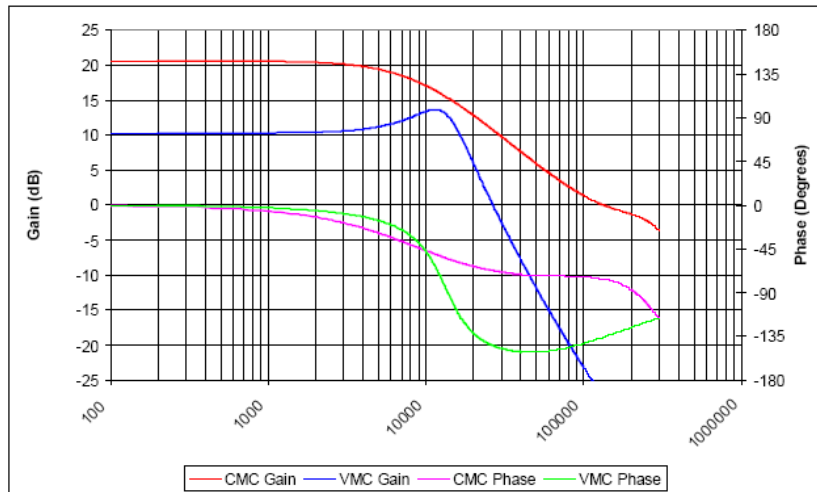
# VMC vs CMC Frequency Response

- Phase and Magnitude roll-off in CMC is not as steep as in VCM
  - Smoother frequency response
- It becomes easier to stabilize the loop due to single pole
  - Only PI (type-II) compensation is required

Brian Lynch, "Current mode vs. voltage mode control in synchronous buck converter", Texas Instruments



Before compensation

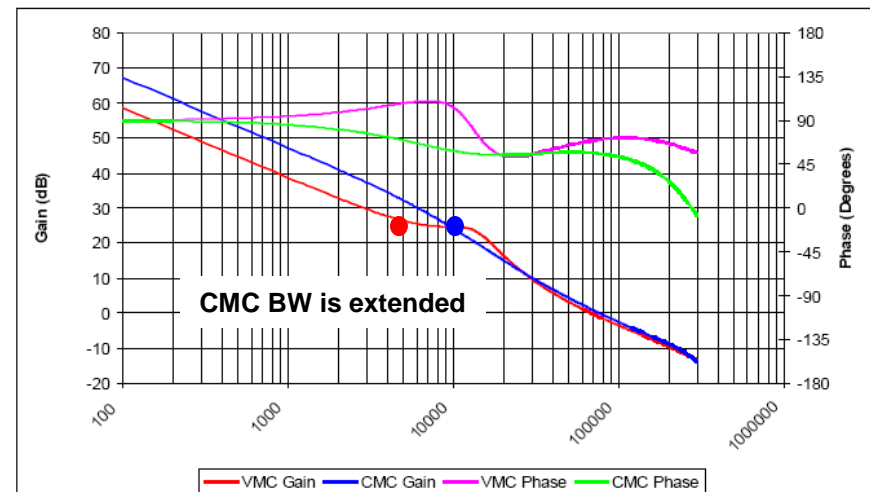

After compensation


# Current Mode Control Techniques

---

- **Peak Current Mode Control**
  - Peak Current (high side) is used to control the duty cycle
  
- **Valley Current Mode Control**
  - Valley current (low side) is used to control the duty cycle
  
- **Emulated Current Mode Control**
  - Both peak and valley currents are used to control the duty cycle
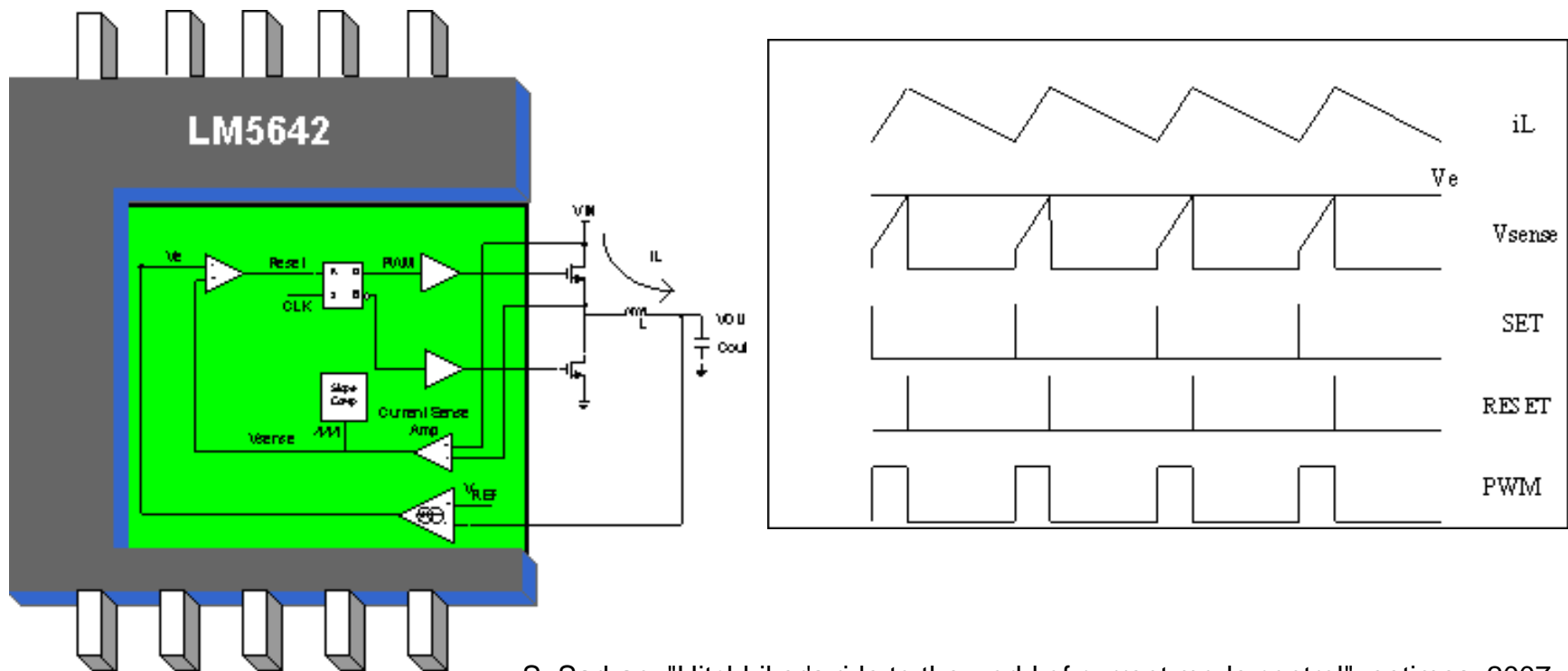
# Peak Current Mode controlled



- Senses the peak inductor current information when the power switch is on, then uses it to turn off the switch → trailing edge PWM
- Suffers from sub-harmonic oscillation at duty cycles higher than 50%
- Easy to operate at higher duty cycle but difficult at lower duty cycle



S. Sarhan, "Hitchhiker's ride to the world of current mode control", eetimes, 2007
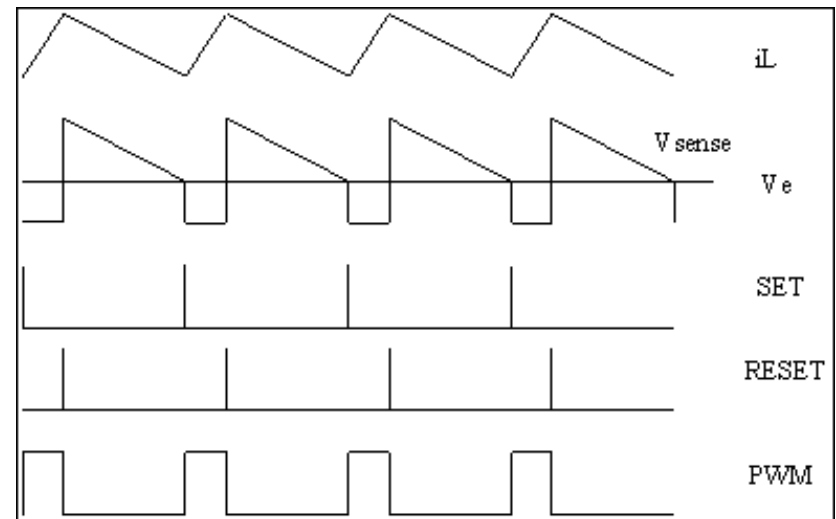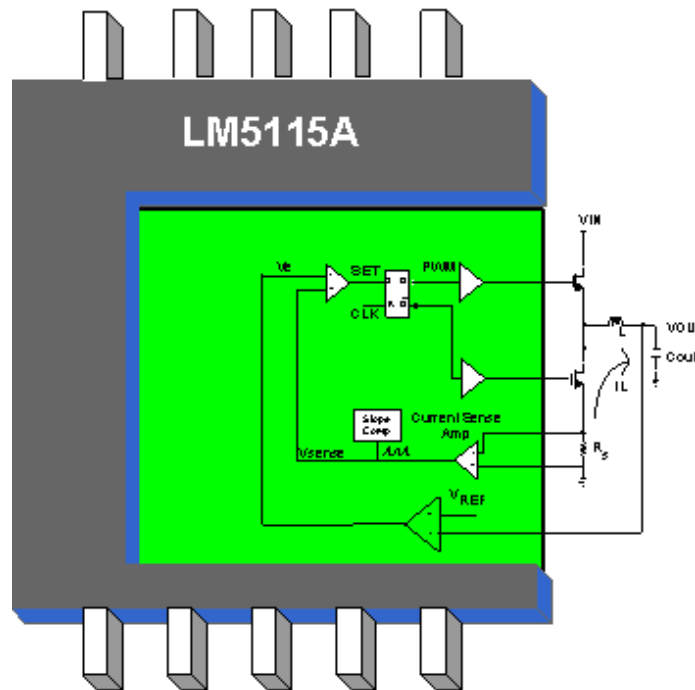
# Valley Current Mode controlled

- Senses the valley inductor current information when the power switch is off, then uses it to turn on the switch → leading edge PWM
- Contrary to Peak CMC, it suffers from sub-harmonic oscillation at duty cycles lower than 50%
- Easy to operate at lower duty cycle but difficult at higher duty cycle





S. Sarhan, "Hitchhiker's ride to the world of current mode control", eetimes, 2007


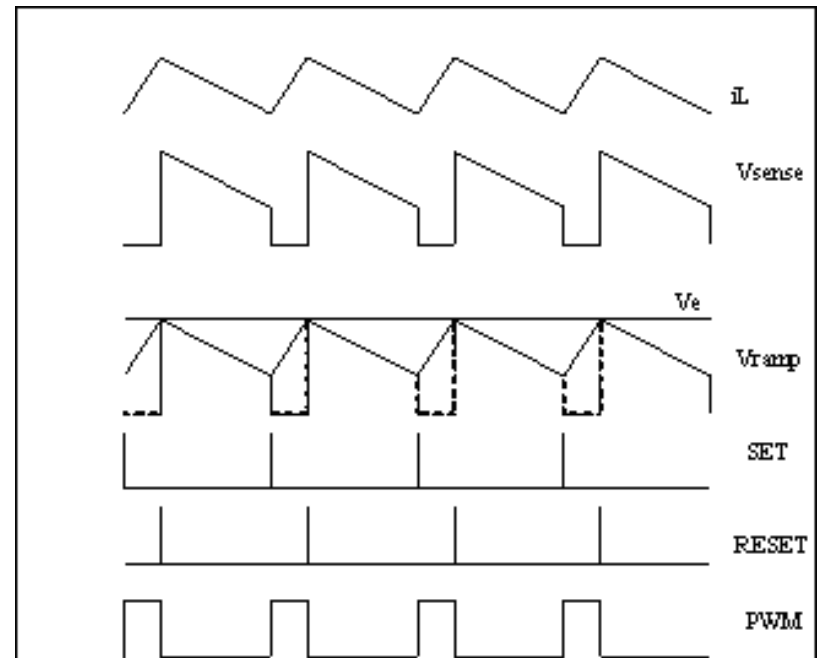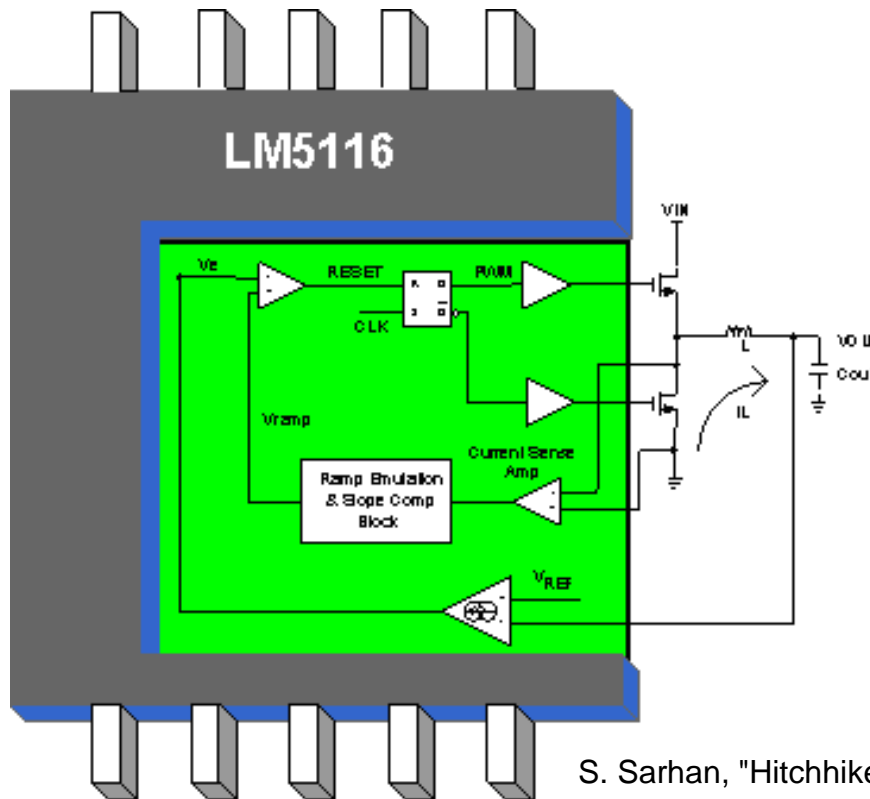
# Emulated Current Mode controlled

- Uses valley current sensing to predict the peak current in order to emulate exact inductor current waveform
- Combines the advantages of valley CMC (low duty cycle operation) and peak CMC (good line transient)



S. Sarhan, "Hitchhiker's ride to the world of current mode control", eetimes, 2007

# Voltage Mode Control (VMC) vs. Current Mode Control (CMC)

Parameter	VMC	CMC
Line transient	Good with line feedforward $(V_M \propto V_{IN})$	Good (inherent line feedforward in peak current mode) Bad in valley CMC
Load transient	Good (bandwidth is independent of load current in CCM)	Good at high BW but degrade at lower load current BW is dependent on load current)
Very low duty cycle operation	Good	Poor
Noise insensitivity	Good	Poor
Simplicity of compensation	Poor	Good