

Hysteretic DC-DC Converter

condition for stability of hysteretic dc-dc. conv.

$$R_{\text{esr}} \cdot C_0 > \frac{T_{\text{on}}}{2} \text{ or } \frac{T_{\text{off}}}{2} \text{ whichever is greater}$$

$\Rightarrow$ for duty cycle $> 50\%$.

$$R_{\text{esr}} \cdot C_0 > T_{\text{on}}/2$$

for $D < 50\%$.



$$R_{\text{esr}} C_0 > T_{\text{off}}/2$$

$\Rightarrow R_{\text{esr}} C_0 > T_{\text{sw}}/2$ satisfies all D .


$$\begin{aligned} \Delta I_L &= \frac{V_{\text{in}} - V_0}{L} \times \frac{D}{F_{\text{sw}}} \\ &= \frac{V_{\text{in}} D (1-D)}{L \times F_{\text{sw}}} \Rightarrow F_{\text{sw}} = \frac{V_{\text{in}} D (1-D)}{L \times \Delta I_L} \end{aligned}$$

$$\Delta I_L = \frac{\Delta V_H}{R_{\text{esr}}}$$
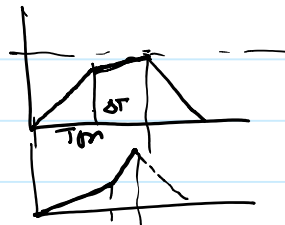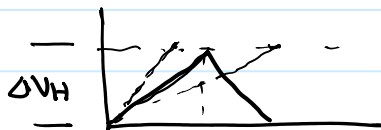
$$F_{\text{sw}} = \frac{V_{\text{in}} D (1-D)}{L \cdot \Delta V_H} R_{\text{esr}}$$



Resetting C of RC filter

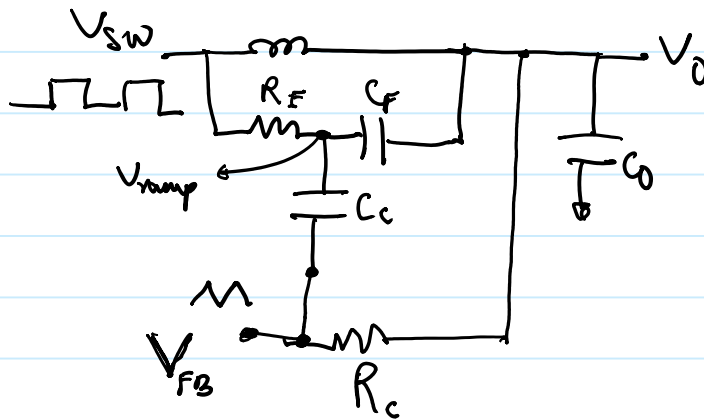

$$V_{FB} \Rightarrow V_o(dc) + V_{ramp}(ac)$$

$C_c \rightarrow$ needed to extract only ac component of V_{ramp}

C_c can be eliminated by resetting V_{ramp} to V_o at rising and falling edges of PWM or V_{sw}

