

---

# ***Lecture-36***

## ***EE5325 Power Management Integrated Circuits***

**Dr. Qadeer Ahmad Khan**

**Integrated Circuits and Systems Group  
Department of Electrical Engineering  
IIT Madras**


---

# ***Buck-Boost Converter***

# Types of DC-DC converter


**BUCK:**  $\frac{V_{out}}{V_{in}} < 1$

$V_{out} = D V_{in}, I_L = I_o$

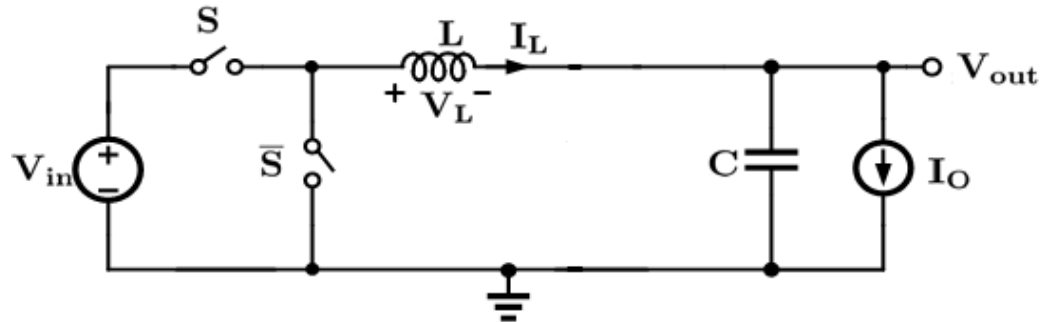

**BOOST:**  $\frac{V_{out}}{V_{in}} > 1$

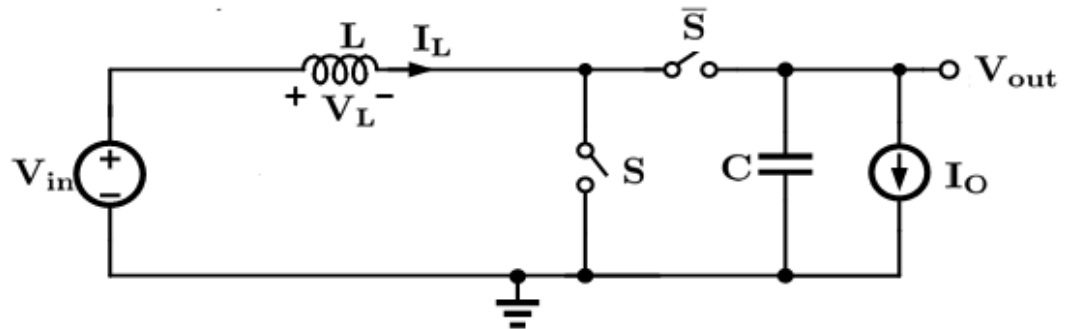
$V_{out} = \frac{1}{1-D} V_{in}, I_L = \frac{1}{1-D} I_o$



**BUCK-BOOST:**  $\frac{V_{out}}{V_{in}} \approx 1$


$V_{out} = \frac{D}{1-D} V_{in}, I_L = \frac{1}{1-D} I_o$

Also works as buck only or boost only

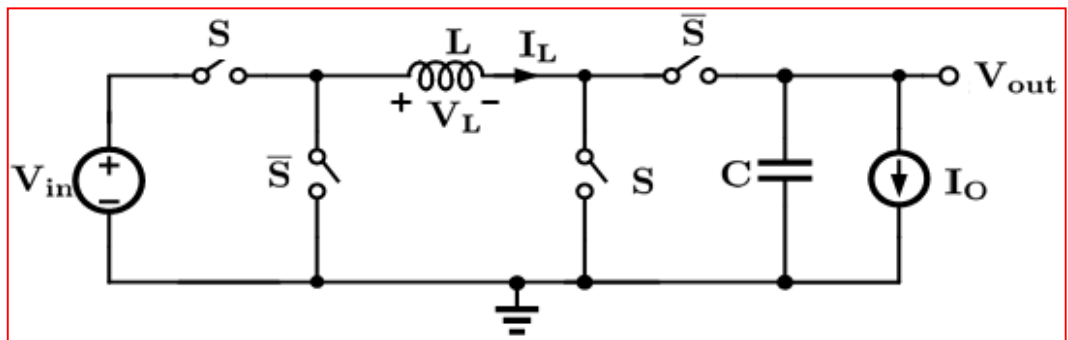

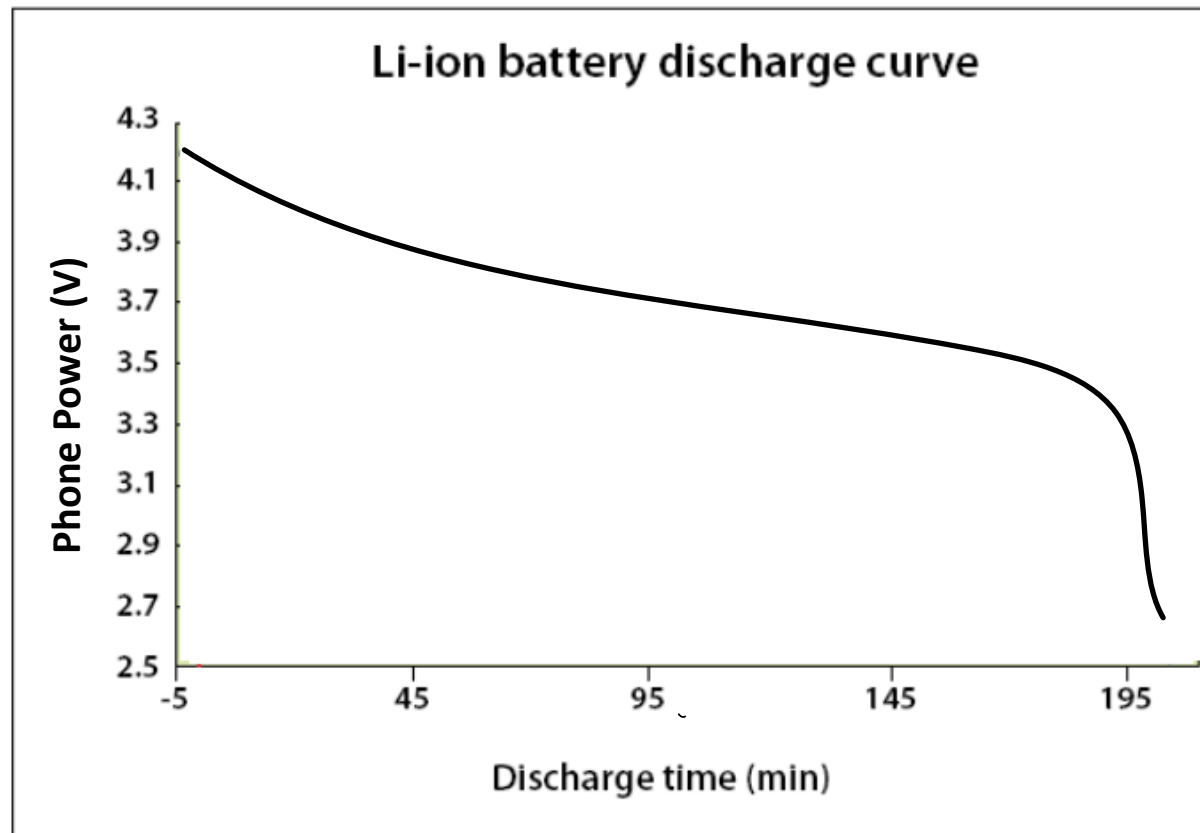
# Why Buck-Boost?

- Considering the Li-ion battery discharge profile, either buck or boost fails to operate for the output voltage of 3.3V - 3.6V
  - Converter needs to be operated in buck-boost mode for most of the time




# Drawback of Conventional BB converter

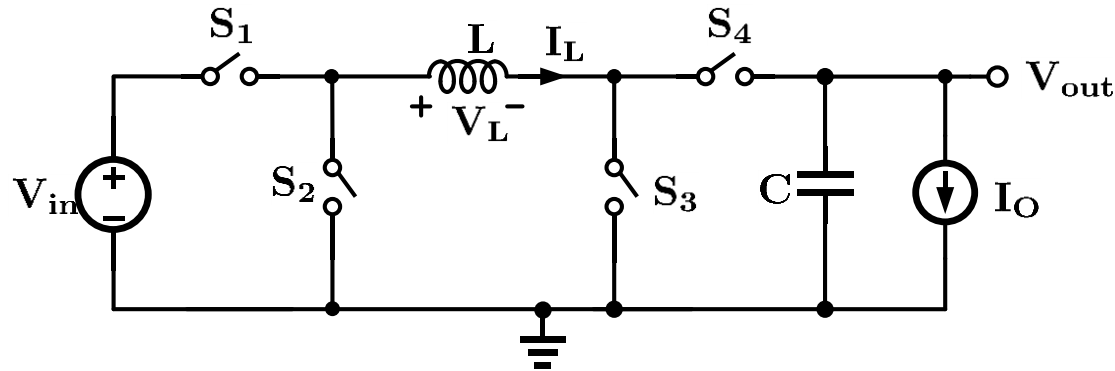

$$S_1 = S_3 = S$$

$$S_2 = S_4 = \bar{S}$$

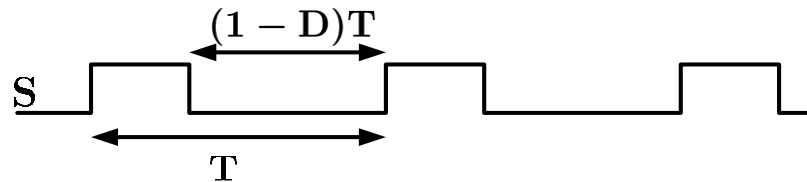


$$\mathbf{V_{out} = \frac{D}{1-D} V_{in}} \quad (1)$$

$$\mathbf{I_L = \frac{1}{1-D} I_o} \quad (2)$$

- Single Duty cycle,  $D$ , controls all the switches.
- Switching losses are higher due to simultaneous operation of 4 switches
- Conduction losses are higher due to larger Inductor current (nearly 2x when  $V_{in} \approx V_{out}$ ).

# Tri-Mode Operation of BB Converter


---

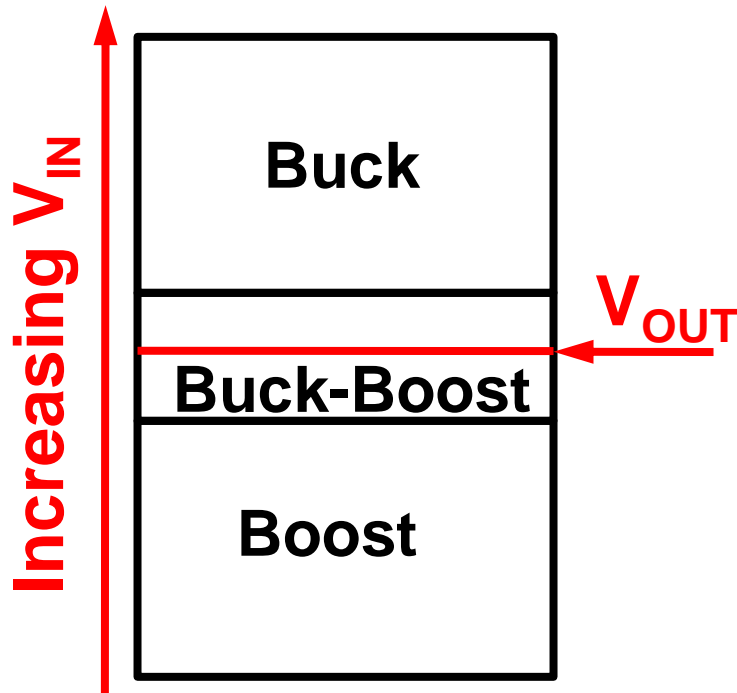


- $V_{IN} > V_{OUT}$  : Buck Mode
- $V_{IN} < V_{OUT}$  : Boost Mode
- $V_{IN} \sim V_{OUT}$  : Buck-Boost Mode
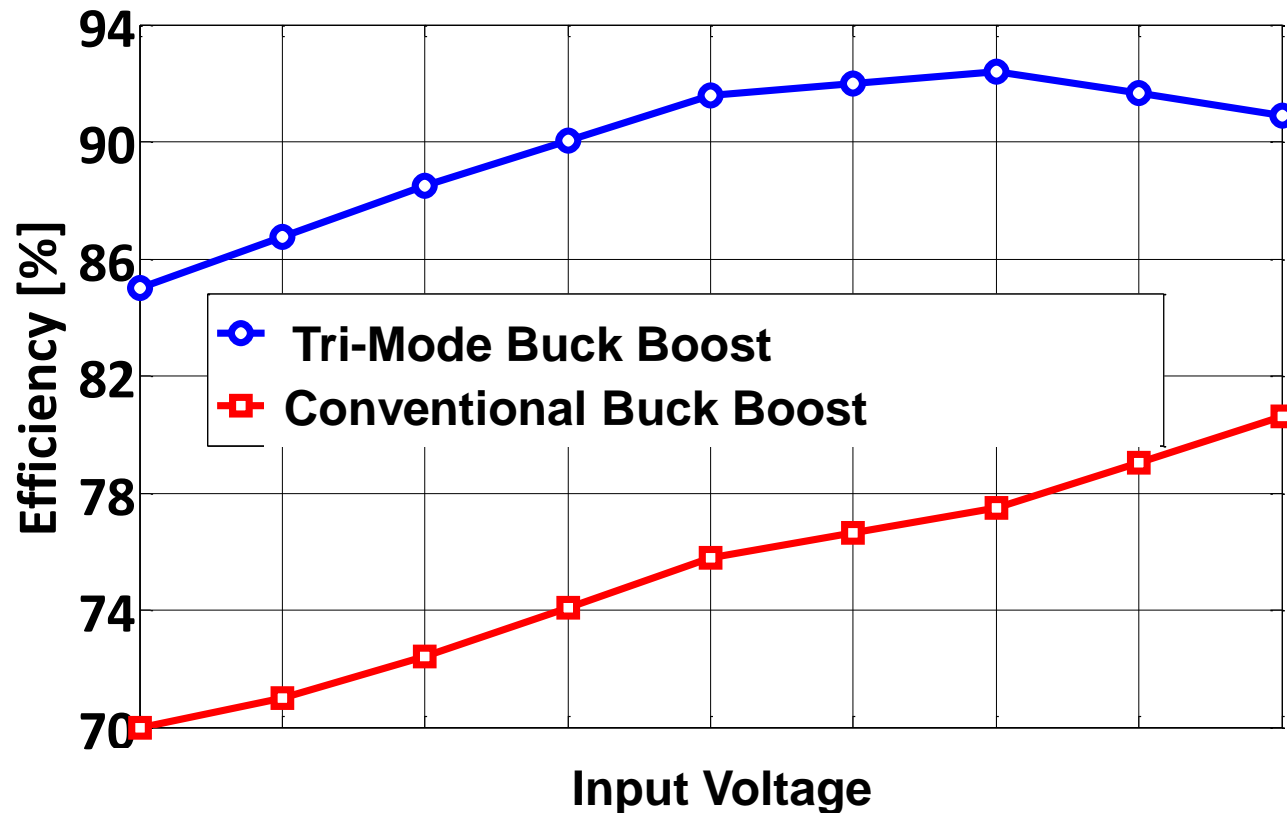
# Conventional vs. Tri-Mode Efficiency

$V_{in} = 2.7V$  to  $5.5V$ ,  $V_{out} = 3.3V$ ,  $I_{load} = 500mA$



# Tri-Mode: Buck

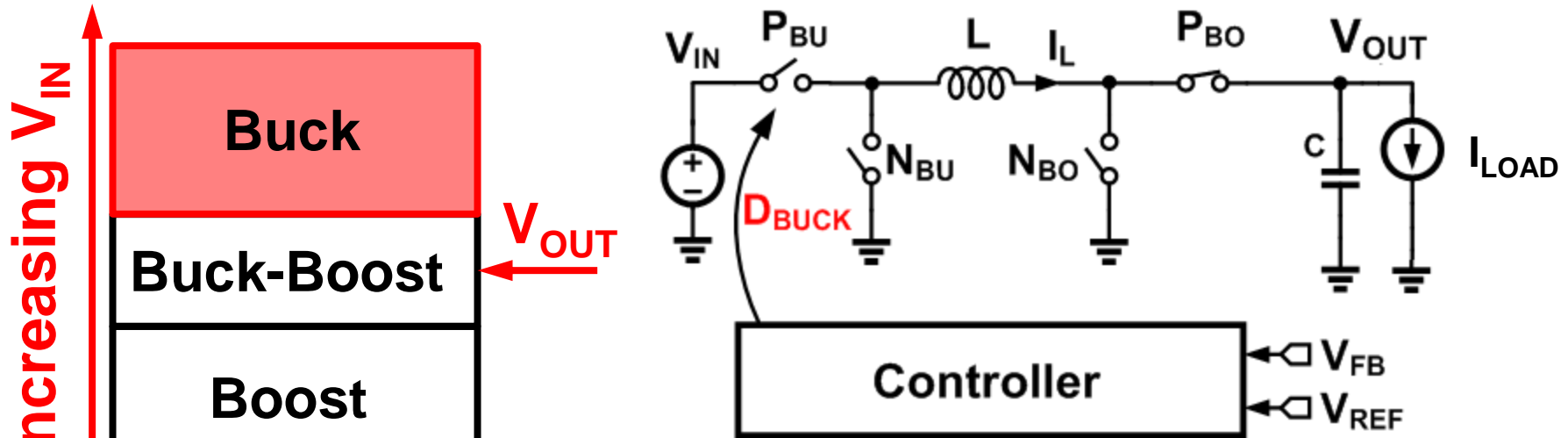


- $P_{BO}$  always ON
- $D_{BUCK}$  controls buck switches

$$V_{OUT} \approx (D_{BUCK})V_{IN} \quad I_L = I_{LOAD}$$





# Tri-Mode: Boost

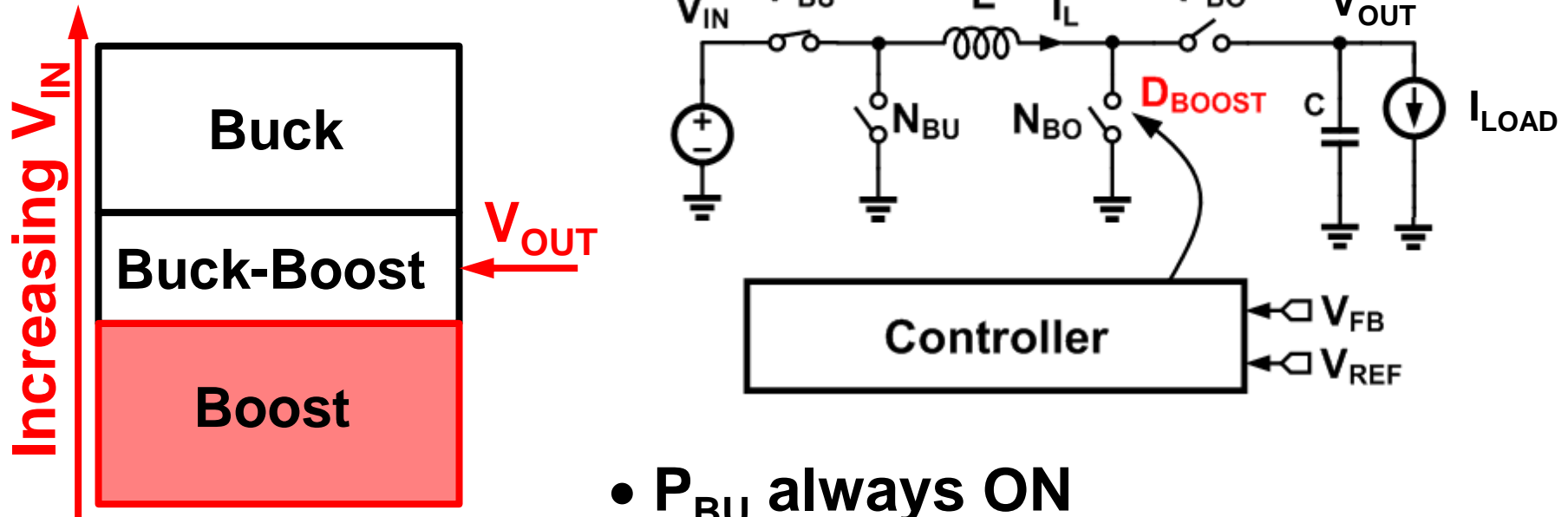

- $P_{BU}$  always ON
- $D_{BOOST}$  controls boost switches

$$V_{OUT} \approx \frac{V_{IN}}{(1 - D_{BOOST})} \quad I_L = \frac{I_{LOAD}}{(1 - D_{BOOST})}$$

# Tri-Mode: Buck-Boost

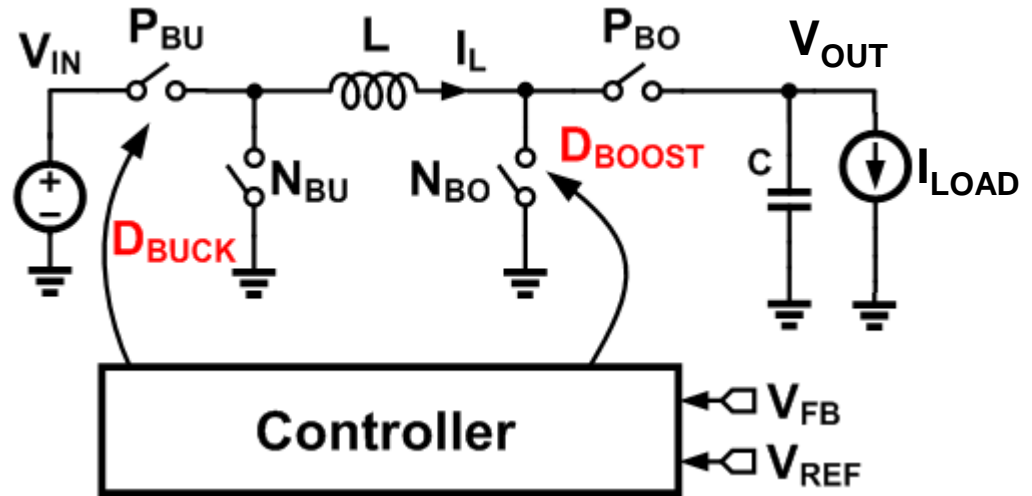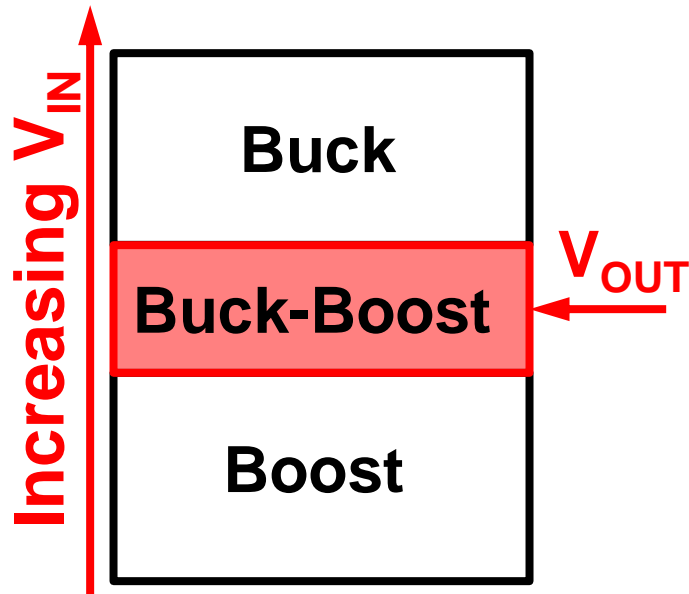


- $D_{BUCK}$  controls buck switches
- $D_{BOOST}$  controls boost switches

$$V_{OUT} \approx \frac{D_{BUCK}}{(1 - D_{BOOST})} V_{IN}$$


$$I_L = \frac{I_{LOAD}}{1 - D_{BOOST}}$$

# Issue with Tri-Mode Buck-Boost

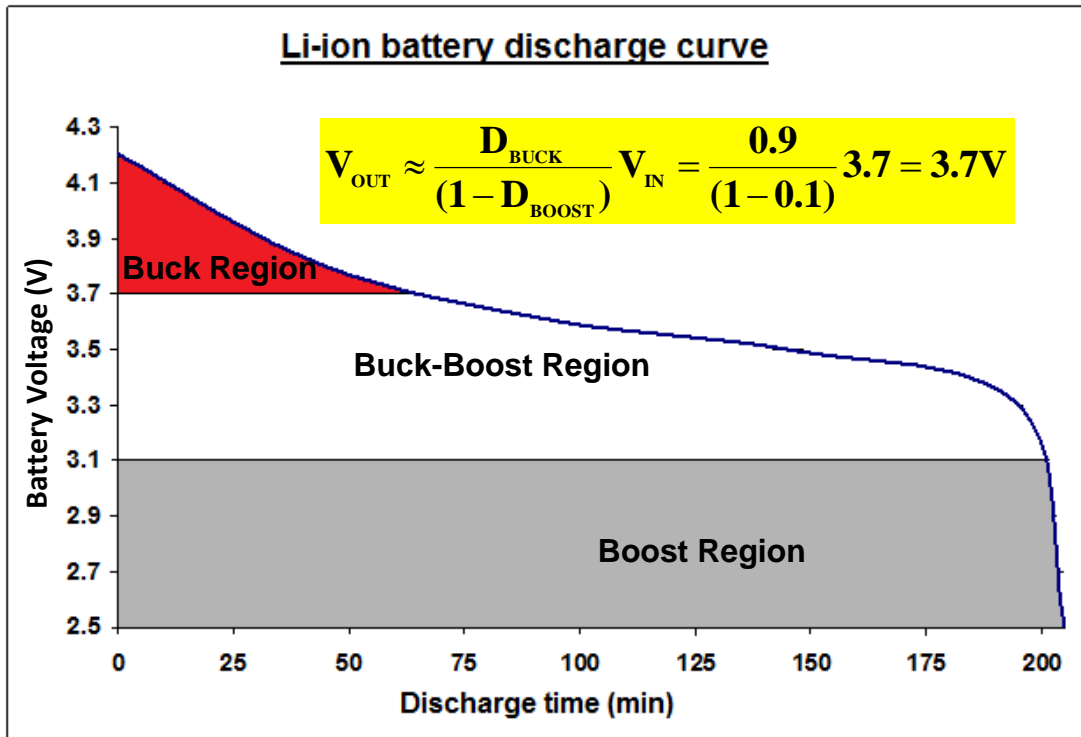

Buck Mode :  $D_{BOOST} = 0$

Boost Mode :  $D_{BUCK} = 1$

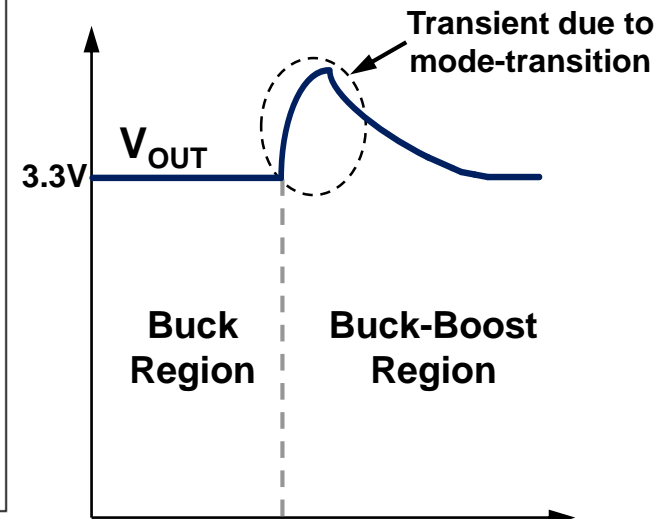

- Mode transition causes large voltage transient
- Boundary condition must be satisfied
  - Varies with load current and losses

## Boundary Condition



$$V_{OUT}(\text{buck}) = V_{OUT}(\text{buck - boost})$$

$$\rightarrow D_{BUCK\_max} = \frac{D_{BUCK}}{1 - D_{BOOST\_min}}$$

$$\rightarrow D_{BUCK} = D_{BUCK\_max} \cdot (1 - D_{BOOST\_min})$$
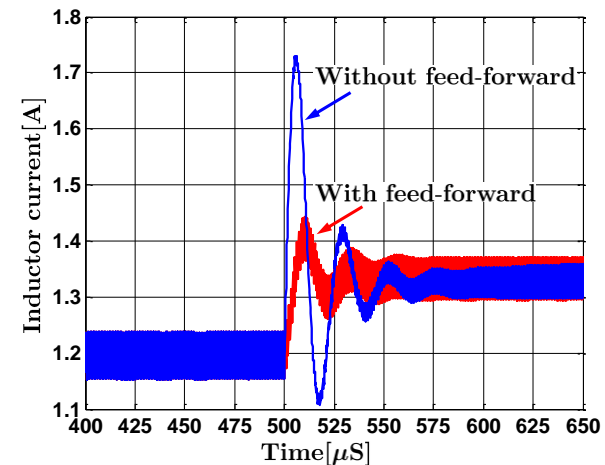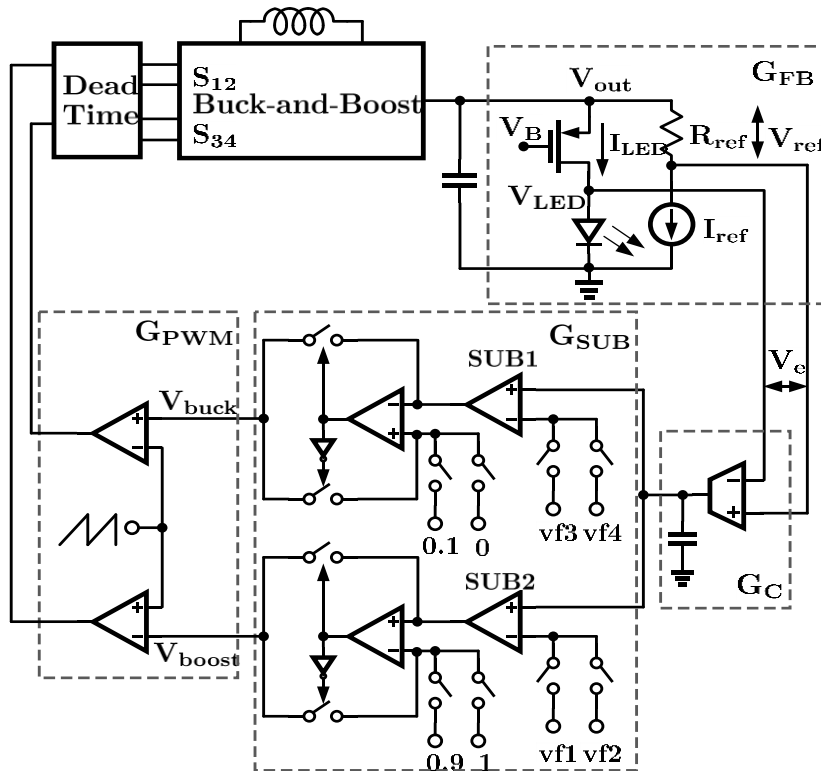
# Solutions for Mode Transitions


- Appropriate Feed-forward voltage  $vf1 - 4$  is subtracted to instantaneously change the duty cycles during mode transition.
- Analog Implementation makes is susceptible to PVT and requires external compensation capacitor



S. Bang, D. Swank, A. Rao, W. McIntyre, Q. Khan and P. K. Hanumolu, 1.2A 2MHz tri-mode Buck-Boost LED driver with feed-forward duty cycle correction, *CICC*, Sept. 2010.
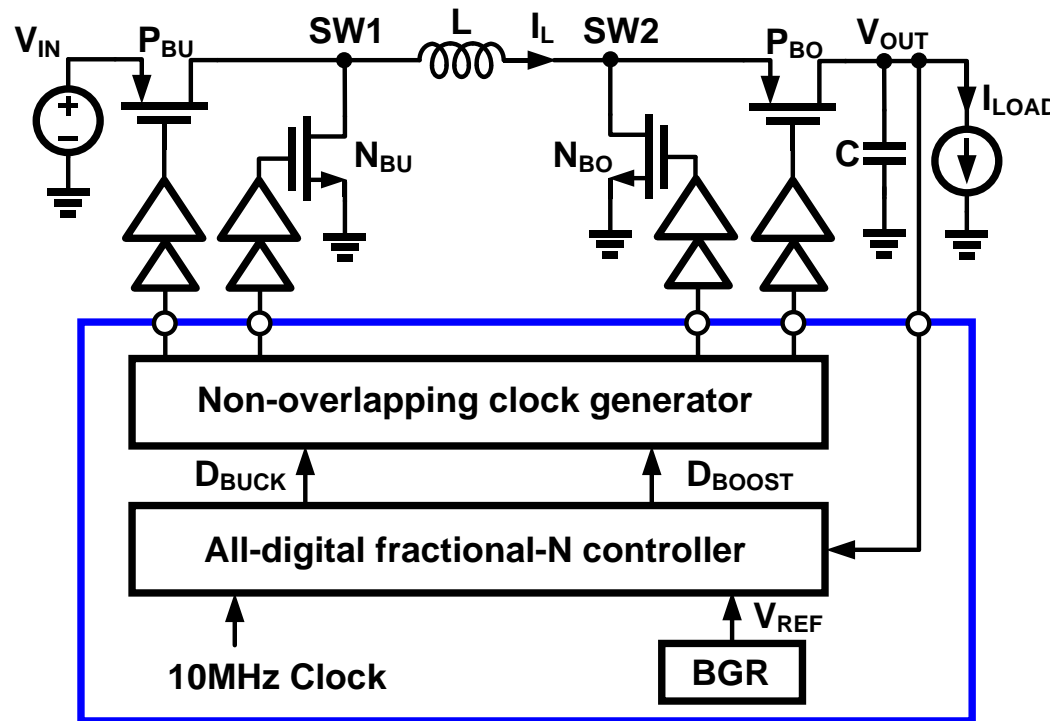
# Digital Constant ON/OFF Time Buck-Boost Converter

- Uses constant ON/OFF technique
- Enables High Switching Frequency Operation
- All digital implementation eliminates the need of external compensation capacitor




Q. Khan, et al, "A 3.3V 500mA Digital Buck-Boost Converter with 92% Peak Efficiency Using Constant ON/OFF Time Delta-Sigma Fractional-N Control, *Proc. ESSCIRC '11*, Sept. 2011.
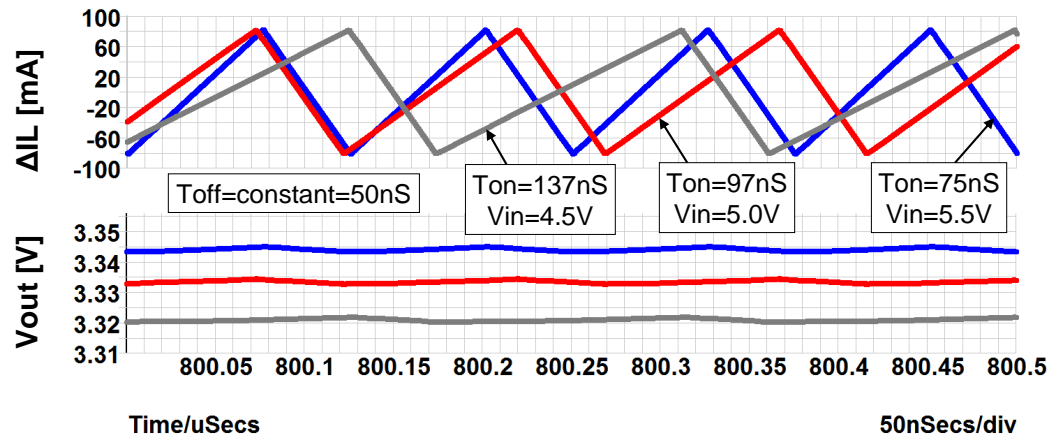
# Constant ON/OFF Time Operation

$$\text{Inductor ripple current, } \Delta I_L = \frac{V_{IN} - V_{OUT}}{L} T_{ON} \quad (1)$$
$$T_{ON} = D \cdot T \quad T_{OFF} = (1 - D) \cdot T$$

- Max ripple occurs at D=0.5 ( $T_{on} = T_{off}$ )
  - The converter can be operated at high switching frequency when D=0.5
- From eq. 1, D increases with  $V_{in}$ 
  - Fixing OFF time and making ON time function of  $V_{in}$  does not affect the inductor ripple
  - Causes variable switching frequency




# Fractional-N Control

---
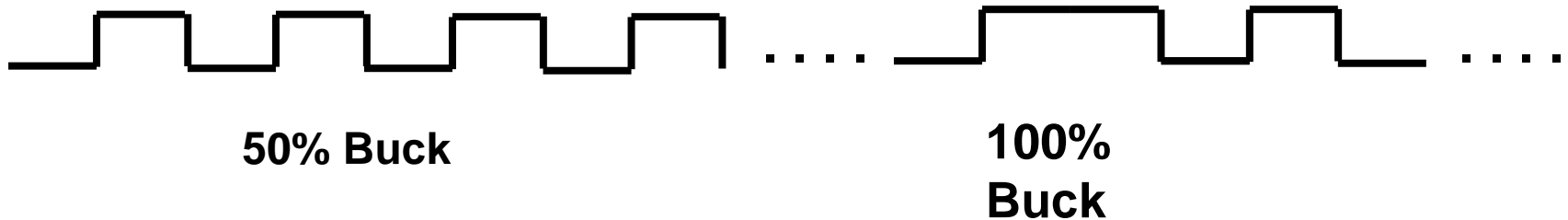
## Buck Mode:

N cycles of 50% Buck : 1 cycle of 100% Buck



## Buck-Boost Mode:

1 cycle of 50% Buck : 1 cycle of 50% Boost


## Boost Mode:

N cycle of 50% Boost : 1 cycle of 0% Boost


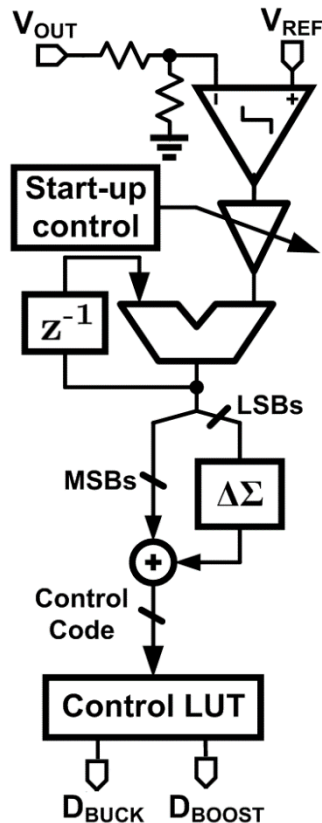
# Fractional-N Control Logic

- Predefined states are stored in the lookup table providing the coarse voltages
- Uses 18-bit acc for integrating the error (4 MSBs, 7 LSBs, 7 dropped bits).
- Any intermediate states are resolved by  $\Delta\Sigma$  Modulator




	Operating States	Control Code	Fraction N:1	
Buck Mode	ST1	0001	50%Buck:100%Buck	Decreasing $V_{IN}$
	ST2	0010	5:1	
	ST3	0011	4:1	
	ST4	0100	3:1	
	ST5	0101	2:1	
Buck-Boost Mode	ST6	0110	50%Buck:50%Boost	
			1:1	
Boost Mode	ST7	0111	50%Boost:0%Boost	
	ST8	1000	1:1	
	ST9	1001	2:1	
	ST10	1010	3:1	
	ST11	1011	4:1	
			5:1	2.7V



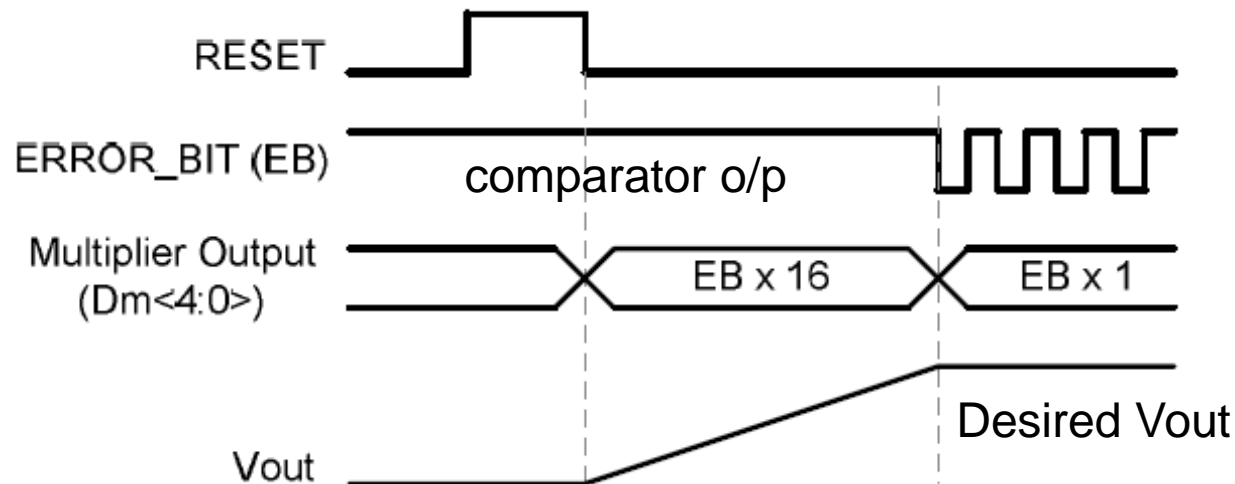
# Start-up Control







- Startup time is the function of no. of bits dropped in the accumulator and converter resolution
- No. of ACC bits dropped = 7
  - The startup time may be more than 10ms
- Speeded up by dropping only 3 bits in accumulator and switch to 7 bits once the output settles







# Inductor Current Profile

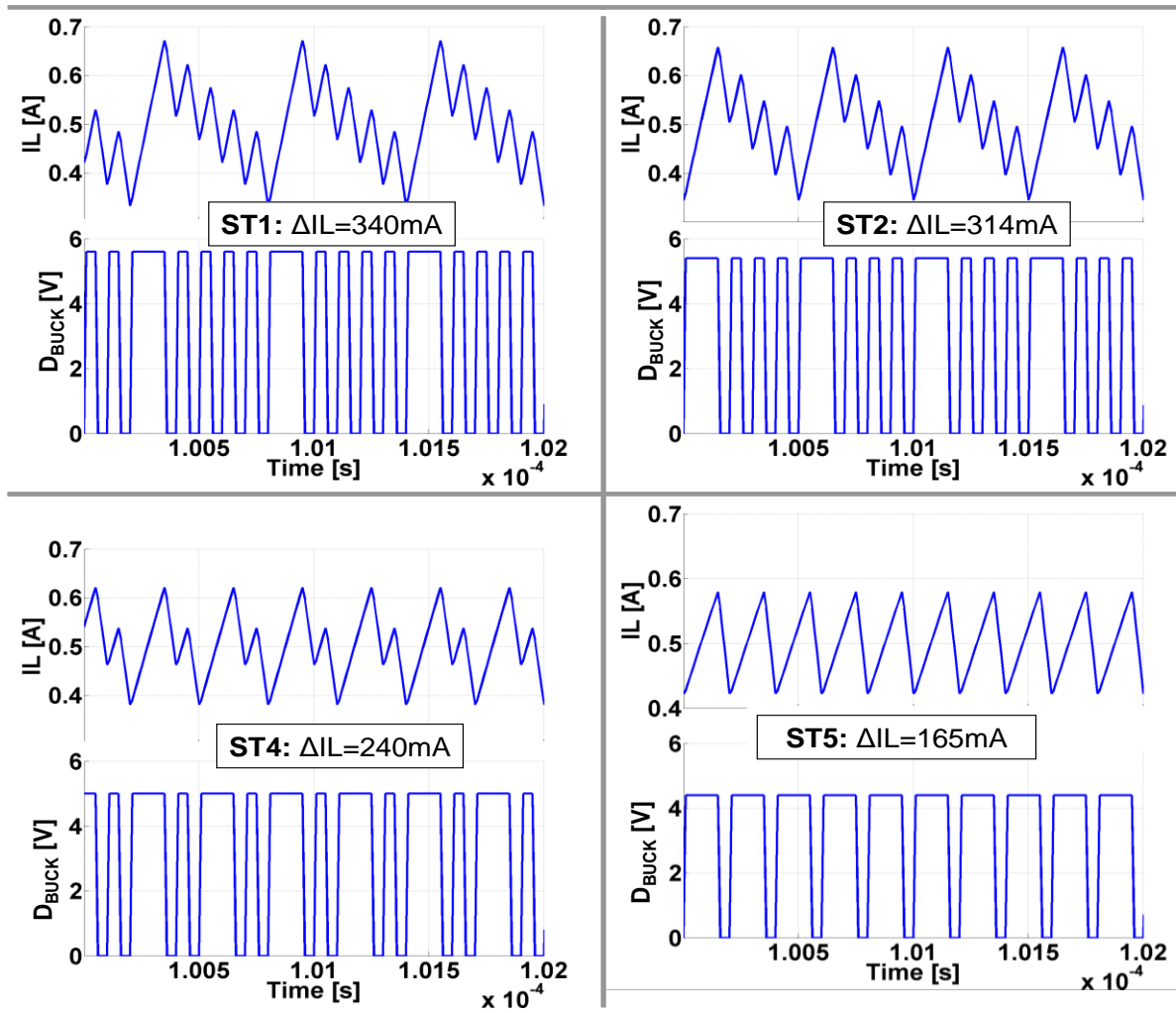



# Controller Response

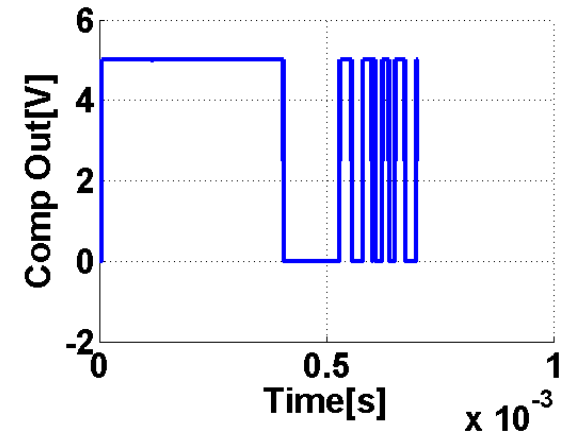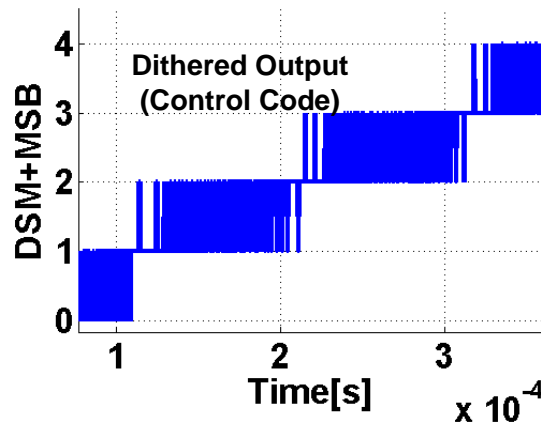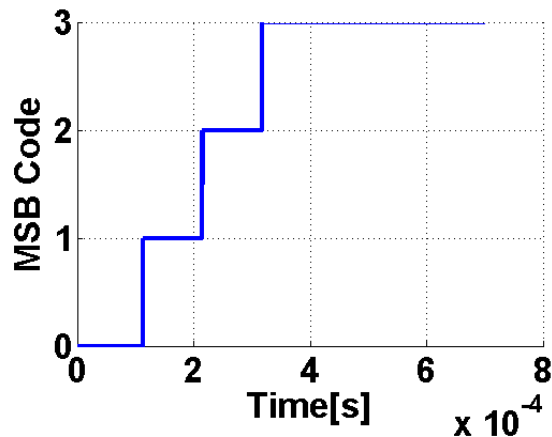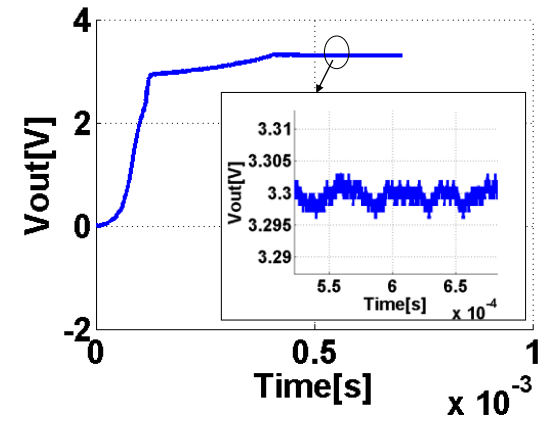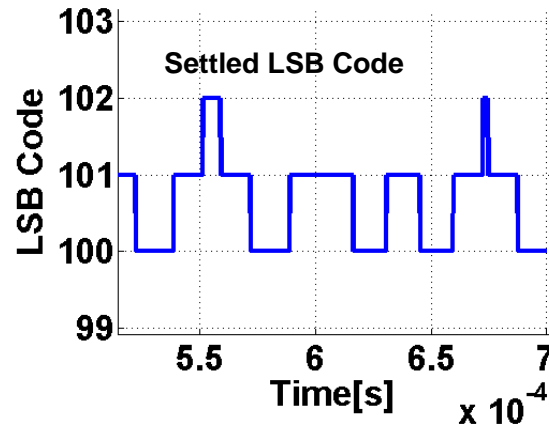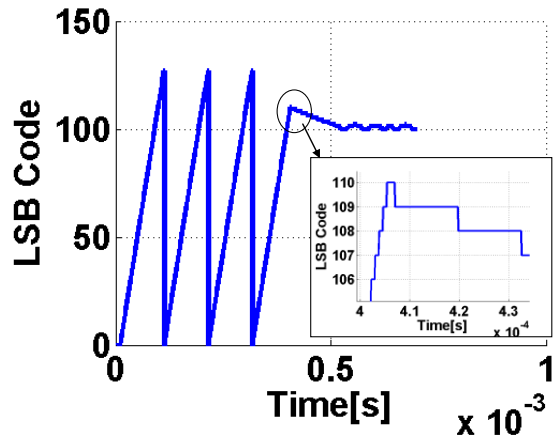


# Output Voltage Ripple

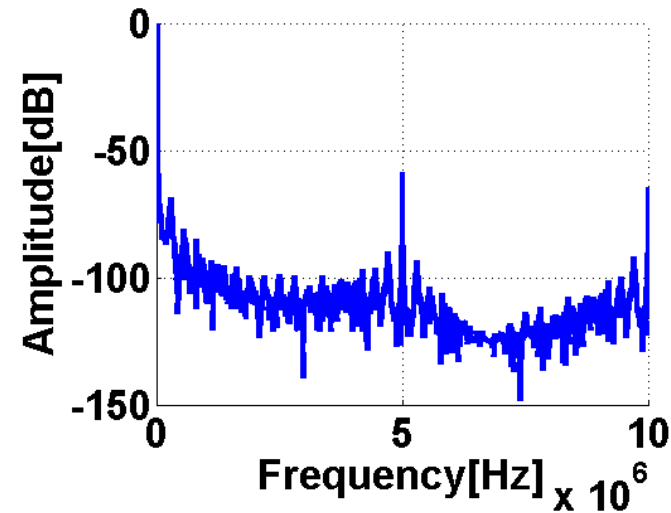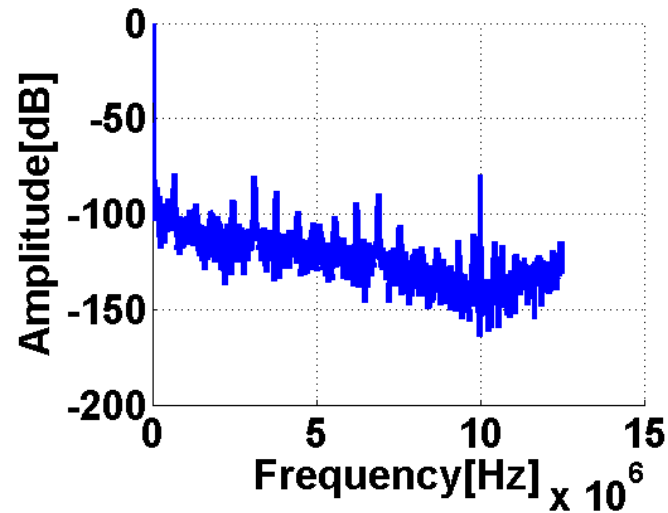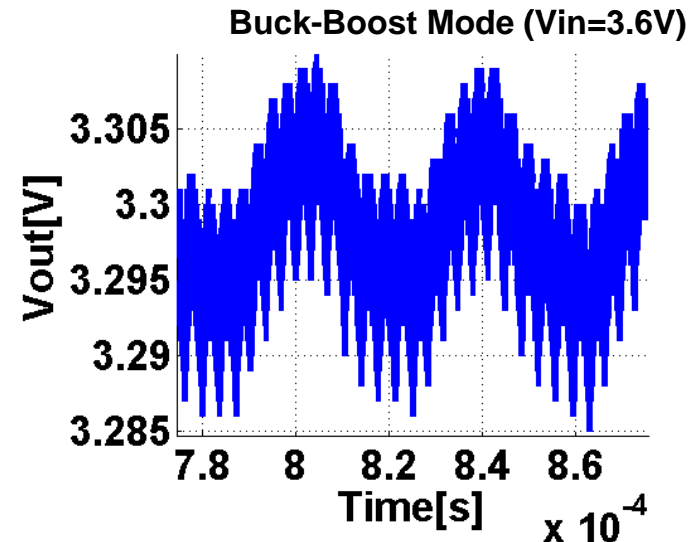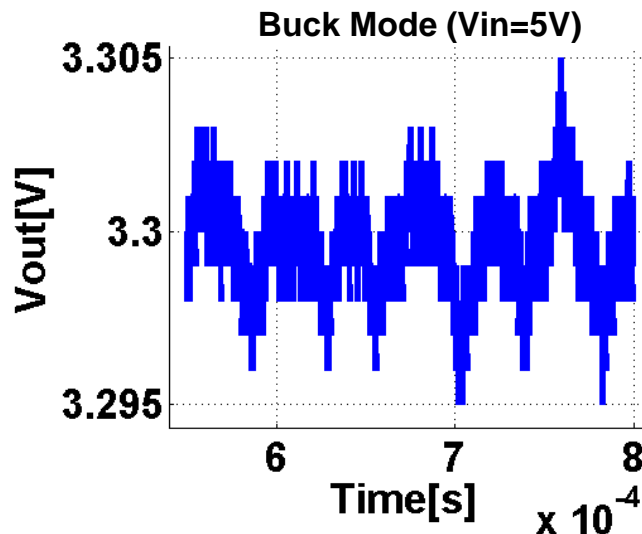

# Mode Transition

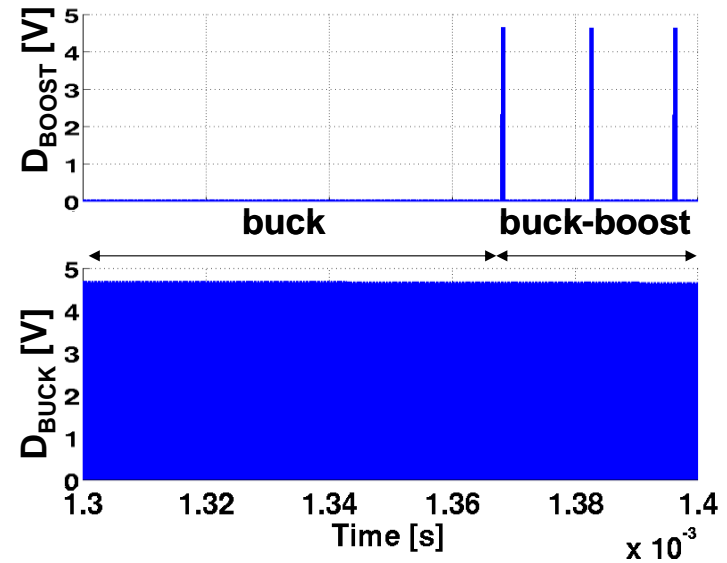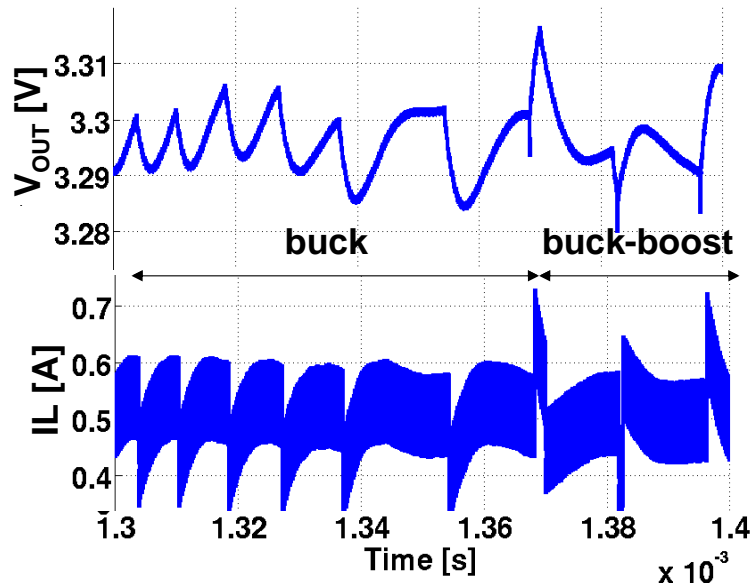

# Hybrid PWM Fractional-N Control

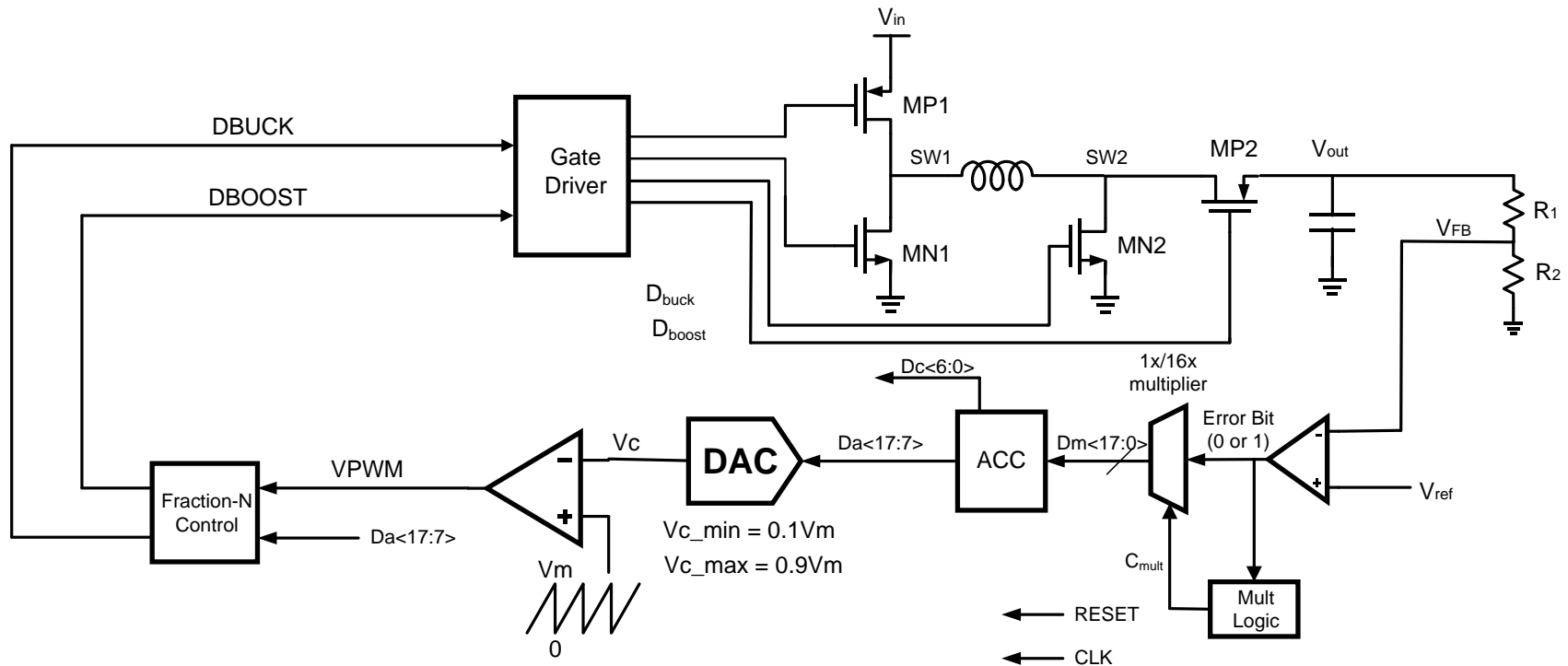

Buck Mode	Buck-Boost Mode (Fractional-N)	Boost Mode
$DBOOST = 0$ $DBUCK = VPWM$	90%Buck:100%Buck 90%Buck:10%Boost 10%Boost:0%Boost	$DBOOST = VPWM$ $DBUCK = 1$