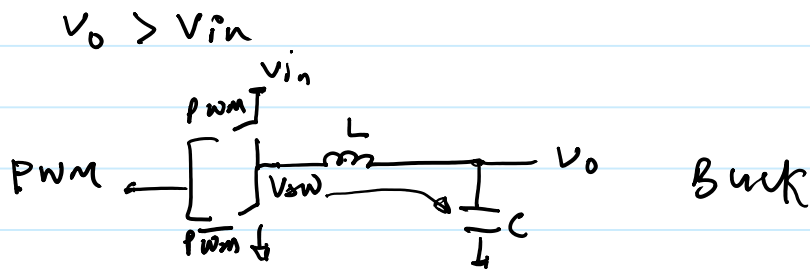




Boost Converter



$$V_o = D \cdot V_{in}$$

$$V_o = \frac{V_{in}}{D} \rightarrow 1-D$$

$$V_o = \frac{V_{in}}{1-D}$$

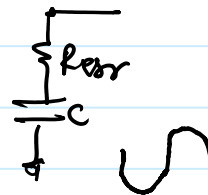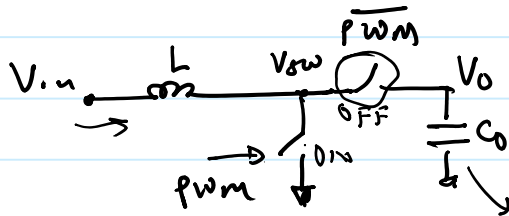

V_L during T_{on}

$$V_L = V_{in}$$

V_L during T_{off}

$$V_L = V_{in} - V_o$$

volt-second balance:



$$V_{in} D \cdot T_{sw} + (V_{in} - V_o)(1-D)T_{sw} = 0$$

$$D \cdot V_{in} + V_{in} - D \cdot V_{in} - V_o(1-D) = 0$$

$$V_o = \frac{V_{in}}{1-D}$$

Buck-Boost Converter

$$V_o = \frac{V_{in}}{1-D}$$

$$P_{in} = P_{out}$$


$$V_{in} \cdot I_{in} = V_o \cdot I_o$$

$$V_{in} \cdot I_{in} = \frac{V_{in}}{1-D} I_o$$

$$I_{in} = \frac{I_o}{1-D} = I_L$$

Buck - Boost

= Buck + Boost

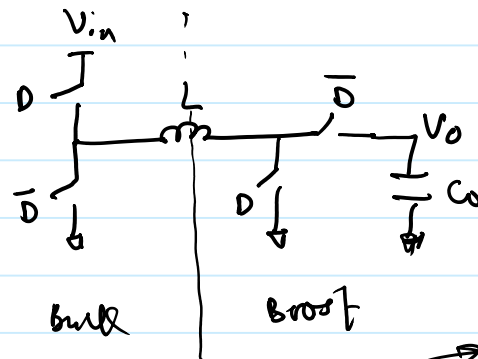

$$V_o = \frac{D}{1-D} V_{in}$$

$$I_o = \frac{1}{1-D} I_{in}$$

$$D = 0.5$$

$$V_o = V_{in}$$


$$\text{Buck} \rightarrow V_o < V_{in} \quad D < 0.5$$

$$\text{Buck-Boost} \rightarrow V_o \approx V_{in} \quad D \approx 0.5$$

$$\text{Boost} \rightarrow V_o > V_{in} \quad D > 0.5$$



Buck-Boost Converter

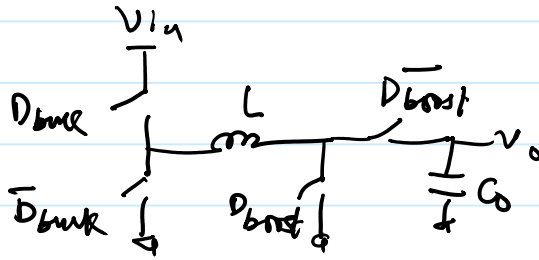

$$V_o = \frac{D_{buck}}{1 - D_{boost}} V_{in}$$

$$D_{buck} = 0.9 \quad D_{boost} = 0.1$$

$$V_o = V_{in} \quad I_{in} = \frac{I_o}{1 - D_{boost}}$$