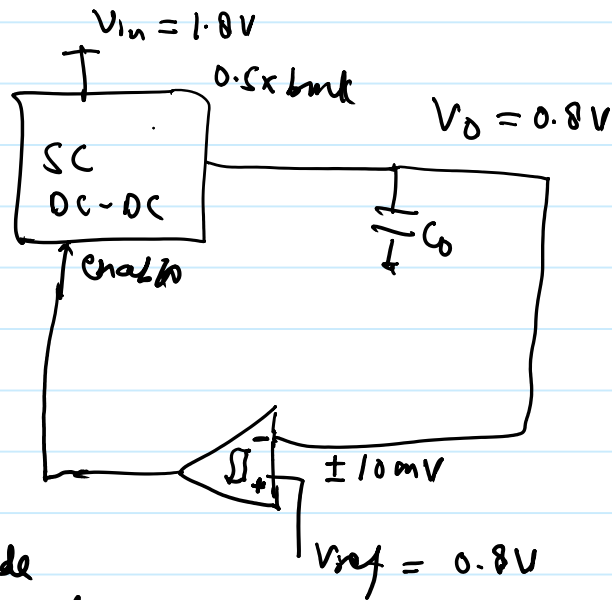



Regulating SC DC-DC using PFM




burst mode
or PFM mode



Hybrid SC and Inductive DC-DC

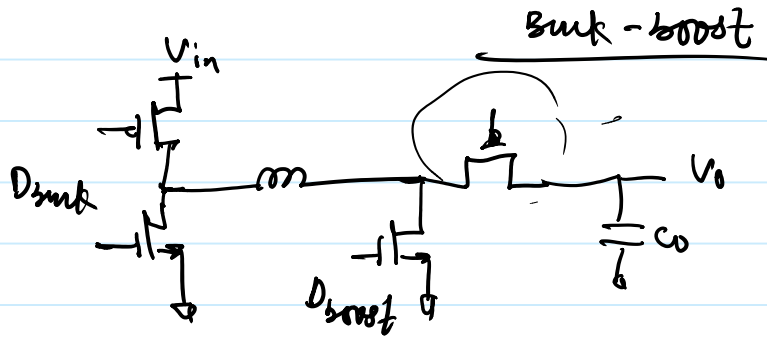
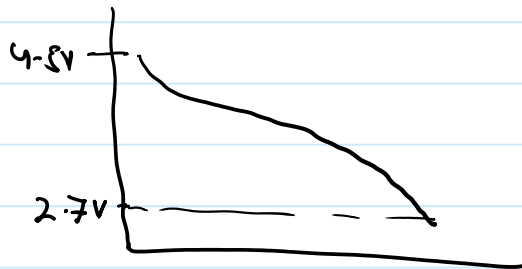
$$V_o = \frac{D_{buck}}{1 - D_{boost}} V_{in}$$



$$V_o = 3.3V$$

$$D_{boost-max} = ?$$

Hybrid SC-Inductive DC-DC

$$V_o = \frac{1}{1-D_{boost}} \cdot V_{in} \Rightarrow 1 - D_{boost} = \frac{V_{in}}{V_o}$$


$$\Rightarrow D_{boost} = 1 - \frac{V_{in}}{V_o}$$

$$I_o = 500 \text{ mA}$$


$$= 1 - \frac{2.7}{3.3} \approx 0.2$$

D_{boost_max} with losses
 $\rightarrow 30\%$
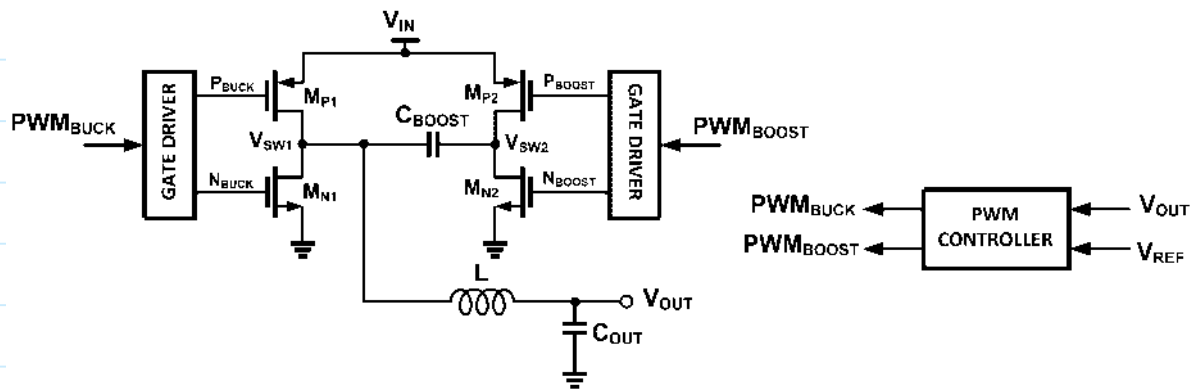
$$I_L = \frac{I_o}{1 - D_{boost}} = \frac{0.5}{0.7} \approx 0.7 \text{ A}$$



Buck Mode


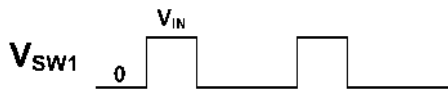


$V_{SW2} \rightarrow$ Floating (High-Z)

$M_{P2}/M_{N2} \rightarrow$ OFF
 $M_{P1}/M_{N1} \rightarrow$ PWM

$$V_{OUT} = D \cdot V_{IN}$$

Boost Mode

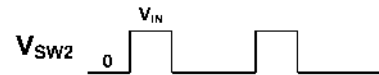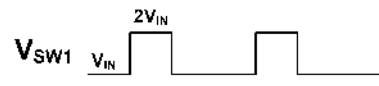

$M_{P2}/M_{N2} \rightarrow$ PWM
 $M_{P1} \rightarrow$ PWM
 $M_{N1} \rightarrow$ OFF

$$V_{OUT} = (1+D) \cdot V_{IN}$$

DC-DC Design Flow

Designing Flow of a DC-DC converter

You are given specifications

V_{in}

V_{out}

I_{load}

η

Accuracy.

Transient.

soft start time

ripple in V_{out}

Example

$$V_{in} = 1.8V, V_o = 0.8V - 1.5V$$

$$I_{load} = 0 \text{ to } 1A$$

$$\eta = 90\%$$

dc Accuracy $< 1\%$

load transient $\pm 5\%$ with $0 - 1A$
 $1A - 0$

line transient

$$\pm 100mV$$

rise/fall $\leftrightarrow 100ns$

1. Topology selection
2. Technology
3. $F_{sw} \rightarrow$ switching losses
4. L & C

