

Loss Estimation

$$V_o = 0.8V, V_{in} = 1.8V$$

$$I_{load} = 1A, \eta = 90\% = 0.9$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{out} + P_{loss}}$$

$$\Rightarrow P_{loss} = \left(\frac{1}{\eta} - 1 \right) P_{out}$$

$$\eta = 0.9$$

$$P_{loss} = 0.11 \times P_{out} \quad P_{out} = 0.8 \times 1A = 0.8W$$
$$\approx 88mW$$

$$88mW = P_{cond-loss} + P_{sw-loss}$$

$$F_{sw} = 10MHz$$

$$CV^2f$$

$$C = 100pF$$

$$10^{-10} \times (0.8)^2 \times 10^7 = 10^{-3}$$

$$P_{sw-loss} = 7mW$$

$$\underline{P_{dead-loss}}$$

$$t_{dead} = 1\mu s$$

$$2 \times \frac{0.7 \times 1 \times 1\mu s}{100ns} \approx 7mW \times 2 = 14mW$$

$$0.8V \rightarrow V_0$$

$$0.6 \rightarrow V_{ref}$$

$$\beta = \frac{V_{ref}}{V_0} = \frac{0.6}{0.8} = 0.75$$

$$V_0 = 1.5V$$

$$\beta = \frac{0.6}{1.5} = 0.4$$

