

---

# ***Lecture-42***

## ***EE5325 Power Management Integrated Circuits***

**Dr. Qadeer Ahmad Khan**

**Integrated Circuits and Systems Group  
Department of Electrical Engineering  
IIT Madras**

# How to Enable PSM Mode


---

PSM mode is usually enabled when converter hits min or max duty cycle


- **For a buck converter:**
  - Minimum duty cycle can hit either under light load or when  $V_o/V_{in}$  ratio is quite low
  - Maximum duty can hit when  $V_o/V_{in} \approx 1$  (close to 100% duty cycle)
- **For a boost converter:**
  - Minimum duty cycle can hit either under light load or when  $V_o/V_{in} \approx 1$  (close to 0% duty cycle)
  - Maximum duty is very rare case in boost (  $>10x$  boost ratio in CCM)
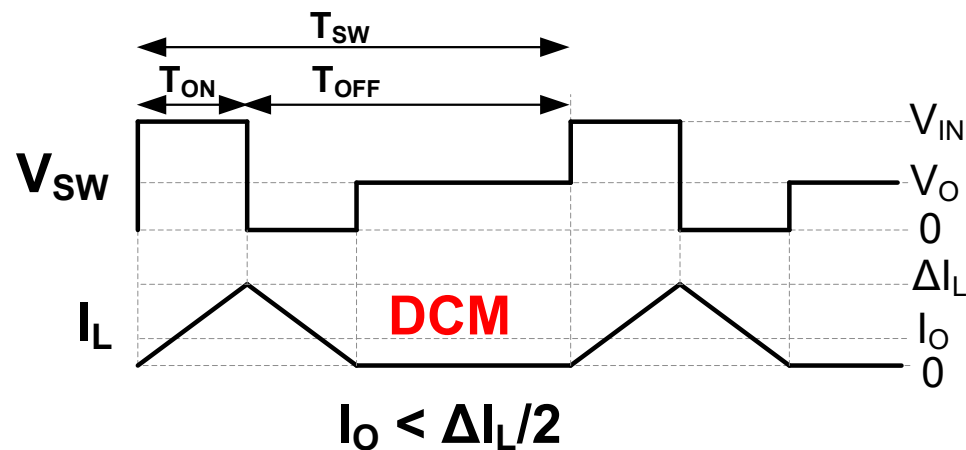
# Detecting CCM-DCM Boundary

- Converter is operated in DCM by turning OFF low side FET ( $S_N$ ) as soon as inductor current goes zero
- Zero current can be detected using zero-cross comparator as  $V_{sw}$  goes from negative to positive
- Can be used to switch from PWM to PFM mode
- Usually CCM-DCM detector output is de-bounced before entering/exiting DCM mode to filter out any transient (momentarily) condition



# Implementing DCM Operation

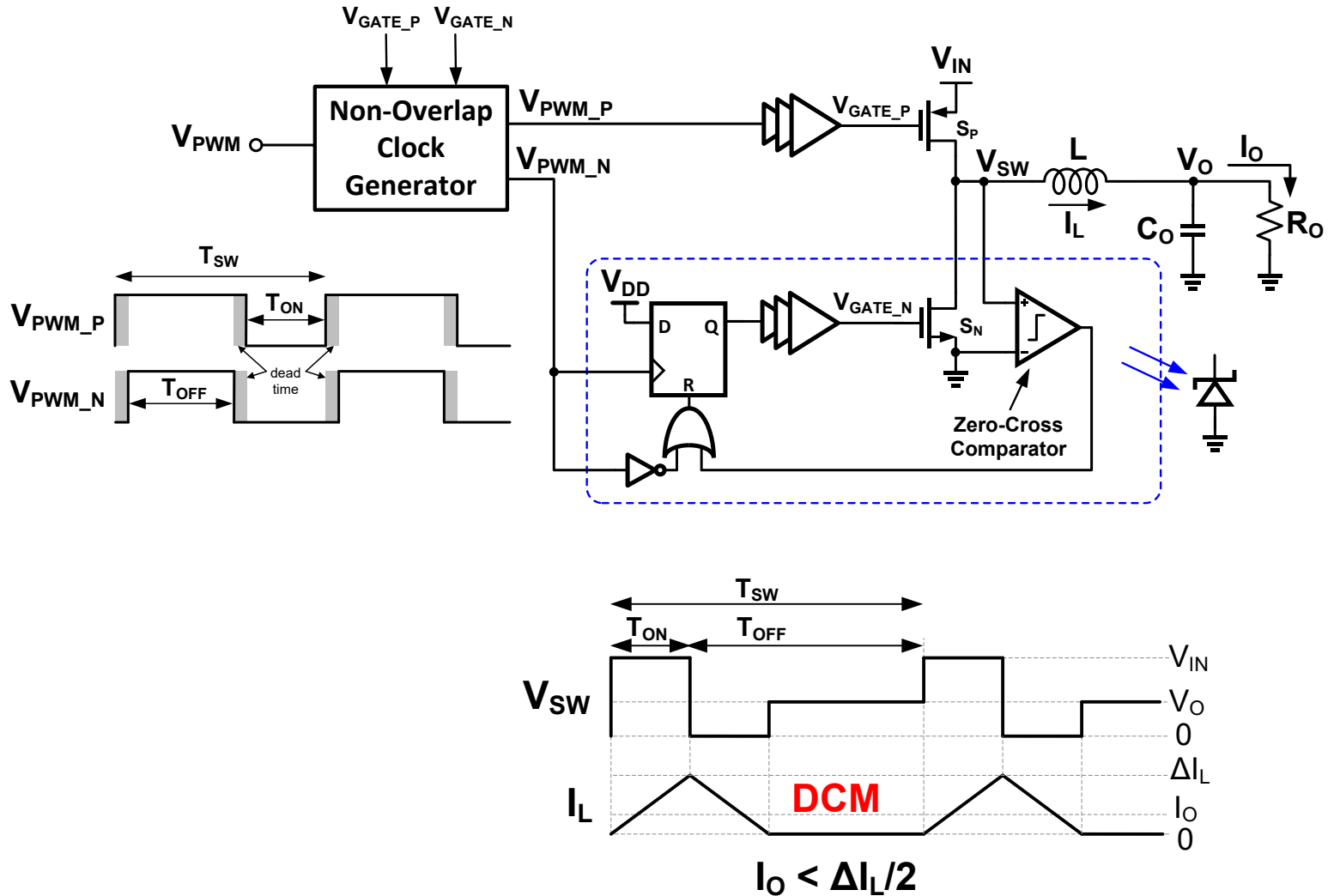

# Zero-Cross Comparator Requirement

---

- Since voltage drop across NFET is low (due to low  $R_{ds\_on}$ ), a very high gain and low offset comparator is required to detect the inductor reverse current
  - Assuming 100mOhm  $R_{ds\_on}$ , 1mV error may cause error of 10mA in zero current detection.
- Comparator delay should be minimized as it may also introduce error
  - Assuming 1MHz and 10% duty cycle, with  $V_{out}=1.2V$ ,  $L=1\mu H$ , inductor current slope is 1.2A/us  $\rightarrow$  10ns delay can cause an error of 12mA in the zero current detection
  - This becomes even more challenging when switching at higher frequencies (10MHz and above).


# Zero-Cross Comparator Topologies

---

- **Conventional two stage comparator is not suitable of zero current detection mainly due to large delay**
- **High speed comparator with offset cancellation is usually required to minimize the error**
- **Current comparator can also be used to minimize the delay**

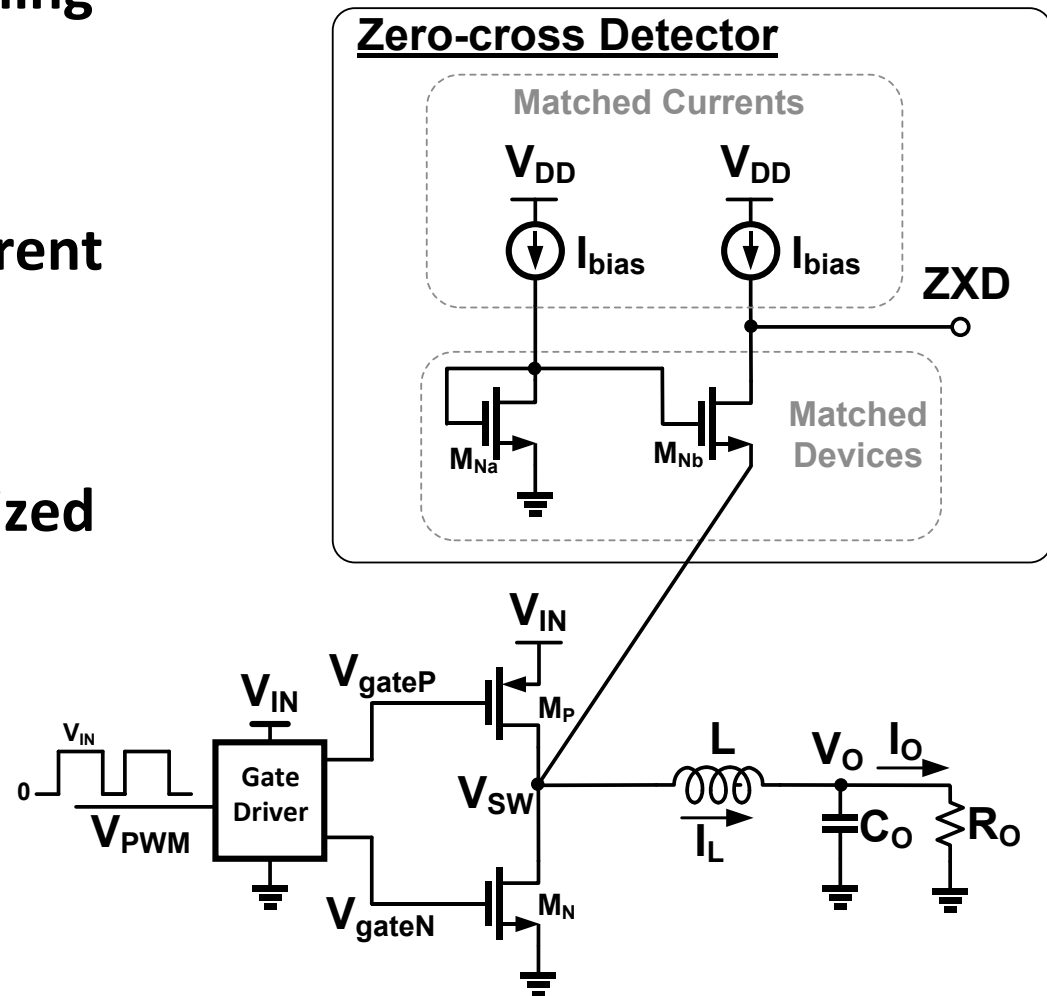
# Current Based Zero-Cross Detector

- Requires good matching between devices
- Any mismatch in current will introduce offset
- Offset can be minimized by good layout and cascaded devices


 
# Inverter Based Auto-Zeroed Comparator

- When  $DRIVE=1$ ,  $C1$  is pre-charged to  $V_{gs}$  of  $MN1$
- When  $DRIVE=0$ ,  $C1$  samples  $V_{SW}$  node
- $COM_{OUT}=1$  if  $V_{SW} < 0$
- Offset is automatically cancelled



Stephen W. Bryson , Using auto-zero comparator techniques to improve PWM performance, *eetimes article*, 2008