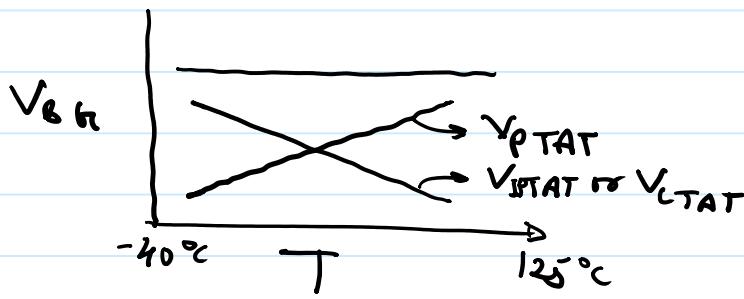



## Bandgap Voltage Reference (Basic Concept)



PTAT  $\rightarrow$  Proportional to absolute Temperature

PTAT  $\rightarrow$  Linearly proportional to absolute temperature

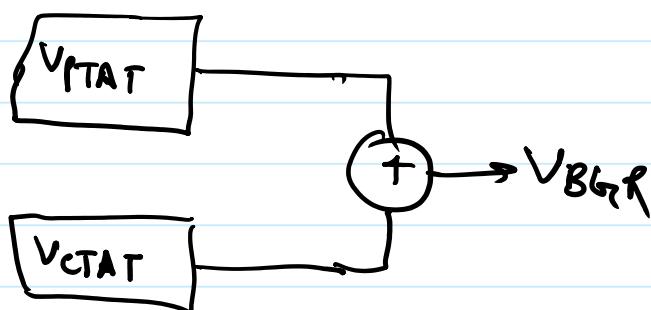CTAT  $\rightarrow$  Complementary to absolute temp



$$V_{BGR} = V_{PTAT} + V_{CTAT}$$

$$\frac{\partial V_{BGR}}{\partial T} = \frac{\partial V_{PTAT}}{\partial T} + \frac{\partial V_{CTAT}}{\partial T} = 0$$

$$\Rightarrow \frac{\partial V_{PTAT}}{\partial T} = -\frac{\partial V_{CTAT}}{\partial T}$$

## CTAT Voltage Reference



$$I_c = I_s e^{V_{be}/V_T}$$

$$\Rightarrow e^{V_{be}/V_T} = \frac{I_c}{I_s}$$

$$\frac{V_{be}}{V_T} = \ln\left(\frac{I_c}{I_s}\right)$$

$$V_{be} = V_T \ln\left(\frac{I_c}{I_s}\right)$$

$$V_T = \frac{kT}{qV}$$


$$\frac{\partial V_T}{\partial T} = \frac{k}{qV}$$

$$k = 1.38 \times 10^{-23}$$

$$q = 1.61 \times 10^{-19} C$$


$$\frac{\partial V_T}{\partial T} = \frac{1.38}{1.61} \times 10^{-4} = 8.61 \times 10^{-5}$$
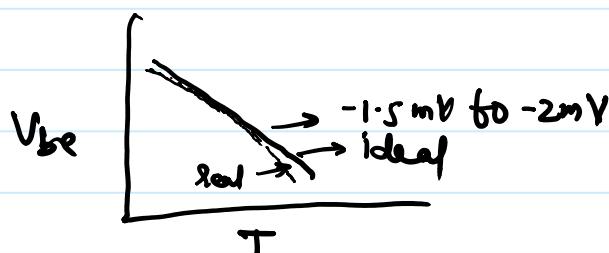
$$\frac{\partial V_{be}}{\partial T} \approx -1.5 \text{ mV to } -2 \text{ mV}$$



# PTAT Voltage Reference

**PTAT**

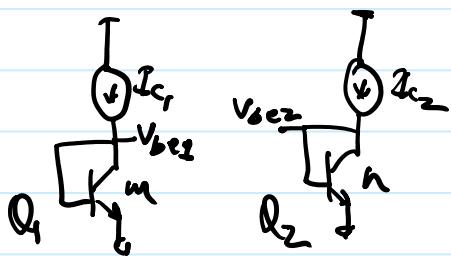

$$V_{be1} = V_T \ln\left(\frac{I_{c1}}{I_{S1}}\right) \quad \text{--- (1)}$$

$$V_{be2} = V_T \ln\left(\frac{I_{c2}}{I_{S2}}\right) \quad \text{--- (2)}$$

$$(1) - (2)$$

$$\Rightarrow \underbrace{V_{be1} - V_{be2}}_{\Delta V_{be}} = V_T \ln\left(\frac{I_{c1}}{I_{S1}} \times \frac{I_{c2}}{I_{c2}}\right)$$

$$\frac{I_{S2}}{I_{S1}} = \frac{n}{m}$$

$$\Delta V_{be} = V_T \ln\left(\frac{n}{m} \times \frac{I_{c1}}{I_{c2}}\right)$$

if  $Q_1$  &  $Q_2$  are symmetric

$$m = n$$

$$\Delta V_{be} = V_T \ln\left(\frac{I_{c1}}{I_{c2}}\right)$$

$$\frac{I_{c1}}{I_{c2}} = k_1$$

$$\Delta V_{be} = V_T \ln(k_1)$$

$$V_T = \frac{kT}{q} \Rightarrow \frac{\partial V_T}{\partial T} = \frac{k}{q}$$


## PTAT Voltage Reference

Let's assume  $\Omega_1 \neq \Omega_2$  have different sizes but  $I_{C_1} = I_{C_2}$

$$\Delta V_{BE} = V_T \ln \left( \frac{n}{m} \right)$$


assume  $m=1$

$$\Delta V_{BE} = V_T \ln(n)$$

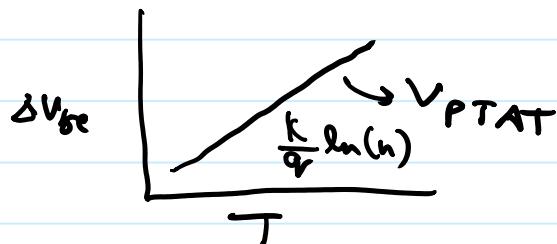


$$V_{BG} = V_{CTAT} + V_{PTAT}$$

$$= V_{BE} + \Delta V_{BE}$$

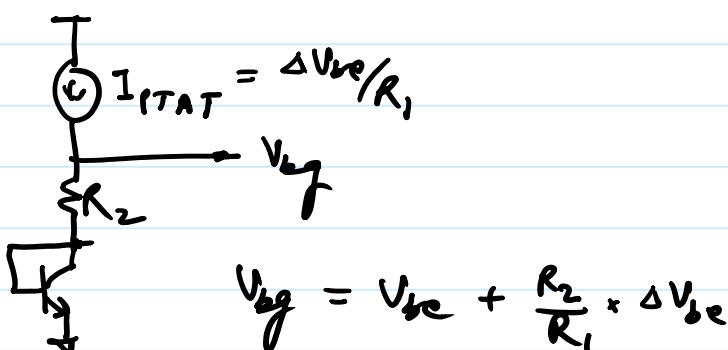

## Bandgap Circuit

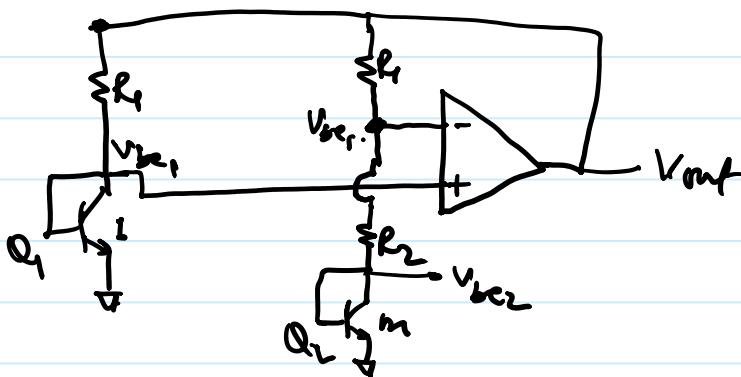

$$I_{R_2} = \frac{V_{be_1} - V_{be_2}}{R_2} = \frac{\Delta V_{be}}{R_2}$$

$$V_{out} = V_{be_1} + \frac{\Delta V_{be}}{R_2} \times R_f$$

$$V_{bg} = V_{be_1} + \frac{R_f}{R_2} \times \Delta V_{be}$$

$$\frac{\partial V_{bg}}{\partial T} = \frac{\partial V_{be_1}}{\partial T} + \frac{\partial \Delta V_{be}}{\partial T} \left( \frac{R_f}{R_2} \right)$$

$$\Delta V_{be} = V_T \ln(m)$$

$$\frac{\partial V_{bg}}{\partial T} = \frac{\partial V_{be_1}}{\partial T} + \underbrace{\left( \frac{R_f}{R_2} \right) (\ln(m))}_{\alpha} \frac{\partial V_T}{\partial T}$$

$$\frac{\partial V_{bg}}{\partial T} = \frac{\partial V_{be}}{\partial T} + \alpha \frac{\partial V_T}{\partial T} = 0 \quad \text{--- (1)}$$